
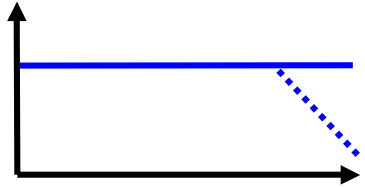
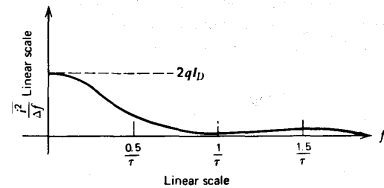
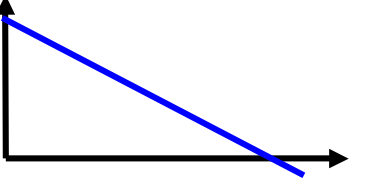


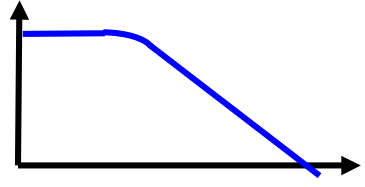

**School of Electronic
and Communications
Engineering**


3. Noise Analysis

Noise Sources (resume)

Noise	Origin	Expression	Spectral density
thermal noise (Gaussian)	random fluctuations of velocity	$i_t^2 = 4kT\Delta f / R$	
shot noise (Gaussian)	due to DC current through p-n junction	$\overline{i_s^2} = 2qI_D \cdot \Delta f$	
flicker noise	traps in crystal lattice (semiconductors, carbon, etc.)	$\overline{i_f^2} = K_1 \frac{I_{DC}^\alpha}{f^\beta} \cdot \Delta f$	
burst noise	heavy-metal ions contamination. (gold, etc.)	$\overline{i_b^2} = K_2 \frac{I^c}{1 + (f / f_c)^2} \cdot \Delta f$	
avalanche noise	due to avalanche breakdown in zener diodes		

Equivalent input noise

- ❖ The significance of the noise performance of a circuit is the limitation it places on the smallest input signals the circuit can handle before the noise degrades the quality of the output signal.
- ❖ For this reason, the noise performance is usually expressed in terms of an *equivalent input noise signal*, which gives the same output noise as the circuit under consideration.
- ❖ The real (noisy) network is replaced by noiseless network and *equivalent input noise signal*, $\overline{v_{iN}^2}$

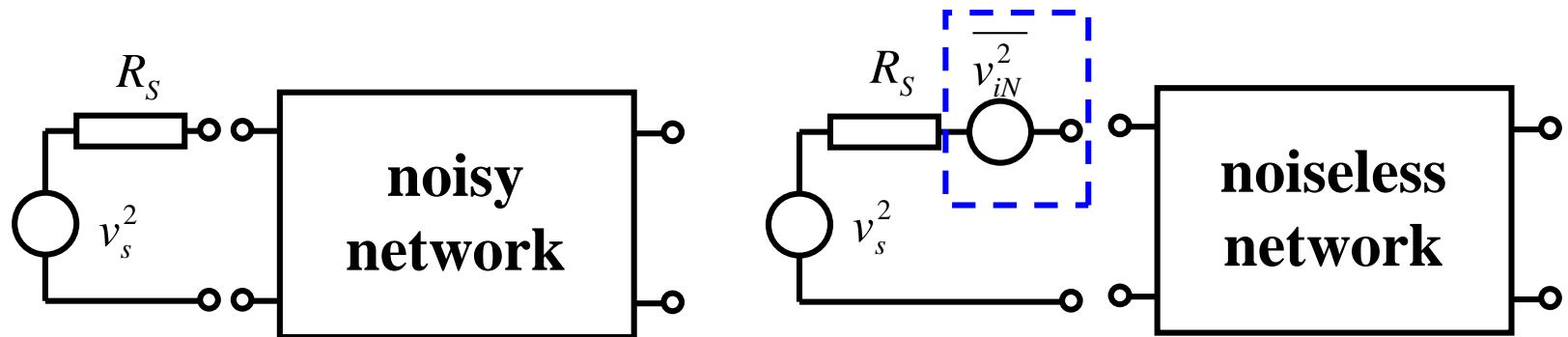

Equivalent input noise (BJT)

- ❖ It was shown that BJT noise can be expressed as:

$$\frac{\overline{v_o^2}}{B} = g_m^2 R_L^2 \frac{|Z|^2}{|Z + r_b + R_S|^2} \left[4kT(R_S + r_b) + (R_S + r_b)^2 2qI_B \right] + R_L^2 \left(\frac{4kT}{R_L} + 2qI_C \right)$$

- ❖ On the other hand BJT noise can be presented as an amplified equivalent input noise: v_{iN}^2

$$\overline{v_o^2} = g_m^2 R_L^2 \frac{|Z|^2}{|Z + r_b + R_S|^2} \overline{v_{iN}^2}$$

- ❖ Combining of these two equations gives the expression for equivalent input noise:

$$\frac{\overline{v_{iN}^2}}{B} = 4kT(R_S + r_b) + (R_S + r_b)^2 2qI_B + \frac{|Z + r_b + R_S|^2}{g_m^2 R_L^2 \cdot |Z|^2} \cdot R_L^2 \left(\frac{4kT}{R_L} + 2qI_C \right)$$


Minimum Detectable Signal

- ❖ In this way, the **equivalent input noise** can be compared directly with **incoming signals** and the effect of the noise on those signals is easily determined.
- ❖ This noise voltage can be used to estimate the smallest signal that the circuit can effectively amplify, sometimes called the ***minimum detectable signal*** (MDS).
- ❖ This depends strongly on the nature of the signal.
- ❖ If no special techniques are used, the MDS can be taken as equal to the equivalent input noise voltage in the passband of the amplifier.

$$MDS = \frac{\overline{V_{iN}^2}}{B} \cdot (\text{Bandwidth of the Network})$$

Equivalent input noise Generators

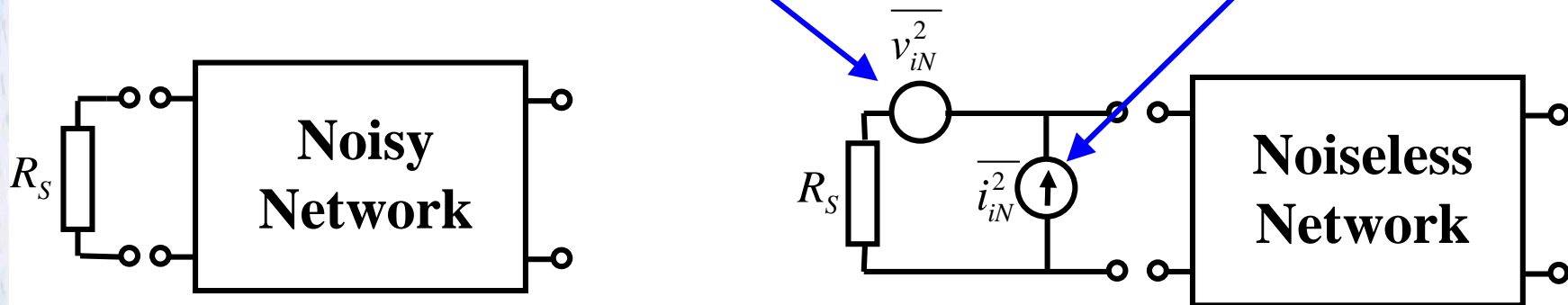- ❖ The **equivalent input noise** voltage for a particular configuration is dependent on the source resistance R_S , as well as the transistor parameters.
- ❖ This method is now extended to a more general and more useful representation by using **two** equivalent input noise generators:
 - equivalent input **voltage**
 - equivalent input **current**



BJT Equivalent input noise Generator

- ❖ The equivalent input noise for BJT is

$$\frac{\overline{v_{iN}^2}}{B} = 4kT(R_S + r_b) + (R_S + r_b)^2 2qI_B + \frac{|Z + r_b + R_S|^2}{g_m^2 R_L^2 \cdot |Z|^2} \cdot R_L^2 \left(\frac{4kT}{R_L} + 2qI_C \right)$$

- ❖ and it can be splitted to
- ❖ The equivalent input current for BJT is

$$\frac{\overline{i_{iN}^2}}{B} = 2qI_{eq} = 2q \left(I_B + K_1' \frac{I_B^a}{f} + \frac{I_C}{|\beta(j\omega)|^2} \right)$$

- ❖ and it appears as shot noise from I_{eq}
- ❖ The equivalent input voltage for BJT is

$$\frac{\overline{v_{iN}^2}}{B} = 4kTR_S + 4kT \left(r_b + \frac{1}{2g_m} \right) + R_S^2 2q \left(I_B + K_1' \frac{I_B^a}{f} + \frac{I_C}{|\beta(jf)|^2} \right)$$


Noise model for linear IC

- ❖ IC amplifiers designed for **low-noise** operation generally use a simple differential-pair input stage with **resistive loads**.
- ❖ The noise of following stages is generally not significant, and the resistive loads make only a small noise contribution.
- ❖ However, circuits of this type (the 725 op amp is an example) are inefficient in terms of gain and bandwidth.
- ❖ Using **active loads** (for example in the 741) allows realization of very high gain in relatively few stages,
- ❖ However, by their very nature, active loads amplify their own internal noise and cause considerable degradation of circuit noise performance.

Noise model for 741

- ❖ Noise model for OpAmp circuits is presented below,
- ❖ The concrete form for input noise generators depends on particular circuit design

For 741 OpAmp these expressions are:

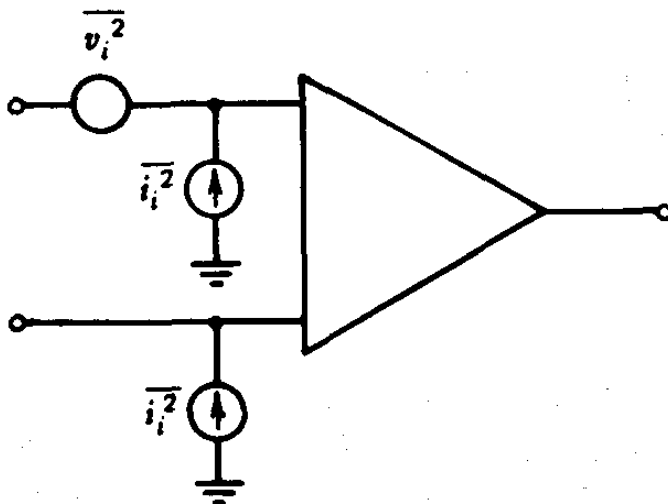

$$\frac{\overline{v_i^2}}{B} = 4kT(16000)$$


$$\frac{\overline{i_i^2}}{B} = 2qI_B \approx 2q(0.2 \cdot 10^{-6})$$

Noise analysis methods


- ❖ The most general method of specifying the noise performance of circuits is by specifying input noise generators as described above.
- ❖ However, a number of specialized methods of specifying noise performance have been developed that are convenient in particular situations.
- ❖ Some of these methods are now described.
 - Noise Bandwidth
 - Signal to Noise Ratio
 - Noise Figure
 - Noise temperature

Noise bandwidth

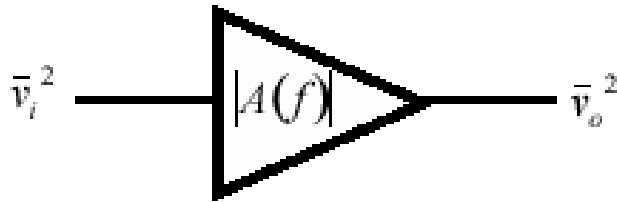- ❖ The total noise depends on the bandwidth of the system.
- ❖ For example, the total noise voltage at the output of a voltage amplifier with the frequency dependent gain $A_v(f)$ is


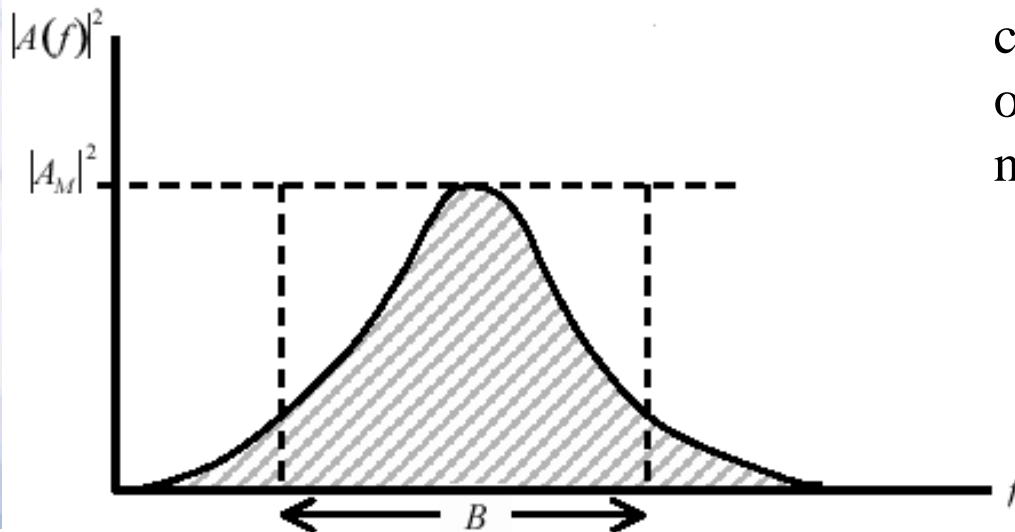
$$\bar{v}_{on}^2 = \int_0^{\infty} \frac{\bar{v}_n^2}{\Delta f} A(f)_v^2 df$$



Note: Since spectral noise components are non-correlated, one must integrate over the noise power.

Bandwidth of white Noise



- ❖ The evaluation of the integral is a complicated task.
- ❖ However, if the equivalent input noise **spectral density** of a circuit is **constant** (i.e., if the noise is white), we can simplify the calculations using the concept of *noise bandwidth* .

$$\overline{v_{on}^2} = \int_0^{\infty} \frac{\overline{v_n^2}}{\Delta f} A(f)_v^2 df = \frac{\overline{v_n^2}}{\Delta f} \int_0^{\infty} |A(f)|^2 df = S_{io} \int_0^{\infty} |A(f)|^2 df$$

- ❖ The evaluation of this integral is often difficult except for very simple transfer functions.
- ❖ However, if the problem is transformed into a *normalized* form, the integrals of common circuit functions can be evaluated and tabulated for use in noise calculations.

Normalized form

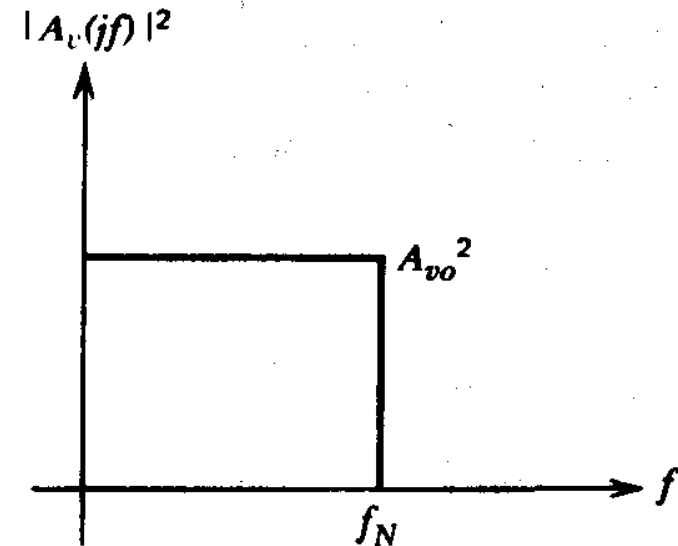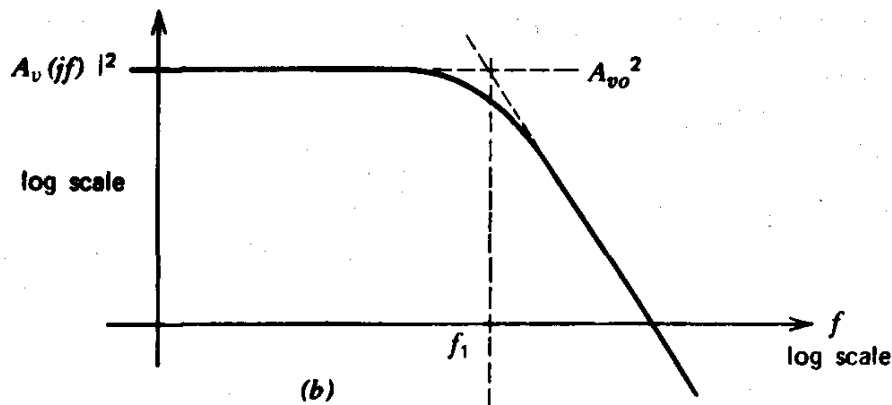- ❖ For this purpose, consider a transfer function as shown with the same low-frequency value A_{vo} as the original circuit but with an abrupt band edge at a frequency f_N .



- ❖ Frequency f_N is chosen to give the *same* total output noise voltage as the original circuit when the same input noise voltage is applied. Thus

Normalized Noise Band

- ❖ If $\overline{v_{oT}^2}$ and $\overline{v_{oT}^2}$ are evaluated, we obtained the *normalized noise band*, f_N :

$$f_N = \frac{1}{A_{vo}^2} \int_0^{\infty} |A_v(f)|^2 df$$

- ❖ Consider an amplifier with a single-pole frequency response given by
- ❖ substitution gives:

$$A_v(f) = \frac{A_{vo}}{1 + j \frac{f}{f_1}}$$

$$f_N = \frac{1}{A_{vo}^2} \int_0^{\infty} \left| \frac{A_{vo}}{1 + j \frac{f}{f_1}} \right|^2 df = \int_0^{\infty} \frac{df}{1 + \left(\frac{f}{f_1} \right)^2} = \frac{\pi}{2} f_1 = 1.57 f_1$$

Signal to Noise ratio

- ❖ The common parameter to characterize signals is their power.
- ❖ In all practical systems the signal always coexists with noise.
- ❖ Therefore it can be described by very important parameter Signal-to-Noise Ratio (SNR or S/N):

$$SNR(dB) \equiv 10 \cdot \lg \left(\frac{\text{Signal Power}}{\text{Noise Power}} \right)$$

Noise Figure

- ❖ The *noise figure (F)* specifies the noise performance of a circuit or a device.
- ❖ The definition of the noise figure of a circuit is

$$F \equiv \frac{\text{Input } S / N \text{ Ratio}}{\text{Output } S / N \text{ Ratio}}$$

- ❖ Its *disadvantage* is that it is limited to situations where the source impedance is *resistive*
- ❖ However, it is widely used as a measure of noise performance in communication systems where the source impedance is often resistive.

Noise Figure (cont.)


- ❖ Consider a circuit as shown below, where S represents signal power and N represents noise power.
- ❖ N_o is the total output noise including the circuit contribution and noise transmitted from the source resistance. The noise figure is .

$$F = \frac{S_i}{N_i} \cdot \frac{N_o}{S_o}$$

Noticing that

$$S_o = GS_i \text{ and } N_o = GN_i$$


$$F = \frac{N_o}{G \cdot N_i}$$

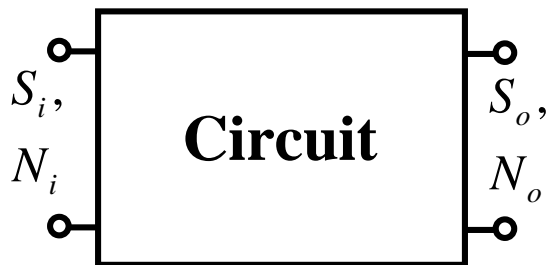

$$F = \frac{\text{Total Noise Power}}{\text{part of noise due to source resistance}}$$

Noise Figure (cont.)

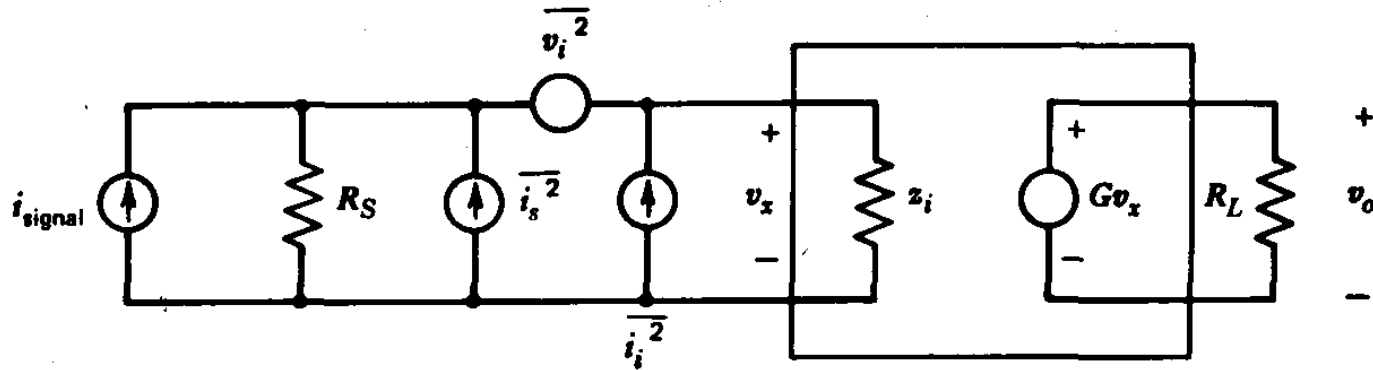- ❖ Consider the circuit below, consisting of the noise generators and signal source



- ❖ The noise at input terminals is

$$v_{xA} = v_i \frac{z_i}{z_i + R_S} + i_i \frac{z_i R_S}{z_i + R_S}$$

and thus

$$\overline{v_{xA}^2} = \overline{v_i^2} \frac{|z_i|^2}{|z_i + R_S|^2} + \overline{i_i^2} \frac{|z_i R_S|^2}{|z_i + R_S|^2}$$

Noise Figure (cont.)

The noise power in R_L from **noise generators** is

$$N_{oA} = \frac{|G|^2}{R_L} \overline{v_{xA}^2} = \frac{|G|^2}{R_L} \left[\overline{v_i^2} \frac{|z_i|^2}{|z_i + R_S|^2} + \overline{i_i^2} \frac{|z_i R_S|^2}{|z_i + R_S|^2} \right]$$

The noise power in R_L from **source resistor** is

$$N_{oB} = \frac{|G|^2}{R_L} \frac{|z_i R_S|^2}{|z_i + R_S|^2} \overline{i_s^2} = \frac{|G|^2}{R_L} \frac{|z_i R_S|^2}{|z_i + R_S|^2} \cdot 4kT \frac{B}{R_S}$$

Finally, the Noise Figure is


$$F = \frac{N_{oA} + N_{oB}}{N_{oB}} = \frac{|G|^2}{R_L} \frac{\overline{v_i^2}}{4kTB R_S} + \frac{\overline{i_i^2}}{4kTB / R_S}$$

Note that F is **independent** of all circuit parameters except the source resistance R_S and the equivalent input noise generators

Noise Figure vs. R_s

- ❖ For very **low** values of R_s , the v -generator is dominant, whereas for **large** R_s the i -generator is the most important.
- ❖ It is apparent, that F has a minimum as R_s varies.
- ❖ By differentiating F with respect to R_s , we can calculate the value of R_s giving minimum F :
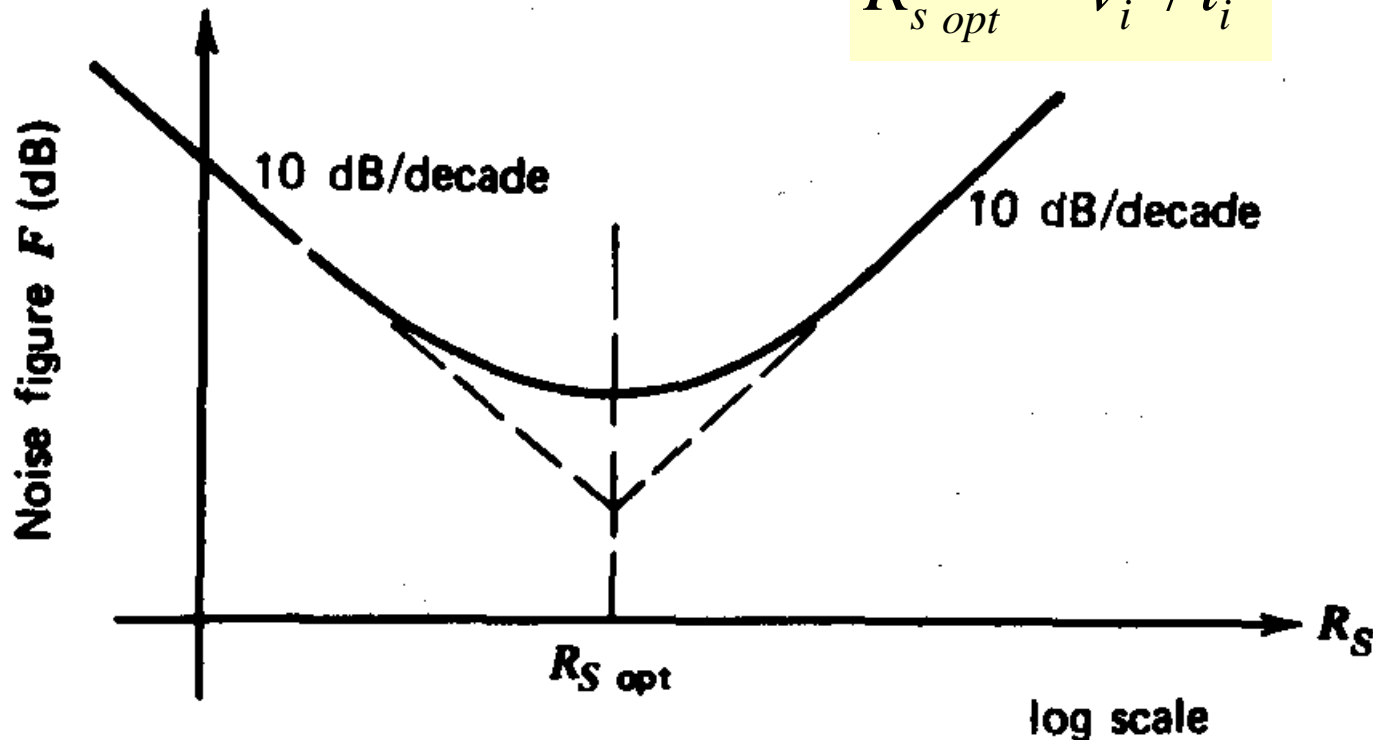
$$R_{s \text{ opt}}^2 = \overline{v_i^2} / \overline{i_i^2}$$



Example for BJT

- ❖ Consider the noise figure of a bipolar transistor at low-to-moderate frequencies where both **flicker noise** and high-frequency effects **are neglected**. Assume collector current of $I_C = 1 \text{ mA}$, and with $\beta_f = 100$ and $r_b = 50$.

Solution

$$\frac{\overline{v_{iN}^2}}{B} = 4kTR_S + 4kT \left(r_b + \frac{1}{2g_m} \right) + R_S^2 2q \left(I_B + K_1 \frac{I_B^a}{f} + \frac{I_C}{|\beta(jf)|^2} \right)$$

$$\frac{\overline{i_{iN}^2}}{B} = 2qI_{eq} = 2q \left(I_B + K_1 \frac{I_B^a}{f} + \frac{I_C}{|\beta(j\omega)|^2} \right)$$

$$\overline{v_{iN}^2} \approx 4kT \left(r_b + \frac{1}{2g_m} \right) B$$

$$\overline{i_{iN}^2} \approx 2q \frac{I_C}{\beta_F} B$$

$$R_{s \text{ opt}} = \frac{\overline{v_i^2}}{\overline{i_i^2}} = \frac{\sqrt{\beta_f}}{g_m} \sqrt{1 + 2g_m r_b}$$

$$F_{opt} \approx 1 + \frac{1}{\sqrt{\beta_f}} \sqrt{1 + 2g_m r_b} \approx 1.22 \text{ (0.9dB)}$$

Noise Temperature

- ❖ The noise temperature T_n of a circuit is defined as the temperature at which the source resistance R_s must be held so that the noise output from the circuit due to R_s equals the noise output due to the circuit itself.
- ❖ For the previous circuit, the output noise N_{oA} due to the circuit itself is unchanged but the output noise due to the source resistance becomes

$$N'_{oB} = \frac{|G|^2}{R_L} \frac{|z_i R_s|^2}{|z_i + R_s|^2} \cdot 4kT_n \frac{B}{R_s}$$

$$N'_{oB} = N_{oB} \frac{T}{T_n}$$

- ❖ From definition:

$$F = 1 + \frac{N_{oA}}{N_{oB}}$$

- ❖ Substitution gives:

$$(F - 1) = \frac{T_n}{T}$$

T_n vs. F

- ❖ Thus noise temperature and noise figure are directly related.
- ❖ The main application of noise temperature provides a convenient expanded measure of noise performance near $F = 1$ for very-low-noise amplifiers.
- ❖ A noise figure of $F = 2$ (3 dB) corresponds to $T_n = 290^\circ\text{K}$ and
- ❖ $F = 1.1$ (0.4 dB) corresponds to $T_n = 29^\circ\text{K}$

Low-Noise Design

- ❖ The main objective of the noise analysis is to design a low-noise circuit.
- ❖ One of the efficient way to do that is a matching of the source resistance to the noise parameters of the circuits as discussed before (to find R_{Sopt})
- ❖ Usually requirements low-noise design contradict to the other important circuit parameters such as: bandwidth, gain, input/output characteristics, etc.
- ❖ The low-noise design is different for each specific case, but there are some general recommendations.

Multistage Circuits

- ❖ In case of multistage circuits the particular effort should be applied for the very first stage.
- ❖ The noise of following stages is generally not significant.
- ❖ In particular multistage circuit - OpAmp designed for **low-noise** operation - generally use a simple differential-pair input stage with **resistive** loads instead of **active** loads
- ❖ JFET transistors are preferable.
- ❖ Zener Diodes should not be used in OpAmp Design to avoid very high avalanche noise.

- ❖ The following stages can use BJTs and active loads to allow very high gain in relatively few stages.
- ❖ Avoid to use carbon resistors due to flicker noise.
- ❖ The total Bandwidth of the circuit should be limited to the bandwidth of the signal spectrum.
- ❖ So that, acoustic amplifiers bandwidth should be 20 Hz to 20kHz or little wider.

