





**School of Electronic
and Communications
Engineering**

2. Noise Models

Noise Models

- ❖ In the above sections, the various physical sources of noise in electronic circuits were described.
- ❖ In this section, these sources of noise are brought together to form the small-signal equivalent circuits:
 - resistors (already discussed)
 - diodes,
 - bipolar (BJT) and
 - field-effect (FET) transistors and
 - linear IC (OpAmp)

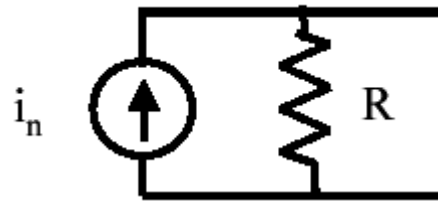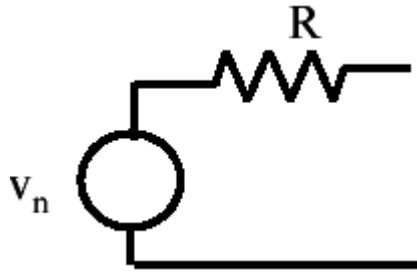- ❖ Noise can be modelled as
 - a Thevenin equivalent voltage source or
 - a Norton equivalent current source.




- ❖ The noise contributed by the resistor is modeled by the source, thus the resistor is considered noiseless.

Two resistors

- ❖ It is important to note that noise sources:
 - Do not have polarity
 - Do not add algebraically, but as RMS sums
- ❖ If the sources are not correlated, then:
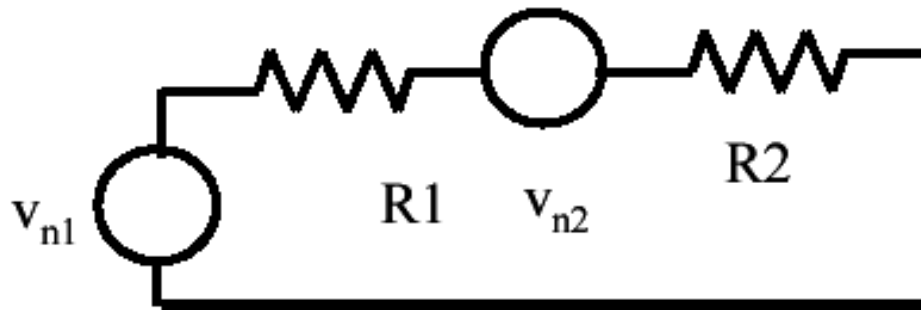
$$v_{n,total}^{-2} = v_{n1}^{-2} + v_{n2}^{-2} = 4kTBR_1 + 4kTBR_2$$



$$v_n(rms) = \sqrt{v_n^2} = \sqrt{v_{n1}^2 + v_{n2}^2} = \sqrt{4kTBR_1 + 4kTBR_2}$$

Correlated resistors

- ❖ If the sources are correlated (derived from the same physical noise source), then there is an additional term: C can vary between -1 and 1 .

$$\overline{v_n^2} = \overline{v_{n1}^2} + \overline{v_{n2}^2} + 2Cv_{n1}v_{n2}$$

$$v_n (rms) = \sqrt{\overline{v_n^2}} = \sqrt{\overline{v_{n1}^2} + \overline{v_{n2}^2} + 2Cv_{n1}v_{n2}}$$

Thermal Noise Power

- ❖ The available noise power can be calculated from the RMS noise voltage or current:

$$P_{no} = \frac{E_{no}^2}{R_L} = \frac{(E_t / 2)^2}{R_S} = kTB$$


- ❖ That is, the available noise power from the source is
 - independent of resistance
 - proportional to temperature
 - proportional to bandwidth
 - has no frequency dependence
- ❖ $P=4 \times 10^{-21}$ watts in a 1 Hz bandwidth at the standard noise room temperature of 290 K.

Can a resistor produce infinite noise voltage?

$$\overline{v_n^2} \equiv \overline{v_t^2} = 4kT \cdot R \cdot B \quad \text{therefore} \quad \overline{v_t^2} \rightarrow \infty \quad \text{when} \quad B \rightarrow \infty$$

Equivalent circuit for noisy resistor always have some shunt. Therefore


$$|V_{no}| = |V_{no}| \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$$

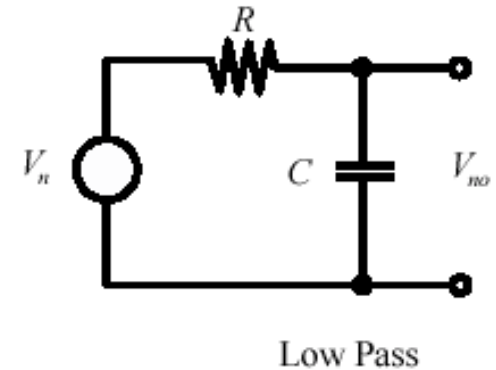

To find the noise power

$$\overline{v_{no}^2} = \int_0^\infty |V_{no}|^2 dt = \frac{kT}{C}$$


$\log_{10}|V_{no}|$

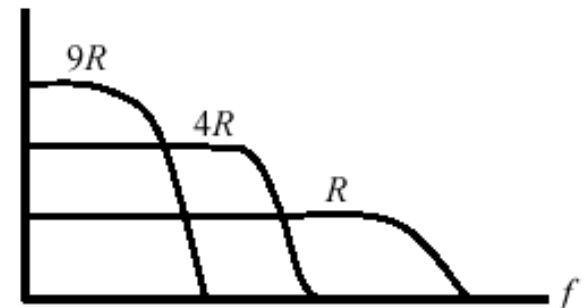

Therefore total noise power is **independent** of R !!!

Junction Diode

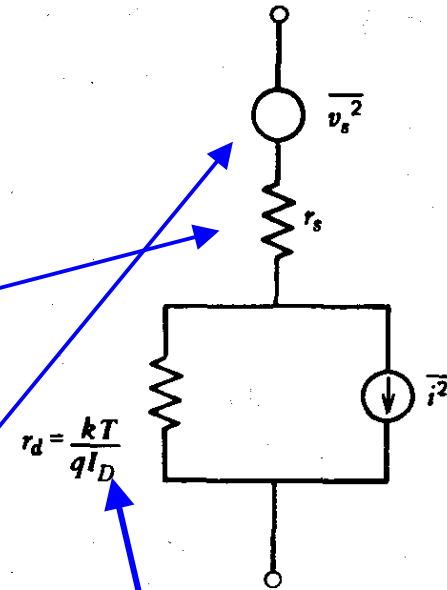- ❖ The equivalent circuit for a junction diode was considered briefly in the consideration of **shot** noise.
- ❖ The basic equivalent circuit of diode (discussed) can be made complete by adding series resistance r_s , as shown.
- ❖ Since r_s is a physical resistor due to the resistivity of the silicon, it exhibits **thermal** noise.



$$\overline{v_t^2} = 4kT \cdot r_s \cdot B$$

- ❖ Experimentally it has been found that any **flicker** noise present can be represented by a current generator in shunt with r_d , and this is conveniently combined with the **shot**-noise

$$\overline{i^2} = 2qI_D \cdot B + K \frac{I_d^\alpha}{f} B$$


BJT (noise model)

- ❖ In a BJT in the forward-active region, minority carriers diffuse and drift across the base region to be collected at the collector-base junction.
- ❖ Minority carriers entering the collector-base depletion region are accelerated by the field existing there and swept across this region to the collector.
- ❖ The time of arrival at the collector-base junction of the diffusing (or drifting) carriers is a purely random process, and thus the transistor collector current consists of a series of random current pulses.

Contribution I

- Consequently, collector current I_C shows *full shot noise*, and this is represented by a shot noise current generator i_c^2 from collector to emitter as shown in the equivalent circuit of BJT


$$\overline{i_c^2} = 2qI_C \cdot B$$

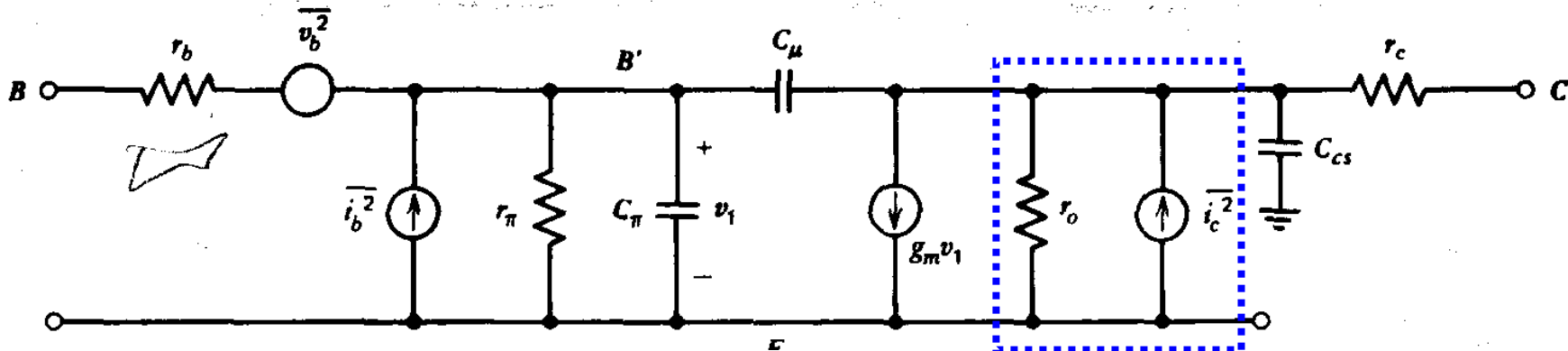

Contribution II

- ❖ Base current I_B in a transistor is due to recombination in the base and to carrier injection from the base into the emitter.
- ❖ All of these are independent random processes, and thus I_B also shows *full shot noise*.
- ❖ **Flicker** noise and **burst** noise in a BJT have been found experimentally. This is represented by shot noise current generator


$$\overline{i_b^2} = 2qI_B \cdot B + K_1 \frac{I_b^\alpha}{f} B + K_2 \frac{I_b^c}{1 + (f / f_c)^2} B$$

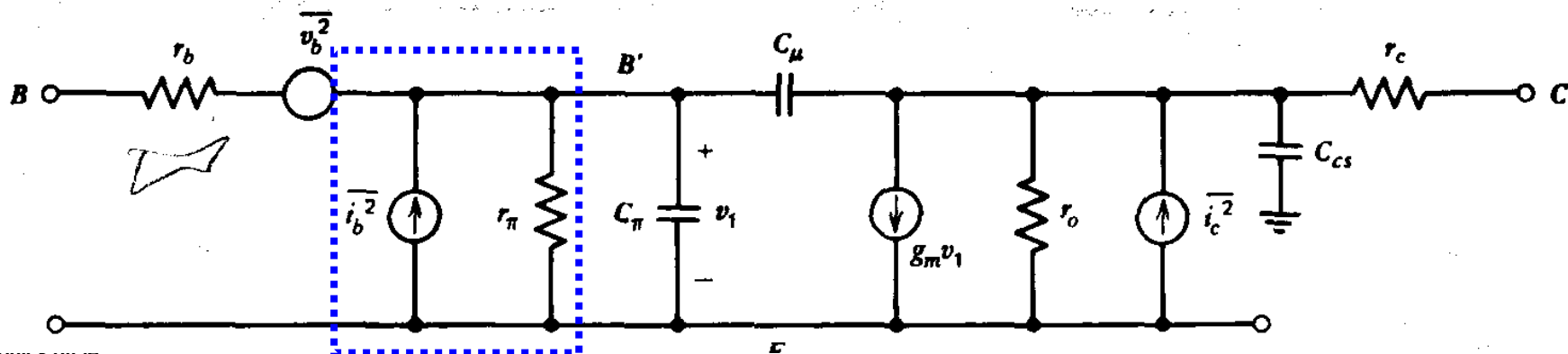

Contribution III

- ❖ Transistor base resistor r_b is a physical resistor and thus has thermal noise.
- ❖ Collector series resistor r_c also shows thermal noise, but since this is in series with the high-impedance collector node, this noise is negligible and is usually not included in the model.

$$\overline{v_b^2} = 4kTB$$

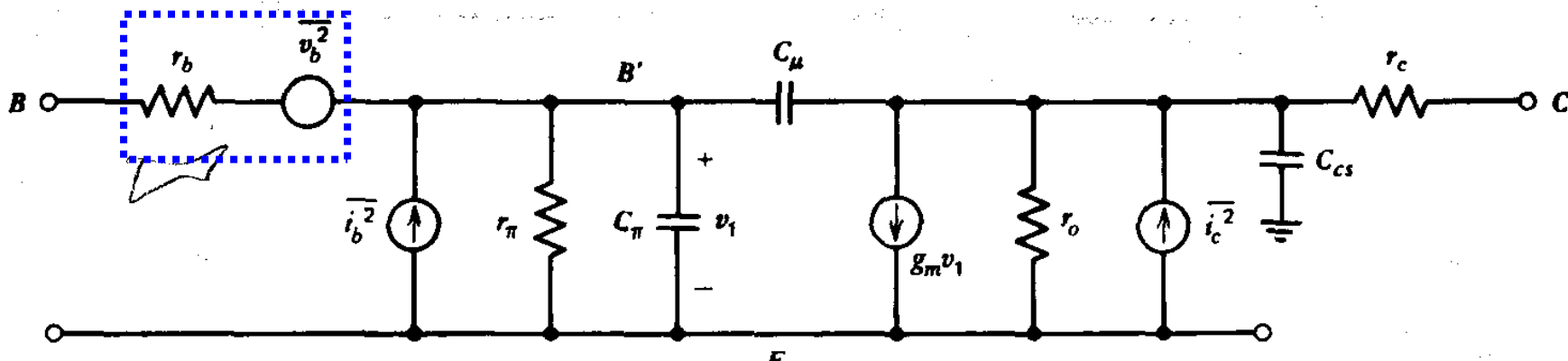

All Contributions

- ❖ Shot noise in collector current I_c ,


$$\overline{i_c^2} = 2qI_c \cdot B$$

- ❖ Shot, Flicker noise and burst noise in Base current I_B

$$\overline{i_b^2} = 2qI_B \cdot B + K_1 \frac{I_b^\alpha}{f} B + K_2 \frac{I_b^c}{1 + (f / f_c)^2} B$$

- ❖ Thermal noise in base resistor r_b .


$$\overline{v_b^2} = 4kTB$$

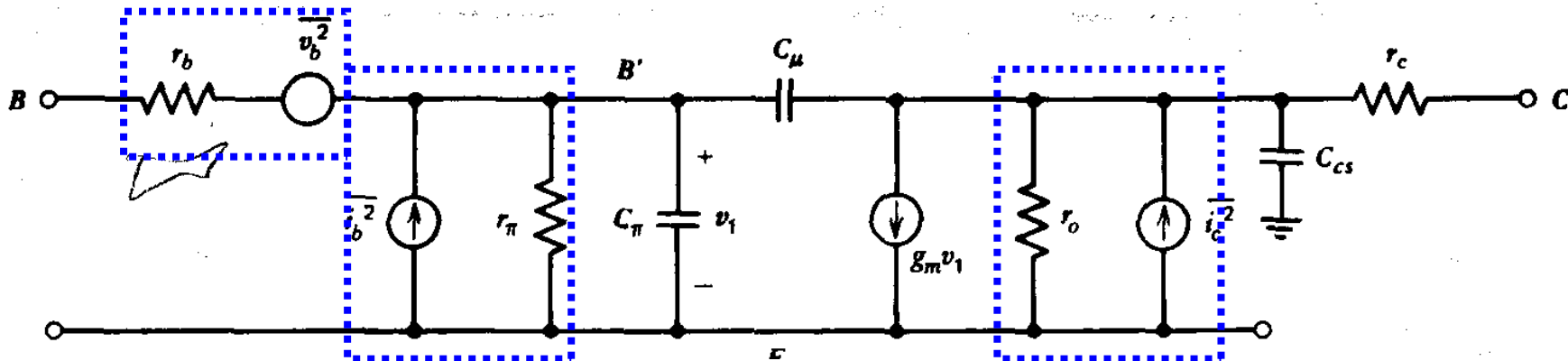

“corner” frequency


- ❖ The base-current noise spectrum can be plotted where burst noise has been neglected for simplicity.
- ❖ The shot noise and flicker noise asymptotes meet at a frequency f_a , which is called the flicker noise "corner" frequency.

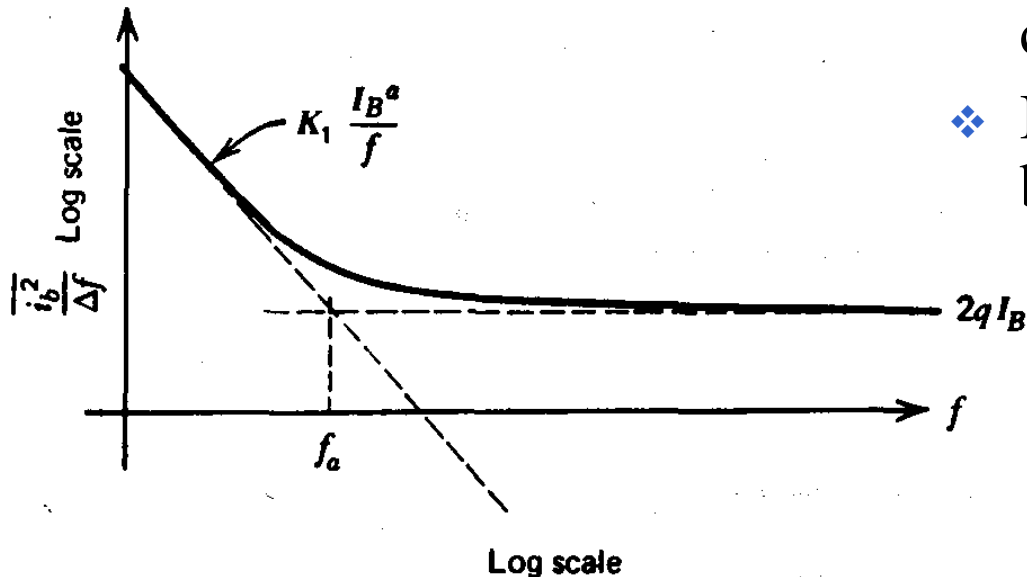- ❖ In some transistors using careful processing, f_a can be as low as 100 Hz.
- ❖ In other transistors f_a can be as high as 10 MHz.



FET noise model

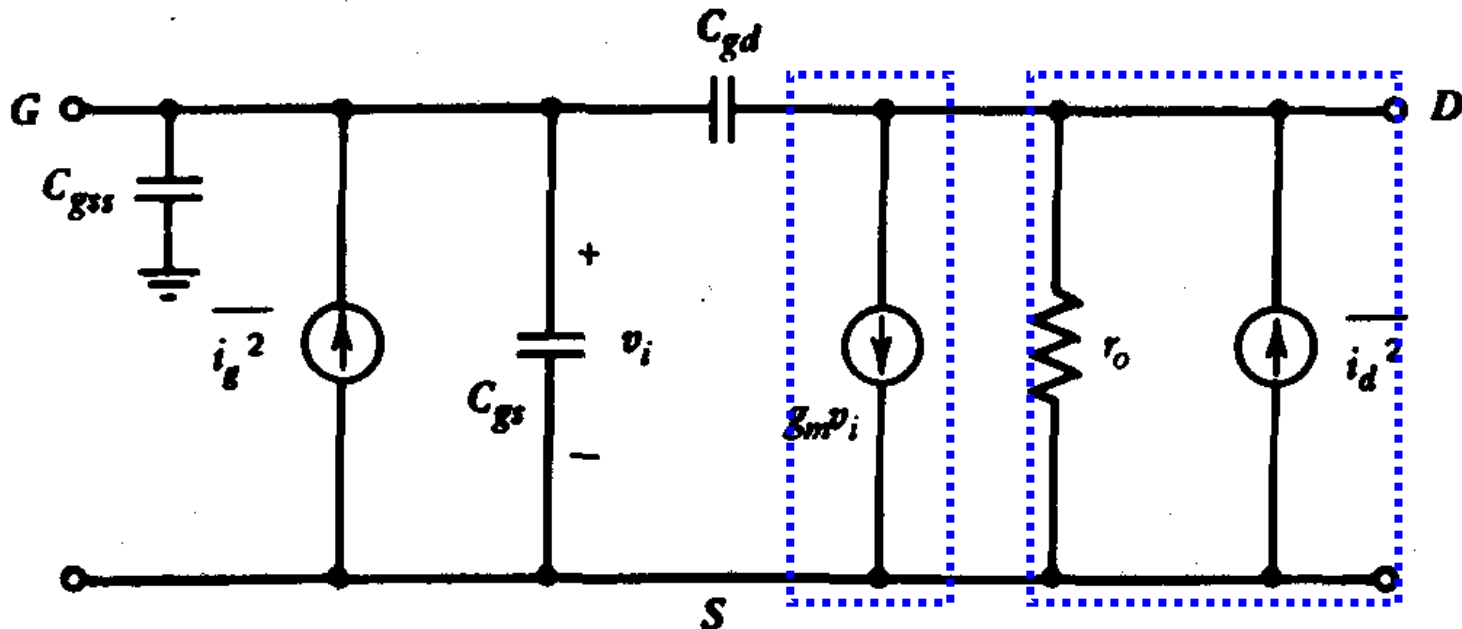- ❖ In FET the resistive channel joining source and drain, so that the drain current is controlled by the gate-source voltage.
- ❖ Since the channel material is *resistive*, it exhibits *thermal noise*, and this is the *major source* of noise in FETs this noise source can be represented by a noise-current generator i_D^2 from drain to source in the FET small-signal equivalent circuit.




Contributions

- ❖ **Flicker** noise in the FET is also found experimentally to be represented by a drain-source current generator,

$$\overline{i_d^2} = 4kT \left(\frac{2}{3} g_m \right) + K_2 \frac{I_D^a}{f} B$$


- ❖ The other source of noise in FETs is **shot noise** generated by the gate leakage current and is usually **very small**. It becomes significant only when the driving-source impedance connected to the FET gate is very large.

$$\overline{i_g^2} = 2qI_G \cdot B$$

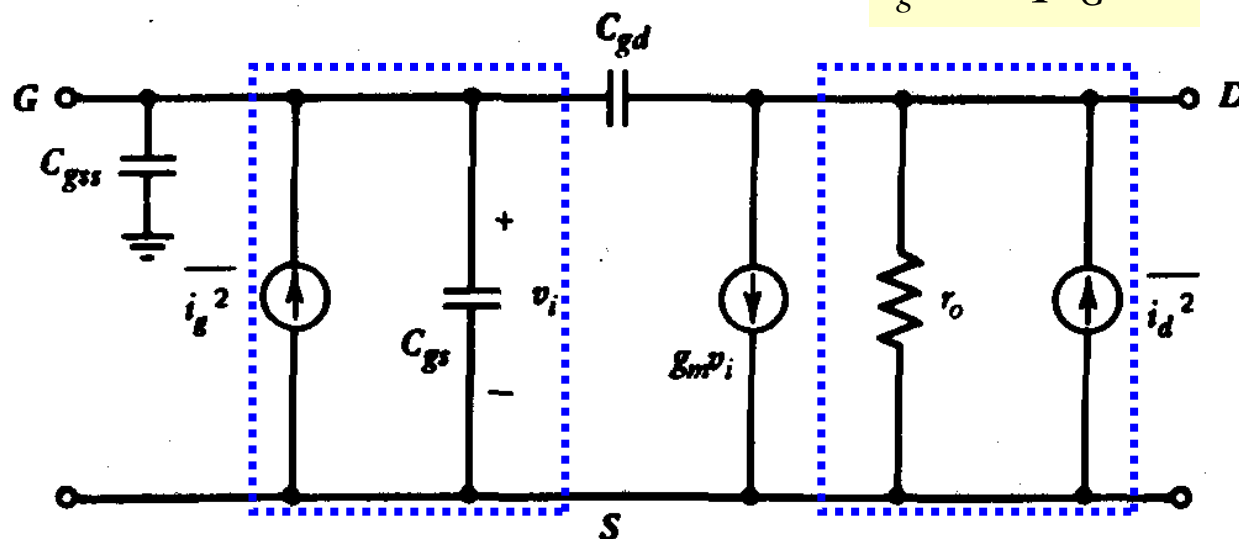


BJT noise performance

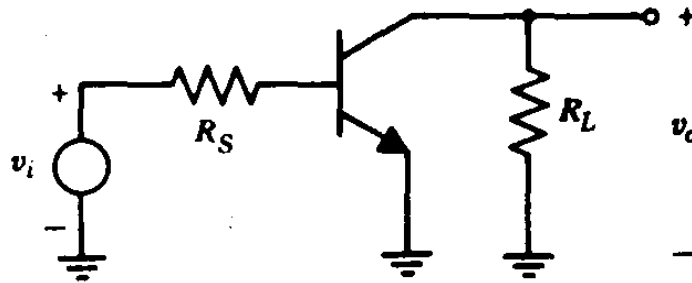- ❖ Consider the noise performance of the simple transistor stage with the ac schematic shown below



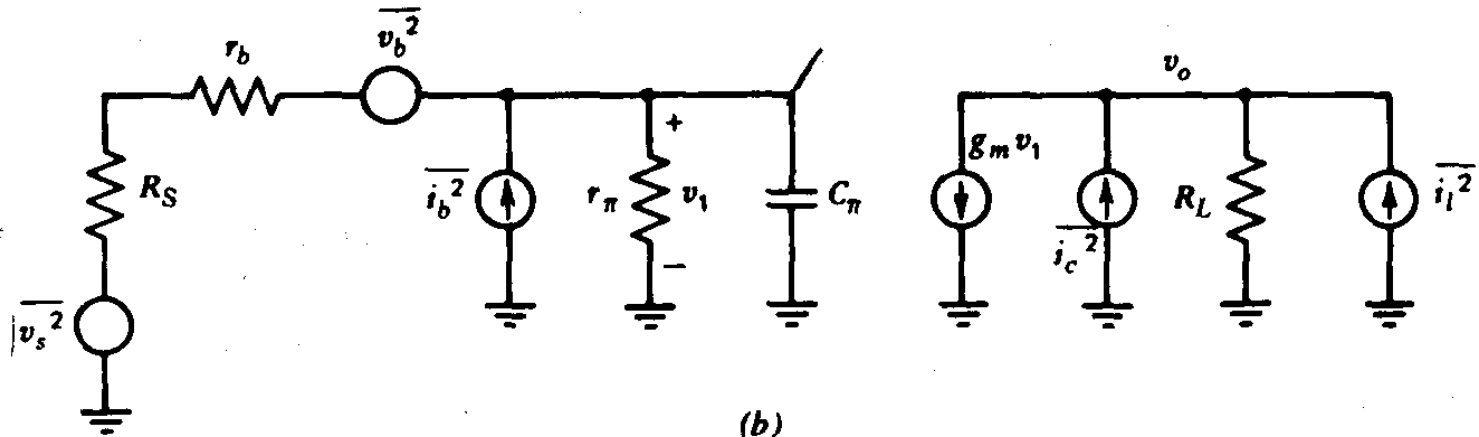- ❖ Consider the noise performance of the simple transistor stage with the ac schematic shown below



BJT noise performance (a)

- ❖ In this equivalent circuit the external input signal v_i , has been ignored so that output signal v_o is due to noise generators only. C_μ is assumed small and is neglected. Output resistance r_o is also neglected. The transistor noise generators are as described previously and in addition

$$\overline{v_s^2} = 4kTR_S B$$

$$\overline{i_l^2} = 4kT \frac{1}{R_L} B$$

- ❖ The total output noise can be calculated by considering each noise source in turn and performing the calculation as *if* each noise source were a sinusoid with rms value equal to that of the noise source being considered.

BJT noise performance

- ❖ The spectral density of the noise generator is equal:

$$\frac{\overline{v_o^2}}{B} = g_m^2 R_L^2 \frac{|Z|^2}{|Z + r_b + R_S|^2} \left[4kT(R_S + r_b) + (R_S + r_b)^2 2qI_B \right] + R_L^2 \left(\frac{4kT}{R_L} + 2qI_C \right) \quad \text{where } Z \text{ is} \quad Z = r_\pi \left\| \frac{1}{j\omega C_\pi} \right.$$

- ❖ Substituting for Z gives:

$$\frac{\overline{v_o^2}}{B} = g_m^2 R_L^2 \frac{r_\pi^2}{(r_\pi + r_b + R_S)^2} \cdot \frac{1}{1 + (f / f_1)^2} \left[4kT(R_S + r_b) + (R_S + r_b)^2 2qI_B \right] + R_L^2 \left(\frac{4kT}{R_L} + 2qI_C \right) \quad \text{where} \quad f_1 = \frac{1}{2\pi [r_\pi \parallel (r_b + R_S)] C_\pi}$$

BJT noise spectral density

- ❖ The output noise-voltage spectral density has a frequency-dependent part and a constant part.
- ❖ The frequency dependence arises because the gain of the stage begins to fall above frequency f_1 , and noise due to generators v_s , v_b , and i_b , which appears amplified, also begins to fall.
- ❖ The constant term is due to noise generators i_l and i_c
- ❖ Assuming $I_C=100 \mu\text{A}$, $R_S=500 \Omega$, $R_L=5 \text{ k}\Omega$, $\beta=100$, $C_\pi=10 \text{ pF}$, $r_b=200\Omega$

