

## Homework #1 Solutions:

**4.2** Refer to Fig. P4.2.

(a) Diode is conducting, thus

$$V = -3 \text{ V}$$

$$I = \frac{+3 - (-3)}{10 \text{ k}\Omega} = 0.6 \text{ mA}$$

(b) Diode is reverse biased, thus

$$I = 0$$

$$V = +3 \text{ V}$$

(c) Diode is conducting, thus

$$V = +3 \text{ V}$$

$$I = \frac{+3 - (-3)}{10 \text{ k}\Omega} = 0.6 \text{ mA}$$


(d) Diode is reverse biased, thus

$$I = 0$$


$$V = -3 \text{ V}$$

**4.3**

(a)

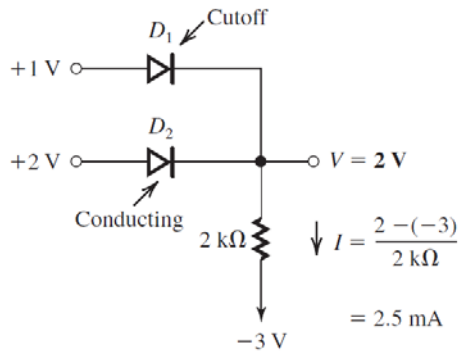

(b)

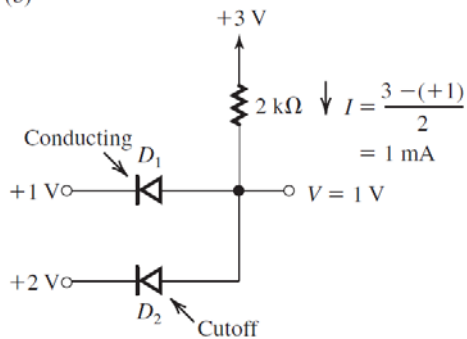

**4.6**

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1


$$X = AB, \quad Y = A + B$$

$X$  and  $Y$  are the same for

$$A = B$$

$X$  and  $Y$  are opposite if  $A \neq B$


4.9

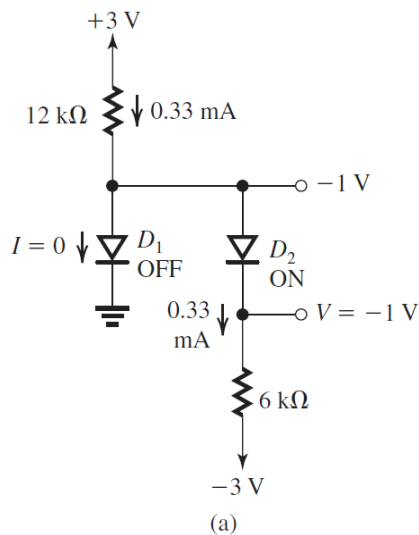

(a) If we assume that both  $D_1$  and  $D_2$  are conducting, then  $V = 0$  V and the current in  $D_2$  will be  $[0 - (-3)]/6 = 0.5$  mA. The current in the 12 kΩ will be  $(3 - 0)/12 = 0.25$  mA. A node equation at the common anodes node yields a negative current in  $D_1$ . It follows that our assumption is wrong and  $D_1$  must be off. Now making the assumption that  $D_1$  is off and  $D_2$  is on, we obtain the results shown in Fig. (a):

$$I = 0$$

$$V = -1 \text{ V}$$

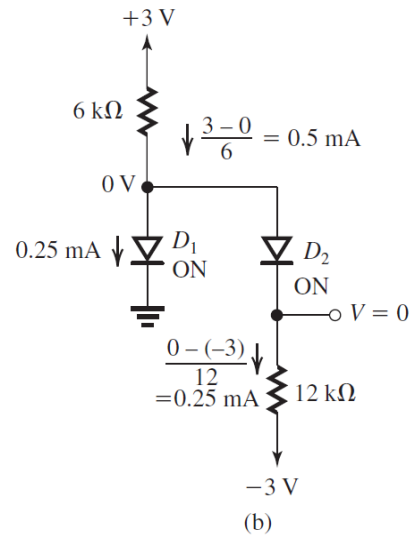

(b) In (b), the two resistors are interchanged. With some reasoning, we can see that the current supplied through the 6-kΩ resistor will exceed that drawn through the 12-kΩ resistor, leaving sufficient current to keep  $D_1$  conducting. Assuming that  $D_1$  and  $D_2$  are both conducting gives the results shown in Fig. (b):

$$I = 0.25 \text{ mA}$$

$$V = 0 \text{ V}$$

4.10:

