

14.7

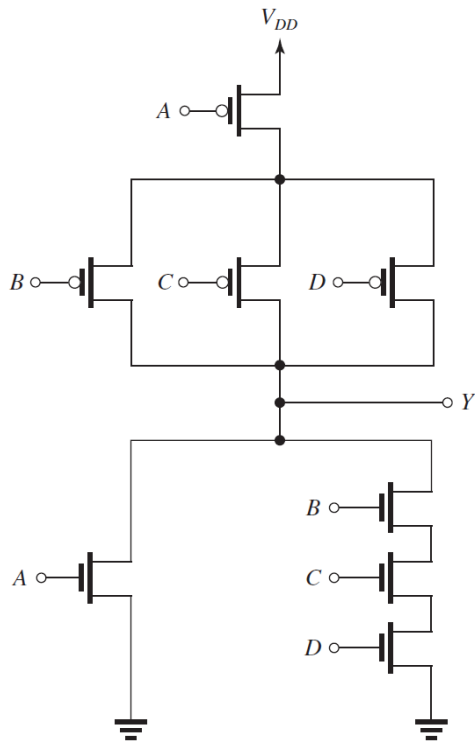


Figure 1

Figure 1 shows the complete CMOS logic circuit where we have obtained the PDN as the dual of the given PUN. The logic function can be written from the PDN as

$$\bar{Y} = A + BCD$$

or equivalently

$$Y = \overline{A + BCD}$$

**14.11** Direct realization of the given expression results in the PUN of the logic circuit shown in Fig. 1. The PDN shown is obtained as the dual of the PUN. Not shown are the two inverters needed to obtain  $\bar{A}$  and  $\bar{B}$ .

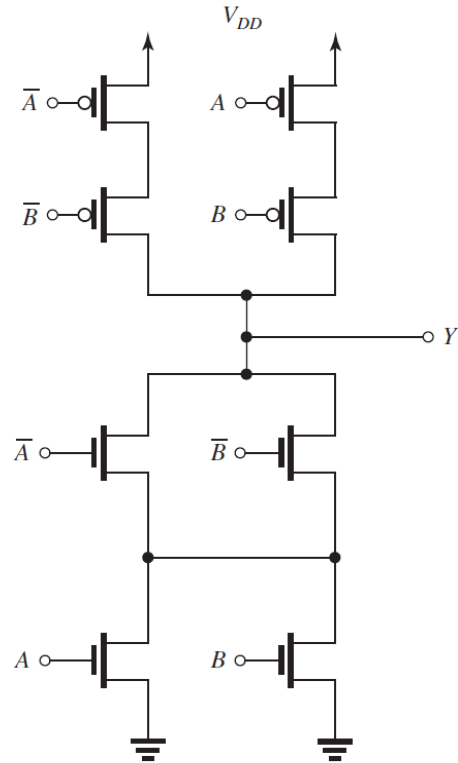


Figure 1

**15.26** Refer to Fig. 15.17. Since  $V_{OH}$  is the value of  $v_O$  at which  $Q$  stops conducting,

$$V_{DD} - V_{OH} - V_t = 0$$

then

$$V_{OH} = V_{DD} - V_t$$

where

$$V_t = V_{t0} + \gamma \left( \sqrt{V_{OH} + 2\phi_f} - \sqrt{2\phi_f} \right)$$

$$= V_{t0} + \gamma \left( \sqrt{V_{DD} - V_t + 2\phi_f} - \sqrt{2\phi_f} \right)$$

Substituting  $V_{t0} = 0.4$  V,  $\gamma = 0.2$  V<sup>1/2</sup>,  $V_{DD} = 1.2$  V, and  $2\phi_f = 0.88$  V, we obtain

$$V_t = 0.4 + 0.2 \left( \sqrt{1.2 - V_t + 0.88} - \sqrt{0.88} \right)$$

$$V_t - 0.4 + 0.2\sqrt{0.88} = 0.2 \sqrt{2.08 - V_t}$$


$$(V_t - 0.212)^2 = 0.04(2.08 - V_t)$$

$$\Rightarrow V_t^2 - 0.384 V_t - 0.038 = 0$$

$$\Rightarrow V_t = 0.466 \text{ V}$$

$$\begin{aligned} V_{OH} &= 1.2 - 0.466 \\ &= 0.734 \end{aligned}$$

## 16.2

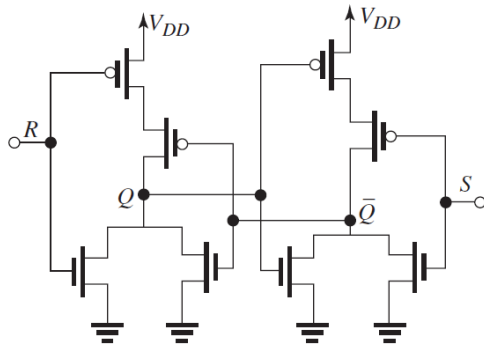

15.31

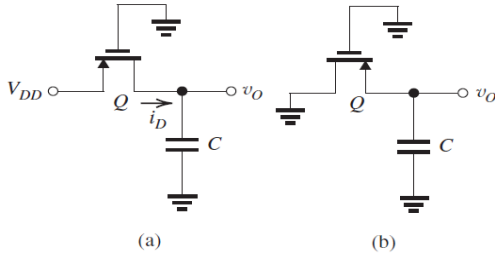


Figure 1

(a) Figure 1(a) shows the situation for  $t \geq 0$ . In this case  $V_i$  remains constant at  $V_{i0}$  and the capacitor charges to  $V_{DD}$ .

Thus,

$$V_{OH} = V_{DD}$$

(b) Figure 1 (b) shows the situation for  $t \geq 0$ . Here as  $C$  discharges through  $Q$ , the threshold voltage changes. The discharge current reduces to zero when  $v_O = |V_i|$ . Thus,

$$V_{OL} = |V_i|$$

where

$$|V_i| = |V_{i0}| + \gamma \left[ \sqrt{V_{DD} - V_{OL} + 2\phi_f} - \sqrt{2\phi_f} \right]$$

Substituting  $|V_i| = V_{OL}$ , we obtain

$$V_{OL} = |V_{i0}| + \gamma \left[ \sqrt{V_{DD} - V_{OL} + 2\phi_f} - \sqrt{2\phi_f} \right]$$

(c) Refer to Fig. 1(a).

At  $t = 0$ ,  $v_O = 0$  and  $Q$  will be operating in saturation. Thus,

$$\begin{aligned} i_D(0) &= \frac{1}{2} k_p (V_{DD} - |V_{i0}|)^2 \\ &= \frac{1}{2} \times 125 (1.2 - 0.4)^2 \\ &= 40 \mu\text{A} \end{aligned}$$

At  $t = t_{PLH}$ ,  $v_O = V_{DD}/2 = 0.6 \text{ V}$  and  $Q$  will be operating in the triode region. Thus,

$$\begin{aligned} i_D(t_{PLH}) &= k_p \left[ (V_{DD} - |V_{i0}|) \left( \frac{V_{DD}}{2} \right) - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right] \\ &= 125 \left[ (1.2 - 0.4) \times 0.6 - \frac{1}{2} (0.6)^2 \right] \\ &= 37.5 \mu\text{A} \end{aligned}$$

The average charging current can now be found as

$$i_{D|av} = \frac{1}{2} (40 + 37.5) = 38.75 \mu\text{A}$$

The propagation delay  $t_{PLH}$  can then be determined from

$$\begin{aligned} t_{PLH} &= \frac{C(V_{DD}/2)}{i_{D|av}} \\ &= \frac{C \times 0.6}{38.75 \times 10^{-6}} = 15.48 \times 10^3 C \text{ s} \end{aligned}$$

No value for  $C$  is given. If  $C = 10 \text{ fF}$ , we get

$$t_{PLH} = 17.8 \times 10^3 \times 10 \times 10^{-15} = 178 \text{ ps}$$