

Homework 2

4.20, 4.28 (both use diode equation, and assume $nV_T = 0.025\text{V}$),
4.40, 4.42, and 4.44

4.20 $I = I_S e^{V_D/V_T}$

$$10^{-3} = I_S e^{0.7/V_T}$$

For $V_D = 0.71\text{ V}$,

$$I = I_S e^{0.71/V_T}$$

Combining (1) and (2) gives

$$I = 10^{-3} e^{(0.71 - 0.7)/0.025}$$

$$= 1.49\text{ mA}$$

For $V_D = 0.8\text{ V}$,

$$I = I_S e^{0.8/V_T}$$

Combining (1) and (3) gives

$$I = 10^{-3} \times e^{(0.8 - 0.7)/0.025}$$

$$= 54.6\text{ mA}$$

Similarly, for $V_D = 0.69\text{ V}$ we obtain

$$I = 10^{-3} \times e^{(0.69 - 0.7)/0.025}$$

$$= 0.67\text{ mA}$$

and for $V_D = 0.6\text{ V}$ we have

$$I = 10^{-3} e^{(0.6 - 0.7)/0.025}$$

$$= 18.3\text{ }\mu\text{A}$$

To increase the current by a factor of 10, V_D must be increased by ΔV_D ,

$$10 = e^{\Delta V_D/0.025}$$

$$\Rightarrow \Delta V_D = 0.025 \ln 10 = 57.6\text{ mV}$$

4.28 We can write the following node equation at the diode anodes:

$$I_{D2} = 10\text{ mA} - V/R$$

$$I_{D1} = V/R$$

We can write the following equation for the diode voltages:

$$V = V_{D2} - V_{D1}$$

We can write the following diode equations:

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$I_{D1} = I_S e^{V_{D1}/V_T}$$

Taking the ratio of the two equations above, we have

$$\frac{I_{D2}}{I_{D1}} = \frac{10\text{ mA} - V/R}{V/R} = e^{(V_{D2} - V_{D1})/V_T} = e^{V/V_T}$$

To achieve $V = 50\text{ mV}$, we need


$$\frac{I_{D2}}{I_{D1}} = \frac{10\text{ mA} - 0.05/R}{0.05/R} = e^{0.05/0.025} = 7.39$$

Solving the above equation, we have


$$R = 42\text{ }\Omega$$

4.40 Refer to Example 4.2.

(a)

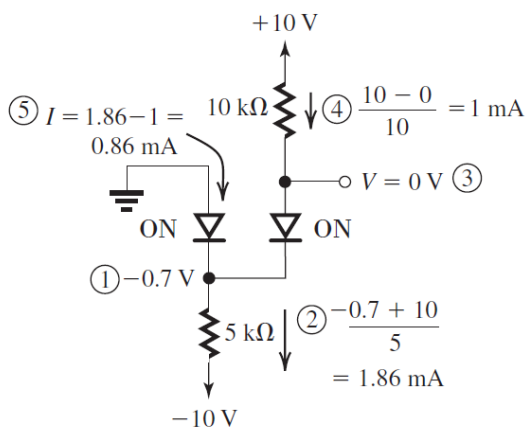


(b)

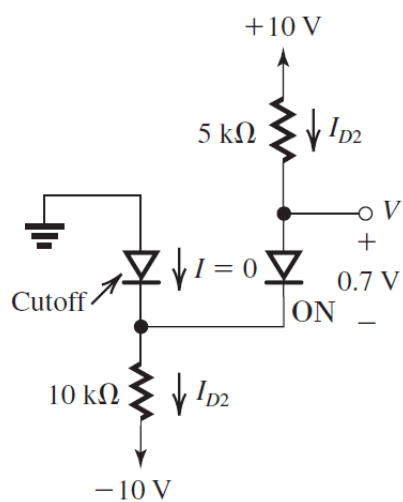

$$I_{D2} = \frac{10 - (-10) - 0.7}{15} = 1.29 \text{ mA}$$

$$V_D = -10 + 1.29(10) + 0.7 = 3.6 \text{ V}$$


(c)

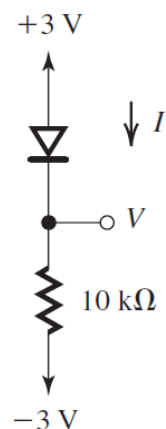

$$V = 3 - 0.7 = 2.3 \text{ V}$$

$$I = \frac{2.3 + 3}{10} = 0.53 \text{ mA}$$

(d)

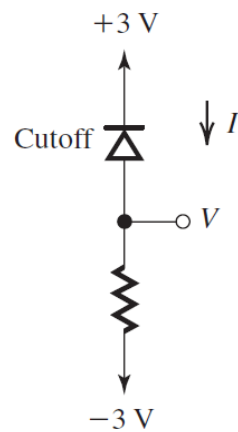


$$I = 0 \text{ A}$$

$$V = -3 \text{ V}$$


4.42

(a)

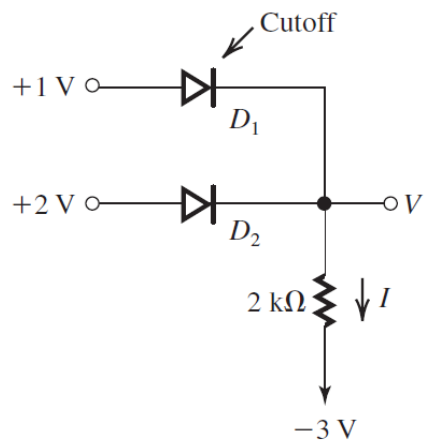


$$\begin{aligned} V &= 2 - 0.7 \\ &= 1.3 \text{ V} \\ I &= \frac{1.3 - (-3)}{2} \\ &= 2.15 \text{ mA} \end{aligned}$$

(b)

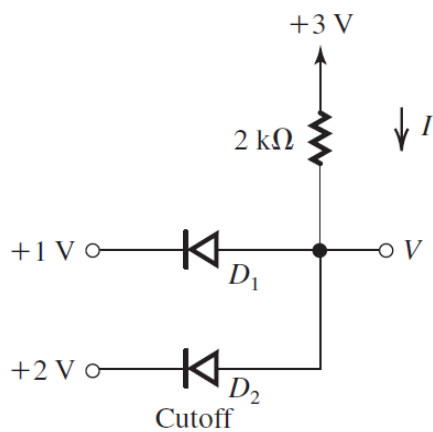


$$\begin{aligned} V &= 1 + 0.7 = 1.7 \text{ V} \\ I &= \frac{3 - 1.7}{2} = 0.65 \text{ mA} \end{aligned}$$

4.44

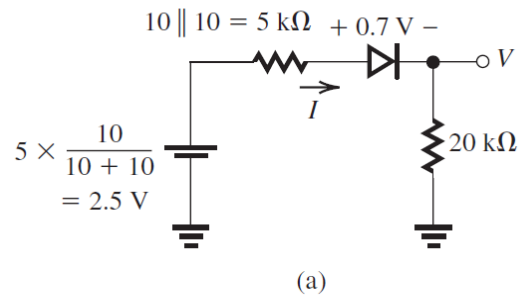

(a)

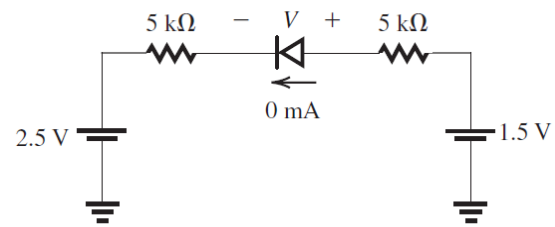

(b)

$$\begin{aligned} \text{(a)} \quad I &= \frac{2.5 - 0.7}{5 + 20} = 0.072 \text{ mA} \\ V &= 0.072 \times 20 = 1.44 \text{ V} \\ \text{(b)} \quad &\text{The diode will be cut off, thus} \\ I &= 0 \\ V &= 1.5 - 2.5 = -1 \text{ V} \end{aligned}$$