

Homework 5 Solution:

5.2 $C_{ox} = 9 \text{ fF}/\mu\text{m}^2$, $V_{OV} = 0.2 \text{ V}$

$L = 0.36 \mu\text{m}$, $V_{DS} = 0 \text{ V}$

$W = 3.6 \mu\text{m}$

$Q = C_{ox} \cdot W \cdot L \cdot V_{OV} = 2.33 \text{ fC}$

5.3 $k'_n = \mu_n C_{ox}$

$$= \frac{\text{m}^2}{\text{V} \cdot \text{s}} \frac{\text{F}}{\text{m}^2} = \frac{\text{F}}{\text{V} \cdot \text{s}} = \frac{\text{C/V}}{\text{V} \cdot \text{s}} = \frac{\text{C}}{\text{s}} \frac{1}{\text{V}^2}$$

$$= \frac{\text{A}}{\text{V}^2}$$


Since $k_n = k'_n W/L$ and W/L is dimensionless, k_n has the same dimensions as k'_n ; that is, A/V^2 .

5.6 $k_n = 5 \text{ mA/V}^2$, $V_m = 0.5 \text{ V}$,

small v_{DS}

$$i_D = k_n (v_{GS} - V_t) v_{DS} = k_n v_{OV} v_{DS}$$
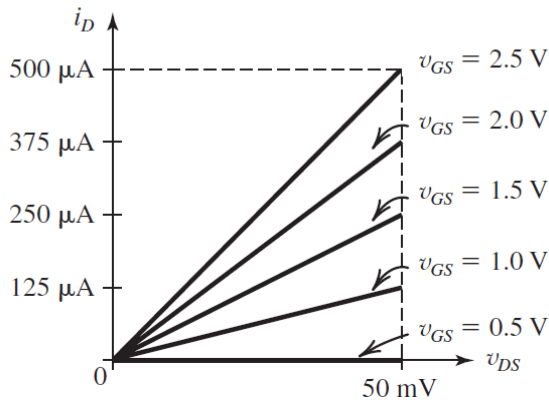
$$g_{DS} = \frac{1}{r_{DS}} = k_n v_{OV}$$



V_{GS} (V)	V_{OV} (V)	g_{DS} (mA/V)	r_{DS} (Ω)
0.5	0	0	∞
1.0	0.5	2.5	400
1.5	1.0	5.0	200
2.0	1.5	7.5	133
2.5	2.0	10	100

5.8 $r_{ds} = 1 / \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{DS} = v_{DS}}$

$$= \left[\frac{\partial}{\partial v_{DS}} \left(k_n \left(V_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right) \right) \right]^{-1}$$

$$= \left[k_n \left(\frac{\partial}{\partial v_{DS}} \right) (v_{OV} v_{DS}) - 1/2 \frac{\partial}{\partial v_{DS}} (v_{DS}^2) \right]^{-1}$$

$$= \left[k_n \left(V_{OV} - \frac{1}{2} \cdot 2 v_{DS} \right) \right]^{-1}$$

$$= \frac{1}{k_n (V_{OV} - v_{DS})}$$

If $V_{DS} = 0 \Rightarrow r_{ds} = \frac{1}{k_n V_{OV}}$

If $V_{DS} = 0.2 V_{OV} \Rightarrow r_{ds} = \frac{1.25}{V_{OV}}$

If $V_{DS} = 0.5 V_{OV} \Rightarrow r_{ds} = \frac{1}{k_n (V_{OV} - 0.5 V_{OV})}$

$$= 1 / k_n (0.5 V_{OV}) = \frac{2}{k_n V_{OV}}$$

If $V_{DS} = 0.8 V_{OV} \Rightarrow r_{ds} = \frac{1}{k_n (V_{OV} - 0.8 V_{OV})}$

$$= 1 / k_n (0.2 V_{OV}) = \frac{5}{k_n V_{OV}}$$

If $V_{DS} = V_{OV}$,

$$r_{ds} = \frac{1}{0} \Rightarrow \infty$$

5.11 $V_{tp} = -0.7 \text{ V}$

(a) $|V_{SG}| = |V_{tp}| + |V_{OV}|$

$$= 0.7 + 0.4 = 1.1 \text{ V}$$

$$\Rightarrow V_G = -1.1 \text{ V}$$

(b) For the p -channel transistor to operate in saturation, the drain voltage must not exceed the gate voltage by more than $|V_{tp}|$. Thus

$$v_{D\max} = -1.1 + 0.7 = -0.4 \text{ V}$$

Put differently, V_{SD} must be at least equal to $|V_{OV}|$, which in this case is 0.4 V. Thus $v_{D\max} = -0.4 \text{ V}$.

(c) In (b), the transistor is operating in saturation, thus

$$I_D = \frac{1}{2} k_p |V_{OV}|^2$$

$$0.5 = \frac{1}{2} \times k_p \times 0.4^2$$

$$\Rightarrow k_p = 6.25 \text{ mA/V}^2$$

For $V_D = -20 \text{ mV}$, the transistor will be operating in the triode region. Thus

$$\begin{aligned} I_D &= k_p \left[v_{SD} |V_{OV}| - \frac{1}{2} v_{SD}^2 \right] \\ &= 6.25 \left[0.02 \times 0.4 - \frac{1}{2} (0.02)^2 \right] \\ &= 0.05 \text{ mA} \end{aligned}$$

For $V_D = -2 \text{ V}$, the transistor will be operating in saturation, thus

$$I_D = \frac{1}{2} k_p |V_{OV}|^2 = \frac{1}{2} \times 6.25 \times 0.4^2 = 0.5 \text{ mA}$$

5.18 $V_{tn} = 0.5 \text{ V}$, $k_n = 1.6 \text{ mA/V}^2$

$$I_D = 0.05 = \frac{1}{2} \times 1.6 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.25 \text{ V and } V_{DS} \geq 0.25 \text{ V}$$

$$V_{GS} = 0.5 + 0.25 = 0.75 \text{ V}$$

$$I_D = 0.2 = \frac{1}{2} \times 1.6 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.5 \text{ V and } V_{DS} \geq 0.5 \text{ V}$$

$$V_{GS} = 0.5 + 0.5 = 1 \text{ V}$$