

## Homework #8 Solutions

7.25, 7.29, 7.31, 7.33 (a) (b), and

$$7.25 \text{ (a)} I_D = \frac{1}{2} k_n (V_{GS} - V_t^2)$$

$$= \frac{1}{2} \times 5(0.6 - 0.4)^2 = 0.1 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D = 1.8 - 0.1 \times 10 = 0.8 \text{ V}$$

$$\text{(b)} g_m = k_n V_{OV} = 5 \times 0.2 = 1 \text{ mA/V}$$

$$\text{(c)} A_v = -g_m R_D = -1 \times 10 = -10 \text{ V/V}$$

$$\text{(d)} \lambda = 0.1 \text{ V}^{-1}, \quad V_A = \frac{1}{\lambda} = 10 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = \frac{10}{0.1} = 100 \text{ k}\Omega$$

$$A_v = -g_m (R_D \parallel r_o)$$

$$= -1(10 \parallel 100) = -9.1 \text{ V/V}$$

$$7.29 \text{ Given } \mu_n C_{ox} = 250 \mu\text{A/V}^2,$$

$$V_t = 0.5 \text{ V},$$

$$L = 0.5 \mu\text{m}$$

$$\text{For } g_m = 2 \text{ mA/V}^2 \text{ and } I_D = 0.25 \text{ mA},$$


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \Rightarrow \frac{W}{L} = 32$$

$$\therefore W = 16 \mu\text{m}$$

$$V_{OV} = \frac{2I_D}{g_m} = 0.25 \text{ V}$$

$$\therefore V_{GS} = V_{OV} + V_t = 0.75 \text{ V}$$

7.31

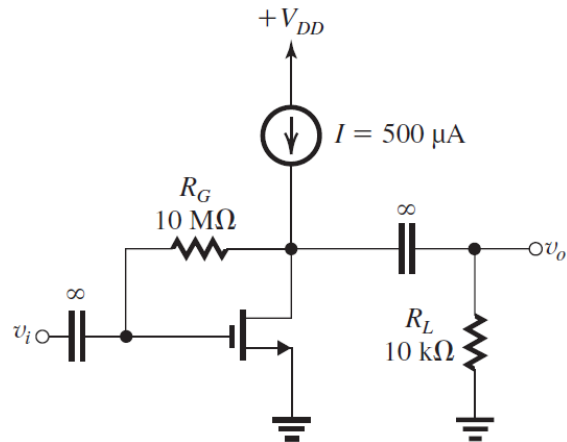

$$V_t = 0.5 \text{ V}$$

$$V_A = 50 \text{ V}$$

$$\text{Given } V_{DS} = V_{GS} = 1 \text{ V. Also, } I_D = 0.5 \text{ mA.}$$

$$V_{OV} = 0.5 \text{ V}, \quad g_m = \frac{2I_D}{V_{OV}} = 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = 100 \text{ k}\Omega$$

$$\frac{v_o}{v_i} = -g_m (R_G \parallel R_L \parallel r_o) = -18.2 \text{ V/V}$$

$$\text{For } I_D = 1 \text{ mA:}$$

$$V_{OV} \text{ increases by } \sqrt{\frac{1}{0.5}} = \sqrt{2} \text{ to}$$

$$\sqrt{2} \times 0.5 = 0.707 \text{ V.}$$

$$V_{GS} = V_{DS} = 1.207 \text{ V}$$

$$g_m = 2.83 \text{ mA/V}, \quad r_o = 50 \text{ k}\Omega \text{ and}$$

$$\frac{v_o}{v_i} = -23.6 \text{ V/V}$$

7.33 (a) Open-circuit the capacitors to obtain the bias circuit shown in Fig. 1, which indicates the given values.

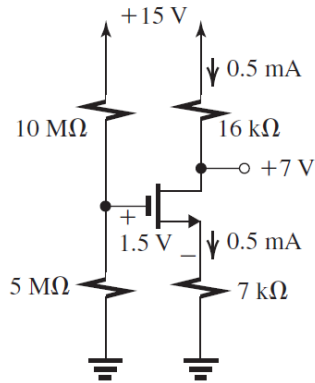


Figure 1

From the voltage divider, we have

$$V_G = 15 \frac{5}{10 + 5} = 5 \text{ V}$$

From the circuit, we obtain

$$\begin{aligned} V_G &= V_{GS} + 0.5 \times 7 \\ &= 1.5 + 3.5 = 5 \text{ V} \end{aligned}$$

which is consistent with the value provided by the voltage divider.

Since the drain voltage (+7 V) is higher than the gate voltage (+5 V), the transistor is operating in saturation.

From the circuit

$$V_D = V_{DD} - I_D R_D = 15 - 0.5 \times 16 = +7 \text{ V, as assumed}$$

Finally,

$$V_{GS} = 1.5 \text{ V, thus } V_{OV} = 1.5 - V_t = 1.5 - 1 = 0.5 \text{ V}$$

$$I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} \times 4 \times 0.5^2 = 0.5 \text{ mA}$$

which is equal to the given value. Thus the bias calculations are all consistent.

$$(b) g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.5}{0.5} = 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{100}{0.5} = 200 \text{ k}\Omega$$

(c) See Fig. 2 below.

$$(d) R_{in} = 10 \text{ M}\Omega \parallel 5 \text{ M}\Omega = 3.33 \text{ M}\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{3.33}{3.33 + 0.2}$$

$$= 0.94 \text{ V/V}$$

$$\frac{v_o}{v_{gs}} = -g_m (200 \parallel 16 \parallel 16)$$


$$= -2 \times 7.69 = -15.38 \text{ V/V}$$

$$\frac{v_o}{v_{sig}} = \frac{v_{gs}}{v_{sig}} \times \frac{v_o}{v_{gs}} = -0.94 \times 15.38$$

$$= -14.5 \text{ V/V}$$

Handout problem 1:

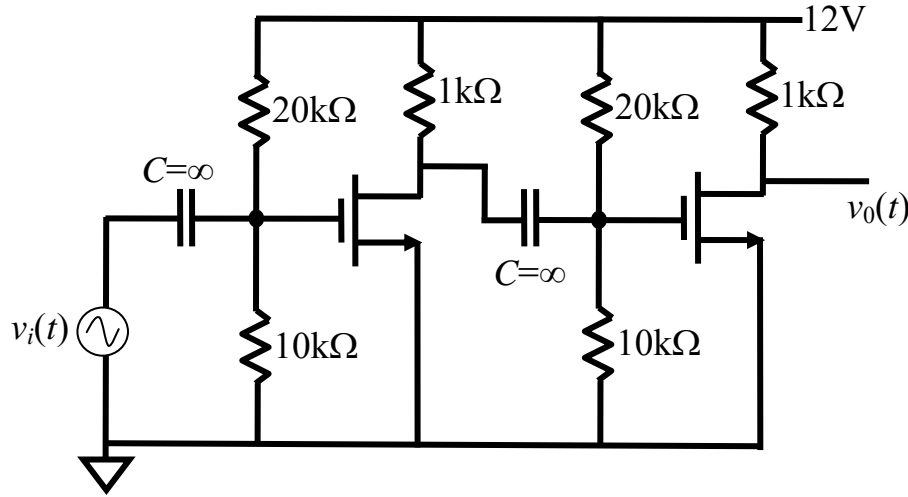In the following MOSFET amplifier circuit, two transistors are identical with  $V_t = 2V$  and  $k_n = 2mA/V^2$ . Please find the small-signal voltage gain  $v_0(t)/v_i(t) = ?$



Solution:

This is an amplifier with 2 identical stages.

(a) DC analysis:

$$V_G = V_{GS} = 12 \times \frac{10}{30} = 4V$$


$$\text{Then } I_D = \frac{k_n}{2} (V_{GS} - V_t)^2 = (4 - 2)^2 = 4mA, \quad V_{DS} = 12 - 1 \times 4 = 8V$$

$V_{DS} > V_{GS} - V_t = 4 - 2 = 2V$ , and therefore the MOSFET is operating in saturation

Small-signal trans-conductive gain of each stage is,  $g_m = k_n (V_{GS} - V_t) = 2 \times 2 = 4mA/V$

(b) small-signal analysis

The small-signal equivalent circuit is,

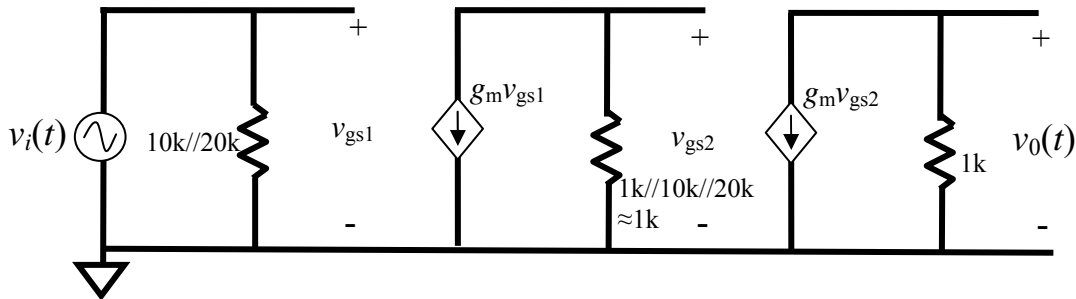

$$v_{gs1} = v_i, \quad v_{gs2} = -1 \times g_m v_{gs1} = -g_m v_i, \quad \text{and } v_0 = -1 \times g_m v_{gs2} = g_m^2 v_i$$

Therefore, the small-signal voltage gain is

$$\frac{v_0}{v_i} = g_m^2 = 16$$

Handout problem 2:

In the following MOSFET amplifier circuit, please find the small-signal voltage gain  $v_0(t)/v_i(t) = ?$

Solution:

(a) DC analysis:

$$V_G = 15 \times \frac{5}{15} = 5V$$

Assume saturation,

$$I_D = \frac{k_n}{2} (V_{GS} - V_t)^2,$$

$$V_{GS} = 5 - 0.1I_D.$$

Combine these two equations,

$$V_{GS} = 5 - 0.1 \frac{k_n}{2} (V_{GS} - V_t)^2,$$

$$\text{that is, } V_{GS} = 5 - 0.1(V_{GS} - 2)^2$$


$$V_{GS}^2 + 6V_{GS} - 46 = 0$$

The solution is,  $V_{GS} = 4.42$

$$\text{Then } I_D = 1 \times (4.42 - 2)^2 = 5.86 \text{ mA}, \quad V_{DS} = 15 - 1 \times 5.86 - 0.1 \times 5.86 = 8.55 \text{ V}$$


$V_{DS} > V_{GS} - V_t = 4.42 - 2 = 2.42$  and therefore the MOSFET is operating in saturation

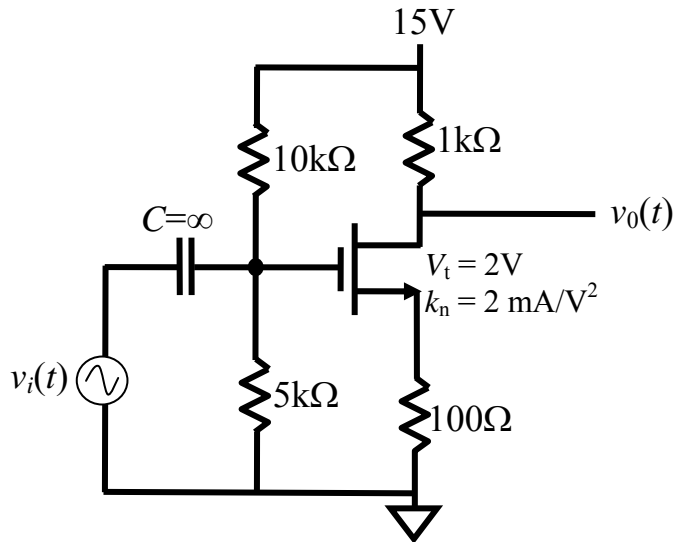Small-signal trans-conductive gain is,  $g_m = k_n (V_{GS} - V_t) = 2 \times 2.42 = 4.84 \text{ mA/V}$



(b) small-signal analysis

The small-signal equivalent circuit is,

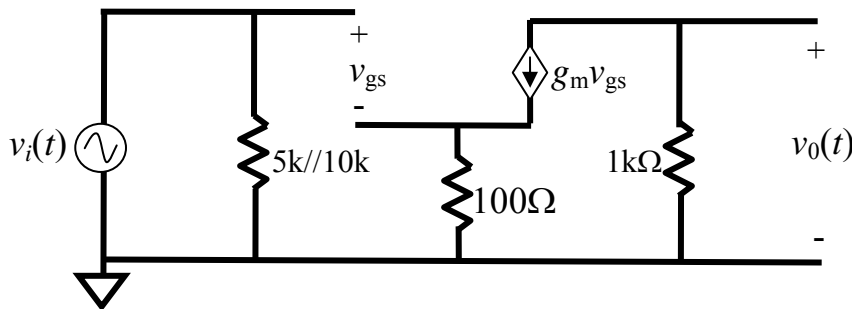

$$v_{gs} = v_i - 0.1 \cdot g_m \cdot v_{gs}, \quad \text{that is, } v_{gs} = \frac{v_i}{1 + 0.1g_m}$$

$$v_0 = -1 \cdot g_m v_{gs} = \frac{-g_m v_i}{1 + 0.1g_m}$$

Therefore, the small-signal voltage gain is

$$\frac{v_0}{v_i} = \frac{-g_m}{1 + 0.1g_m} = -\frac{4.84}{1 + 0.484} = -3.26$$