

EECS 312 - Electronics Circuits I (Spring 2018)

Material for Exam II: Chapter 5 (MOSFET) + section 7.2.1 (small-signal analysis of MOSFET circuits as amplifiers)

Structure and operation principle of an FET:

Basic structure: source, drain, gate and body

Gate is electrically isolated from the body by the oxide layer, and thus the gate current is always zero.

The “channel” between source and drain is controlled by the voltage between gate and source

Understand mechanisms of channel *pinch-off*, *channel length modulation* and their impacts.

I-V characteristics of an enhancement NMOS

Three different operation modes: cutoff, saturation and triode

(1) Bias condition for each mode: Relations among V_{GS} , V_{DS} , and V_t

(2) Expression of current for each operation mode

$$\text{In triode region: } I_D = k \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right] = k' \left(\frac{W}{L} \right) \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$\text{In Saturation region: } I_D = \frac{1}{2}k(V_{GS} - V_t)^2 = k' \left(\frac{W}{2L} \right) (V_{GS} - V_t)^2$$

$$\text{Where: } k = k' \left(\frac{W}{L} \right) = \mu C_{ox} \left(\frac{W}{L} \right)$$

Special characteristics of I - V relationship

In triode region, if $V_{DS} \ll (V_{GS} - V_t)$, I_D linearly increases with V_{DS} : equivalently this is a voltage-controlled resistor

In saturation region, ideally I_D is independent of V_{DS} (if channel-length modulation is not considered). If the effect of channel-length modulation is considered, I_D slightly increases with the increase of V_{DS} even in saturation region, resulting in a drain output resistance, so that $I_D = 0.5k(V_{GS} - V_t)^2(1 + V_{DS}/V_A)$.

Four types of MOSFETs:

Enhancement NMOS

Enhancement PMOS

Depletion NMOS

Depletion PMOS

n -type or p -type doping for the body, source and drain regions, how these devices operate.

Familiar with conditions of operating modes (cutoff, triode and saturation), and I_D equations for each of mode (*know similarities and differences between these 4 types of devices*)

MOSFET circuit at DC

Steps of circuit analysis: Assume operation mode, enforce conditions according to the assumed operation mode, analyze circuit and check the assumption. ***Exercise is necessary and very important***

Application: MOSFET as an amplifier

Transfer function of a MOSFET circuit (Output as the function of the input)

Small-signal response: small-signal AC voltage gain $A_v = v_o(t)/v_i(t)$ of the circuit, and transconductive gain $g_m = i_d/v_{gs}$ of the MOSFET. Both of these are related to DC operation condition of the MOSFET, commonly referred to as the operating Q point.

FET small-signal equivalent circuit: for an ideal MOSFET it is a voltage controlled current source. But if channel-length modulation is consider it has an extra output resistance r_o .

Solve circuit problems. Pay special attention to the construction of DC and AC equivalent circuits.

Body Effect: understand its physical mechanism, circuit model, and impact in circuit design