

# 10.4 NMOS Logic Design

**Reading Assignment:** 974-980

An alternative to CMOS logic is **NMOS logic**.

**Q:**

**A:** HO: NMOS Logic Circuits

HO: The Depletion Load


HO: The Pseudo-NMOS Load

# The Pseudo-NMOS Load

There is another type of active load that is used for NMOS logic, but this load is made from a **PMOS** transistor!

Hence, NMOS logic that uses this load is referred to as **Pseudo NMOS Logic**, since not all of the devices in the circuit will be NMOS (the load will be **PMOS**!).

 We therefore call this load the "**Pseudo NMOS Load**", since it is the load used in **Pseudo NMOS logic**. But, keep in mind that the **pseudo NMOS load** is made from a **PMOS** device (this can cause great confusion!).



$$\begin{aligned}
 i_D &= i \\
 V_{GS} &= 0 - V_{DD} = -V_{DD} \\
 V_{DS} &= -V \\
 V_{GS} - V_t &= -(V_{DD} + V_t)
 \end{aligned}$$

*The Pseudo-NMOS Load*

Note that  $v_{GS} = -V_{DD} < V_t$ , so that the load is **not** in cutoff—it can either be in **saturation** or **triode**.

The PMOS will be in **triode** if:

$$\begin{aligned}v_{DS} &> v_{GS} - V_t \\ -v &> -(V_{DD} + V_t) \\ v &< (V_{DD} + V_t)\end{aligned}$$

In which case the **current** is:

$$\begin{aligned}i_D &= K \left[ 2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right] \\ i &= K \left[ -2(V_{DD} + V_t)(-v) - (-v)^2 \right] \\ i &= K \left[ 2(V_{DD} + V_t)v - v^2 \right]\end{aligned}$$

Likewise, the PMOS will be in **saturation** if:

$$\begin{aligned}v_{DS} &< v_{GS} - V_t \\ -v &< -(V_{DD} + V_t) \\ v &> (V_{DD} + V_t)\end{aligned}$$



In which case the **current** is:


$$\begin{aligned}i_D &= K (v_{GS} - V_t)^2 - \frac{v_{DS}}{r_o} \\ i &= K (V_{DD} + V_t)^2 + \frac{v}{r_o}\end{aligned}$$

where in this case:

$$r_o = \frac{1}{\lambda K (v_{GS} - V_t)^2} = \frac{1}{\lambda K (V_{DD} + V_t)^2}$$

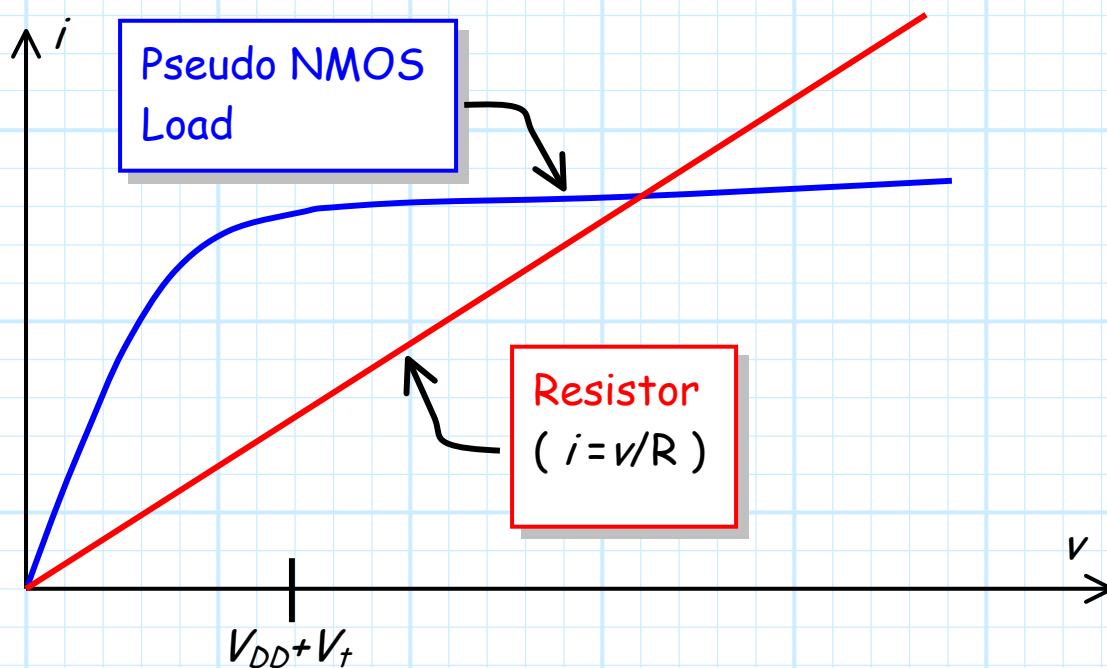 Combining these two results, we find that the pseudo NMOS load behaves very much like the depletion load:



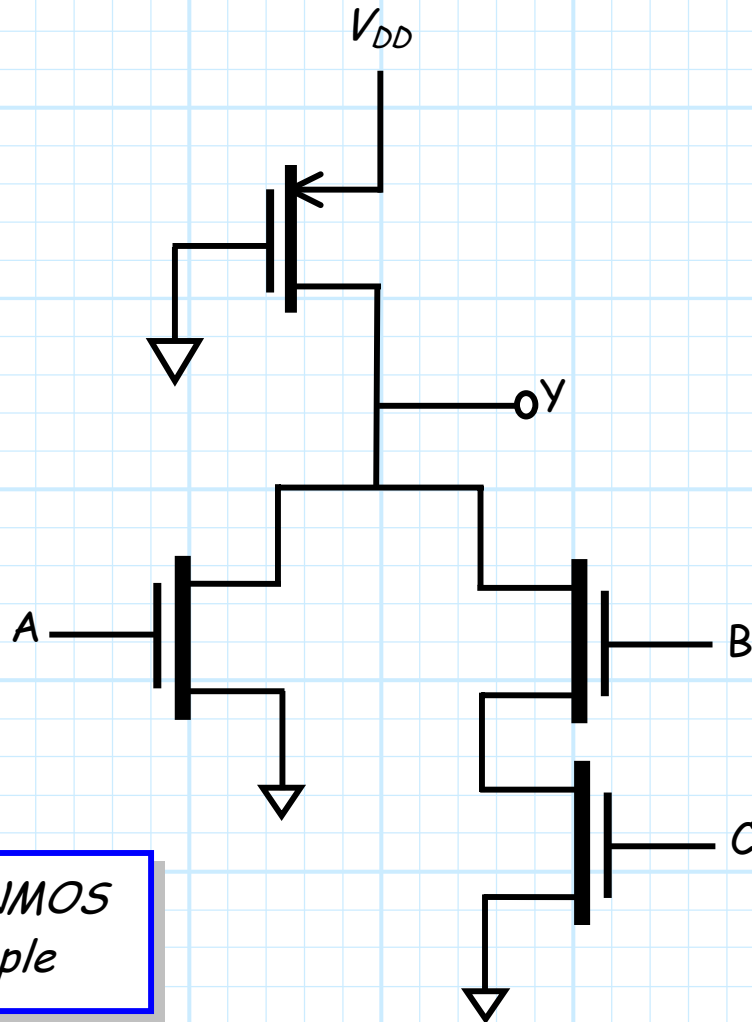


*A Pseudo-NMOS  
Logic Example*
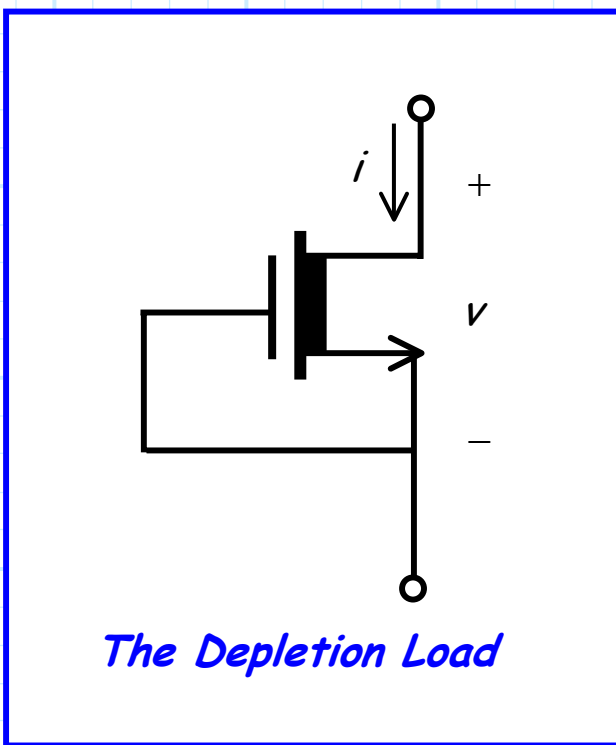
# The Depletion Load

Say we connect the gate of a **depletion** NMOS to its source—we now have a **two-terminal device**!

This device is called a **depletion load**.



Since the depletion load is a two-terminal device, its **behavior** is defined by the relationship between the **voltage**  $v$  across the device and the **current**  $i$  through it.


For example, a **resistor** is a two terminal device whose behavior (i.e., its relationship between  $i$  and  $v$ ) is defined by **Ohm's Law** ( $i = v/R$ ).

Although the **depletion load** is decidedly **not** a resistor, its  $i-v$  relationship does have **some** similarities with Ohm's Law.

**Q:** So what is "Ohm's Law" for a **depletion load** (i.e., what is  $i = f(v)$ )?

**A:** A result easily found by implementing our knowledge of depletion MOSFETs!

For a depletion load, we find that:

 

**Q:** But since  $v_{GS} = 0$ , isn't the NMOS device in **cutoff**?

**A:** **Nope!** Notice that this is a depletion MOSFET, and a depletion MOSFET **will** conduct when  $v_{GS} = 0$ !

Thus the MOSFET in a depletion load will always be either in:  
**a)** triode or **b)** saturation.

**a)** Depletion load MOSFET is in **triode** if:

$$\begin{aligned}
 v_{DS} &< v_{GS} - V_t \\
 v &< 0 - V_t \\
 v &< -V_t
 \end{aligned}$$

Therefore, the **current** will be:

$$i_D = K [2(v_{GS} - V_t)v_{DS} - v_{DS}^2]$$

$$i = K [2(0 - V_t)v - v^2]$$

$$i = K [-2V_t v - v^2]$$

**b)** Depletion load MOSFET is in **saturation** if:

$$v_{DS} > v_{GS} - V_t$$

$$v > 0 - V_t$$

$$v > -V_t$$


Therefore, the **current** will be:

$$i_D = K (v_{GS} - V_t)^2 + \frac{v_{DS}}{r_o}$$

$$i = K (0 - V_t)^2 + \frac{v}{r_o}$$

$$i = K (-V_t)^2 + \frac{v}{r_o}$$

$$i = K V_t^2 + \frac{v}{r_o}$$

 


where in this case:

$$r_o = \frac{1}{\lambda K (v_{GS} - V_t)^2} = \frac{1}{\lambda K (0 - V_t)^2} = \frac{1}{\lambda V_t^2}$$




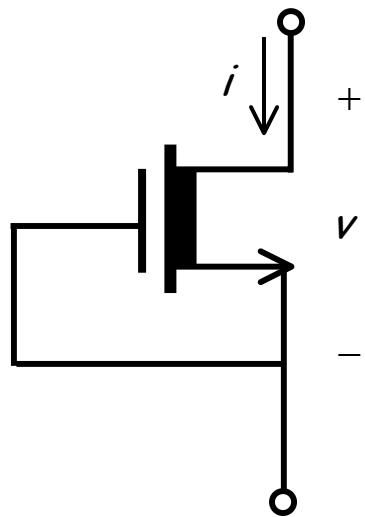Combining the two results, we find that "Ohm's Law" for a depletion load is:



$$i = \begin{cases} K[-2V_t v - v^2] & \text{if } 0 < v < -V_t \\ KV_t^2 + \frac{v}{r_o} & \text{if } v > -V_t \end{cases}$$

 
Plotting this function, we find something like this:



Note that the behavior of a Depletion Load and a resistor are **very different**—however they are precisely the **same** in two key ways:

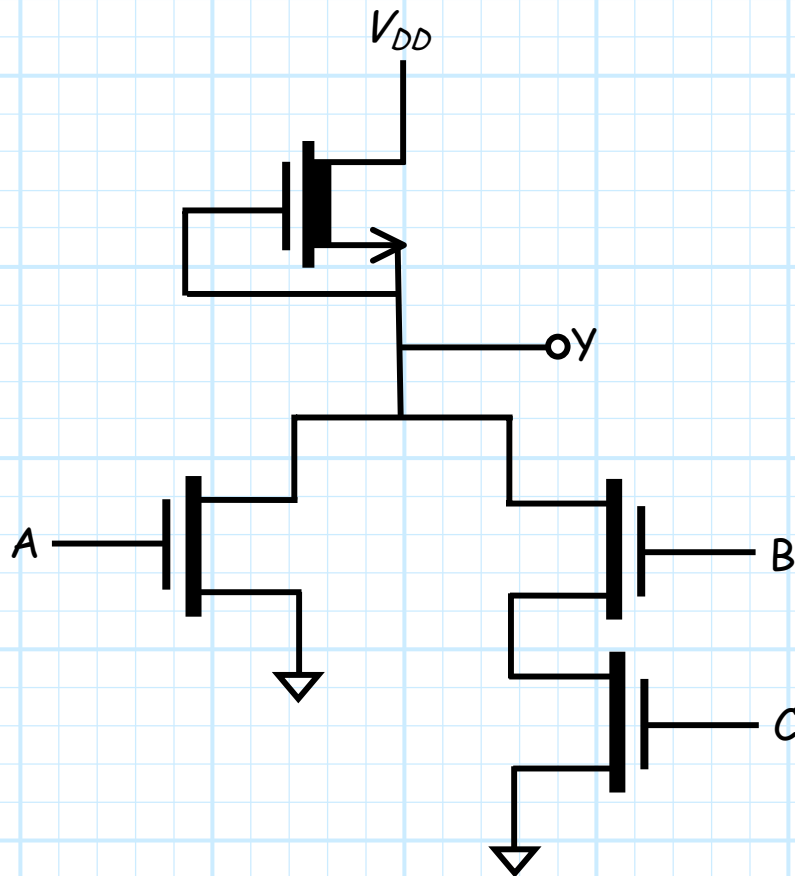
1. When the voltage across each device (i.e., resistor and depletion load) is **zero**, the current through each device is likewise **zero** (and vice versa!).
2. As the voltage across each device **increases**, the current through each device **increases**.

As a result, we can use a depletion load as the “**pull-up resistor**” in our integrated circuit NMOS logic!


 
# NMOS Logic Circuits

An alternative way to construct a digital logic gate is to simply use a single **large resistor** as the pull-up network!



If the PDN is **open**, no current will flow ( $i_R = 0$ ), and thus there will be **no** voltage drop across the **Pull-Up Resistor  $R$** —the output will be **high**, **just** like before!

**But**, if the PDN is conducting, current **will** flow ( $i_R \neq 0$ ), and thus there **will** be a large voltage drop across  $R$ —the output will be **low** (sort of)!

This method of constructing digital devices is called **NMOS logic** (for hopefully **obvious** reasons!).

**Q:** *Why would we want use NMOS logic?*

**A:** Replacing the PUN with a single resistor greatly **simplifies** and **shrinks** the circuit. For complex gates (i.e., gates with **many** inputs), we can reduce the number of required devices (transistors and resistors) by **nearly half!**

**Q:** *Yikes! This seems to be a lot better. Why wouldn't we always use NMOS logic?*

**A:** There are **two** really big problems with NMOS logic (at least, when compared to **CMOS**):

1. Since current flows when the output is low, the static power dissipation is **not zero**.
2. Since current flows when the output is low,  $V_{OL}$  is **not** equal to its ideal value of **zero** (i.e.,  $V_{OL} \neq 0$ )!

Additionally, there is **one more** problem when implementing NMOS in **integrated circuits**. IC resistors are (relatively) very large and difficult to construct.

→ This problem, though, is easily solved—we replace the **pull-up resistor** with an **active load**.