

### Special Problem 5.4-6

Assume both transistors are in **saturation**.

1. Using these assumptions, determine for each transistor the base, collector and emitter **voltages**, and also the base, collector and emitter **currents**.

2. Determine if **each** assumption was correct.

