

Drain Output Resistance

I fibbed!

I have been saying that for a MOSFET in **saturation**, the drain current is **independent** of the drain-to-source voltage v_{DS} . *I.E.:*

$$i_D = K (v_{GS} - V_t)^2$$

In reality, this is only **approximately** true!

Due to a phenomenon known as **channel-length modulation**, we find that drain current i_D is **slightly dependent** on v_{DS} . We find that a **more accurate** expression for drain current for a MOSFET in **saturation** is:

$$i_D = K (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

Where the value λ is a MOSFET **device parameter** with units of $1/V$ (i.e., V^{-1}). Typically, this value is small (thus the dependence on v_{DS} is slight), ranging from 0.005 to 0.02 V^{-1} .

Often, the channel-length modulation parameter λ is expressed as the **Early Voltage** V_A , which is simply the inverse value of λ :

$$V_A = \frac{1}{\lambda} \quad [\text{V}]$$

Thus, the drain current for a MOSFET in **saturation** can **likewise** be expressed as:

$$i_D = K (v_{GS} - V_t)^2 \left(1 + \frac{v_{DS}}{V_A} \right)$$

Now, let's **define** a value I_D , which is simply the drain current in saturation **if** no channel-length modulation actually occurred—in other words, the **ideal** value of the drain current:

$$I_D \doteq K (v_{GS} - V_t)^2$$

Thus, we can **alternatively** write the drain current in saturation as:

$$i_D = I_D \left(1 + \frac{v_{DS}}{V_A} \right)$$

This **explicitly** shows how the drain current behaves as a function of voltage v_{DS} . For example, consider a **typical** case case where $v_{DS} = 5.0 \text{ V}$ and $V_A = 50.0 \text{ V}$. We find that:

$$\begin{aligned}
 i_D &= I_D \left(1 + \frac{v_{DS}}{V_A} \right) \\
 &= I_D \left(1 + \frac{5.0}{50.0} \right) \\
 &= I_D (1 + 0.1) \\
 &= 1.1 I_D
 \end{aligned}$$

In other words, the drain current is **10% larger** than its "ideal" value I_D .

We can thus interpret the value v_{DS}/V_A as the **percent increase** in drain current i_D over its ideal (i.e., no channel-length modulation) saturation value $I_D = K(v_{GS} - V_t)^2$.

Thus, as v_{DS} increases, the drain current i_D will **increase slightly**.


Now, let's introduce a **third** way (i.e. in addition to λ, V_A) to describe the "extra" current created by channel-length modulation. Define the **Drain Output Resistance** r_o :

$$r_o \doteq \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$

Using this definition, we can write the **saturation** drain current expression as:

$$\begin{aligned}
 i_D &= I_D \left(1 + \frac{v_{DS}}{V_A} \right) \\
 &= I_D + \frac{I_D}{V_A} v_{DS} \\
 &= I_D + \frac{v_{DS}}{r_o} \\
 &= K (v_{GS} - V_t)^2 + \frac{v_{DS}}{r_o}
 \end{aligned}$$

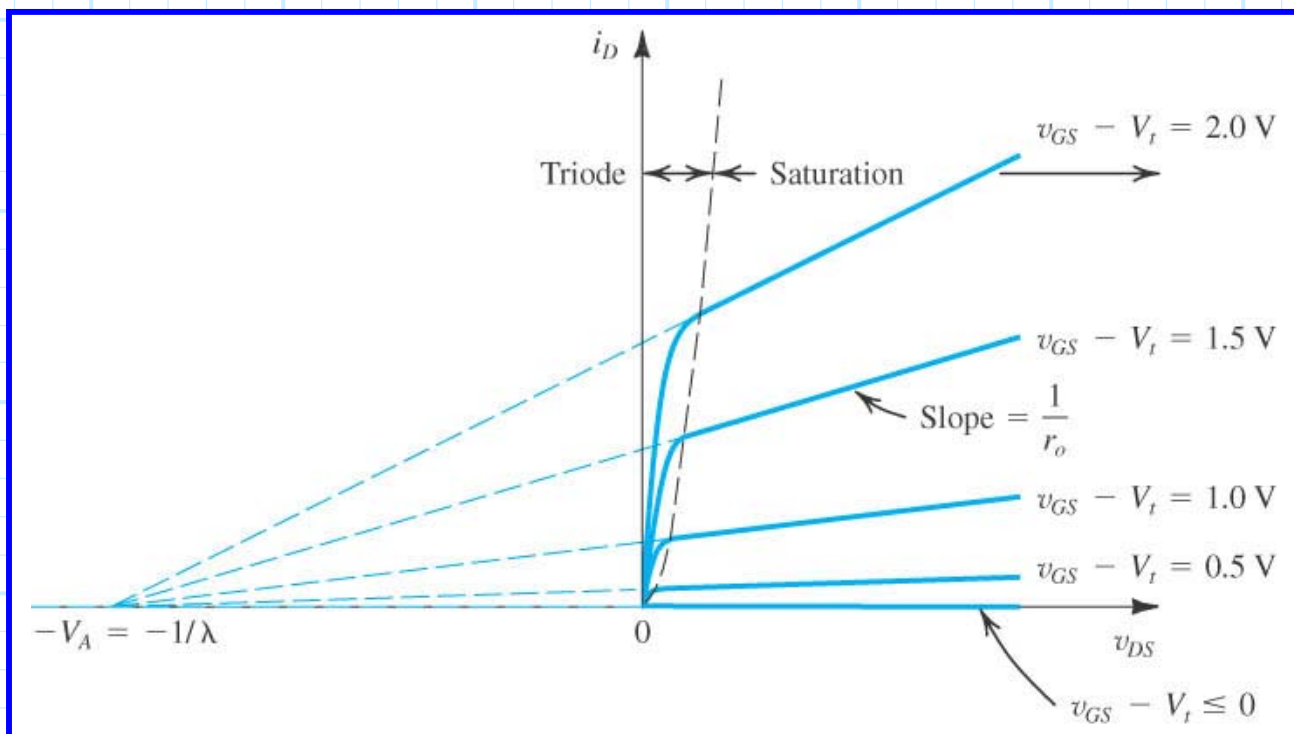Thus, we **interpret** the "extra" drain current (due to channel-length modulation) as the current flowing through a **drain output resistor** r_o .



Finally, there are **three** important things to remember about channel-length modulation:

- * The values λ and V_A are MOSFET device parameters, but drain output resistance r_o is **not** (r_o is dependent on I_D !).
- * Often, we "neglect the effect of channel-length modulation", meaning that we use the **ideal** case for saturation-- $i_D = K(V_{GS} - V_t)^2$. Effectively, we assume that $\lambda = 0$, meaning that $V_A = \infty$ and $r_o = \infty$ (i.e., **not** $V_A = 0$ and $r_o = 0$!).
- * The drain output resistance r_o is **not** the same as channel resistance r_{DS} ! The two are different in **many, many** ways:

$$i_D = K(V_{GS} - V_t)^2 + \frac{V_{DS}}{r_o} \quad \text{for a MOSFET in saturation}$$

$$i_D = \frac{V_{DS}}{r_{DS}} \quad \text{for a MOSFET in triode and } v_{DS} \text{ small}$$

$$\therefore r_o \neq r_{DS} \quad \text{!!!!!!!}$$