

# Example: Constructing a PWL Model

For a certain junction diode, we **know** that:

$$i_D = 10 \text{ mA} \quad \text{when} \quad v_D = 0.7 \text{ V}$$

and

$$i_D = 1 \text{ mA} \quad \text{when} \quad v_D = 0.6 \text{ V}$$

Say we wish to **construct a PWL model** that will approximate this junction diode behavior for diode currents from, say, approximately 1 mA to approximately 10 mA.

Recall that the resulting model will relate diode voltage  $V_D$  to diode current  $i_D$  as a **line** of the form:

$$i_D = \left( \frac{1}{r_d} \right) v_D - \left( \frac{V_{D0}}{r_d} \right)$$

We therefore need to determine the values of  $V_{D0}$  and  $r_d$  such that this PWL model "line" will **intersect** the two points  $i_{D1} = 1.0$ ,  $v_{D1} = 0.6$  and  $i_{D2} = 10.0$ ,  $v_{D2} = 0.7$ .

The **slope** of this line must therefore be:

$$m = \frac{i_{D2} - i_{D1}}{V_{D2} - V_{D1}} =$$

Thus our PWL model **resistor value**  $r_d$  must be:

$$r_d = \frac{1}{m} =$$

Or in other words,  $r_d = 11.1 \Omega$ .

**Q:** *Wow! That's a **very small** resistance value. Are you **sure** we calculated  $r_d$  correctly?*

**A:** Typically, we find that the resistor value in the PWL model is small. In fact, it is frequently **less than 1  $\Omega$**  when we attempt to match the junction diode curve in a "high" current region (e.g., from  $i_D = 50 \text{ mA}$  to  $i_D = 500 \text{ mA}$ ).

Now that we have determined  $r_d$ , we can insert **either** point into the model **line equation** and solve for  $V_{D0}$ . For example, the equations:

$$i_{D1} = \left( \frac{1}{r_d} \right) V_{D1} - \left( \frac{V_{D0}}{r_d} \right) \quad \text{or} \quad i_{D2} = \left( \frac{1}{r_d} \right) V_{D2} - \left( \frac{V_{D0}}{r_d} \right)$$

become either:

$$\begin{aligned} V_{D0} &= v_{D1} - i_{D1} r_d \\ &= \\ &= \end{aligned}$$


or

$$\begin{aligned} V_{D0} &= v_{D2} - i_{D2} r_d \\ &= \\ &= \end{aligned}$$


In other words, we can use **either** point to determine  $V_{D0}$ .

Our PWL model is therefore:

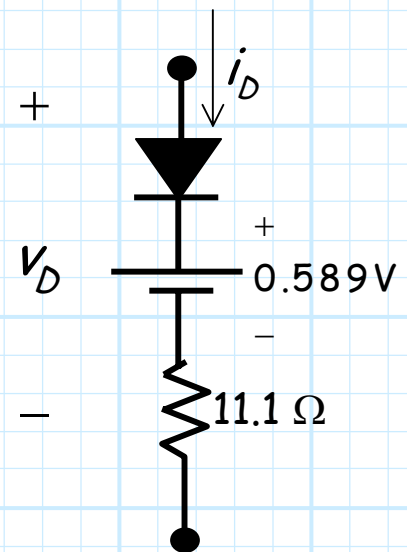
$$i_D = \begin{cases} 0 & \text{for } v_D < 0.589 \text{ V} \\ \frac{v_D}{0.0111} - \frac{0.589}{0.0111} \text{ mA} & \text{for } v_D > 0.589 \text{ V} \end{cases}$$



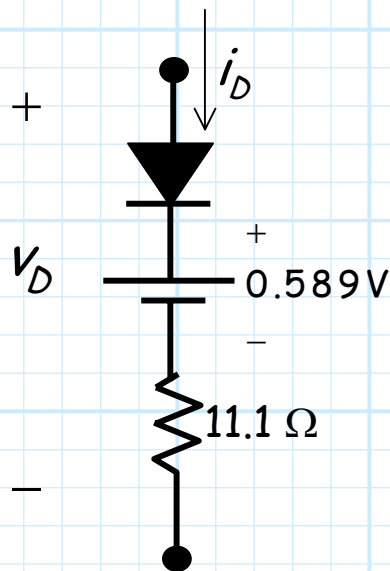Now, **compare** this PWL model to the CVD model:



PWL

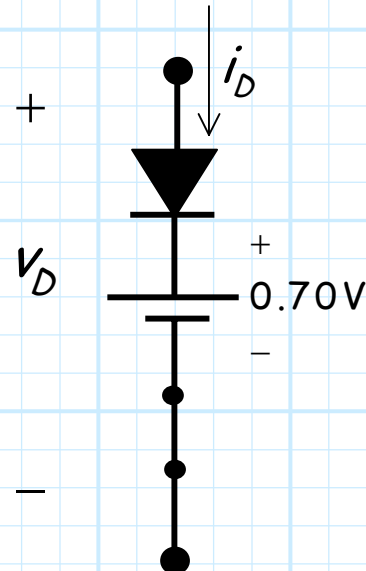

CVD

Note that the CVD model can be viewed as a PWL model with  $V_{D0} = 0.7 \text{ V}$  and  $r_d = 0.0$ . **Compare** those values with our model ( $V_{D0} = 0.589 \text{ V}$  and  $r_d = 11.1 \Omega$ )—**not** much difference!

Thus, the PWL model is **not** a radical departure from the CVD model (typically  $V_{D0}$  is close to  $0.7 \text{ V}$  and  $r_d$  is **very** small). Instead, the PWL can be view as **slight improvement** of the CVD model.