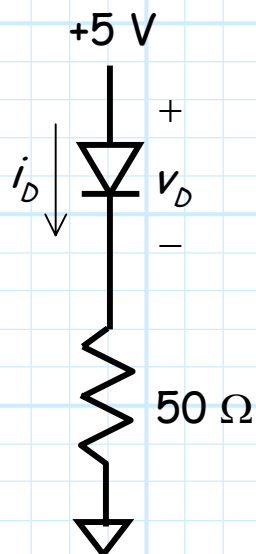


# Example: Junction Diode Models

Consider the **junction** diode circuit, where the junction diode has device parameters  $I_S = 10^{-12}$  A, and  $n = 1$ :




I **numerically** solved the resulting transcendental equation, and determined the **exact** solution:


$$i_D = 87.40 \text{ mA}$$

$$v_D = 0.630 \text{ V}$$

Now, let's determine **approximate** values using diode **models** !

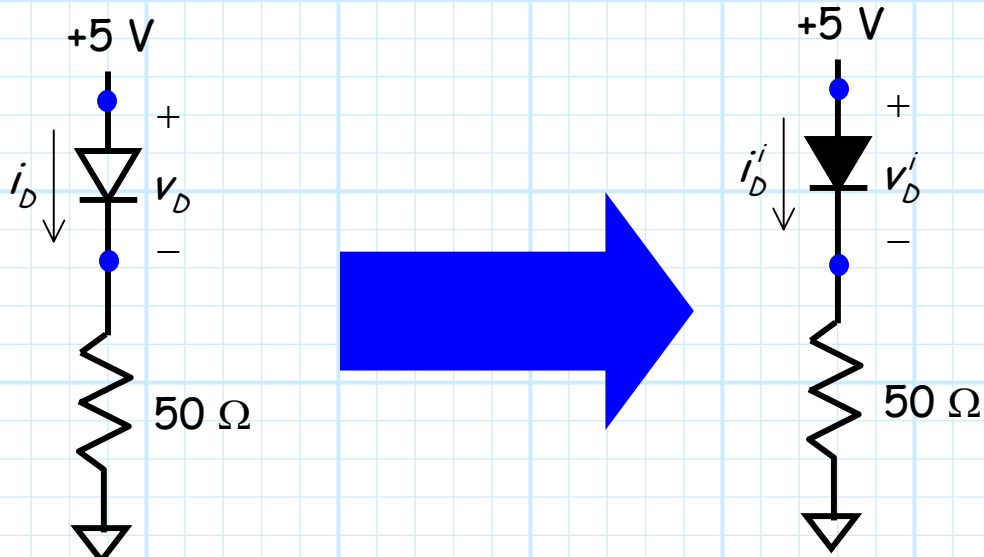First, let's try the **ideal diode model**.



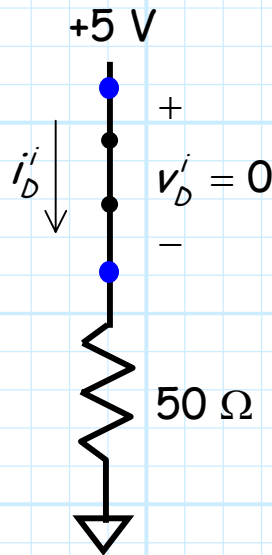

Assume IDEAL diode is "on".

Enforce  $v_D^i = 0$ .

Analyze the IDEAL diode circuit.

From KVL:

$$= 0$$

$$\therefore i_D^i =$$

Check result:

We therefore can **approximate** the **junction diode** current as the current through the ideal diode **model**:

$$i_D \approx i_D^i = 100 \text{ mA}$$





And **approximate** the **junction** diode voltage as the voltage across the ideal diode **model**:

$$v_D \approx v_D^i = 0$$

**Compare** these approximations to the **exact** solutions:

$$i_D = 87.4 \text{ mA} \text{ and } v_D = 0.630 \text{ V}$$

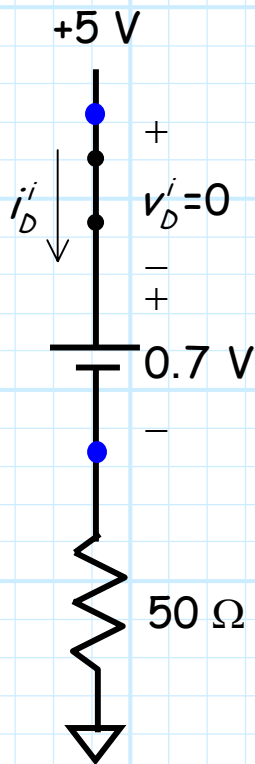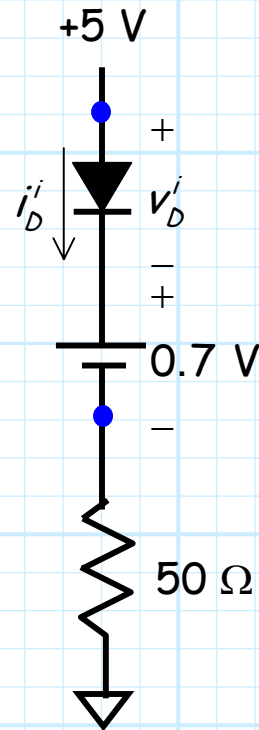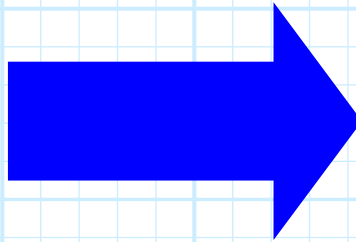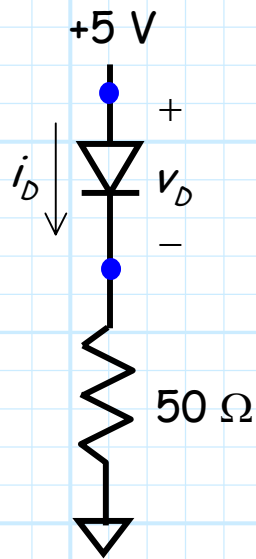Close, but we can do better! Let's use the **CVD** model.



Assume IDEAL diode is "on".

Enforce  $v'_D = 0$ .

Analyze the **IDEAL** diode circuit.  
From KVL:

$$= 0$$

$$\therefore i'_D =$$

Check the result:

We therefore can **approximate** the **junction** diode current as the current through the **CVD model**:

$$i_D \approx i_D^i = 86.0 \text{ mA}$$


And **approximate** the **junction** diode voltage as the voltage across the **CVD model**:

$$\begin{aligned} v_D &\approx v_D^i + 0.7 \\ &= 0.0 + 0.7 \\ &= 0.7 \text{ V} \end{aligned}$$

Compare these approximations to the **exact** solutions:

$$i_D = 87.4 \text{ mA} \quad \text{and} \quad v_D = 0.630 \text{ V}$$

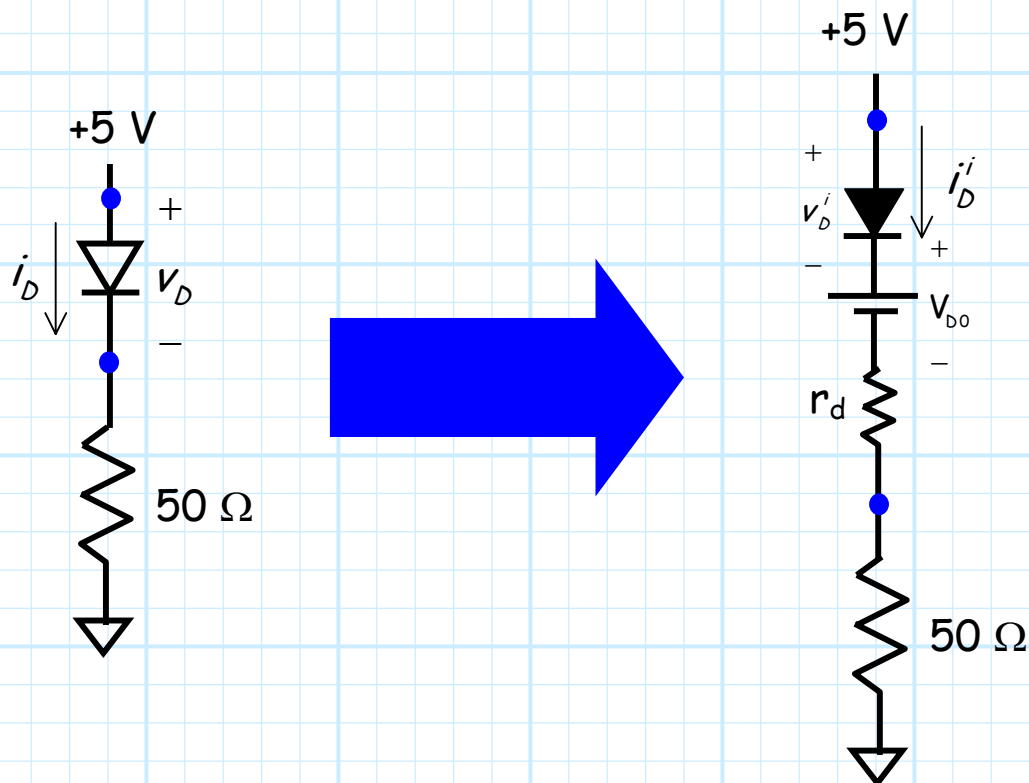**Much better** than before, but we can do even better! Let's use the **PWL model**.



**Q:** But, what *values* should we use for model parameters  $V_{D0}$  and  $r_d$ ??

**A:** From the CVD model, we know that  $i_D$  is approximately 86mA. Therefore, let's create a **PWL model** that is accurate in the region between, say,  $50 \text{ mA} < i_D < 125 \text{ mA}$ .

**First**, we determine  $v_D$  at 50 mA and 125 mA.

$$\begin{aligned} v_D &= nV_T \ln(i_D/I_S) \\ &= \\ &= \end{aligned}$$

We now know two points lying on the junction diode curve! Let's construct a PWL model whose "line" **intersects** these two points.

Recall that when the ideal diode is forward biased, applying KVL to the PWL model results in:

$$v_D = V_{D0} + i_D r_d$$

or equivalently:

$$i_D = \frac{v_D}{r_d} - \frac{V_{D0}}{r_d}$$

Inserting the junction diode values into this PWL model equation provides:


$$0.616 = V_{D0} + (0.05)r_d$$

$$0.639 = V_{D0} + (0.125)r_d$$

Two equations and two unknowns !! Solving, we get:

$$V_{D0} = 0.600 \text{ V and } r_d = 0.31 \Omega \text{ (small !!)}$$

Therefore, the ideal diode circuit is:

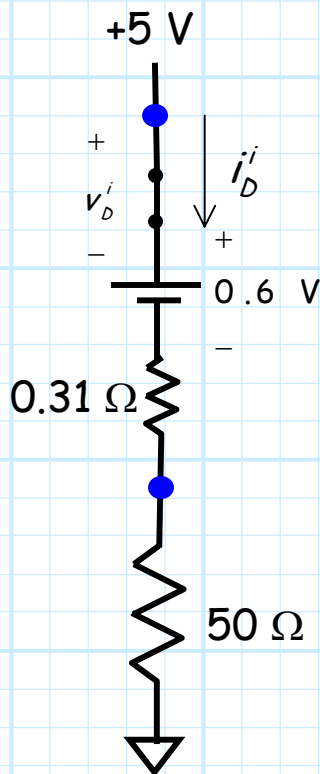

Assume the **IDEAL** diode is "on".

Enforce  $v_D^i = 0$ .

Analyze the **IDEAL** diode circuit.

From KVL:

$$= 0$$

$$\therefore i_D^i =$$

Check the result:

We can therefore **approximate** the **junction** diode current as the current through the PWL model:

$$i_D \approx i_D^i = 87.5 \text{ mA}$$

and **approximate** the **junction** diode voltage as the voltage across the PWL model:

$$\begin{aligned} v_D &= v_D^i + V_{D0} + i_D^i r_D \\ &= 0 + 0.600 + (0.087)0.31 \\ &= 0.627 \text{ V} \end{aligned}$$

Now, compare these values to the **exact** values  $v_D = 0.630 \text{ V}$  and  $i_D = 87.4 \text{ mA}$ .

The **error** of the PWL model estimates is just 0.003 Volts and 0.1 mA !

Each model provides **better** estimates than the previous one!