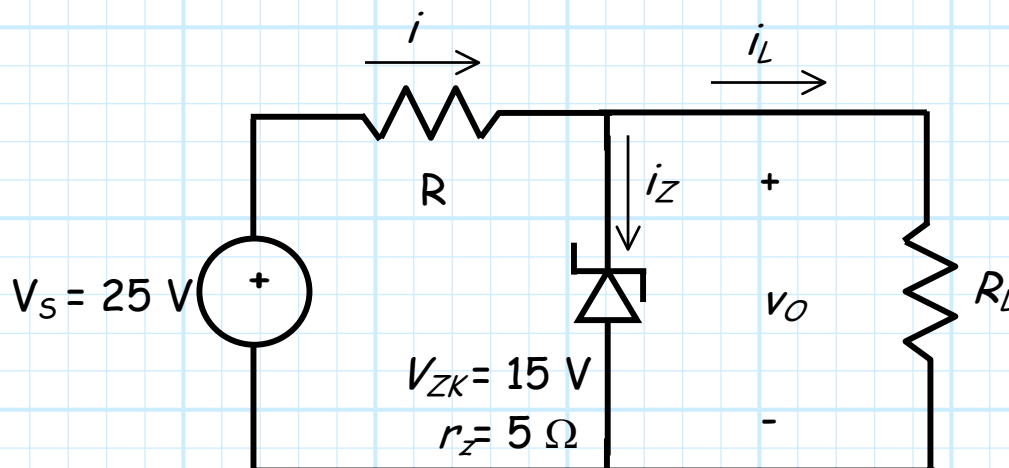


Example: The Shunt Regulator

Consider the shunt regulator, built using a zener diode with $V_{ZK}=15.0$ V and incremental resistance $r_z=5\Omega$:



1. Determine R if the largest possible value of i_L is 20 mA.
2. Using the value of R found in part 1 determine i_Z if $R_L=1.5$ K.
3. Determine the change in v_O if V_S increases one volt.
4. Determine the change in v_O if i_L increases 1 mA.

Part 1:

From KCL we know that $i = i_Z + i_L$.

We also know that for the diode to remain in breakdown, the zener current must be **positive**.


$$\text{i.e., } i_Z = i - i_L > 0$$

Therefore, if i_L can be as large as 20 mA, then i must be greater than 20 mA for i_Z to remain greater than zero.

$$\text{i.e. } i > 20\text{mA}$$

Q: But, what is i ??

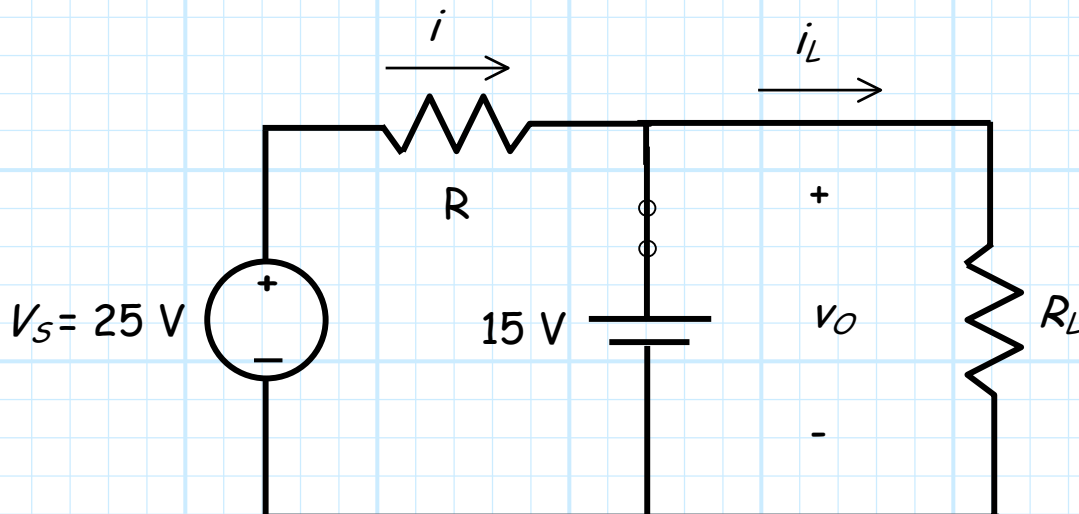A: Use the zener CVD model to analyze the circuit.



Therefore from Ohm's Law:

$$i =$$

and thus $i > 20\text{mA}$ if:


$$R <$$

Note we want R to be as large as possible, as large R improves both **line** and **load** regulation.

Therefore, set $R = 500\ \Omega = 0.5\ \text{K}$

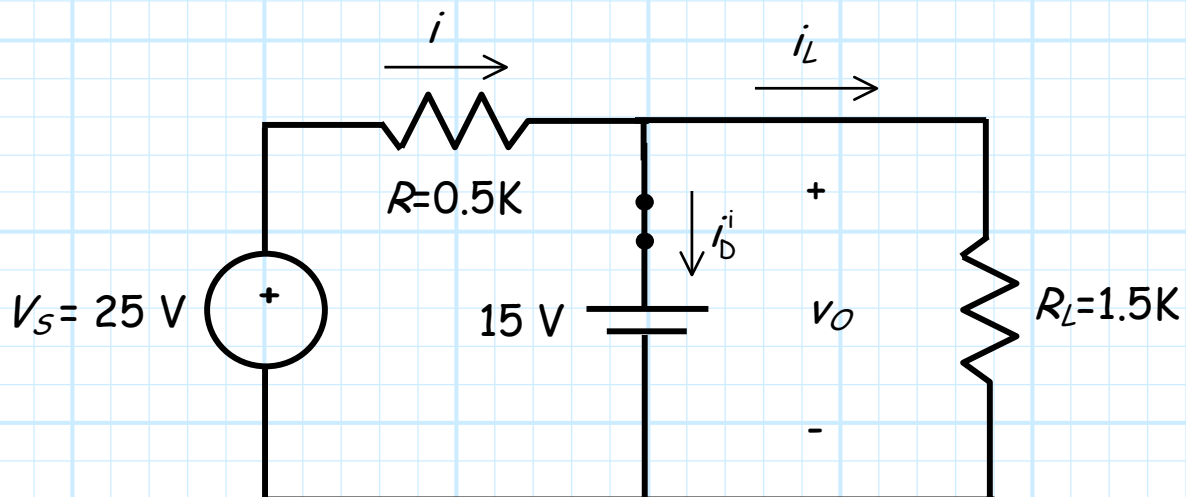Part 2:

Again, use the zener **CVD model**, and enforce $v_D' = 0$:



Analyzing, from KCL:

$$i_D^i =$$

and from Ohm's Law:

$$i =$$

$$i_L =$$

Therefore $i_D^i = i - i_L = 20 - 10 = 10.0 \text{ mA}$ ($\because i_D^i = 10 > 0$ ✓)

And thus we **estimate** $i_Z = i_D^i = 10.0 \text{ mA}$

Part 3:

The shunt regulator **line regulation** is:

$$\text{Line Regulation} = \frac{r_z}{R + r_z} =$$

Therefore if $\Delta v_s = 1 \text{ V}$, then $\Delta v_o = (0.01) \Delta v_s = \mathbf{0.01 \text{ V}}$

Part 4:

The shunt regulator **load regulation** is:

$$\text{Load Regulation} = \frac{-R r_z}{R + r_z} =$$

Therefore if $\Delta i_L = 1 \text{ mA}$, then $\Delta v_o = -(4.95) \Delta i_L = \mathbf{-4.95 \text{ mV}}$