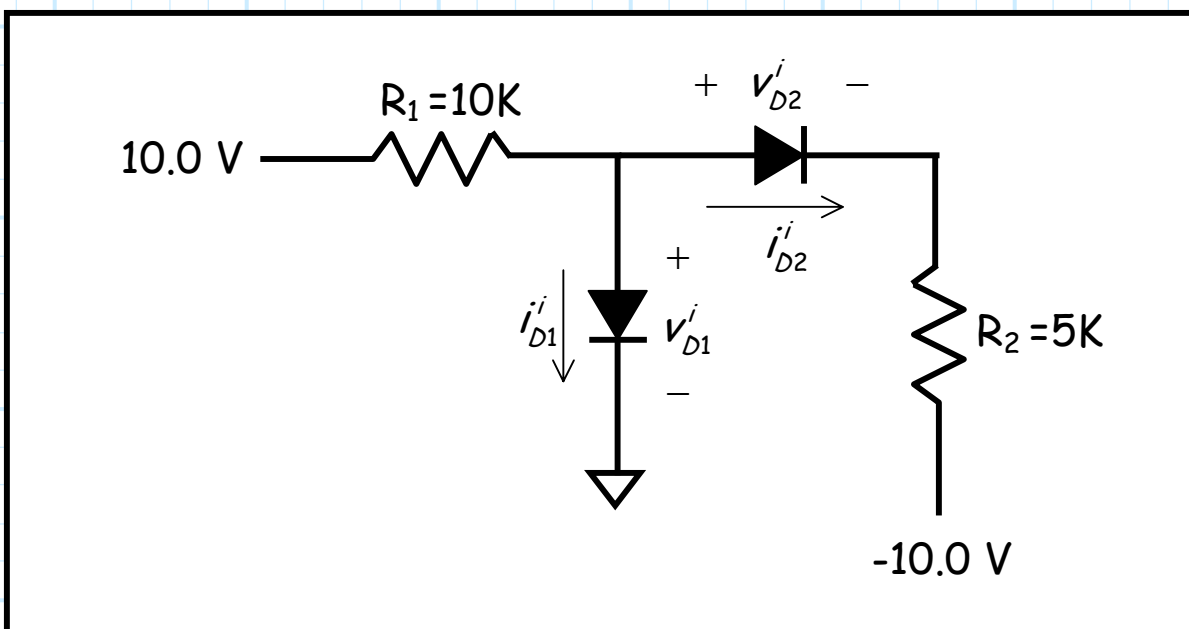


Example: Analysis of a Complex Diode Circuit

Consider this circuit with **two ideal diodes**:




Let's analyze this circuit and find v_{D1}^i , i_{D1}^i , v_{D2}^i , and i_{D2}^i !

Remember, we must accomplish each of the **five** steps:

Step 1: *ASSUME* that both D_1 and D_2 are "on" (might as well!).

Step 2: *ENFORCE* the equalities $v_{D1}^i = 0 = v_{D2}^i$, by replacing each ideal diode with a **short** circuit.

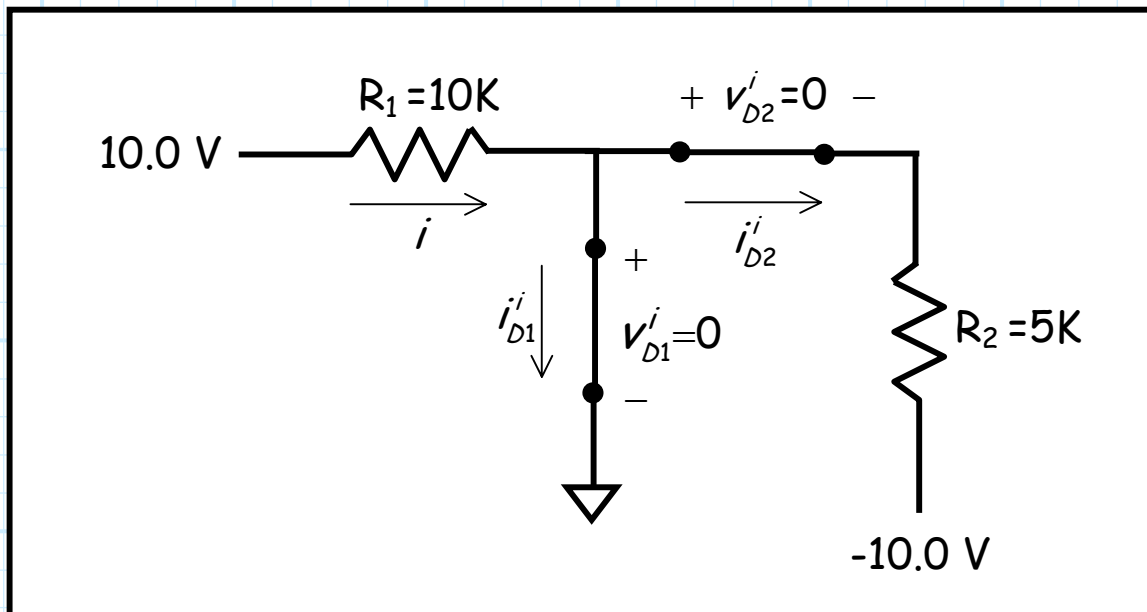Step 3: *ANALYZE* the resulting circuit, and find i_{D1}^i and i_{D2}^i .



Begin with **KCL**:

$$i = i_{D1}^i + i_{D2}^i$$

where $i =$

and $i_{D2}^i =$

Therefore, $i_{D1}^i =$


Step 4: Now we must *CHECK inequalities* to see if our assumptions are correct!

$$i_{D1}^i =$$

$$i_{D2}^i =$$



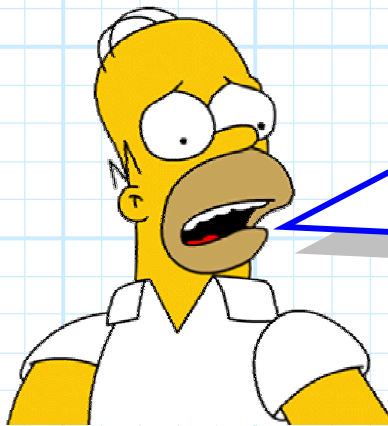One assumption is therefore **INCORRECT**. We must proceed to **step 5**—change our assumptions and **completely** start again!



Q: *Wait a second! We don't have to **completely** start from the beginning, do we? After all, our assumption about diode D_2 turned out to be **true**—so we **already** know that $i_{D2}^i =$ and $v_{D2}^i = 0$, **right?***


A: **NO!** The solution for diode D_2 is dependent on the state of both diodes D_1 and D_2 . If the assumption of just **one** diode turns out to be incorrect, then the solutions for **all** diodes are **wrong!**

So, let's change our assumption and start all over again!

Step 1: Now *ASSUME* that D_1 is "off" and D_2 is "on".

Step 2: *ENFORCE* $i_{D1}^i = 0$ (D_1 open) and $v_{D2}^i = 0$ (D_2 short).

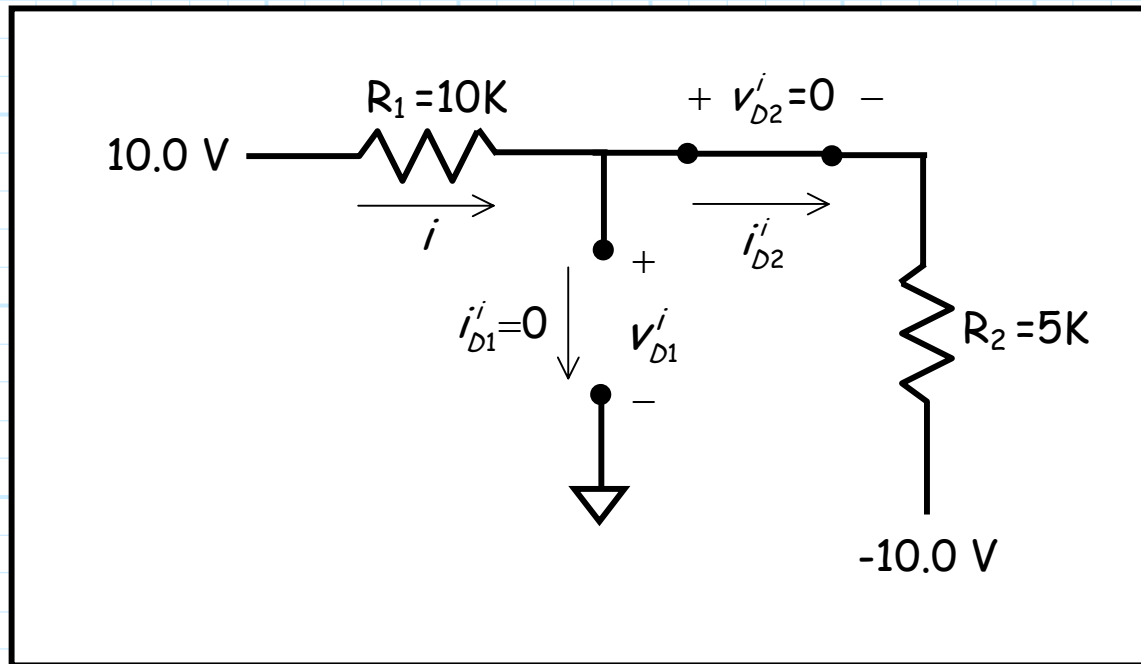Step 3: *ANALYZE* resulting circuit, and find v_{D1}^i and i_{D2}^i .



Note $i = i_{D2}^i =$

and from KVL:

$$\therefore v_D^i =$$

4) CHECK our assumptions.

$$i_{D2}^i =$$

$$v_{D1}^i =$$

\therefore Assumptions are **correct!** We are finished!



$$v_{D1}^i =$$

$$i_{D1}^i = 0$$

$$v_{D2}^i = 0$$

$$i_{D2}^i =$$