 



# Small-Signal Analysis

Consider this simple junction diode circuit:



The DC voltage source ( $V_{DD}$ ) results in a DC current ( $I_D$ ), as well as a DC voltage across the junction diode  $V_D$ .

 
Now let's add an AC (e.g., small-signal) source ( $v_d$ ) to the circuit:




Note that this results in an **additional AC** (small-signal) **component** for the junction diode current and voltage.

**Q:** What *are* the DC and small-signal components of the diode current and voltage, and how are they *related* to the DC ( $V_{DD}$ ) and small-signal ( $v_s$ ) voltage sources?

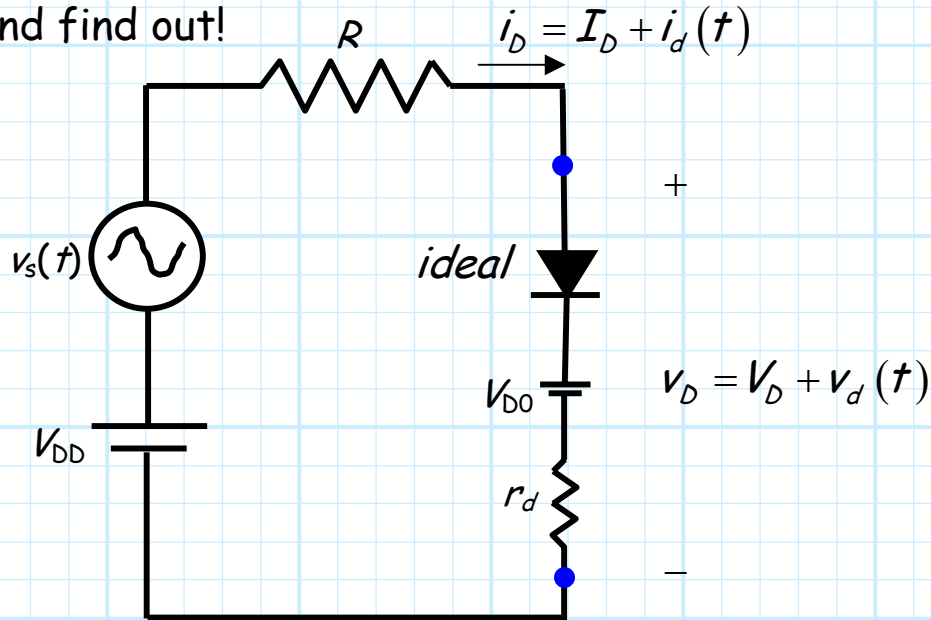**A:** Let's replace the junction diode with a small-signal PWL model and find out!



 If the DC voltage source is sufficiently large (e.g.,  $V_{DD} \gg V_{D0}$ ), we will find that the ideal diode is **forward biased** ( $v_D^i = 0$ ):



Now, let's apply **KVL** and analyze the circuit!

First, we'll consider the case where the **small-signal voltage source is zero** ( $v_s(t) = 0$ ). In this case, the remaining **DC sources** ( $V_{DD}$  and  $V_{D0}$ ) produce a DC voltage and current ( $V_D$  and  $I_D$ ).

These DC values are related from KVL as:

$$V_{DD} = I_D(R + r_d) + V_{D0}$$

We call this the **DC circuit equation**.

Now let's "**turn on**" the small-signal source, so that  $v_s(t) \neq 0$ . Now we have, in **addition** to the DC currents and voltages, **small-signal components**  $i_d$  and  $v_d$  as well!

Again using **KVL**, we find that the DC and small-signal components are related as:

$$\begin{aligned} V_{DD} + v_s &= (I_D + i_d)R + V_{D0} + (I_D + i_d)r_d \\ &= (R + r_d)I_D + V_{D0} + (R + r_d)i_d \end{aligned}$$

Now, just for fun, let's **subtract** the **DC equation** from this KVL:

$$\begin{aligned} v_s + V_{DD} &= (R + r_d)I_D + V_{D0} + (R + r_d)i_d \\ -V_{DD} &= -(R + r_d)I_D - V_{D0} \end{aligned}$$

---


$$v_s = (R + r_d)i_d$$

The resulting equation:

$$v_s(t) = (R + r_d)i_d(t)$$

is known as the AC, or **small-signal circuit equation**.

Thus, the **total KVL** can be divided into two parts, the **DC equation** and the **small-signal equation**, i.e.:

$$V_{DD} + v_s = (R + r_d)I_D + V_{D0} + (R + r_d)i_d$$


where the **DC equation** is:

$$V_{DD} = (R + r_d)I_D + V_{D0}$$

and the **small-signal equation** is:


$$v_s = (R + r_d)i_d$$

 Now, it is **very important** that you note this interesting result. The **DC equation** can be **directly derived** from KVL applied to this circuit:



$$V_{DD} = (R + r_d)I_D + V_{D0}$$

 Likewise, the **small-signal equation** can be **directly derived** from KVL applied to **this** circuit:




**Just** as we can separate the total circuit KVL equation into DC and small-signal equations, we can **separate** the total **circuit** into DC and small-signal **circuits**!

Look **closely** at the two circuits. All we really have done is apply **superposition**! I.E.:


1. We turned **off** the small-signal source and then determined the **DC solution** (i.e., the DC equation):

$$V_{DD} = (R + r_d) I_D + V_{D0}$$

 



2. We then turned **off** the DC sources and determined the **small-signal solution** (i.e., the small-signal equation):

$$v_s(t) = (R + r_d) i_d(t)$$

 


**Q:** *Hold on dude! Earlier in the course you said that diodes are **non-linear** devices, meaning that superposition **cannot** be applied!?!*

  **A:** True! But look at the circuit we are analyzing—there are **no diodes** in this circuit!



- \* Recall the (assumed) forward biased ideal diode was replaced with a **short circuit**—and a short circuit is a linear device!
- \* Thus, applying superposition to this circuit is a valid analysis technique, provided that **ideal diode remains forward biased** for all time  $t$  (i.e.,  $i_d(t) > 0$  for all time  $t$ ).
- \* If the DC source is sufficiently large to place the ideal diode “firmly” into forward bias (i.e.,  $I_D \gg 0$ ), then the addition of a small AC source (i.e., the small signal source) will typically **not** change the ideal bias state (i.e.,  $I_D + i_d(t) > 0$  for all  $t$ ).

 Thus, we can perform a **small-signal analysis** of a junction diode circuit (once a junction diode **model** is applied) by applying **superposition**—turn off the DC sources and analyze the resulting **small-signal circuit!**



**Q:** *But what junction diode model should I use when performing a small-signal analysis??*


**A:** We can theoretically use **any** valid diode model (e.g., CVD, PWL) in a small-signal analysis. However, when we consider the type of small signal problem that we **typically** encounter, we find that **one model** stands out as **most** appropriate.

Consider the **total** diode current and **total** diode voltage when **both** DC and small-signal components are present:

$$i_D(t) = I_D + i_d(t)$$


$$v_D(t) = V_D + v_d(t)$$

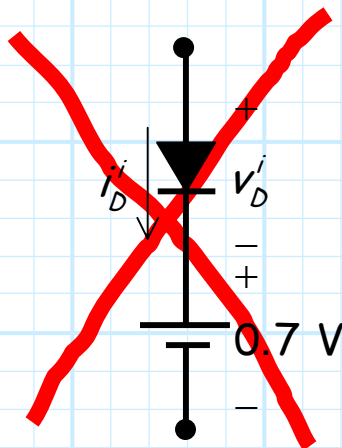First of all, we can assume that the small-signal current  $i_d$  and small-signal voltage  $v_d$  is indeed—**small**. As such, we typically need some **precision** in our diode model if we are in search of **accurate** small-signal estimates.



For example, the **CVD** model would **always** provide an estimate of the small-signal diode voltage of  $v_d(t)=0$  (i.e., for CVD  $v_D(t)=0.7$  V always, thus  $V_D=0.7$  V and  $v_d=0$  **always!**)—this is **not** precise enough!

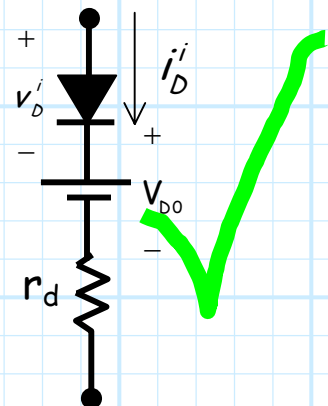
Thus we might conclude that a **PWL model** is our best bet. The problem then becomes how to **construct** this model (i.e., **what values** of  $r_D$  and  $V_{D0}$  should we use??).





First, we note that since if the small-signal diode currents and voltages are **small**, the **largest total** diode current and **total** diode voltage ( $i_D(t)$  and  $v_D(t)$ ) will **never** be much larger than the **DC** diode current and voltage  $I_D$  and  $V_D$ .

 Likewise, the **smallest total** diode voltage and **total** diode current will **never** be much smaller than the **DC** diode current and voltage  $I_D$  and  $V_D$ .




→ We need a model that **matches** the junction diode curve around the **DC diode** voltages  $I_D$  and  $V_D$ !

**Q:** Hey! Doesn't the *small-signal PWL model* do that ?

**A:** Precisely! That's **why** we called it the small-signal PWL model—it works **best** for accurate **small-signal analysis**!

 The DC diode current  $I_D$  and voltage  $V_D$  is the "**bias point**" that we spoke of when explaining the small-signal PWL model. Recall that **once** we determine these DC bias values, we can **immediately** find the model values of  $V_{D0}$  and  $r_D$ !





**Q:** *But dude, how can I determine the DC "bias" values  $I_D$  and  $V_D$  if I do not **first** know the parameters ( $V_{D0}$  and  $r_D$ ) of my PWL junction diode model?*

**A:** Easy! We simply perform a **DC analysis** with the **DC circuit** to find  $I_D$  and  $V_D$ . The "trick" is that we perform the DC analysis using the **CVD model**—and we **know** the model parameters of the CVD model!

