

Synthesis of CMOS Gates

Let's consider the design synthesis of CMOS gates by considering the design synthesis of PUN and PDN separately.

PDN Design Synthesis

1. If the PDN is **conducting**, then the **output** will be **low**. Thus, we must find a Boolean expression for the **complemented output** \bar{Y} .


In turn, the PDN can only be conducting if **one or more** of the NMOS devices are **conducting**—and NMOS devices will be conducting (i.e., **triode mode**) when the **inputs are high** ($V_{GSN} = V_{DD}$).

Thus, we **must** express \bar{Y} in terms of **un-complemented inputs** A, B, C , etc (i.e., $\bar{Y} = f(A, B, C)$).

$$\text{e.g., } \rightarrow \bar{Y} = A + BC$$

This step may test our **Boolean algebraic skills!**

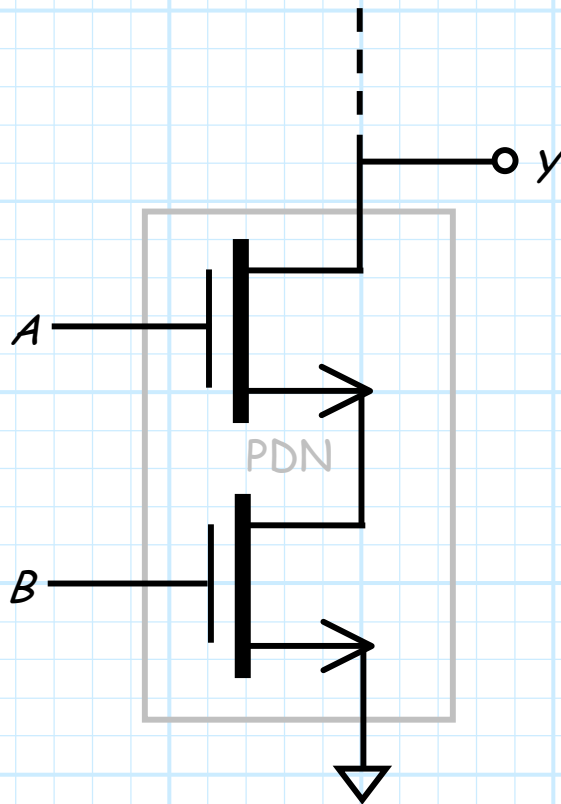
2. Then, we realize **AND** operations in $\bar{Y} = f(A, B, C)$ with **series NMOS** devices. E.G.:



Note that $Y=0$ if
both $A = V_{DD}$ **AND** $B = V_{DD}$.

$$\therefore \bar{Y} = AB$$

 3. Likewise, we realize **OR** operations with **parallel NMOS** devices. E.G.:



Note that $Y=0$ if **either**
 $A = V_{DD}$ **OR** $B = V_{DD}$.

$$\therefore \bar{Y} = A + B$$

PUN Design Synthesis

1. If the PUN is **conducting**, then the **output** will be **high**. Thus, we must find a Boolean expression for the **un-complemented output** Y .


In turn, the PUN can only be conducting if **one or more** of the PMOS devices are **conducting**—and PMOS devices will be conducting (i.e., **triode mode**) when the **inputs are low** ($V_{GSP} = -V_{DD}$).

Thus, we **must** express Y in terms of complemented inputs $\bar{A}, \bar{B}, \bar{C}$, etc (i.e., $Y = f(\bar{A}, \bar{B}, \bar{C})$).

$$\text{e.g., } \rightarrow Y = \bar{A} + \bar{B}\bar{C}$$

This step may test our **Boolean algebraic** skills!

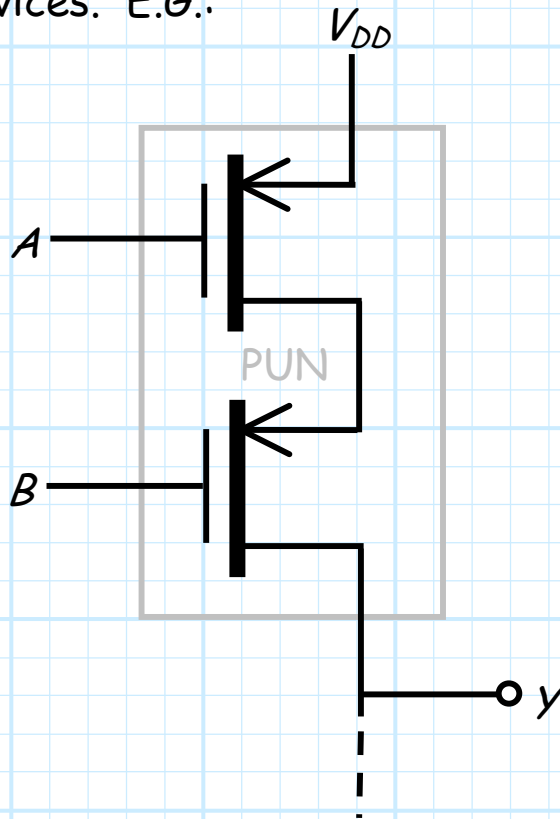
2. Then, we realize **AND** operations with **series PMOS** devices. E.G.:



Note that $Y = V_{DD}$ if
both $A = 0$ AND $B = 0$.

$$\therefore Y = \overline{A} \overline{B}$$

 3. Likewise, we realize **OR** operations with **parallel PMOS** devices. E.G.:



Note that $Y = V_{DD}$ if
either $A = 0$ OR $B = 0$.

$$\therefore Y = \overline{A} + \overline{B}$$