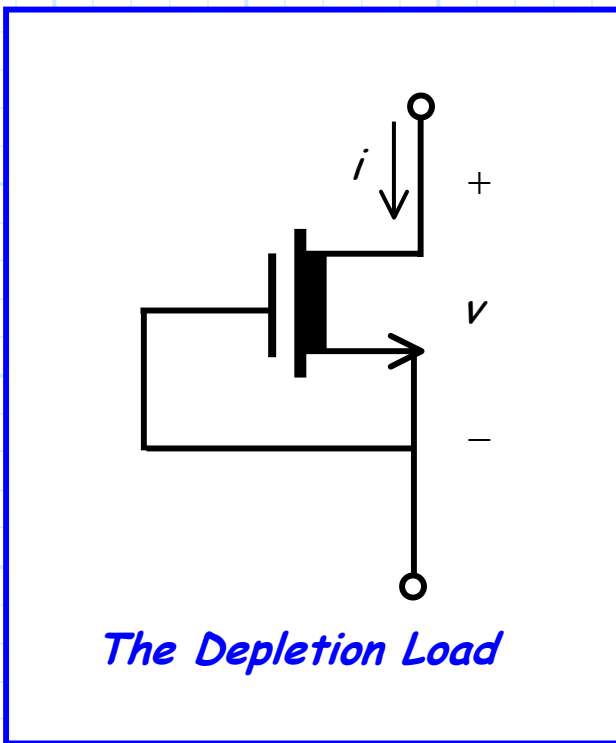


The Depletion Load

Say we connect the gate of a **depletion** NMOS to its source—we now have a **two-terminal device**!

This device is called a **depletion load**.



Since the depletion load is a two-terminal device, its **behavior** is defined by the relationship between the **voltage** v across the device and the **current** i through it.


For example, a **resistor** is a two terminal device whose behavior (i.e., its relationship between i and v) is defined by **Ohm's Law** ($i = v/R$).

Although the **depletion load** is decidedly **not** a resistor, its i - v relationship does have **some** similarities with Ohm's Law.

Q: *So what is "Ohm's Law" for a depletion load (i.e., what is $i = f(v)$)?*

A: A result easily found by implementing our knowledge of depletion MOSFETs!

For a depletion load, we find that:

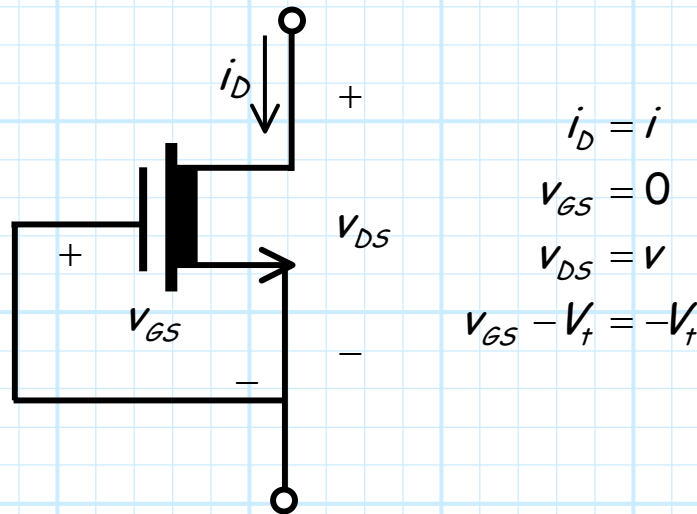

Q: But since $v_{GS} = 0$, isn't the NMOS device in *cutoff*?

A: **Nope!** Notice that this is a depletion MOSFET, and a depletion MOSFET **will** conduct when $v_{GS} = 0$!

Thus the MOSFET in a depletion load will always be either in:
a) triode or **b)** saturation.

a) Depletion load MOSFET is in **triode** if:

$$\begin{aligned}
 v_{DS} &< v_{GS} - V_t \\
 v &< 0 - V_t \\
 v &< -V_t
 \end{aligned}$$

Therefore, the **current** will be:

$$i_D = K \left[2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right]$$

$$i = K \left[2(0 - V_t)v - v^2 \right]$$

$$i = K \left[-2V_t v - v^2 \right]$$

b) Depletion load MOSFET is in **saturation** if:

$$v_{DS} > v_{GS} - V_t$$

$$v > 0 - V_t$$

$$v > -V_t$$


Therefore, the **current** will be:

$$i_D = K(v_{GS} - V_t)^2 + \frac{v_{DS}}{r_o}$$

$$i = K(0 - V_t)^2 + \frac{v}{r_o}$$

$$i = K(-V_t)^2 + \frac{v}{r_o}$$


$$i = K V_t^2 + \frac{v}{r_o}$$

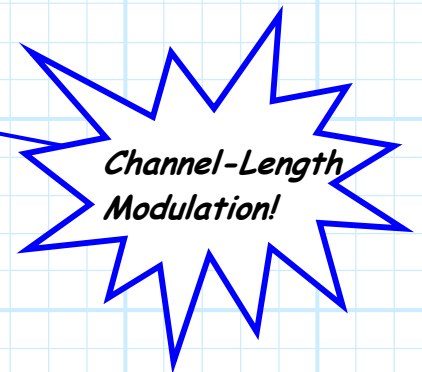

where in this case:


$$r_o = \frac{1}{\lambda K (v_{GS} - V_t)^2} = \frac{1}{\lambda K (0 - V_t)^2} = \frac{1}{\lambda V_t^2}$$

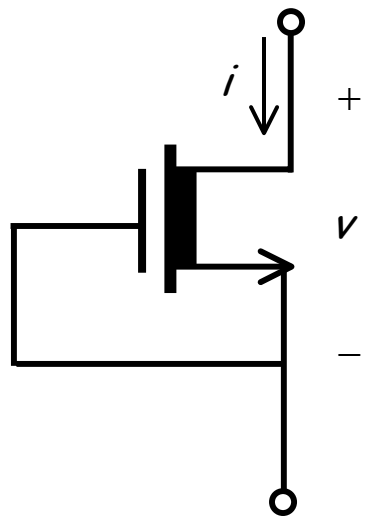Combining the two results, we find that "Ohm's Law" for a depletion load is:



$$i = \begin{cases} K[-2V_t v - v^2] & \text{if } 0 < v < -V_t \\ KV_t^2 + \frac{v}{r_o} & \text{if } v > -V_t \end{cases}$$

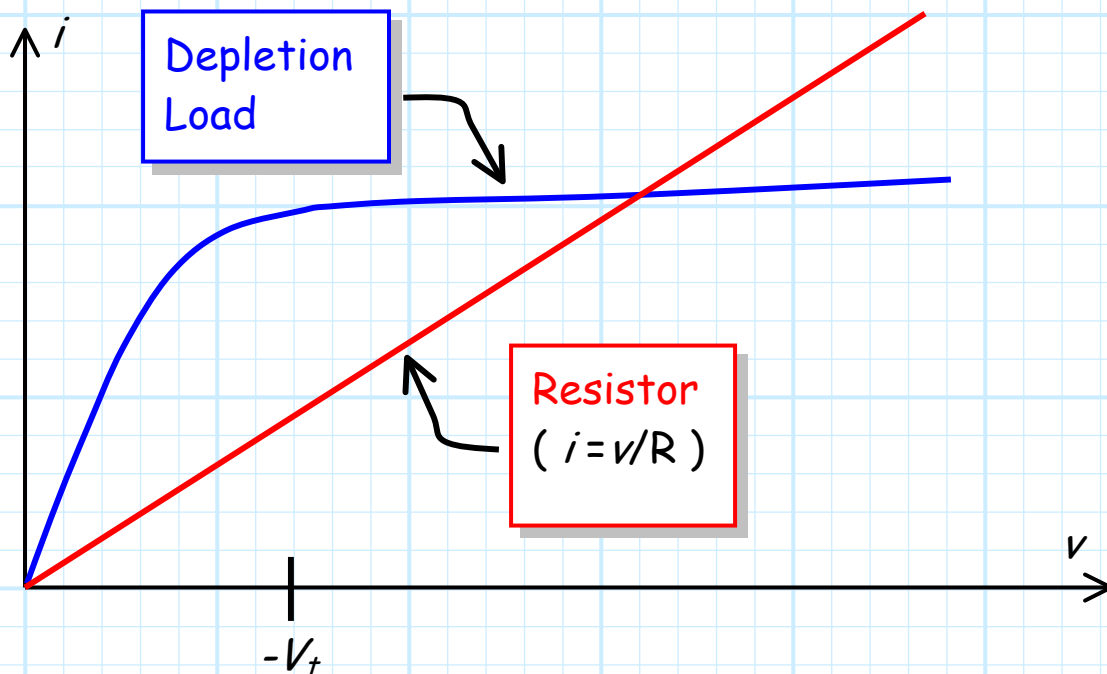Plotting this function, we find something like this:



Note that the behavior of a Depletion Load and a resistor are **very different**—however they are precisely the **same** in two key ways:

1. When the voltage across each device (i.e., resistor and depletion load) is **zero**, the current through each device is likewise **zero** (and vice versa!).
2. As the voltage across each device **increases**, the current through each device **increases**.

As a result, we can use a depletion load as the “**pull-up resistor**” in our integrated circuit NMOS logic!

