
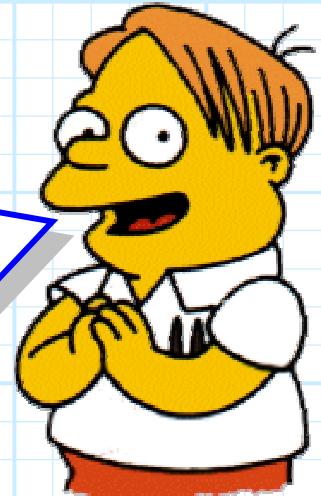


The Ideal Diode

An **ideal diode**—the circuit device with a split personality!

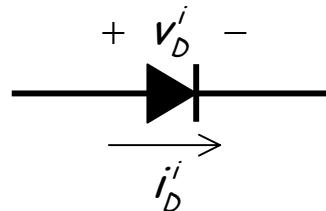→ Is it a **short**? Or is it an **open**?



	$v_D^i < 0$	$v_D^i = 0$	$v_D^i > 0$
$i_D^i > 0$	invalid	forward biased	invalid
$i_D^i = 0$	reverse biased	no bias	invalid
$i_D^i < 0$	invalid	invalid	invalid