
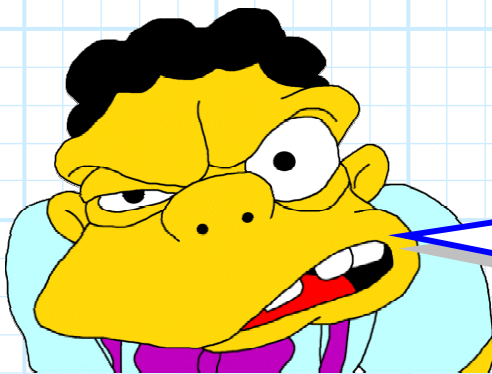

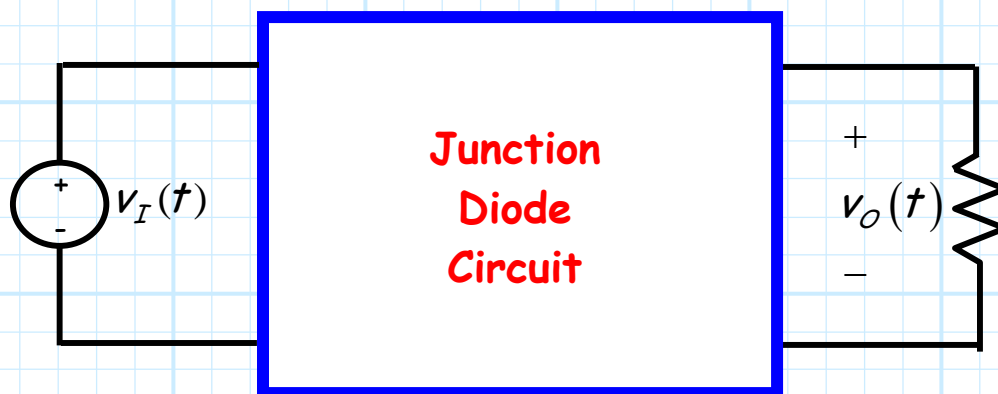
# The Transfer Function of Diode Circuits

For many junction diode circuits, we find that one of the voltage sources is in fact **unknown**! This unknown voltage is typically some **input** signal of the form  $v_I(t)$ , which results in an output voltage  $v_O(t)$ .



**Q:** *How the heck do you expect us to determine  $v_O(t)$  if we have **no idea** what  $v_I(t)$  is??*

**A:** We of course cannot determine an **explicit** value or expression for  $v_O(t)$ , since it **depends** on the input  $v_I(t)$ . Instead, we will attempt to explicitly determine this **dependence** of  $v_O(t)$  on  $v_I(t)$ !

In other words, we seek to find an expression for  $v_O$  in **terms** of  $v_I$ . Mathematically speaking, our goal is to determine the **function**:


$$v_O = f(v_I)$$

We refer to this as the **circuit transfer function**.

Note that we can **plot** a circuit transfer function on a 2-dimensional plane, just as if the function related values  $x$  and  $y$  (e.g.  $y = f(x)$ ). For **example**, say our circuit transfer function is:

$$\begin{aligned} v_O &= f(v_I) \\ &= 3v_I + 2 \end{aligned}$$

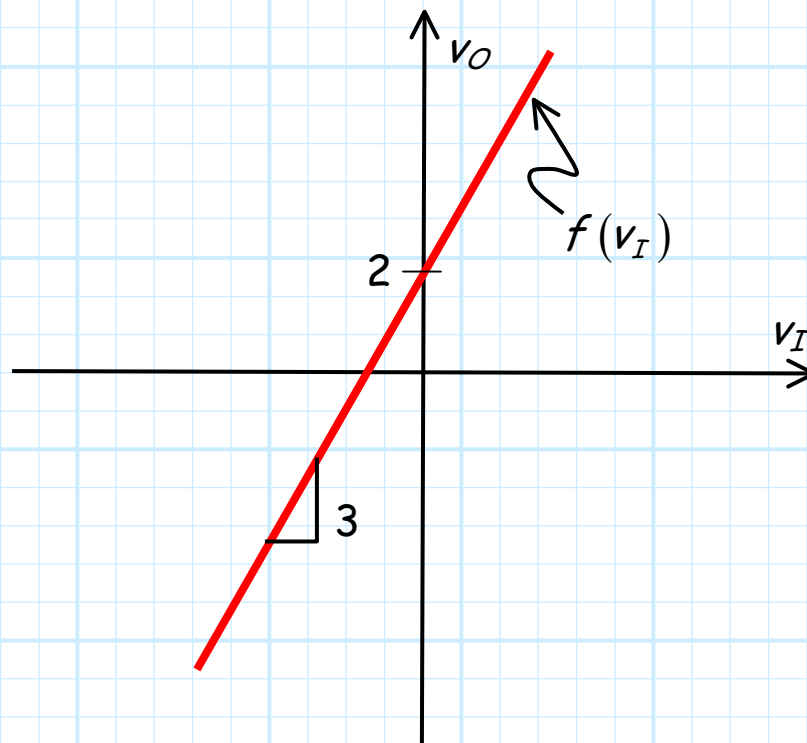Note this is simply the **equation of a line** (e.g.,  $y = 3x + 2$ ), with slope  $m=3$  and intercept  $b=2$ .



**Q:** A "function" eh? Isn't a "function" just your annoyingly pretentious way of saying we need to find some mathematic equation relating  $v_O$  and  $v_I$ ?





**A:** Actually **no!** Although a function is a mathematical equation, there are in fact **scads** of equations relating  $v_O$  and  $v_I$  that are **not** functions!

→ The set of all possible functions  $y = f(x)$  are a **subset** of the set of all possible equations relating  $y$  and  $x$ .



A **function**  $v_O = f(v_I)$  is a mathematical expression such that for **any** value of  $v_I$  (i.e.,  $-\infty < v_I < \infty$ ), there is **one**, but **only one**, value  $v_O$ .

Note this definition of a function is consistent with our **physical** understanding of circuits—we can place **any** voltage on the input that we want (i.e.,  $-\infty < v_I < \infty$ ), and the result will be **one** specific voltage value  $v_O$  on the output.

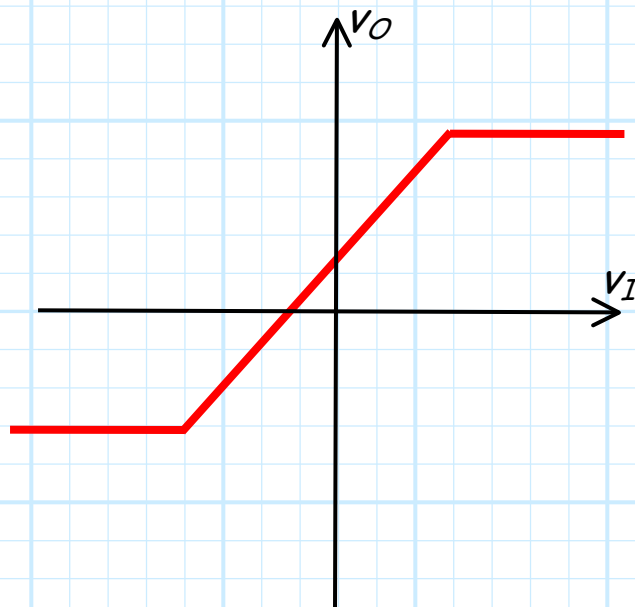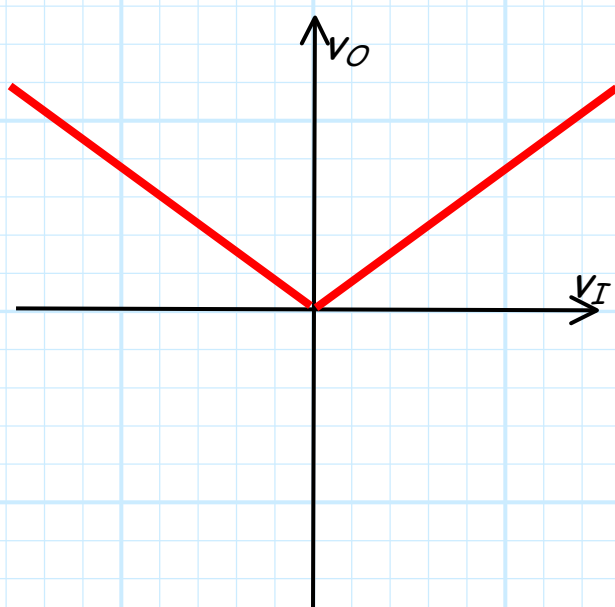
Therefore, examples of **valid** circuit transfer **functions** include:



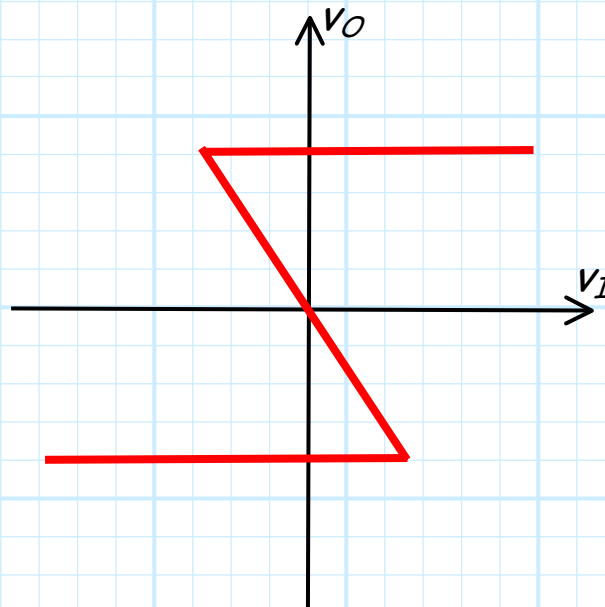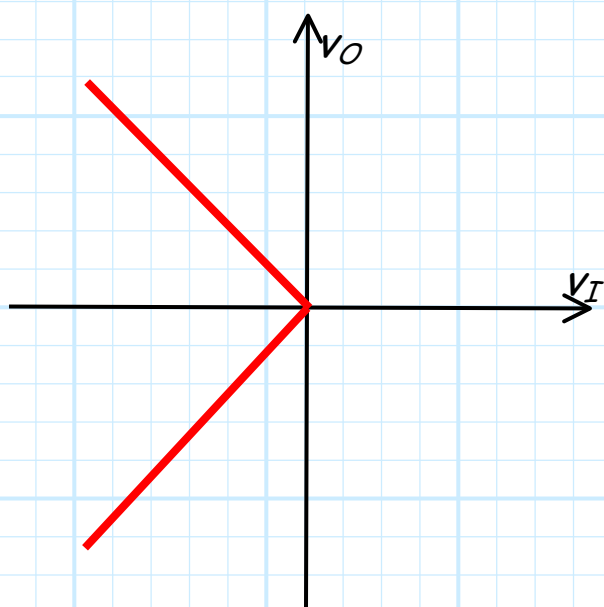
Conversely, the transfer "functions" **below** are **invalid**—they **cannot** represent the behavior of circuits, since they are **not** functions!



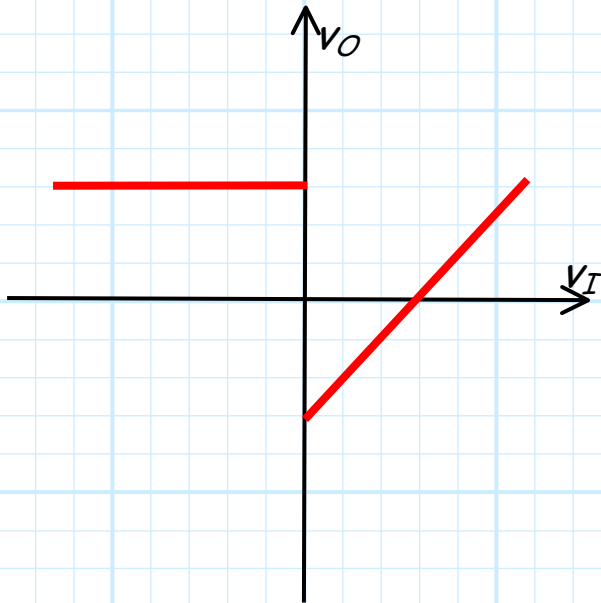Moreover, we find that **circuit** transfer functions must be **continuous**. That is,  $v_O$  **cannot** "instantaneously change" from one value to another as we increase (or decrease) the value  $v_I$ .



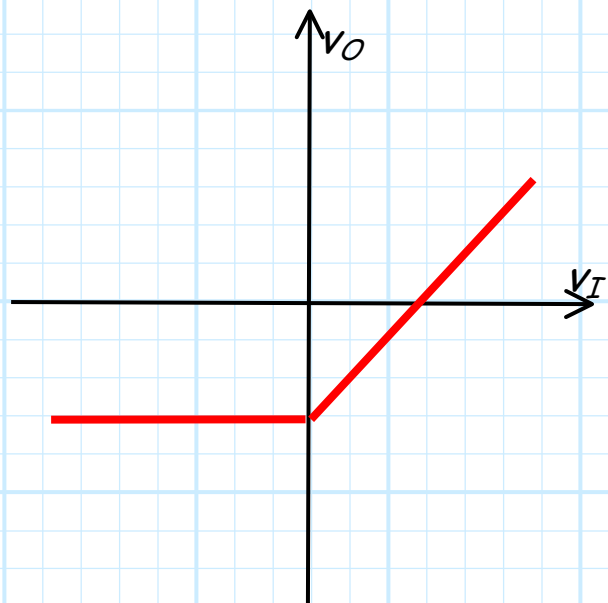**A Discontinuous  
Function**  
(*Invalid circuit  
transfer function*)



**A Continuous  
Function**  
(*Valid circuit  
transfer function*)



*Remember, the transfer function of **every** junction diode circuit must be a **continuous function**. If it is **not**, you've done something **wrong**!*