

EECS 312

EECS 312 - **Electronic Circuits I**

You already understand these **linear** devices:

All useful, but we need other devices to:

- 1.
- 2.

Vacuum tubes were once used to achieve this—now engineers use **semiconductor devices!**

Examples of semiconductor devices:

Q: So why semiconductor devices?

A: Orders of magnitude improvement in:


- 1.
- 2.
- 3.
- 4.

3.1 The Ideal Diode

Reading Assignment: pp.139-141

Diodes:

A) The Ideal Diode Symbol

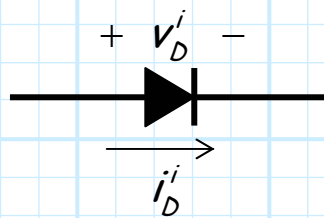

Note:

1. Device is **not** symmetric!
2. Positive current **defined** as flowing from anode to cathode.

3. Voltage across diode **defined** as positive when anode voltage $>$ cathode voltage.


B) Ideal Diode Behavior

The **ideal** diode \rightarrow

First, let's recall **linear device behavior!**

HO: Linear Device Behavior

For an **ideal** diode:

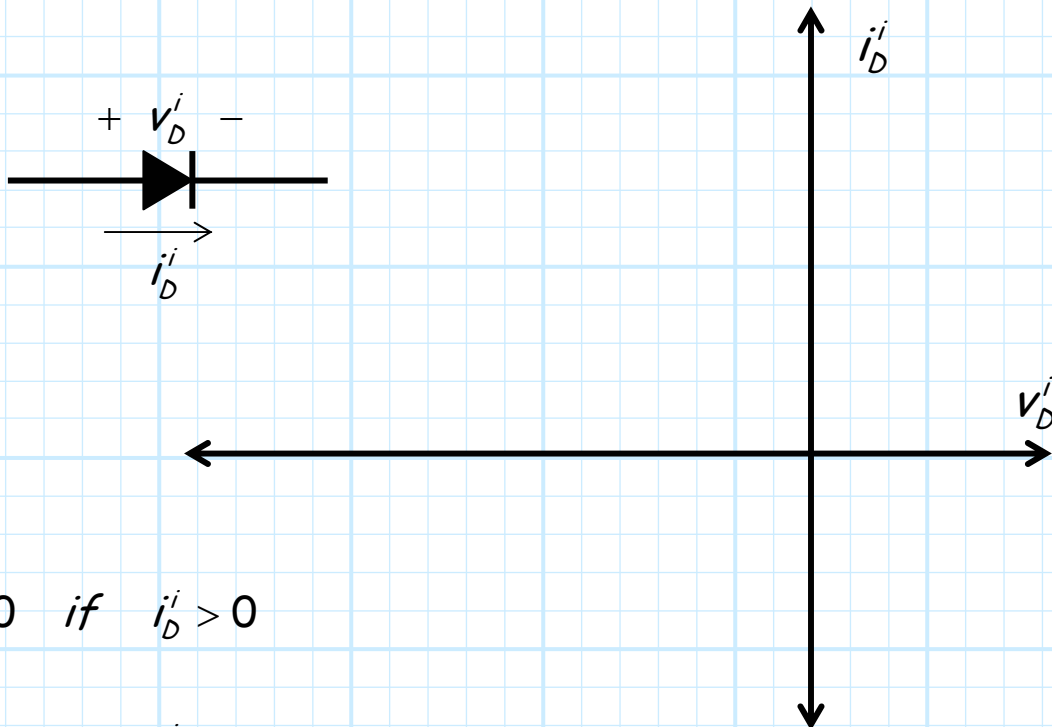

$$v_D^i = 0 \quad \text{if} \quad i_D^i > 0$$

$$i_D^i = 0 \quad \text{if} \quad v_D^i < 0$$

The **Ideal** Diode is non-linear!

C) Diode Bias Regions

An **ideal** diode operates in one of **two states**:

1) Forward Biased →

$$v_D^i = 0 \quad \text{if} \quad i_D^i > 0$$

i.e., acts as a short, IF current is positive.

2) Reverse Biased →

$$i_D^i = 0 \quad \text{if} \quad v_D^i < 0$$

i.e., acts as a open, IF voltage is negative.

Note: No power is dissipated in either mode!

$$\rightarrow P_D^i =$$

HO: The Ideal Diode

HO: Diode Mechanical Analogy

Q: What turns a diode "on" or "off"?

A:

Problem: It is **very** difficult to determine what the circuit is trying to do!

Therefore we must precisely follow a set of analysis steps to analyze circuits with these non-linear ideal diodes.

HO: The Ideal Diode Circuit Analysis Guide


A few examples to help illustrate this procedure:

Example: A Simple Ideal Diode Circuit


Example: Analysis of a Complex Ideal Diode Circuit

Linear Device Behavior

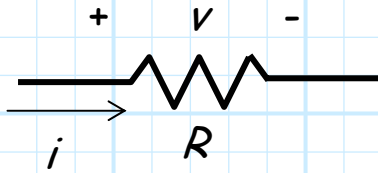
1) Recall the circuit behavior of a **resistor**:




$$i = \frac{v}{R}$$

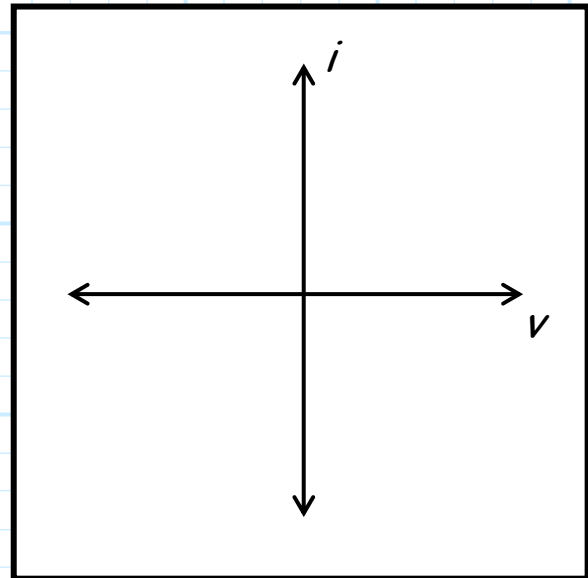


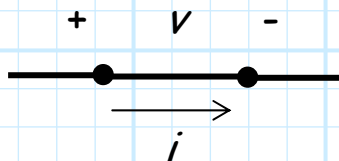
2) If $R=0$, then we have a **short circuit**:







$$v = 0$$

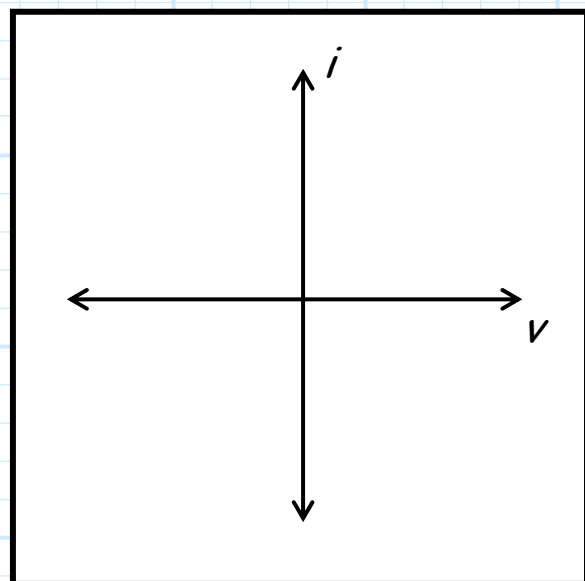

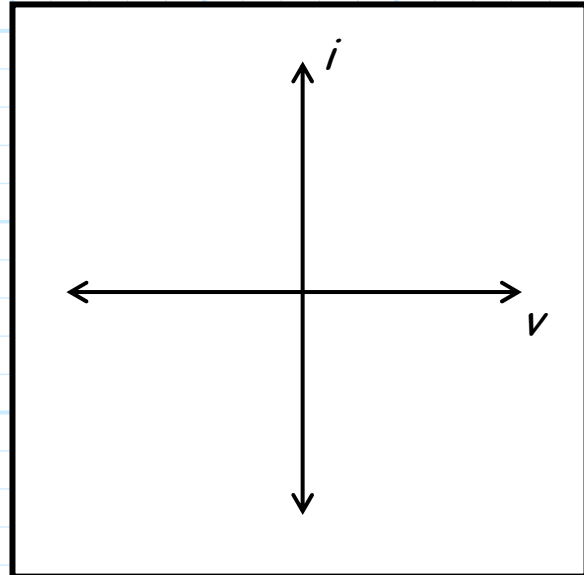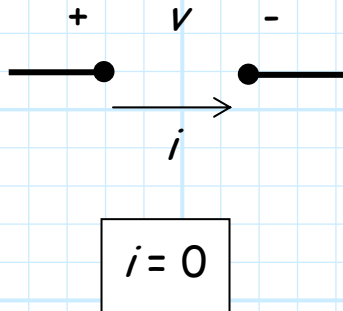3) If $R = \infty$, then we have an **open circuit**:



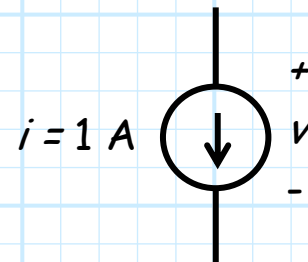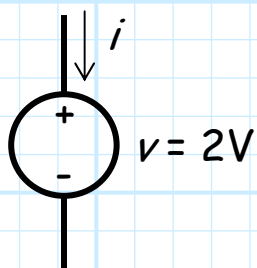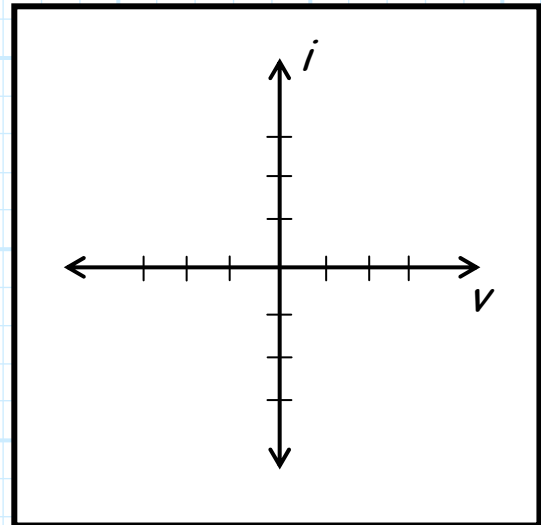
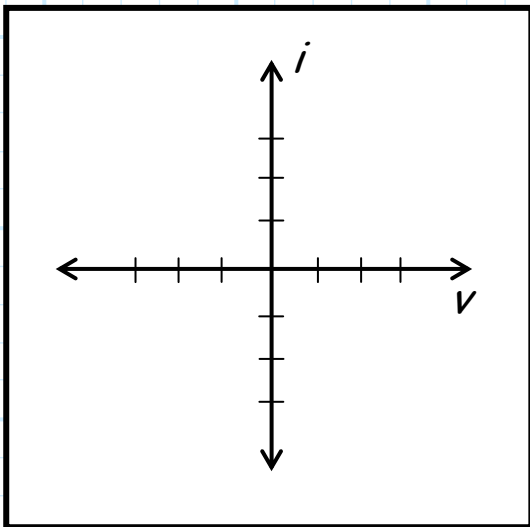
4) We can also plot the behavior of both current and voltage sources:



The Ideal Diode

An **ideal diode**—the circuit device with a split personality!

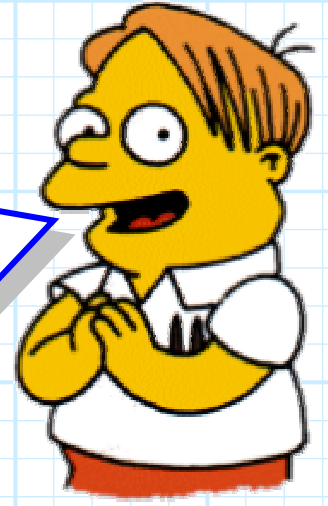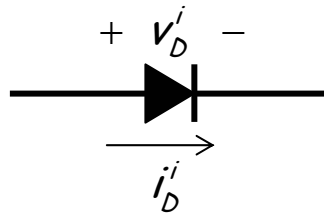→ Is it a **short**? Or is it an **open**?




	$v_D^i < 0$	$v_D^i = 0$	$v_D^i > 0$
$i_D^i > 0$	invalid	forward biased	invalid
$i_D^i = 0$	reverse biased	no bias	invalid
$i_D^i < 0$	invalid	invalid	invalid


The Diode

Mechanical Analogy

An ideal diode is sort of like a mechanical valve !

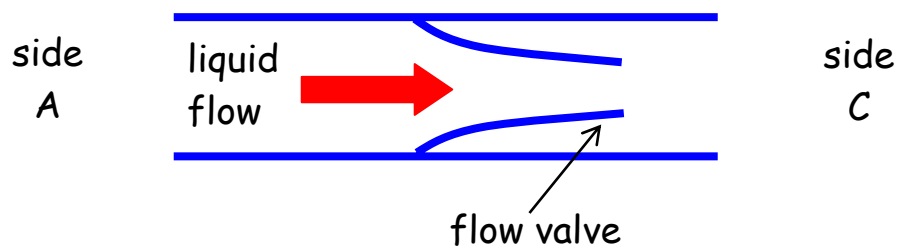

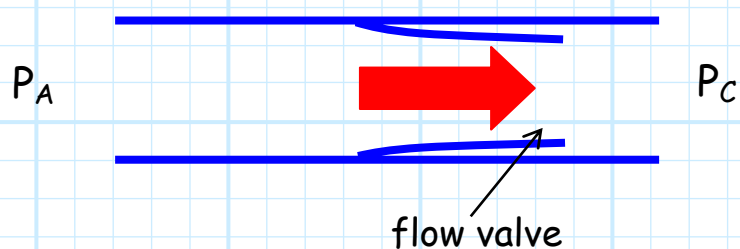
Case 1: Valve allows liquid to flow in pipe from side A to side C.



There is no drop in pressure (P) from side A to side C.

$$\rightarrow P_A - P_C = 0$$

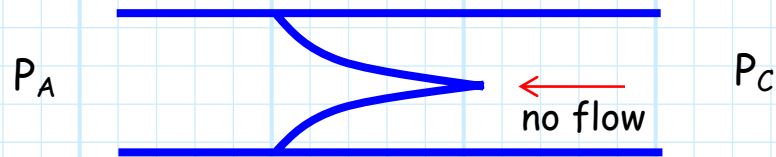Case 2: Valve prevents liquid from flowing **back** from side C to side A.



No flow occurs when pressure P_C is greater than pressure P_A

→ $P_A - P_C < 0$

Note the **analogies** with an ideal diode:

Valve

Pressure

Liquid Flow

Side A

Side C

Case 1

Case 2

Diode

Voltage

Current

Anode

Cathode

Forward Bias

Reverse Bias



The Ideal Diode Circuit Analysis Guide

Follow these easy steps to successfully analyze a circuit containing one or more **ideal** diodes !

Step 1: *ASSUME* a bias state for each ideal diode.

⇒ In other words, **GUESS !!**

Either,

- a) *ASSUME* an ideal diode is **forward biased**, or
- b) *ASSUME* it is **reversed biased**.

Step 2: *ENFORCE* the **equality** condition consistent with your assumption.

- a) If you assume an ideal diode is **f.b.**, then *ENFORCE* the equality:

$$v_D' = 0$$


HOW ? ⇒ By replacing the **ideal** diode with a **short** circuit!

b) If you assumed an ideal diode was **r.b.**, then **ENFORCE** the condition that:

$$i_D^i = 0$$

HOW ? \Rightarrow By replacing the ideal diode with an **open** circuit.

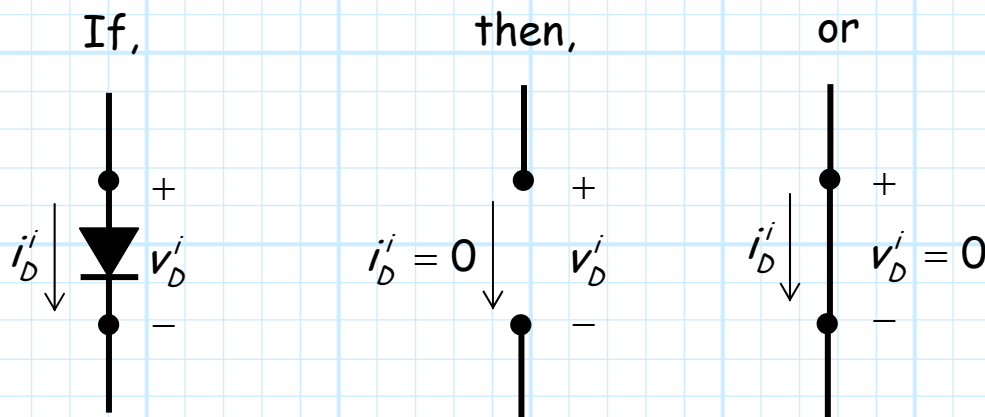IMPORTANT !!! Retain the **same** current and voltage definitions when you replace the ideal diode!



Step 3: ANALYZE the circuit.

After the all **ideal** diodes have been replaced with either shorts or opens:

- Determine **all** desired (required) circuit values.
- Determine i_D^i through each **short** circuit and v_D^i across each **open** circuit.

Step 4: *CHECK* the **inequality** consistent with your assumption to see **if** this assumption is correct.

HOW ??

a) An **ideal** diode cannot have negative current flowing through it. If you **ASSUMED** the ideal diode was **forward biased**, *CHECK* to see if the **short** circuit current is positive, i.e.:

$$i_D^i > 0$$

If true, you *ASSUMED* correctly ! **If not**, your **f.b.** assumption is wrong.

b) An **ideal** diode cannot have positive voltage across it. If you **ASSUMED** the ideal diode was **reversed biased**, *CHECK* to see if the **open** circuit voltage is negative, i.e.:

$$v_D^i < 0$$

If true, you *ASSUMED* correctly ! **If not**, your **r.b.** assumption is wrong.

Step 5: **If** you **ASSUMED** incorrectly, then **change** your assumptions and return to step 1 !

Notes on ideal diode circuit analysis:


- 1) You **must** check all assumptions in this form:

$$i_D^i = 2 \text{ mA} > 0 \checkmark \quad \text{or} \quad v_D^i = 2.2 > 0 \text{ X}$$

- 2) Do **not** check the condition that you enforced!
- 3) For **every** circuit, one and only one assumption will be valid.

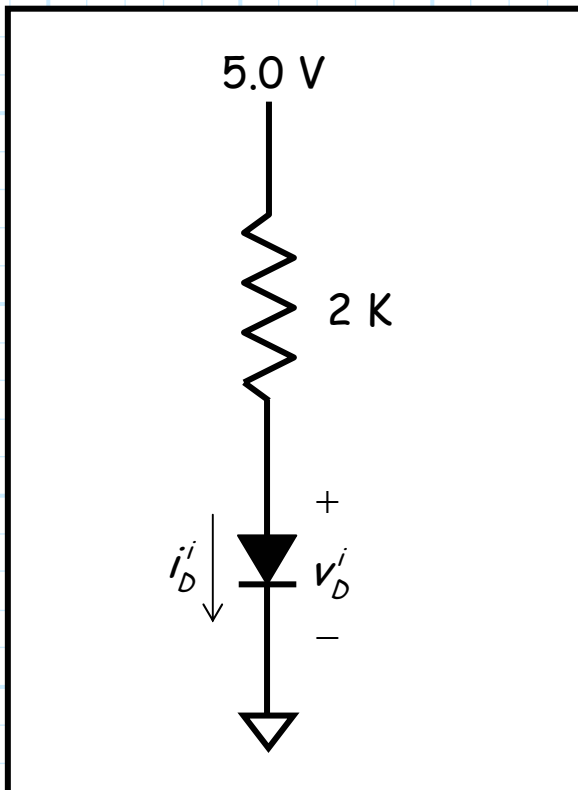Example: A Simple Ideal Diode Circuit

Consider this simple circuit that includes an **ideal** diode:




Q: What are i_D^i and v_D^i ?

A: Follow the five easy analysis steps!

Step 1: Let's *ASSUME* the ideal diode is **reverse biased** (we're just guessing!).

Step 2: We therefore *ENFORCE* $i_D^i = 0$ by replacing the ideal diode with an **open circuit**.

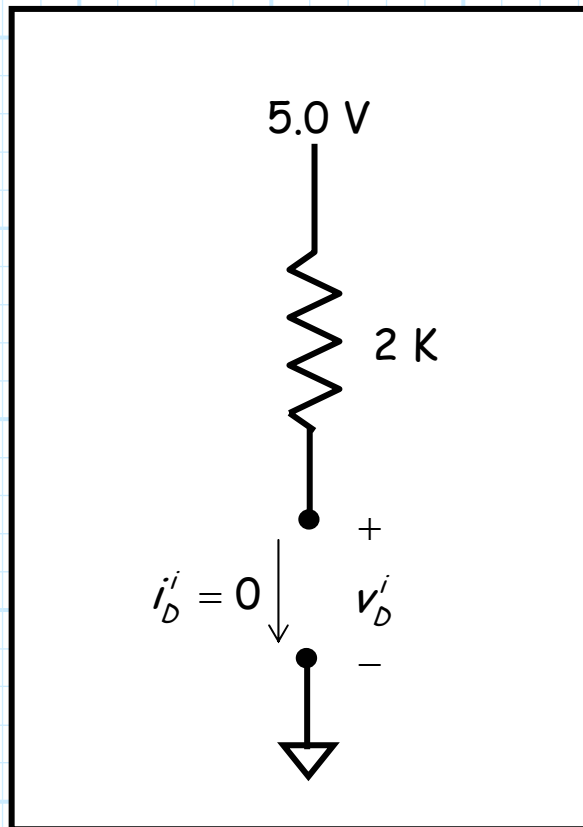Step 3: Now we *ANALYZE* the circuit; finding the value of v_D^i .



(KVL)

 \therefore

(KCL)

(Ohm's)

(enforced)


$$\therefore i_R =$$

$$\therefore v_R =$$

$$\therefore v_D^i =$$

Step 4: Now let's CHECK our result. \Rightarrow Is $v_D^i < 0$??

$$v_D^i =$$

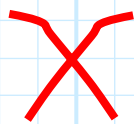


We must change our assumption, and then **start over** (Doh!).

1) Now *ASSUME* the ideal diode is **forward biased** (what's left?).

2) We therefore *ENFORCE* $v_D^i = 0$ by replacing the ideal diode with an **short circuit**.

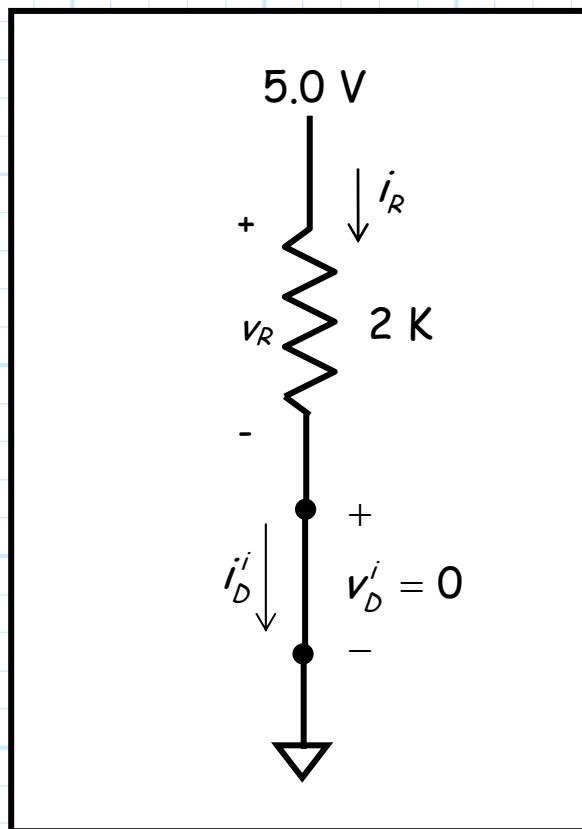3) Now we *ANALYZE* the circuit; finding the value of i_D^i .



(KVL)

 \therefore

(KCL)

(Ohm's)

(enforced)

$$\therefore V_R =$$

$$\therefore i_R =$$

$$\therefore i_D^i =$$

4) Now, let's *CHECK* our result. \Rightarrow **Is $i_D^i > 0$??**

$$i_D^i =$$




Our assumption is correct !

Therefore, in this circuit, we now **know** that:

$$v_D^i = 0 \text{ and } i_D^i =$$

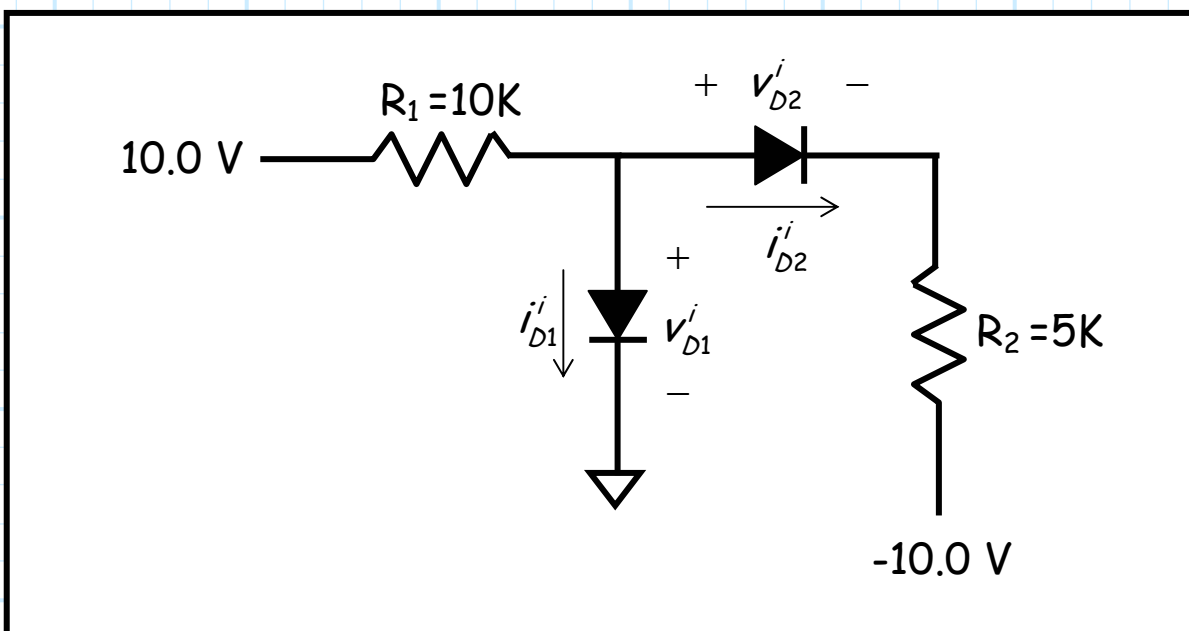Example: Analysis of a Complex Diode Circuit

Consider this circuit with **two ideal diodes**:




Let's analyze this circuit and find v_{D1}^i , i_{D1}^i , v_{D2}^i , and i_{D2}^i !

Remember, we must accomplish each of the **five** steps:

Step 1: *ASSUME* that both D_1 and D_2 are "on" (might as well!).

Step 2: *ENFORCE* the equalities $v_{D1}^i = 0 = v_{D2}^i$, by replacing each ideal diode with a **short** circuit.

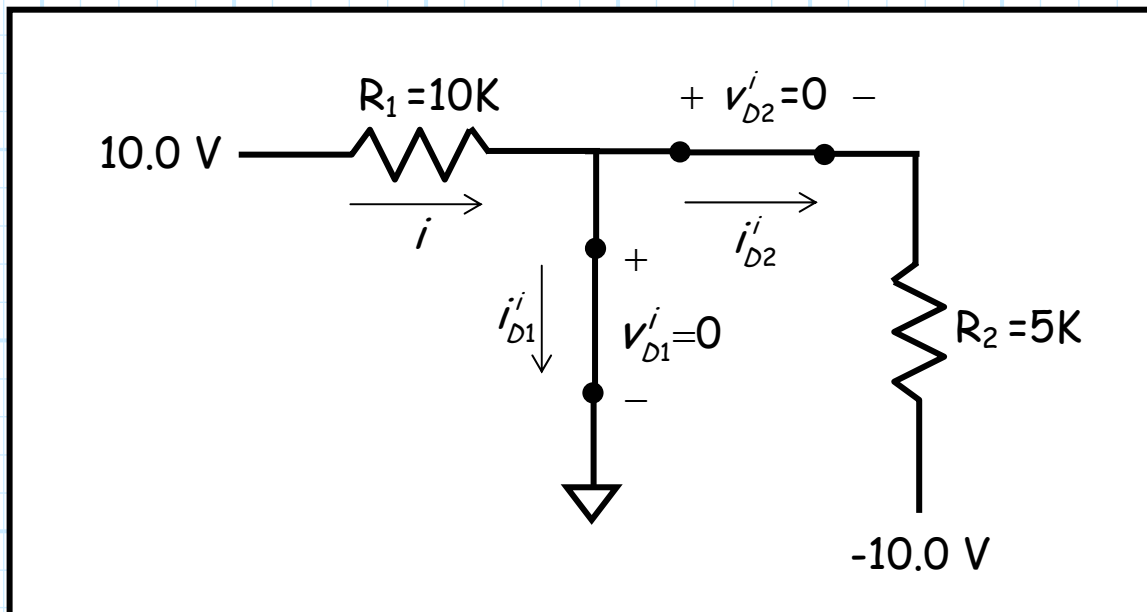Step 3: *ANALYZE* the resulting circuit, and find i_{D1}^i and i_{D2}^i .



Begin with **KCL**:

$$i = i_{D1}^i + i_{D2}^i$$

where $i =$

and $i_{D2}^i =$

Therefore, $i_{D1}^i =$


Step 4: Now we must *CHECK inequalities* to see if our assumptions are correct!

$$i_{D1}^i =$$

$$i_{D2}^i =$$



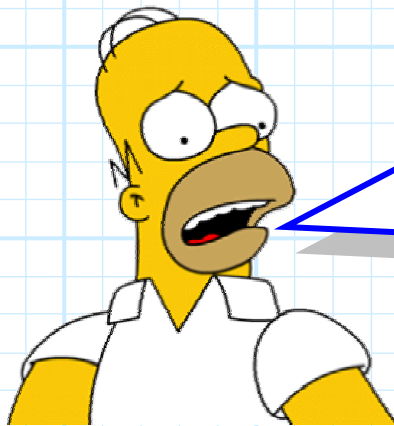One assumption is therefore **INCORRECT**. We must proceed to **step 5**—change our assumptions and **completely** start again!



Q: *Wait a second! We don't have to **completely** start from the beginning, do we? After all, our assumption about diode D_2 turned out to be **true**—so we **already** know that $i_{D2}^i =$ and $v_{D2}^i = 0$, **right?***


A: **NO!** The solution for diode D_2 is dependent on the state of both diodes D_1 and D_2 . If the assumption of just **one** diode turns out to be incorrect, then the solutions for **all** diodes are **wrong!**

So, let's change our assumption and start all over again!

Step 1: Now *ASSUME* that D_1 is "off" and D_2 is "on".

Step 2: *ENFORCE* $i_{D1}^i = 0$ (D_1 open) and $v_{D2}^i = 0$ (D_2 short).

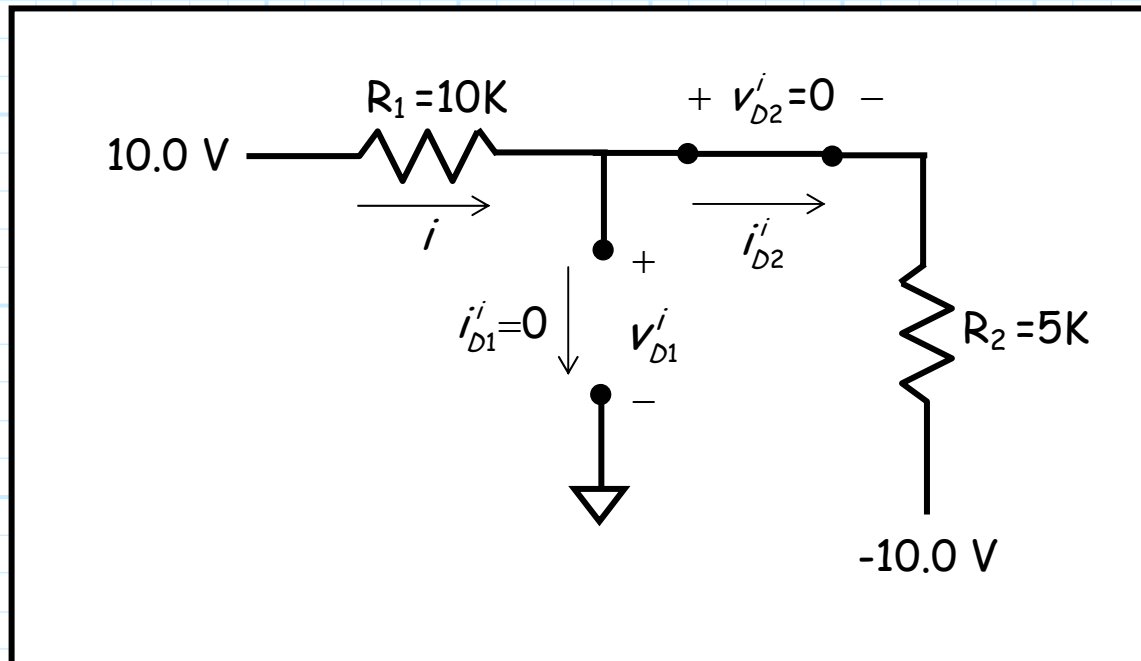Step 3: *ANALYZE* resulting circuit, and find v_{D1}^i and i_{D2}^i .



Note $i = i_{D2}^i =$

and from KVL:

$$\therefore v_D^i =$$

4) CHECK our assumptions.

$$i_{D2}^i =$$

$$v_{D1}^i =$$

\therefore Assumptions are **correct!** We are finished!



$$v_{D1}^i =$$

$$i_{D1}^i = 0$$

$$v_{D2}^i = 0$$

$$i_{D2}^i =$$