

10.3 CMOS Logic Gate Circuits

Reading Assignment: *pp. 963-974*

Q: Can't we build a more **complex** digital device than a simple digital inverter?

A:

HO: CMOS Device Structure

Q:

A: HO: Synthesis of CMOS Gates

HO: Examples of CMOS Logic Gates

Example: CMOS Logic Gate Synthesis


Example: Another CMOS Logic Gate Synthesis

CMOS Device Structure

For every CMOS device, there are essentially **two** separate circuits:


- 1) *The Pull-Up Network*
- 2) *The Pull-Down Network*

The basic **CMOS** structure is:

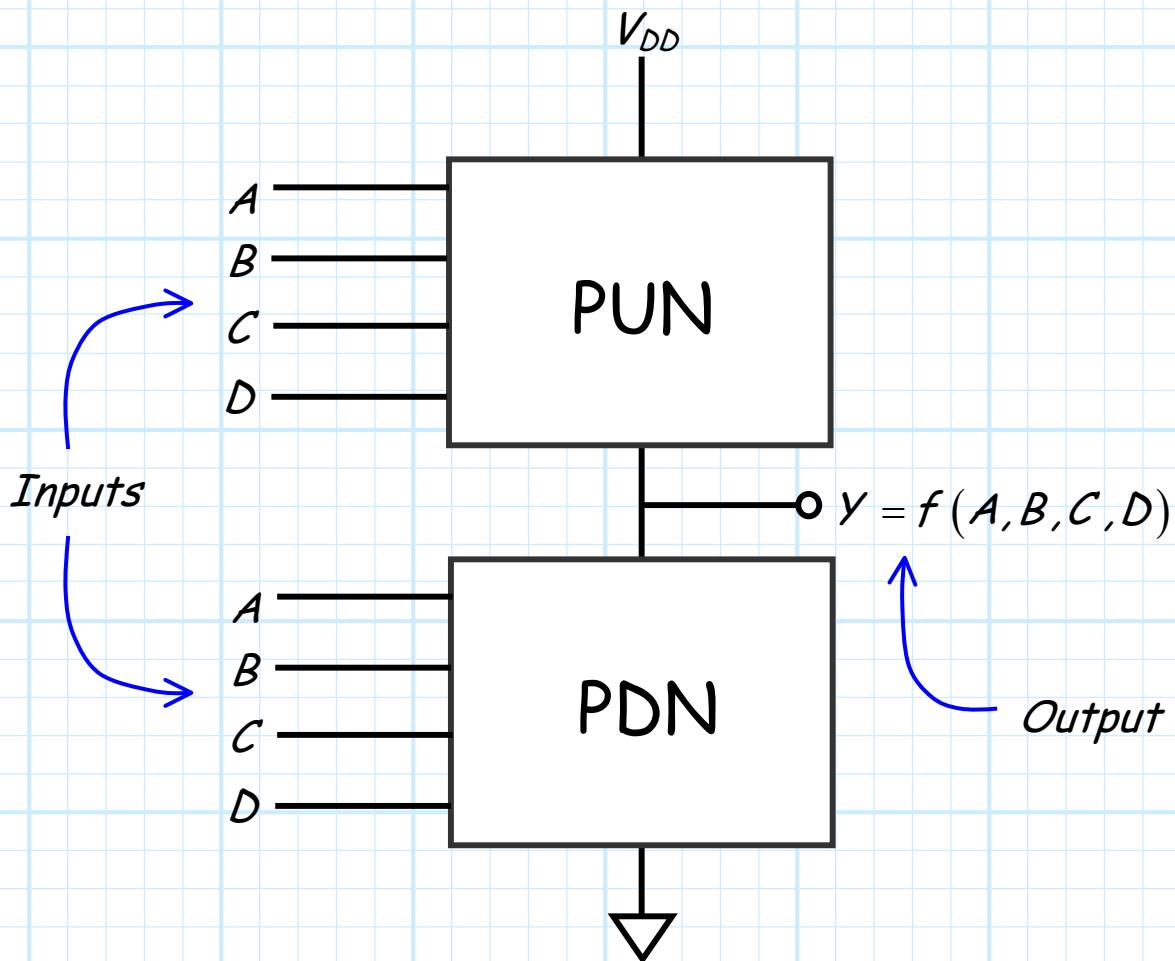


A CMOS logic gate **must** be in one of **two** states!

 State 1: PUN is open and PDN is conducting.




In this state,
the output is
LOW (i.e., $y=0$).

 State 2: PUN is conducting and PDN is open.




In this state,
the output is
HIGH (i.e., $y=1$).

 Thus, the PUN and the PDN essentially act as **switches**, connecting the output to **either** V_{DD} or to ground:



- * Note that the key to proper operation is that **one** switch must be closed, while the **other** must be open.
- * **Both** switches closed or **both** switches open would cause an **ambiguous** digital output!
- * To prevent this from occurring, the PDN and PUN must be **complementary** circuits.

 For example, consider the **CMOS inverter**:



For more **complex** digital CMOS gates (e.g., a 4-input OR gate), we find:

- 1) The PUN will consist of **multiple** inputs, therefore requires a circuit with **multiple PMOS** transistors.
- 2) The PDN will consist of **multiple** inputs, therefore requires a circuit with **multiple NMOS** transistors.

Synthesis of CMOS Gates

Let's consider the design synthesis of CMOS gates by considering the design synthesis of PUN and PDN separately.

PDN Design Synthesis

1. If the PDN is **conducting**, then the **output** will be **low**. Thus, we must find a Boolean expression for the **complemented output** \bar{Y} .


In turn, the PDN can only be conducting if **one or more** of the NMOS devices are **conducting**—and NMOS devices will be conducting (i.e., **triode mode**) when the **inputs are high** ($V_{GSN} = V_{DD}$).

Thus, we **must** express \bar{Y} in terms of **un-complemented inputs** A, B, C , etc (i.e., $\bar{Y} = f(A, B, C)$).

$$\text{e.g., } \rightarrow \bar{Y} = A + BC$$

This step may test our **Boolean algebraic** skills!

 
2. Then, we realize **AND** operations in $\bar{Y} = f(A, B, C)$ with **series NMOS** devices. E.G.:



Note that $Y=0$ if
both $A = V_{DD}$ **AND** $B = V_{DD}$.

$$\therefore \bar{Y} = AB$$

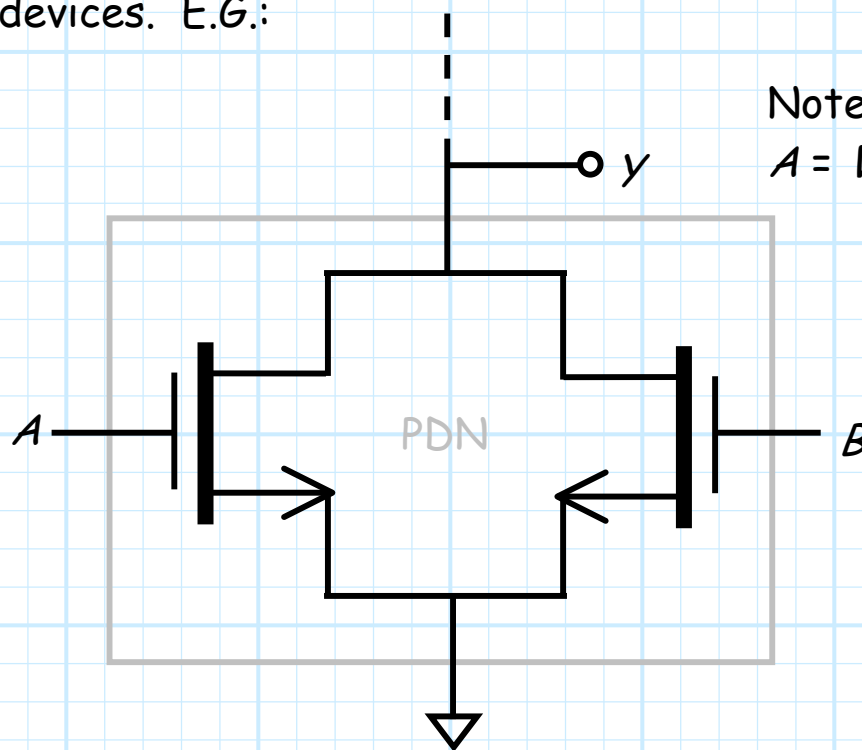3. Likewise, we realize **OR** operations with **parallel NMOS** devices. E.G.:



Note that $Y=0$ if **either**
 $A = V_{DD}$ **OR** $B = V_{DD}$.

$$\therefore \bar{Y} = A + B$$

PUN Design Synthesis

1. If the PUN is **conducting**, then the **output** will be **high**. Thus, we must find a Boolean expression for the **un-complemented output** Y .


In turn, the PUN can only be conducting if **one or more** of the PMOS devices are **conducting**—and PMOS devices will be conducting (i.e., **triode mode**) when the **inputs are low** ($V_{GSP} = -V_{DD}$).

Thus, we **must** express Y in terms of complemented inputs $\bar{A}, \bar{B}, \bar{C}$, etc (i.e., $Y = f(\bar{A}, \bar{B}, \bar{C})$).

$$\text{e.g., } \rightarrow Y = \bar{A} + \bar{B}\bar{C}$$

This step may test our **Boolean algebraic** skills!

 
2. Then, we realize **AND** operations with **series PMOS** devices. E.G.:



Note that $Y = V_{DD}$ if both $A = 0$ AND $B = 0$.

$$\therefore Y = \overline{A} \overline{B}$$

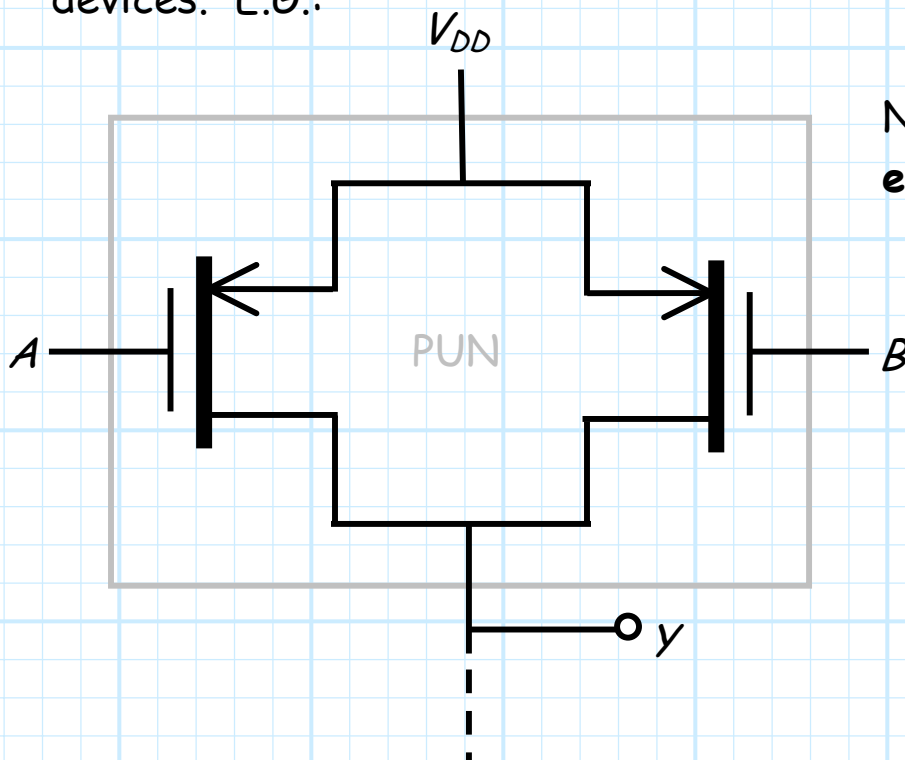3. Likewise, we realize **OR** operations with **parallel PMOS** devices. E.G.:




Note that $Y = V_{DD}$ if either $A = 0$ OR $B = 0$.


$$\therefore Y = \overline{A} + \overline{B}$$

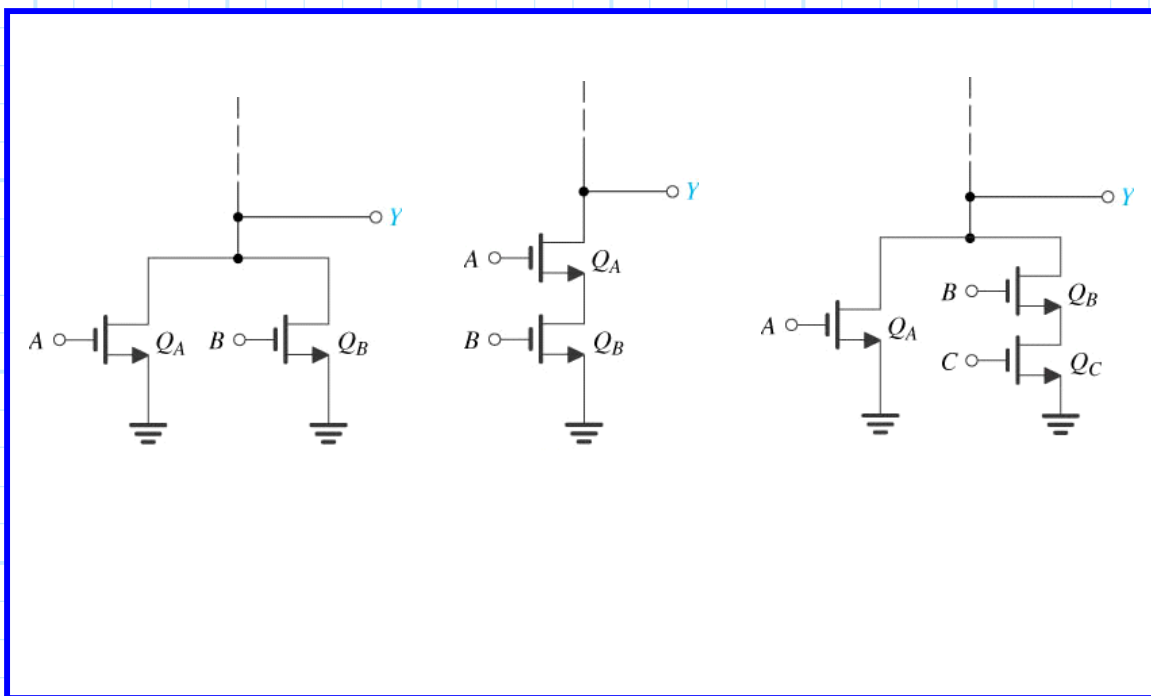Examples of CMOS Logic Gates


See if you can determine the **Boolean expression** that describes these **pull-down networks**:



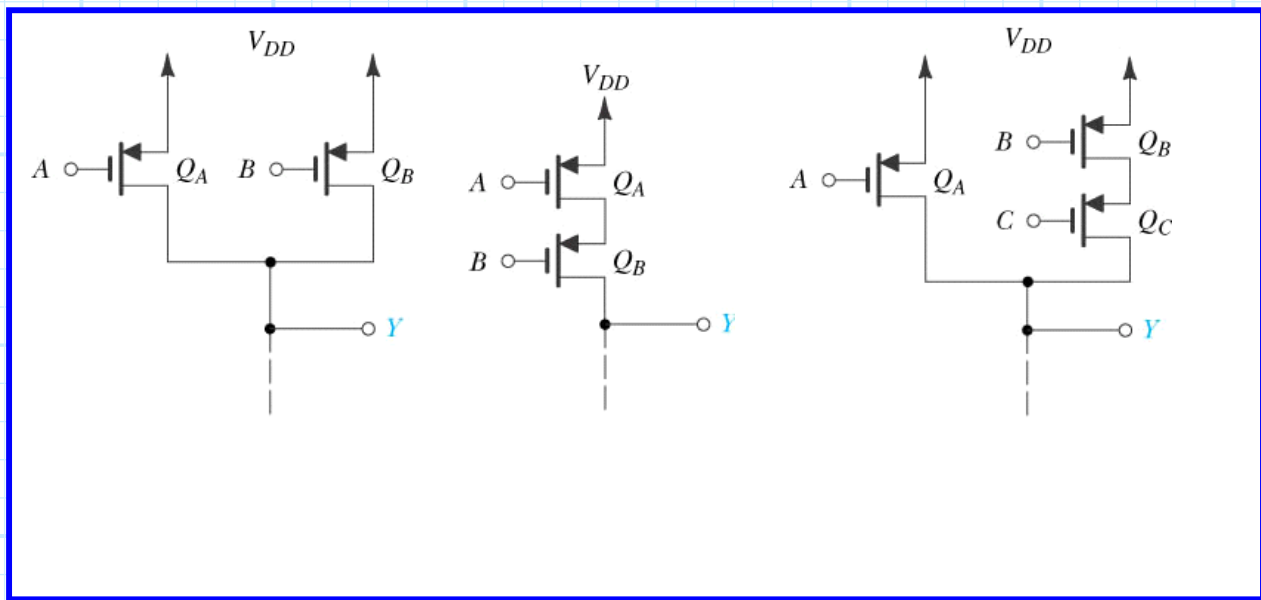See now if you can determine the **Boolean algebraic expression** for these **pull-up networks**:





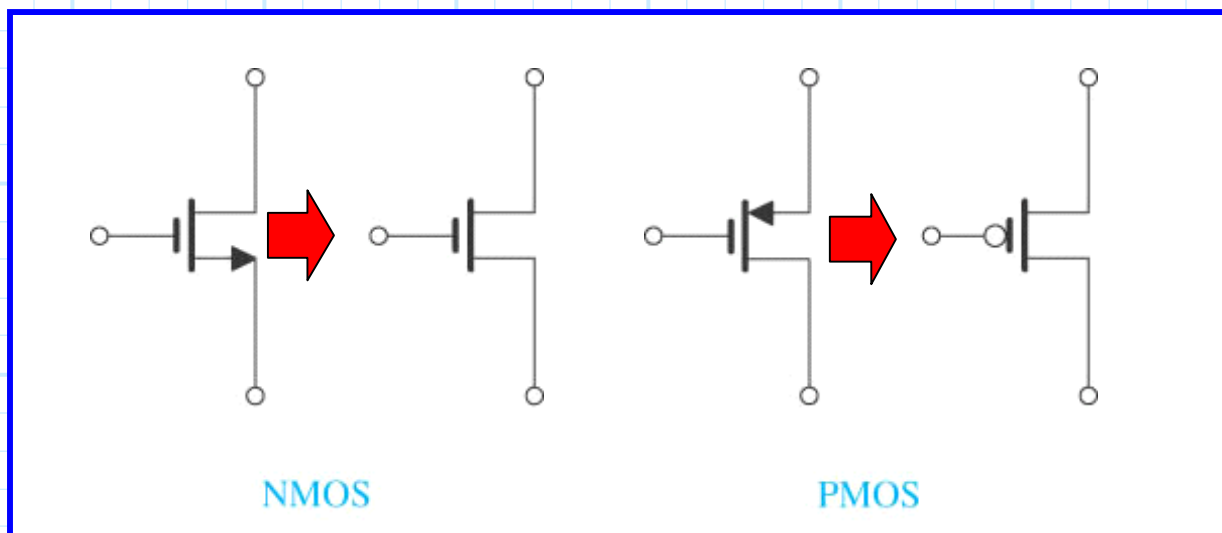
Now, we will make a simplifying change of symbols:



Effectively, these symbols represent the fact that we are now considering MOSFETs as **switches**, which can be placed either in an **open** state or a **conducting** state.

Note there are **two** kinds of "switches"—the ones that conduct when the input is high (i.e., **NMOS**) and ones that conduct when the input is low (i.e., **PMOS**).

And now consider **these** logic gates:

   

Note the PUN and the PDN for each of these circuits have **equivalent Boolean expressions** (make sure you see this!).

Example: CMOS Logic Gate Synthesis

Problem: Design a CMOS digital circuit that realizes the Boolean function:

$$Y = \overline{A + B + \overline{A} \overline{C}}$$


Solution: Follow the steps of the **design synthesis** handout!

Step1: Design the PDN

First, we must **rewrite** the Boolean function as:

$$\overline{Y} = f(A, B, C)$$

 In other words, write the **complemented output** in terms of **un-complemented inputs**.



*Time to recall our
Boolean algebra skills!*

We must first complement this equation, and then apply **DeMorgan's Theorem** (several times!).


$$\begin{aligned}
 Y &= \overline{A+B} + \overline{A} \overline{C} \\
 \overline{Y} &= \overline{\overline{A+B} + \overline{A} \overline{C}} \\
 &= \overline{(\overline{A+B})} \overline{(\overline{A} \overline{C})} \\
 &= (A+B) (\overline{\overline{A}} + \overline{\overline{C}}) \\
 &= (A+B) (A+C) \\
 &= AA + AC + BA + BC \\
 &= A(A+B+C) + BC \\
 &= A + BC
 \end{aligned}$$

Logically, this result says:



*Y is low if A is high, **OR** if both B **AND** C are high.*

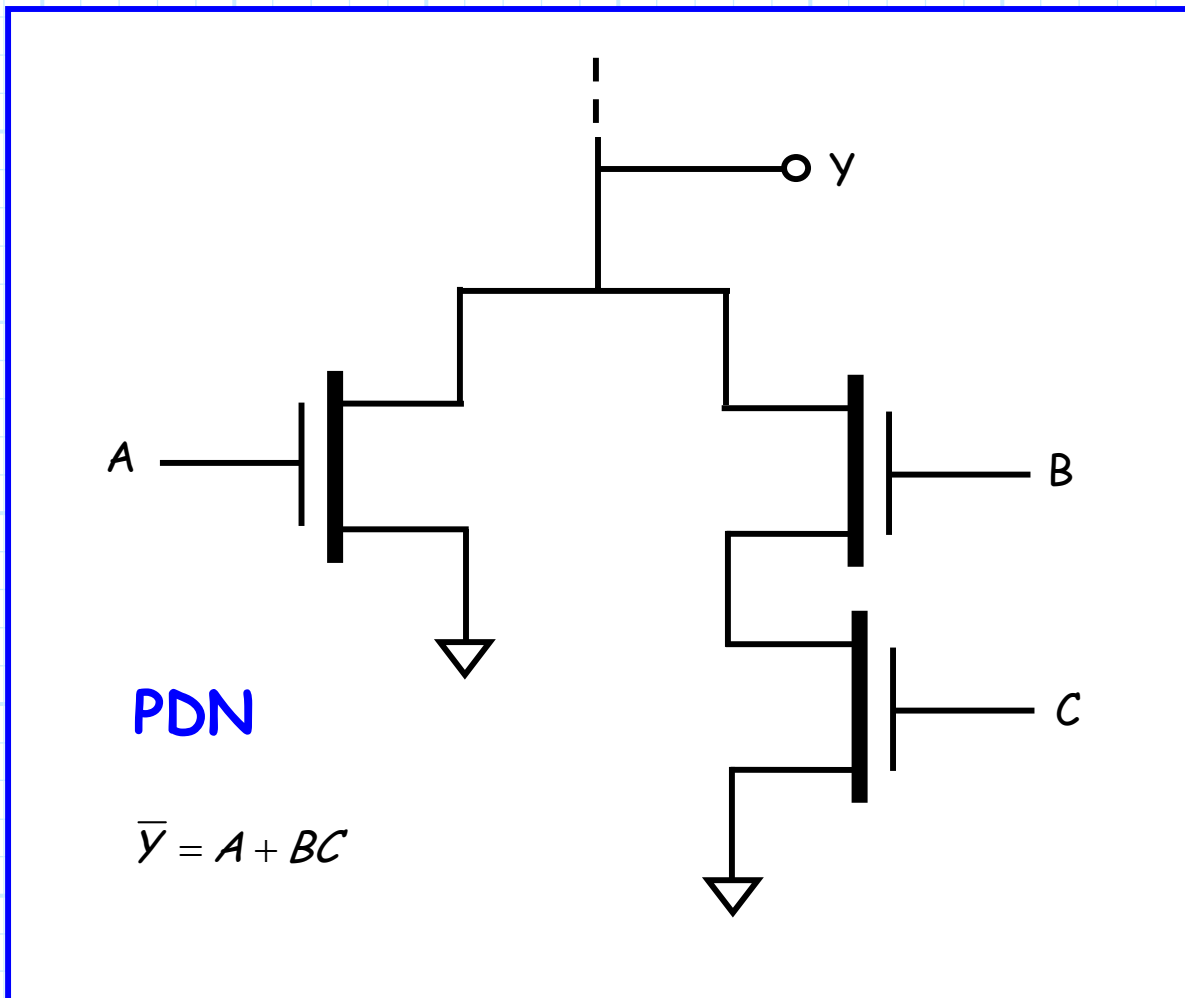We can thus realize this logic with the following **NMOS PDN**:



Step2: Design the PUN

First, we must **rewrite** the Boolean function as:


$$Y = f(\bar{A}, \bar{B}, \bar{C})$$

In other words, write the **un-complemented output** in terms of **complemented inputs**.


Again, using **DeMorgan's Theorem**:

$$\begin{aligned} Y &= \overline{A + B + \overline{A} \overline{C}} \\ &= \overline{A} \overline{B} + \overline{A} \overline{C} \\ &= \overline{A} (\overline{B} + \overline{C}) \end{aligned}$$


Logically, this result says:

 

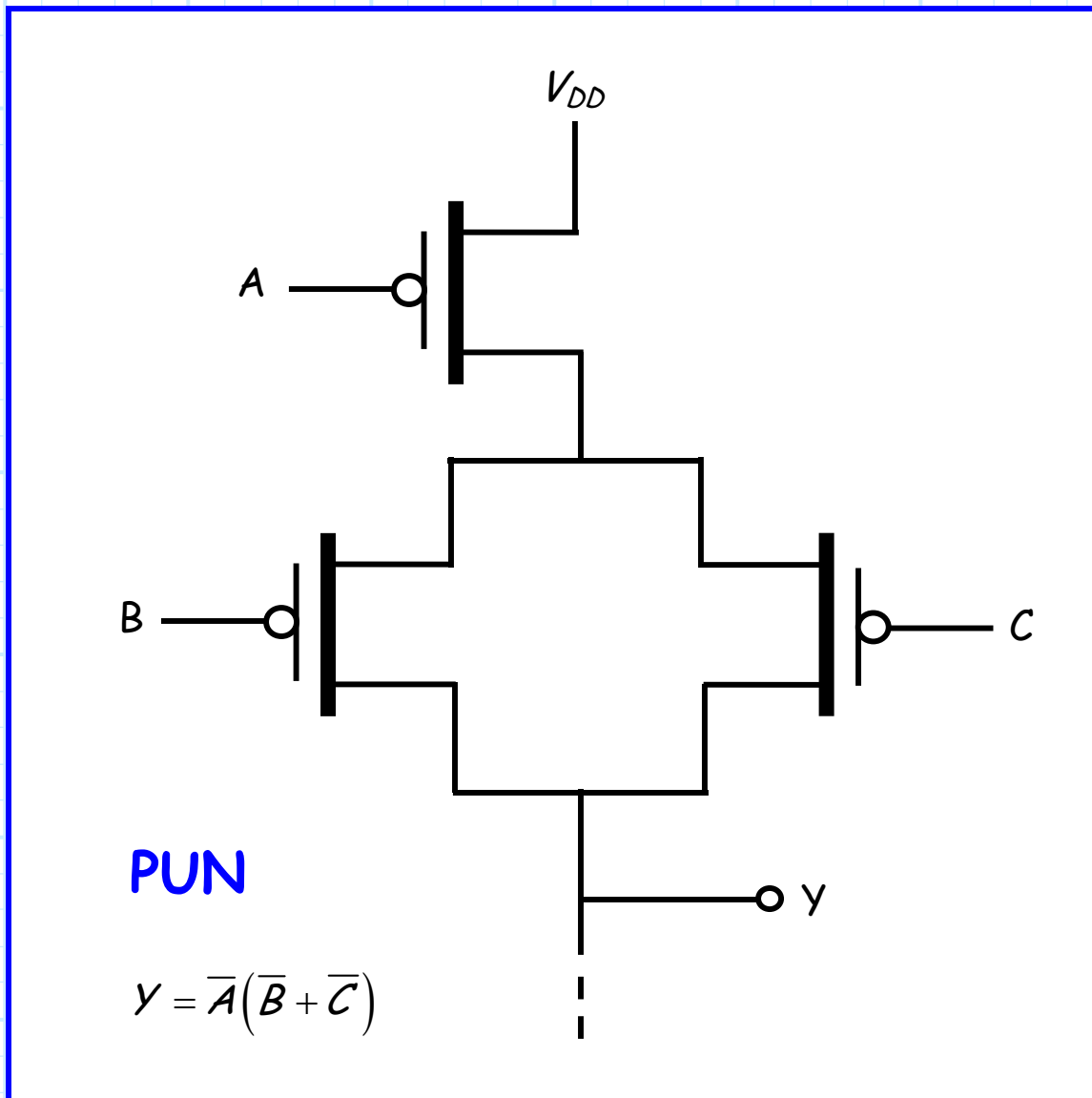We can thus realize this logic with the following **PMOS PUN**:



 Thus, the **entire** CMOS realization is:



Example: Another CMOS Logic Gate Synthesis

Now let's design a gate that realizes this Boolean algebraic expression:

$$Y = (\bar{A} + \bar{B})C$$

Step 1: Design PDN

First, let's rewrite Boolean expression as $\bar{Y} = f(A, B, C)$:

$$Y = (\bar{A} + \bar{B})C$$

$$\bar{Y} = \overline{(\bar{A} + \bar{B})C}$$

$$\bar{Y} = \overline{(\bar{A} + \bar{B})} + \bar{C}$$

$$\bar{Y} = AB + \bar{C}$$

Q: *Yikes! We cannot write this expression explicitly in terms of uncomplemented inputs A, B, and C! The input C appears as \bar{C} in the expression. What do we do now?*

A: An easy problem to solve! We can essentially make a substitution of variables:

$$C' = \bar{C}$$

And thus:

$$\bar{Y} = AB + C'$$

Therefore, the inputs to this logic gate should be A, B, and C' (i.e, A, B, and the complement of C).


Note that this Boolean expression "says" that:

"The output is low if either, A AND B are both high, OR C' is high"

Of course another way of "saying" this is:

"The output is low if either A AND B are both high, OR C is low"

The PDN is therefore:

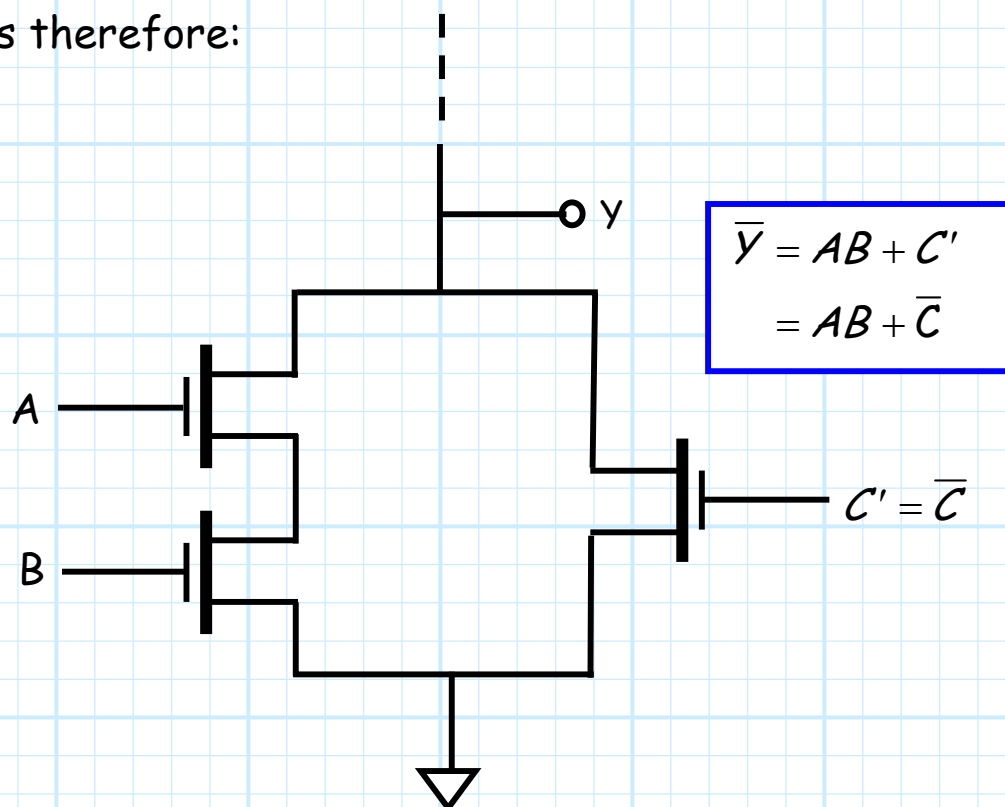

Step 2: Design the PUN

Note we have a similar problem as before—the expression for Y **cannot** explicitly be written in terms of complemented inputs \bar{A} , \bar{B} , and \bar{C} :

$$Y = (\bar{A} + \bar{B})C$$

Note we can again solve this problem by using the same substitution of variable C :

$$C' = \bar{C}$$

$$\bar{C}' = C$$

Therefore:

$$\begin{aligned} Y &= (\bar{A} + \bar{B})\bar{C}' \\ &= (\bar{A} + \bar{B})C \end{aligned}$$

This expression “says” that:

“The output will be high if, either A OR B are low, AND C is **low**”

Which is equivalent to saying:

“The output will be high if, either A OR B are low, AND C is **high**”

The CMOS digital logic device is therefore:

