

10.4 NMOS Logic Design

Reading Assignment: 974-980

An alternative to CMOS logic is **NMOS logic**.

Q:


A: HO: NMOS Logic Circuits

HO: The Depletion Load

HO: The Pseudo-NMOS Load

NMOS Logic Circuits

 An alternative way to construct a digital logic gate is to simply use a single **large resistor** as the pull-up network!



If the PDN is **open**, no current will flow ($i_R = 0$), and thus there will be **no** voltage drop across the **Pull-Up Resistor R** —the output will be **high**, **just** like before!

But, if the PDN is conducting, current **will** flow ($i_R \neq 0$), and thus there **will** be a large voltage drop across R —the output will be **low** (sort of)!

This method of constructing digital devices is called **NMOS logic** (for hopefully **obvious** reasons!).

Q: *Why would we want use NMOS logic?*

A: Replacing the PUN with a single resistor greatly **simplifies** and **shrinks** the circuit. For complex gates (i.e., gates with **many** inputs), we can reduce the number of required devices (transistors and resistors) by **nearly half!**

Q: *Yikes! This seems to be a lot better. Why wouldn't we always use NMOS logic?*

A: There are **two** really big problems with NMOS logic (at least, when compared to **CMOS**):

1. Since current flows when the output is low, the static power dissipation is **not zero**.
2. Since current flows when the output is low, V_{OL} is **not** equal to its ideal value of **zero** (i.e., $V_{OL} \neq 0$)!


Additionally, there is **one more** problem when implementing NMOS in **integrated circuits**. IC resistors are (relatively) very large and difficult to construct.

→ This problem, though, is easily solved—we replace the **pull-up resistor** with an **active load**.

The Depletion Load

Say we connect the gate of a **depletion** NMOS to its source—we now have a **two-terminal device**!

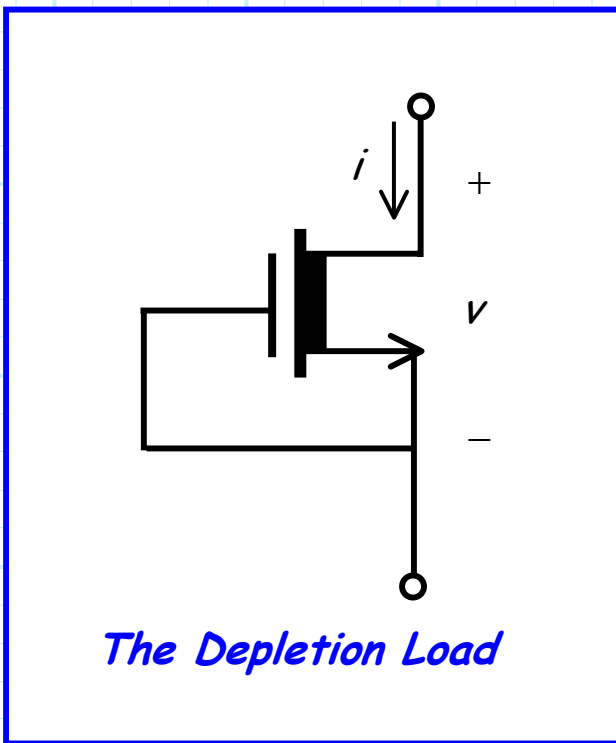This device is called a **depletion load**.



Since the depletion load is a two-terminal device, its **behavior** is defined by the relationship between the **voltage** v across the device and the **current** i through it.


For example, a **resistor** is a two terminal device whose behavior (i.e., its relationship between i and v) is defined by **Ohm's Law** ($i = v/R$).

Although the **depletion load** is decidedly **not** a resistor, its i - v relationship does have **some** similarities with Ohm's Law.

Q: So what is "Ohm's Law" for a **depletion load** (i.e., what is $i = f(v)$)?

A: A result easily found by implementing our knowledge of depletion MOSFETs!

For a depletion load, we find that:

 

Q: But since $v_{GS} = 0$, isn't the NMOS device in *cutoff*?

A: **Nope!** Notice that this is a depletion MOSFET, and a depletion MOSFET **will** conduct when $v_{GS} = 0$!

Thus the MOSFET in a depletion load will always be either in:
a) triode or **b)** saturation.

a) Depletion load MOSFET is in **triode** if:

$$\begin{aligned}
 v_{DS} &< v_{GS} - V_t \\
 v &< 0 - V_t \\
 v &< -V_t
 \end{aligned}$$

Therefore, the **current** will be:

$$i_D = K \left[2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right]$$

$$i = K \left[2(0 - V_t)v - v^2 \right]$$

$$i = K \left[-2V_t v - v^2 \right]$$

b) Depletion load MOSFET is in **saturation** if:

$$v_{DS} > v_{GS} - V_t$$

$$v > 0 - V_t$$

$$v > -V_t$$

Therefore, the **current** will be:

$$i_D = K(v_{GS} - V_t)^2 + \frac{v_{DS}}{r_o}$$

$$i = K(0 - V_t)^2 + \frac{v}{r_o}$$

$$i = K(-V_t)^2 + \frac{v}{r_o}$$

$$i = K V_t^2 + \frac{v}{r_o}$$




**Channel-Length
Modulation!**

where in this case:


$$r_o = \frac{1}{\lambda K (v_{GS} - V_t)^2} = \frac{1}{\lambda K (0 - V_t)^2} = \frac{1}{\lambda V_t^2}$$

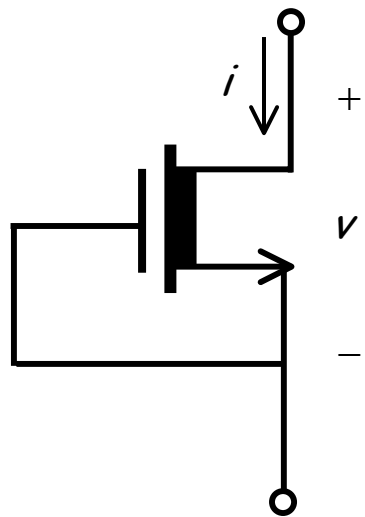Combining the two results, we find that "Ohm's Law" for a depletion load is:



$$i = \begin{cases} K[-2V_t v - v^2] & \text{if } 0 < v < -V_t \\ KV_t^2 + \frac{v}{r_o} & \text{if } v > -V_t \end{cases}$$

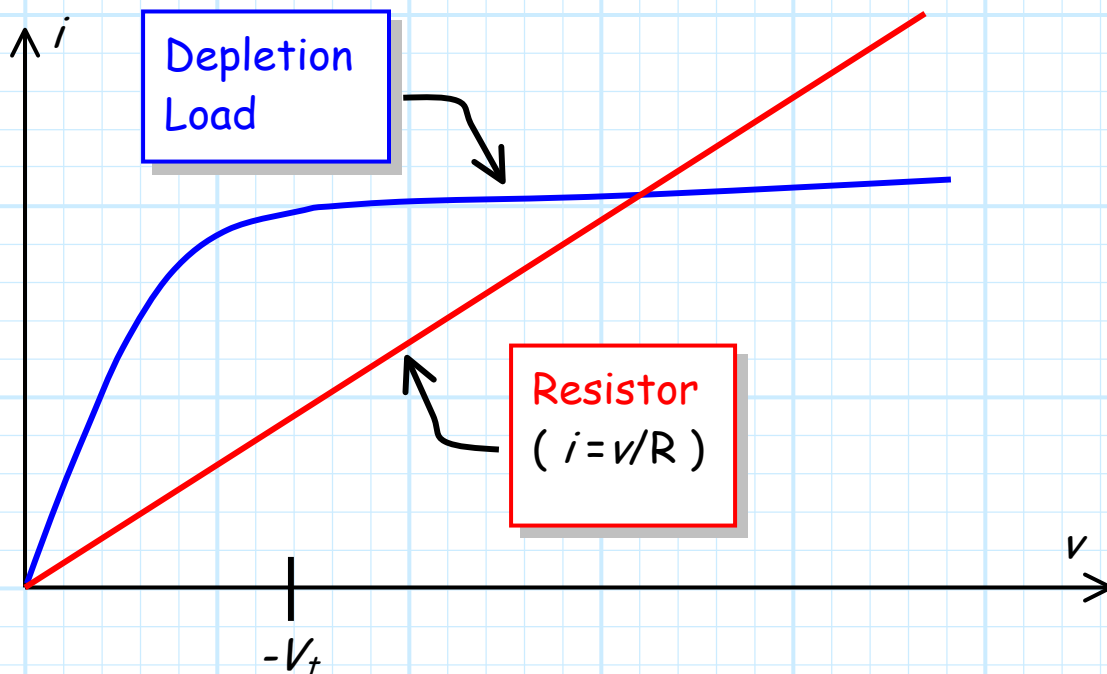
Plotting this function, we find something like this:



Note that the behavior of a Depletion Load and a resistor are **very different**—however they are precisely the **same** in two key ways:

 1. When the voltage across each device (i.e., resistor and depletion load) is **zero**, the current through each device is likewise **zero** (and vice versa!).
2. As the voltage across each device **increases**, the current through each device **increases**.

As a result, we can use a depletion load as the “**pull-up resistor**” in our integrated circuit NMOS logic!




The Pseudo-NMOS Load

There is another type of active load that is used for NMOS logic, but this load is made from a **PMOS** transistor!

Hence, NMOS logic that uses this load is referred to as **Pseudo NMOS Logic**, since not all of the devices in the circuit will be NMOS (the load will be **PMOS**!).

 We therefore call this load the "**Pseudo NMOS Load**", since it is the load used in **Pseudo NMOS logic**. But, keep in mind that the **pseudo NMOS load** is made from a **PMOS** device (this can cause great confusion!).



$$\begin{aligned}
 i_D &= i \\
 V_{GS} &= 0 - V_{DD} = -V_{DD} \\
 V_{DS} &= -V \\
 V_{GS} - V_t &= -(V_{DD} + V_t)
 \end{aligned}$$

The Pseudo-NMOS Load

Note that $v_{GS} = -V_{DD} < V_t$, so that the load is **not** in cutoff—it can either be in **saturation** or **triode**.

The PMOS will be in **triode** if:

$$\begin{aligned}v_{DS} &> v_{GS} - V_t \\ -v &> -(V_{DD} + V_t) \\ v &< (V_{DD} + V_t)\end{aligned}$$

In which case the **current** is:

$$\begin{aligned}i_D &= K \left[2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right] \\ i &= K \left[-2(V_{DD} + V_t)(-v) - (-v)^2 \right] \\ i &= K \left[2(V_{DD} + V_t)v - v^2 \right]\end{aligned}$$

Likewise, the PMOS will be in **saturation** if:

$$\begin{aligned}v_{DS} &< v_{GS} - V_t \\ -v &< -(V_{DD} + V_t) \\ v &> (V_{DD} + V_t)\end{aligned}$$



In which case the **current** is:


$$\begin{aligned}i_D &= K (v_{GS} - V_t)^2 - \frac{v_{DS}}{r_o} \\ i &= K (V_{DD} + V_t)^2 + \frac{v}{r_o}\end{aligned}$$

where in this case:

$$r_o = \frac{1}{\lambda K (v_{GS} - V_t)^2} = \frac{1}{\lambda K (V_{DD} + V_t)^2}$$

  Combining these two results, we find that the pseudo NMOS load behaves very much like the depletion load:



 

*A Pseudo-NMOS
Logic Example*