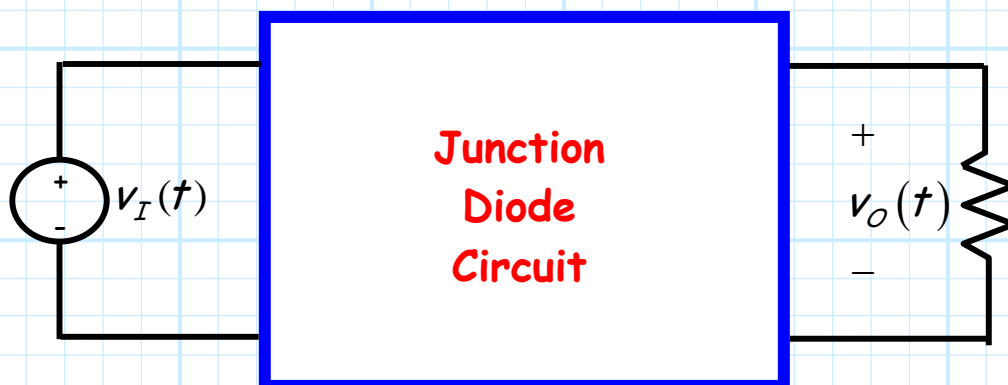


## 3.5 Rectifier Circuits

**Reading Assingment:** pp. 171-177 (i.e., neglect sections 3.5.4, and 3.5.5)

### A. Junction Diode 2-Port Networks

Consider when junction diodes appear in a 2-port network (i.e., a circuit with an **input** and an **output**).



### HO: The Transfer Function of Diode Circuits

Q:

A: HO: Steps for finding a Junction Diode Circuit Transfer Function

## Example: Diode Circuit Transfer Function

### B. Diode Rectifiers

#### HO: Signal Rectification



Q:

A: { HO: The Full-Wave Rectifier  
HO: The Bridge Rectifier

#### HO: Peak Inverse Voltage
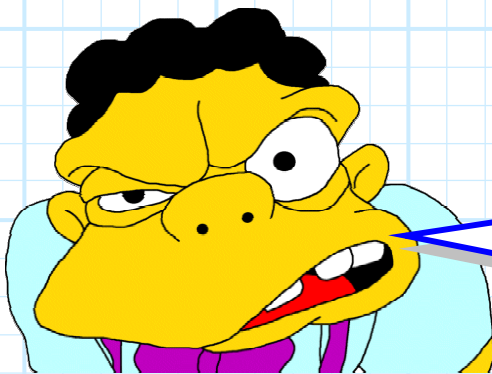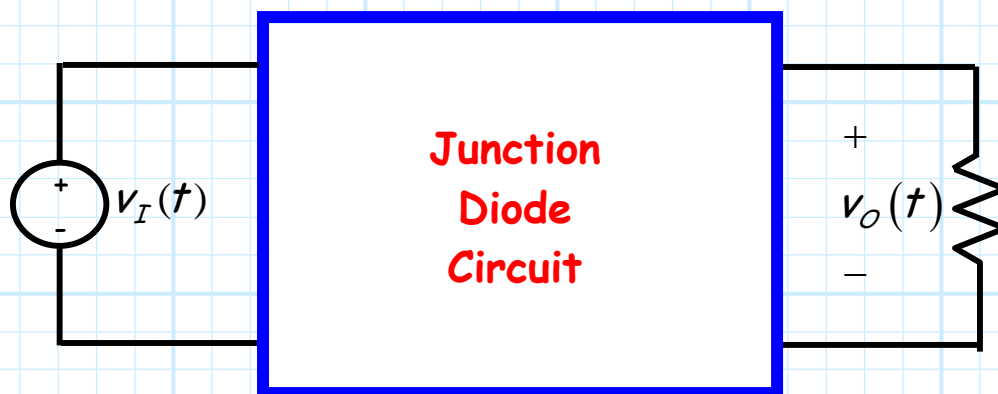
# The Transfer Function of Diode Circuits

For many junction diode circuits, we find that one of the voltage sources is in fact **unknown**! This unknown voltage is typically some **input** signal of the form  $v_I(t)$ , which results in an output voltage  $v_O(t)$ .



**Q:** *How the heck do you expect us to determine  $v_O(t)$  if we have **no idea** what  $v_I(t)$  is??*

**A:** We of course cannot determine an **explicit** value or expression for  $v_O(t)$ , since it **depends** on the input  $v_I(t)$ . Instead, we will attempt to explicitly determine this **dependence** of  $v_O(t)$  on  $v_I(t)$ !

In other words, we seek to find an expression for  $v_O$  in **terms** of  $v_I$ . Mathematically speaking, our goal is to determine the **function**:


$$v_O = f(v_I)$$

We refer to this as the **circuit transfer function**.

Note that we can **plot** a circuit transfer function on a 2-dimensional plane, just as if the function related values  $x$  and  $y$  (e.g.  $y = f(x)$ ). For **example**, say our circuit transfer function is:

$$\begin{aligned} v_O &= f(v_I) \\ &= 3v_I + 2 \end{aligned}$$

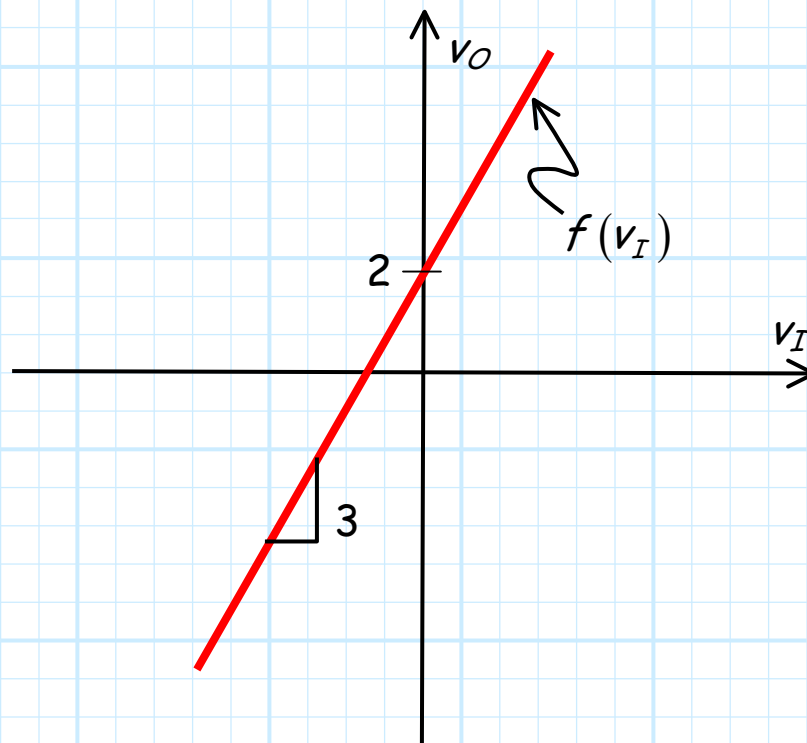Note this is simply the **equation of a line** (e.g.,  $y = 3x + 2$ ), with slope  $m=3$  and intercept  $b=2$ .



**Q:** A "function" eh? Isn't a "function" just your annoyingly pretentious way of saying we need to find some mathematic equation relating  $v_O$  and  $v_I$ ?





**A:** Actually **no!** Although a function is a mathematical equation, there are in fact **scads** of equations relating  $v_O$  and  $v_I$  that are **not** functions!

→ The set of all possible functions  $y = f(x)$  are a **subset** of the set of all possible equations relating  $y$  and  $x$ .



A **function**  $v_O = f(v_I)$  is a mathematical expression such that for **any** value of  $v_I$  (i.e.,  $-\infty < v_I < \infty$ ), there is **one**, but **only one**, value  $v_O$ .

Note this definition of a function is consistent with our **physical** understanding of circuits—we can place **any** voltage on the input that we want (i.e.,  $-\infty < v_I < \infty$ ), and the result will be **one** specific voltage value  $v_O$  on the output.

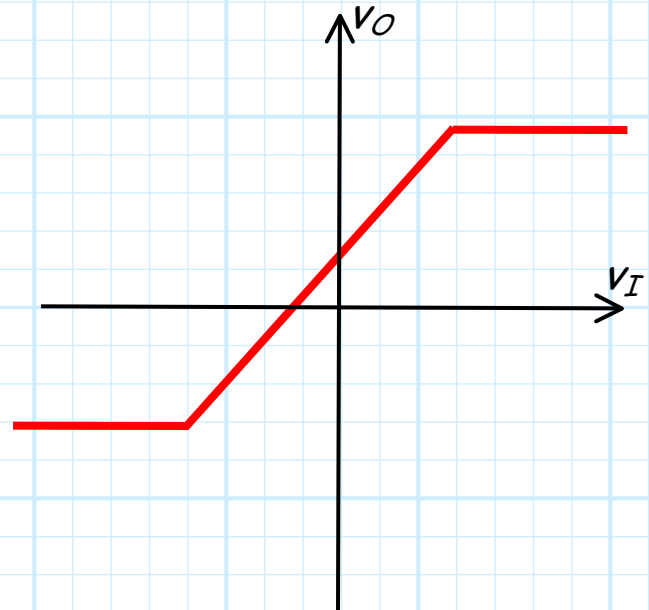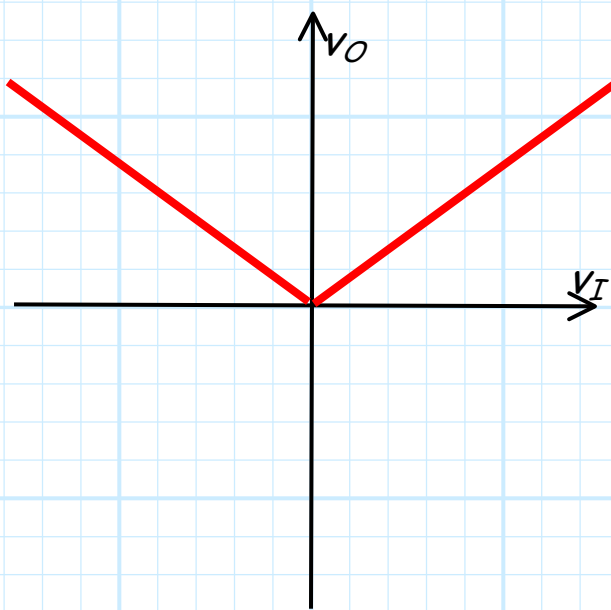
Therefore, examples of **valid** circuit transfer **functions** include:



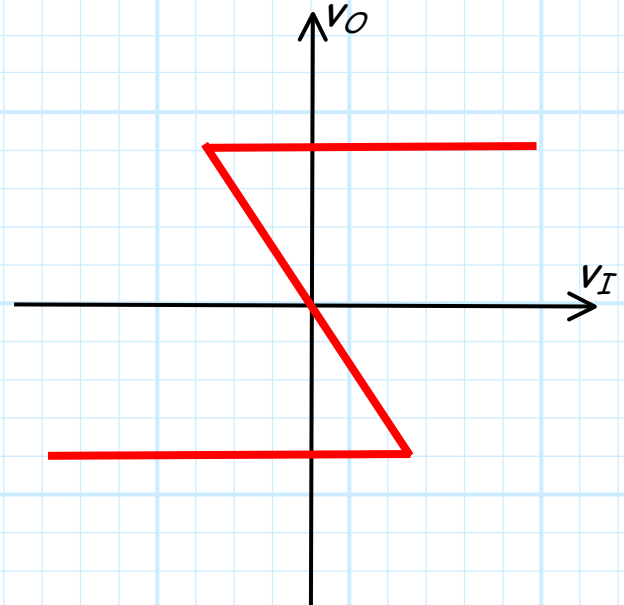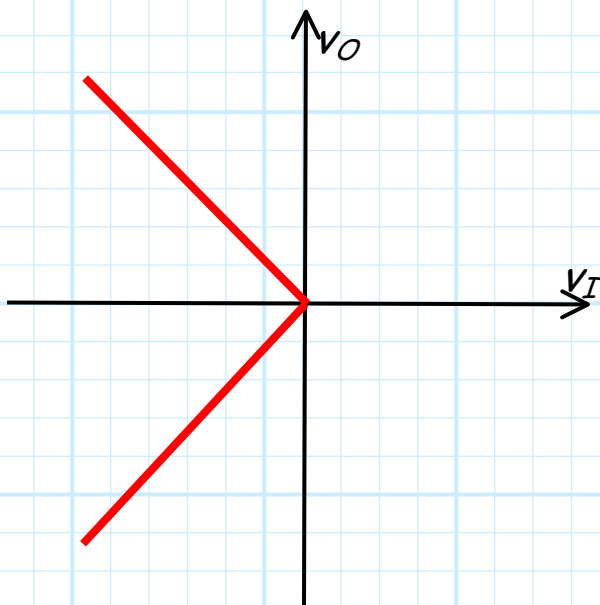
Conversely, the transfer "functions" **below** are **invalid**—they **cannot** represent the behavior of circuits, since they are **not** functions!



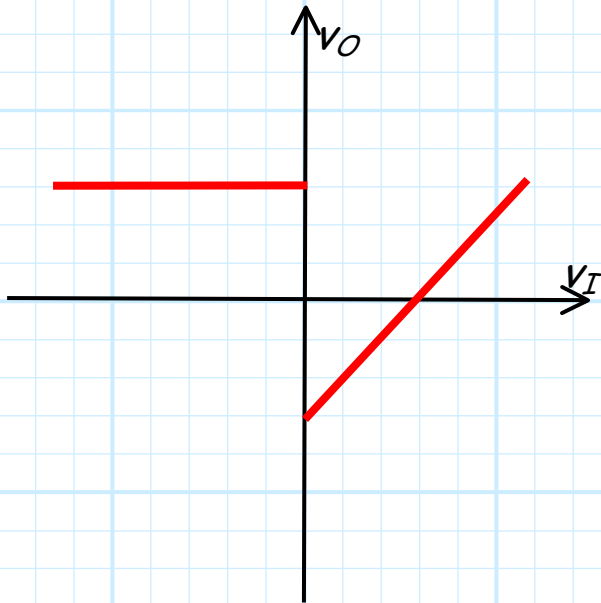Moreover, we find that **circuit** transfer functions must be **continuous**. That is,  $v_O$  **cannot** "instantaneously change" from one value to another as we increase (or decrease) the value  $v_I$ .



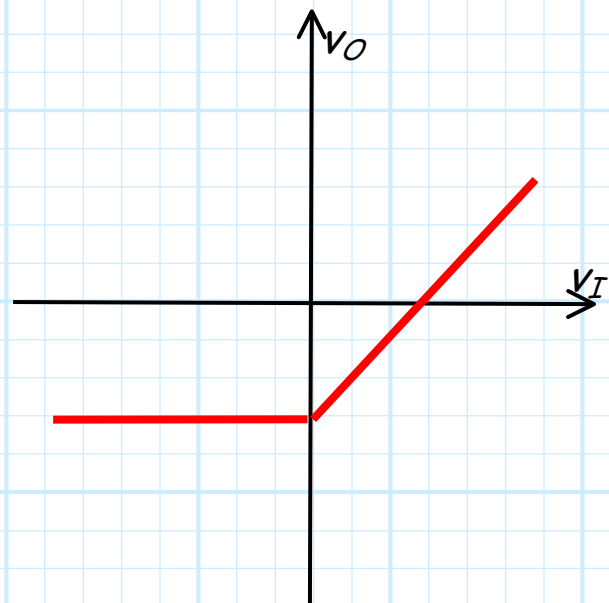**A Discontinuous  
Function**  
(*Invalid circuit  
transfer function*)



**A Continuous  
Function**  
(*Valid circuit  
transfer function*)



*Remember, the transfer function of **every** junction diode circuit must be a **continuous function**. If it is **not**, you've done something **wrong**!*

# Steps for Finding a Junction Diode Circuit Transfer Function

Determining the **transfer function** of a junction diode circuit is in many ways **very similar** to the analysis steps we followed when analyzing previous junction diode circuits (i.e., circuits where all sources were **explicitly known**).

However, there are also some **important differences** that we must understand completely if we wish to successfully determine the **correct transfer function!**

**Step 1:** *Replace all junction diodes with an appropriate junction diode model.*

**Just like before!** We will now have an **IDEAL** diode circuit.

**Step 2:** *ASSUME some mode for all ideal diodes.*

**Just like before!** An **IDEAL** diode can be either forward or reverse biased.



### Step 3: ENFORCE the bias assumption.

**Just** like before! ENFORCE the bias assumption by replacing the ideal diode with short circuit or open circuit.

### Step 4: ANALYZE the remaining circuit.

Sort of, kind of, like before!

1. If we assumed an IDEAL diode was forward biased, we must determine  $i_D^i$ --**just** like before! However, **instead** of finding the numeric value of  $i_D^i$ , we determine  $i_D^i$  as a **function** of the unknown source (e.g.,  $i_D^i = f(v_I)$ ).

2. Or, if we assumed an IDEAL diode was reversed biased, we must determine  $v_D^i$ --**just** like before! However, **instead** of finding the numeric value of  $v_D^i$ , we determine  $v_D^i$  as a **function** of the unknown source (e.g.,  $v_D^i = f(v_I)$ ).

3. Finally, we must determine all the **other** voltages and/or currents we are interested in (e.g.,  $v_O$ )--**just** like before! However, **instead** of finding its numeric value, we determine it as a **function** of the unknown source (e.g.,  $v_O = f(v_I)$ ).

**Step 5:** Determine *WHEN* the assumption is valid.

**Q:** OK, we get the picture. Now we have to **CHECK** to see if our **IDEAL** diode assumption was correct, right?



**A:** Actually, **no!** This step is **very different** from what we did before!

We **cannot** determine **IF**  $i_D^i > 0$  (forward bias assumption), or **IF**  $v_D^i < 0$  (reverse bias assumption), since we **cannot** say for certain what the value of  $i_D^i$  or  $v_D^i$  is!

Recall that  $i_D^i$  and  $v_D^i$  are **functions** of the unknown voltage source (e.g.,  $i_D^i = f(v_I)$  and  $v_D^i = f(v_I)$ ). Thus, the values of  $i_D^i$  or  $v_D^i$  are **dependent** on the unknown source ( $v_I$ , say). For **some** values of  $v_I$ , we will find that  $i_D^i > 0$  or  $v_D^i < 0$ , and so our assumption (and thus our solution for  $v_O = f(v_I)$ ) will be **correct**

**However**, for **other** values of  $v_I$ , we will find that  $i_D^i < 0$  or  $v_D^i > 0$ , and so our assumption (and thus our solution for  $v_O = f(v_I)$ ) will be **incorrect!**



**Q:** Yikes! What do we do? How can we determine the circuit transfer function if we can't determine **IF** our ideal diode assumption is correct??

**A:** Instead of determining **IF** our assumption is correct, we must determine **WHEN** our assumption is correct!

In other words, we must determine for **what values** of  $v_I$  is  $i_D^i > 0$  (forward bias), or for **what values** of  $v_I$  is  $v_D^i < 0$  (reverse bias).

We can do this since we earlier (in step 4) determined the function  $i_D^i = f(v_I)$  or the function  $v_D^i = f(v_I)$ .

Perhaps this step is best explained by an **example**. Let's say we assumed that our ideal diode was **forward biased** and, say we determined (in step 4) that  $v_O$  is related to  $v_I$  as:

$$\begin{aligned}v_O &= f(v_I) \\ &= 2v_I - 3\end{aligned}$$

Likewise, say that we determined (in step 4) that our ideal diode current is related to  $v_I$  as:

$$\begin{aligned}i_D^i &= f(v_I) \\ &> \frac{v_I - 5}{4}\end{aligned}$$

Thus, in order for our forward bias assumption to be **correct**, the function  $i_D^i = f(v_I)$  must be **greater than zero**:

$$i_D^i > 0$$

$$f(v_I) > 0$$

$$\frac{v_I - 5}{4} > 0$$

We can now "solve" this **inequality** for  $v_I$ :

$$\frac{v_I - 5}{4} > 0$$

$$v_I - 5 > 0$$

$$v_I > 5$$

**Q:** What does *this* mean? Does it mean that  $v_I$  is some value **greater than 5.0V**??



**A:** **NO!** Recall that  $v_I$  can be **any** value. What the inequality above means is that  $i_D^i > 0$  (i.e., the ideal diode is forward biased) **WHEN**  $v_D^i > 5.0$ .

Thus, we know  $v_O = 2v_I - 3$  is valid **WHEN** the ideal diode is forward biased, and the ideal diode is forward biased **WHEN** (for this example)  $v_D^i > 5.0$ . As a result, we can mathematically state that:

$$v_O = 2v_I - 3 \quad \text{when} \quad v_I > 5.0 \text{ V}$$

**Conversely**, this means that if  $v_I < 5.0$  V, the **ideal** diode will be **reverse biased**—our forward bias assumption would **not** be valid, and thus our expression  $v_O = 2v_I - 3$  is **not** correct ( $v_O \neq 2v_I - 3$  for  $v_I < 5.0$  V)!

**Q:** So how do we determine  $v_O$  for values of  $v_I < 5.0$  V?



**A:** Time to move to the **last** step!

**Step 6:** *Change assumption and repeat steps 2 through 5!*

For our **example**, we would change our bias assumption and now **ASSUME** reverse bias. We then **ENFORCE**  $i_D' = 0$ , and then **ANALYZE** the circuit to find both  $v_D' = f(v_I)$  and a **new** expression  $v_O = f(v_I)$  (it will **no longer** be  $v_O = 2v_I - 3$ !).


We then determine **WHEN** our reverse bias assumption is valid, by solving the **inequality**  $v_D' = f(v_I) > 0$  for  $v_I$ . For the example used here, we would find that the **IDEAL** diode is reverse biased **WHEN**  $v_I < 5.0$  V.

For junction diode circuits with **multiple** diodes, we may have to repeat this entire process **multiple** times, until **all possible** bias conditions are analyzed.

If we have done our analysis **properly**, the result will be a valid **continuous function**! That is, we will have an expression (but only **one** expression) relating  $v_O$  to **all** possible values of  $v_I$ .


This transfer function will typically be **piecewise linear**. An **example** of a piece-wise linear transfer function is:
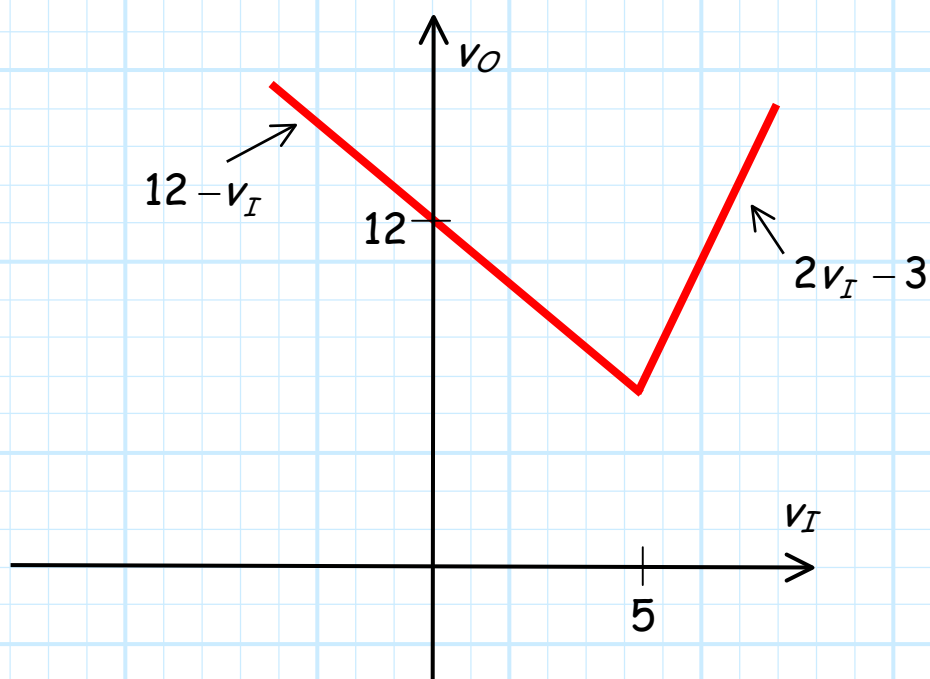
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 5.0 \\ 12 - v_I & \text{for } v_I < 5.0 \end{cases}$$




Just to make **sure** that we understand what a function is, note that the following expression is **not** a function:
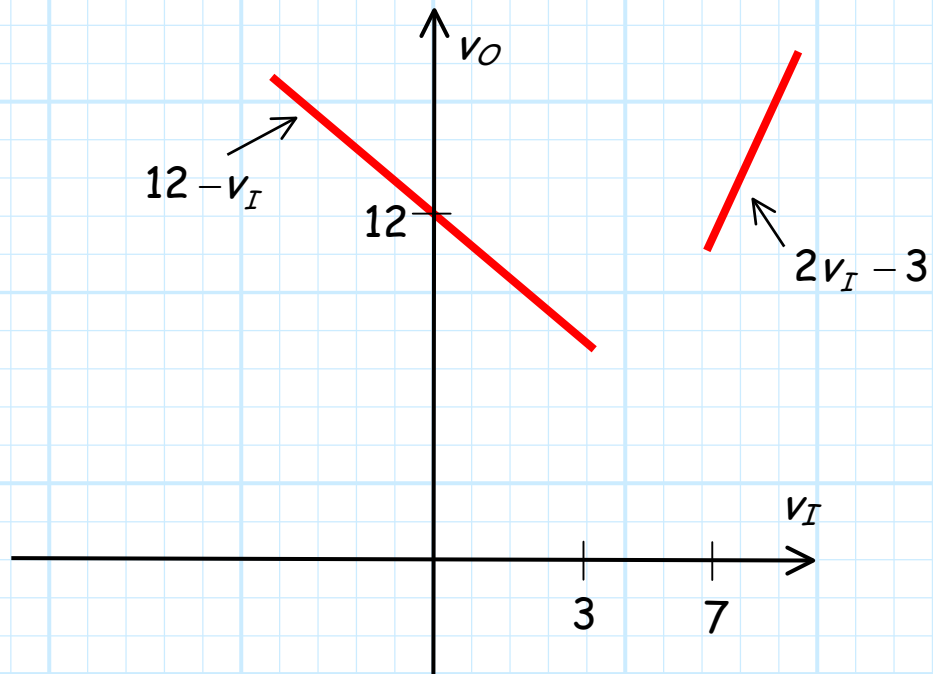
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 7.0 \\ 12 - v_I & \text{for } v_I < 3.0 \end{cases}$$




Nor is this expression a function:
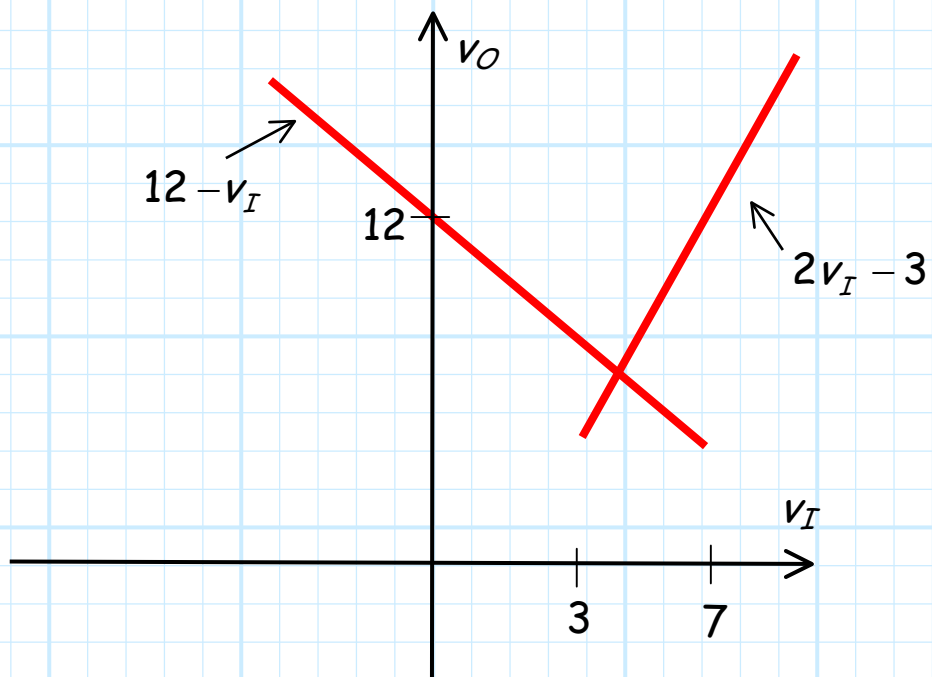
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 3.0 \\ 12 - v_I & \text{for } v_I < 7.0 \end{cases}$$



Finally, note that the following expression is a function, but it is **not continuous**:
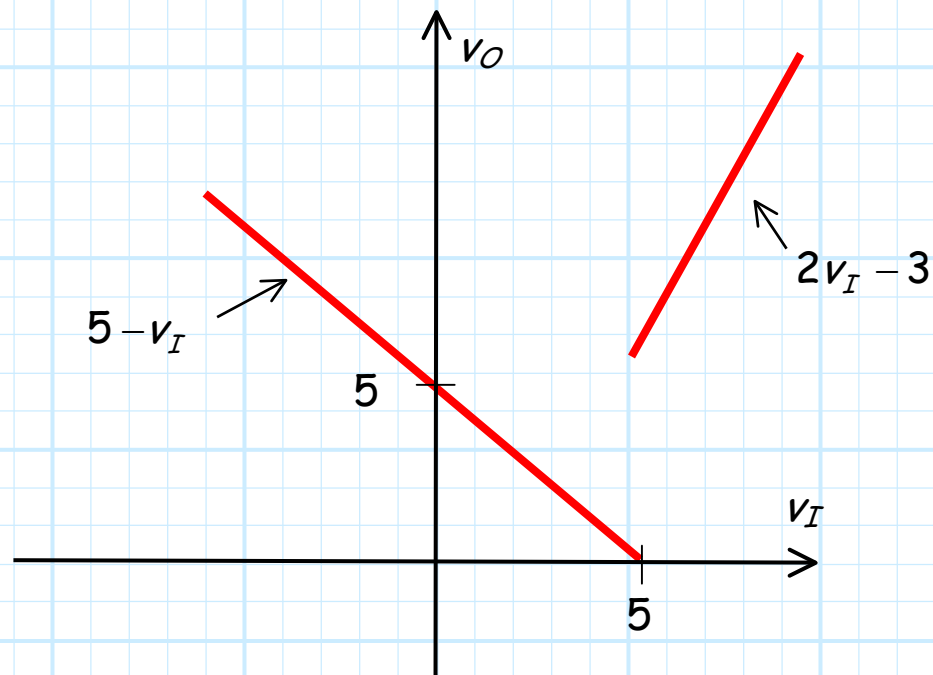
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 5.0 \\ 5 - v_I & \text{for } v_I < 5.0 \end{cases}$$




*Make sure that the piece-wise transfer function that you determine is in fact a function, and is continuous!*



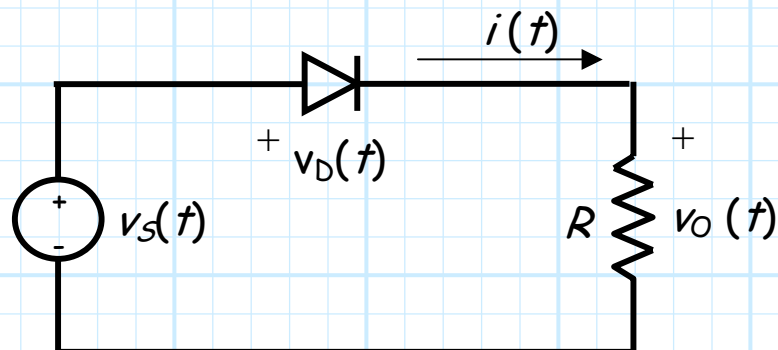
# Example: Diode Circuit Transfer Function

Consider the following circuit, called a **half-wave rectifier**:



Let's use the **CVD model** to determine the output voltage  $v_O$  in terms of the input voltage  $v_S$ . In other words, let's determine the diode circuit **transfer function**  $v_O = f(v_S)$ !

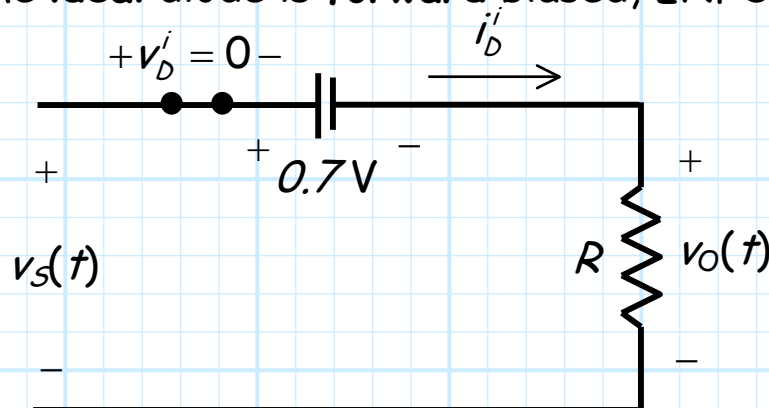**ASSUME** the **ideal** diode is **forward** biased, **ENFORCE**  $v_D^i = 0$ .



From KVL, we find that:


$$v_O(t) = v_S(t) - 0.7$$

This result is of course true if our original assumption is correct— it is valid if the ideal diode is forward biased (i.e.,  $i_D^i > 0$ )!

From Ohm's Law, we find that:

$$i_D^i = \frac{v_O}{R} = \frac{v_S - 0.7}{R}$$

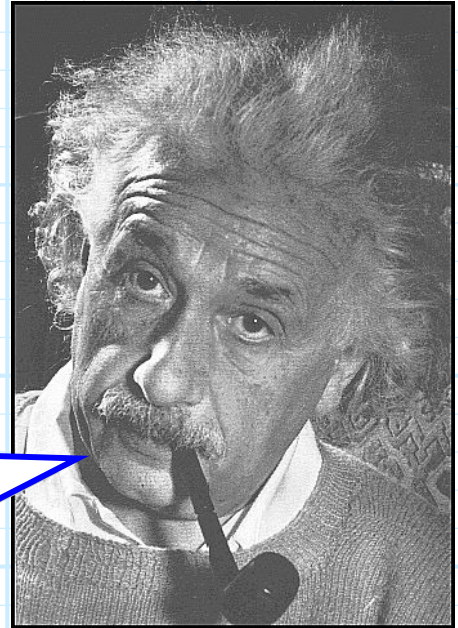**Q:** *I'm so confused! Is this current **greater** than zero or **less** than zero? Is our assumption correct? How can we tell?*




**A:** The ideal diode current is **dependent** on the value of source voltage  $v_S(t)$ . As such, we **cannot** determine if our assumption is correct, we **instead** must find out **when** our assumption is correct!

In other words, we know that the forward bias assumption is correct **when**  $i_D^i > 0$ . We can rearrange our diode current expression to determine for what values of source voltage  $v_S(t)$  this is true:

$$\begin{aligned} i_D^i &> 0 \\ \frac{v_S(t) - 0.7}{R} &> 0 \\ v_S(t) - 0.7 &> 0 \\ v_S(t) &> 0.7 \end{aligned}$$


So, we have found that **when** the source voltage  $v_s(t)$  is greater than 0.7 V, the output voltage  $v_o(t)$  is:

$$v_o(t) = v_s(t) - 0.7$$

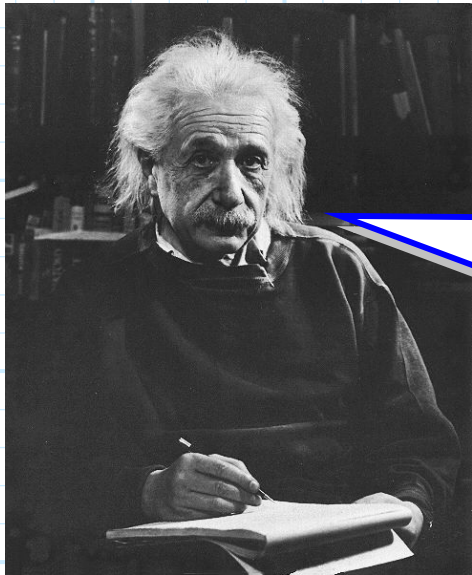

**Q:** *OK, I've got this result written down. However, I still don't know what the output voltage  $v_o(t)$  is **when** the source voltage  $v_s(t)$  is **less** than 0.7V!?!?*

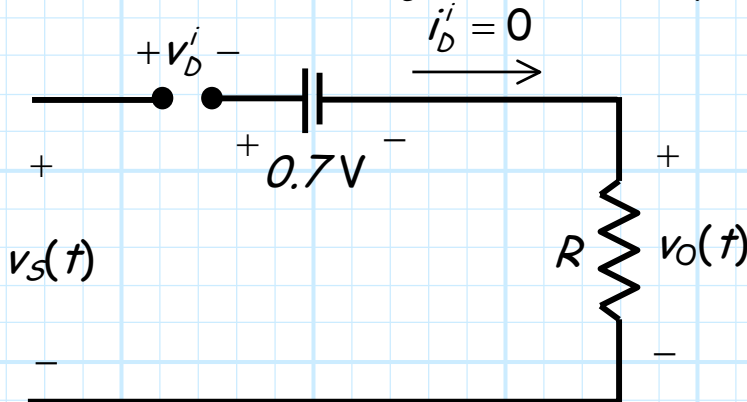
Now we **change** our assumption and **ASSSSUME** the ideal diode in the CVD model is **reverse** biased, an assumption **ENFORCED** with the condition that  $i_D^i = 0$  (i.e., an open circuit).



**Q:** *Fascinating! The output voltage is **zero** when the ideal diode is reverse biased. But, precisely when **is** the ideal diode reverse biased? For **what** values of  $v_s$  does this occur?*

From Ohm's Law, we find that the output voltage is:
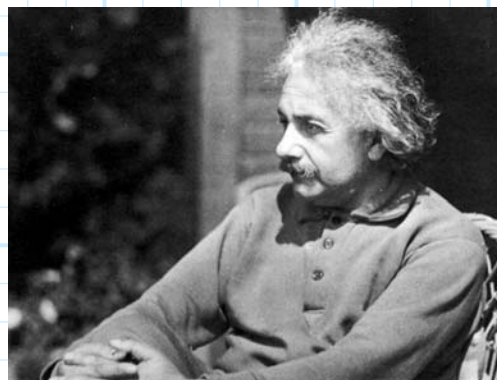
$$\begin{aligned} v_o &= R i_D^i \\ &= R(0) \\ &= 0 \text{ V !!!} \end{aligned}$$



**A:** To answer these questions, we must determine the **ideal** diode voltage in terms of  $v_S$  (i.e.,  $v_D' = f(v_S)$ ):

From KVL: 
$$v_S - v_D' - 0.7 = v_O$$

Therefore:

$$\begin{aligned} v_D' &= v_S - 0.7 - v_O \\ &= v_S - 0.7 - 0.0 \\ &= v_S - 0.7 \end{aligned}$$

Thus, the ideal diode is in reverse bias **when**:

$$\begin{aligned} v_D' &< 0 \\ v_S - 0.7 &< 0 \end{aligned}$$

Solving for  $v_S$ , we find:

$$\begin{aligned} v_S - 0.7 &< 0 \\ v_S &< 0.7 \text{ V} \end{aligned}$$

In other words, we have determined that the **ideal** diode will be reverse biased **when**  $v_S < 0.7 \text{ V}$ , and that the output voltage will be  $v_O = 0$ .



**Q:** So, we have found that:

$$v_O = v_S - 0.7 \quad \text{when } v_S > 0.7 \text{ V}$$


and,

$$v_O = 0.0 \quad \text{when } v_S < 0.7 \text{ V}$$

*It appears we have a valid, continuous, function!*

**A:** That's right! The **transfer function** for this circuit is therefore:

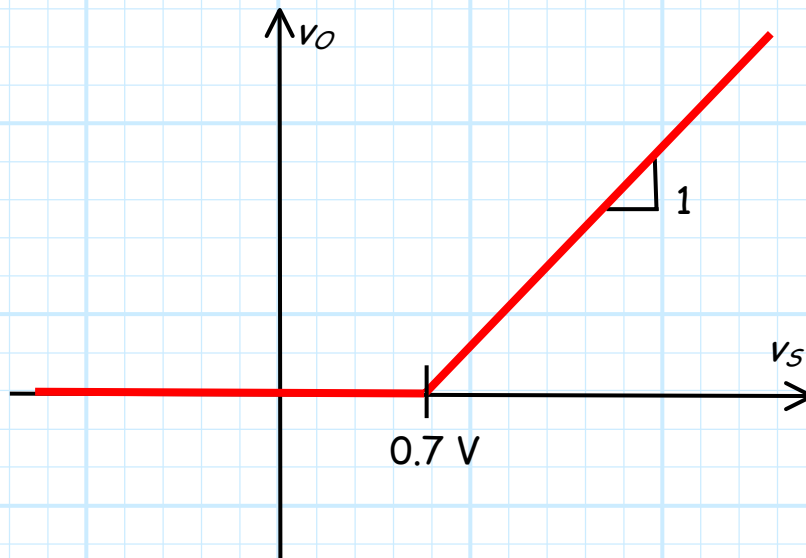
$$v_o = \begin{cases} v_s - 0.7 & \text{for } v_s > 0.7 \\ 0 & \text{for } v_s < 0.7 \end{cases}$$



*Although the circuit in this example may **seem** trivial, it is actually **very important!***

*It is called a **half-wave rectifier**, and provides **signal rectification**.*

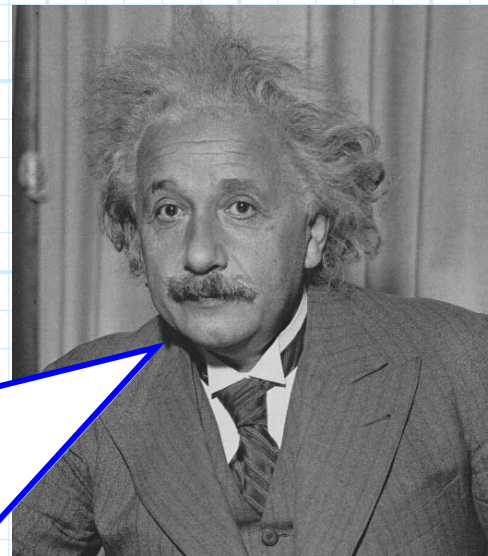*Rectifiers are an **essential part** of every **AC to DC power supply!***




# Signal Rectification


An important application of junction diodes is **signal rectification**.

There are **two** types of signal rectifiers, **half-wave** and **full-wave**.

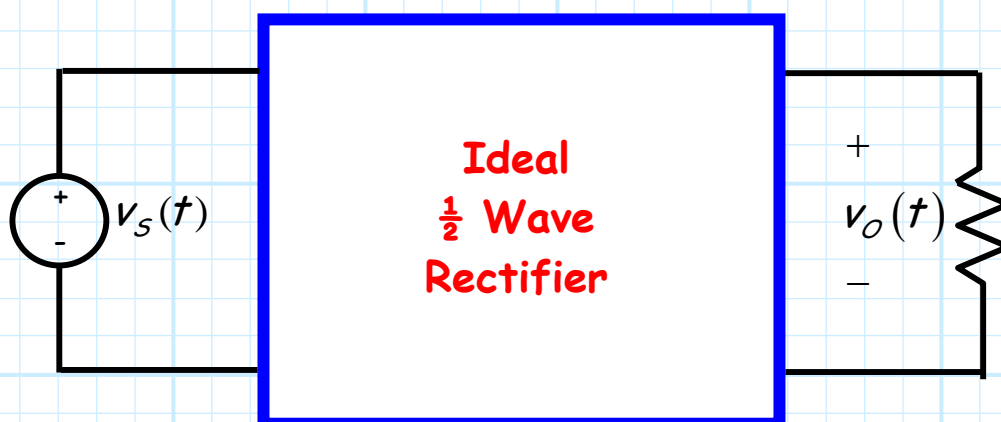
Let's first consider the **ideal half-wave rectifier**. It is a circuit with the transfer function  $v_o = f(v_s)$ :


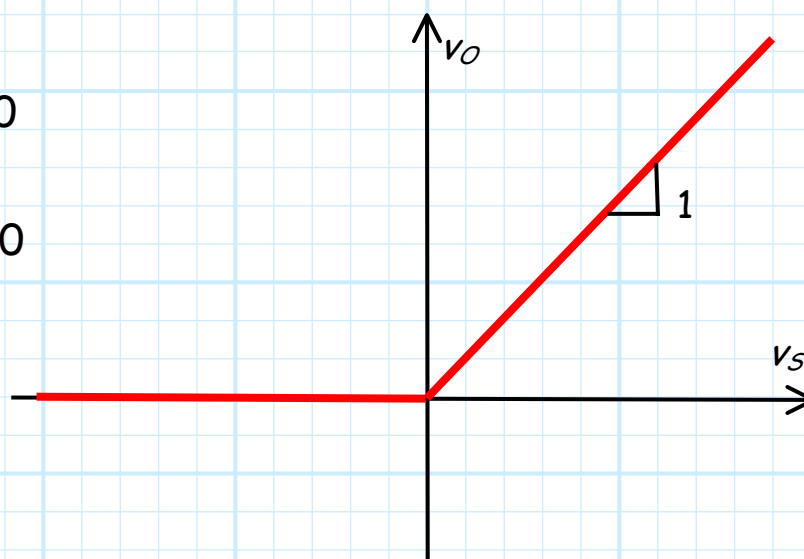
$$v_o = \begin{cases} 0 & \text{for } v_s < 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$





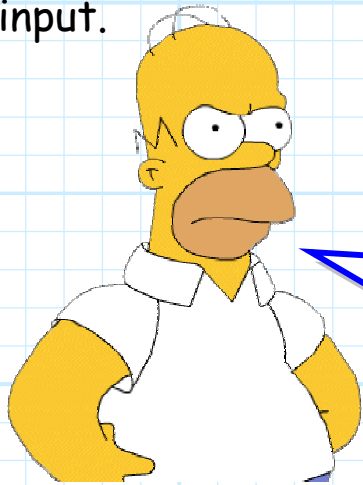Pretty simple! **When** the input is negative, the output is **zero**, whereas **when** the input is positive, the output is the **same** as the input.



**Q:** *Pretty simple and pretty stupid I'd say! This might be your most **pointless** circuit yet. How is **this** circuit even remotely useful??*

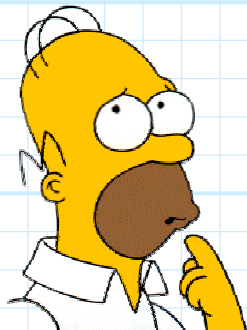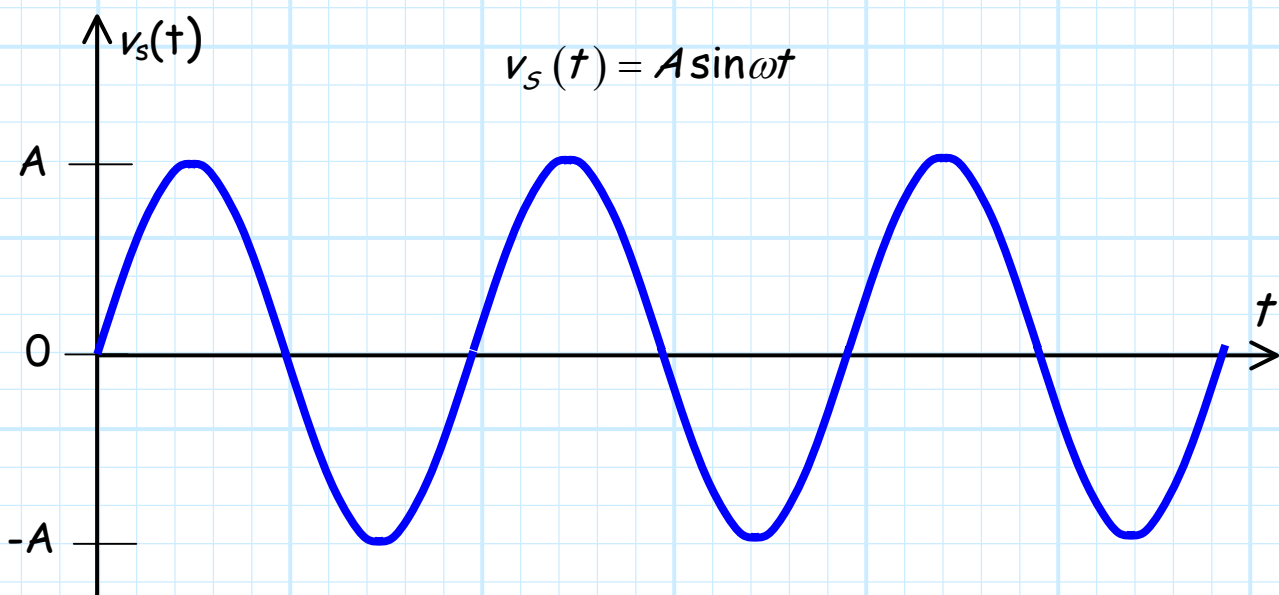
**A:** To see **why** a half-wave rectifier is useful, consider the **typical** case where the input source voltage is a **sinusoidal** signal with **frequency**  $\omega$  and peak **magnitude**  $A$ :




**Think** about what the **output** of the half-wave rectifier would be! Remember the rule: when  $v_s(t)$  is **negative**, the output is **zero**, when  $v_s(t)$  is **positive**, the output is **equal** to the input.



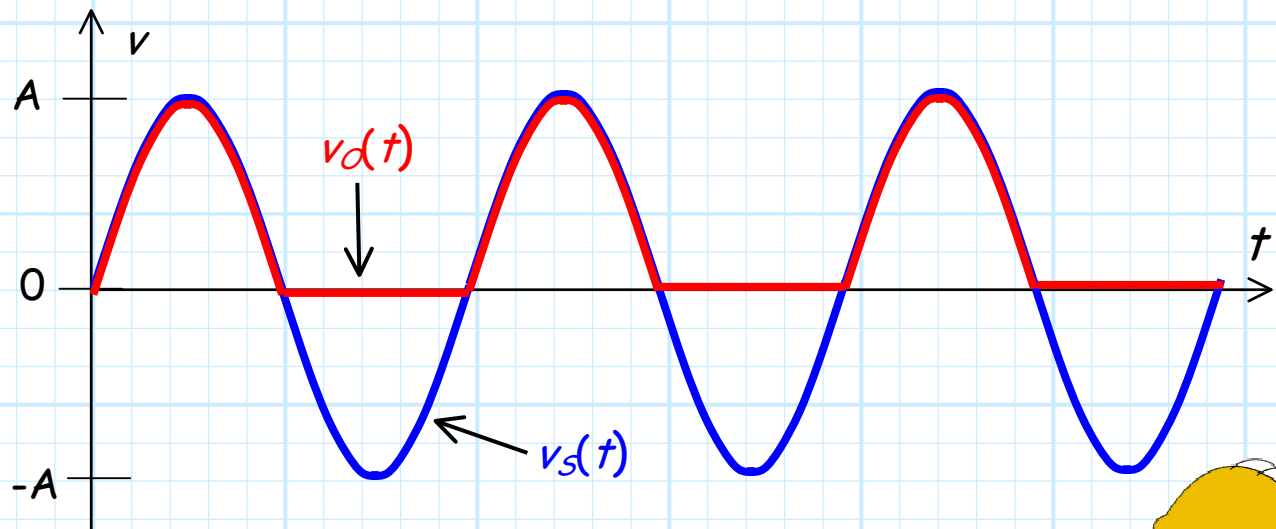The **output** of the half-wave rectifier for **this** example is therefore:



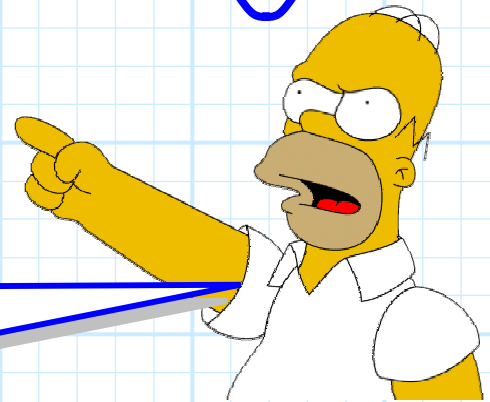**Q:** *That's the **lamest** result I've ever seen. What good is **half** a sine wave? Why even bother?*



**A:** Although it may appear that our rectifier had **little** useful effect on the input signal  $v_s(t)$ , in fact the difference between input  $v_s(t)$  and output  $v_d(t)$  is both **important** and **profound**.

To see how, consider first the **DC component** (i.e. the time-averaged value) of the **input** sine wave:

$$\begin{aligned} V_S &= \frac{1}{T} \int_0^T v_s(t) dt \\ &= \frac{1}{T} \int_0^T A \sin \omega t dt = 0 \end{aligned}$$





Thus, (as you probably already knew) the **DC component** of a sine wave is **zero**—a sine wave is an **AC signal**!

Now, contrast this with the **output**  $v_o(t)$  of our half-wave rectifier. The **DC component** of the **output** is:

$$\begin{aligned} V_o &= \frac{1}{T} \int_0^T v_o(t) dt \\ &= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt + \frac{1}{T} \int_{T/2}^T 0 dt = \frac{A}{\pi} \end{aligned}$$

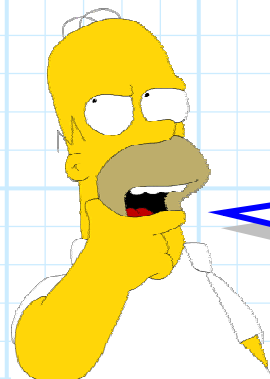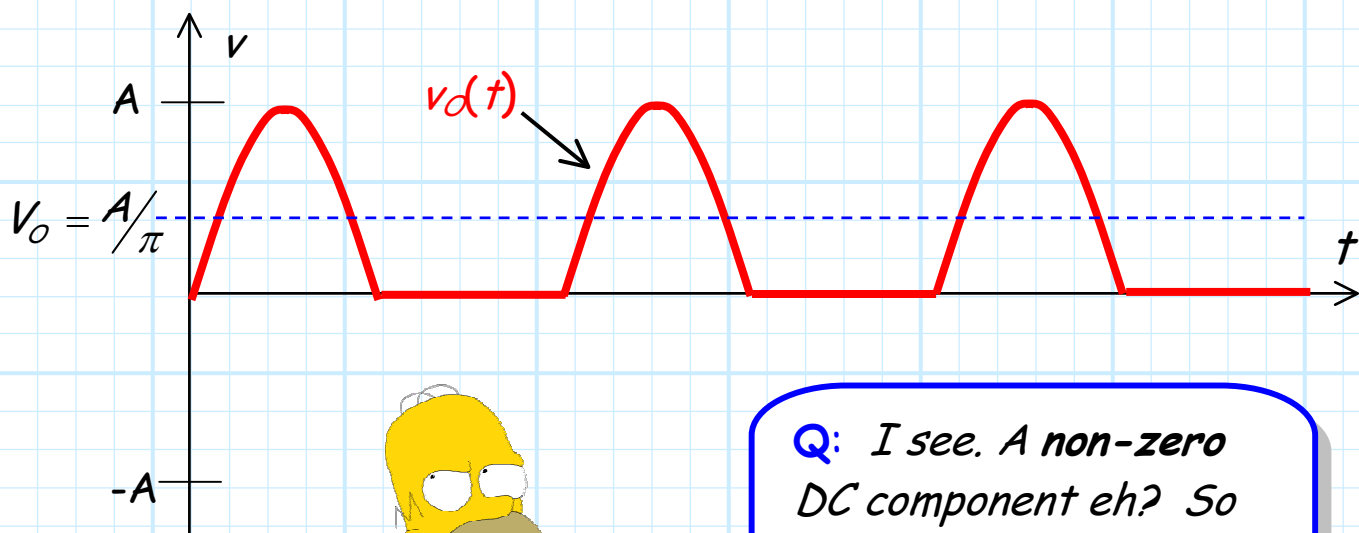
Unlike the input, the **output** has a **non-zero** (positive) **DC component** ( $V_o = A/\pi$ )!



**Q:** *I see. A non-zero DC component eh? So refresh my memory, why is that important?*

**A:** Recall that the **power distribution system** we use is an **AC system**. The source voltage  $v_s(t)$  that we get when we plug our "**power cord**" into the wall socket is a 60 Hz **sinewave**—a source with a **zero DC component**!

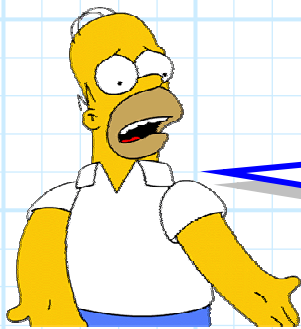
The **problem** with this is that most **electronic devices** and systems, such as TVs, stereos, computers, etc., require a **DC voltage(s)** to operate!




**Q:** *But, how can we create a DC supply voltage if our power source  $v_s(t)$  has no DC component??*

**A:** That's **why** the half-wave rectifier is so **important**! It takes an AC source with **no DC component** and creates a signal with **both** a DC and AC component.

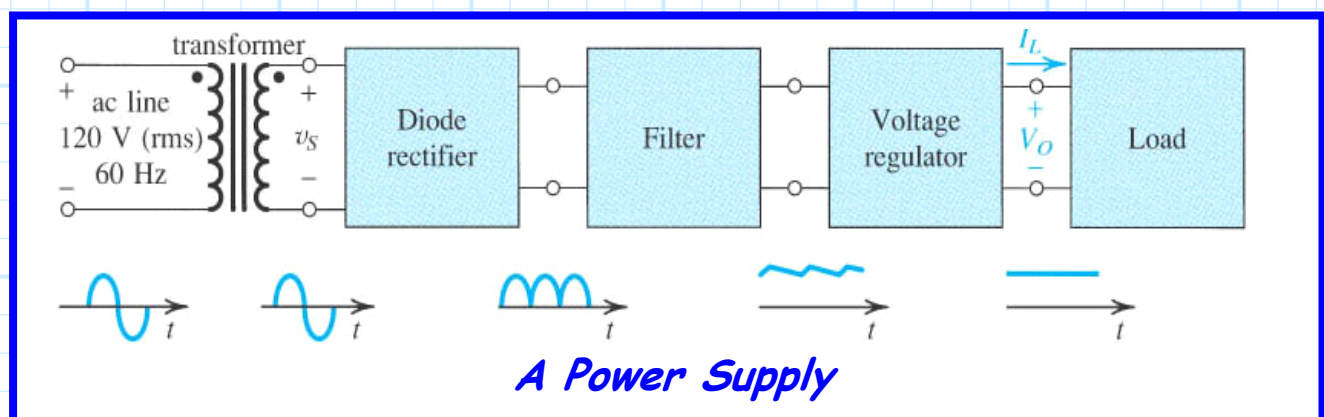
We can then pass the output of a half-wave rectifier through a **low-pass filter**, which **suppresses** the AC component but lets the DC value ( $V_o = A/\pi$ ) pass through. We then **regulate** this output and form a **useful DC voltage source**—one suitable for powering our electronic systems!



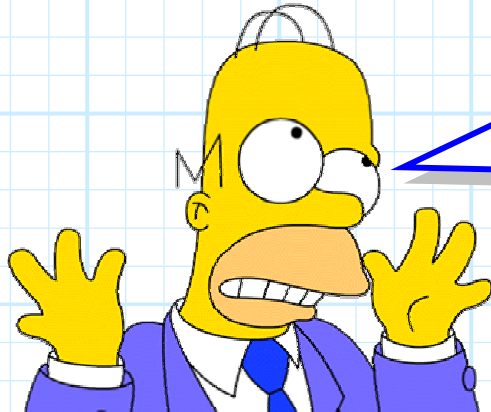


**Q:** *OK, now I see why the ideal half-wave rectifier might be useful. But, is there any way to actually build this magical device?*

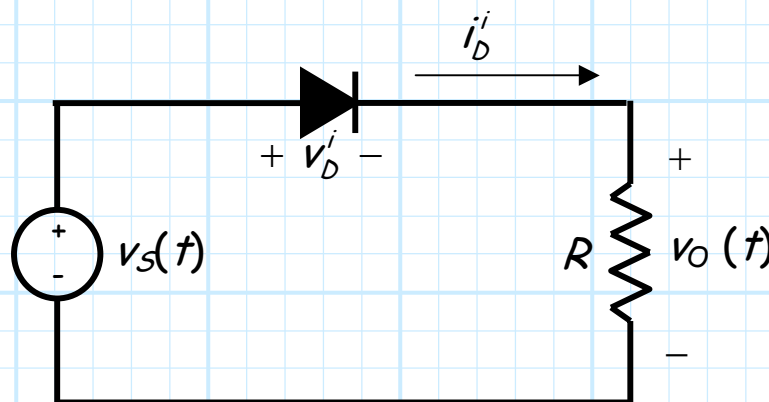**A:** An ideal half-wave rectifier can be "built" if we use an ideal diode.





If we follow the transfer function **analysis steps** we studied earlier, then we will find that this circuit is indeed an **ideal half-wave rectifier!**
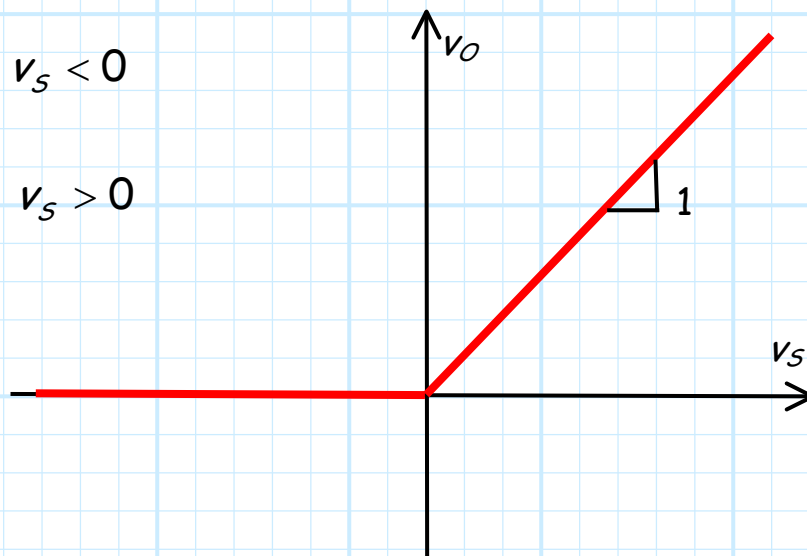
$$v_O = \begin{cases} 0 & \text{for } v_S < 0 \\ v_S & \text{for } v_S > 0 \end{cases}$$



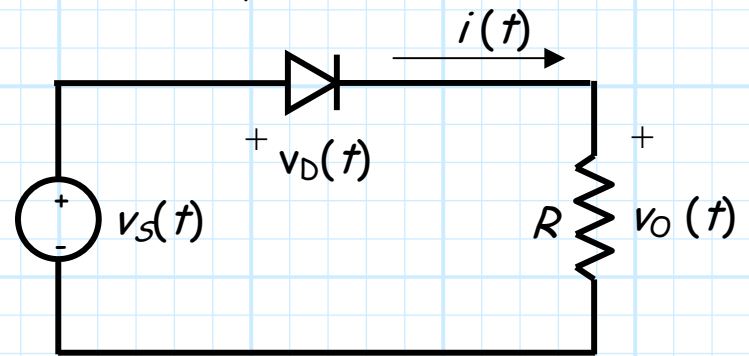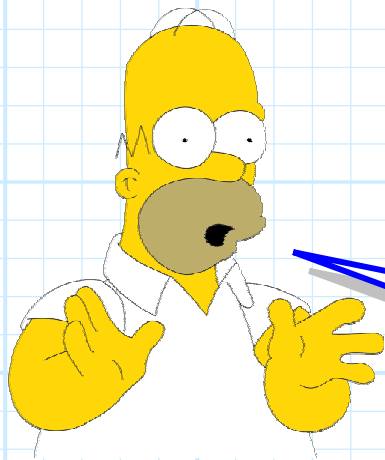
Of course, since **ideal** diodes do **not** exist, we must use a **junction diode** instead:




**Q:** *This circuit looks so familiar!  
Haven't we studied it before?*

**A:** Yes! It was an **example** where we determined the junction diode circuit transfer function. Recall that the **result** was:
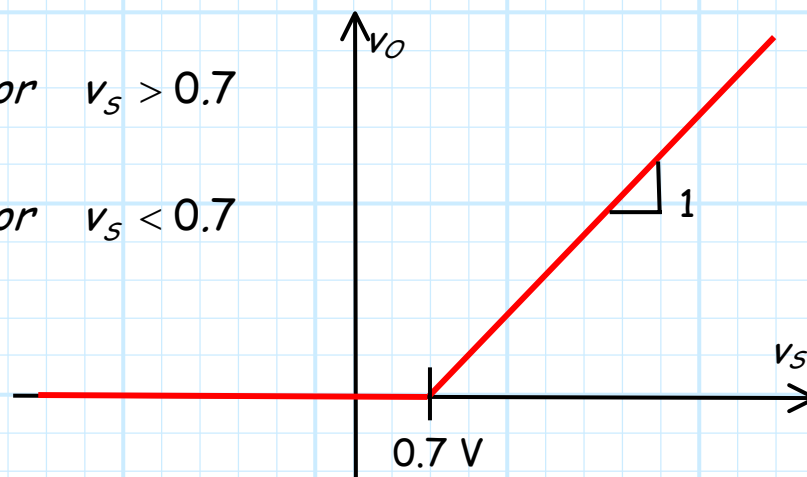
$$v_O = \begin{cases} v_S - 0.7 & \text{for } v_S > 0.7 \\ 0 & \text{for } v_S < 0.7 \end{cases}$$



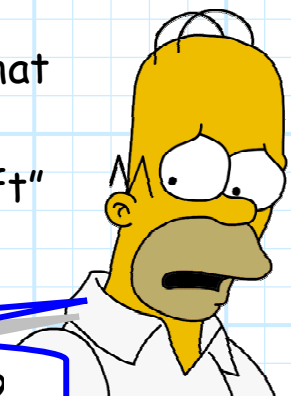Note that this result is **slightly different** from that of the **ideal** half-wave rectifier! The **0.7 V drop** across the junction diode causes a horizontal "shift" of the transfer function from the ideal case.




**Q:** *So then this junction diode circuit is worthless?*

**A:** Hardly! Although the transfer function is **not quite** ideal, it works **well enough** to achieve the goal of signal rectification—it takes an input with **no** DC component and creates an output with a **significant** DC component!


Note what the transfer function “**rule**” is now:

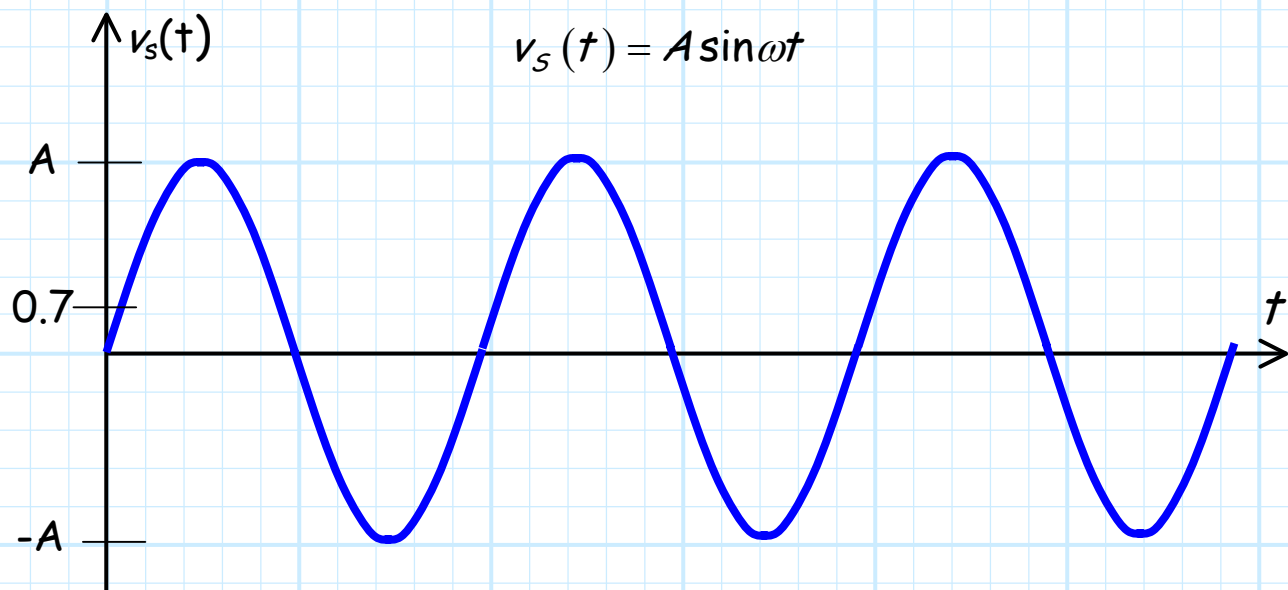1. When the input is **greater** than 0.7 V, the output voltage is **equal** to the input voltage minus 0.7 V.
2. When the input is **less** than 0.7 V, the output voltage is **zero**.

So, let's consider **again** the case where the **source** voltage is **sinusoidal** (just like the source from a “wall socket”!):



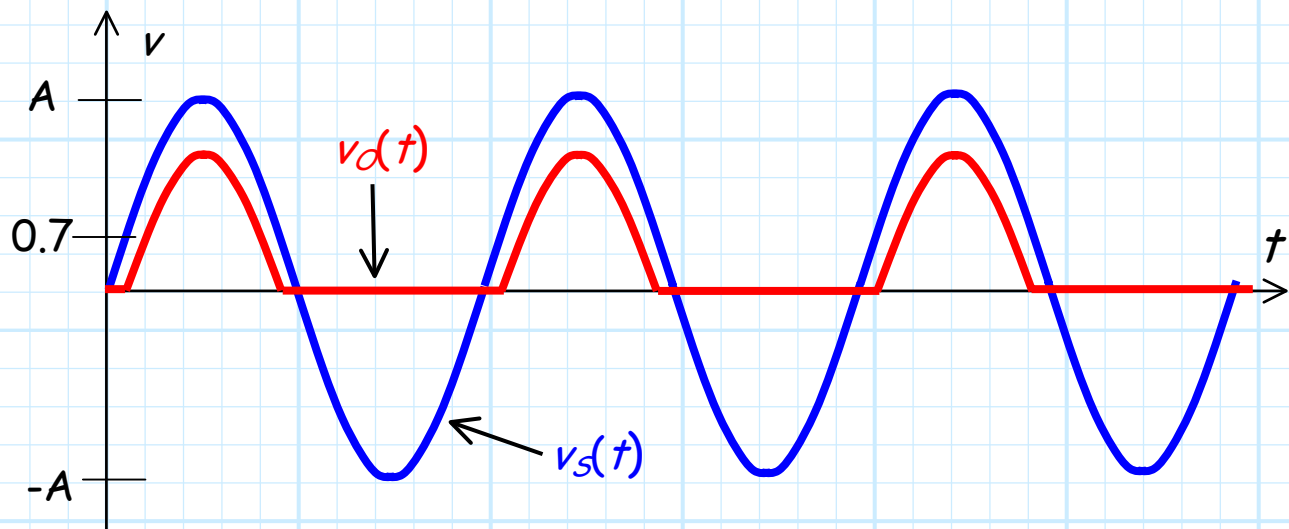The output of our **junction diode** half-wave rectifier would therefore be:



Although the output is **shifted downward** by 0.7 V (note in the plot above this is **exaggerated**, typically  $A \gg 0.7V$ ), it should be apparent that the **output signal**  $v_d(t)$ , unlike the input signal  $v_s(t)$ , has a **non-zero** (positive) **DC component**.

Because of the 0.7 V shift, this DC component is **slightly smaller** than the **ideal** case. In fact, we find that if  $A \gg 0.7$ , this **DC component** is approximately:


$$V_o \approx \frac{A}{\pi} - 0.35 \text{ V}$$

In other words, **just 350 mV less than ideal!**


**Q:** *Way back on the first page you said that there were **two** types of rectifiers. I now understand **half-wave** rectification, but what about these so-called **full-wave** rectifiers?*



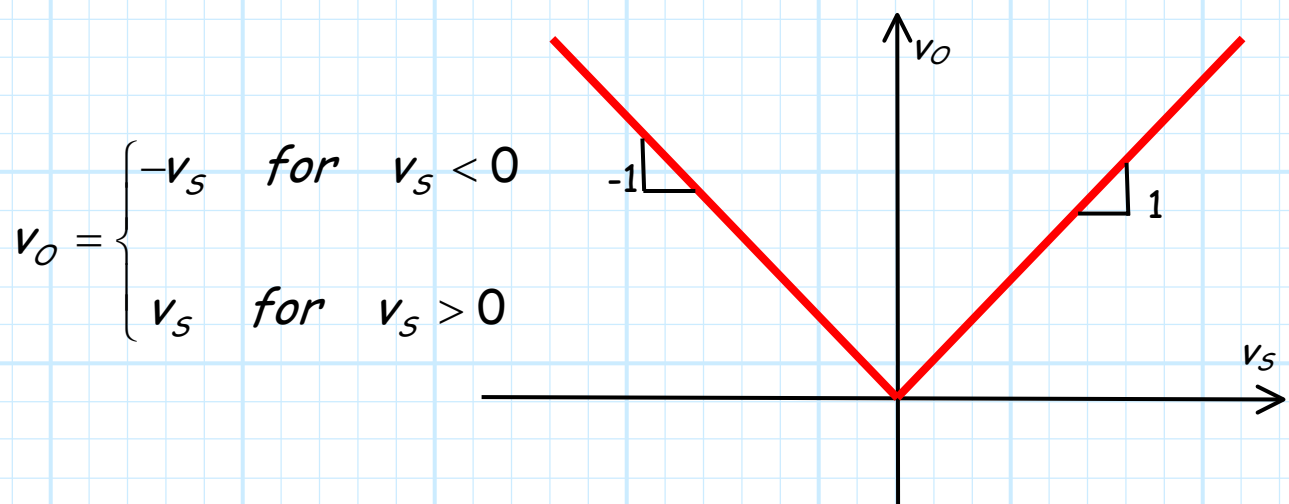**A:** Almost forgot! Let's examine the transfer function of an ideal full-wave rectifier:




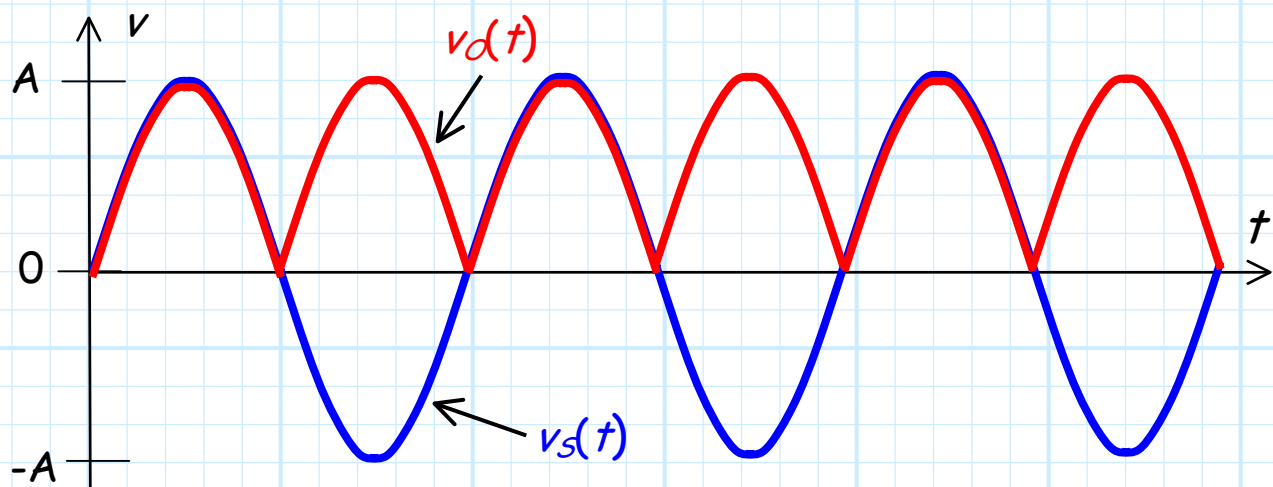
If the ideal half-wave rectifier makes **negative** inputs **zero**, the ideal full-wave rectifier makes **negative** inputs—**positive**! For **example**, if we again consider our **sinusoidal** input, we find that the output will be:



The result is that the output signal will have a DC component **twice** that of the ideal half-wave rectifier!

$$V_o = \frac{1}{T} \int_0^T v_o(t) dt$$
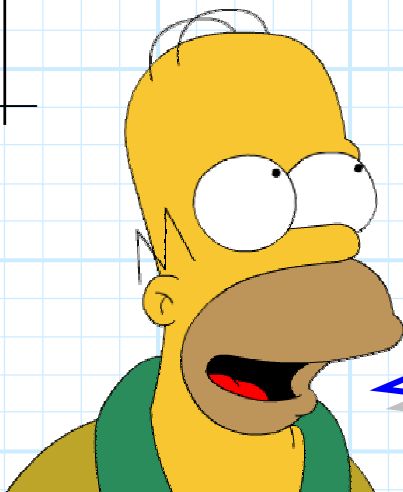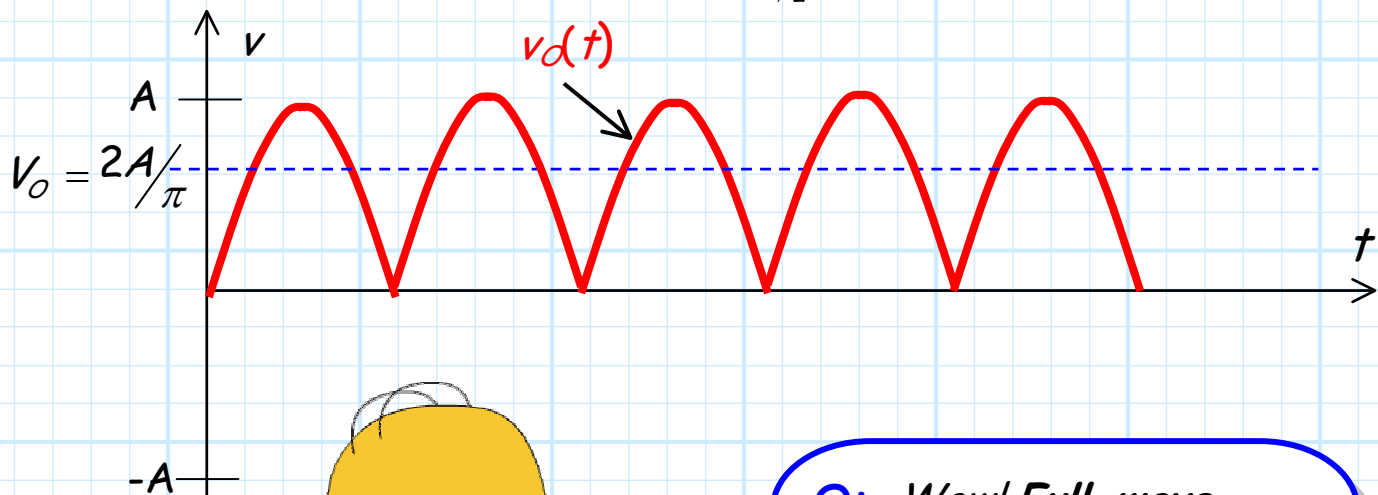
$$= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt - \frac{1}{T} \int_{T/2}^T A \sin \omega t dt = \frac{2A}{\pi}$$




**Q:** *Wow! Full-wave rectification appears to be twice as good as half-wave. Can we build an ideal full-wave rectifier with junction diodes?*

**A:** Although we cannot build an **ideal** full-wave rectifier with **junction** diodes, we can build full-wave rectifiers that are **very close** to ideal with junction diodes!


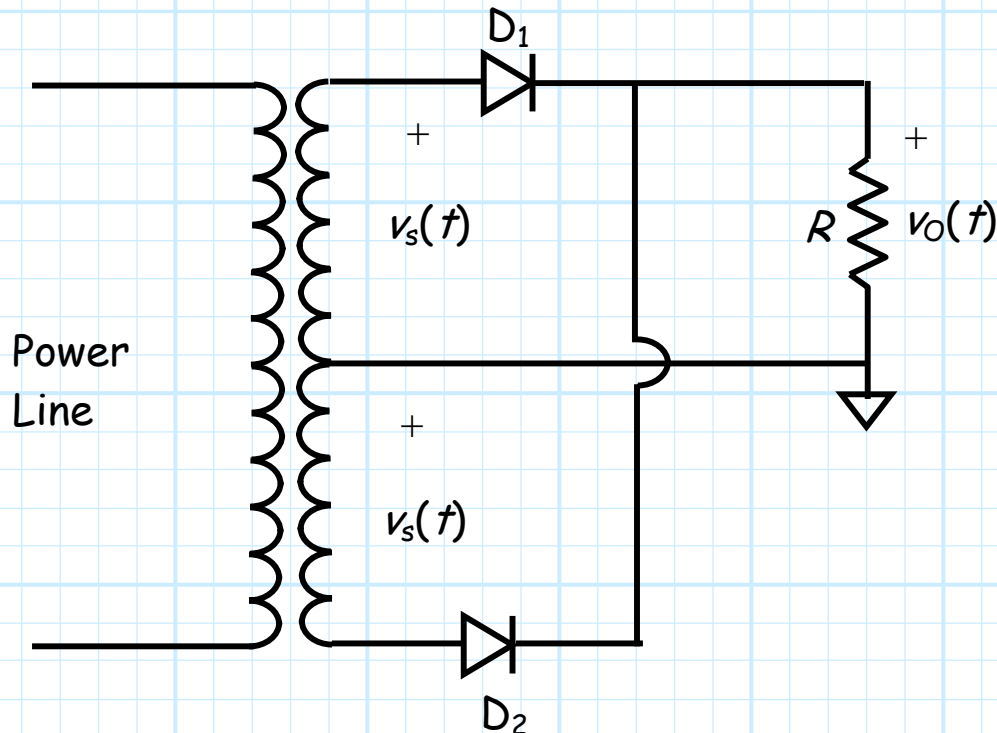
# The Full-Wave Rectifier


Consider the following **junction diode** circuit:




Note that we are using a **transformer** in this circuit. The job of this transformer is to **step-down** the large voltage on our power line (120 V rms) to some **smaller** magnitude (typically 20-70 V rms).

Note the secondary winding has a **center tap** that is **grounded**. Thus, the secondary voltage is distributed **symmetrically** on either side of this center tap.

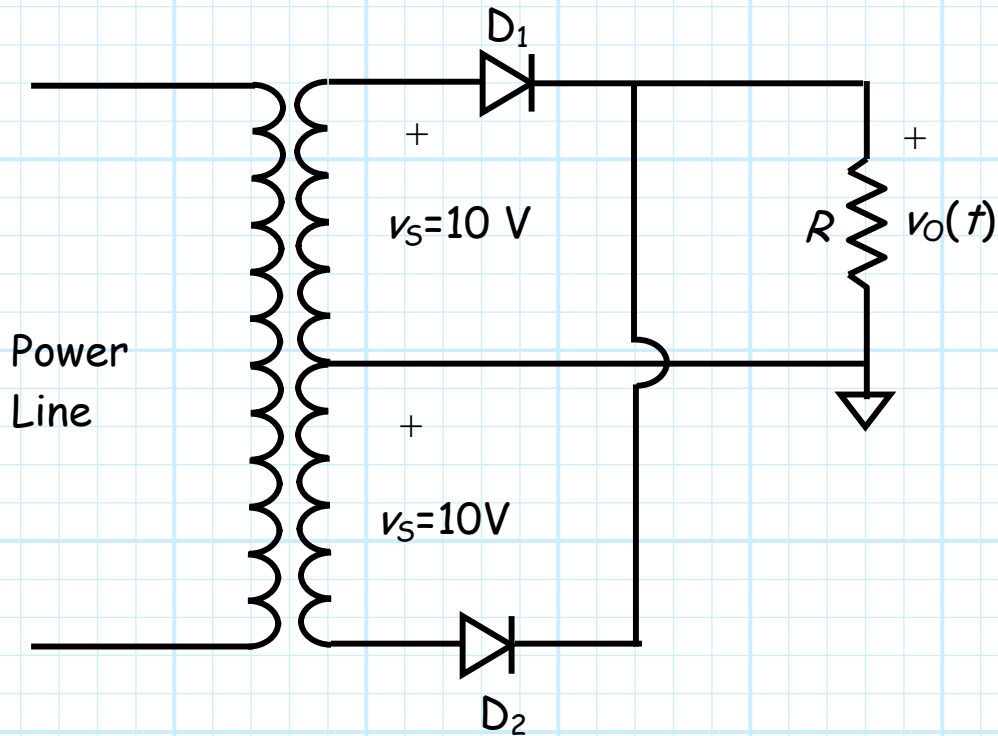For **example**, if  $v_s = 10$  V, the anode of  $D_1$  will be 10V **above** ground potential, while the anode of  $D_2$  will be 10V **below** ground potential (i.e., -10V):




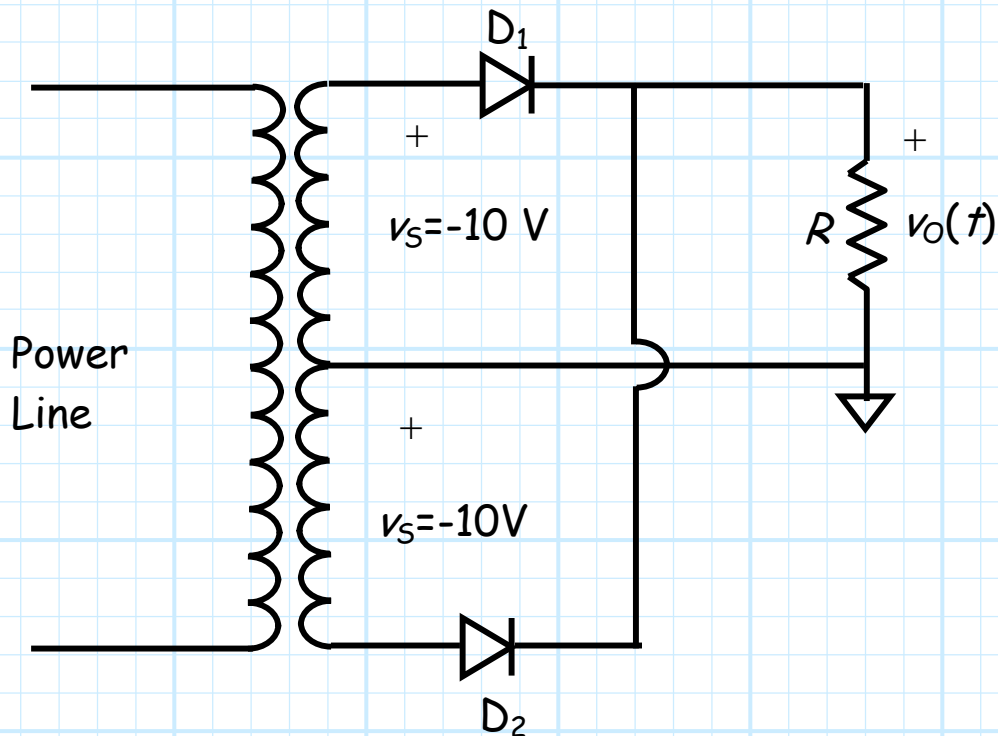Conversely, if  $v_s = -10$  V, the anode of  $D_1$  will be 10V **below** ground potential (i.e., -10V), while the anode of  $D_2$  will be 10V **above** ground potential:




The more important question is, what is the value of **output**  $v_o$ ? More specifically, how is  $v_o$  related to the value of source  $v_s$ —what is the **transfer function**  $v_o = f(v_s)$ ?

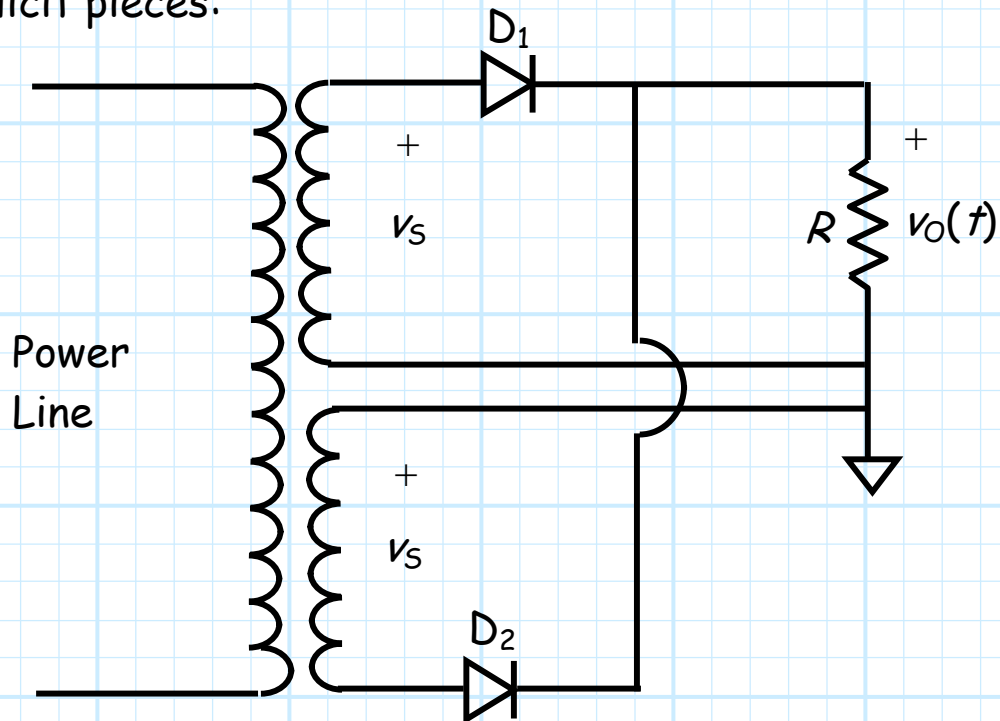
To help simplify our analysis, we are going **redraw** this circuit in another way. First, we will **split** the secondary winding into two explicit pieces:



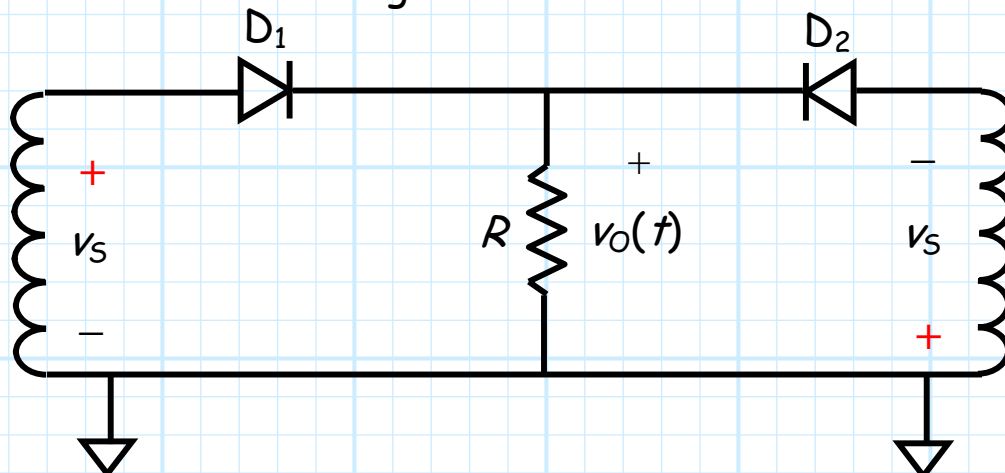We will now **ignore the primary** winding of the transformer and redraw the remaining circuit as:



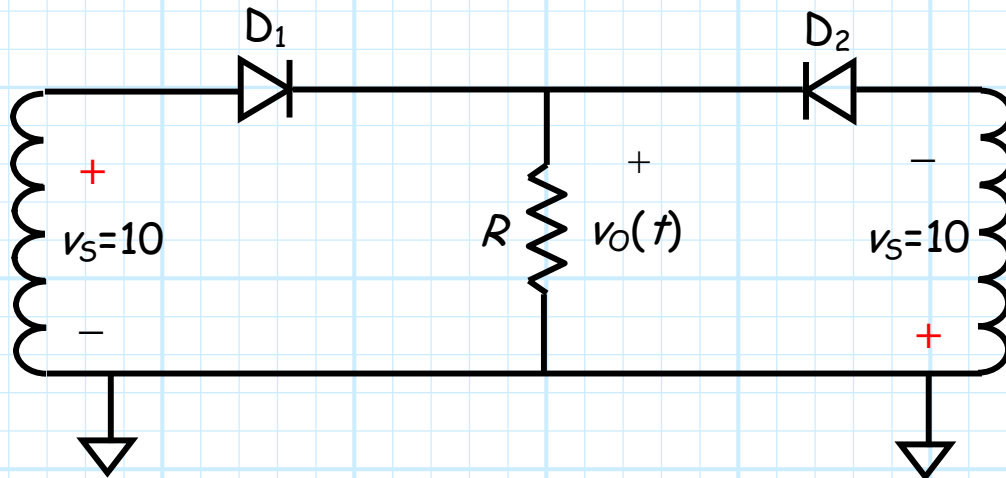
Note that the secondary voltages at either end of this circuit are the **same**, but have **opposite** polarity. As a result, if  $v_S=10$ , then the anode of diode  $D_1$  will be 10 V **above** ground, and the anode at diode  $D_2$  will be 10V **below** ground—just like before!



Now, let's attempt to determine the **transfer function**  $v_O = f(v_S)$  of this circuit.

First, we will replace the junction diodes with **CVD models**.

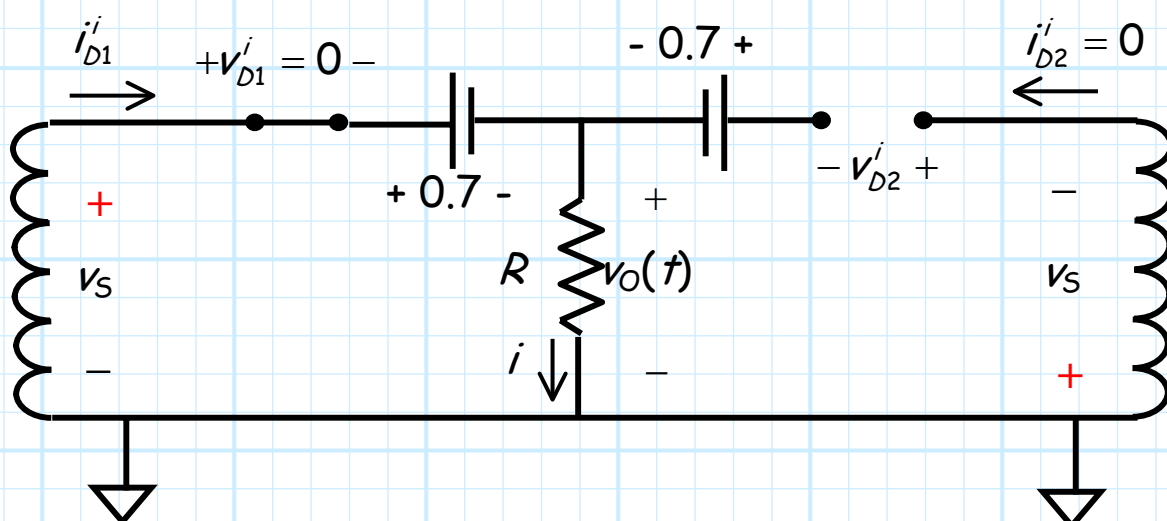Then let's **ASSUME**  $D_1$  is **forward** biased and  $D_2$  is **reverse** biased, thus **ENFORCE**  $v_{D1}^i = 0$  and  $i_{D2}^i = 0$ . Thus **ANALYZE**:



Note that we need to determine **3** things: the **ideal diode current**  $i_{D1}^i$ , the **ideal diode voltage**  $v_{D2}^i$ , and the **output voltage**  $v_O$ . However, **instead** of finding numerical values for these 3 quantities, we must express them in terms of **source voltage**  $v_S$ !

From KCL: 
$$i = i_{D1}^i + i_{D2}^i = i_{D1}^i + 0 = i_{D1}^i$$

From KVL: 
$$v_S - v_{D1}^i - 0.7 - R i_D^i = 0$$

Thus the **ideal diode current** is:

$$i_{D1}^i = \frac{v_S - 0.7}{R}$$

Likewise, from KVL: 
$$v_S - v_{D1}^i - 0.7 + 0.7 + v_{D2}^i + v_S = 0$$

Thus, the **ideal diode voltage** is:

$$v_{D2}^i = -2v_S$$

And finally, from KVL: 
$$v_S - v_{D1}^i - 0.7 = v_O$$

Thus, the **output voltage** is:

$$v_O = v_S - 0.7$$

Now, we must determine **when** both  $i_{D1}^i > 0$  and  $v_{D2}^i < 0$ . When **both** these conditions are true, the output voltage will be  $v_o = v_s - 0.7$ . When one **or** both conditions  $i_{D1}^i > 0$  and  $v_{D2}^i < 0$  are **false**, then our assumptions are **invalid**, and  $v_o \neq v_s - 0.7$ .

Using the results we just determined, we know that  $i_{D1}^i > 0$  **when**:

$$\frac{v_s - 0.7}{R} > 0$$

Solving for  $v_s$ :

$$\begin{aligned} \frac{v_s - 0.7}{R} &> 0 \\ v_s - 0.7 &> 0 \\ v_s &> 0.7 \text{ V} \end{aligned}$$

Likewise, we find that  $v_{D2}^i < 0$  **when**:

$$-2v_s < 0$$

Solving for  $v_s$ :

$$\begin{aligned} -2v_s &< 0 \\ 2v_s &> 0 \\ v_s &> 0 \end{aligned}$$


Thus, our assumptions are correct **when**  $v_s > 0.0$  **AND**  $v_s > 0.7$ . This is the **same** thing as saying our assumptions are valid when  $v_s > 0.7$ !

Thus, we have found that the following statement is true about this circuit:

$$v_o = v_s - 0.7 \text{ V} \quad \text{when} \quad v_s > 0.7 \text{ V}$$

Note that this statement does **not** constitute a **function** (what about  $v_s < 0.7$ ?), so we must **continue** with our analysis!

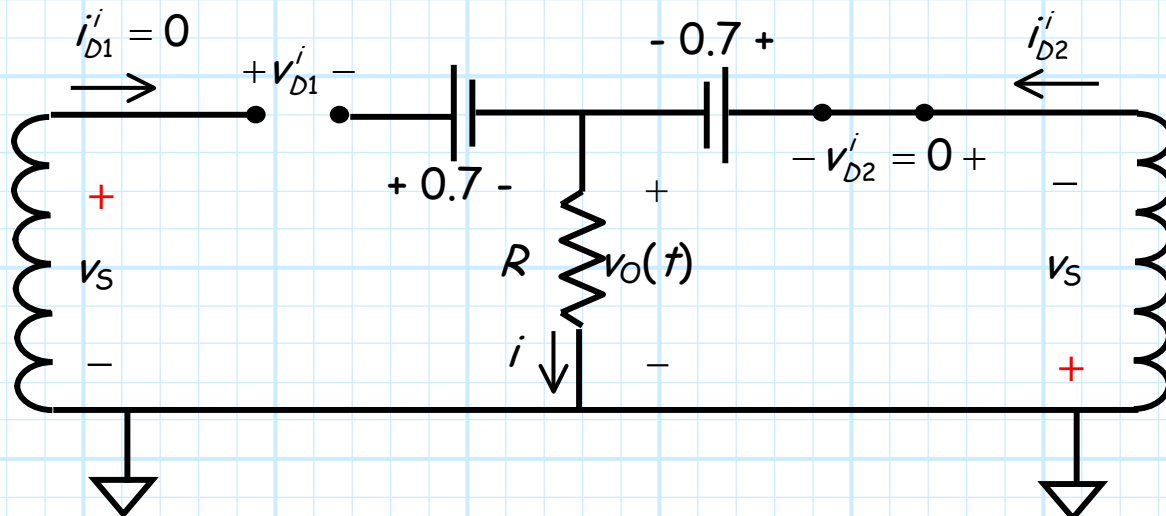Say we now **ASSUME** that  $D_1$  is **reverse** biased and  $D_2$  is **forward** biased, so we **ENFORCE**  $i_{D1}^i = 0$  and  $v_{D2}^i = 0$ . Thus, we **ANALYZE this** circuit:




Using the **same procedure** as before, we find that  $v_o = -v_s - 0.7$ , and both our assumptions are true **when**  $v_s < -0.7 \text{ V}$ . In other words:

$$v_o = -v_s - 0.7 \text{ V} \quad \text{when} \quad v_s < -0.7 \text{ V}$$

Note we are still **not** done! We **still** do not have a complete transfer **function** (what happens when  $-0.7 \text{ V} < v_s < 0.7 \text{ V}$ ?).

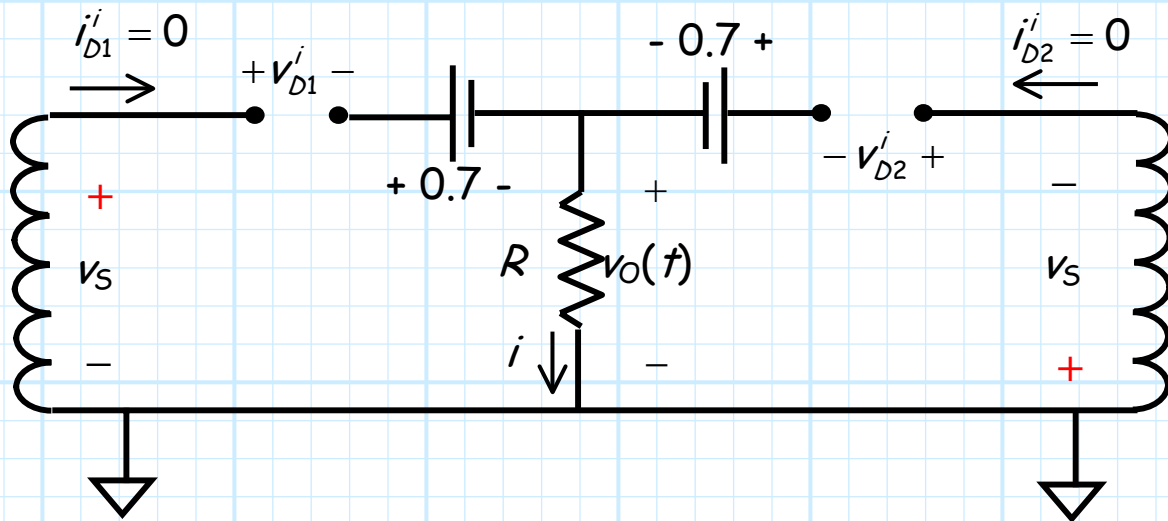Finally then, we ASSUME that **both** ideal diodes are **reverse** biased, so we ENFORCE  $i_{D1}^i = 0$  and  $i_{D2}^i = 0$ . Thus ANALYZE:



Following the **same procedures** as before, we find that  $v_S = 0$ , and both assumptions are true **when**  $-0.7 < v_S < 0.7$ . In other words:


$$v_S = 0 \quad \text{when} \quad -0.7 < v_S < 0.7$$

**Now we have a function!** The transfer function of this circuit is:


$$v_O = \begin{cases} v_S - 0.7V & \text{for } v_S > 0.7V \\ 0V & \text{for } -0.7 > v_S > 0.7V \\ -v_S - 0.7V & \text{for } v_S < -0.7V \end{cases}$$

**Plotting this function:**



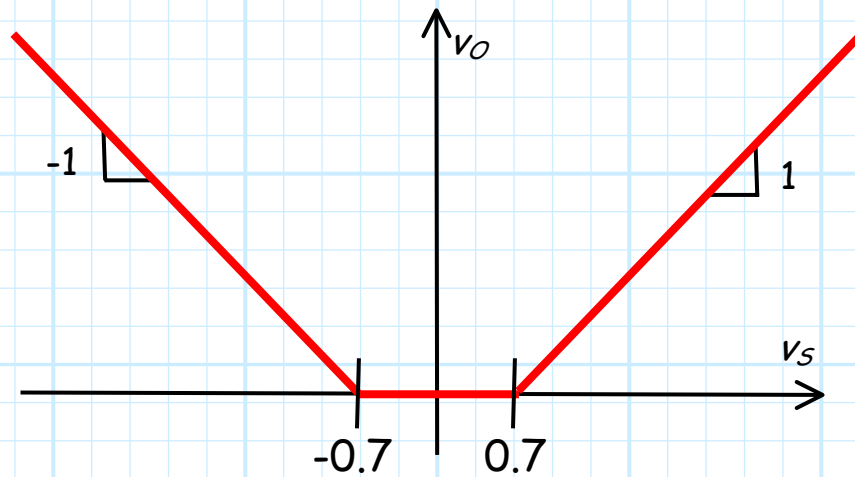


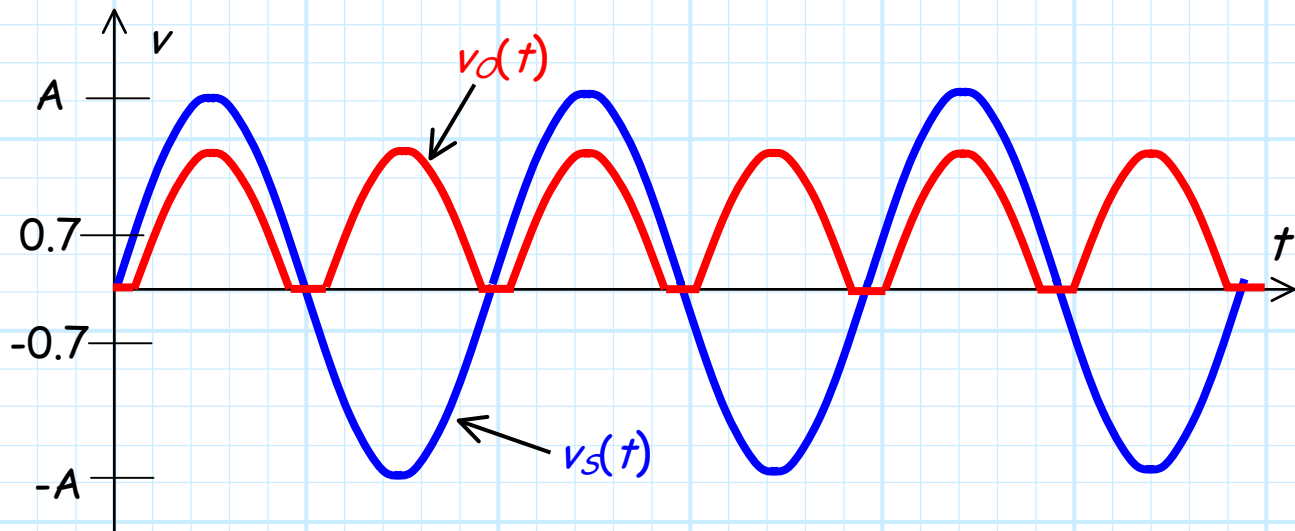The output of this full-wave rectifier with a **sine wave input** is therefore:




Note how this **compares** to the transfer function of the **ideal** full-wave rectifier:
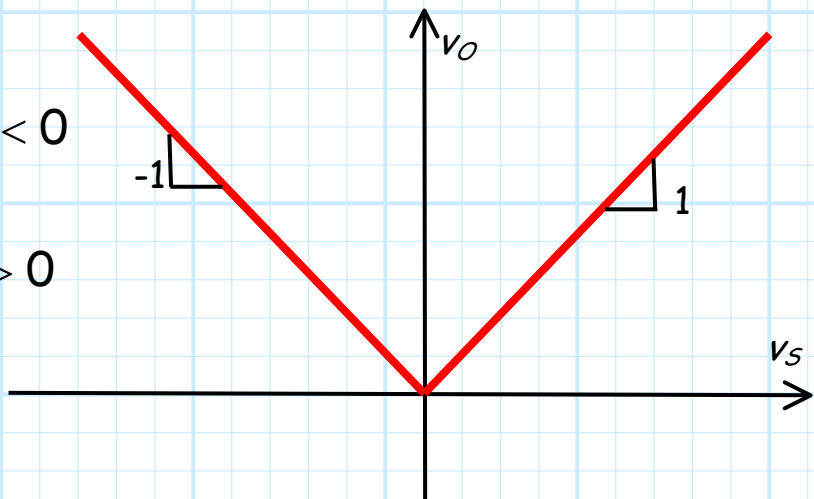
$$v_o = \begin{cases} -v_s & \text{for } v_s < 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$



Very similar!

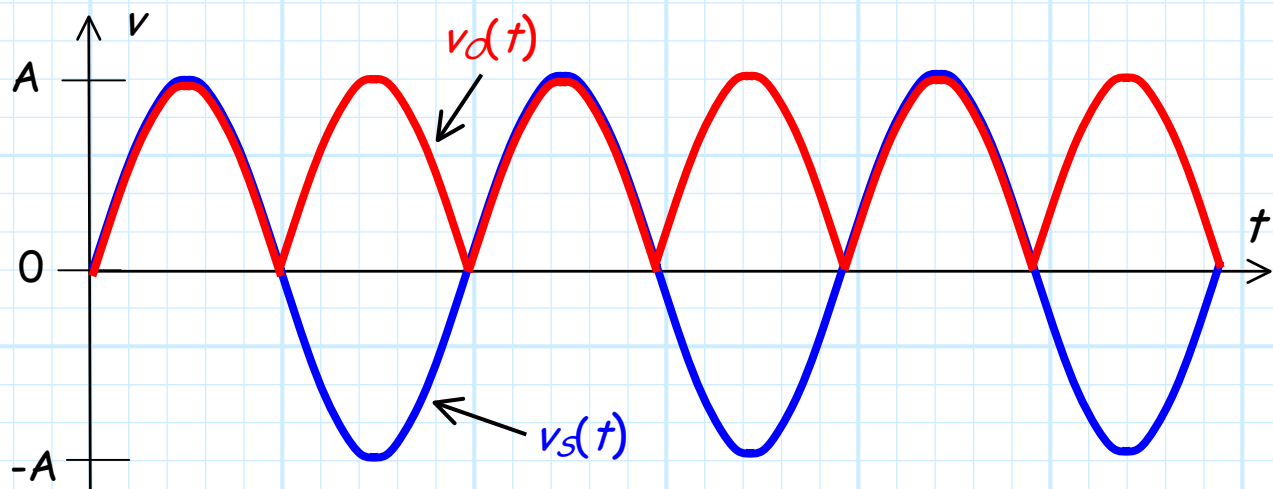Likewise, compare the output of this junction diode full-wave rectifier to the output of an **ideal** full-wave rectifier:




Again we see that the junction diode full-wave rectifier output is **very close** to ideal. In fact, if  $A \gg 0.7 \text{ V}$ , the **DC component** of this junction diode full wave rectifier is approximately:

$$V_o \approx \frac{2A}{\pi} - 0.7 \text{ V}$$

**Just 700 mV** less than the **ideal** full-wave rectifier DC component!

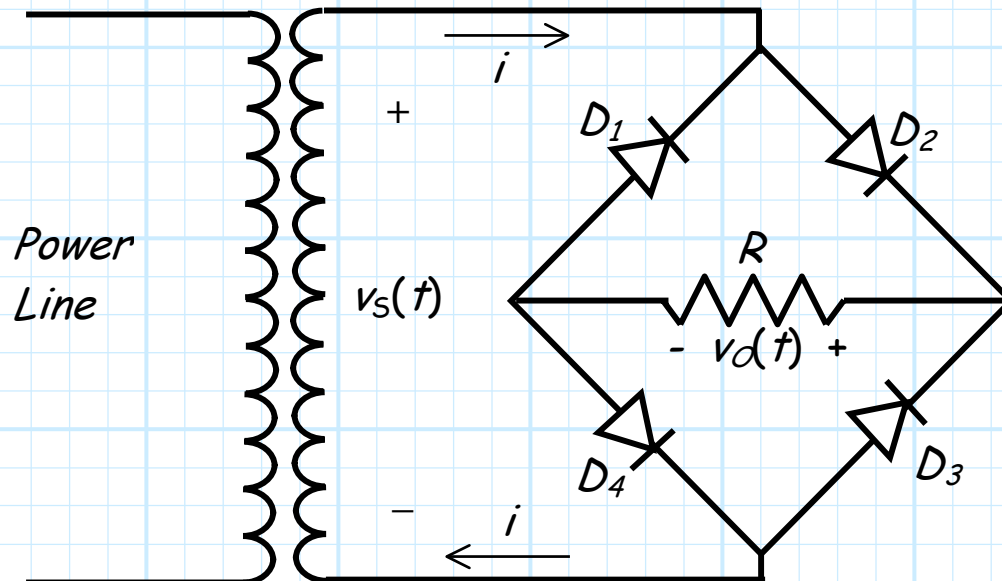
# The Bridge Rectifier

Now consider this **junction diode** rectifier circuit:



We call this circuit the **bridge rectifier**. Let's **analyze** it and see what it does!

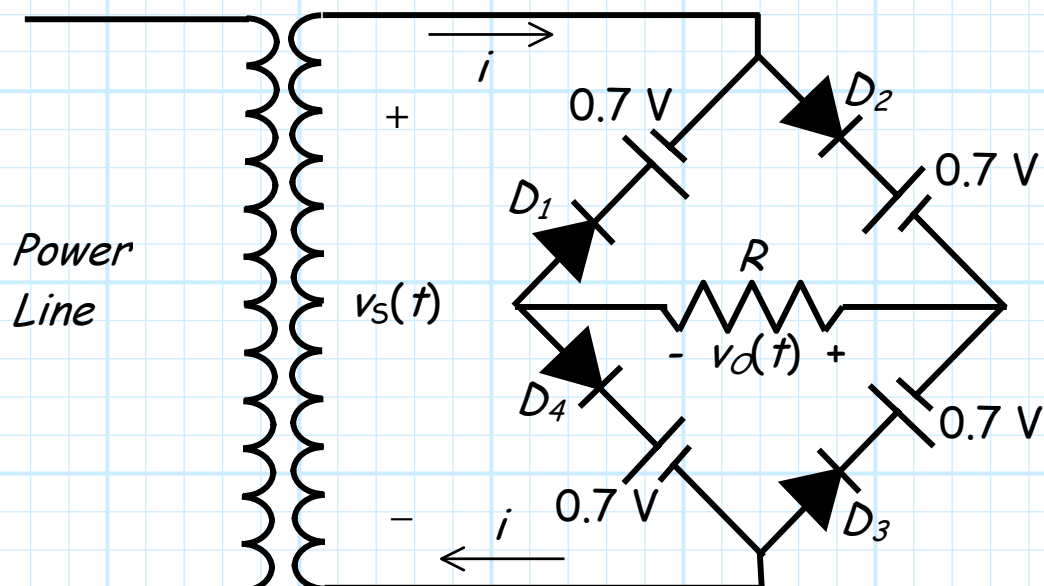First, we **replace** the junction diodes with the **CVD model**:





**Q:** *Four gul-durn ideal diodes! That means 16 sets of dad-gum assumptions!*

**A:** True! However, there are only **three** of these sets of assumptions are actually **possible!**

Consider the **current**  $i$  flowing through the rectifier. This current of course can be positive, negative, or zero. It turns out that there is only **one** set of diode assumptions that would result in positive current  $i$ , **one** set of diode assumptions that would lead to negative current  $i$ , and **one** set that would lead to zero current  $i$ .

**Q:** *But what about the remaining 13 sets of dog gone diode assumptions?*



**A:** **Regardless** of the value of source  $v_S$ , the remaining 13 sets of diode assumptions simply **cannot occur** for this particular circuit design!


Let's look at the **three** possible sets of assumptions:

$i > 0$

The rectifier current  $i$  can be **positive** only if these assumptions are true:

$D_1$  and  $D_3$  are reverse biased.

$D_2$  and  $D_4$  are forward biased.

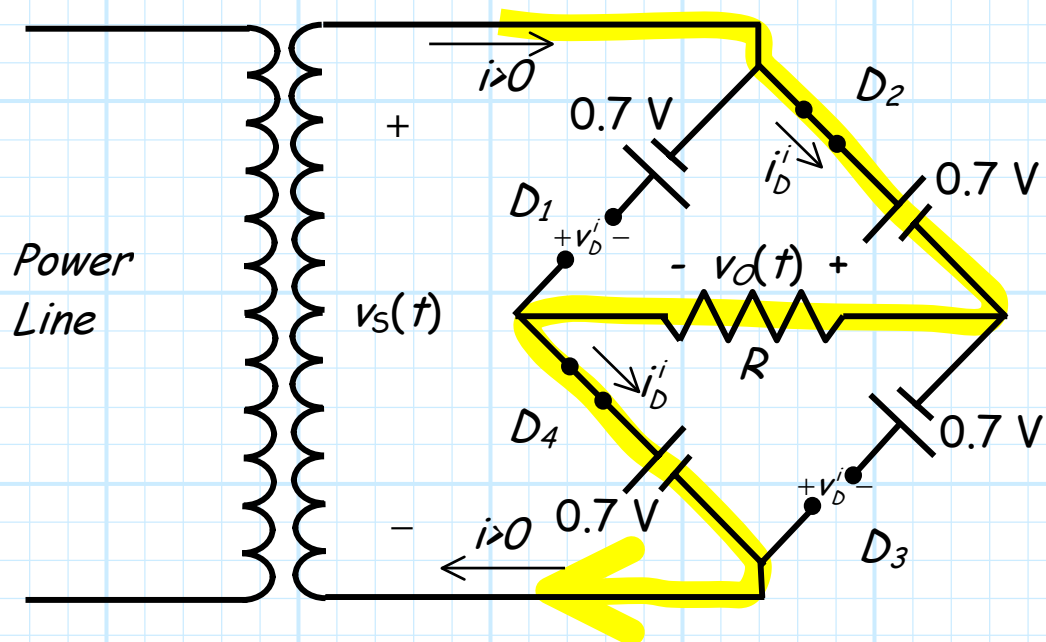

Analyzing this circuit, we find that the **output voltage** is:

$$v_o = v_s - 1.4 \text{ V}$$

and the f.b. ideal diode currents are:

$$i = i_D^j = \frac{v_s - 1.4}{R}$$

and, finally the r.b. **ideal diode voltages** are:

$$v_D^i = -v_S$$

Thus,  $i_D^i > 0$  when:

$$\frac{v_S - 1.4}{R} > 0$$

$$v_S - 1.4 > 0$$

$$v_S > 1.4 \text{ V}$$

and  $v_D^i < 0$  when:

$$-v_S < 0$$

$$v_S > 0$$

Therefore, we find that for this circuit:


$$v_O = v_S - 1.4 \text{ V} \quad \text{when} \quad v_S > 1.4 \text{ V}$$

$i < 0$

The rectifier current  $i$  can be **negative** only if these assumptions are true:

$D_1$  and  $D_3$  are forward biased.

$D_2$  and  $D_4$  are reverse biased.

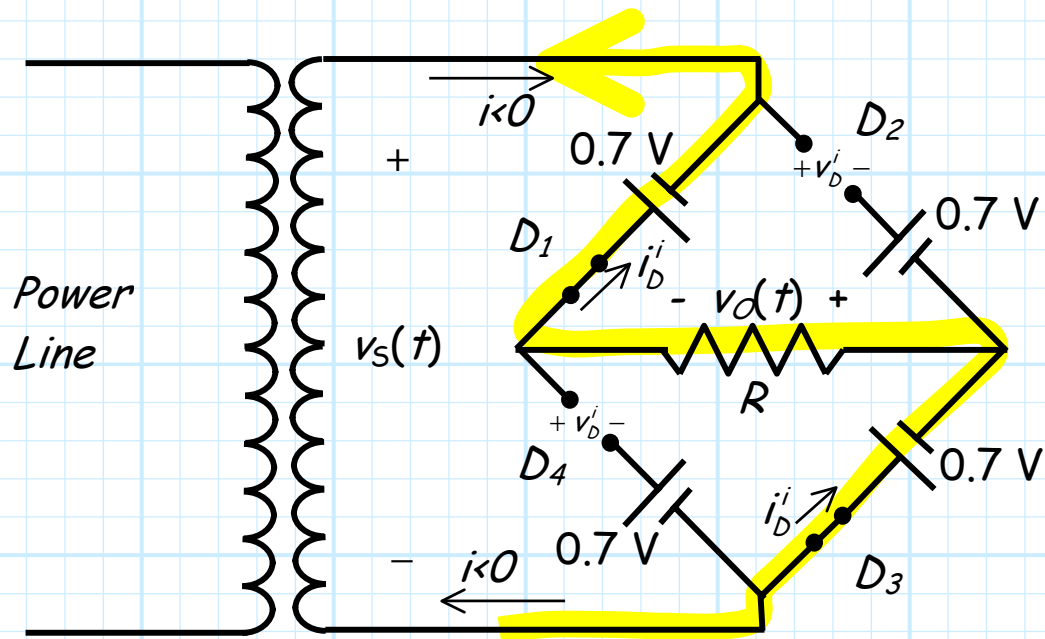

Analyzing this circuit, we find that the **output voltage** is:

$$v_o = -v_s - 1.4\text{ V}$$

while the f.b. **ideal diode currents** are both :

$$-i = i_D^i = \frac{-v_s - 1.4}{R}$$

and the r.b. **ideal diode voltages** are both:

$$v_D^i = v_s$$

Thus,  $i_D^i > 0$  when:

$$\frac{-v_s - 1.4}{R} > 0$$

$$-v_s - 1.4 > 0$$

$$-v_s > 1.4 \text{ V}$$

$$v_s < -1.4 \text{ V}$$

and,  $v_D^i < 0$  when:

$$v_s < 0$$


Therefore, we likewise find for this circuit:

$$v_o = -v_s - 1.4 \text{ V} \quad \text{when} \quad v_s < -1.4 \text{ V}$$

$i = 0$

The rectifier current  $i$  can be **zero** only if these assumptions are true:

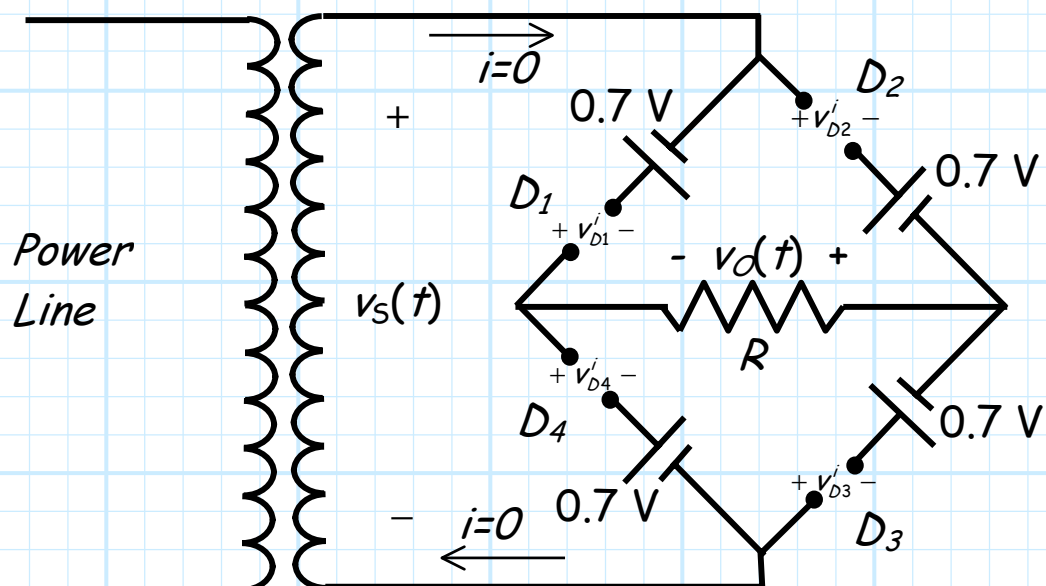**All** ideal diodes are **reverse** biased!





Analyzing this circuit, we find that the **output voltage** is:

$$v_o = Ri = 0$$

while the **ideal diode voltages** of  $D_2$  and  $D_4$  are each:

$$v_{D2}^i = \frac{v_s - 1.4}{2} = v_{D4}^i$$

and the **ideal diode voltages** of  $D_1$  and  $D_3$  are each:

$$v_{D1}^i = \frac{-v_s - 1.4}{2} = v_{D3}^i$$

Thus,  $v_{D2}^i < 0$  when:

$$\begin{aligned} \frac{v_s - 1.4}{2} &< 0 \\ v_s - 1.4 &< 0 \\ v_s &< 1.4 \end{aligned}$$

and,  $v_{D1}^i < 0$  when:

$$\begin{aligned} \frac{-v_s - 1.4}{2} &< 0 \\ -v_s - 1.4 &< 0 \\ -v_s &< 1.4 \\ v_s &> -1.4 \end{aligned}$$

Therefore, we also find for this circuit that:


$$v_o = 0 \quad \text{when both } v_s < 1.4\text{V and } v_s > -1.4\text{V } (-1.4 < v_s < 1.4\text{V})$$



**Q:** You know, that dang *Mizzou* grad said we only needed to consider these **three** sets of diode assumptions, yet I am **still** concerned about the other 13. How can we be **sure** that we have analyzed every **possible** set of **valid** diode assumptions?


**A:** We know that we have considered **every** possible case, because when we combine the three results we find that we have a piece-wise linear **function!** I.E.;
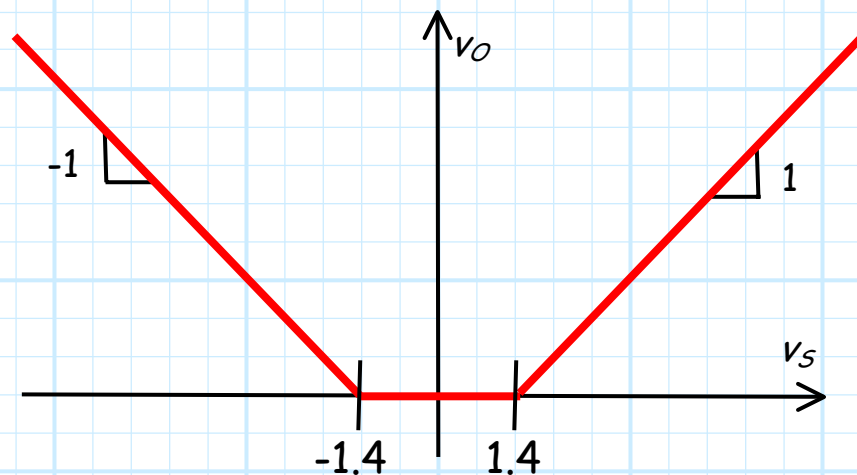
$$v_o = \begin{cases} -v_s - 1.4 \text{ V} & \text{if } v_s < -1.4 \text{ V} \\ 0 & \text{if } -1.4 < v_s < 1.4 \text{ V} \\ v_s - 1.4 \text{ V} & \text{if } v_s > 1.4 \text{ V} \end{cases}$$



Note that the **bridge** rectifier is a **full-wave** rectifier!

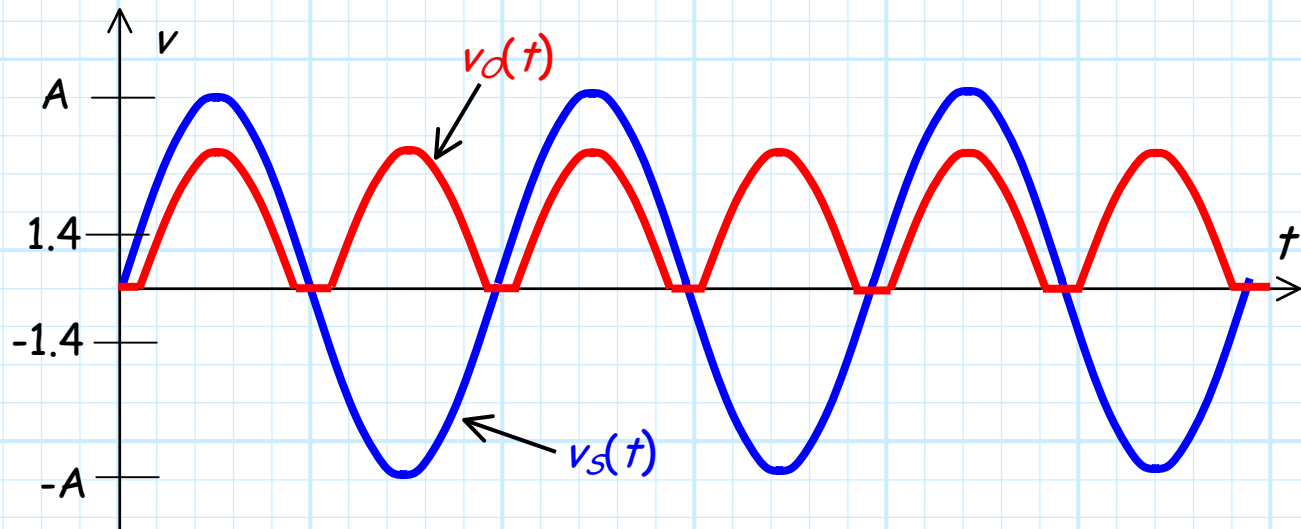If the input to this rectifier is a **sine wave**, we find that the **output** is approximately that of an ideal **full-wave rectifier**:




We see that the junction diode bridge rectifier output is **very close** to ideal. In fact, if  $A \gg 1.4$  V, the **DC component** of this junction diode bridge rectifier is approximately:

$$V_o \approx \frac{2A}{\pi} - 1.4 \text{ V}$$

**Just 1.4 V less** than the **ideal** full-wave rectifier DC component!
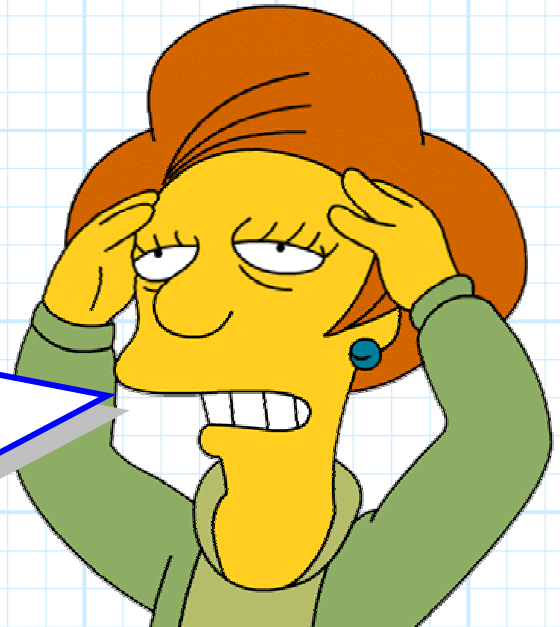
# Peak Inverse Voltage

**Q:** *I'm so confused! The bridge rectifier and the full-wave rectifier **both** provide full-wave rectification. Yet, the bridge rectifier use **4** junction diodes, whereas the full-wave rectifier only uses **2**. Why would we **ever** want to use the **bridge rectifier**?*



**A:** First, a slight **confession**—the results we derived for the bridge and full-wave rectifiers are **not** precisely correct!

Recall that we used the junction diode **CVD model** to determine the transfer function of each rectifier circuit. The problem is that the CVD model does **not** predict **junction diode breakdown**!

If the **source** voltage  $v_S$  becomes too **large**, the junction diodes can in fact **breakdown**—but the transfer functions we derived do **not** reflect this fact!

**Q:** *You mean that we must **rework** our analysis and find **new** transfer functions!?*



**A:** Fortunately **no**. Breakdown is an **undesirable** mode for circuit rectification. Our job as engineers is to design a rectifier that **avoids** it—that why the **bridge** rectifier is helpful!

To see why, consider the voltage across a **reversed biased** junction diode in **each** of our rectifier circuit designs.

Recall that the voltage across a **reverse biased ideal diode** in the **full-wave rectifier** design was:

$$v_{D2}' = -2v_S$$

so that the voltage across the **junction diode** is approximately:


$$\begin{aligned} v_D &= v_D' + 0.7 \\ &= -2v_S + 0.7 \end{aligned}$$

Now, assuming that the **source** voltage is a **sine wave**  $v_S = A \sin \omega t$ , we find that diode voltage is at it **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value  $A$ . I.E.;

$$v_D^{min} = -2A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in **forward** bias:

$$v_D^{max} = 0.7 \text{ V}$$

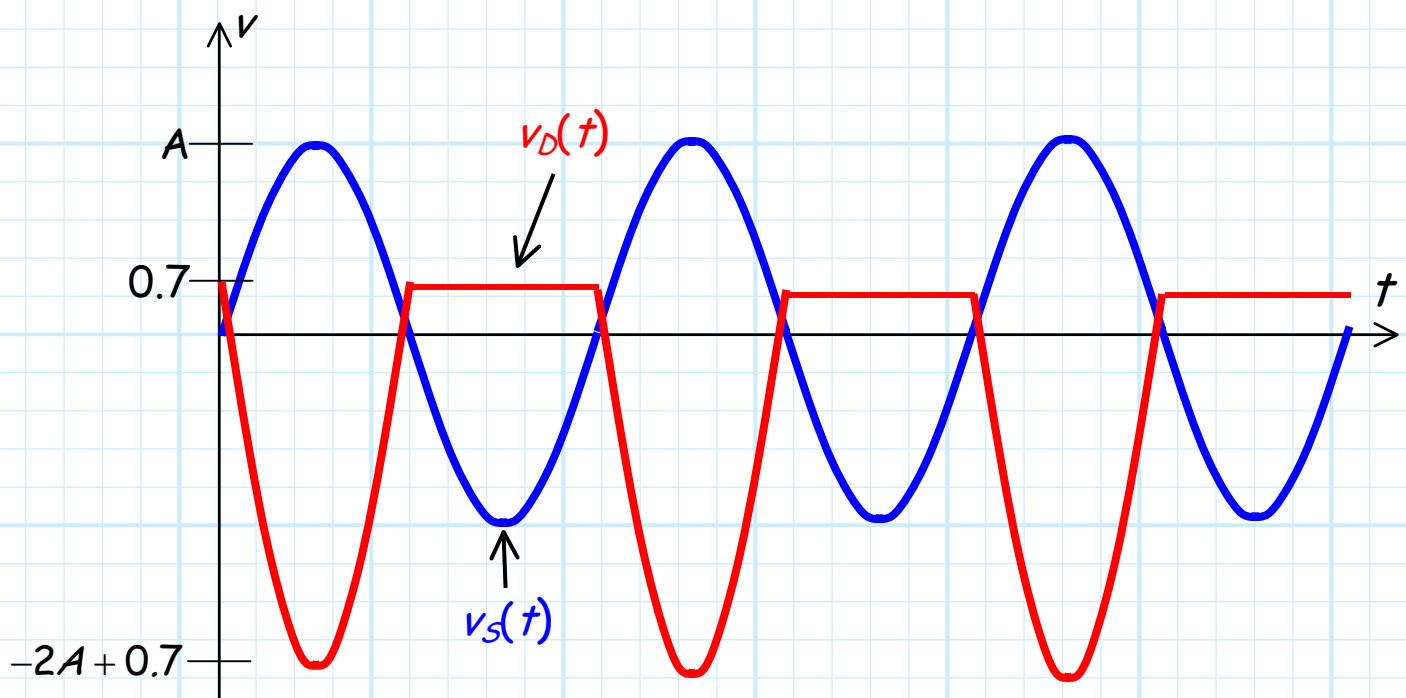

Note that this **minimum** diode voltage  $v_D$  is **very negative**, with an absolute value ( $|v_D^{min}| = 2A - 0.7$ ) nearly **twice** as large as the source magnitude  $A$ .

We call the absolute value of the minimum diode voltage the **Peak Inverse Voltage (PIV)**:

$$PIV = |v_D^{min}|$$

Note that this value is dependent on **both** the rectifier design **and** the magnitude of the source voltage  $v_s$ .



**Q:** *So, why do we need to determine PIV? I'm not sure I see what difference this value makes.*

**A:** The Peak Inverse Voltage **answers** one important question—**will** the junction diodes in our rectifier **breakdown**?

→ **If** the PIV is **less** than the Zener breakdown voltage of our rectifier diodes (i.e., if  $PIV < V_{ZK}$ ), then we know that our junction diodes will **remain** in either forward or reverse bias for all time  $t$ . The rectifier will operate “properly”!

→ However, **if** the PIV is **greater** than the Zener breakdown voltage of our rectifier diodes (i.e., if  $PIV > V_{ZK}$ ), then we know that our junction diodes will **breakdown** for at least **some** small amount of time  $t$ . The rectifier will **NOT** operate properly!



**Q:** So what do we do if PIV is greater than  $V_{ZK}$ ? How do we fix this problem?

**A:** We have **two** possible **solutions**:

1. Use junction diodes with **larger** values of  $V_{ZK}$  (if they exist!).
2. Use the **bridge** rectifier design.

**Q:** The **bridge** rectifier! How would that solve our **breakdown** problem?



**A:** To see how a **bridge** rectifier can be **useful**, let's determine its Peak Inverse Voltage **PIV**.

First, we recall that the voltage across the **reverse biased ideal diodes** was:

$$v_D^i = -v_S$$

so that the voltage across the **junction diode** is approximately:

$$\begin{aligned} v_D &= v_D^i + 0.7 \\ &= -v_S + 0.7 \end{aligned}$$


Now, assuming that the **source** voltage is a **sine wave**  $v_S = A \sin \omega t$ , we find that diode voltage is at its **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value  $A$ . I.E.:

$$v_D^{min} = -A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in forward bias:

$$v_D^{max} = 0.7 \text{ V}$$



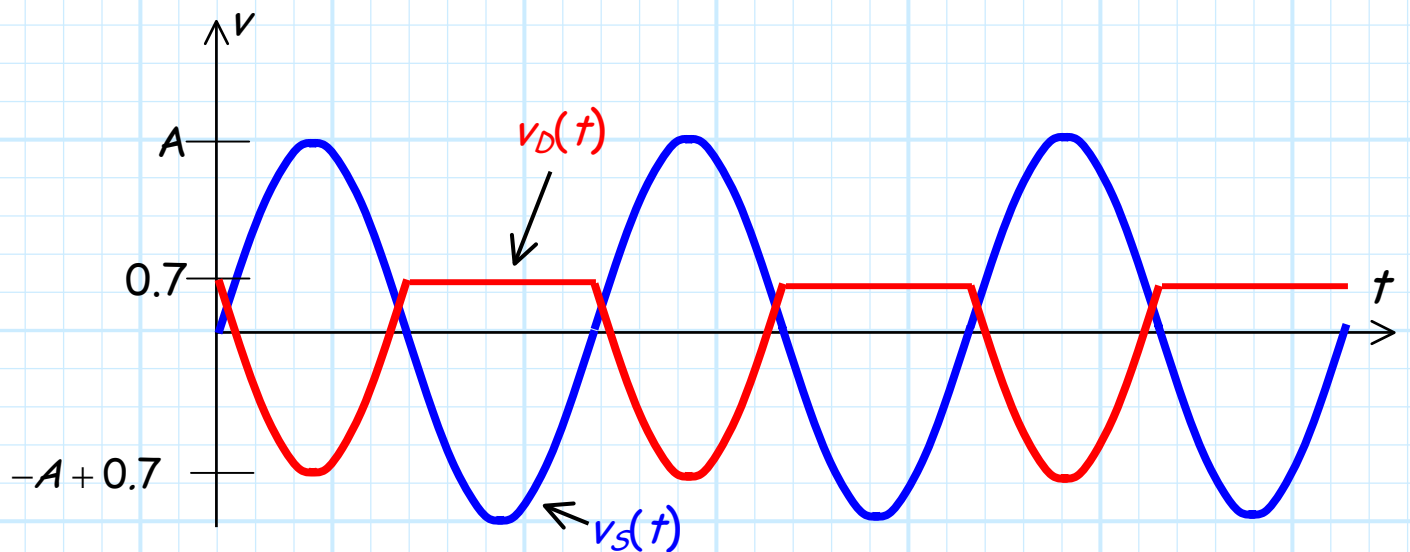

Note that this minimum diode voltage is **very negative**, with an absolute value ( $|v_D^{min}| = A - 0.7$ ), approximately **equal** to the value of the **source magnitude A**.

Thus, the **PIV** for a **bridge** rectifier with a **sinusoidal source** voltage is:

$$PIV = A - 0.7$$

Note that this **bridge** rectifier value is approximately **half** the PIV we determined for the **full-wave** rectifier design!

Thus, the source voltage (and the output DC component) of a **bridge** rectifier can be **twice** that of the full-wave rectifier design—this is why the **bridge** rectifier is a very **useful** rectifier design!