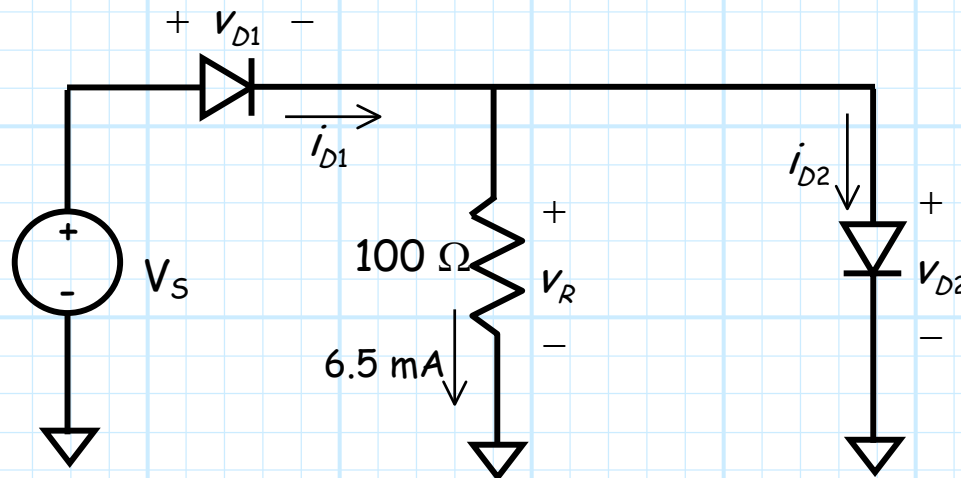


Example: A Junction Diode Circuit

Consider the following circuit with two junction diodes:




The diodes are identical, with $n = 1$ and $I_S = 10^{-14}\ \text{A}$.

Q: *If the current through the resistor is $6.5\ \text{mA}$, what is the voltage of source V_S ??*

A: This is a **difficult** problem to solve ! Certainly, we cannot just write:

$$V_S =$$

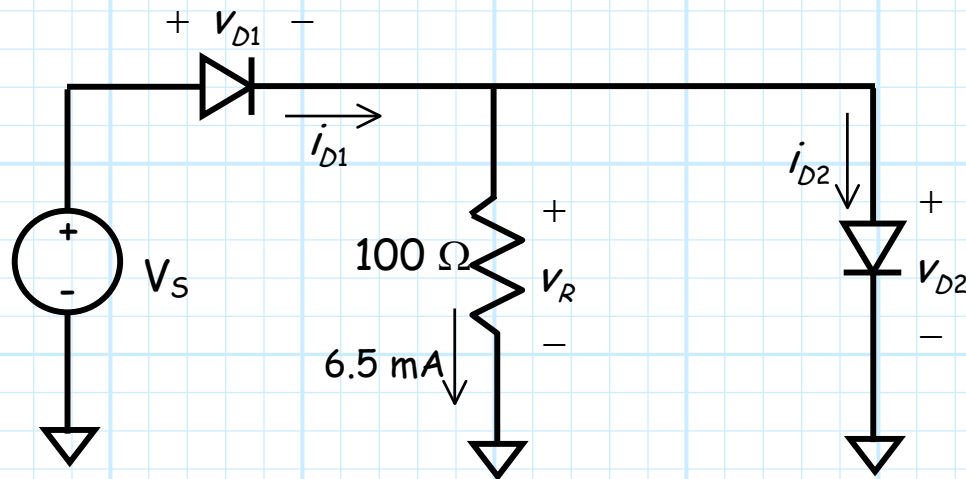and then the answer. Instead, let's just determine **what we can**, and see what happens !



- 1) If 6.5 mA flows through a 0.1 K resistor, the voltage across that resistor is:

$$V_R = 0.1(6.5) = 0.65\ \text{V}$$

- 2) If the voltage across the resistor is 0.65 V, then the voltage across the diode D_2 , which is **parallel** to the resistor, is the **same** value:


$$V_{D2} = V_R = 0.65\ \text{V}$$

- 3) If we know the **voltage** across a p-n junction diode, then we also know its **current** !

$$i_{D2} = I_S \exp\left[\frac{V_{D2}}{nV_T}\right] = 10^{-14} \exp\left[\frac{0.650}{0.025}\right] = 1.96\ \text{mA}$$

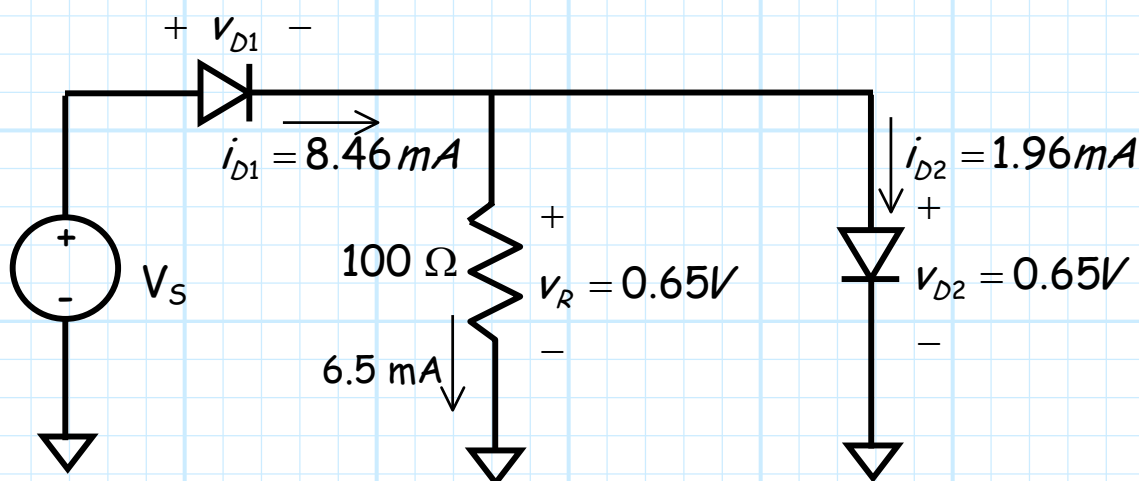- 4) If we know i_{D2} and the current through the resistor, we know (using KCL) the current through D_1 :

$$\begin{aligned} i_{D1} &= 6.5 + i_{D2} \\ &= 6.5 + 1.96 \\ &= 8.46\ \text{mA} \end{aligned}$$



5) If we know the **current** through a junction diode, then we can find the **voltage** across it:

$$v_{D1} = nV_T \ln\left(\frac{i_{D1}}{I_S}\right) = 0.025 \ln\left(\frac{0.00846}{10^{-14}}\right) = 0.69 \text{ V}$$

6) Finally, if we know v_{D1} and v_{D2} , we can find V_S using KVL:

$$V_S = v_{D1} + v_{D2} = 0.69 + 0.65 = 1.34 \text{ V}$$

