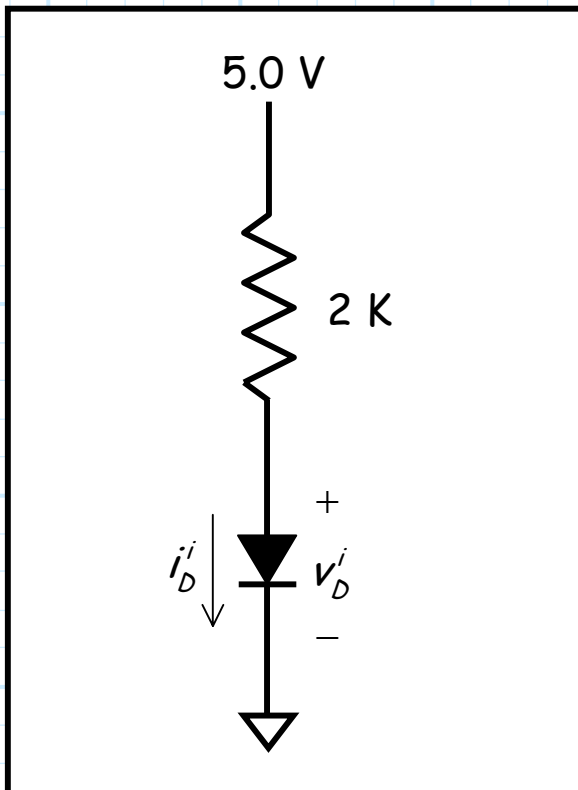


Example: A Simple Ideal Diode Circuit

Consider this simple circuit that includes an **ideal** diode:




Q: What are i_D^i and v_D^i ?

A: Follow the five easy analysis steps!

Step 1: Let's *ASSUME* the ideal diode is **reverse biased** (we're just guessing!).

Step 2: We therefore *ENFORCE* $i_D^i = 0$ by replacing the ideal diode with an **open circuit**.

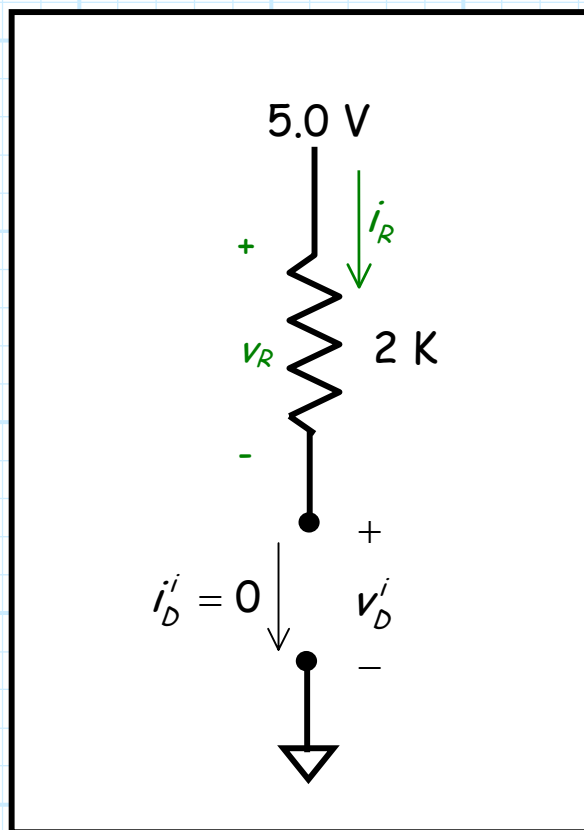Step 3: Now we *ANALYZE* the circuit; finding the value of v_D^i .



$$5.0 - v_R - v_D^i = 0 \quad (\text{KVL})$$

$$\therefore v_D^i = 5.0 - v_R$$

$$i_R = i_D^i \quad (\text{KCL})$$

$$v_R = 2 i_R \quad (\text{Ohm's})$$

$$i_D^i = 0 \quad (\text{enforced})$$


$$\therefore i_R = 0$$

$$\therefore v_R = 2(0) = 0$$

$$\therefore v_D^i = 5.0 - 0 = 5.0 \text{ V}$$

Step 4: Now let's CHECK our result. \Rightarrow Is $v_D^i < 0$??

$$v_D^i = 5.0 > 0$$

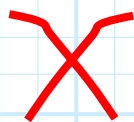


We must change our assumption, and then **start over** (Doh!).

1) Now *ASSUME* the ideal diode is **forward biased** (what's left?).

2) We therefore *ENFORCE* $v_D^i = 0$ by replacing the ideal diode with an **short** circuit.

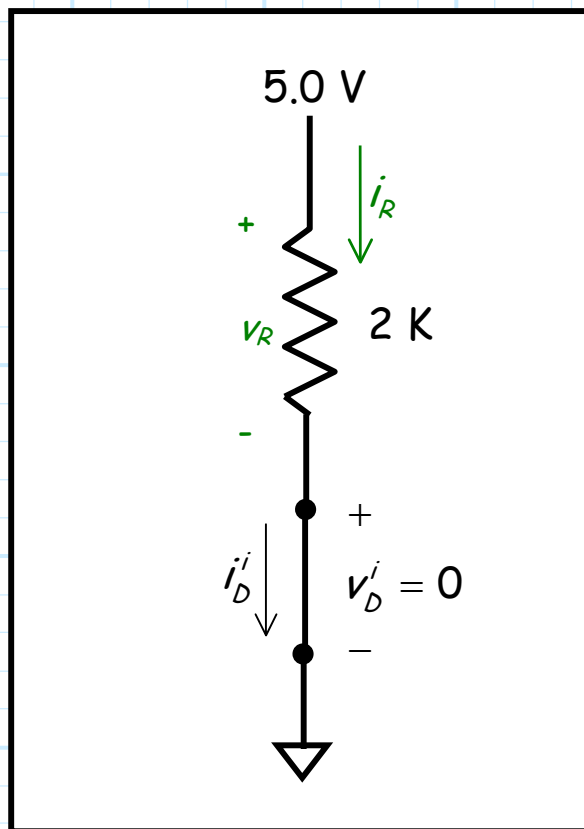3) Now we *ANALYZE* the circuit; finding the value of i_D^i .



$$5.0 - v_R - v_D^i = 0 \quad (\text{KVL})$$

$$\therefore v_R = 5.0 - v_D^i$$

$$i_D^i = i_R \quad (\text{KCL})$$

$$i_R = v_R / 2 \quad (\text{Ohm's})$$

$$v_D^i = 0 \quad (\text{enforced})$$

$$\therefore v_R = 5.0 - 0 = 5.0 \text{ V}$$

$$\therefore i_R = 5.0 / 2 = 2.5 \text{ mA}$$

$$\therefore i_D^i = 2.5 \text{ mA}$$

4) Now, let's *CHECK* our result. \Rightarrow **Is $i_D^i > 0$??**

$$i_D^i = 2.5 \text{ mA} > 0 \quad \checkmark$$

Our assumption is correct !

Therefore, in this circuit, we now **know** that:

$$v_D^i = 0 \quad \text{and} \quad i_D^i = 2.5 \text{ mA}$$