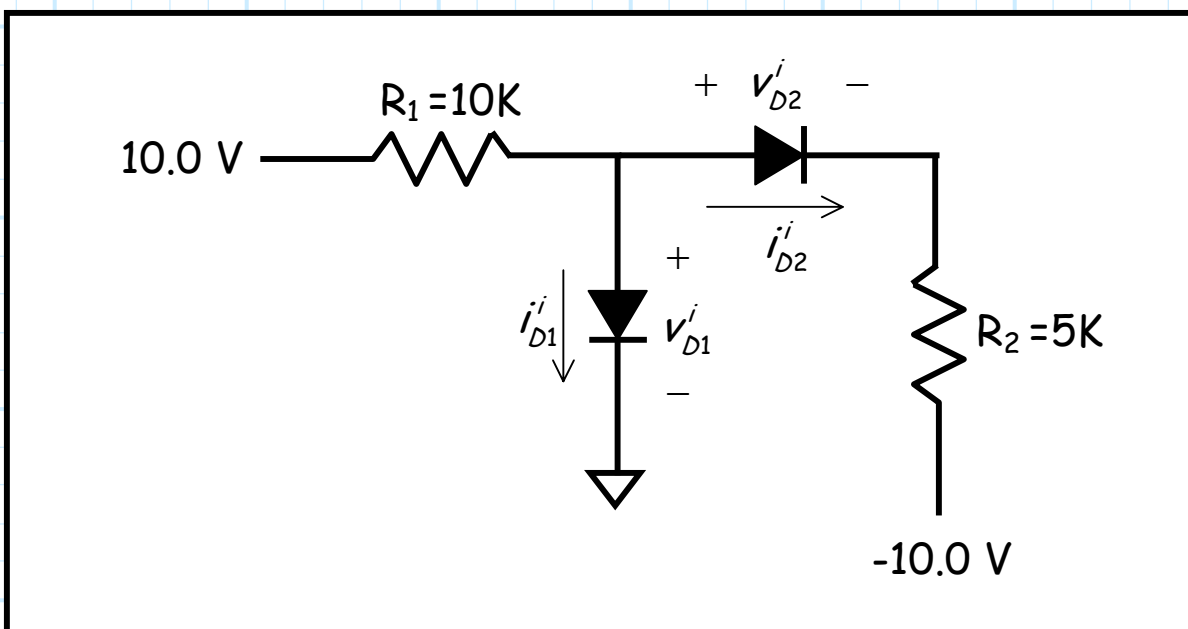


Example: Analysis of a Complex Diode Circuit

Consider this circuit with **two ideal diodes**:




Let's analyze this circuit and find v_{D1}^i , i_{D1}^i , v_{D2}^i , and i_{D2}^i !

Remember, we must accomplish each of the **five** steps:

Step 1: *ASSUME* that both D_1 and D_2 are "on" (might as well!).

Step 2: *ENFORCE* the equalities $v_{D1}^i = 0 = v_{D2}^i$, by replacing each ideal diode with a **short** circuit.

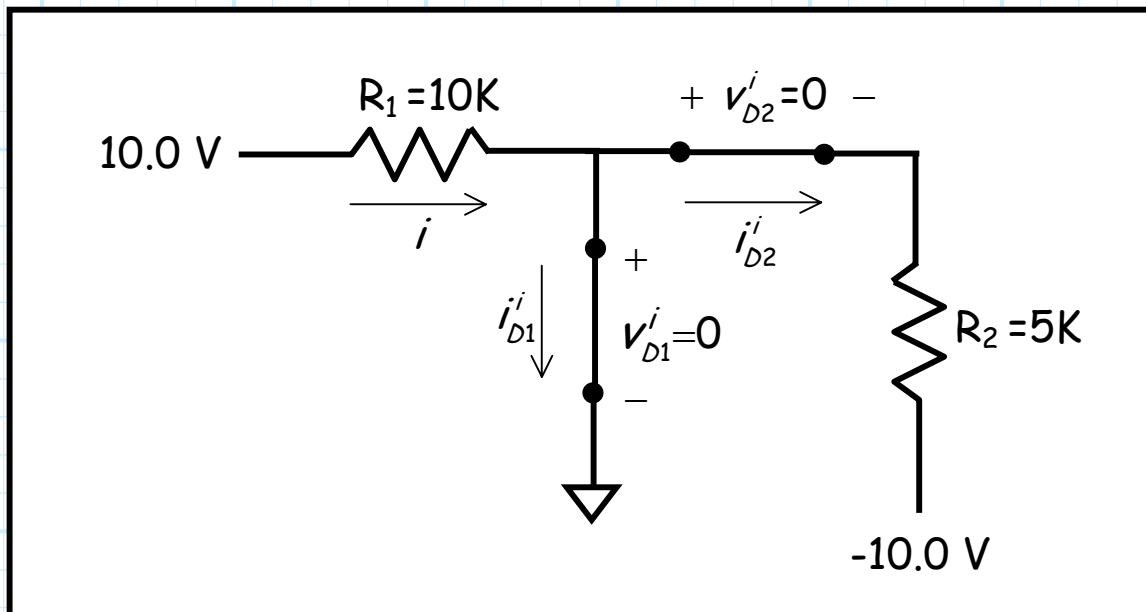Step 3: *ANALYZE* the resulting circuit, and find i_{D1}^i and i_{D2}^i .



Begin with **KCL**:

$$i = i_{D1}^i + i_{D2}^i$$

where
$$i = \frac{10.0 - 0}{10} = 1.0 \text{ mA}$$

and
$$i_{D2}^i = \frac{0 - (-10)}{5} = \frac{10}{5} = 2.0 \text{ mA}$$

Therefore,
$$i_{D1}^i = i - i_{D2}^i = 1.0 - 2.0 = -1.0 \text{ mA}$$


Step 4: Now we must *CHECK inequalities* to see if our assumptions are correct!

$$i_{D1}^i = -1.0 \text{ mA} < 0 \quad \times$$

$$i_{D2}^i = 2.0 \text{ mA} > 0 \quad \checkmark$$



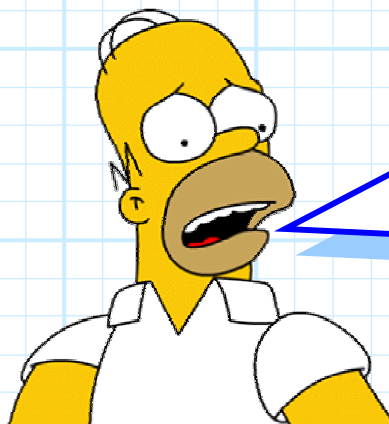One assumption is therefore **INCORRECT**. We must proceed to **step 5**—change our assumptions and **completely** start again!



Q: *Wait a second! We don't have to **completely** start from the beginning, do we? After all, our assumption about diode D_2 turned out to be **true**—so we **already** know that $i_{D2}^i = 2.0$ and $v_{D2}^i = 0$, right?*


A: **NO!** The solution for diode D_2 is dependent on the state of both diodes D_1 and D_2 . If the assumption of just **one** diode turns out to be incorrect, then the solutions for **all** diodes are **wrong!**

So, let's change our assumption and start all over again!

Step 1: Now *ASSUME* that D_1 is "off" and D_2 is "on".

Step 2: *ENFORCE* $i_{D1}^i = 0$ (D_1 open) and $v_{D2}^i = 0$ (D_2 short).

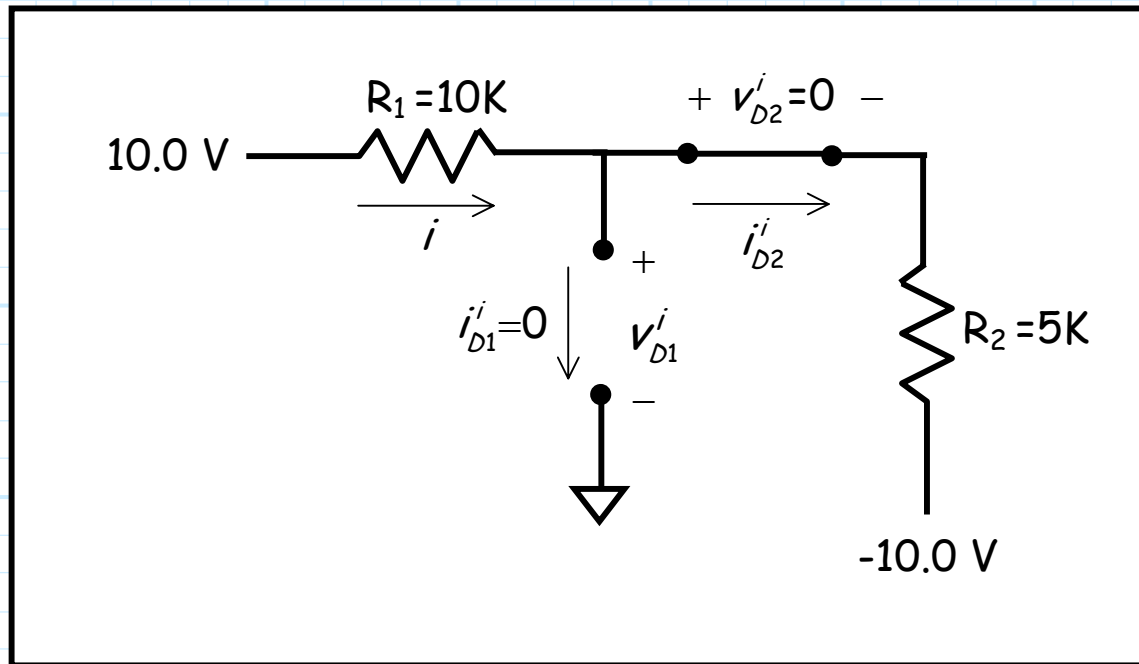Step 3: *ANALYZE* resulting circuit, and find v_{D1}^i and i_{D2}^i .



$$\text{Note } i = i_{D2}^i = \frac{10.0 - (-10.0)}{10 + 5} = \frac{20.0}{15} = 1.33 \text{ mA}$$

and from KVL:

$$10.0 - 10i - v_D^i = 0$$

$$10.0 - 10(1.33) - v_D^i = 0$$

$$\therefore v_D^i = 10.0 - 10(1.33) = -3.33 \text{ V}$$

4) CHECK our assumptions.

$$i_{D2}^i = 1.33 \text{ mA} > 0 \quad \checkmark$$

$$v_{D1}^i = -3.33 \text{ V} < 0 \quad \checkmark$$

\therefore Assumptions are **correct!** We are finished!



$$v_{D1}^i = -3.33 \text{ V}$$

$$i_{D1}^i = 0$$

$$v_{D2}^i = 0$$

$$i_{D2}^i = 1.33 \text{ mA}$$