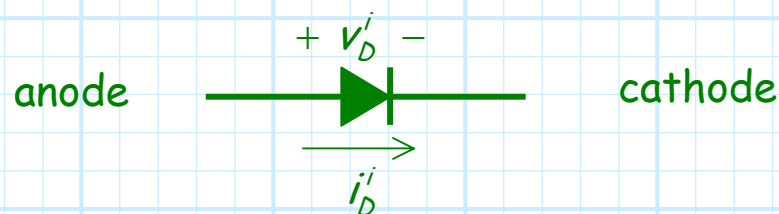


3.1 The Ideal Diode (pp.139-141)

Diodes: The most fundamental non-linear circuit element

A. The Ideal Diode Symbol



Note:

1. Device is not symmetric!
2. Positive current defined as flowing from anode to cathode.
3. Voltage across diode defined as positive when anode voltage $>$ cathode voltage.


B. Ideal Diode Behavior

The ideal diode \rightarrow a close approx. of a physical diode.

First, let's recall linear device behavior!

HO: Linear Device Behavior

For an ideal diode:

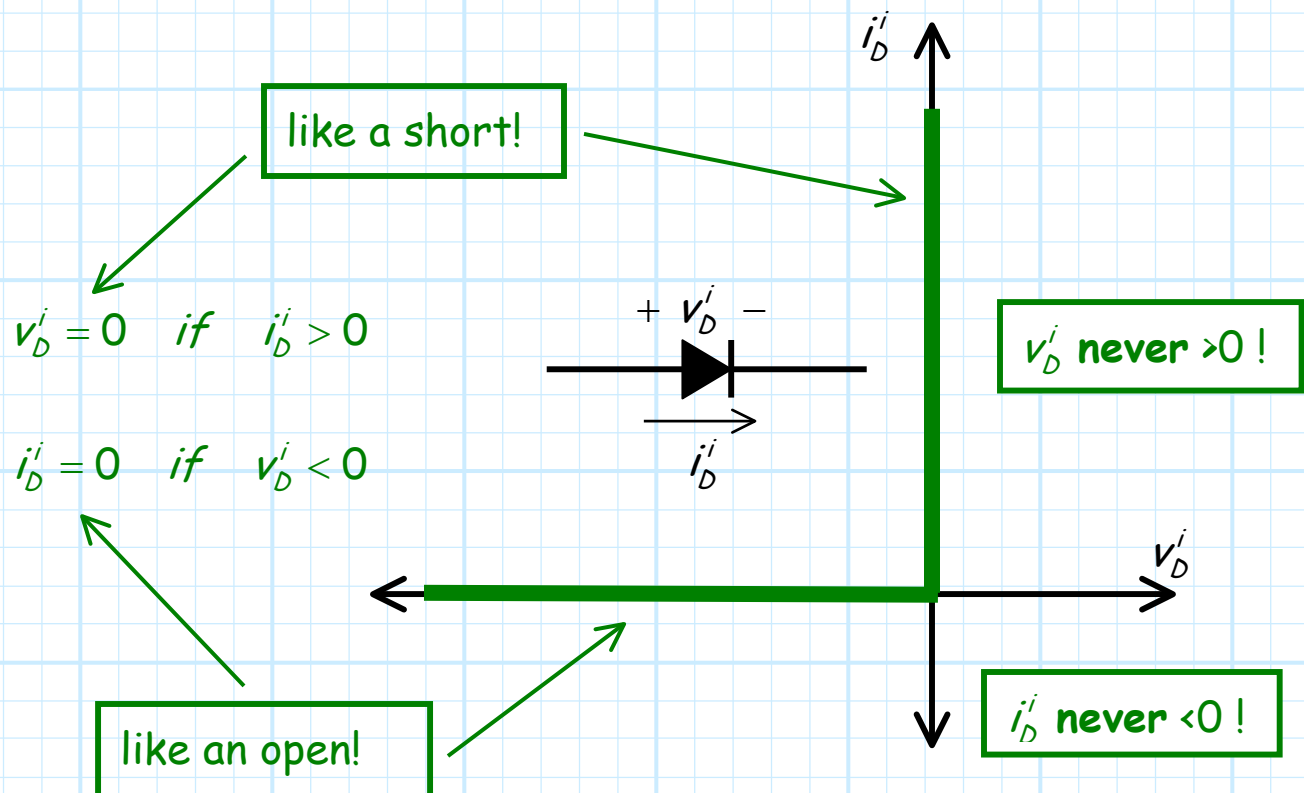

The Ideal Diode is non-linear!

C. Diode Bias Regions

Ideal diode operates in one of two states:

1) **Forward Biased** \rightarrow "on" or "active"

$$v_D^i = 0 \quad \text{if} \quad i_D^i > 0$$

i.e., acts as a short, IF current is positive.

2) Reverse Biased → "off" or "inactive"

$$i_D^i = 0 \quad \text{if} \quad v_D^i < 0$$

i.e., acts as a open, IF voltage is negative.

Note: No power is dissipated in either mode!

$$\rightarrow P_D^i = v_D^i i_D^i = 0 \quad \text{always!}$$

HO The Ideal Diode

HO Diode Mechanical Analogy


Q: What turns a diode "on" or "off"?

A: The circuit attached to it!


Problem: It is very difficult to determine what the circuit is trying to do!

D. Ideal Diode Circuit Analysis

Consider this ideal diode circuit:

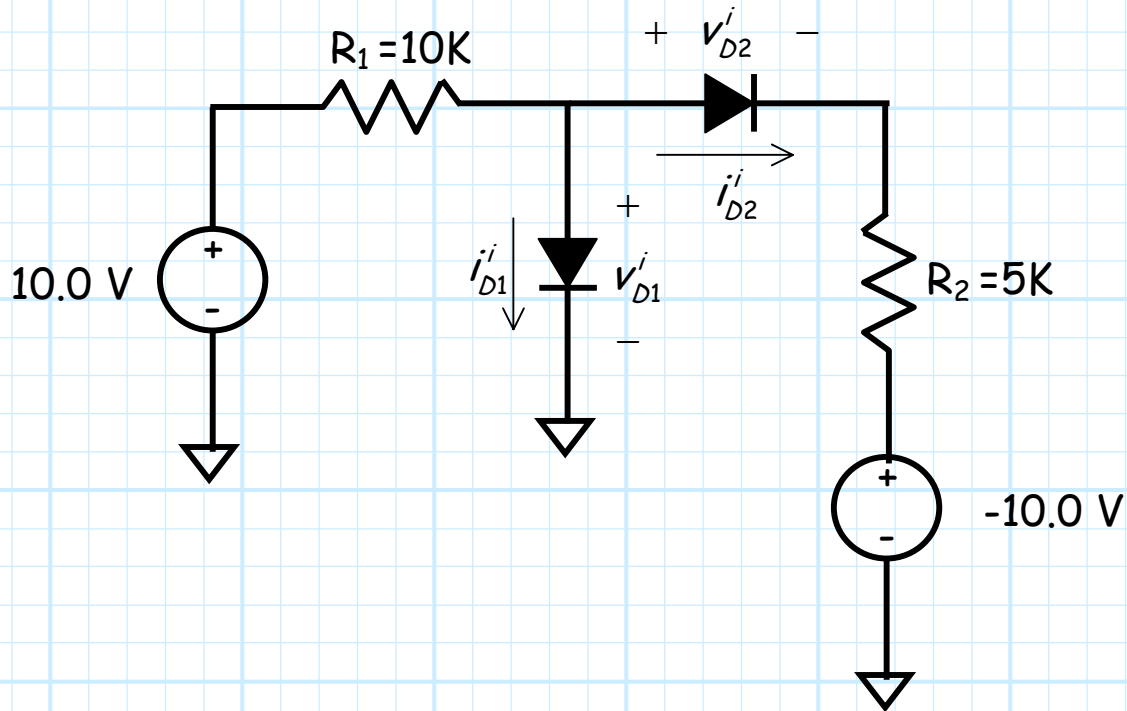

Which we more compactly write as:

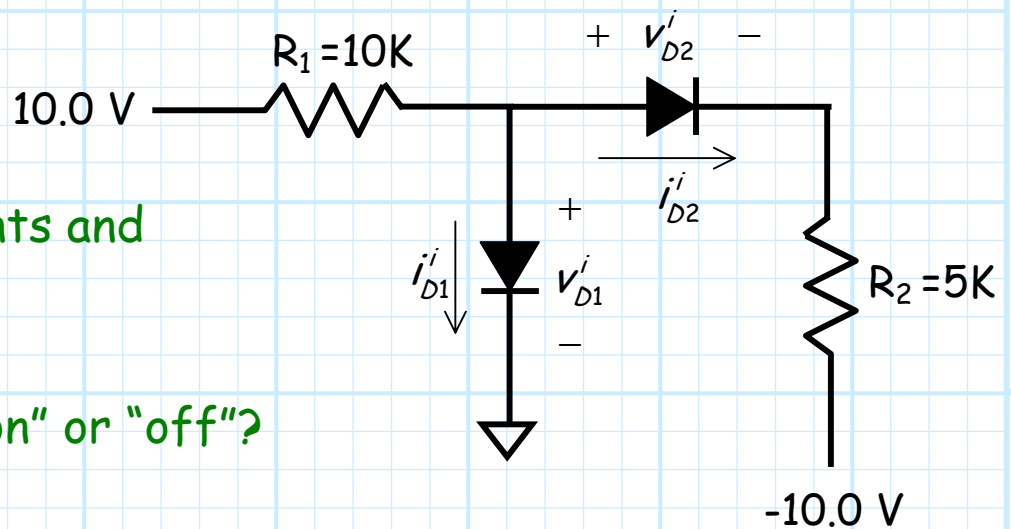

What are currents and Voltages ?

Q: Are diodes "on" or "off"?

A: Can't tell! We must GUESS !!!


HO: The Ideal Diode Circuit Analysis Guide

HO: Example: A Simple Ideal Diode Circuit


HO: Example: Analysis of a Complex Diode Circuit

Linear Device Behavior

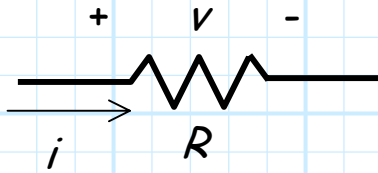
1) Recall the circuit behavior of a **resistor**:




$$i = \frac{V}{R}$$

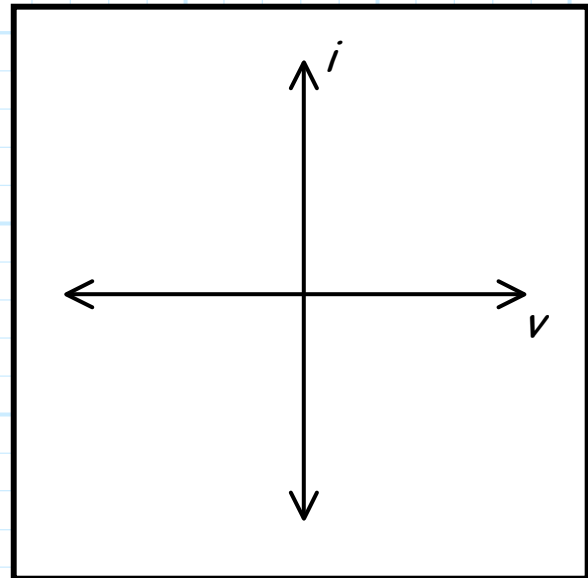

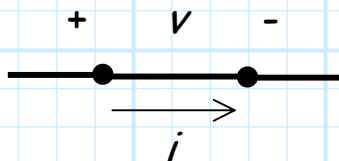2) If $R=0$, then we have a **short circuit**:




$$V = 0$$

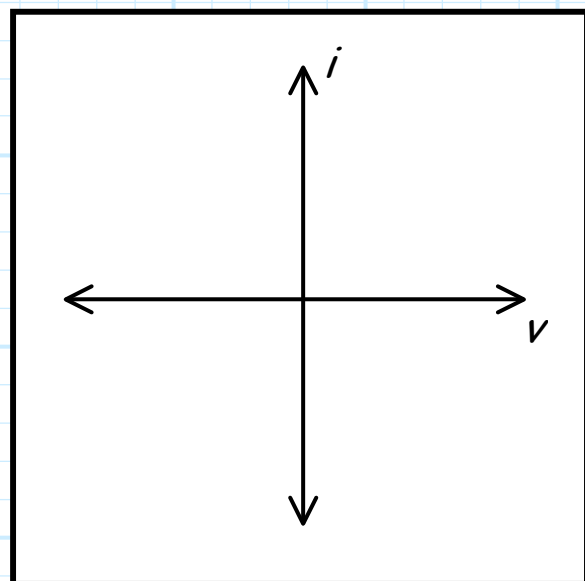


Linear Device Behavior

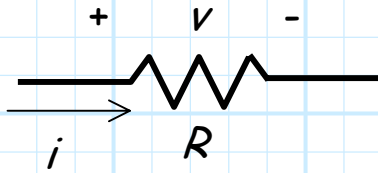
1) Recall the circuit behavior of a **resistor**:




$$i = \frac{V}{R}$$

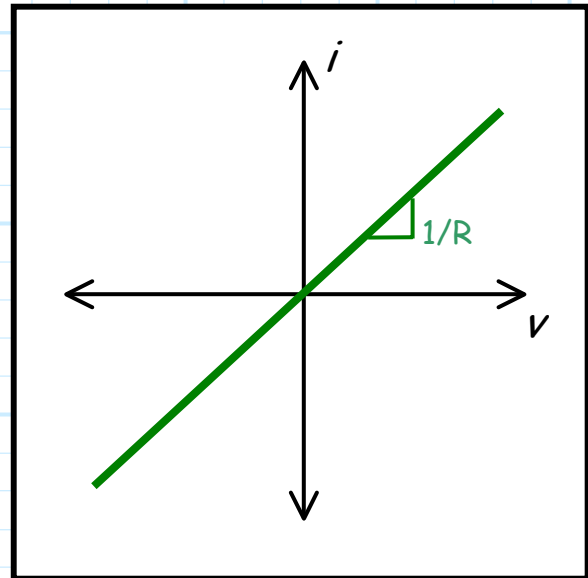


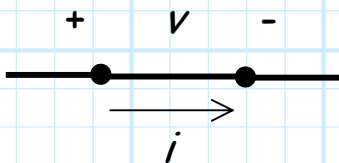
2) If $R=0$, then we have a **short circuit**:







$$V = 0$$

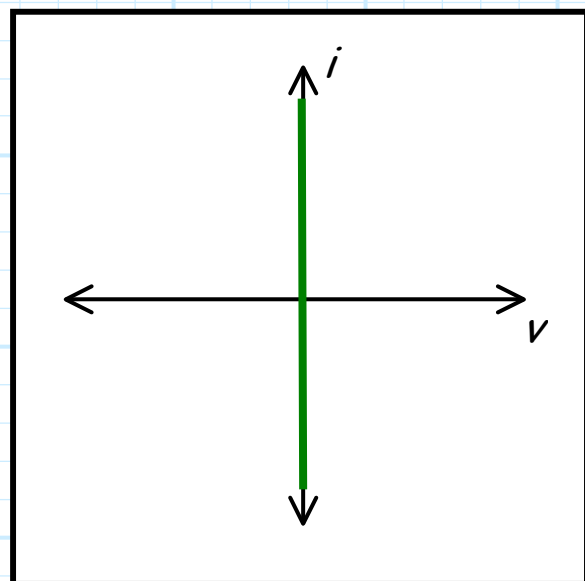

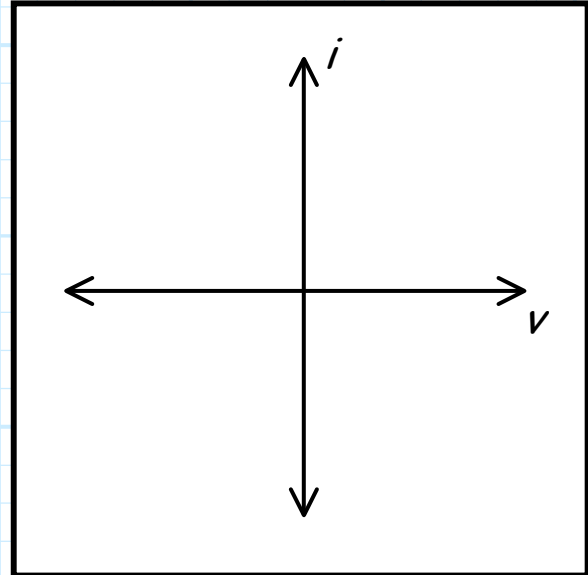
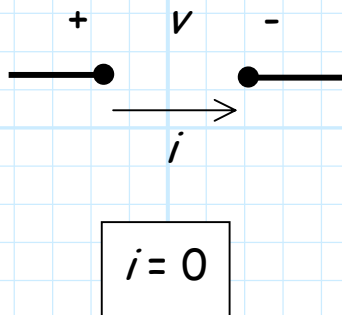
3) If $R = \infty$, then we have a **open circuit**:



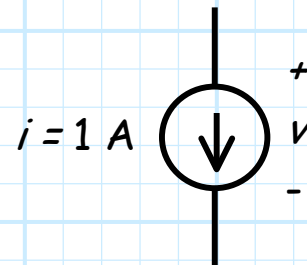
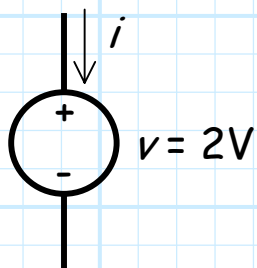
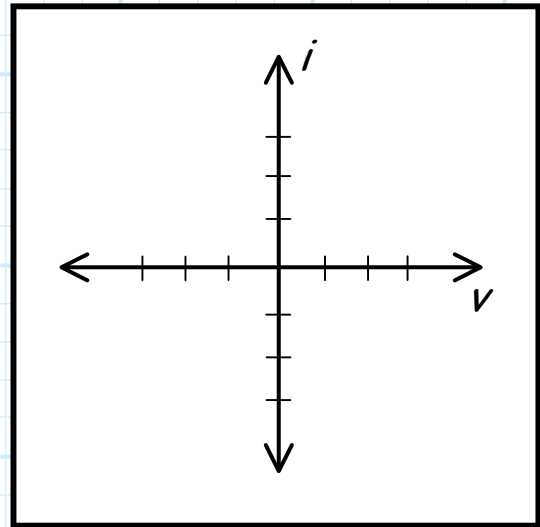
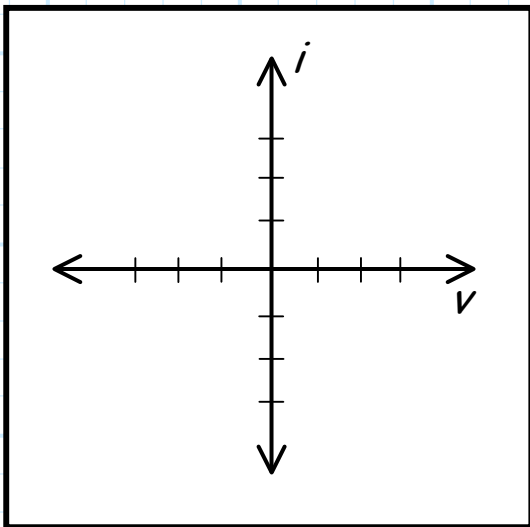
4) We can also plot the behavior of both current and voltage sources:



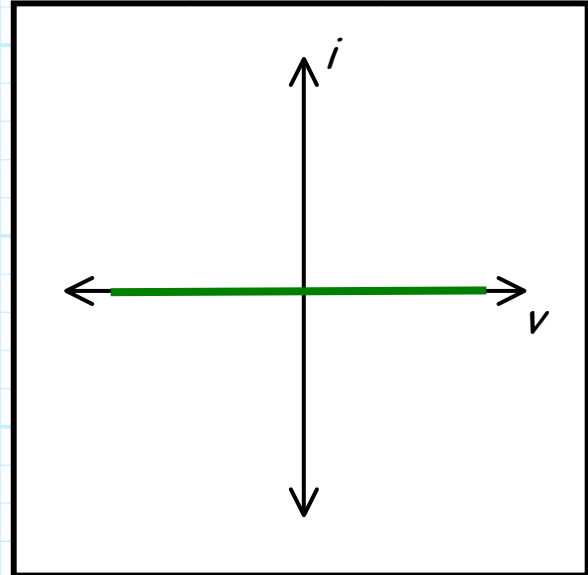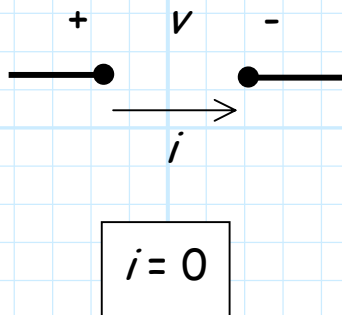3) If $R = \infty$, then we have a **open circuit**:



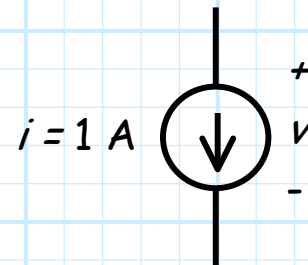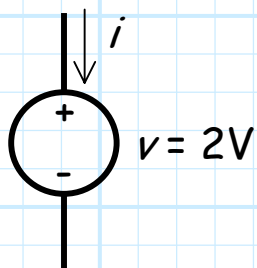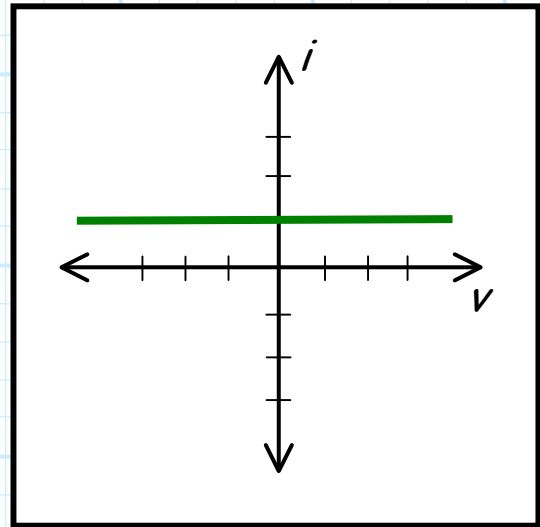
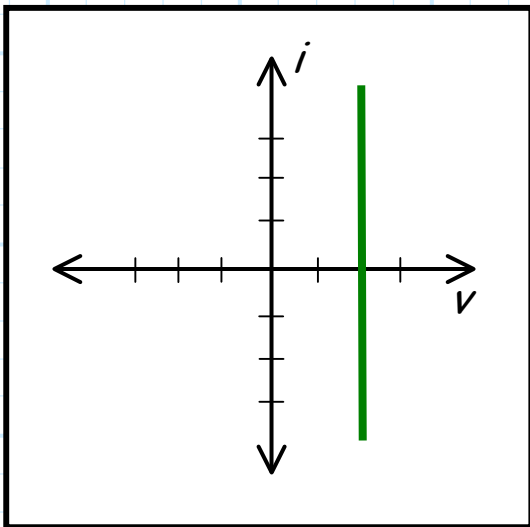
4) We can also plot the behavior of both current and voltage sources:



The Ideal Diode

An **ideal diode**—the circuit device with a split personality!

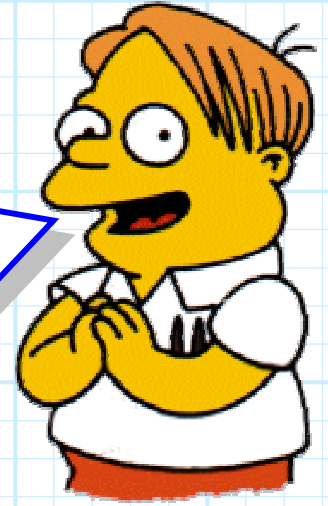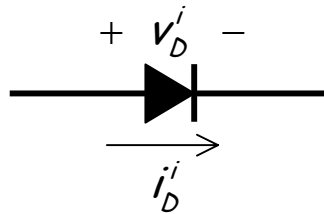→ Is it a **short**? Or is it an **open**?




	$v_D^i < 0$	$v_D^i = 0$	$v_D^i > 0$
$i_D^i > 0$	invalid	forward biased	invalid
$i_D^i = 0$	reverse biased	no bias	invalid
$i_D^i < 0$	invalid	invalid	invalid


The Diode

Mechanical Analogy

An ideal diode is sort of like a mechanical valve !

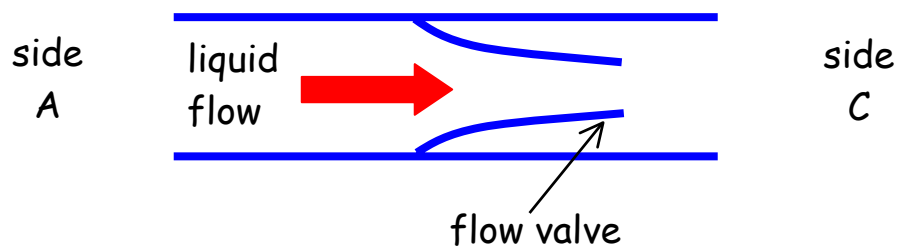

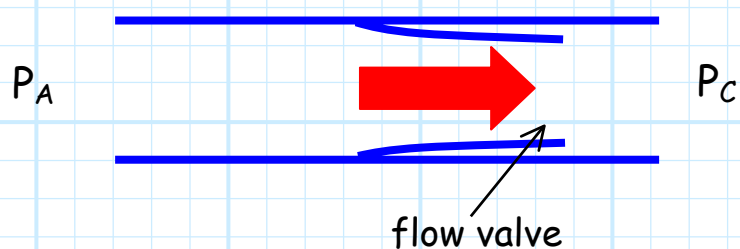
Case 1: Valve allows liquid to flow in pipe from side A to side C.



There is no drop in pressure (P) from side A to side C.

$$\rightarrow P_A - P_C = 0$$

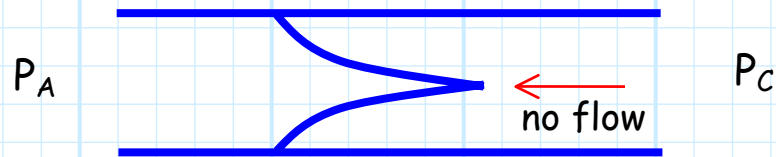Case 2: Valve prevents liquid from flowing **back** from side C to side A.



No flow occurs when pressure P_C is greater than pressure P_A

→ $P_A - P_C < 0$

Note the **analogies** with an ideal diode:

Valve

Pressure

Liquid Flow

Side A

Side C

Case 1

Case 2

Diode

Voltage

Current

Anode

Cathode

Forward Bias

Reverse Bias



The Ideal Diode Circuit Analysis Guide

Follow these easy steps to successfully analyze a circuit containing one or more **ideal** diodes !

Step 1: *ASSUME* a bias state for each ideal diode.

⇒ In other words, **GUESS !!**

Either,

- a) *ASSUME* an ideal diode is **forward biased**, or
- b) *ASSUME* it is **reversed biased**.

Step 2: *ENFORCE* the **equality** condition consistent with your assumption.

- a) If you assume an ideal diode is **f.b.**, then *ENFORCE* the equality:

$$v_D' = 0$$


HOW ? ⇒ By replacing the **ideal** diode with a **short** circuit!

b) If you assumed an ideal diode was **r.b.**, then **ENFORCE** the condition that:

$$i_D^i = 0$$

HOW ? \Rightarrow By replacing the ideal diode with an **open** circuit.

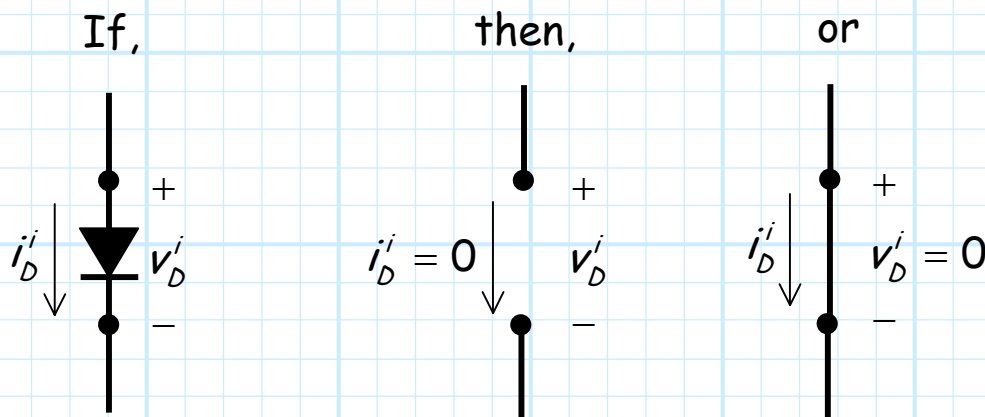IMPORTANT !!! Retain the **same** current and voltage definitions when you replace the ideal diode!



Step 3: *ANALYZE* the circuit.

After the all **ideal** diodes have been replaced with either shorts or opens:

- Determine **all** desired (required) circuit values.
- Determine i_D^i through each **short** circuit and v_D^i across each **open** circuit.

Step 4: *CHECK* the **inequality** consistent with your assumption to see if this assumption is correct.

HOW ??

a) An **ideal** diode cannot have negative current flowing through it. If you **ASSUMED** the ideal diode was **forward biased**, *CHECK* to see if the **short** circuit current is positive, i.e.:

$$i_D^i > 0$$

If true, you *ASSUMED* correctly ! If **not**, your **f.b.** assumption is wrong.

b) An **ideal** diode cannot have positive voltage across it. If you **ASSUMED** the ideal diode was **reversed biased**, *CHECK* to see if the **open** circuit voltage is negative, i.e.:

$$v_D^i < 0$$

If true, you *ASSUMED* correctly ! If **not**, your **r.b.** assumption is wrong.

Step 5: If you **ASSUMED** incorrectly, then change your assumptions and return to step 1 !

Notes on ideal diode circuit analysis:


- 1) You **must** check all assumptions in this form:

$$i_D^i = 2 \text{ mA} > 0 \checkmark \quad \text{or} \quad v_D^i = 2.2 > 0 \text{ X}$$

- 2) Do **not** check the condition that you enforced!
- 3) For **every** circuit, one and only one assumption will be valid.

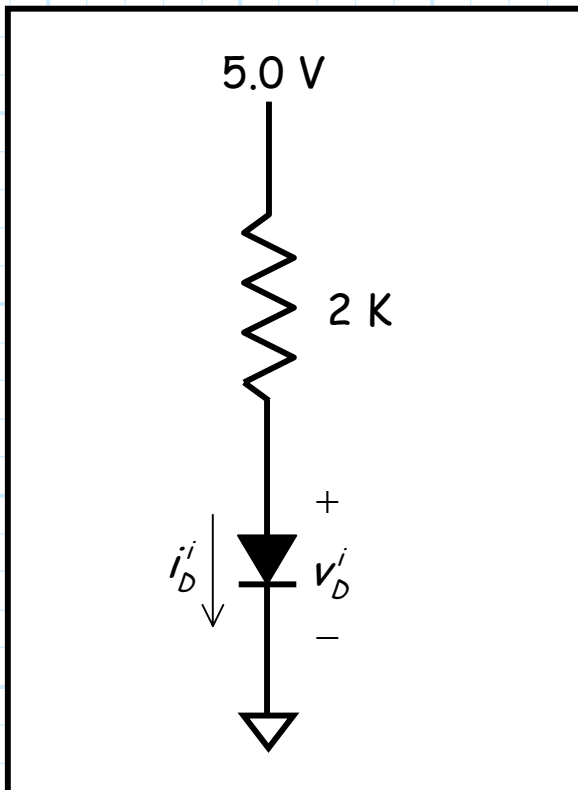Example: A Simple Ideal Diode Circuit

Consider this simple circuit that includes an **ideal** diode:




Q: What are i_D^i and v_D^i ?

A: Follow the five easy analysis steps!

Step 1: Let's *ASSUME* the ideal diode is **reverse biased** (we're just guessing!).

Step 2: We therefore *ENFORCE* $i_D^i = 0$ by replacing the ideal diode with an **open circuit**.

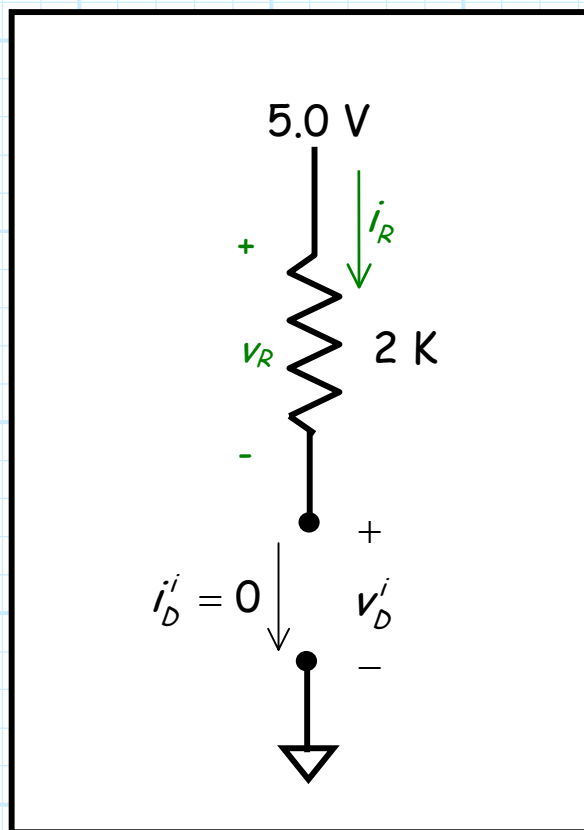Step 3: Now we *ANALYZE* the circuit; finding the value of v_D^i .



$$5.0 - v_R - v_D^i = 0 \quad (\text{KVL})$$

$$\therefore v_D^i = 5.0 - v_R$$

$$i_R = i_D^i \quad (\text{KCL})$$

$$v_R = 2 i_R \quad (\text{Ohm's})$$

$$i_D^i = 0 \quad (\text{enforced})$$


$$\therefore i_R = 0$$

$$\therefore v_R = 2(0) = 0$$

$$\therefore v_D^i = 5.0 - 0 = 5.0 \text{ V}$$

Step 4: Now let's CHECK our result. \Rightarrow Is $v_D^i < 0$??

$$v_D^i = 5.0 > 0$$

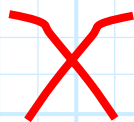


We must change our assumption, and then **start over** (Doh!).

1) Now *ASSUME* the ideal diode is **forward biased** (what's left?).

2) We therefore *ENFORCE* $v_D^i = 0$ by replacing the ideal diode with an **short** circuit.

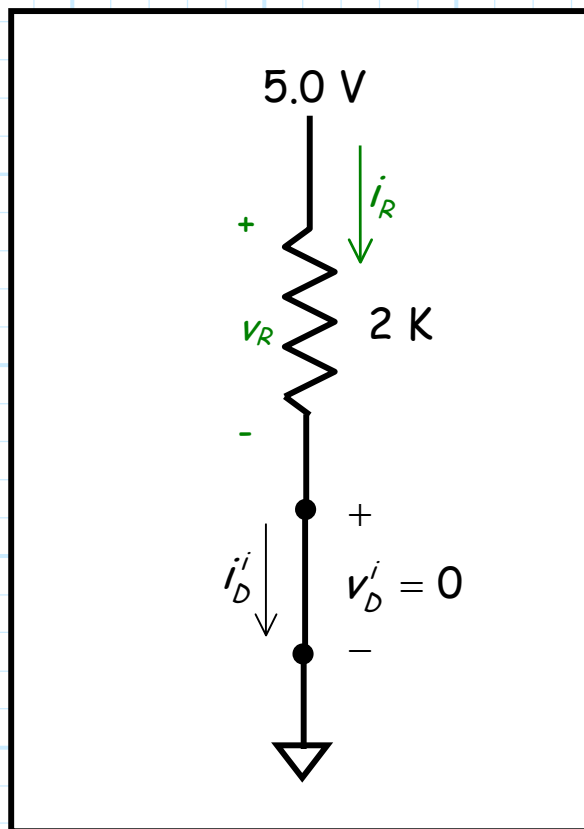3) Now we *ANALYZE* the circuit; finding the value of i_D^i .



$$5.0 - v_R - v_D^i = 0 \quad (\text{KVL})$$

$$\therefore v_R = 5.0 - v_D^i$$

$$i_D^i = i_R \quad (\text{KCL})$$

$$i_R = v_R / 2 \quad (\text{Ohm's})$$

$$v_D^i = 0 \quad (\text{enforced})$$

$$\therefore v_R = 5.0 - 0 = 5.0 \text{ V}$$

$$\therefore i_R = 5.0 / 2 = 2.5 \text{ mA}$$

$$\therefore i_D^i = 2.5 \text{ mA}$$

4) Now, let's *CHECK* our result. \Rightarrow **Is $i_D^i > 0$??**

$$i_D^i = 2.5 \text{ mA} > 0 \quad \checkmark$$


Our assumption is correct !

Therefore, in this circuit, we now **know** that:

$$v_D^i = 0 \quad \text{and} \quad i_D^i = 2.5 \text{ mA}$$

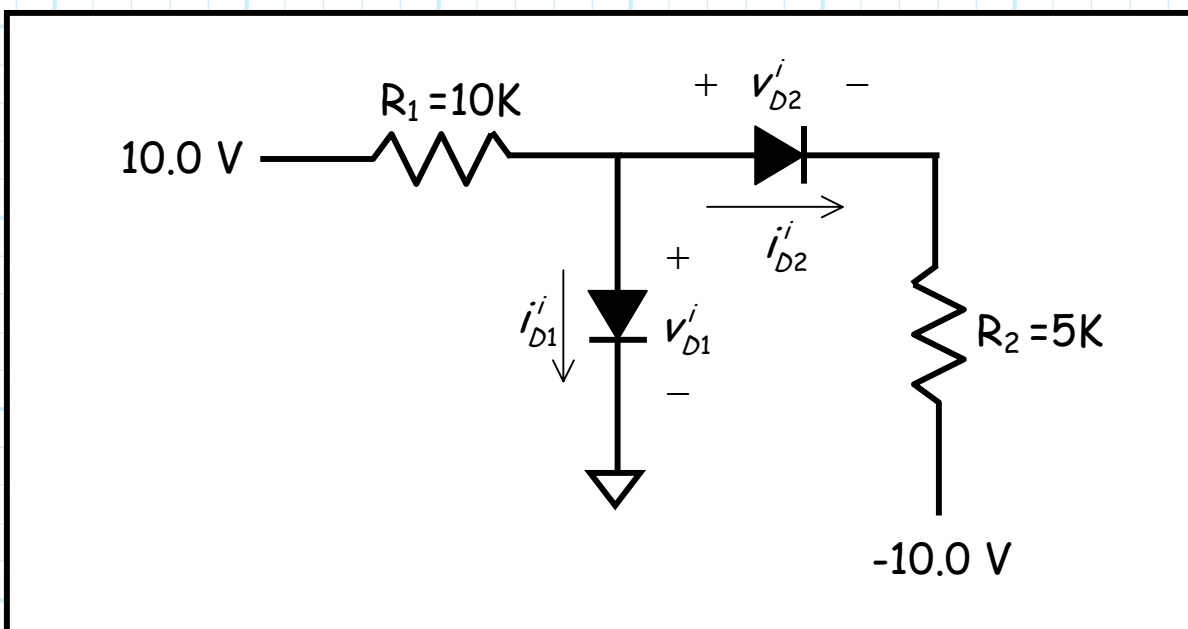Example: Analysis of a Complex Diode Circuit

Consider this circuit with **two ideal diodes**:




Let's analyze this circuit and find v_{D1}^i , i_{D1}^i , v_{D2}^i , and i_{D2}^i !

Remember, we must accomplish each of the **five** steps:

Step 1: *ASSUME* that both D_1 and D_2 are "on" (might as well!).

Step 2: *ENFORCE* the equalities $v_{D1}^i = 0 = v_{D2}^i$, by replacing each ideal diode with a **short** circuit.

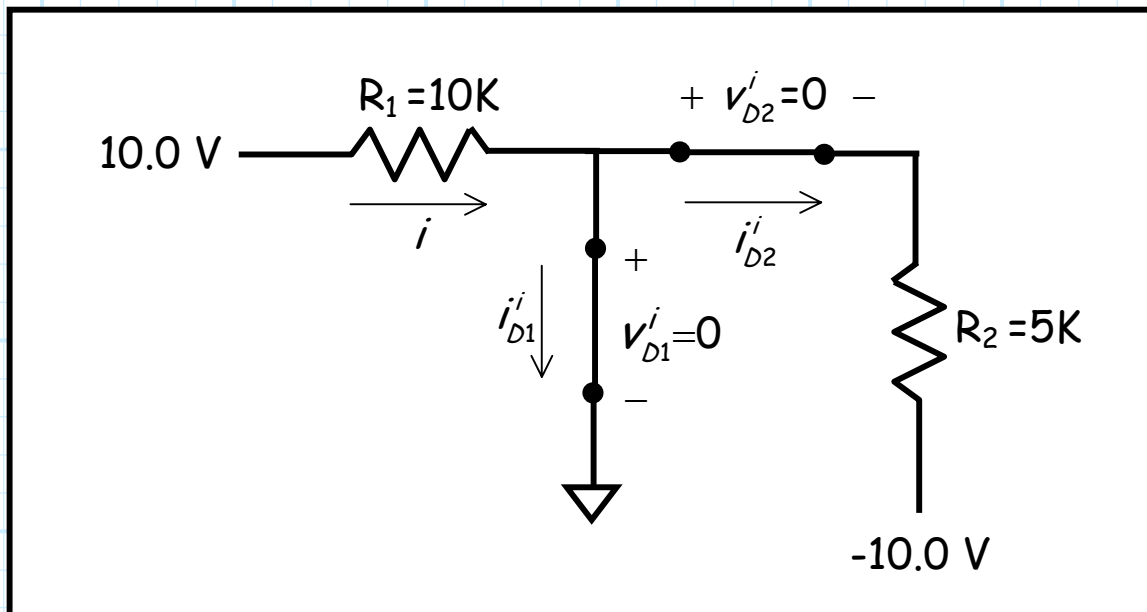Step 3: *ANALYZE* the resulting circuit, and find i_{D1}^i and i_{D2}^i .



Begin with **KCL**:

$$i = i_{D1}^i + i_{D2}^i$$

where
$$i = \frac{10.0 - 0}{10} = 1.0 \text{ mA}$$

and
$$i_{D2}^i = \frac{0 - (-10)}{5} = \frac{10}{5} = 2.0 \text{ mA}$$

Therefore,
$$i_{D1}^i = i - i_{D2}^i = 1.0 - 2.0 = -1.0 \text{ mA}$$


Step 4: Now we must *CHECK inequalities* to see if our assumptions are correct!

$$i_{D1}^i = -1.0 \text{ mA} < 0 \quad \times$$

$$i_{D2}^i = 2.0 \text{ mA} > 0 \quad \checkmark$$



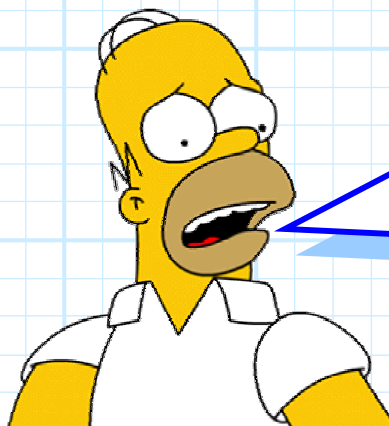One assumption is therefore **INCORRECT**. We must proceed to **step 5**—change our assumptions and **completely** start again!



Q: *Wait a second! We don't have to **completely** start from the beginning, do we? After all, our assumption about diode D_2 turned out to be **true**—so we **already** know that $i_{D2}^i = 2.0$ and $v_{D2}^i = 0$, **right?***


A: **NO!** The solution for diode D_2 is dependent on the state of both diodes D_1 and D_2 . If the assumption of just **one** diode turns out to be incorrect, then the solutions for **all** diodes are **wrong!**

So, let's change our assumption and start all over again!

Step 1: Now *ASSUME* that D_1 is "off" and D_2 is "on".

Step 2: *ENFORCE* $i_{D1}^i = 0$ (D_1 open) and $v_{D2}^i = 0$ (D_2 short).

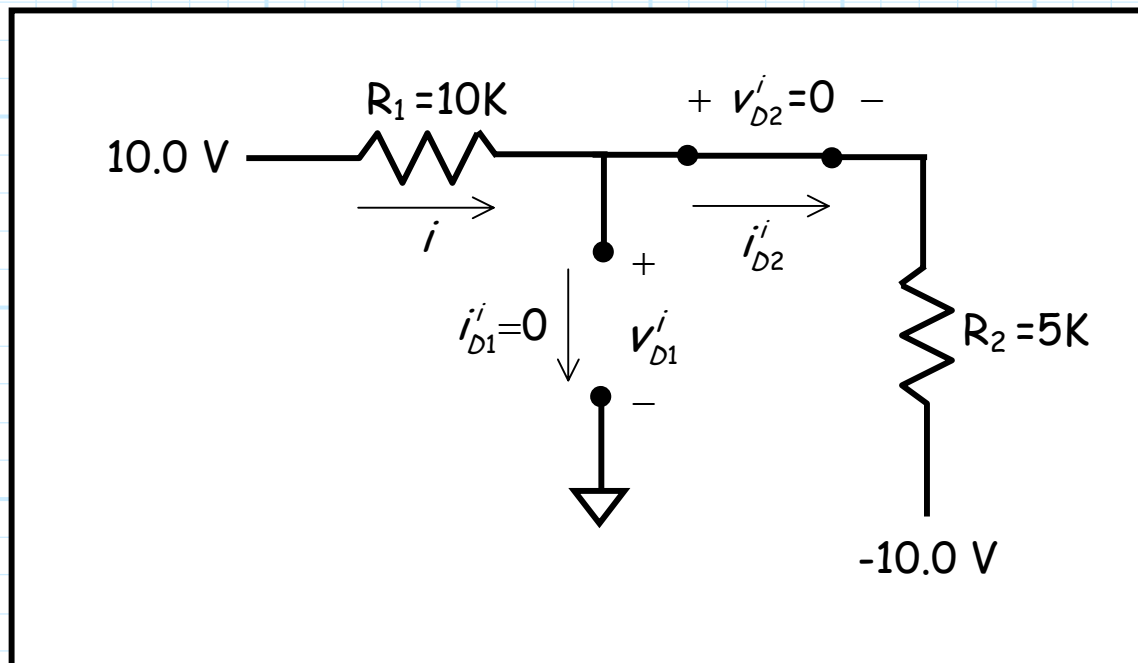Step 3: *ANALYZE* resulting circuit, and find v_{D1}^i and i_{D2}^i .



$$\text{Note } i = i_{D2}^i = \frac{10.0 - (-10.0)}{10 + 5} = \frac{20.0}{15} = 1.33 \text{ mA}$$

and from KVL:

$$10.0 - 10i - v_D^i = 0$$

$$10.0 - 10(1.33) - v_D^i = 0$$

$$\therefore v_D^i = 10.0 - 10(1.33) = -3.33 \text{ V}$$

4) CHECK our assumptions.

$$i_{D2}^i = 1.33 \text{ mA} > 0 \quad \checkmark$$

$$v_{D1}^i = -3.33 \text{ V} < 0 \quad \checkmark$$

\therefore Assumptions are **correct!** We are finished!



$$v_{D1}^i = -3.33 \text{ V}$$

$$i_{D1}^i = 0$$

$$v_{D2}^i = 0$$

$$i_{D2}^i = 1.33 \text{ mA}$$