
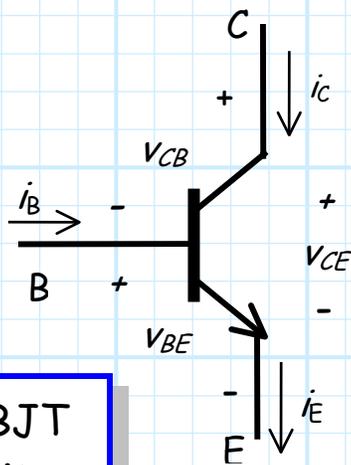


BJT Symbols and Conventions

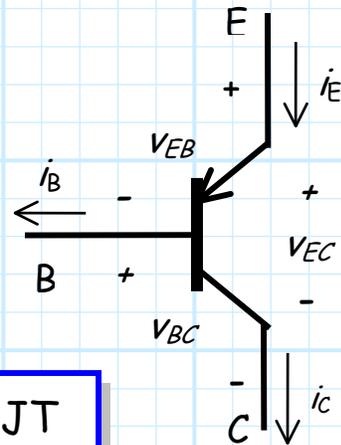

nnp BJT
Circuit
Symbol



pnp BJT
Circuit
Symbol

From KCL only we find:

$$i_E = i_B + i_C$$

From KVL only we find:

$$V_{CE} = V_{CB} + V_{BE} \quad (\text{nnp})$$

$$V_{EC} = V_{EB} + V_{BC} \quad (\text{pnp})$$

Note that:

- * The circuit **symbols** are very **similar** to MOSFETs, with *nnp* like N-MOS and *pnnp* like P-MOS.
- * Positive **current** is defined in **opposite** directions for *nnp* and for *pnnp* (just like N-MOS and PMOS!).
- * The **voltages** are of **opposite** polarity for *nnp* and *pnnp*. Specifically, for *nnp* we use v_{BE} , v_{CE} and v_{CB} , whereas for *pnnp* we use v_{EB} , v_{EC} and v_{BC} . This convention typically results in **positive** voltage values for **both** *nnp* and *pnnp* (**unlike** the MOSFET convention!).
- * The **base current** i_B is **not** equal to zero, therefore $i_E \neq i_C$ (**unlike** MOSFETS)!