
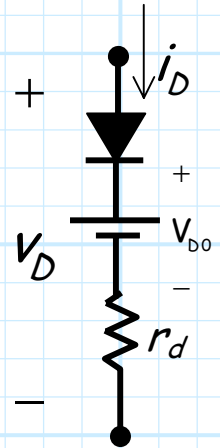



Constructing the PWL Junction Diode Model

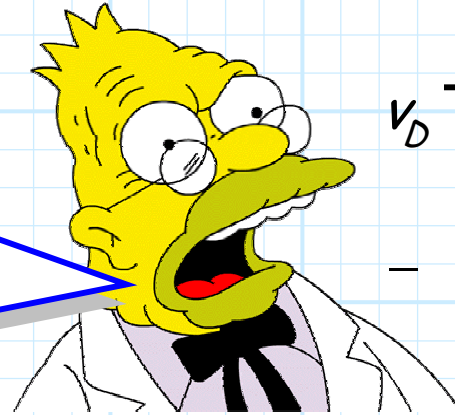Q: Wait a minute! How the heck are we supposed to use the **PWL model** to analyze junction diode circuits? You have yet to tell us the **numeric values** of voltage source V_{D0} and resistor r_d !



A: That's right! The reason is that the **proper** values of voltage source V_{D0} and resistor r_d are up to **you** to determine! To see why, consider the current voltage relationship of the **PWL model**:
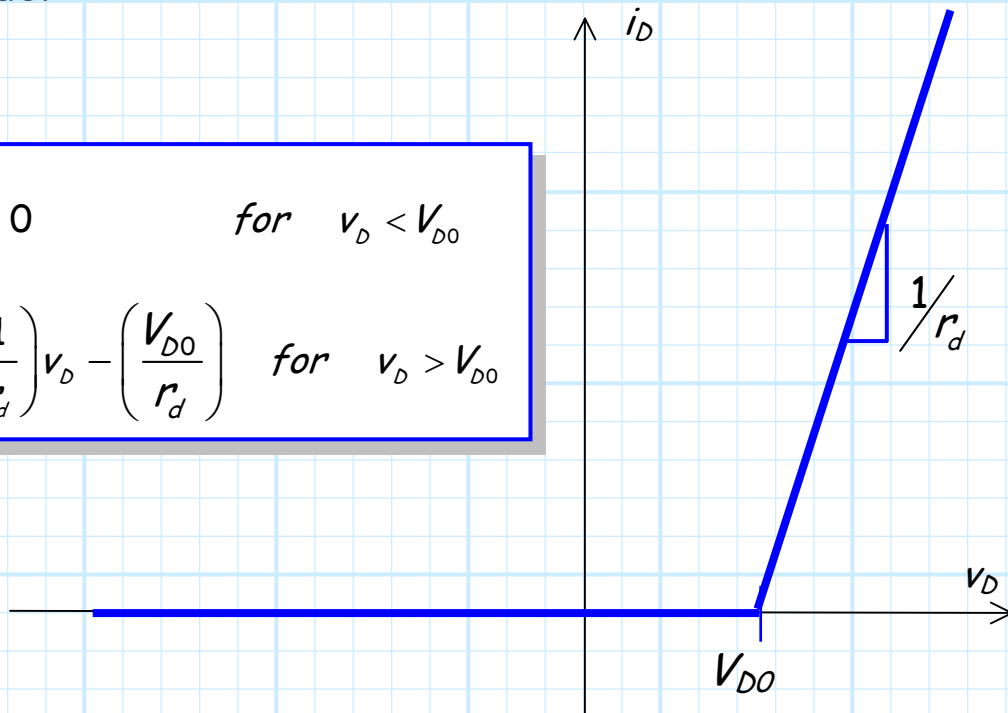
$$i_D = \begin{cases} 0 & \text{for } v_D < V_{D0} \\ \left(\frac{1}{r_d}\right)v_D - \left(\frac{V_{D0}}{r_d}\right) & \text{for } v_D > V_{D0} \end{cases}$$



Note that when the **ideal** diode in the PWL model is forward biased, the current-voltage relationship is simply the equation of a **line**!

$$i_D = \left(\frac{1}{r_d} \right) v_D - \left(\frac{V_{D0}}{r_d} \right)$$


y = m x + b

Compare the above to the forward biased junction diode approximation:

$$i_D = I_s e^{v_D/nV_T}$$

An **exponential** equation!

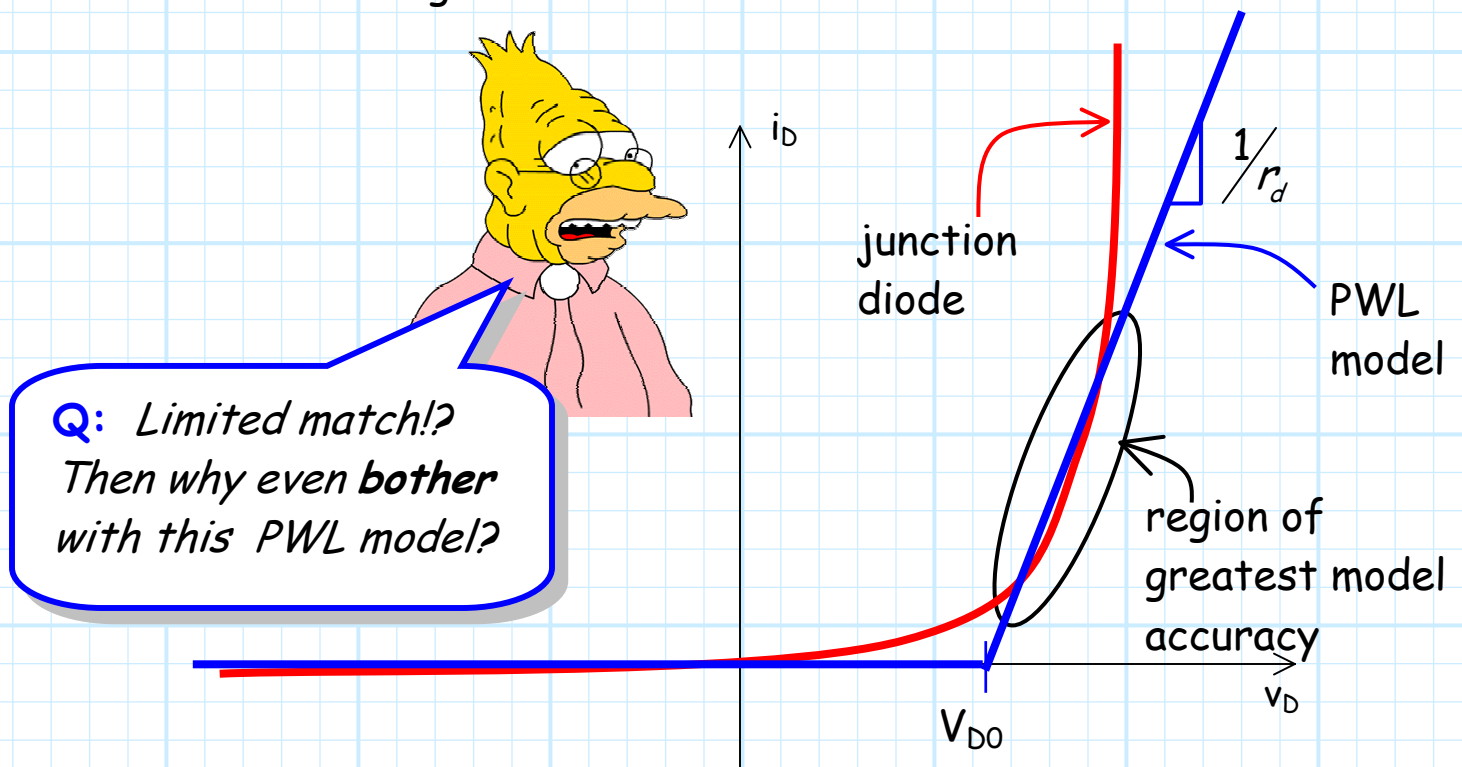An exponential function and the equation of a line are **very** different—the two functions can approximately “match” only over a **limited** region:



A: Remember, the PWL model is **more accurate** than our two **alternatives**—the ideal diode model and the CVD model.

At the very least, the PWL model (**unlike** the two alternatives) shows an **increasing** voltage v_D with **increasing** i_D . Moreover, if we select the values of V_{D0} and r_d properly, the PWL can **very accurately** “match” the actual (exponential) junction diode curve over a **decade** or more of current (e.g., accurate from $i_D = 1$ mA to 10 mA, or from $i_D = 20$ mA to 200 mA).

Q: *Yes well I asked you a long time ago what r_d and V_{D0} should be, but you **still** have not given me an **answer!***



A: OK. We now know that the values of r_d and V_{D0} specify a **line**. We also know there are **4** potential ways to **specify** a line:

1. Specify **two points** on the line.
2. Specify one **point** on the line, as well as its **slope** m .
3. Specify one **point** on the line, as well as its **y-intercept** b .
4. Specify both its **slope** and its **y-intercept** b .


We will find that the **first two** methods are the most useful. Let's address them one at a time.

1. Specify two points on the line

The **obvious** question here is: **Which** two points ?

Hopefully it is **equally** obvious that the two points should be points lying on the **junction diode** exponential curve (after all, it is this curve that we are **attempting to approximate!**).

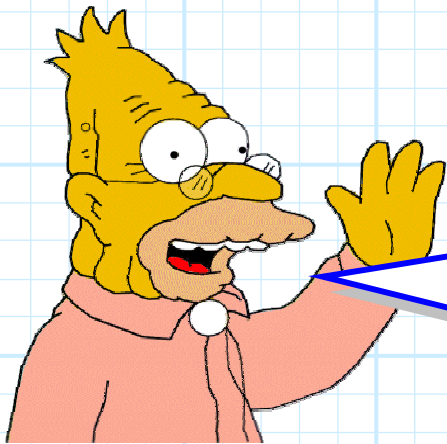Typically, we pick **two current values** separated by about a **decade** (i.e., 10 times). For **example**, we might select $i_{D1}=10$ mA and $i_{D2}=100$ mA. We will find that the resulting PWL model will be **fairly accurate** over this region.



Q: *I've got a **question!**
How do we find the
corresponding **voltage**
values v_{D1} and v_{D2} for
these two currents?*

A: Remember, we are selecting two points **on** the exponential junction diode curve. Thus, we can use the **junction diode equation** to determine the corresponding voltages:


$$v_{D1} = nV_T \ln \left[\frac{i_{D1}}{I_s} \right]$$

$$v_{D2} = nV_T \ln \left[\frac{i_{D2}}{I_s} \right]$$

Now, the rest is simply **Middle School mathematics**. If our PWL "line" intersects these two points, then:

$$i_{D1} = \left(\frac{1}{r_d} \right) v_{D1} - \left(\frac{V_{D0}}{r_d} \right)$$
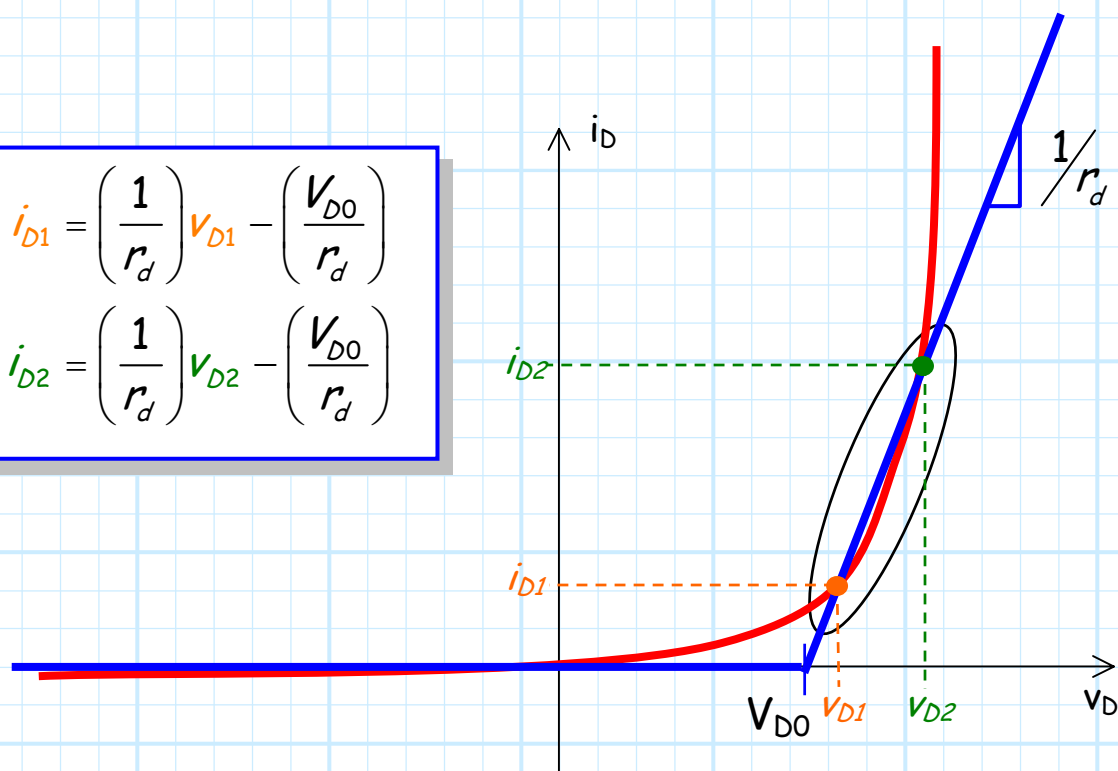
$$i_{D2} = \left(\frac{1}{r_d} \right) v_{D2} - \left(\frac{V_{D0}}{r_d} \right)$$



Thus, we can solve the above **two equations** to determine the **two unknown** values of V_{D0} and r_d , such that our PWL "line" will intersect the two specified points on the junction diode curve:

$$m = \frac{1}{r_d} = \frac{i_{D2} - i_{D1}}{v_{D2} - v_{D1}} \quad \therefore \quad r_d = \frac{v_{D2} - v_{D1}}{i_{D2} - i_{D1}}$$

And then we use our PWL "line" equation to find r_d :

$$V_{D0} = v_{D1} - i_{D1} r_d \quad \text{or} \quad V_{D0} = v_{D2} - i_{D2} r_d$$

(note these two equations are **KVL!**).

2. Specify one point and the slope

Now let's examine **another** way of constructing our PWL model. We first specify just **one** point that the PWL "line" must intersect. Let's denote this point as (I_D, V_D) and call this point our **bias point**.


Of course, we want our bias point to **lie on** the exponential junction diode curve, i.e.:

$$I_D = I_s e^{V_D/nV_T} \quad \text{or equivalently} \quad V_D = nV_T \ln \left[\frac{I_D}{I_s} \right]$$


Now, **instead** of specifying a **second** intersection point, we merely **specify directly** the PWL line **slope** (i.e., directly specify the value of r_d):

$$m = \frac{1}{r_d}$$

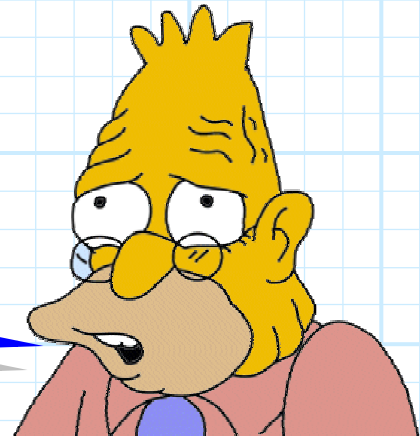Q: *But I have no idea what the value of this slope should be!?!*



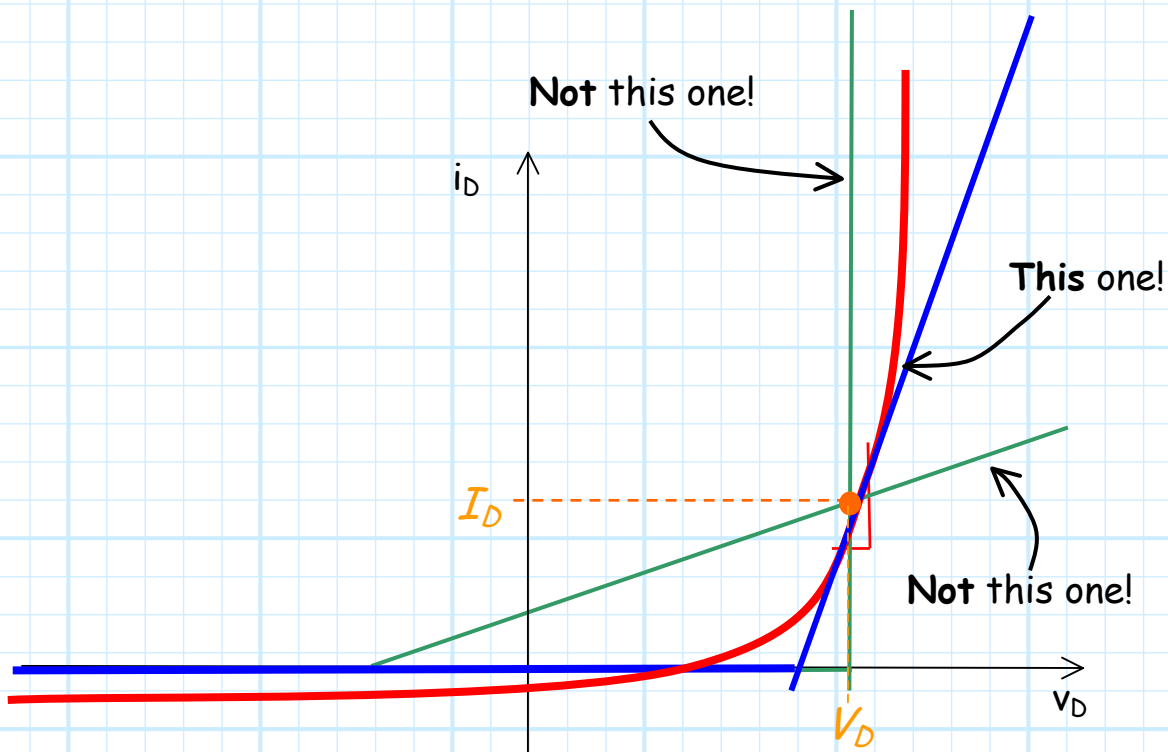A: **Think** about it. Of all possible PWL models that intersect the bias point, the one that is most accurate is the one that has a slope **equal** to the slope of the exponential junction diode curve (that is, **at** the bias point)!



Q: *What! Just how is it possible to **determine** the slope of the junction diode curve at the bias point?!?*

A: Easy! We simply take the **first derivative** of the junction diode equation:

$$\begin{aligned} \frac{di_D}{dv_D} &= \frac{d}{dv_D} \left(I_s e^{v_D/nV_T} \right) \\ &= \frac{I_s e^{v_D/nV_T}}{nV_T} \end{aligned}$$



Q: *Of course! This **equation** is the slope of the junction diode curve at the bias point!*



A: Actually **no**. The above equation is **not** the slope of the junction diode curve at the bias point. This equation provides the slope of the curve **as a function diode voltage v_D** . The slope of the junction diode curve is in fact different at **every** point on the junction diode curve.

In fact, as the equation above clearly states, the slope of the junction diode curve **exponential increases** with increasing v_D !

Q: *Yikes! So what is the derivate equation good for?*

A: Remember, we are interested in the value of the slope of the curve at **one** particular point—the **bias point**. Thus, we simply **evaluate** the derivative function at that point. The result is a numeric value of the slope **at our bias point!**

$$\begin{aligned}
 m &= \frac{d}{dv_D} \left(I_s e^{v_D/nV_T} \right) \Big|_{v_D=V_D} \\
 &= \frac{I_s e^{v_D/nV_T}}{nV_T} \Big|_{v_D=V_D} \\
 &= \frac{I_s e^{V_D/nV_T}}{nV_T}
 \end{aligned}$$

Note the **numerator** of this result! We recognize this numerator as simply the value of the **bias current I_D** :

$$I_D = I_s e^{V_D/nV_T}$$

Therefore, we find that the **slope** at the bias point is:

$$m = \frac{I_s e^{V_D/nV_T}}{nV_T} = \frac{I_D}{nV_T}$$

Now, we want the slope of our **PWL model** line to be **equal** to the slope of the **junction diode curve** at our bias point.

Therefore, we desire:

$$\frac{1}{r_d} = m = \frac{I_D}{nV_T}$$

Thus, **rearranging** this equation, we find that the **PWL model resistor value** should be:

$$r_d = \frac{nV_T}{I_D}$$

We likewise can rearrange the PWL "line" equation to determine the value of the **model voltage source** V_{D0} :

$$V_{D0} = V_D - I_D r_d \quad (\text{KVL !})$$

Now, combining the previous two equations, we find:

$$\begin{aligned} V_{D0} &= V_D - I_D r_d \\ &= V_D - I_D \left(\frac{nV_T}{I_D} \right) \\ &= V_D - nV_T \end{aligned}$$

So, let's **recap** what we have learned about constructing a PWL model using this particular approach.

1. We first select a single **bias point** (I_D , V_D), a point that lies on the junction diode curve, i.e.:

$$I_D = I_s e^{V_D/nV_T}$$

2. Using the current and voltage values of this bias point, we can then determine **directly** the PWL model **resistor value**:

$$r_d = \frac{nV_T}{I_D}$$

3. We can also directly determine the **value** of the model **voltage source**:

$$V_{D0} = V_D - nV_T$$

*This method for constructing a **PWL model** produces a very **precise** match over a relatively small region of the junction diode curve.*

*We will find that this is **very useful** for many practical diode circuit problems and analysis!*

*This PWL model produced by this last method (as described by the equations of the previous page) is called the junction diode **small-signal model**.*

*We will use the **small-signal model** again—make sure that you know **what** it is and **how** we construct it!*

