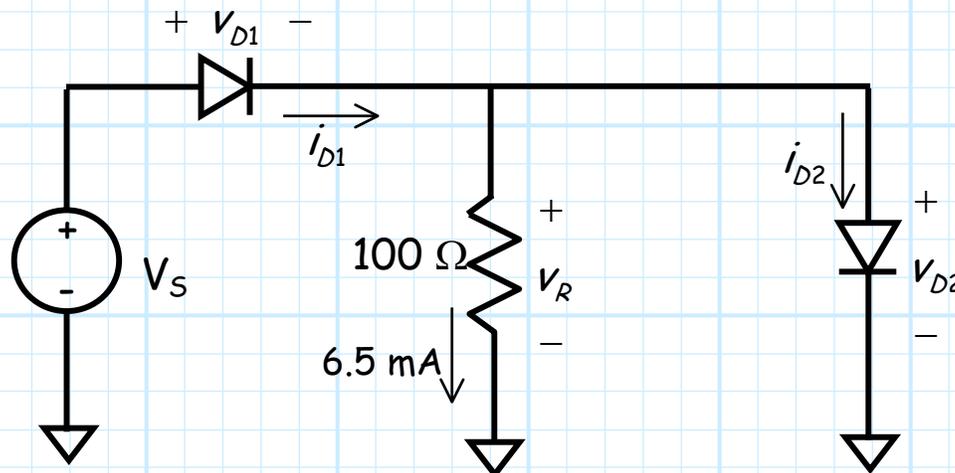


# Example: A Junction Diode Circuit

Consider the following circuit with two junction diodes:




The diodes are identical, with  $n = 1$  and  $I_S = 10^{-14}\ \text{A}$ .

**Q:** *If the current through the resistor is  $6.5\ \text{mA}$ , what is the voltage of source  $V_S$ ??*

**A:** This is a **difficult** problem to solve ! Certainly, we cannot just write:

$$V_S =$$

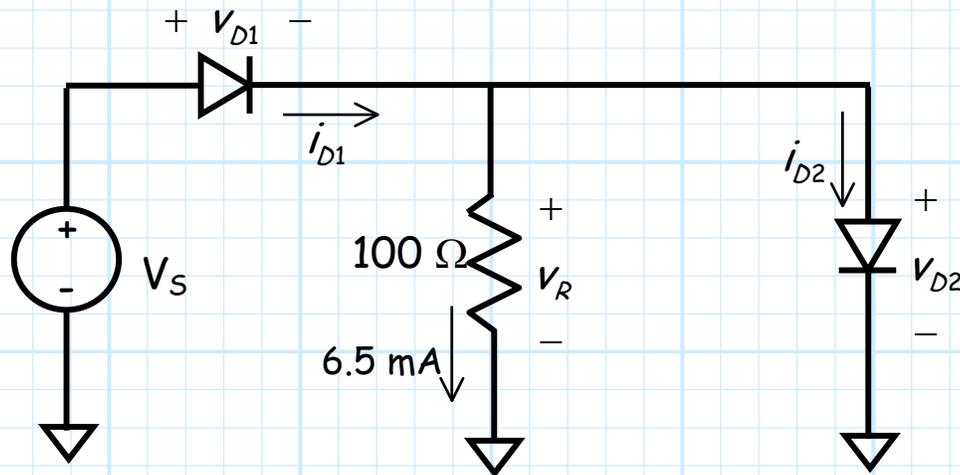and then the answer. Instead, let's just determine **what we can**, and see what happens !



- 1) If  $6.5\ \text{mA}$  flows through a  $0.1\ \text{K}$  resistor, the voltage across that resistor is:

$$V_R =$$

- 2) If the voltage across the resistor is  $0.65\ \text{V}$ , then the voltage across the diode  $D_2$ , which is **parallel** to the resistor, is the **same** value:


$$V_{D2} =$$

- 3) If we know the **voltage** across a p-n junction diode, then we also know its **current** !

$$i_{D2} = I_S \exp\left[\frac{V_{D2}}{nV_T}\right] = 10^{-14} \exp\left[\frac{0.650}{0.025}\right] = 1.96\ \text{mA}$$

- 4) If we know  $i_{D2}$  and the current through the resistor, we know (using KCL) the current through  $D_1$  :

$$i_{D1} =$$

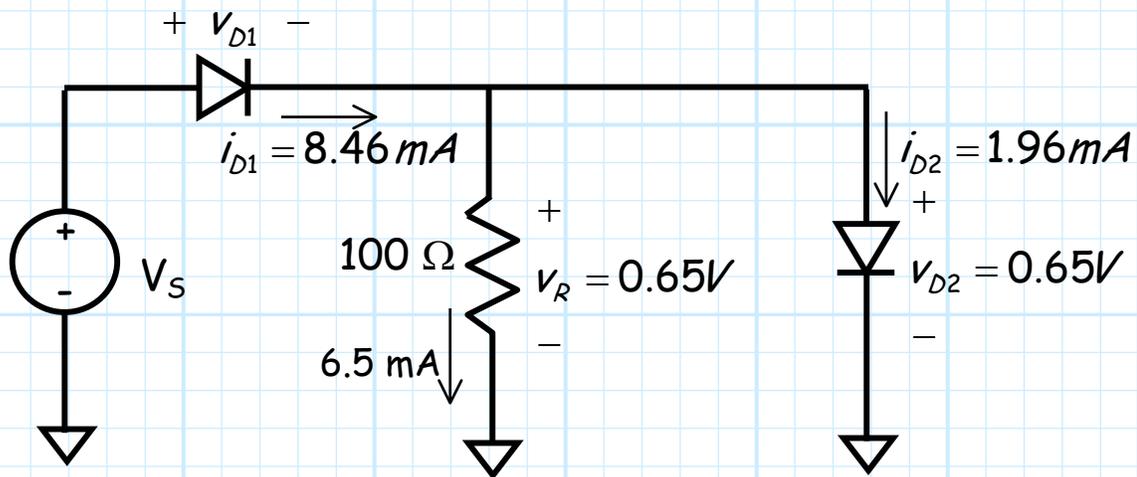

5) If we know the **current** through a junction diode, then we can find the **voltage** across it:

$$v_{D1} = nV_T \ln\left(\frac{i_{D1}}{I_S}\right) = 0.025 \ln\left(\frac{0.00846}{10^{-14}}\right) = 0.69V$$

6) Finally, if we know  $v_{D1}$  and  $v_{D2}$ , we can find  $V_S$  using KVL:

$$V_S =$$

