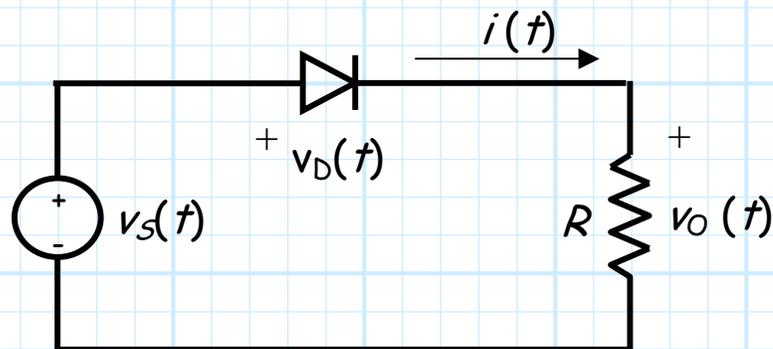



Example: Diode Circuit Transfer Function

Consider the following circuit, called a **half-wave rectifier**:



Let's use the **CVD model** to determine the output voltage v_O in terms of the input voltage v_s . In other words, let's determine the diode circuit **transfer function** $v_O = f(v_s)$!

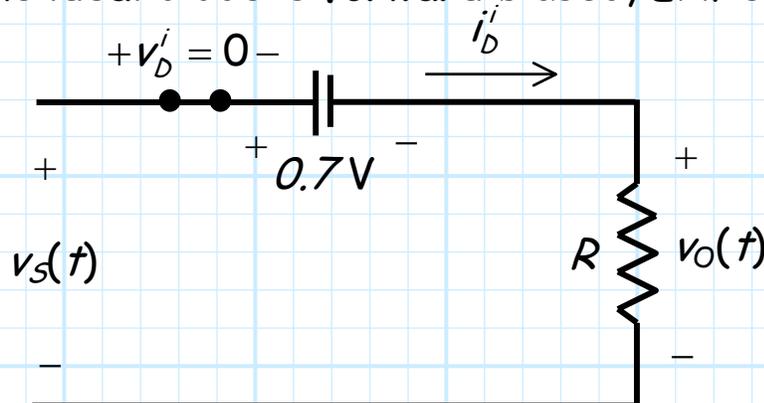ASSUME the **ideal** diode is **forward** biased, **ENFORCE** $v_D^i = 0$.



From KVL, we find that:


$$v_O(t) = v_s(t) - 0.7$$

This result is of course true if our original assumption is correct— it is valid if the ideal diode is forward biased (i.e., $i_D^i > 0$)!

From Ohm's Law, we find that:

$$i_D^i = \frac{v_O}{R} = \frac{v_S - 0.7}{R}$$

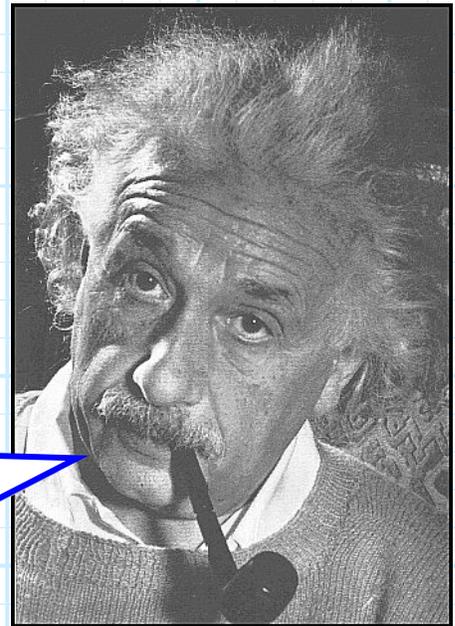Q: *I'm so confused! Is this current **greater** than zero or **less** than zero? Is our assumption correct? How can we tell?*



A: The ideal diode current is **dependent** on the value of source voltage $v_S(t)$. As such, we **cannot** determine if our assumption is correct, we **instead** must find out **when** our assumption is correct!

In other words, we know that the forward bias assumption is correct **when** $i_D^i > 0$. We can rearrange our diode current expression to determine for what values of source voltage $v_S(t)$ this is true:

$$i_D^i > 0$$


$$\frac{v_S(t) - 0.7}{R} > 0$$

$$v_S(t) - 0.7 > 0$$

$$v_S(t) > 0.7$$


So, we have found that **when** the source voltage $v_s(t)$ is greater than 0.7 V, the output voltage $v_o(t)$ is:

$$v_o(t) = v_s(t) - 0.7$$

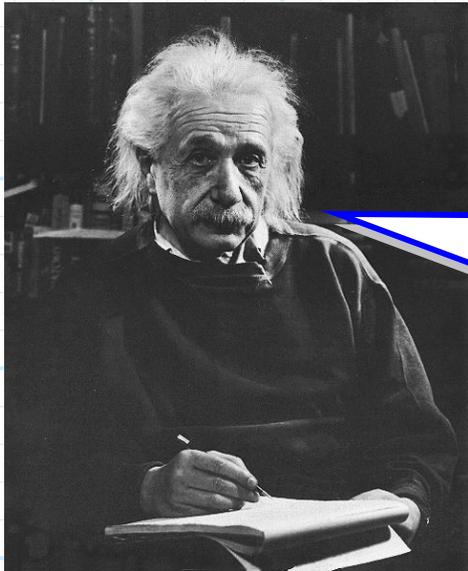

Q: *OK, I've got this result written down. However, I still don't know what the output voltage $v_o(t)$ is **when** the source voltage $v_s(t)$ is **less** than 0.7V!?!*

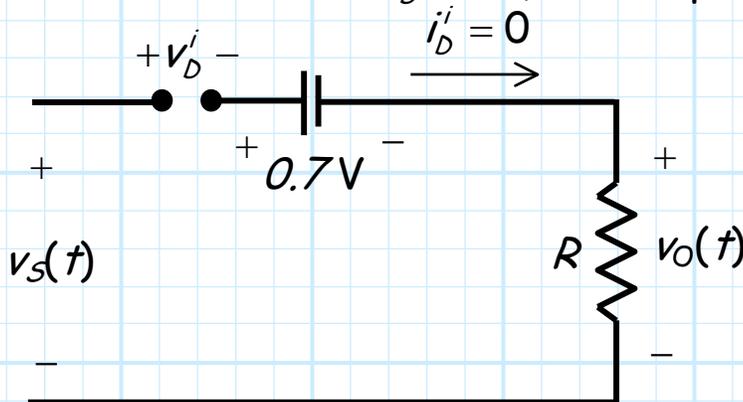
Now we **change** our assumption and **ASSUME** the ideal diode in the CVD model is **reverse** biased, an assumption **ENFORCED** with the condition that $i_D^i = 0$ (i.e., an open circuit).



Q: *Fascinating! The output voltage is **zero** when the ideal diode is reverse biased. But, precisely when **is** the ideal diode reverse biased? For **what** values of v_s does this occur?*

From Ohm's Law, we find that the output voltage is:
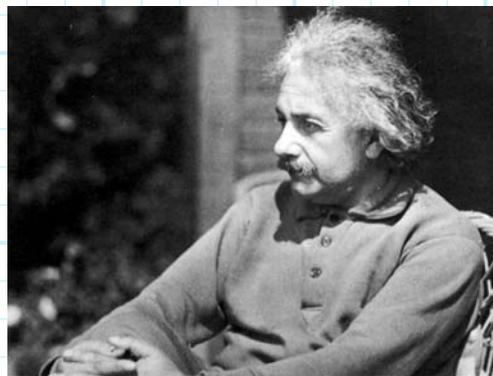
$$\begin{aligned} v_o &= R i_D^i \\ &= R(0) \\ &= 0 \text{ V !!!} \end{aligned}$$



A: To answer these questions, we must determine the **ideal** diode voltage in terms of v_S (i.e., $v_D' = f(v_S)$):

From KVL:
$$v_S - v_D' - 0.7 = v_O$$

Therefore:

$$\begin{aligned} v_D' &= v_S - 0.7 - v_O \\ &= v_S - 0.7 - 0.0 \\ &= v_S - 0.7 \end{aligned}$$

Thus, the ideal diode is in reverse bias **when**:

$$\begin{aligned} v_D' &< 0 \\ v_S - 0.7 &< 0 \end{aligned}$$

Solving for v_S , we find:

$$\begin{aligned} v_S - 0.7 &< 0 \\ v_S &< 0.7 \text{ V} \end{aligned}$$

In other words, we have determined that the **ideal** diode will be reverse biased **when** $v_S < 0.7 \text{ V}$, and that the output voltage will be $v_O = 0$.



Q: So, we have found that:

$$v_O = v_S - 0.7 \quad \text{when } v_S > 0.7 \text{ V}$$


and,

$$v_O = 0.0 \quad \text{when } v_S < 0.7 \text{ V}$$

It appears we have a valid, continuous, function!

A: That's right! The **transfer function** for this circuit is therefore:
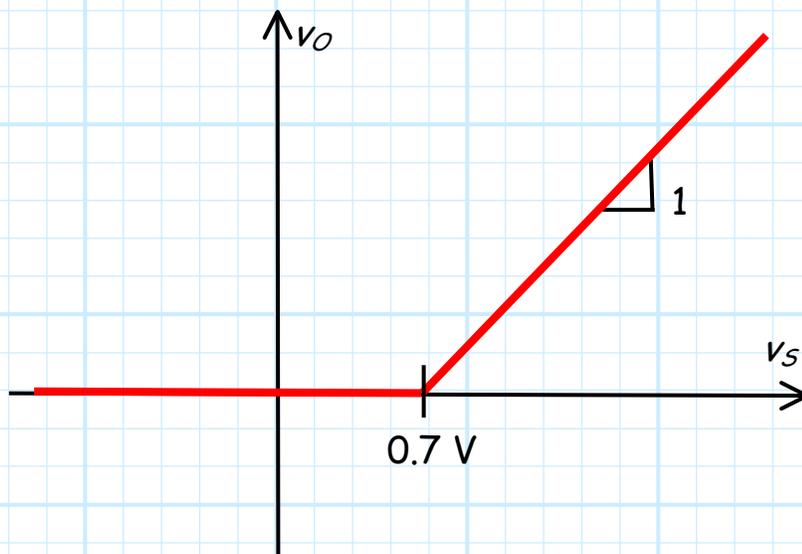
$$v_o = \begin{cases} v_s - 0.7 & \text{for } v_s > 0.7 \\ 0 & \text{for } v_s < 0.7 \end{cases}$$



*Although the circuit in this example may **seem** trivial, it is actually **very important!***

*It is called a **half-wave rectifier**, and provides **signal rectification**.*

*Rectifiers are an **essential part** of every **AC to DC power supply!***

