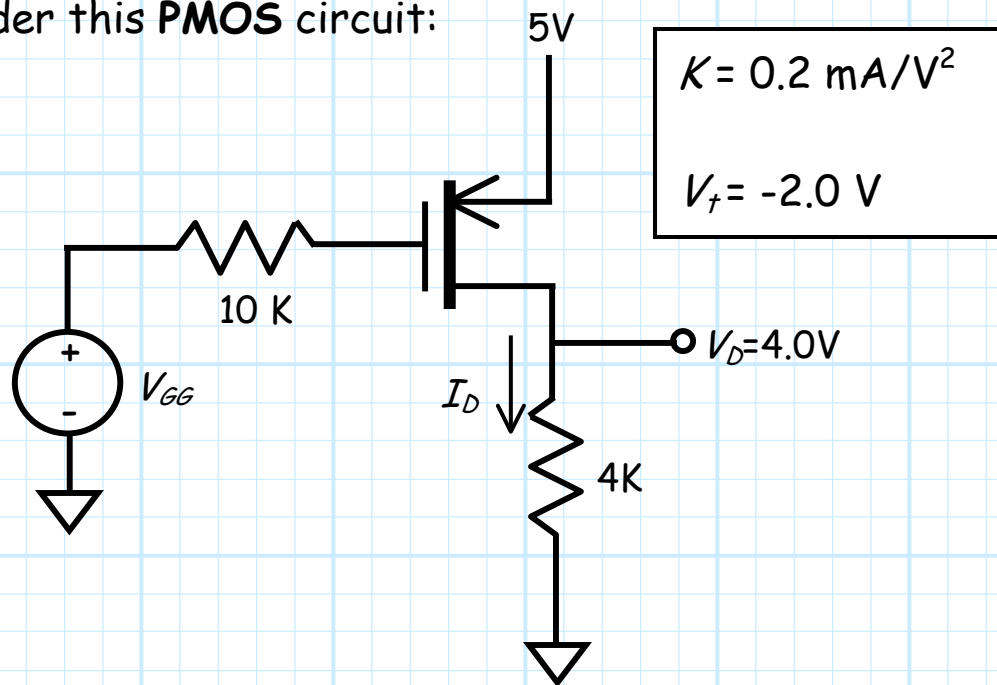


Example: PMOS Circuit

Analysis

Consider this PMOS circuit:



For this problem, we know that the **drain voltage** $V_D = 4.0\text{ V}$ (with respect to ground), but we do **not** know the value of the voltage source V_{GG} .

Let's attempt to **find** this value V_{GG} !


First, let's **ASSUME** that the PMOS is in **saturation** mode.

Therefore, we **ENFORCE** the **saturation** drain current equation $I_D = K(V_{GS} - V_t)^2$.

Now we must ANALYZE this circuit!

Q: *Yikes! Where do we start?*

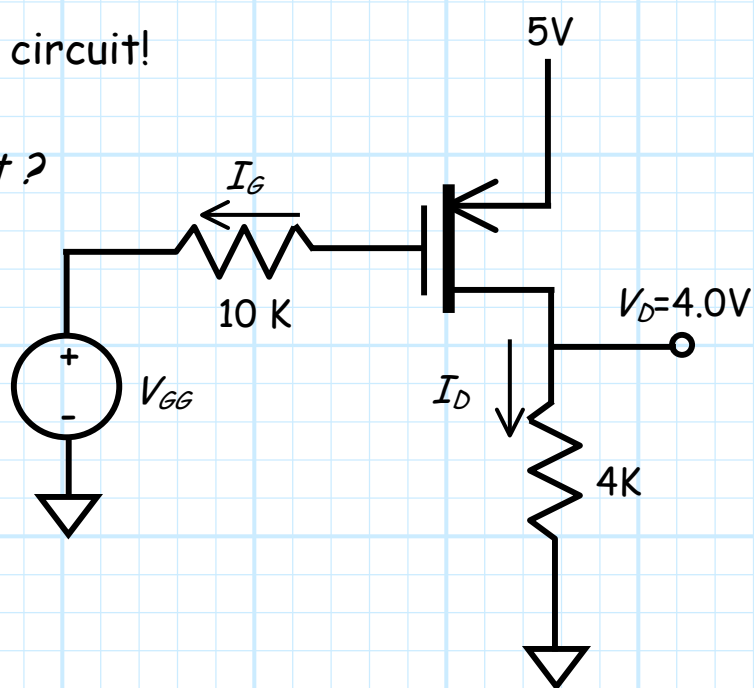A: The best way to start is by "picking the low-hanging fruit". In other words, determine the obvious and easy values. Don't ask, "What is V_{GG} ?", but instead ask, "What do I know?"!



There are lots of things that we can quickly determine about this circuit!

$$I_G = 0.0 \text{ mA}$$

$$V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0}{4} = \frac{4.0 - 0}{4} = 1 \text{ mA}$$

$$V_G = V_{GG} - 10 I_G = V_{GG} - 10(0) = V_{GG}$$

Therefore, we can likewise determine:

$$V_{DS} = V_D - V_S = 4.0 - 5.0 = -1.0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5.0 \text{ V}$$

Note what we have **quickly determined**—the **numeric** value of drain current ($I_D=1.0$ mA) and the voltage drain-to-source ($V_{DS}=-1.0$) Moreover, we have determined the value V_{GS} in terms of **unknown** voltage V_{GG} ($V_{GS} = V_{GG} - 5.0$).

We've determined all the **important stuff** (i.e., V_{GS}, V_{DS}, I_D)!

We can now relate these values using our PMOS **drain current equation**. Recall that we **ASSUMED saturation**, so if this assumption is correct:

$$I_D = K(V_{GS} - V_T)^2$$

Inserting into this equation our knowledge from above, along with our **PMOS** values $K=0.2$ mA/V² and $V_T=-2.0$, we get:

$$\begin{aligned} I_D &= K(V_{GS} - V_T)^2 \\ 1.0 &= 0.2(V_{GS} - (-2.0))^2 \\ 5.0 &= (V_{GS} + 2.0)^2 \end{aligned}$$

Be **careful** here! Note in the above equation that threshold voltage V_T is **negative** (since PMOS) and that I_D and K are both written in terms of **milliamps** (mA).

Now, we solve this equation to find the value of V_{GS} !

$$5.0 = (V_{GS} + 2.0)^2$$

$$\pm\sqrt{5} = V_{GS} + 2.0$$

$$\pm\sqrt{5} - 2.0 = V_{GS}$$

Q: So V_{GS} is **both** $\sqrt{5} - 2.0 = 0.24 \text{ V}$ **and** $-\sqrt{5} - 2.0 = -4.23 \text{ V}$?
How can this be possible?

A: It's **not** possible! The solution is **either** $V_{GS} = 0.24 \text{ V}$ **or** $V_{GS} = -4.23 \text{ V}$.

Q: But how can we tell **which** solution is correct?

A: We must choose a solution that is **consistent** with our original ASSUMPTION. Note that **neither** of the solutions **must** be consistent with the saturation ASSUMPTION, an event meaning that our ASSUMPTION was wrong.

However, **one** (but **only one!**) of the two solutions may be consistent with our saturation ASSUMPTION—**this** is the value that we choose for V_{GS} !

For this example, where we have ASSUMED that the PMOS device is in **saturation**, the voltage gate-to-source V_{GS} must be **less** (remember, it's a **PMOS** device!) than the **threshold voltage**:

$$V_{GS} < V_t$$

$$V_{GS} < -2.0 \text{ V}$$

Clearly, one of our solutions **does** satisfy this equation ($V_{GS} = -4.23 < -2.0$), and therefore we choose the **solution** $V_{GS} = -4.23 \text{ V}$.

Q: *Does this mean our saturation ASSUMPTION is correct?*

A: **NO!** It merely means that our saturation ASSUMPTION **might** be correct! We need to **CHECK** the other inequalities to know for **sure**.

Now, returning to our circuit **analysis**, we can quickly determine the **unknown** value of V_{GG} . Recall that we **earlier** determined that:

$$V_{GS} = V_{GG} - 5.0$$

And now, since we "know" that the $V_{GS} = -4.23 \text{ V}$, we can determine that:

$$\begin{aligned} V_{GG} &= V_{GS} + 5.0 \\ &= -4.23 + 5.0 \\ &= 0.77 \text{ V} \end{aligned}$$

This solution ($V_{GG} = 0.77 \text{ V}$) is of course true **only if** our original ASSUMPTION was correct. Thus, we must **CHECK** to see if our **inequalities** are valid:

We of course already know that the **first** inequality is true—a p-type channel is induced:

$$V_{GS} = -4.23 < -2.0 = V_t \quad \checkmark$$

And, since the **excess gate voltage** is $V_{GS} - V_t = -2.23 \text{ V}$, the **second inequality**:

$$V_{DS} = -1.0 > -2.23 = V_{GS} - V_t \quad \times$$

shows us that our **ASSUMPTION** was **incorrect!**

→ Time to make a **new ASSUMPTION** and **start over!**

So, let's **now ASSUME** the PMOS device is in **triode** region.

Therefore **ENFORCE** the drain current equation:

$$i_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

Now let's **ANALYZE** our circuit!

Note that most of our **original** analysis was **independent** of our PMOS mode **ASSUMPTION**. Thus, we **again** conclude that:

$$I_G = 0.0 \text{ mA}$$

$$V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0}{4} = \frac{4.0 - 0}{4} = 1 \text{ mA}$$

$$V_G = V_{GG} - 10 I_G = V_{GG} - 10(0) = V_{GG}$$

Therefore,

$$V_{DS} = V_D - V_S = 4.0 - 5.0 = -1.0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5.0 \text{ V}$$

Now, inserting these values in the **triode drain current equation**:

$$i_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

$$1.0 = 0.2 [2(V_{GS} - (-2))(-1) - (-1)^2]$$

$$5.0 = [-2(V_{GS} + 2) - 1]$$

Look! **One** equation and **one** unknown! Solving for V_{GS} we find:

$$5.0 = [-2(V_{GS} + 2) - 1]$$

$$6.0 = -2(V_{GS} + 2)$$

$$-3.0 = V_{GS} + 2$$

$$-5.0 = V_{GS}$$

Thus, we find that $V_{GS} = -5.0 \text{ V}$, so that we can find the **value** of voltage source V_{GG} :

$$V_{GS} = V_{GG} - 5.0$$

$$-5.0 = V_{GG} - 5.0$$

$$0.0 = V_{GG}$$

The voltage source V_{GG} is equal to **zero**—provided that our triode **ASSUMPTION** was **correct**.

To find out if the **ASSUMPTION** is correct, we must **CHECK** our **triode inequalities**.

First, we **CHECK** to see if a channel has indeed been **induced**:

$$V_{GS} = -5.0 < -2.0 = V_t \quad \checkmark$$

Next, we **CHECK** to make sure that our channel is **not** in pinch-off. Noting that the **excess gate voltage** is $V_{GS} - V_t = -5.0 - (-2.0) = -3.0 \text{ V}$, we find that:

$$V_{DS} = -1.0 > -3.0 = V_{GS} - V_t \quad \checkmark$$

Our **triode ASSUMPTION** is **correct**! Thus, the voltage source $V_{GG} = 0.0 \text{ V}$.