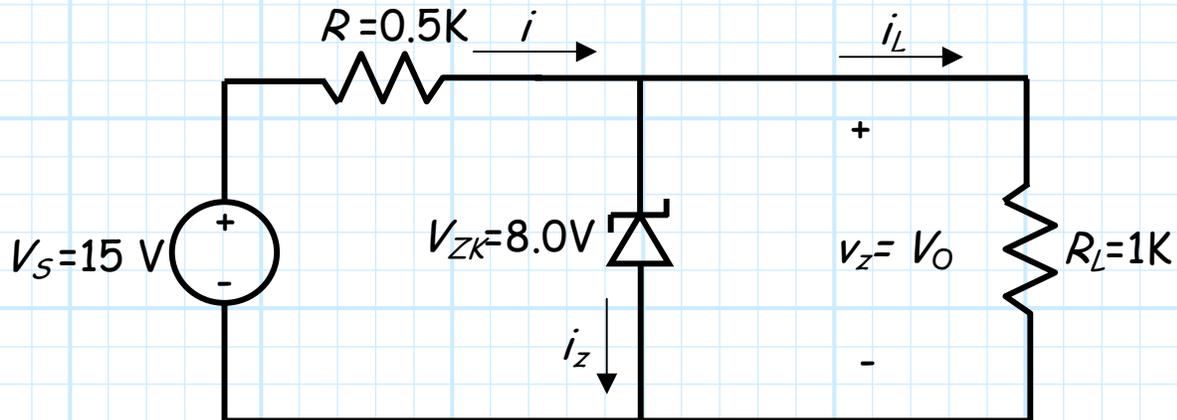


# Example: Zener Diode

## Circuit Analysis


Consider the circuit below:



Note that the load resistor  $R_L$  is in **parallel** with the Zener diode, so that the voltage  $V_O$  across this load resistor is **equal** to the Zener diode voltage  $v_Z$ .

**Q:** *So just what is the value of voltage  $V_O$ ?*

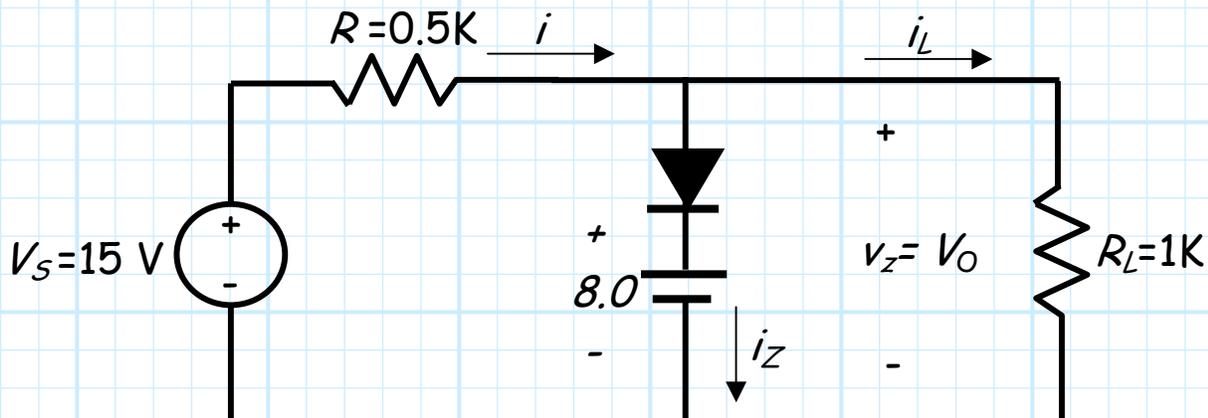**A:** Let's **replace** the Zener diode with a **Zener CVD model** and find out!




**Q:** *Yikes! We have an **IDEAL** diode circuit!*

**A:** Yes! We analyze it **precisely** like we did in section 3.1—remember, there are **no** Zener diodes in the circuit above!

**ASSUME:** IDEAL diode is **forward biased**.

**ENFORCE:**  $v_d^i = 0$

**ANALYZE:**

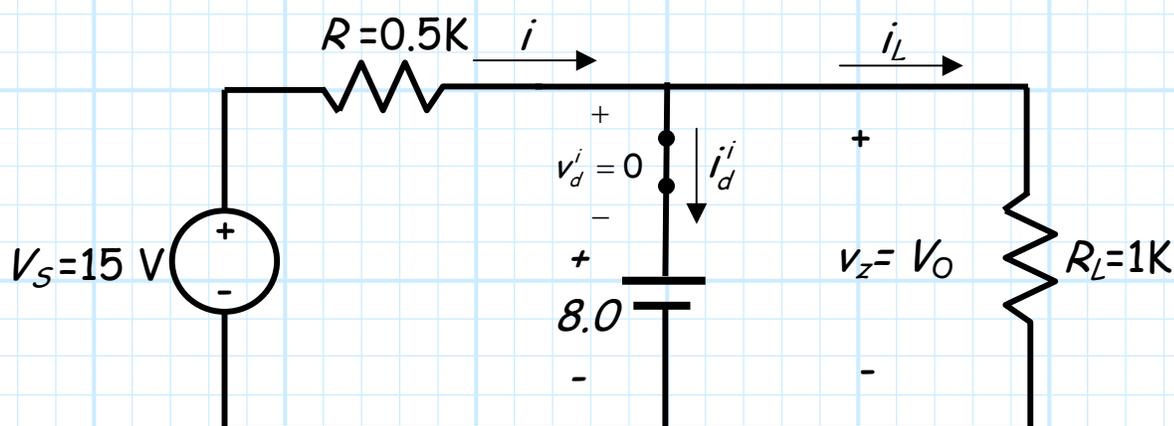

From KVL:

$$v_z = V_O =$$

From KCL:

$$i =$$

where from Ohm's Law:

$$i =$$

and:

$$i_L =$$

Therefore:

$$i_D^i =$$

$$=$$

$$=$$

CHECK:

$$i_D^i =$$



Look at what this means!

- The voltage across load resistor  $R_L$  is equal to the Zener breakdown voltage  $V_{ZK}$ —**regardless** of the value of load resistor  $R_L$  or source voltage  $V_S$  (provided, of course, that the Zener diode is in breakdown)!

This is an example of a primary **application** of Zener diodes—**voltage regulation**.

We call this particular regulator circuit the **shunt regulator**.