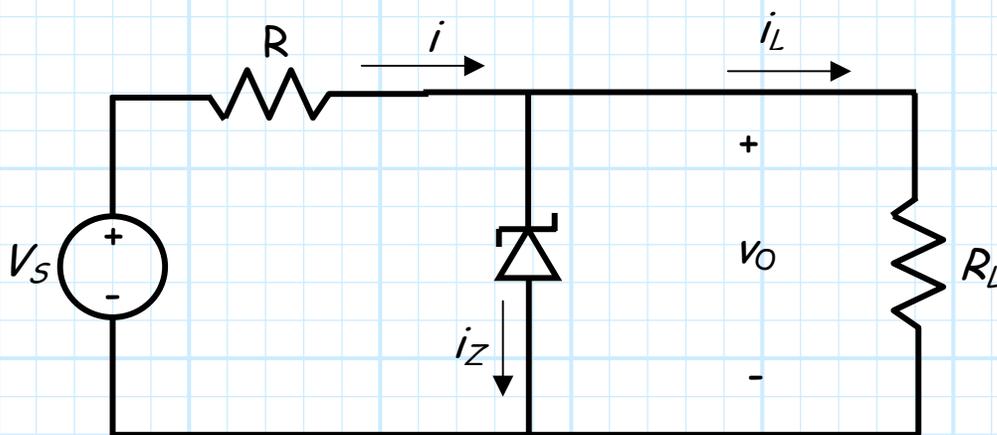


# Load Regulation



For voltage regulators, we typically define a load  $R_L$  in terms of its current  $i_L$ , where:

$$i_L = \frac{v_O}{R_L}$$

Note that since the load (i.e., regulator) voltage  $v_O$  is a constant (approximately), specifying  $i_L$  is **equivalent** to specifying  $R_L$ , and vice versa!

Now, since the Zener diode in a shunt regulator has some small (but non-zero) dynamic resistance  $r_Z$ , we find that the load voltage  $v_O$  will also have a **very small** dependence on load resistance  $R_L$  (or equivalently, load current  $i_L$ ).

In fact, if the load current  $i_L$  **increases** (decreases), the load voltage  $v_O$  will actually **decrease** (increase) by some small amount.

**Q:** *Why would the load current  $i_L$  ever change?*

**A:** You must realize that the load resistor  $R_L$  simply **models** a more **useful** device. The "load" may in fact be an amplifier, or a component of a cell phone, or a circuit board in a digital computer.

These are all **dynamic** devices, such that they may require **more** current at some times than at others (e.g., the computational load increases, or the cell phone begins to transmit).

As a result, it is more appropriate to represent the **total** load current as a time-varying signal ( $i_L(t)$ ), consisting of both a **DC** component ( $I_L$ ) and a **small-signal** component ( $\Delta i_L(t)$ ):


$$i_L(t) = I_L + \Delta i_L(t)$$

This small-signal load current of course leads to a load voltage that is **likewise** time-varying, with both a DC ( $V_O$ ) and small-signal ( $\Delta v_o$ ) component:

$$v_o(t) = V_O + \Delta v_o(t)$$

So, we know that the DC load current  $I_L$  produces the DC load voltage  $V_O$ , whereas the small-signal **load current**  $\Delta i_L(t)$  results in the small-signal **load voltage**  $\Delta v_o$ .

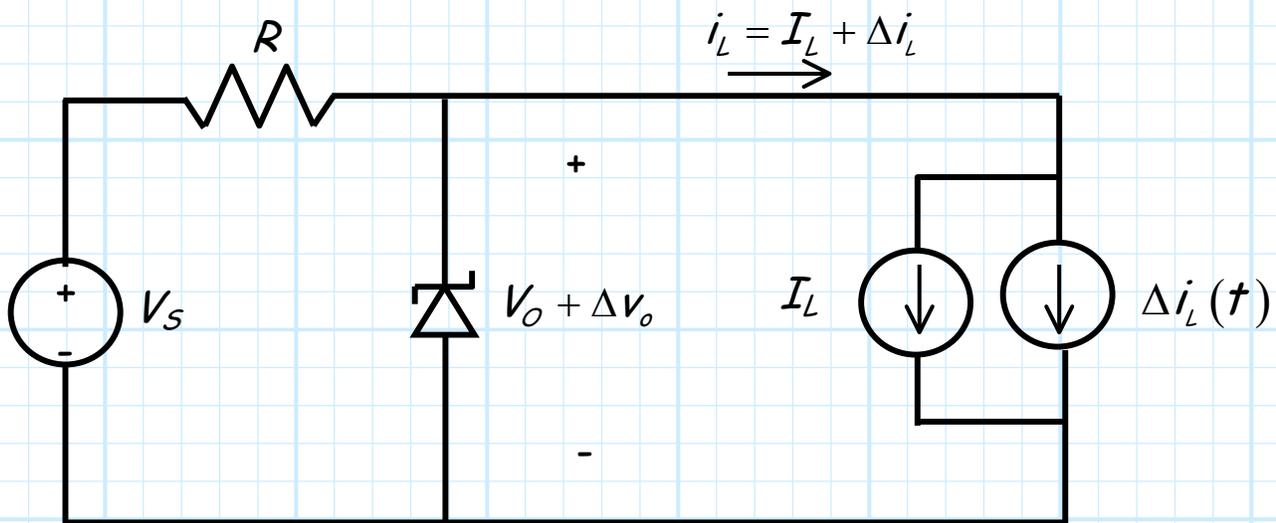
We can **replace** the load resistor with **current sources** to represent this load current:




**Q:** Just how are  $\Delta i_L$  and  $\Delta v_o$  related? I mean, if  $\Delta i_L$  equals, say,  $50 \text{ mA}$ , what will value of  $\Delta v_o$  be?

**A:** Determining this answer is **easy!** We simply need to perform a **small-signal analysis**.

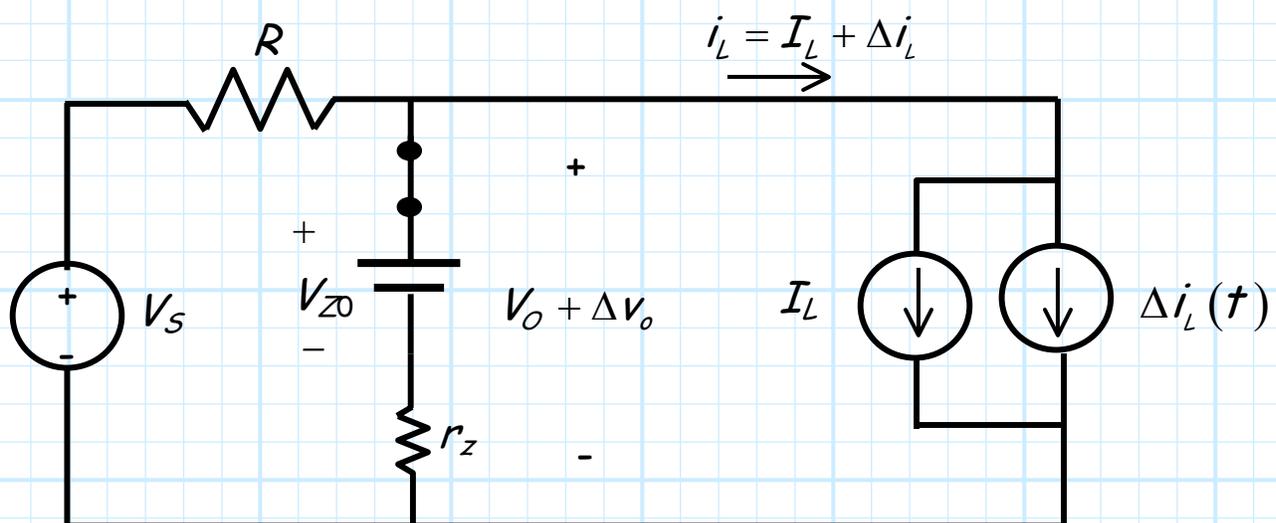In other words, we first replace the Zener diode with its **Zener PWL model**.



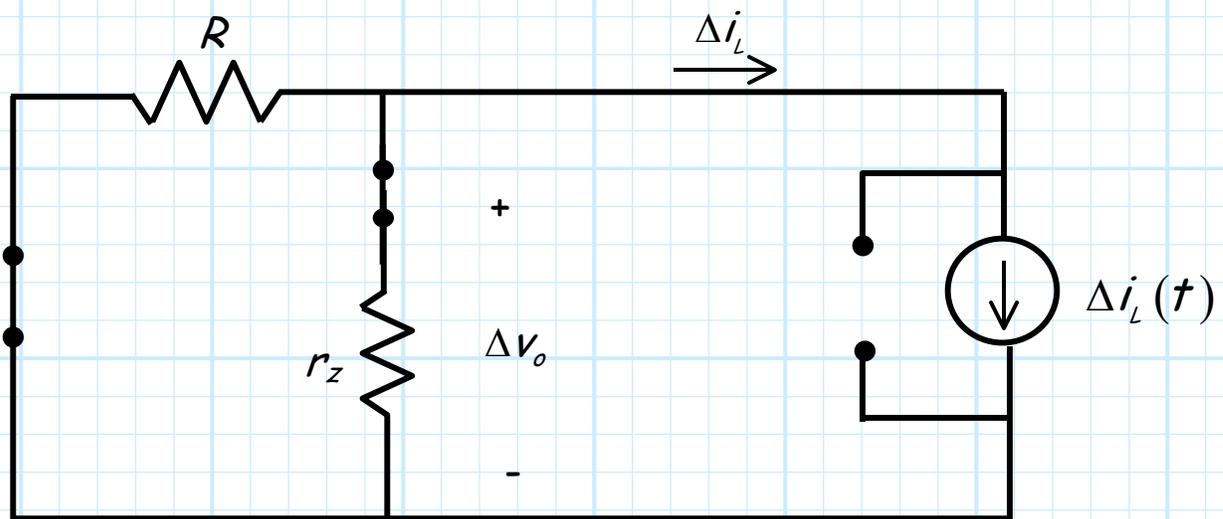We then turn **off** all the **DC** sources (including  $V_{Z0}$ ) and analyze the remaining **small-signal circuit!**



From **Ohm's Law**, it is evident that:

$$\begin{aligned}\Delta v_o &= -\Delta i_L (r_z \parallel R) \\ &= -\Delta i_L \left( \frac{r_z R}{r_z + R} \right)\end{aligned}$$

Rearranging, we find:

$$\text{load regulation} \doteq \frac{\Delta v_o}{\Delta i_L} = -\frac{r_z R}{r_z + R} = -r_z \parallel R \approx -r_z \quad [\text{Ohms}]$$

This equation describes an important performance parameter for shunt regulators. We call this parameter the **load regulation**.

- \* Note load regulation is expressed in units of **resistance** (e.g.,  $\Omega$ ).
- \* Note also that load regulation is a **negative** value. This means that **increasing**  $i_L$  leads to a **decreasing**  $v_o$  (and vice versa).
- \* Load regulation allows us to determine the **amount** that the load voltage changes ( $\Delta v_o$ ) when the load current changes ( $\Delta i_L$ ).
- \* For example, if load regulation is  $-0.0005 \text{ K}\Omega$ , we find that the load voltage will **decrease** 25 mV when the load current **increases** 50mA  
(i.e.,  $\Delta v_o = -0.0005 \Delta i_L = -0.0005(50) = -0.025 \text{ V}$ ).
- \* **Ideally**, load regulation is **zero**. Since dynamic resistance  $r_z$  is typically very small (i.e.,  $r_z \ll R$ ), we find that the load regulation of most shunt regulators is likewise **small** (this is a **good thing!**).