

# MOSFET Output Resistance

Recall that due to **channel-length modulation**, the MOSFET drain current is **slightly** dependent on  $v_{DS}$ , and thus is more accurately described as:

$$i_D = K (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

In order to determine the relationship between the small-signal voltage  $v_{gs}$  and small-signal current  $i_d$  we can apply a **small-signal analysis** of this equation:

$$\begin{aligned} i_d &= \left. \frac{di_D}{dv_{GS}} \right|_{v_{GS}=V_{GS}} v_{gs} \\ &= 2K (v_{GS} - V_t) \Big|_{v_{GS}=V_{GS}} v_{gs} \\ &= 2K (V_{GS} - V_t) v_{gs} \\ &= g_m v_{gs} \end{aligned}$$

Note that we evaluated the derivative at the DC bias point  $V_{GS}$ . The result, as we expected, was the **transconductance**  $g_m$ .

We can likewise determine the relationship between small-signal voltage  $v_{ds}$  and the small-signal current  $i_d$ :

$$\begin{aligned}
 i_d &= \left. \frac{di_D}{dv_{DS}} \right|_{v_{GS}=V_{GS}} v_{ds} \\
 &= \lambda K (v_{GS} - V_t)^2 \Big|_{v_{GS}=V_{GS}} v_{ds} \\
 &= \lambda K (V_{GS} - V_t)^2 v_{ds} \\
 &= \frac{v_{ds}}{r_o}
 \end{aligned}$$

where  $r_o$  is defined as the MOSFET output resistance:

$$\begin{aligned}
 r_o &= \frac{1}{\lambda K (V_{GS} - V_t)^2} \\
 &= \frac{1}{\lambda I_D}
 \end{aligned}$$

The small signal drain current  $i_d$  of a MOSFET (biased at a DC operating point  $I_D, V_{GS}$ ) is therefore:

$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_o}$$

where:

$$g_m = 2K (V_{GS} - V_t)$$

$$r_o = \frac{1}{\lambda K (V_{GS} - V_t)^2}$$