 


# NMOS Logic Circuits

An alternative way to construct a digital logic gate is to simply use a single **large resistor** as the pull-up network!



If the PDN is **open**, no current will flow ( $i_R = 0$ ), and thus there will be **no** voltage drop across the **Pull-Up Resistor  $R$** —the output will be **high**, **just** like before!

**But**, if the PDN is conducting, current **will** flow ( $i_R \neq 0$ ), and thus there **will** be a large voltage drop across  $R$ —the output will be **low** (sort of)!

This method of constructing digital devices is called **NMOS logic** (for hopefully **obvious** reasons!).

**Q:** *Why would we want use NMOS logic?*

**A:** Replacing the PUN with a single resistor greatly **simplifies** and **shrinks** the circuit. For complex gates (i.e., gates with **many** inputs), we can reduce the number of required devices (transistors and resistors) by **nearly half!**

**Q:** *Yikes! This seems to be a lot better. Why wouldn't we always use NMOS logic?*

**A:** There are **two** really big problems with NMOS logic (at least, when compared to **CMOS**):

1. Since current flows when the output is low, the static power dissipation is **not zero**.
2. Since current flows when the output is low,  $V_{OL}$  is **not** equal to its ideal value of **zero** (i.e.,  $V_{OL} \neq 0$ )!

Additionally, there is **one more** problem when implementing NMOS in **integrated circuits**. IC resistors are (relatively) very large and difficult to construct.

→ This problem, though, is easily solved—we replace the **pull-up resistor** with an **active load**.