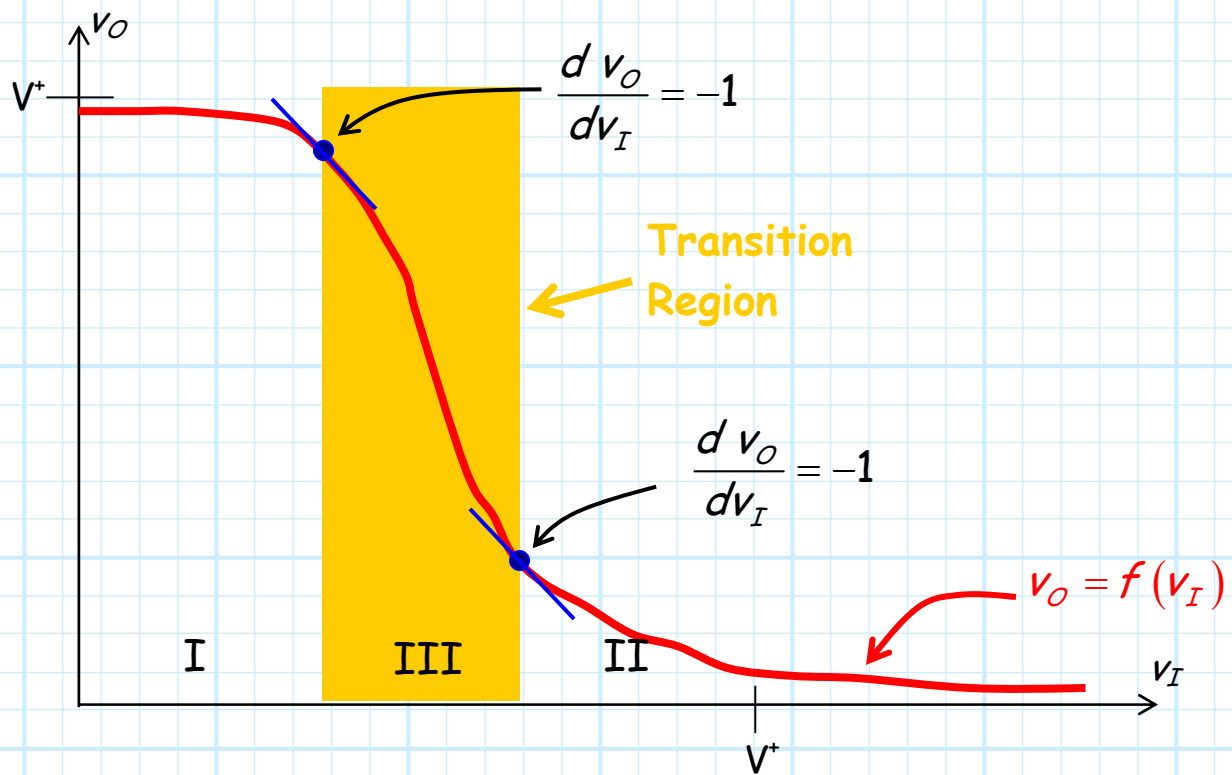


# Noise Margins

The transfer function of a digital inverter will typically look something like this:



Note that there are essentially **three** regions to this curve:

- I.** The region where  $v_I$  is relatively **low**, so that the output voltage  $v_O$  is **high**.
- II.** The region where  $v_I$  is relatively **high**, so that the output voltage  $v_O$  is **low**.
- III.** The **transition region**, where the input/output voltage is in an **indeterminate state** (i.e., an **ambiguous** region between high and low).

Note that the **transition region** is rather **arbitrarily** defined by the points on the transfer function where the magnitude of the **slope** is **greater than one** (i.e., where  $|dv_O/dv_I| > 1.0$ ).

Although this transfer function **looks** rather simple, there are actually **several parameters** that we use to **characterize** this transfer function—and thus characterize the digital inverter **as well!**

**1.** First of all, let's consider the case when  $v_I=0$ . The **output** of the digital inverter in this condition is **defined** as  $V_{OH}$  (i.e., OH  $\rightarrow$  "output high"), i.e.:


$$V_{OH} \doteq v_O \text{ when } v_I = 0$$

Thus,  $V_{OH}$  is essentially the "**ideal**" inverter **high** output, as it is the output voltage when the inverter input is at its ideal low input value  $v_I=0$ . Typically,  $V_{OH}$  is a value just **slightly** less than supply voltage  $V^+$ .

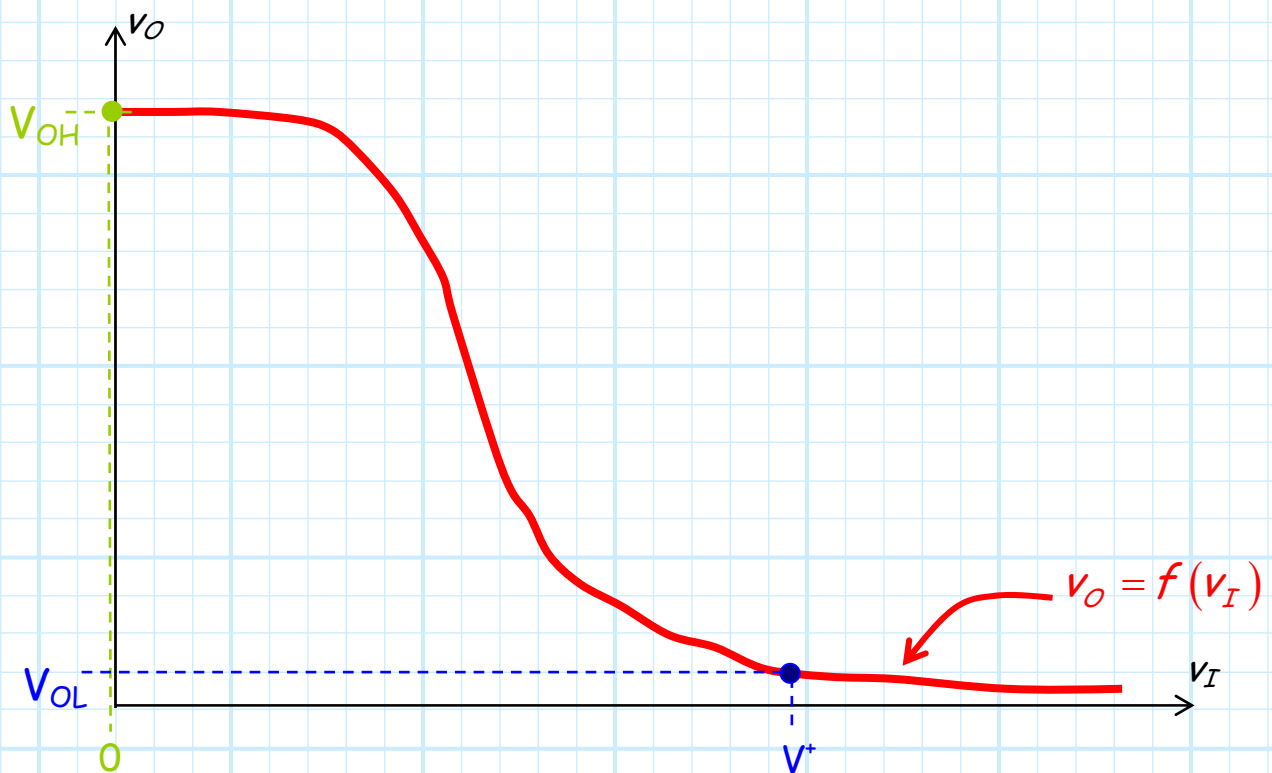**2.** Now, let's consider the case when  $v_I=V^+$ . The output of the digital inverter in this condition is **defined** as  $V_{OL}$  (i.e., OL  $\rightarrow$  "output low"), i.e.:

$$V_{OL} \doteq v_O \text{ when } v_I = V^+$$

Thus,  $V_{OL}$  is essentially the "ideal" inverter low output, as it is the output voltage when the inverter input is at its ideal high input value  $v_I = V^+$ . Typically,  $V_{OL}$  is a value just slightly greater than 0.



3. The "boundary" between region I and the transition region of the transfer function is denoted as  $V_{IL}$  (i.e., IL  $\rightarrow$  "input low"). Specifically, this is the value of the input voltage that corresponds to the first point on the transfer function where the slope is equal to -1.0 (i.e., where  $dv_O/dv_I = -1.0$ ).


Effectively, the value  $V_{IL}$  places an upper bound on an acceptably "low" value of input  $v_I$ —any  $v_I$  greater than  $V_{IL}$  is not considered to be a "low" input value. I.E.:

$v_I$  considered "low" only if  $v_I < V_{IL}$

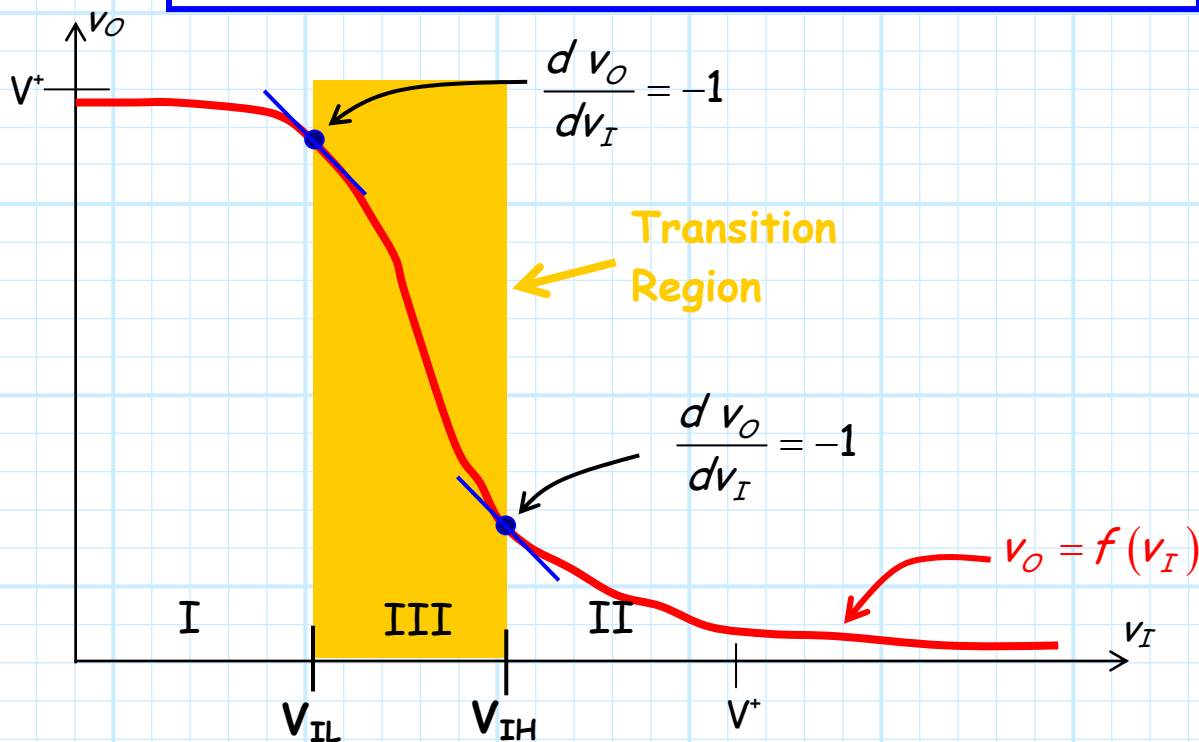4. Likewise, the "boundary" between region II and the transition region of the transfer function is denoted as  $V_{IH}$  (i.e., IH  $\rightarrow$  "input high"). Specifically, this is the value of the input voltage that corresponds to the **second** point on the transfer function where the **slope** is equal to -1.0 (i.e., where  $dv_o/dv_I = -1.0$ ).

Effectively, the value  $V_{IH}$  places a **lower bound** on an acceptably "high" value of input  $v_I$ —any  $v_I$  **lower** than  $V_{IH}$  is **not** considered to be a "high" input value. I.E.:

$v_I$  considered "high" only if  $v_I > V_{IH}$




Note then that the **input** voltages of the **transition region** (i.e.,  $V_{IL} < v_I < V_{IH}$ ) are **ambiguous** values—we **cannot** classify them as either a digital “low” value or a digital “high” value.

Accordingly, the **output** voltages in the transition region are both significantly less than  $V_{OH}$  and significantly larger than  $V_{OL}$ . Thus, the **output** voltages that occur in the transition region are **likewise ambiguous** (cannot be assigned a logical state).

**Lesson learned** → Stay away from the transition region!

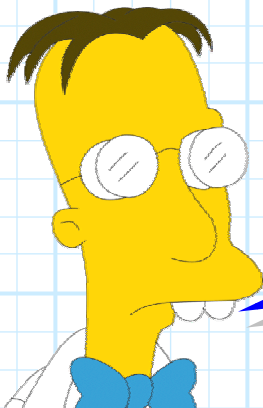In other words, we must ensure that an **input** voltage representing a logical “low” value is **significantly lower** than  $V_{IL}$ , and an **input** voltage representing a logical “high” value is **significantly higher** than  $V_{IH}$ .




**Q:** *Seems simple enough! Why don't we **end** this exceedingly dull handout and **move on** to something more interesting!?*



**A:** Actually, staying **out** of the transition region is sometimes **more difficult** than you might first imagine!

The reason for this is that in a **digital system**, the devices are **connected** together—the input of one device is the output of the other, and vice versa.

For example:

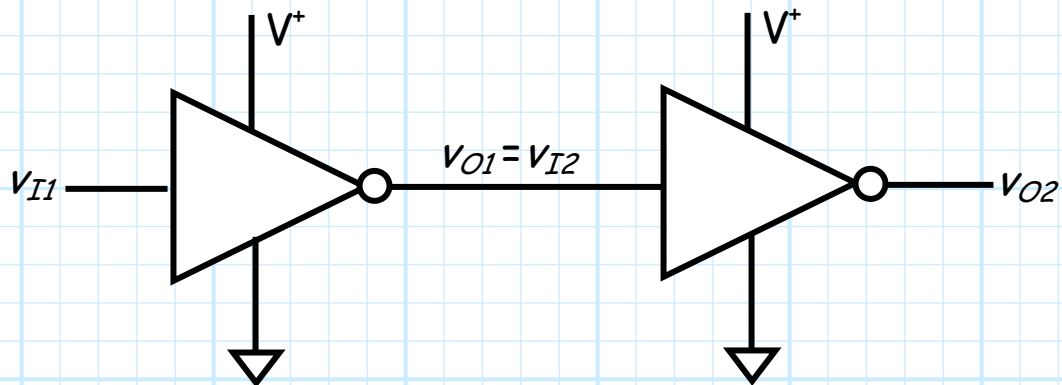

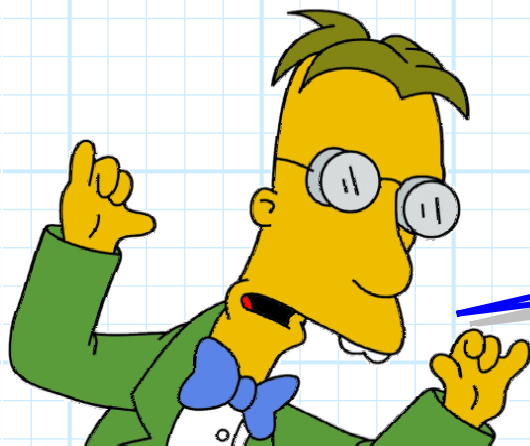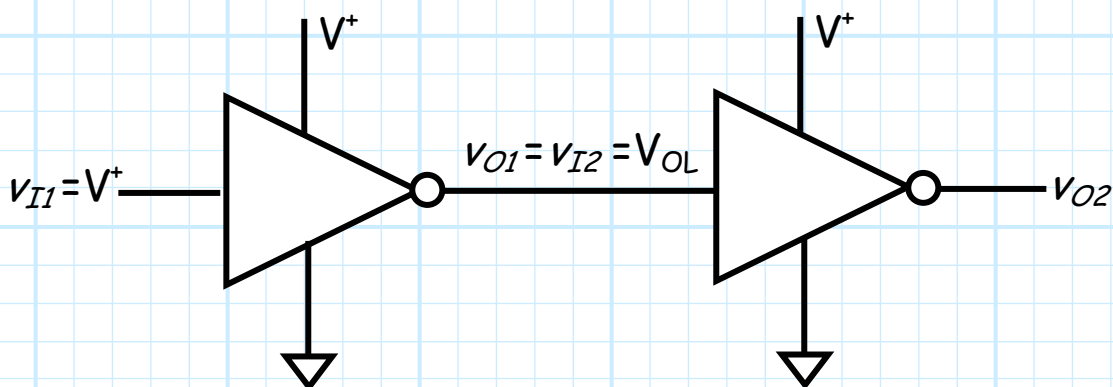Say that the **input** to the **first** digital inverter is  $v_{I1} = V^+$ . The **output** of that inverter is therefore  $v_{O1} = V_{OL}$ . Thus, the **input** to the **second** inverter is **likewise** equal to  $V_{OL}$  (i.e.,  $v_{I2} = v_{O2} = V_{OL}$ ).




**Q:** *So? This doesn't seem to be a problem—after all, isn't  $V_{OL}$  much lower than  $V_{IL}$ ??*

**A:** True enough! The input  $v_{I2}=V_{OL}$  is typically **well below** the maximum acceptable value  $V_{IL}$ . In fact, we have a specific name for the **difference** between  $V_{IL}$  and  $V_{OL}$ —we call this value **Noise Margin (NM)**:


$$NM_L = V_{IL} - V_{OL} \quad [Volts]$$

The noise margin essentially tells us **how close** we are to the **ambiguous** transition region for a typical case where  $v_I = V_{OL}$ . Of course, we do **not** wish to be close to this transition region at all, so **ideally** this noise margin is **very large**!

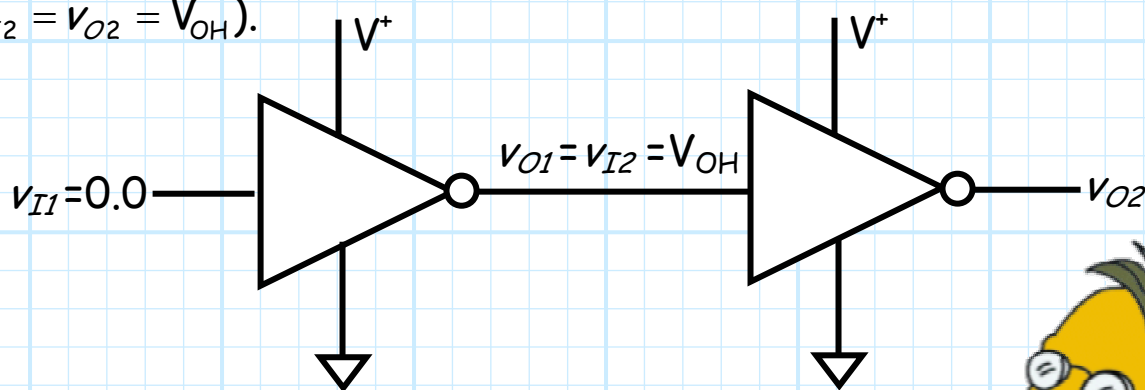Now, consider the **alternate** case where  $v_{I1}=0.0$  V. The **output** of the **first** inverter is therefore  $v_{O1} = V_{OH}$ . Thus, the **input** to the **second** inverter is **likewise** equal to  $V_{OH}$  (i.e.,  $v_{I2} = v_{O2} = V_{OH}$ ).



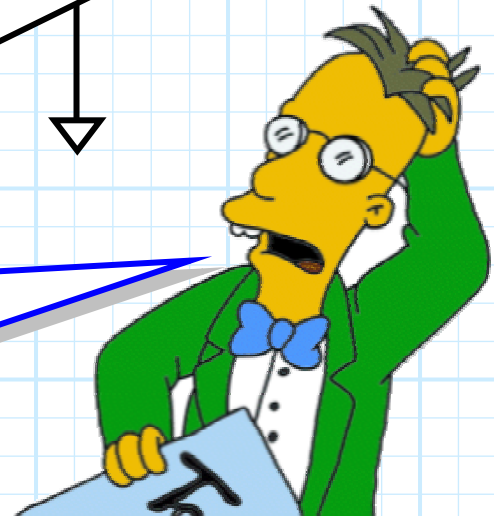**Q:** *This still doesn't seem to be a problem—after all, isn't  $V_{OH}$  much larger than  $V_{IH}$ ??*




**A:** Again, this is **true** enough! The input  $v_{I2}=V_{OH}$  is typically **well** above the minimum acceptable value  $V_{IH}$ . We can **again** specify the **difference** between  $V_{IH}$  and  $V_{OH}$  as a **noise margin** (NM):

$$NM_H = V_{OH} - V_{IH} \quad [Volts]$$


This **noise margin** essentially tells us how **close** we are to the ambiguous **transition region** for a typical case where  $v_I = 0.0V$ . Of course, we do **not** wish to be close to this transition region at all, so ideally this noise margin is **very large**!

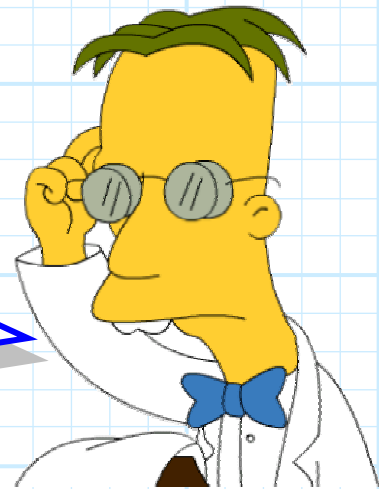**Q:** *I don't see why we care about the values of these "noise margins". Isn't the simple fact that  $V_{OL} < V_{IL}$  and  $V_{OH} > V_{IH}$  sufficient?*




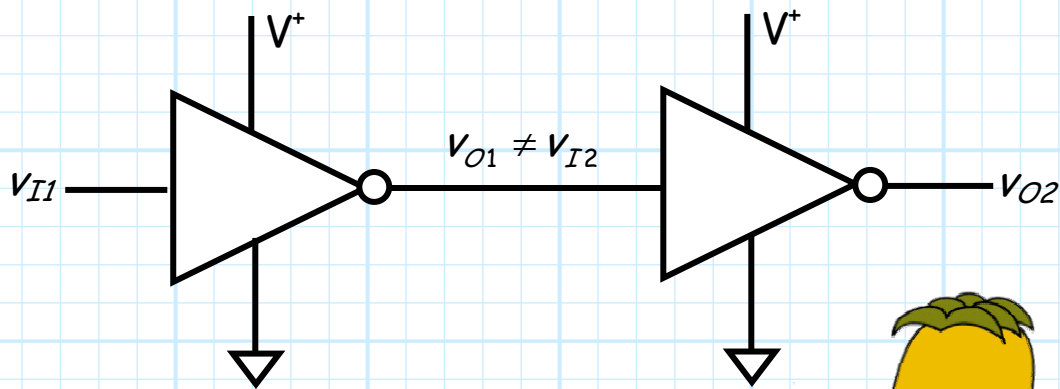**A:** **Ideally** yes. However, in our example we have made one important **assumption** that in fact may **not** be true! It turns out that in a **real** digital circuit,  $v_{I2}$  may **not** be equal to  $v_{O1}$  !!





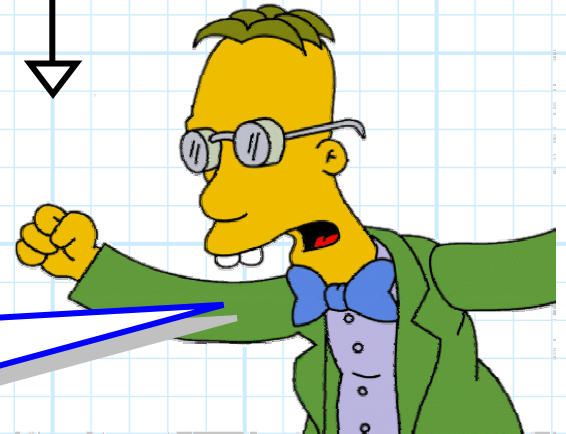**Q:** *What! How can this be possible? It appears to me that  $v_{I2}$  **must** be equal to  $v_{O1}$  !?*




**A:** It turns out that for a **real** digital circuit, a lot can happen **between** the output of one device and the input to another. The voltage at the input of a device might be affected by **many** sources—**only one** of which is the output device connected to it!

Examples of these “**extra**” sources include:

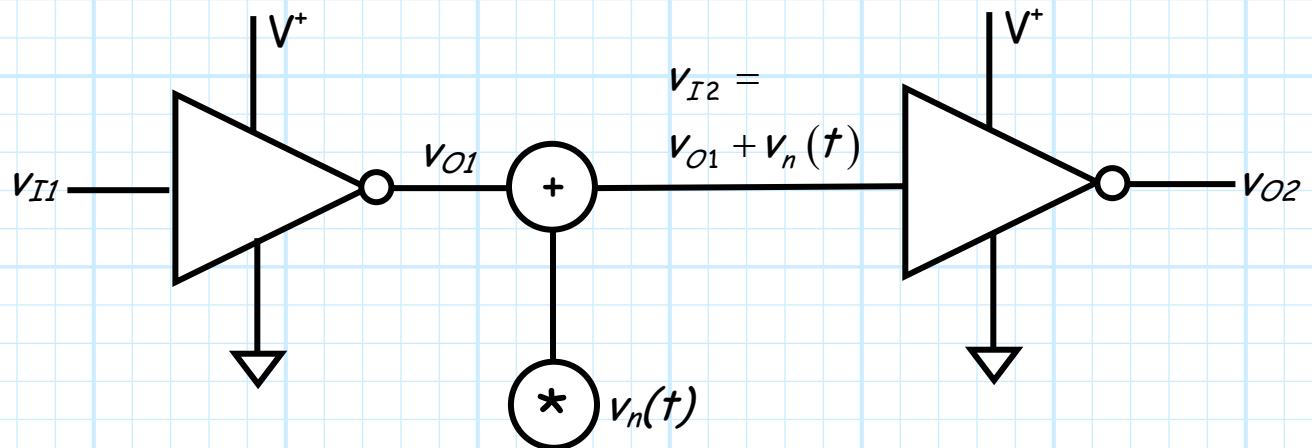
1. Thermal **noise**
2. Coupled signals
3. Power supply **transients**

We will **combine** the effect of **all** of these sources together into one “**noise**” source  $v_n(t)$ . Thus, a **better model** for our digital circuit example is:



Now, let's **reconsider** the case where  $V_{I1} = V^+$ . We find that the **input** to the **second** digital inverter is then

$$V_{I2} = V_{OL} + v_n(t):$$

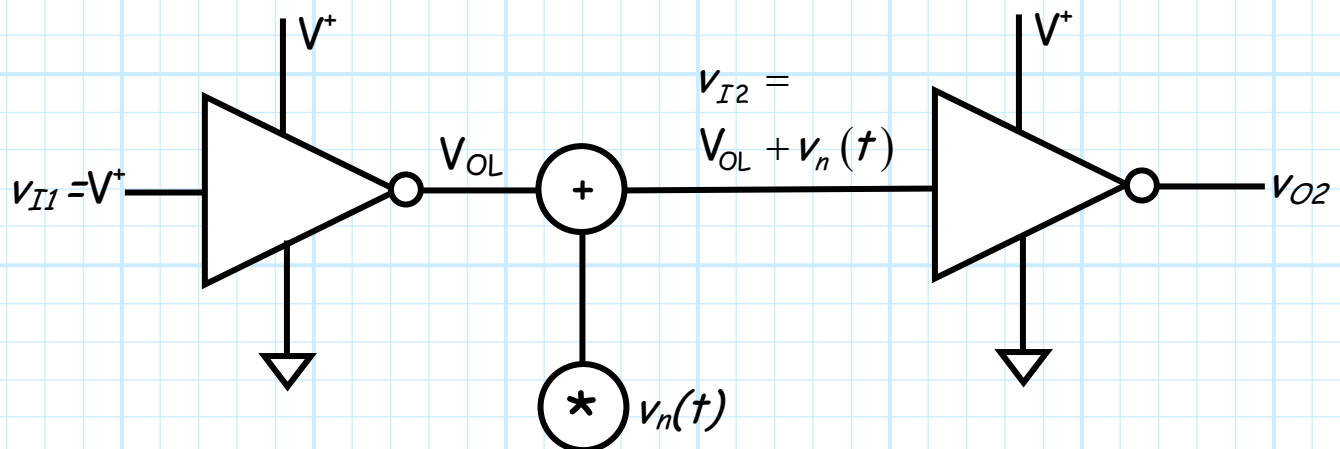

Now we see the **problem!** If the **noise** voltage is **too large**, then the **input** to the **second** inverter will **exceed** the maximum low input level of  $V_{IL}$ —we will have entered the dreaded **transition region!!!!**

To **avoid** the transition region, we find that the **input** to the **second** inverter must be less than  $V_{IL}$ :

$$V_{OL} + v_n(t) < V_{IL}$$

$$v_n(t) < V_{IL} - V_{OL}$$

$$v_n(t) < NM_L$$

**Look** at what this means! It says to avoid the transition region (i.e., for the input voltage to have an unambiguously "low" digital level), the **noise** must be **less** than **noise margin**  $NM_L$  for **all time** !

Thus, if the **noise margin**  $NM_L$  is **large**, the noise  $v_n(t)$  can be large **without** causing any deleterious effect (deleterious effect  $\rightarrow$  transition region). Conversely, if the noise margin  $NM_L$  is **small**, then the noise **must** be small to avoid **ambiguous** voltage levels.

**Lesson learned**  $\rightarrow$  **Large noise margins are very desirable!**

Considering **again** the example circuit, only this time with  $v_I = 0.0$  V, we find that to **avoid** the transition region (verify this for yourself!):

$$V_{OH} + v_n(t) > V_{IH}$$

$$v_n(t) > V_{IH} - V_{OH}$$

$$v_n(t) > -NM_H$$

$$-v_n(t) < NM_H$$

Note that the noise  $v_n(t)$  is **as likely** to be positive as negative—it is in fact **negative** valued noise that will send  $v_{I2}$  to a value **less** than  $V_{IH}$ !

Thus, we can make the statement that the **magnitude** of the **noise**  $v_n(t)$  must be **less** than the **noise margins** to avoid the ambiguous values of the disturbing **transition region!** I.E., make sure that:

$$|v_n(t)| < NM \quad \text{for all time } t$$