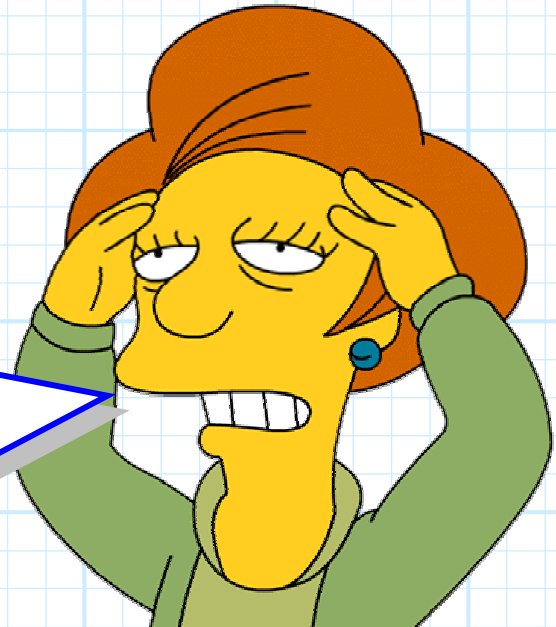


# Peak Inverse Voltage

**Q:** *I'm so confused! The bridge rectifier and the full-wave rectifier **both** provide full-wave rectification. Yet, the bridge rectifier use **4** junction diodes, whereas the full-wave rectifier only uses **2**. Why would we **ever** want to use the **bridge rectifier**?*



**A:** First, a slight **confession**—the results we derived for the bridge and full-wave rectifiers are **not** precisely correct!

Recall that we used the junction diode **CVD model** to determine the transfer function of each rectifier circuit. The problem is that the CVD model does **not** predict **junction diode breakdown**!

If the **source** voltage  $v_S$  becomes too **large**, the junction diodes can in fact **breakdown**—but the transfer functions we derived do **not** reflect this fact!

**Q:** *You mean that we must **rework** our analysis and find **new** transfer functions!?*



**A:** Fortunately **no**. Breakdown is an **undesirable** mode for circuit rectification. Our job as engineers is to design a rectifier that **avoids** it—that why the **bridge** rectifier is helpful!

To see why, consider the voltage across a **reversed biased** junction diode in **each** of our rectifier circuit designs.

Recall that the voltage across a **reverse biased ideal diode** in the **full-wave rectifier** design was:

$$v_{D2}' = -2v_S$$

so that the voltage across the **junction diode** is approximately:


$$\begin{aligned} v_D &= v_D' + 0.7 \\ &= -2v_S + 0.7 \end{aligned}$$

Now, assuming that the **source** voltage is a **sine wave**  $v_S = A \sin \omega t$ , we find that diode voltage is at it **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value  $A$ . I.E.;

$$v_D^{min} = -2A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in **forward** bias:

$$v_D^{max} = 0.7 \text{ V}$$

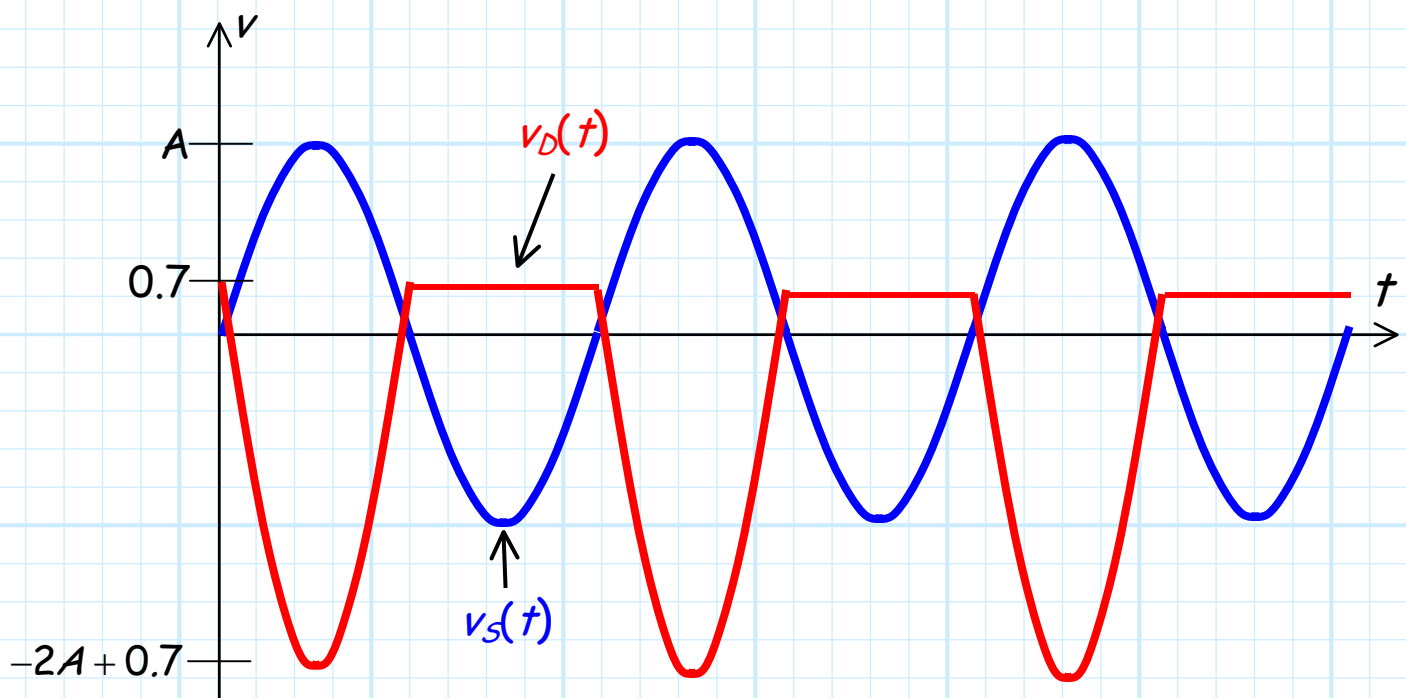

Note that this **minimum** diode voltage  $v_D$  is **very negative**, with an absolute value ( $|v_D^{min}| = 2A - 0.7$ ) nearly **twice** as large as the source magnitude  $A$ .

We call the absolute value of the minimum diode voltage the **Peak Inverse Voltage (PIV)**:

$$PIV = |v_D^{min}|$$

Note that this value is dependent on **both** the rectifier design **and** the magnitude of the source voltage  $v_s$ .



**Q:** *So, why do we need to determine PIV? I'm not sure I see what difference this value makes.*

**A:** The Peak Inverse Voltage **answers** one important question—**will** the junction diodes in our rectifier **breakdown**?

→ **If** the PIV is **less** than the Zener breakdown voltage of our rectifier diodes (i.e., if  $PIV < V_{ZK}$ ), then we know that our junction diodes will **remain** in either forward or reverse bias for all time  $t$ . The rectifier will operate “properly”!

→ However, **if** the PIV is **greater** than the Zener breakdown voltage of our rectifier diodes (i.e., if  $PIV > V_{ZK}$ ), then we know that our junction diodes will **breakdown** for at least **some** small amount of time  $t$ . The rectifier will **NOT** operate properly!



**Q:** So what do we do if PIV is greater than  $V_{ZK}$ ? How do we fix this problem?

**A:** We have **two** possible **solutions**:

1. Use junction diodes with **larger** values of  $V_{ZK}$  (if they exist!).
2. Use the **bridge** rectifier design.

**Q:** The **bridge** rectifier! How would that solve our **breakdown** problem?



**A:** To see how a **bridge** rectifier can be **useful**, let's determine its Peak Inverse Voltage **PIV**.

First, we recall that the voltage across the **reverse biased ideal diodes** was:

$$v_D^i = -v_S$$

so that the voltage across the **junction diode** is approximately:


$$\begin{aligned} v_D &= v_D^i + 0.7 \\ &= -v_S + 0.7 \end{aligned}$$

Now, assuming that the **source** voltage is a **sine wave**  $v_S = A \sin \omega t$ , we find that diode voltage is at its **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value  $A$ . I.E.:

$$v_D^{min} = -A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in forward bias:

$$v_D^{max} = 0.7 \text{ V}$$

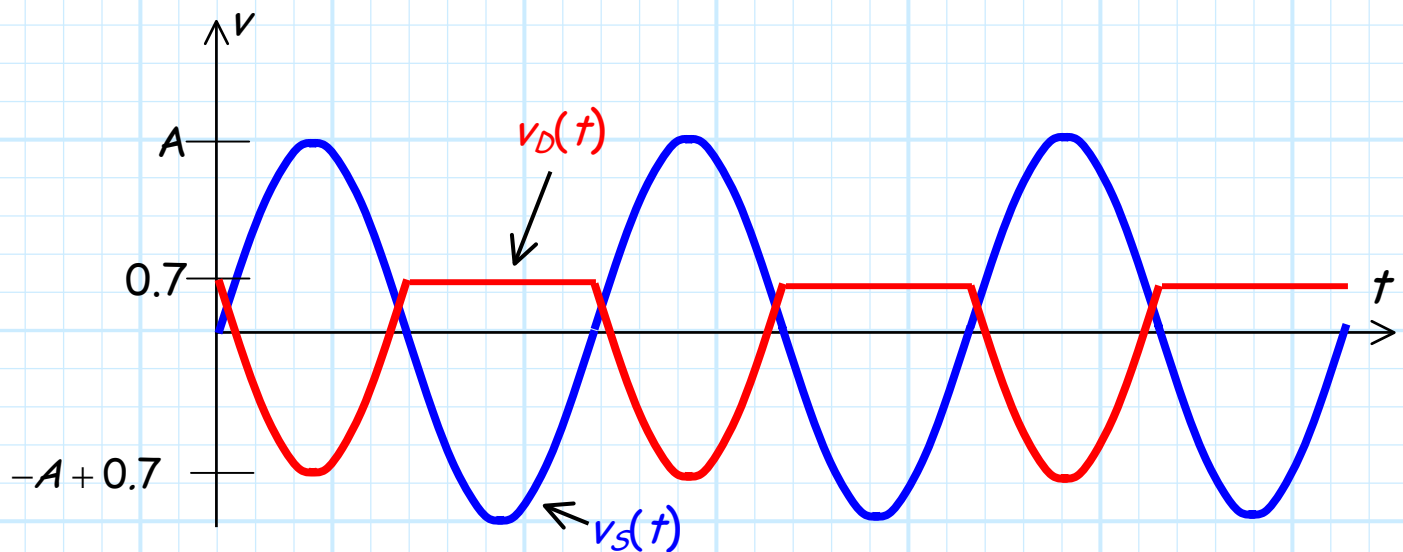

Note that this minimum diode voltage is **very negative**, with an absolute value ( $|v_D^{min}| = A - 0.7$ ), approximately **equal** to the value of the **source magnitude**  $A$ .

Thus, the **PIV** for a **bridge** rectifier with a **sinusoidal source** voltage is:

$$PIV = A - 0.7$$

Note that this **bridge** rectifier value is approximately **half** the PIV we determined for the **full-wave** rectifier design!

Thus, the source voltage (and the output DC component) of a **bridge** rectifier can be **twice** that of the full-wave rectifier design—this is why the **bridge** rectifier is a very **useful** rectifier design!