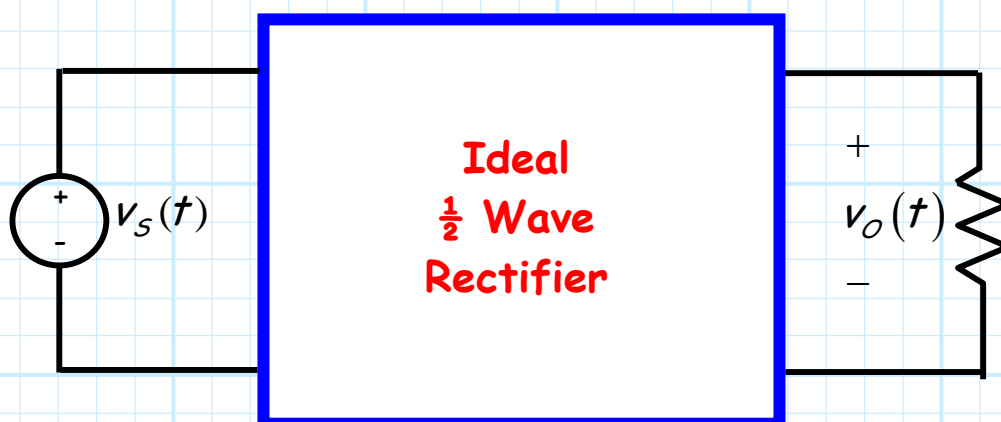


Signal Rectification


An important application of junction diodes is **signal rectification**.

There are **two** types of signal rectifiers, **half-wave** and **full-wave**.


Let's first consider the **ideal half-wave rectifier**. It is a circuit with the transfer function $v_o = f(v_s)$:


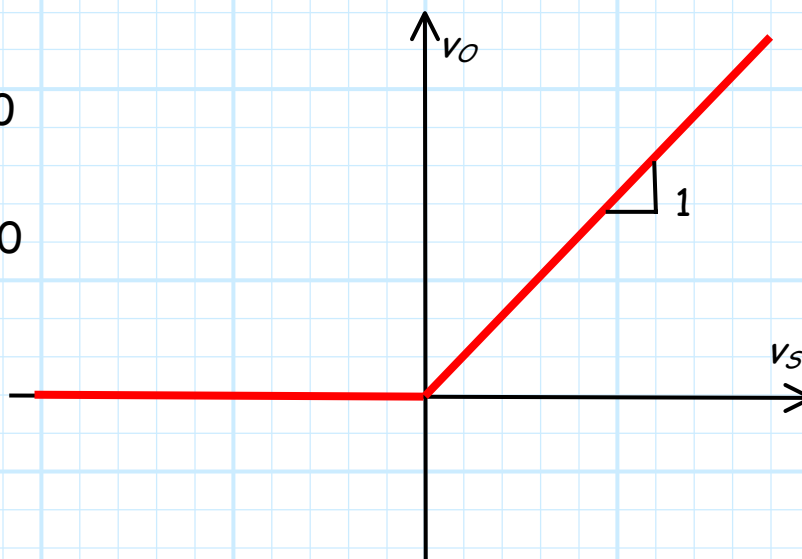
$$v_o = \begin{cases} 0 & \text{for } v_s < 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$





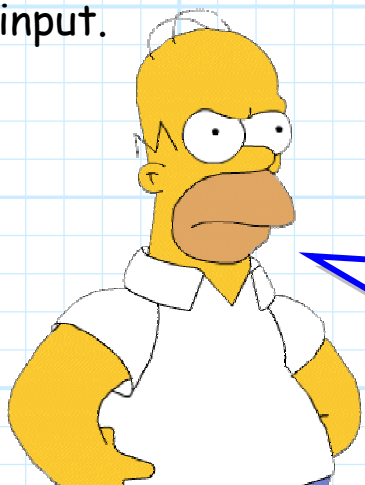Pretty simple! **When** the input is negative, the output is **zero**, whereas **when** the input is positive, the output is the **same** as the input.




Q: *Pretty simple and pretty stupid I'd say! This might be your most **pointless** circuit yet. How is **this** circuit even remotely useful??*

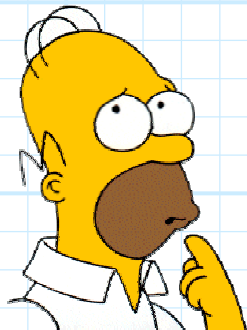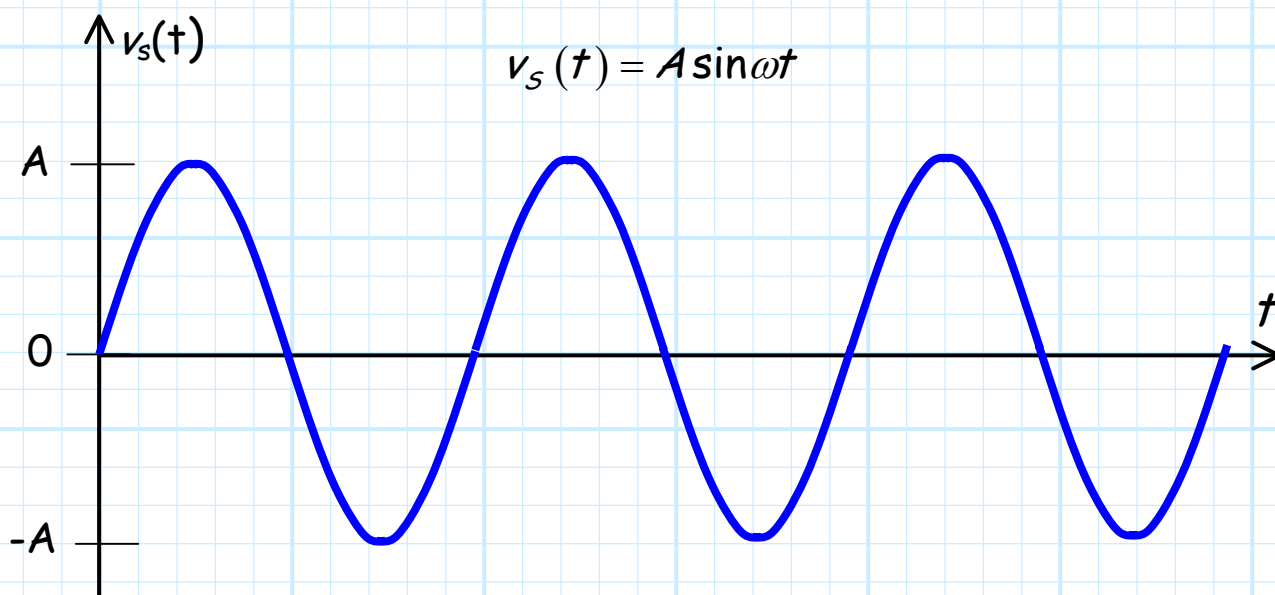A: To see **why** a half-wave rectifier is useful, consider the **typical** case where the input source voltage is a **sinusoidal** signal with **frequency** ω and peak **magnitude** A :




Think about what the **output** of the half-wave rectifier would be! Remember the rule: when $v_s(t)$ is **negative**, the output is **zero**, when $v_s(t)$ is **positive**, the output is **equal** to the input.

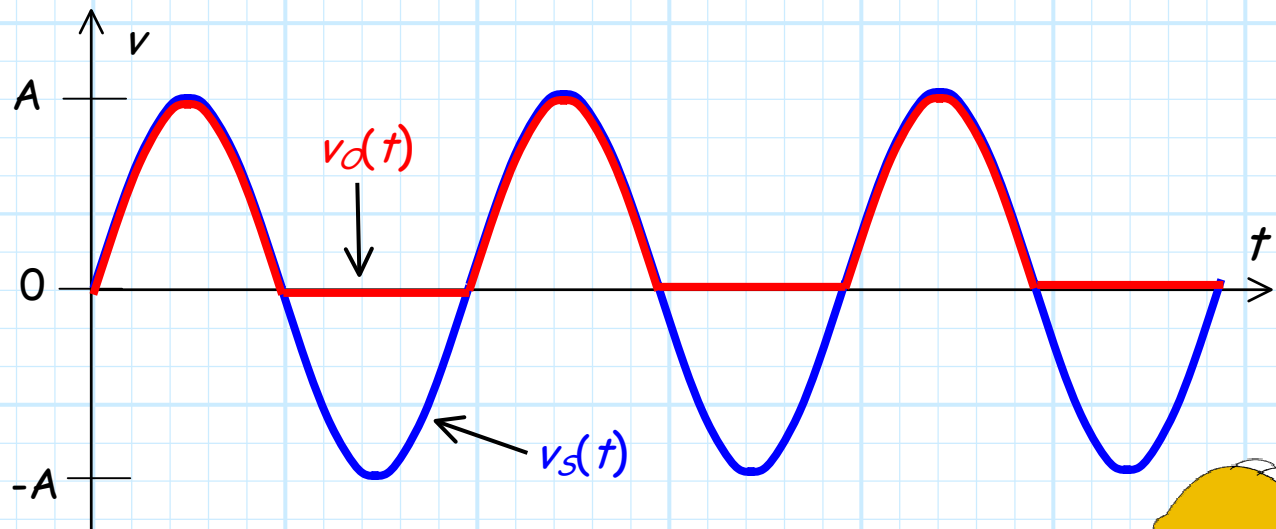The **output** of the half-wave rectifier for **this** example is therefore:



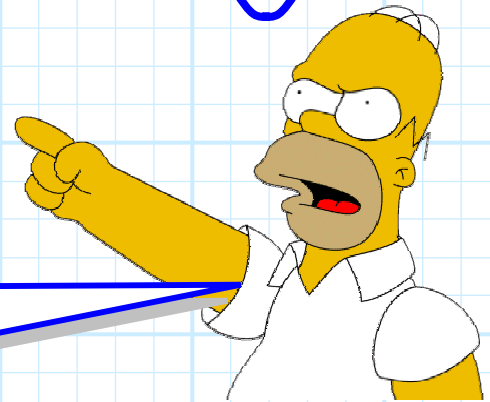Q: *That's the **lamest** result I've ever seen. What good is **half** a sine wave? Why even bother?*



A: Although it may appear that our rectifier had **little** useful effect on the input signal $v_s(t)$, in fact the difference between input $v_s(t)$ and output $v_d(t)$ is both **important** and **profound**.

To see how, consider first the **DC component** (i.e. the time-averaged value) of the **input** sine wave:



$$\begin{aligned} V_S &= \frac{1}{T} \int_0^T v_s(t) dt \\ &= \frac{1}{T} \int_0^T A \sin \omega t dt = 0 \end{aligned}$$

Thus, (as you probably already knew) the **DC component** of a sine wave is **zero**—a sine wave is an **AC signal**!

Now, contrast this with the **output** $v_o(t)$ of our half-wave rectifier. The **DC component** of the **output** is:

$$\begin{aligned} V_o &= \frac{1}{T} \int_0^T v_o(t) dt \\ &= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt + \frac{1}{T} \int_{T/2}^T 0 dt = \frac{A}{\pi} \end{aligned}$$

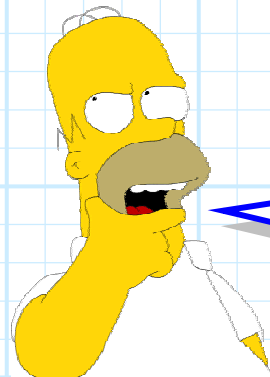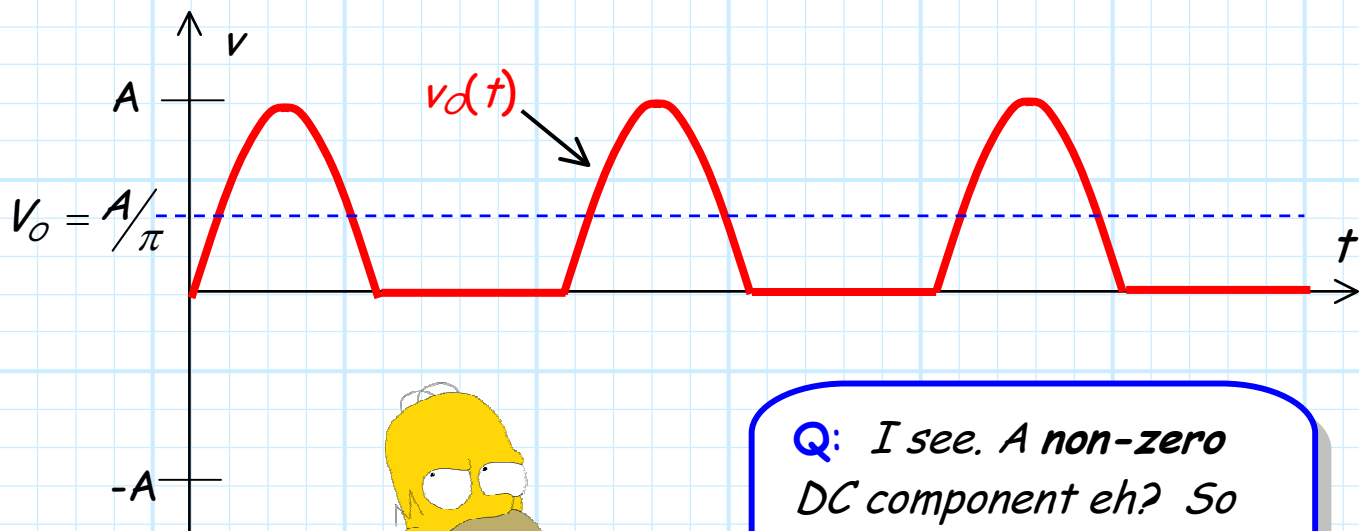
Unlike the input, the **output** has a **non-zero** (positive) **DC component** ($V_o = A/\pi$)!



Q: *I see. A non-zero DC component eh? So refresh my memory, why is that important?*

A: Recall that the **power distribution system** we use is an **AC system**. The source voltage $v_s(t)$ that we get when we plug our "**power cord**" into the wall socket is a 60 Hz **sinewave**—a source with a **zero DC component**!

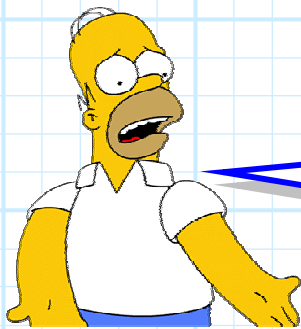
The **problem** with this is that most **electronic devices** and systems, such as TVs, stereos, computers, etc., require a **DC voltage(s)** to operate!




Q: *But, how can we create a DC supply voltage if our power source $v_s(t)$ has no DC component??*

A: That's **why** the half-wave rectifier is so **important**! It takes an AC source with **no DC component** and creates a signal with **both** a DC and AC component.

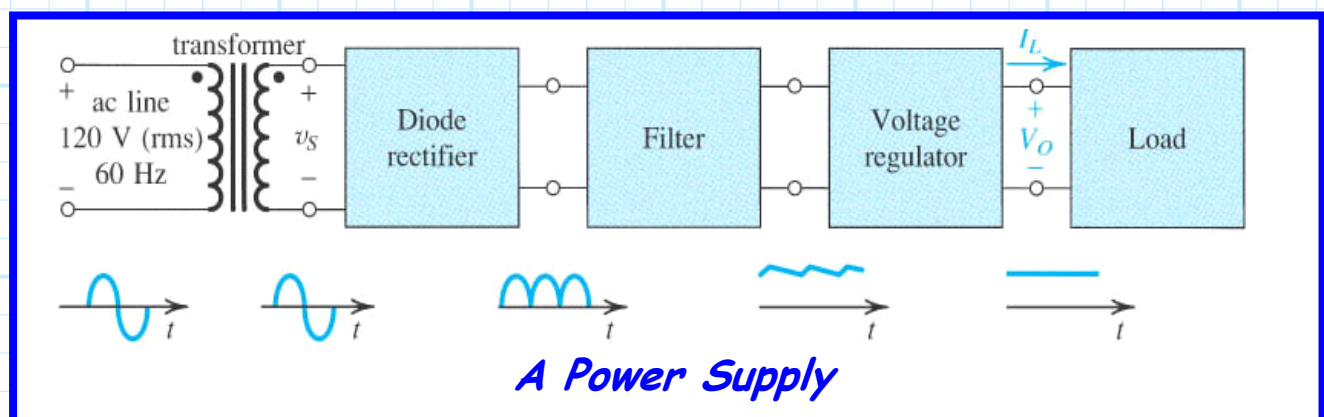
We can then pass the output of a half-wave rectifier through a **low-pass filter**, which **suppresses** the AC component but lets the DC value ($V_o = A/\pi$) pass through. We then **regulate** this output and form a **useful DC voltage source**—one suitable for powering our electronic systems!



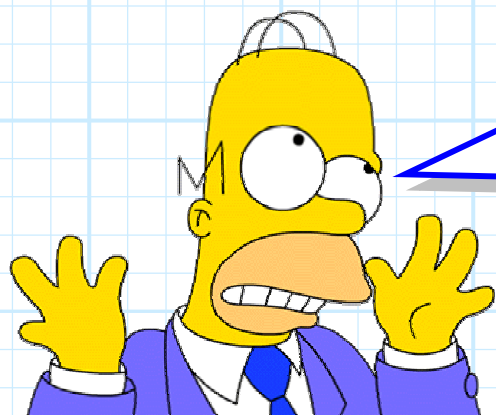


Q: *OK, now I see why the ideal half-wave rectifier might be useful. But, is there any way to actually build this magical device?*

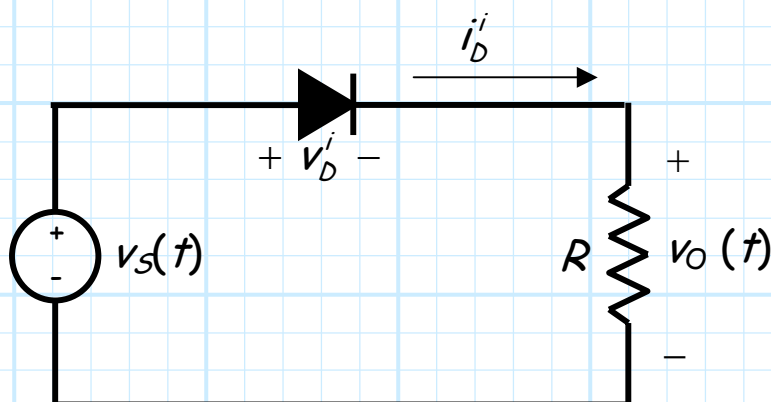A: An ideal half-wave rectifier can be "built" if we use an ideal diode.





If we follow the transfer function **analysis steps** we studied earlier, then we will find that this circuit is indeed an **ideal half-wave rectifier!**
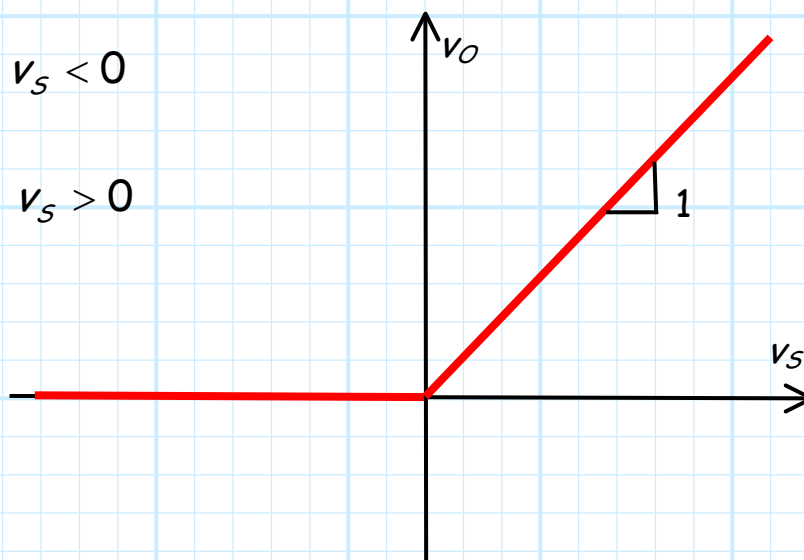
$$v_O = \begin{cases} 0 & \text{for } v_S < 0 \\ v_S & \text{for } v_S > 0 \end{cases}$$




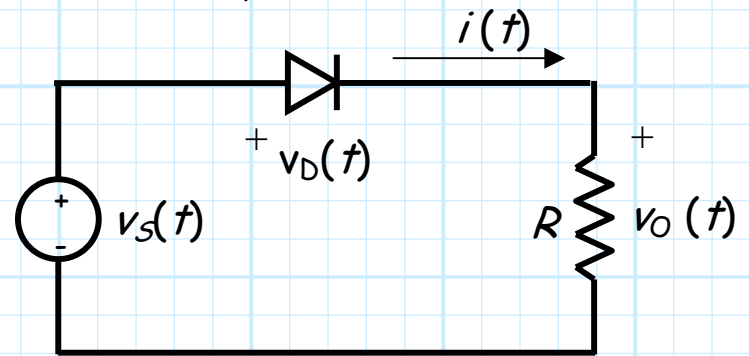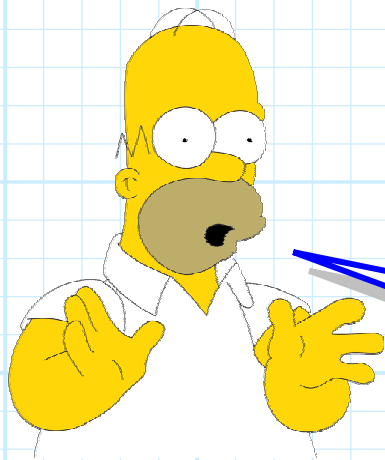Of course, since **ideal** diodes do **not** exist, we must use a **junction diode** instead:




Q: *This circuit looks so familiar! Haven't we studied it before?*

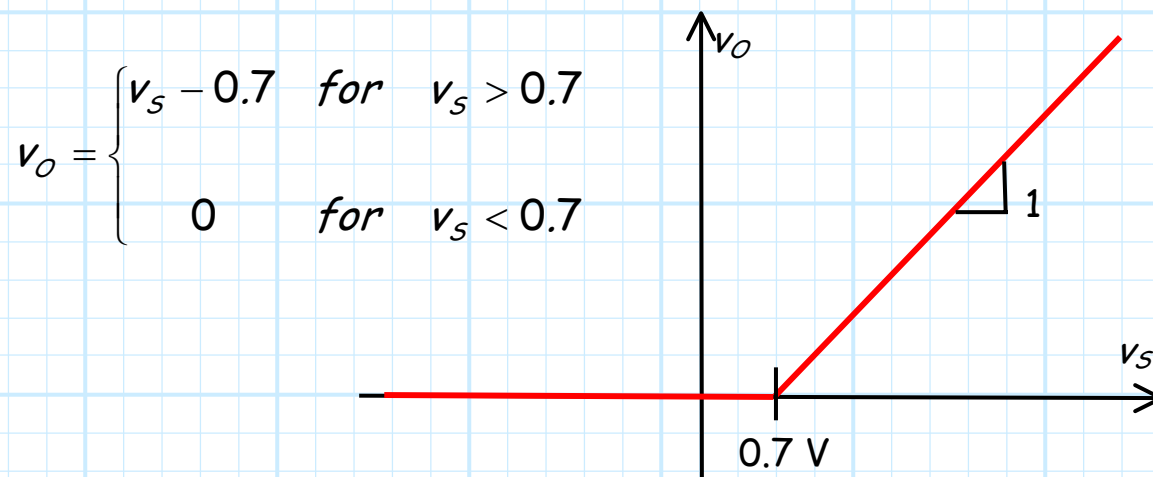A: Yes! It was an **example** where we determined the junction diode circuit transfer function. Recall that the **result** was:



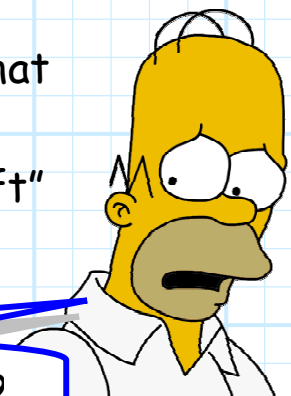Note that this result is **slightly different** from that of the **ideal** half-wave rectifier! The **0.7 V drop** across the junction diode causes a horizontal "shift" of the transfer function from the ideal case.




Q: *So then this junction diode circuit is worthless?*

A: Hardly! Although the transfer function is **not quite** ideal, it works **well enough** to achieve the goal of signal rectification—it takes an input with **no** DC component and creates an output with a **significant** DC component!


Note what the transfer function “**rule**” is now:

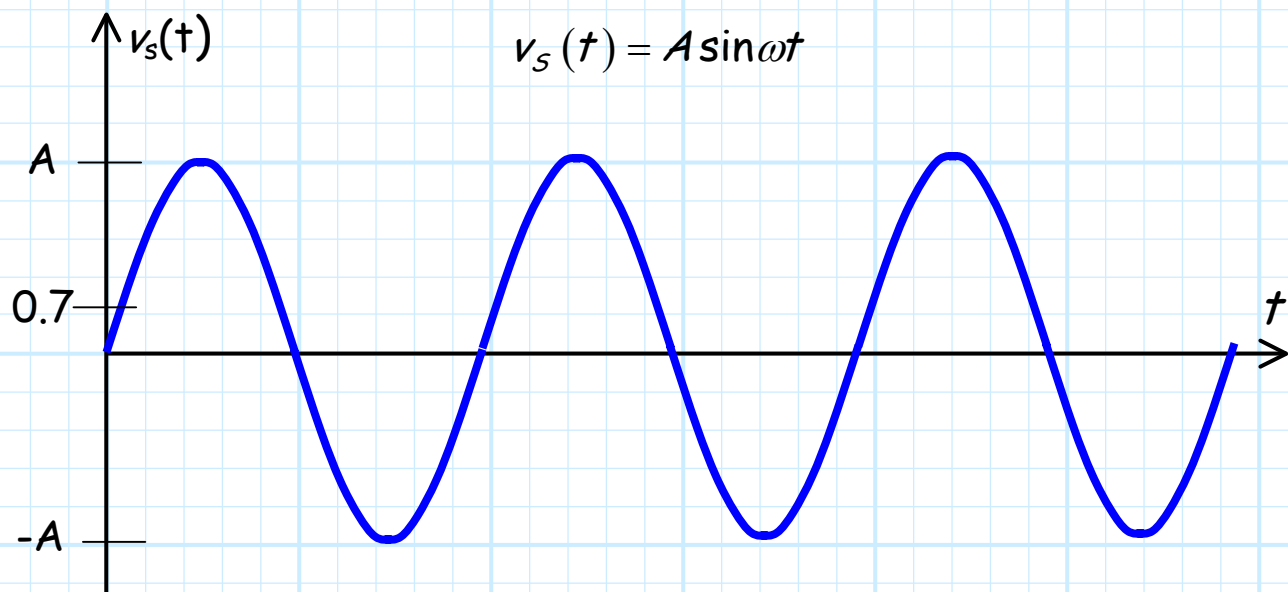1. When the input is **greater** than 0.7 V, the output voltage is **equal** to the input voltage minus 0.7 V.
2. When the input is **less** than 0.7 V, the output voltage is **zero**.

So, let's consider **again** the case where the **source** voltage is **sinusoidal** (just like the source from a “wall socket”!):



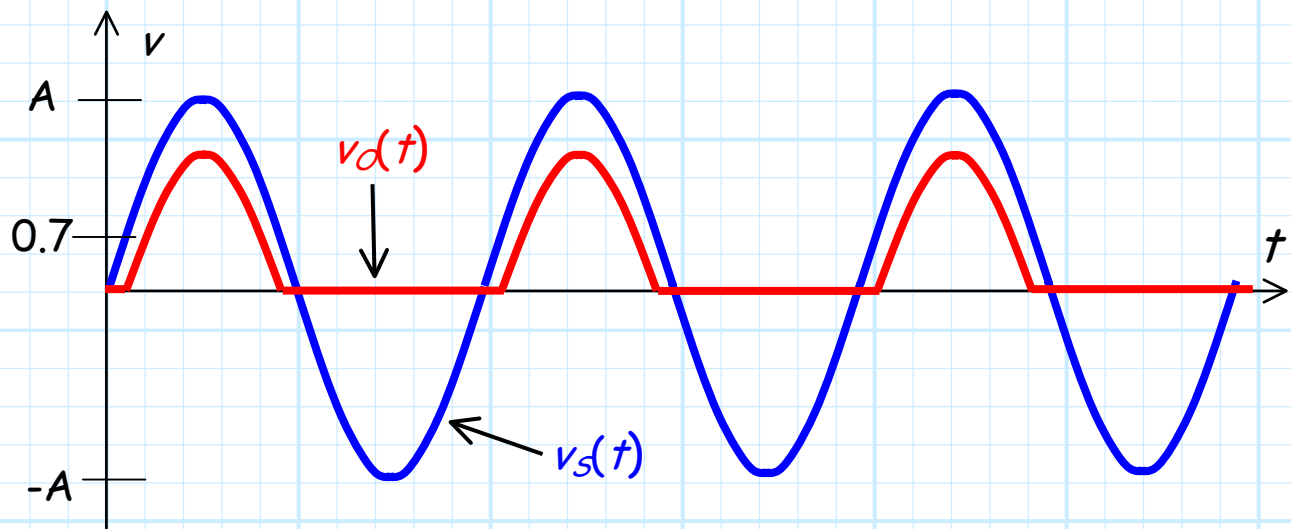The output of our **junction diode** half-wave rectifier would therefore be:




Although the output is **shifted downward** by 0.7 V (note in the plot above this is **exaggerated**, typically $A \gg 0.7V$), it should be apparent that the **output signal** $v_d(t)$, unlike the input signal $v_s(t)$, has a **non-zero** (positive) **DC component**.

Because of the 0.7 V shift, this DC component is **slightly smaller** than the **ideal** case. In fact, we find that if $A \gg 0.7$, this **DC component** is approximately:


$$V_o \approx \frac{A}{\pi} - 0.35 \text{ V}$$

In other words, **just 350 mV less than ideal!**

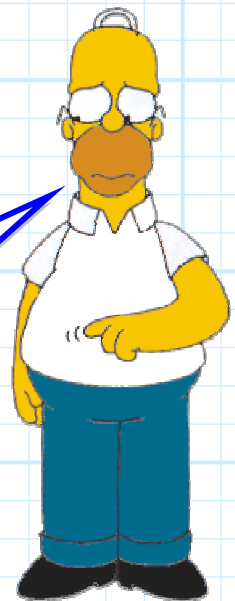
Q: *Way back on the first page you said that there were **two** types of rectifiers. I now understand **half-wave** rectification, but what about these so-called **full-wave** rectifiers?*



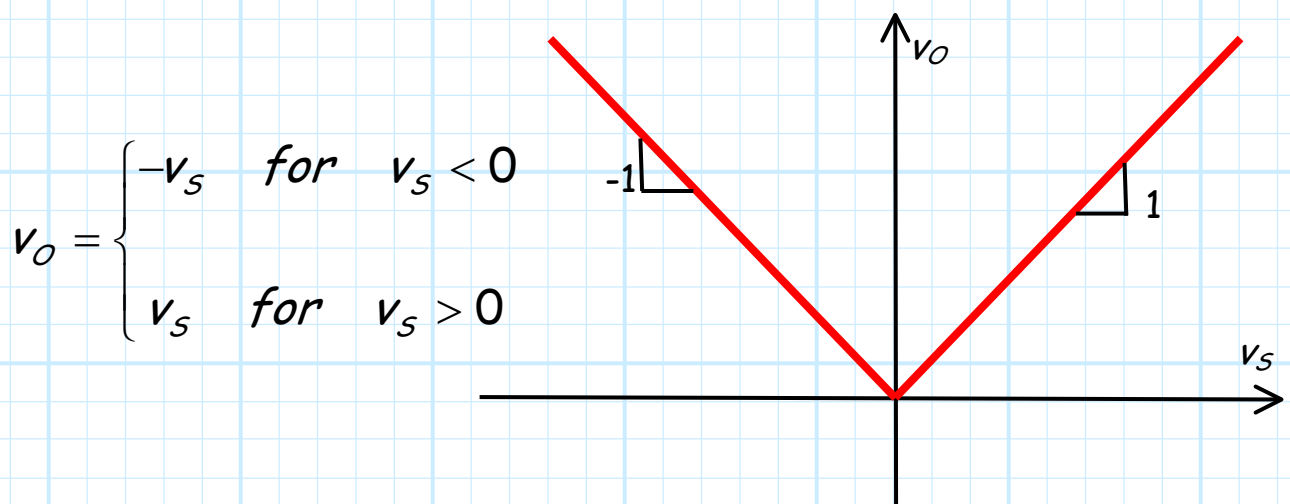A: Almost forgot! Let's examine the transfer function of an ideal full-wave rectifier:




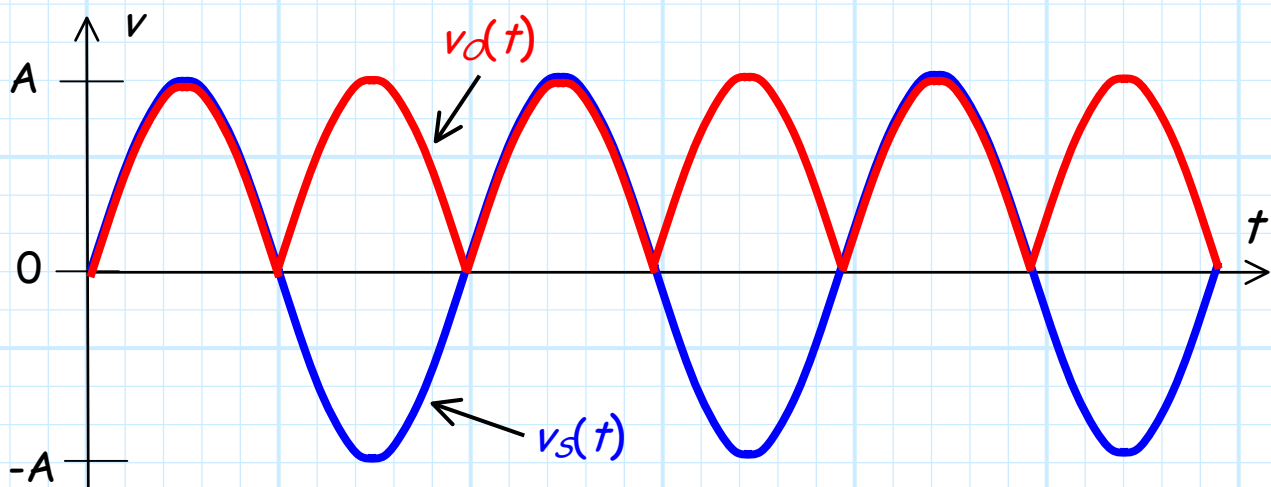
If the ideal half-wave rectifier makes **negative** inputs **zero**, the ideal full-wave rectifier makes **negative** inputs—**positive**! For **example**, if we again consider our **sinusoidal** input, we find that the output will be:



The result is that the output signal will have a DC component **twice** that of the ideal half-wave rectifier!

$$V_o = \frac{1}{T} \int_0^T v_o(t) dt$$
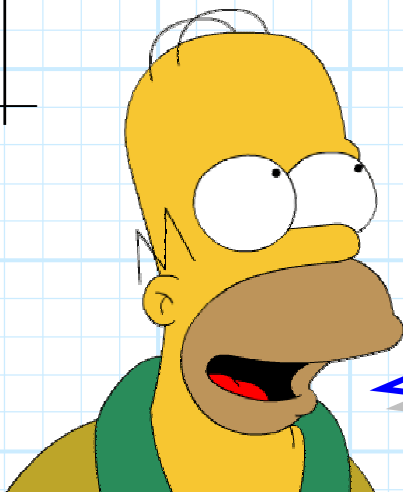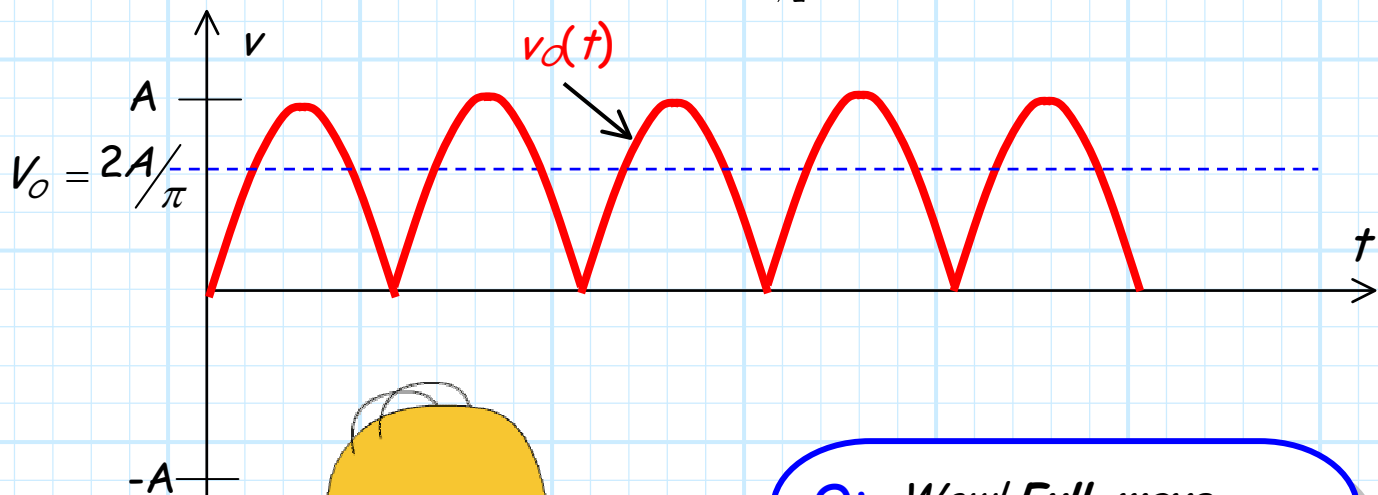
$$= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt - \frac{1}{T} \int_{T/2}^T A \sin \omega t dt = \frac{2A}{\pi}$$



Q: *Wow! Full-wave rectification appears to be twice as good as half-wave. Can we build an ideal full-wave rectifier with junction diodes?*

A: Although we cannot build an **ideal** full-wave rectifier with **junction** diodes, we can build full-wave rectifiers that are **very close** to ideal with junction diodes!