

# The CMOS Inverter

Consider the **complementary MOSFET (CMOS)** inverter circuit:


In this circuit:

$$i_{DP} = i_{DN} \doteq i_D$$

$$K_n = K_p \doteq K$$

$$V_{tp} = V_{tn} \doteq V_t$$

$$(V_{DD} > 2V_t)$$

 

**Q:** Why do we call it "**Complementary**"?

**A:** Because the device consists of an NMOS and PMOS transistor, each with **equal**  $K$  and equal but opposite  $V_t$ .


**Q:** What makes the **CMOS** inverter so great?

**A:** Let's **analyze** the circuit and find out!

First, let's consider the case where the **input voltage** is at the perfect "high" state  $v_I = V_{DD}$ .

For this case, it is readily **apparent** that:
 
$$v_{GSN} = V_{DD} \text{ and } v_{GSP} = 0.0 \text{ V}$$



Hence, we can conclude:

$$v_{GSN} = V_{DD} > V_{tn} \rightarrow Q_N \text{ has an induced channel!}$$

and:

$$v_{GSP} = 0.0 \text{ V} > V_{tp} \rightarrow Q_P \text{ has no induced channel!}$$

Thus, we can conclude that  $Q_P$  is in **cutoff**, and  $Q_N$  is **either** in saturation or triode.

Let's **ASSUME** that  $Q_N$  is in **triode**, so we **ENFORCE** the condition that:

$$i_D = K_n \left[ 2(v_{GSN} - V_{tn})v_{DSN} - v_{DSN}^2 \right]$$

Note that:

$$v_{GSN} = v_I = V_{DD} \quad \text{and} \quad v_{DSN} = v_O$$

Therefore:

$$\begin{aligned} i_D &= K_n \left[ 2(v_{GSN} - V_{tn})v_{DSN} - v_{DSN}^2 \right] \\ &= K \left[ 2(V_{DD} - V_t)v_O - v_O^2 \right] \end{aligned}$$

Now, we actually KNOW that  $Q_P$  is in **cutoff**, so we likewise ENFORCE:

$$i_D = 0.0$$

Equating these two ENFORCED conditions, we find that:

$$i_D = 0 = K \left[ 2(V_{DD} - V_t)v_O - v_O^2 \right]$$

Solving, we find that the **output** voltage must be **zero**!


$$v_O = v_{DSN} = 0.0 \text{ V}$$

Thus,  $v_{DSN} = 0 < v_{GSN} - V_{tn} = V_{DD} - V_t$ . ✓

$Q_N$  is indeed in the **triode** mode!

So, let's **summarize**. When  $v_I = V_{DD}$ :

 
1.  $Q_P$  is in cutoff and  $Q_N$  is in triode
2.  $i_D = 0.0$
3.  $v_O = 0.0$



Now, let's consider the case where the **input** voltage is at the perfect "low" state  $v_I = 0.0$ .

For this case, it is readily apparent that:
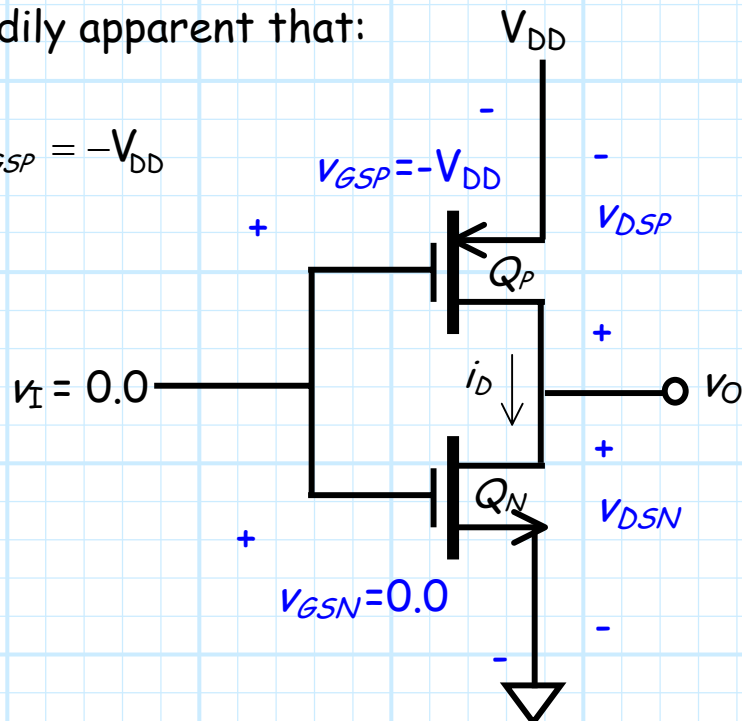
$$v_{GSN} = 0.0 \text{ and } v_{GSP} = -V_{DD}$$



Hence, we can conclude:

$$v_{GSN} = 0.0 < V_{tn} \rightarrow Q_N \text{ has no induced channel!}$$

and:

$$v_{GSP} = -V_{DD} < V_{tp} \rightarrow Q_P \text{ has an induced channel!}$$

Thus, we can conclude that  $Q_N$  is in **cutoff**, and  $Q_P$  is either in saturation or triode.

Let's ASSUME that  $Q_P$  is in **triode**, so we ENFORCE the condition that:

$$i_D = K_p \left[ 2(v_{GSP} - V_{tp})v_{DSP} - v_{DSP}^2 \right]$$

Note that:

$$v_{GSP} = v_I - V_{DD} = -V_{DD} \quad \text{and} \quad v_{DSP} = v_O - V_{DD}$$

Therefore:

$$\begin{aligned} i_D &= K_p \left[ 2(v_{GSP} - V_{tp})v_{DSP} - v_{DSP}^2 \right] \\ &= K \left[ 2(V_t - V_{DD})(v_O - V_{DD}) - (v_O - V_{DD})^2 \right] \end{aligned}$$

Now, we actually KNOW that  $Q_N$  is in **cutoff**, so we likewise ENFORCE:

$$i_D = 0.0$$

**Equating** these two ENFORCED conditions, we find that:

$$i_D = 0.0 = K \left[ 2(V_t - V_{DD})(v_O - V_{DD}) - (v_O - V_{DD})^2 \right]$$

**Solving**, we find that the **output** voltage must be  $V_{DD}$ !


$$v_O = V_{DD}$$

Thus,  $v_{D_{SP}} = 0 > v_{G_{SP}} - V_{tp} = V_t - V_{DD}$ . ✓

$Q_P$  is indeed in the triode mode!

So, let's **summarize**. When  $v_I = 0.0$ :

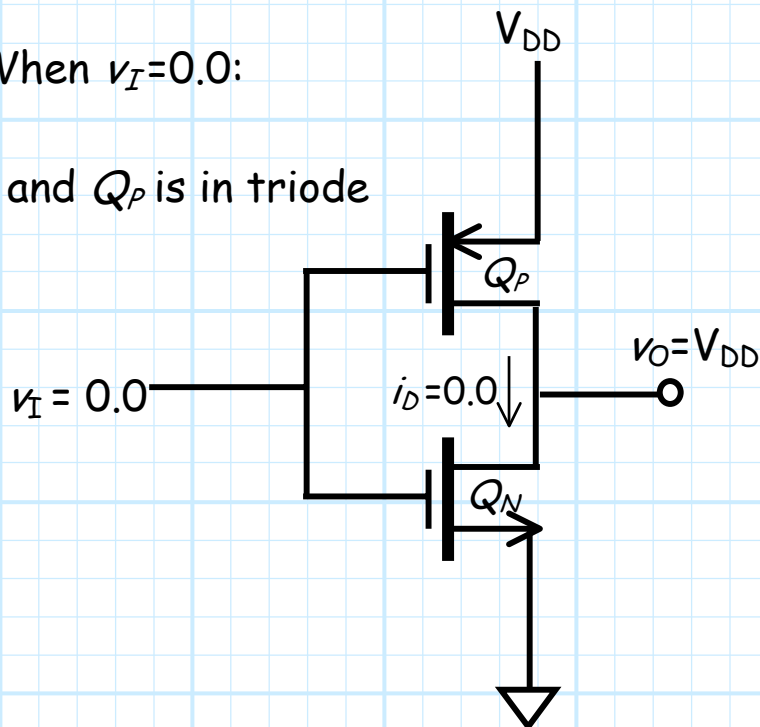1.  $Q_N$  is in cutoff and  $Q_P$  is in triode
2.  $i_D = 0.0$
3.  $v_O = V_{DD}$



So, the overall behavior of the CMOS inverter is displayed in this **table**:

$V_I$	$V_O$	$i_D$
0.0	$V_{DD}$	0.0
$V_{DD}$	0.0	0.0

Look at what this means! The CMOS inverter provides **lots of ideal** inverter parameters:

$$V_{OL} = 0.0 \text{ V} \quad (\text{ideal!})$$

$$V_{OH} = 5.0 \text{ V} \quad (\text{ideal!})$$

And since  $i_D$  is **zero** for either state, the **static power** dissipation is likewise **zero**:

$$P_D \text{ static} = 0.0 \quad (\text{ideal!})$$

This is one of the **most attractive** features of **CMOS** digital logic.