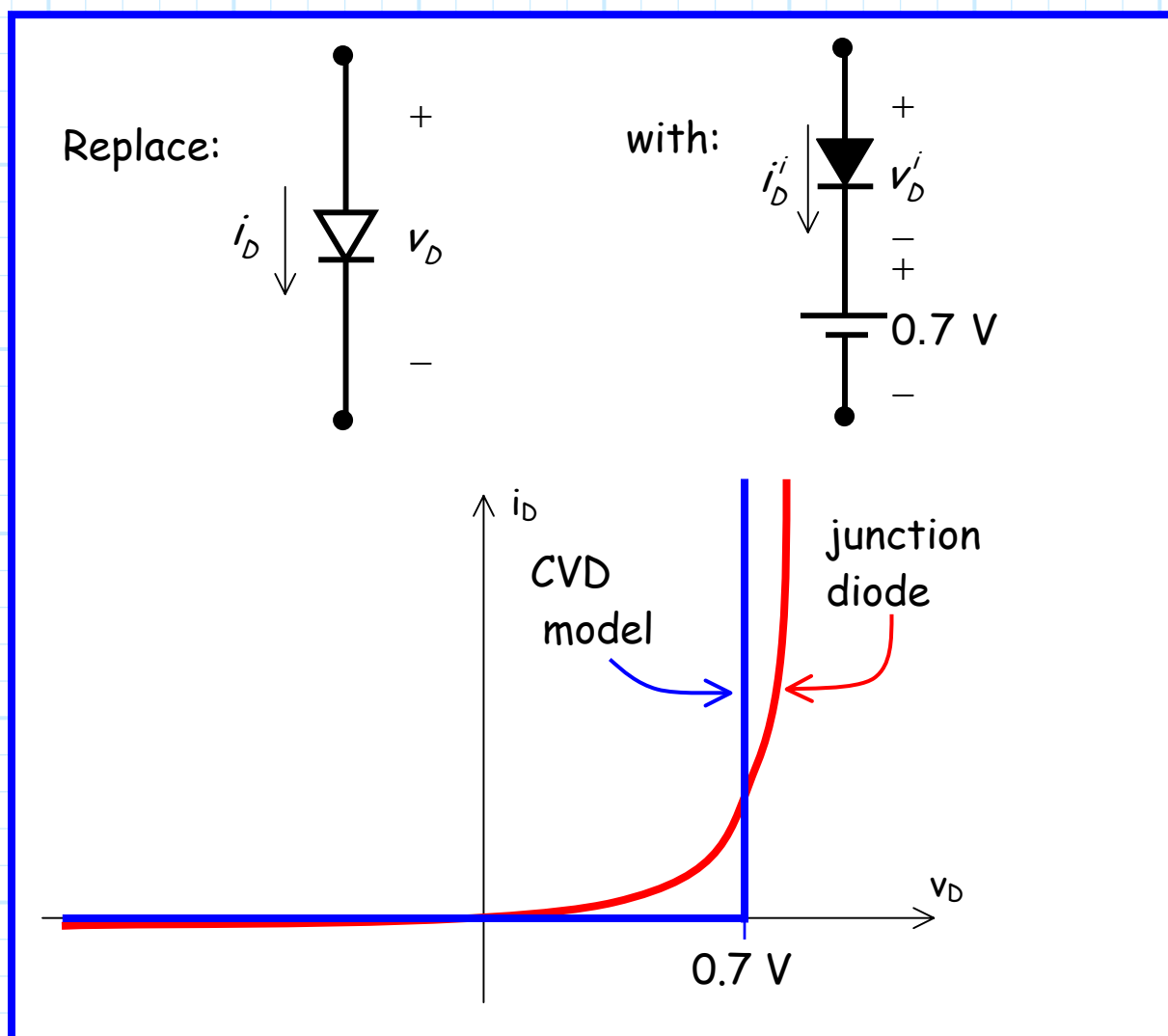


# The Constant Voltage Drop (CVD) Model

**Q:** We know if *significant positive current flows through a junction diode*, the diode voltage will be some value near 0.7 V. Yet, the ideal diode model provides an approximate answer of  $v_D = 0$  V. Isn't there a more *accurate* model?

**A:** Yes! Consider the **Constant Voltage Drop (CVD)** model.



In other words, replace the junction diode with **two** devices—an **ideal diode** in series with a **0.7 V voltage source**.

To find **approximate** current and voltage values of a junction diode circuit, follow these steps:

**Step 1** - Replace each junction diode with the **two** devices of the **CVD model**.


Note you now have an **IDEAL** diode circuit! There are **no junction diodes** in the circuit, and therefore **no junction diode** knowledge need be (or should be) used to analyze it.

**Step 2** - Analyze the **IDEAL** diode circuit. Determine  $i'_D$  and  $v'_D$  for each ideal diode.

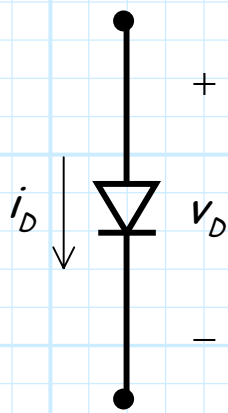**IMPORTANT NOTE!!! PLEASE READ THIS CAREFULLY:**


Make sure you analyze the resulting circuit **precisely** as we did in section 3.1. You **assume** the same **IDEAL** diode modes, you **enforce** the same **IDEAL** diode values, and you **check** the same **IDEAL** diode results, **precisely** as before. Once we replace the junction diodes with the CVD model, we have an **IDEAL** diode circuit—**no junction diodes** are involved!

**Step 3** - Determine the **approximate** values  $i_D$  and  $v_D$  of the **junction diode** from the **ideal** diode values  $i'_D$  and  $v'_D$ :



$$i_D \approx i_D^i$$

$$v_D \approx v_D^i + 0.7$$

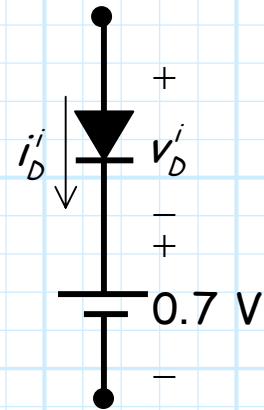

Note therefore, if the **IDEAL** diode (note here I said **IDEAL** diode) is **forward** biased ( $i_D^i > 0$ ), then the **approximation** of the **junction** diode current will likewise be positive ( $i_D > 0$ ), and the **approximation** of the **junction** diode voltage (unlike the **ideal** diode voltage of  $v_D^i = 0$ ) will be:

$$\begin{aligned} v_D &= v_D^i + 0.7 \\ &= 0.0 + 0.7 \\ &= 0.7 \text{ V} \end{aligned}$$

However, if the **IDEAL** diode is **reversed** biased ( $i_D^i = 0$ ), then the **approximation** of the **junction** diode current will likewise be zero ( $i_D = 0$ ), and the approximation of the junction diode voltage (unlike the **ideal** diode voltage of  $v_D^i < 0$ ) will be:

$$\begin{aligned} v_D &= v_D^i + 0.7 \\ &< 0.7 \text{ V} \end{aligned}$$

**NOTE:** Do **not** check the resulting **junction** diode approximations. You do not **assume** anything about the **junction** diode, so there is **nothing to check** regarding the junction diode answers.