

The Junction Diode Forward Bias Equation

In **forward bias**, we have learned that the diode current i_D can be related to the diode voltage v_D using the following **approximation**:

$$i_D = I_S \left(e^{v_D/nV_T} - 1 \right) \approx I_S e^{v_D/nV_T},$$

provided that $v_D \gg 25 \text{ mV}$.

We can **invert** this approximation to alternatively express v_D in terms of diode current i_D :

$$I_S e^{v_D/nV_T} = i_D$$

$$e^{v_D/nV_T} = \frac{i_D}{I_S}$$

$$\frac{v_D}{nV_T} = \ln \left(\frac{i_D}{I_S} \right)$$

$$v_D = nV_T \ln \left(\frac{i_D}{I_S} \right)$$

Now, say a voltage v_1 across some junction diode results in a current i_1 . Likewise, **different** voltage v_2 across this same diode a diode of course results in a **different** current i_2 . We can define the difference between these two voltages as $\Delta v = v_2 - v_1$, and then using the above equation can express this voltage difference as:

$$\begin{aligned}\Delta v &= v_2 - v_1 \\ &= nV_T \ln\left(\frac{i_2}{I_S}\right) - nV_T \ln\left(\frac{i_1}{I_S}\right) \\ &= nV_T \ln\left(\frac{i_2}{I_S} \frac{I_S}{i_1}\right) \\ \Delta v &= nV_T \ln\left(\frac{i_2}{i_1}\right)\end{aligned}$$

Yikes! Look at what this equation says:

- * The **difference** in the two voltages is dependent on the **ratio** of the two currents.
- * This voltage difference is **independent** of scale current I_S .

We can likewise **invert** the above equation and express the ratio of the two currents in terms of the difference of the two voltages:

$$nV_T \ln \left[\frac{i_2}{i_1} \right] = v_2 - v_1$$

$$\ln \left[\frac{i_2}{i_1} \right] = \frac{(v_2 - v_1)}{nV_T}$$

$$\frac{i_2}{i_1} = \exp \left[\frac{(v_2 - v_1)}{nV_T} \right]$$

Again, we find that this expression is **independent** of scale current I_s .



Q: *Stop wasting my time with these pointless derivations! Are these expressions even remotely useful !?!*

A: These expressions are often **very** useful! Frequently, instead of explicitly providing **device parameters** n and I_s , a junction diode is specified by stating n , and then a statement of the specific diode current resulting from a specific diode voltage.

For **example**, a junction diode might be specified as:

"A junction diode with $n = 1$ pulls 2mA of current at a voltage $v_D = 0.6$ V."

The above statement **completely specifies** the performance of this particular junction diode—we can now determine the current flowing through this diode for **any** other value of diode voltage v_D . Likewise, we can find the voltage across the diode for **any** other diode current value i_D .

For **example**, say we wish to find the current through the junction diode specified above when a potential difference of $v_D=0.7$ V is placed across it. We have **two** options for finding this current:

Option 1:

We know that $n=1$ and that $i_D=2$ mA when $v_D=0.6$ V. Thus, we can use this information to solve for **scale current** I_S :

$$I_S e^{\frac{v_D}{nV_T}} = i_D$$

$$I_S e^{\frac{0.6}{0.025}} = 2$$

$$I_S = 2 e^{\frac{-0.6}{0.025}}$$

$$I_S = 7.55 \times 10^{-11} \text{ mA}$$

Now, we use the forward-biased junction diode equation to determine the current through this device at the new voltage of $v_D=0.7$ V:

$$i_D = I_S e^{\frac{v_D}{nV_T}}$$

$$= (7.55 \times 10^{-11}) e^{\frac{0.7}{0.025}}$$

$$= 109.2 \text{ mA}$$

Option 2

Here, we directly determine the current at $v_D = 0.7$ using one of the expressions derived earlier in **this** handout! Using $i_I = 2$ mA, $v_1 = 0.6$, and $v_2 = 0.7$ V we can find current i_2 as:

$$\begin{aligned} \frac{i_2}{i_1} &= \exp\left[\frac{(v_2 - v_1)}{nV_T}\right] \\ i_2 &= i_1 \exp\left[\frac{(v_2 - v_1)}{nV_T}\right] \\ &= 2 \exp\left[\frac{(0.7 - 0.6)}{0.025}\right] \\ &= \mathbf{109.2 \text{ mA}} \end{aligned}$$

Option 2 (using the equations we derived in this handout) is obviously **quicker** and **easier** (note in option 2 we did **not** have to deal with **annoying numbers** like 7.55×10^{-11} !).

Finally, we should also note that junction diodes are often specified **simply** as "a 2mA diode" or "a 10 mA diode" or "a 100 mA diode". These statement **implicitly** provide the diode current at the **standard** diode test voltage of $v_D = 0.7$ V.

Q: *But what about the value of junction diode idealty factor n ?*



A: If no value of n is provided (and there is not sufficient information given to determine it), we typically just **assume** that $n = 1$.

For **example**, consider the following problem:

"Determine the voltage across a 100 mA junction diode when there is 2 mA of current flowing through it."

A "100 mA junction diode" simply means a junction diode that will have a current of 100 mA flowing through it ($i_D = 100$ mA) if the voltage across it is $v_D = 0.7$ V. We will **assume** that $n = 1$, since no other information about that parameter was given.

Thus, using $v_1 = 0.7$, $i_1 = 100$ mA, and $i_2 = 2$ mA, we can determine the value of v_2 :

$$v_2 - v_1 = nV_T \ln\left(\frac{i_2}{i_1}\right)$$

$$v_2 - 0.7 = (0.025) \ln\left(\frac{2}{100}\right)$$

$$\begin{aligned} v_2 &= 0.7 - 0.10 \\ &= 0.60 \text{ V} \end{aligned}$$

EXCELENT!

