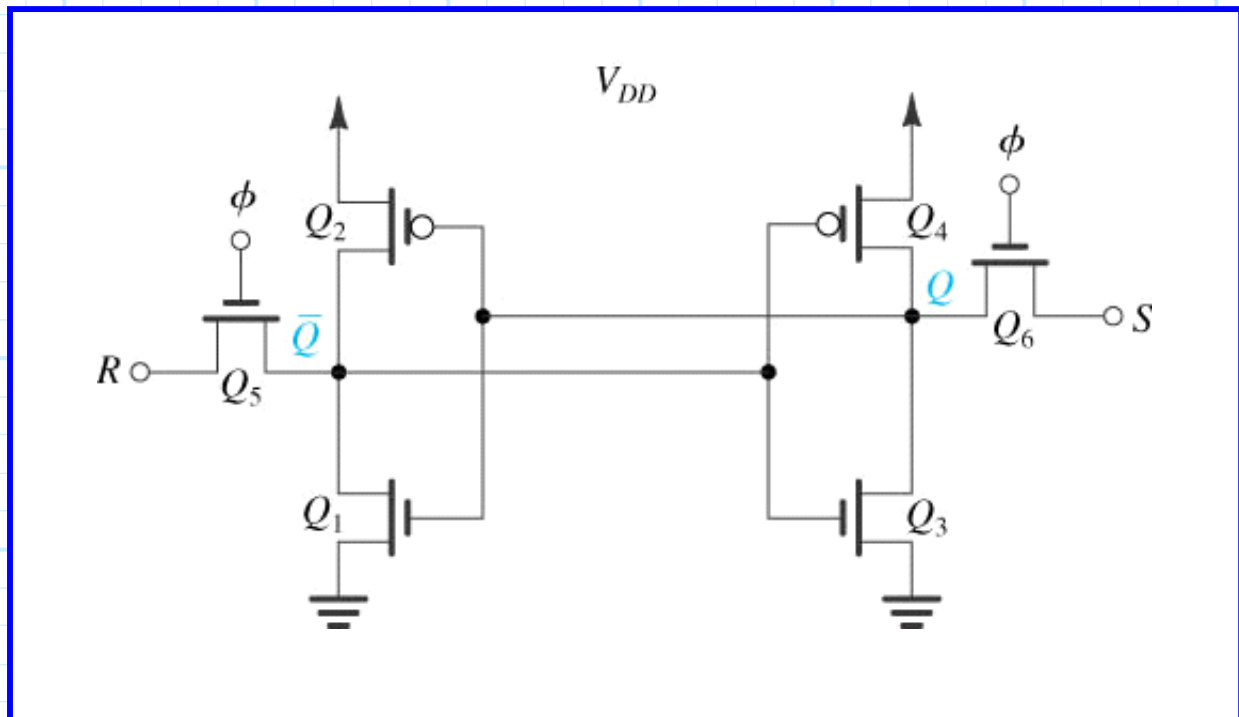


# The S/R Flip-Flop

A **Set/Reset Flip-Flop** can be constructed by attaching **external inputs** to a **CMOS latch**:



Essentially, when **S (Set)** is high, the latch is set such that **Q is high**. Likewise, when **R (Reset)** is high, the latch is set such that **Q is low**.

Of course, if **neither S nor R** are high, then the state of the latch remains **unchanged**. We of course **never** wish to make **both R and S** high at the same time (confusion and ambiguity will result!).

The **truth table** for this circuit is thus that of a **Set/Reset Flip Flop**:

$R$	$S$	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	Not used

The value  $\phi$  in the circuit above is an **enable line**, this must likewise be high if the latch is to change state.

The S/R Flip-Flop is thus a great **memory device**, storing the value of a **single bit** (1 or 0). Likewise, we can **write** to this storage device, setting its value to either 1 or 0 by enabling the S or R inputs, respectively.