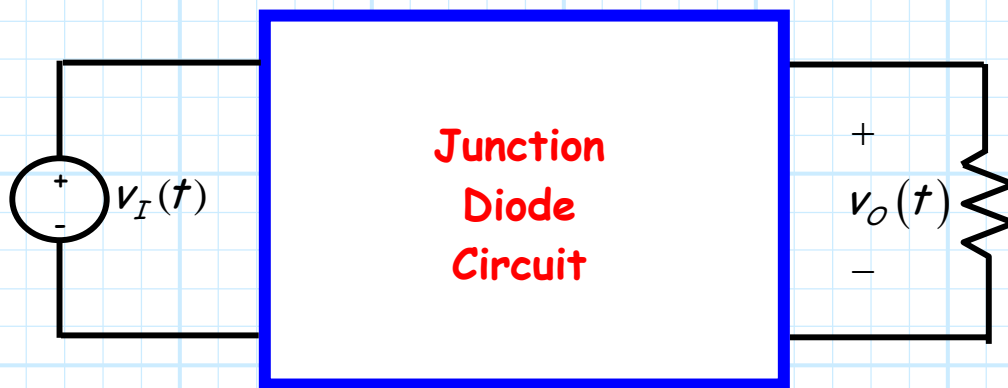


3.5 Rectifier Circuits

A. Junction Diode 2-Port Networks



HO: The Transfer Function of Diode Circuits

Q:

A: HO: Steps for finding a Junction Diode Circuit Transfer Function

Example: Diode Circuit Transfer Function

B. Diode Rectifiers

HO: Signal Rectification



Q:

A: { HO: The Full-Wave Rectifier
HO: The Bridge Rectifier

HO: Peak Inverse Voltage

The Transfer Function of Diode Circuits

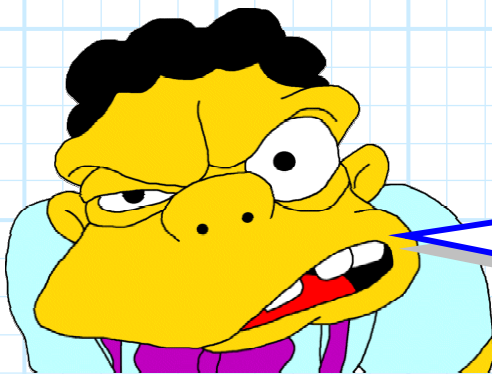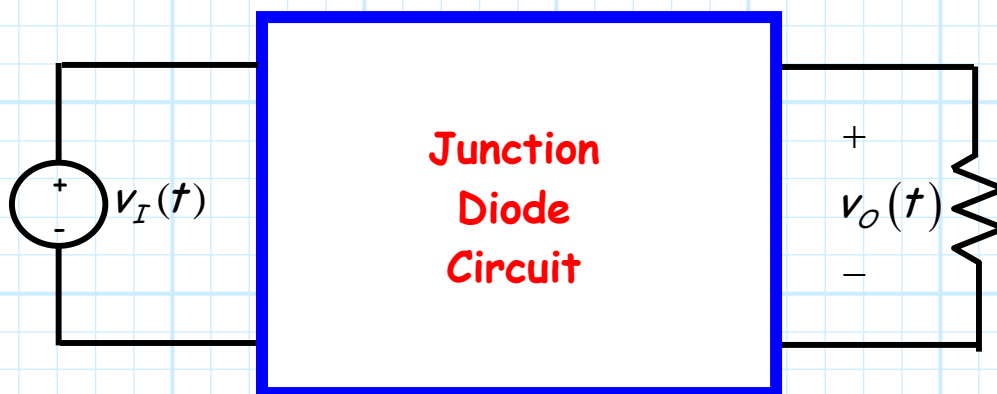For many junction diode circuits, we find that one of the voltage sources is in fact **unknown**! This unknown voltage is typically some **input** signal of the form $v_I(t)$, which results in an output voltage $v_O(t)$.



Q: *How the heck do you expect us to determine $v_O(t)$ if we have **no idea** what $v_I(t)$ is??*

A: We of course cannot determine an **explicit** value or expression for $v_O(t)$, since it **depends** on the input $v_I(t)$. Instead, we will attempt to explicitly determine this **dependence** of $v_O(t)$ on $v_I(t)$!

In other words, we seek to find an expression for v_O in **terms** of v_I . Mathematically speaking, our goal is to determine the **function**:


$$v_O = f(v_I)$$

We refer to this as the **circuit transfer function**.

Note that we can **plot** a circuit transfer function on a 2-dimensional plane, just as if the function related values x and y (e.g. $y = f(x)$). For **example**, say our circuit transfer function is:

$$\begin{aligned} v_O &= f(v_I) \\ &= 3v_I + 2 \end{aligned}$$

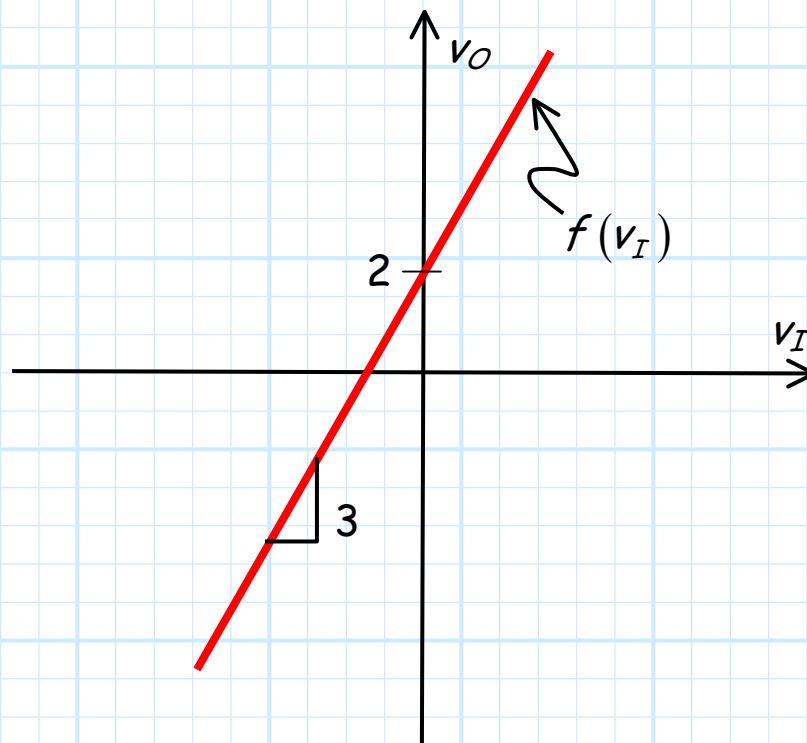Note this is simply the **equation of a line** (e.g., $y = 3x + 2$), with slope $m=3$ and intercept $b=2$.



Q: A "function" eh? Isn't a "function" just your annoyingly pretentious way of saying we need to find some mathematic equation relating v_O and v_I ?





A: Actually **no!** Although a function is a mathematical equation, there are in fact **scads** of equations relating v_O and v_I that are **not** functions!

→ The set of all possible functions $y = f(x)$ are a **subset** of the set of all possible equations relating y and x .



A **function** $v_O = f(v_I)$ is a mathematical expression such that for **any** value of v_I (i.e., $-\infty < v_I < \infty$), there is **one**, but **only one**, value v_O .

Note this definition of a function is consistent with our **physical** understanding of circuits—we can place **any** voltage on the input that we want (i.e., $-\infty < v_I < \infty$), and the result will be **one** specific voltage value v_O on the output.

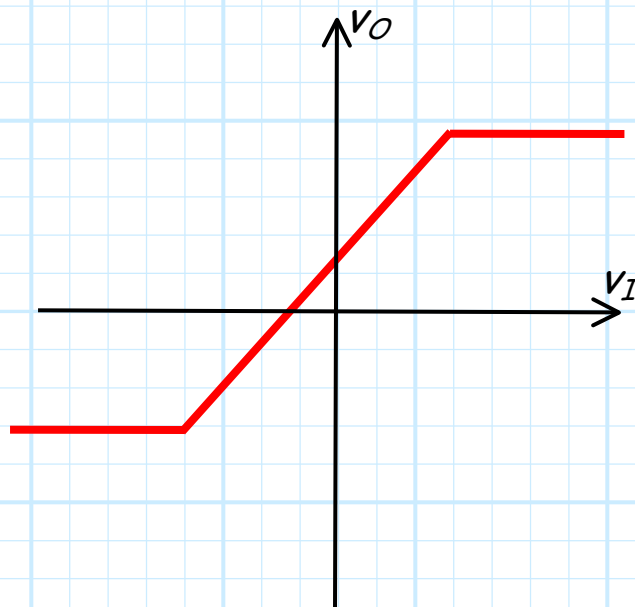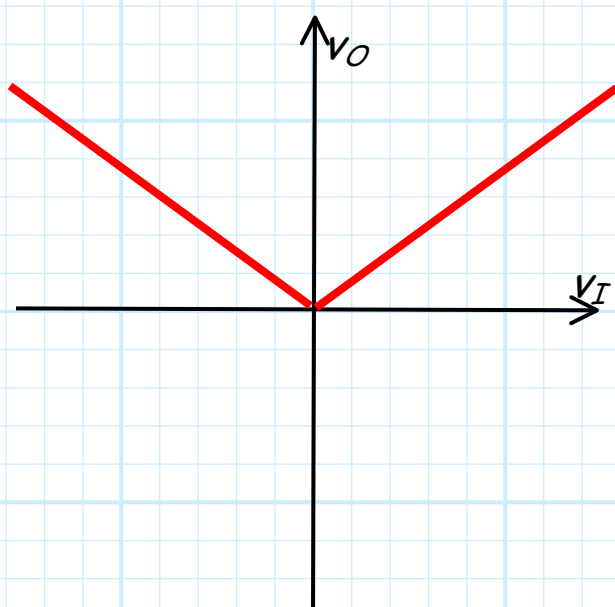
Therefore, examples of **valid** circuit transfer **functions** include:



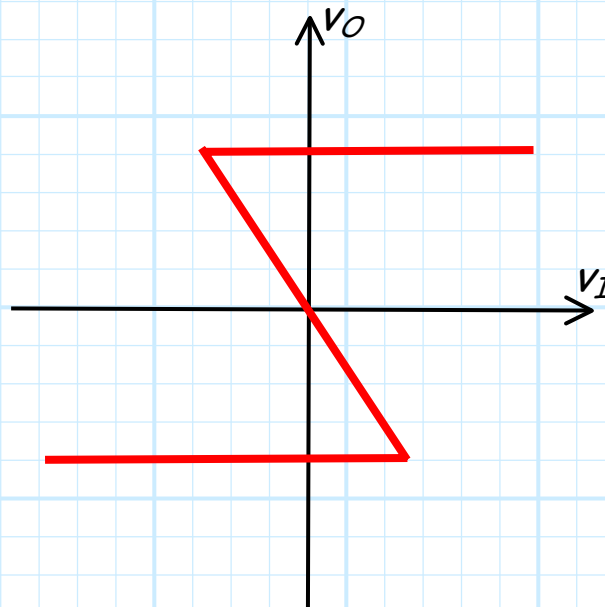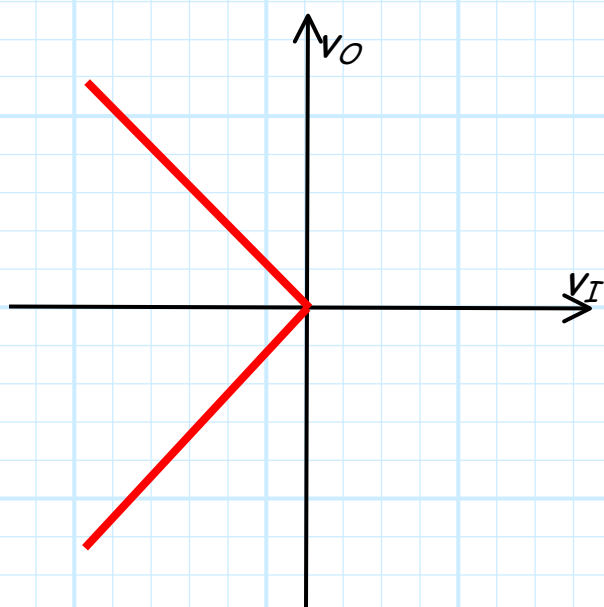
Conversely, the transfer "functions" **below** are **invalid**—they **cannot** represent the behavior of circuits, since they are **not** functions!



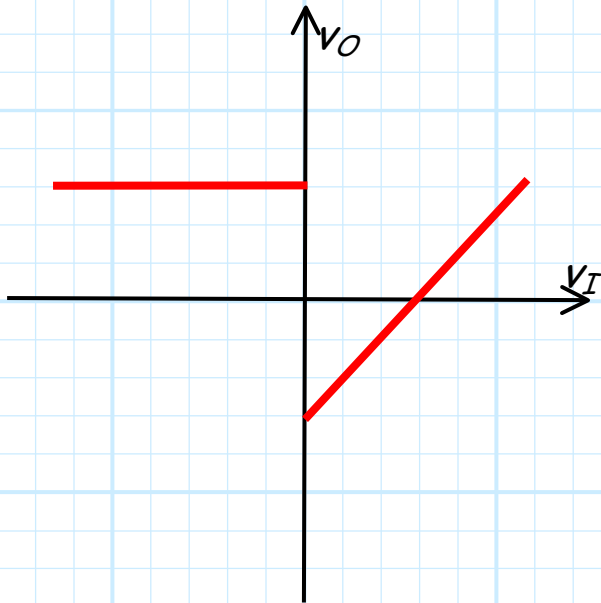Moreover, we find that **circuit** transfer functions must be **continuous**. That is, v_O **cannot** "instantaneously change" from one value to another as we increase (or decrease) the value v_I .



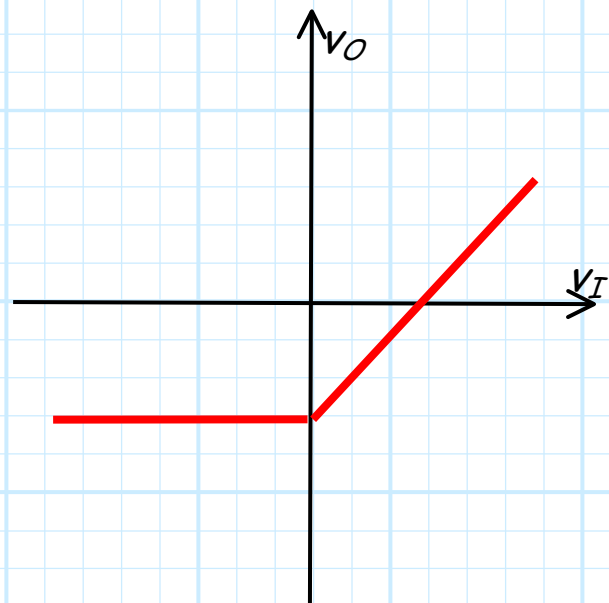**A Discontinuous
Function**
(*Invalid circuit
transfer function*)



**A Continuous
Function**
(*Valid circuit
transfer function*)



*Remember, the transfer function of **every** junction diode circuit must be a **continuous function**. If it is **not**, you've done something **wrong**!*

Steps for Finding a Junction Diode Circuit Transfer Function

Determining the **transfer function** of a junction diode circuit is in many ways **very similar** to the analysis steps we followed when analyzing previous junction diode circuits (i.e., circuits where all sources were **explicitly known**).

However, there are also some **important differences** that we must understand completely if we wish to successfully determine the **correct transfer function!**

Step 1: *Replace all junction diodes with an appropriate junction diode model.*

Just like before! We will now have an **IDEAL** diode circuit.

Step 2: *ASSUME some mode for all ideal diodes.*

Just like before! An **IDEAL** diode can be either forward or reverse biased.

Step 3: ENFORCE the bias assumption.

Just like before! ENFORCE the bias assumption by replacing the ideal diode with short circuit or open circuit.

Step 4: ANALYZE the remaining circuit.

Sort of, kind of, like before!

1. If we assumed an IDEAL diode was forward biased, we must determine i_D^i --**just** like before! However, **instead** of finding the numeric value of i_D^i , we determine i_D^i as a **function** of the unknown source (e.g., $i_D^i = f(v_I)$).

2. Or, if we assumed an IDEAL diode was reversed biased, we must determine v_D^i --**just** like before! However, **instead** of finding the numeric value of v_D^i , we determine v_D^i as a **function** of the unknown source (e.g., $v_D^i = f(v_I)$).

3. Finally, we must determine all the **other** voltages and/or currents we are interested in (e.g., v_O)--**just** like before! However, **instead** of finding its numeric value, we determine it as a **function** of the unknown source (e.g., $v_O = f(v_I)$).

Step 5: Determine *WHEN* the assumption is valid.

Q: OK, we get the picture. Now we have to **CHECK** to see if our **IDEAL** diode assumption was correct, right?



A: Actually, **no!** This step is **very different** from what we did before!

We **cannot** determine **IF** $i_D^i > 0$ (forward bias assumption), or **IF** $v_D^i < 0$ (reverse bias assumption), since we **cannot** say for certain what the value of i_D^i or v_D^i is!

Recall that i_D^i and v_D^i are **functions** of the unknown voltage source (e.g., $i_D^i = f(v_I)$ and $v_D^i = f(v_I)$). Thus, the values of i_D^i or v_D^i are **dependent** on the unknown source (v_I , say). For **some** values of v_I , we will find that $i_D^i > 0$ or $v_D^i < 0$, and so our assumption (and thus our solution for $v_O = f(v_I)$) will be **correct**

However, for **other** values of v_I , we will find that $i_D^i < 0$ or $v_D^i > 0$, and so our assumption (and thus our solution for $v_O = f(v_I)$) will be **incorrect!**



Q: Yikes! What do we do? How can we determine the circuit transfer function if we can't determine **IF** our ideal diode assumption is correct??

A: Instead of determining **IF** our assumption is correct, we must determine **WHEN** our assumption is correct!

In other words, we must determine for **what values** of v_I is $i_D^i > 0$ (forward bias), or for **what values** of v_I is $v_D^i < 0$ (reverse bias).

We can do this since we earlier (in step 4) determined the function $i_D^i = f(v_I)$ or the function $v_D^i = f(v_I)$.

Perhaps this step is best explained by an **example**. Let's say we assumed that our ideal diode was **forward biased** and, say we determined (in step 4) that v_O is related to v_I as:

$$\begin{aligned}v_O &= f(v_I) \\ &= 2v_I - 3\end{aligned}$$

Likewise, say that we determined (in step 4) that our ideal diode current is related to v_I as:

$$\begin{aligned}i_D^i &= f(v_I) \\ &> \frac{v_I - 5}{4}\end{aligned}$$

Thus, in order for our forward bias assumption to be **correct**, the function $i_D^i = f(v_I)$ must be **greater than zero**:

$$i_D^i > 0$$

$$f(v_I) > 0$$

$$\frac{v_I - 5}{4} > 0$$

We can now "solve" this **inequality** for v_I :

$$\frac{v_I - 5}{4} > 0$$

$$v_I - 5 > 0$$

$$v_I > 5$$

Q: What does *this* mean? Does it mean that v_I is some value **greater than 5.0V**??



A: **NO!** Recall that v_I can be **any** value. What the inequality above means is that $i_D^i > 0$ (i.e., the ideal diode is forward biased) **WHEN** $v_D^i > 5.0$.

Thus, we know $v_O = 2v_I - 3$ is valid **WHEN** the ideal diode is forward biased, and the ideal diode is forward biased **WHEN** (for this example) $v_D^i > 5.0$. As a result, we can mathematically state that:

$$v_O = 2v_I - 3 \quad \text{when} \quad v_I > 5.0 \text{ V}$$

Conversely, this means that if $v_I < 5.0$ V, the **ideal** diode will be **reverse biased**—our forward bias assumption would **not** be valid, and thus our expression $v_O = 2v_I - 3$ is **not** correct ($v_O \neq 2v_I - 3$ for $v_I < 5.0$ V)!

Q: So how do we determine v_O for values of $v_I < 5.0$ V?



A: Time to move to the **last** step!

Step 6: *Change assumption and repeat steps 2 through 5!*

For our **example**, we would change our bias assumption and now **ASSUME** reverse bias. We then **ENFORCE** $i_D' = 0$, and then **ANALYZE** the circuit to find both $v_D' = f(v_I)$ and a **new** expression $v_O = f(v_I)$ (it will **no longer** be $v_O = 2v_I - 3$!).


We then determine **WHEN** our reverse bias assumption is valid, by solving the **inequality** $v_D' = f(v_I) > 0$ for v_I . For the example used here, we would find that the **IDEAL** diode is reverse biased **WHEN** $v_I < 5.0$ V.

For junction diode circuits with **multiple** diodes, we may have to repeat this entire process **multiple** times, until **all possible** bias conditions are analyzed.

If we have done our analysis **properly**, the result will be a valid **continuous function**! That is, we will have an expression (but only **one** expression) relating v_O to **all** possible values of v_I .


This transfer function will typically be **piecewise linear**. An **example** of a piece-wise linear transfer function is:
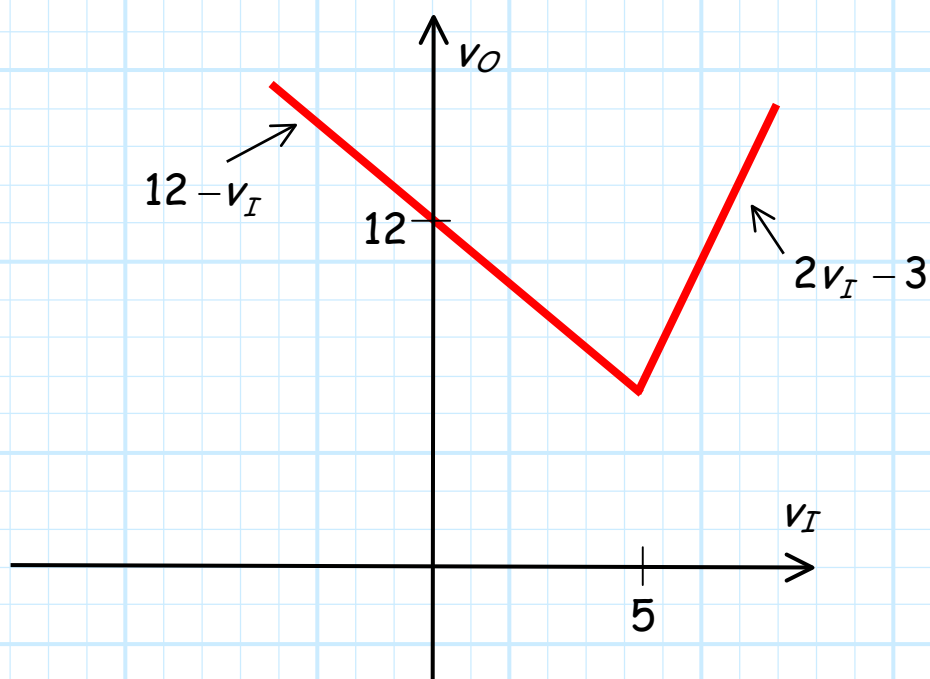
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 5.0 \\ 12 - v_I & \text{for } v_I < 5.0 \end{cases}$$




Just to make **sure** that we understand what a function is, note that the following expression is **not** a function:
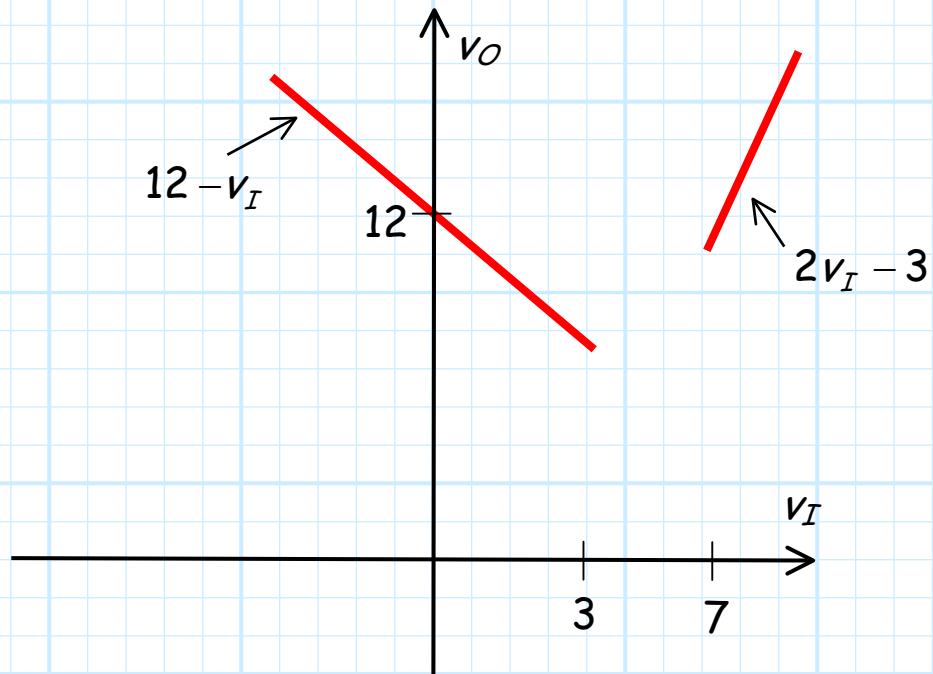
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 7.0 \\ 12 - v_I & \text{for } v_I < 3.0 \end{cases}$$




Nor is this expression a function:
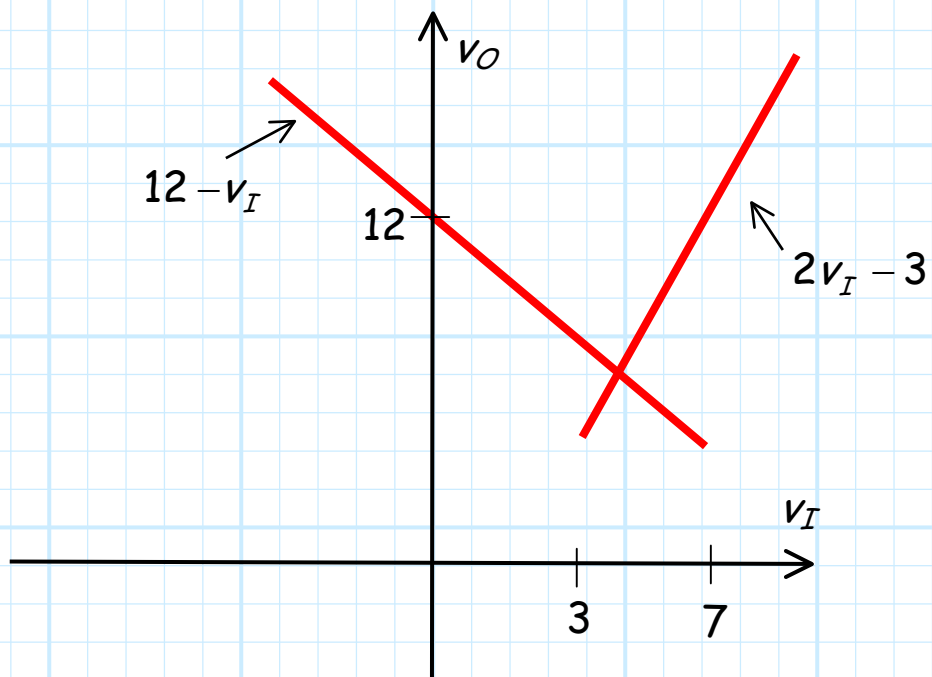
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 3.0 \\ 12 - v_I & \text{for } v_I < 7.0 \end{cases}$$



Finally, note that the following expression is a function, but it is **not continuous**:

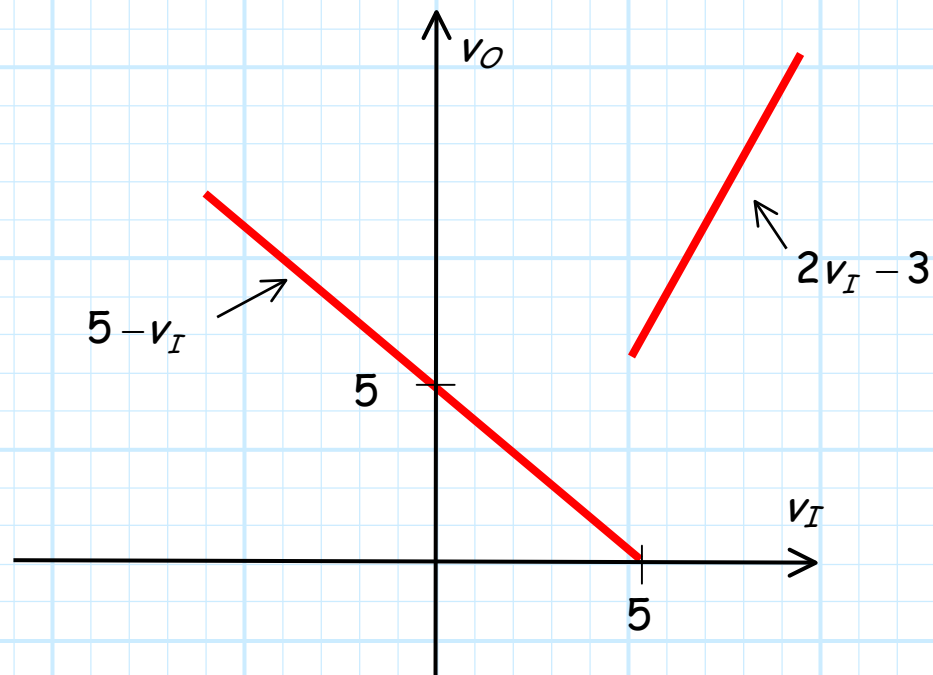
$$v_O = \begin{cases} 2v_I - 3 & \text{for } v_I > 5.0 \\ 5 - v_I & \text{for } v_I < 5.0 \end{cases}$$



Make sure that the piece-wise transfer function that you determine is in fact a function, and is continuous!

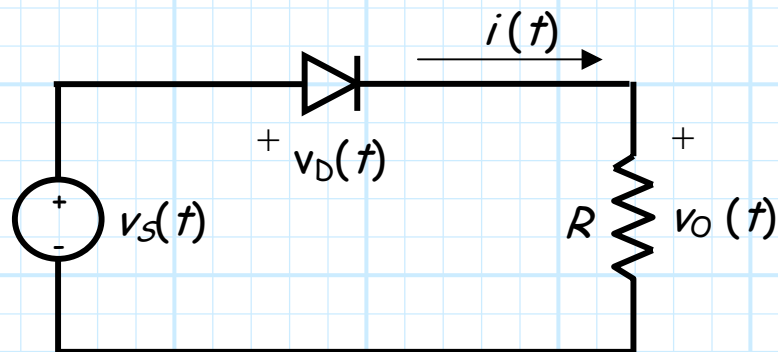
Example: Diode Circuit Transfer Function

Consider the following circuit, called a **half-wave rectifier**:



Let's use the **CVD model** to determine the output voltage v_O in terms of the input voltage v_s . In other words, let's determine the diode circuit **transfer function** $v_O = f(v_s)$!

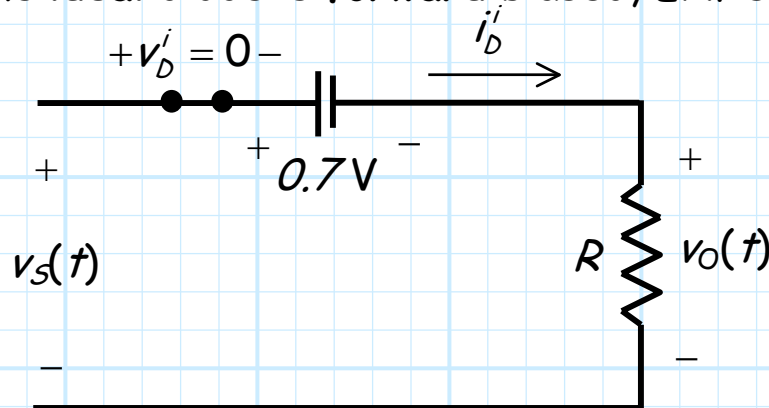ASSUME the **ideal** diode is **forward** biased, **ENFORCE** $v_D^i = 0$.



From KVL, we find that:


$$v_O(t) = v_s(t) - 0.7$$

This result is of course true if our original assumption is correct— it is valid if the ideal diode is forward biased (i.e., $i_D^i > 0$)!

From Ohm's Law, we find that:

$$i_D^i = \frac{v_O}{R} = \frac{v_S - 0.7}{R}$$

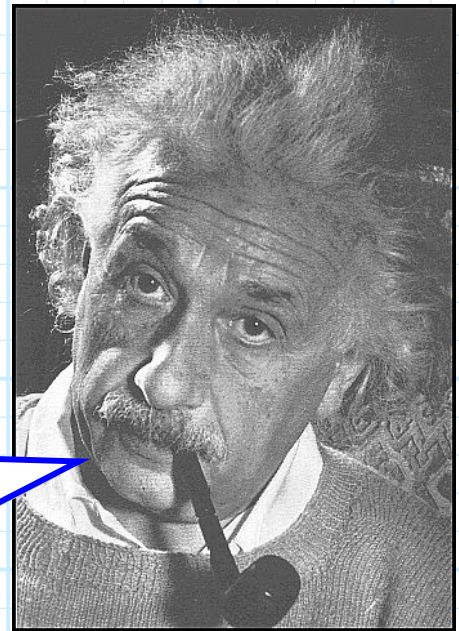Q: *I'm so confused! Is this current **greater** than zero or **less** than zero? Is our assumption correct? How can we tell?*



A: The ideal diode current is **dependent** on the value of source voltage $v_S(t)$. As such, we **cannot** determine if our assumption is correct, we **instead** must find out **when** our assumption is correct!

In other words, we know that the forward bias assumption is correct **when** $i_D^i > 0$. We can rearrange our diode current expression to determine for what values of source voltage $v_S(t)$ this is true:

$$i_D^i > 0$$


$$\frac{v_S(t) - 0.7}{R} > 0$$

$$v_S(t) - 0.7 > 0$$

$$v_S(t) > 0.7$$


So, we have found that **when** the source voltage $v_s(t)$ is greater than 0.7 V, the output voltage $v_o(t)$ is:

$$v_o(t) = v_s(t) - 0.7$$

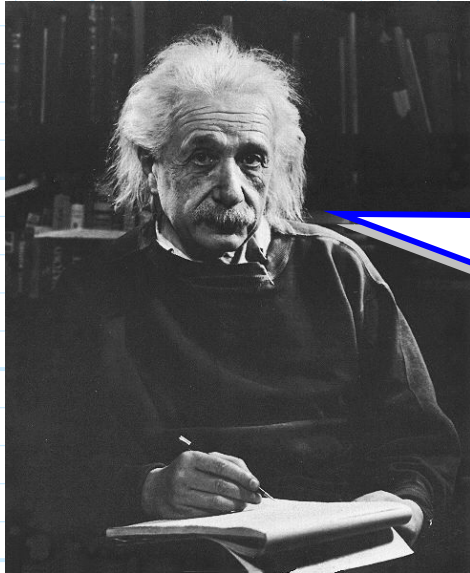

Q: *OK, I've got this result written down. However, I still don't know what the output voltage $v_o(t)$ is **when** the source voltage $v_s(t)$ is **less** than 0.7V!?!*

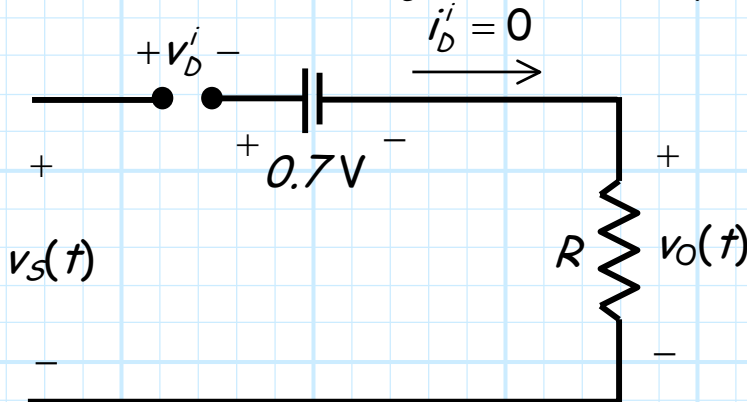
Now we **change** our assumption and **ASSUME** the ideal diode in the CVD model is **reverse** biased, an assumption **ENFORCED** with the condition that $i_D^i = 0$ (i.e., an open circuit).



Q: *Fascinating! The output voltage is **zero** when the ideal diode is reverse biased. But, precisely when **is** the ideal diode reverse biased? For **what** values of v_s does this occur?*

From Ohm's Law, we find that the output voltage is:
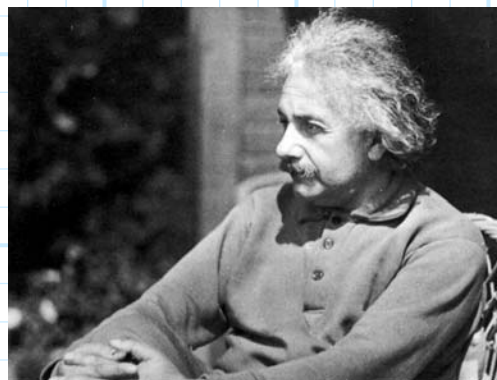
$$\begin{aligned} v_o &= R i_D^i \\ &= R(0) \\ &= 0 \text{ V !!!} \end{aligned}$$



A: To answer these questions, we must determine the **ideal** diode voltage in terms of v_S (i.e., $v_D^i = f(v_S)$):

From KVL:
$$v_S - v_D^i - 0.7 = v_O$$

Therefore:

$$\begin{aligned} v_D^i &= v_S - 0.7 - v_O \\ &= v_S - 0.7 - 0.0 \\ &= v_S - 0.7 \end{aligned}$$

Thus, the ideal diode is in reverse bias **when**:

$$\begin{aligned} v_D^i &< 0 \\ v_S - 0.7 &< 0 \end{aligned}$$

Solving for v_S , we find:

$$\begin{aligned} v_S - 0.7 &< 0 \\ v_S &< 0.7 \text{ V} \end{aligned}$$

In other words, we have determined that the **ideal** diode will be reverse biased **when** $v_S < 0.7 \text{ V}$, and that the output voltage will be $v_O = 0$.



Q: So, we have found that:

$$v_O = v_S - 0.7 \quad \text{when } v_S > 0.7 \text{ V}$$


and,

$$v_O = 0.0 \quad \text{when } v_S < 0.7 \text{ V}$$

It appears we have a valid, continuous, function!

A: That's right! The transfer function for this circuit is therefore:

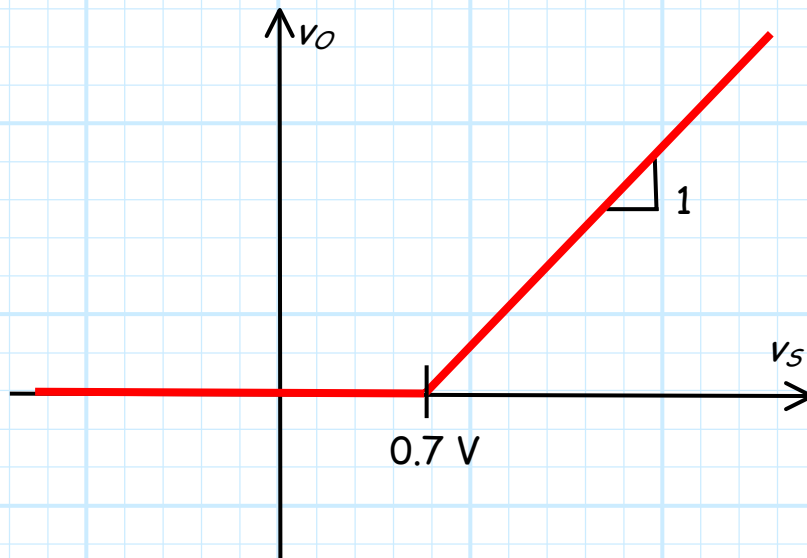
$$v_o = \begin{cases} v_s - 0.7 & \text{for } v_s > 0.7 \\ 0 & \text{for } v_s < 0.7 \end{cases}$$



*Although the circuit in this example may **seem** trivial, it is actually **very important!***

*It is called a **half-wave rectifier**, and provides signal **rectification**.*

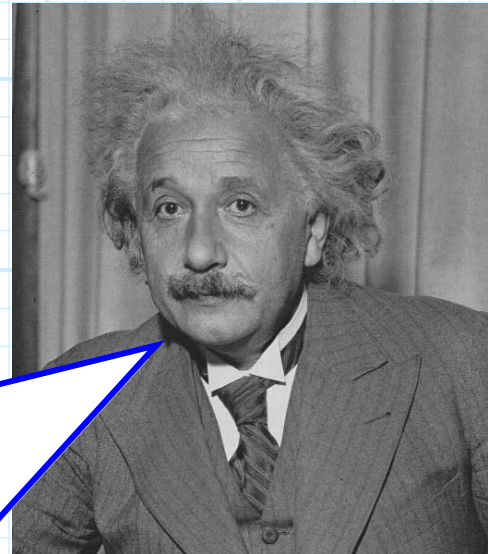*Rectifiers are an **essential part** of every **AC to DC power supply!***




Signal Rectification


An important application of junction diodes is **signal rectification**.

There are **two** types of signal rectifiers, **half-wave** and **full-wave**.

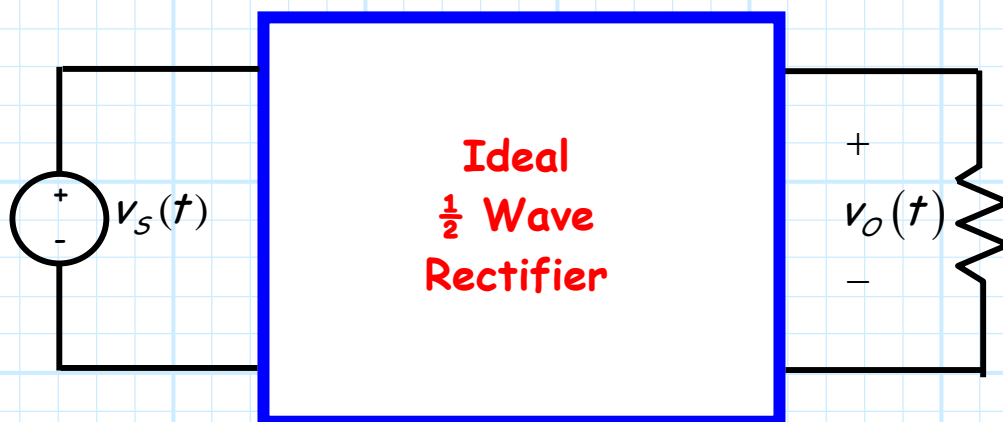
Let's first consider the **ideal half-wave rectifier**. It is a circuit with the transfer function $v_o = f(v_s)$:


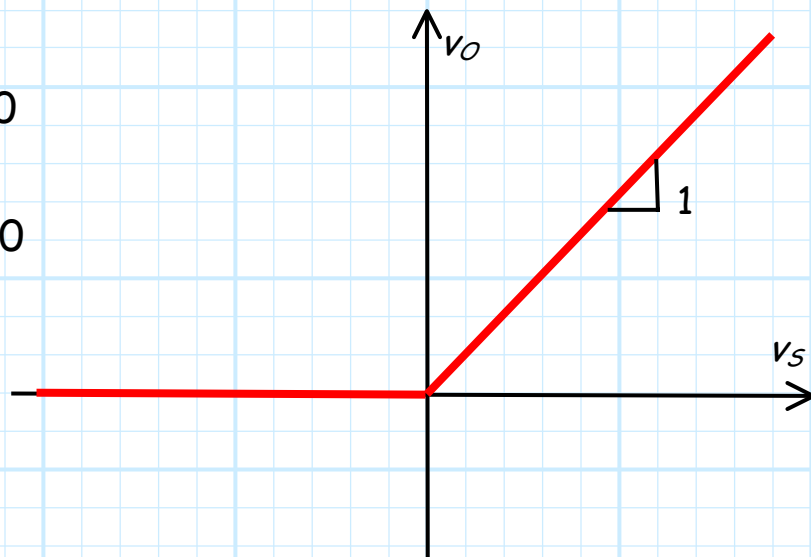
$$v_o = \begin{cases} 0 & \text{for } v_s < 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$




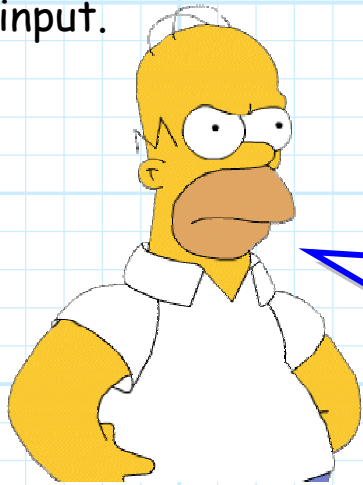Pretty simple! **When** the input is negative, the output is **zero**, whereas **when** the input is positive, the output is the **same** as the input.




Q: *Pretty simple and pretty stupid I'd say! This might be your most **pointless** circuit yet. How in the world is **this** circuit useful??*

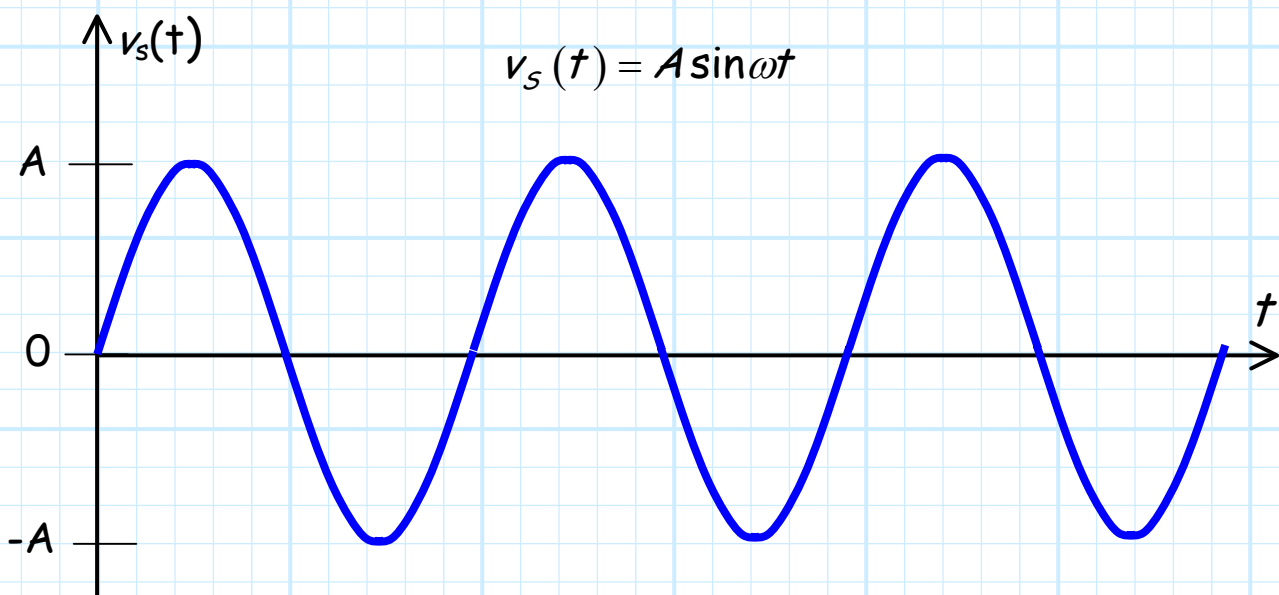A: To see **why** a half-wave rectifier is useful, consider the **typical** case where the input source voltage is a **sinusoidal** signal with **frequency** ω and peak **magnitude** A :




Think about what the **output** of the half-wave rectifier would be! Remember the rule: when $v_s(t)$ is **negative**, the output is **zero**, when $v_s(t)$ is **positive**, the output is **equal** to the input.

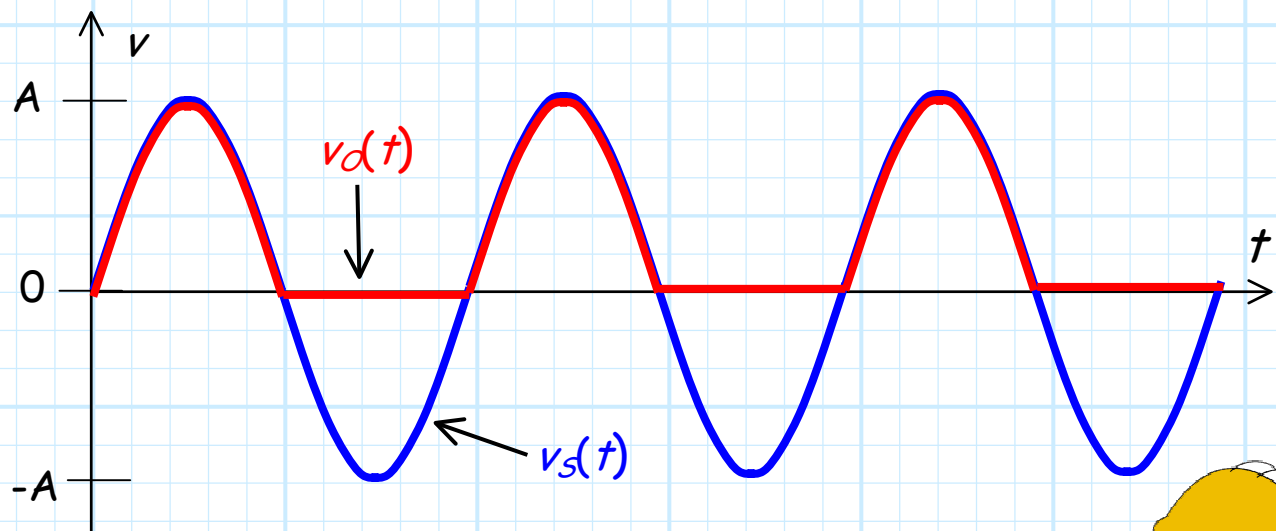The **output** of the half-wave rectifier for **this** example is therefore:



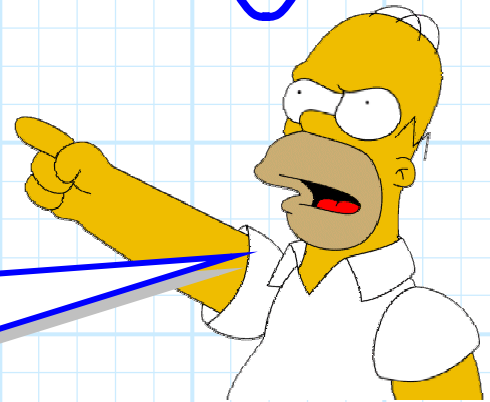Q: *That's maybe the lamest result I've ever seen. What good is **half** a sine wave? Why do we even bother?*



A: Although it may appear that our rectifier had **little** useful effect on the input signal $v_s(t)$, in fact the difference between input $v_s(t)$ and output $v_d(t)$ is both **important** and **profound**.

To see how, consider first the **DC component** (i.e. the time-averaged value) of the **input** sine wave:



$$\begin{aligned} V_S &= \frac{1}{T} \int_0^T v_s(t) dt \\ &= \frac{1}{T} \int_0^T A \sin \omega t dt = 0 \end{aligned}$$

Thus, (as you probably already knew) the **DC component** of a sine wave is **zero**—a sine wave is an **AC signal**!

Now, contrast this with the **output** $v_o(t)$ of our half-wave rectifier. The **DC component** of the **output** is:

$$\begin{aligned} V_o &= \frac{1}{T} \int_0^T v_o(t) dt \\ &= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt + \frac{1}{T} \int_{T/2}^T 0 dt = \frac{A}{\pi} \end{aligned}$$

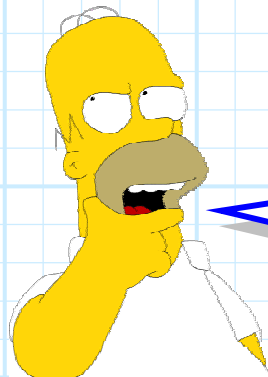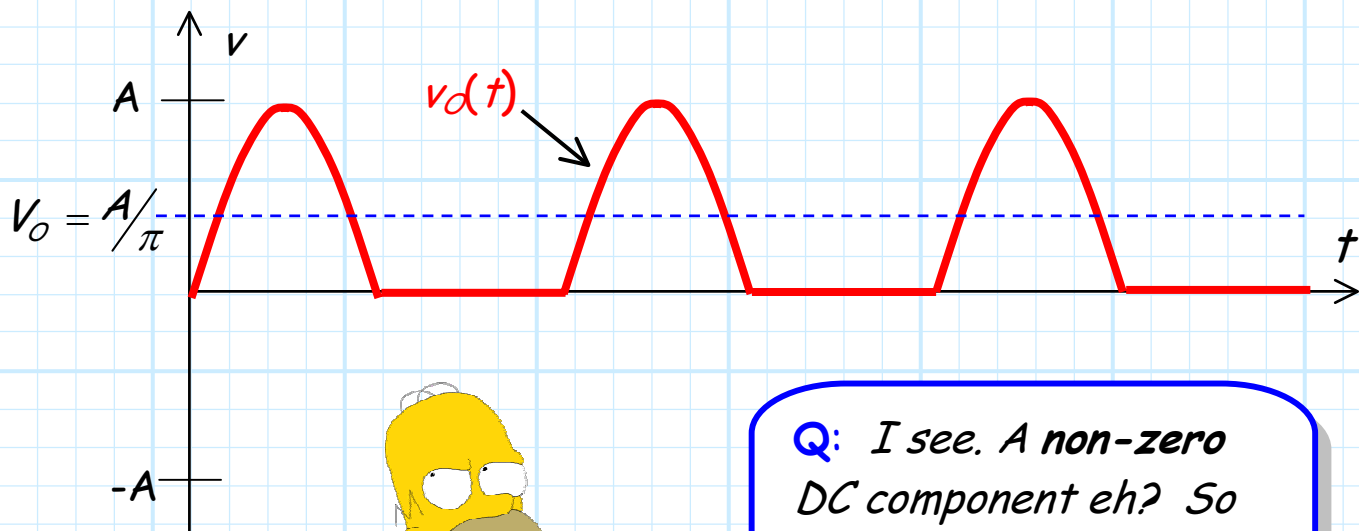
Unlike the input, the **output** has a **non-zero** (positive) **DC component** ($V_o = A/\pi$)!



Q: *I see. A non-zero DC component eh? So refresh my memory, why is that important?*

A: Recall that the **power distribution system** we use is an **AC** system. The source voltage $v_s(t)$ that we get when we plug our "**power cord**" into the wall socket is a 60 Hz **sinewave**—a source with a **zero DC component**!

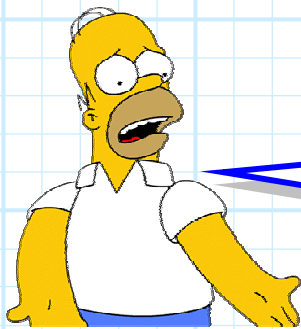
The **problem** with this is that most **electronic devices** and systems, such as TVs, stereos, computers, etc., require a **DC voltage(s)** to operate!




Q: *But, how can we create a DC supply voltage if our power source $v_s(t)$ has no DC component??*

A: That's **why** the half-wave rectifier is so **important**! It takes an AC source with **no DC component** and creates a signal with **both** a DC and AC component.

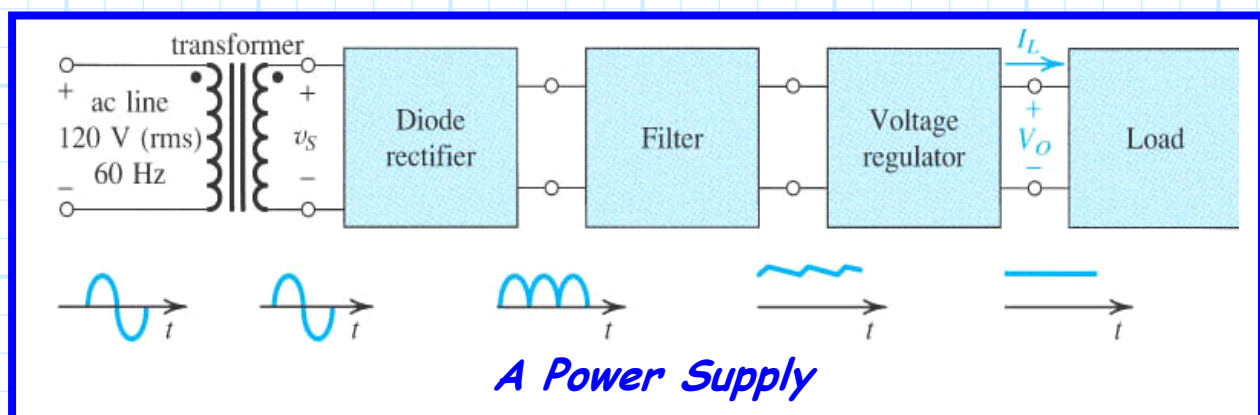
We can then pass the output of a half-wave rectifier through a **low-pass filter**, which **suppresses** the AC component but lets the DC value ($V_o = A/\pi$) pass through. We then **regulate** this output and form a **useful DC voltage source**—one suitable for powering our electronic systems!



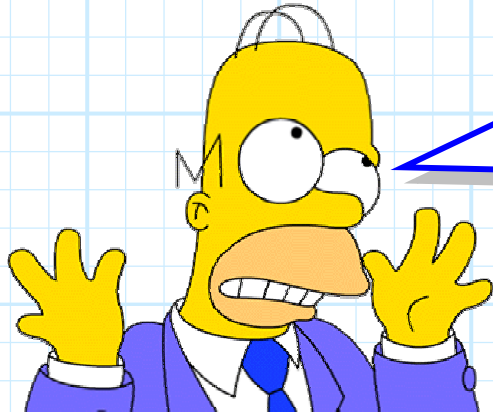


Q: *OK, now I see why the ideal half-wave rectifier might be useful. But, is there any way to actually build this magical device?*


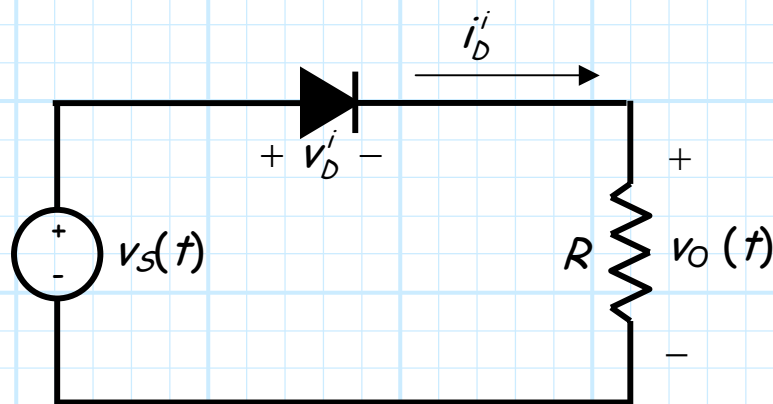
A: An ideal half-wave rectifier can be "built" if we use an ideal diode.



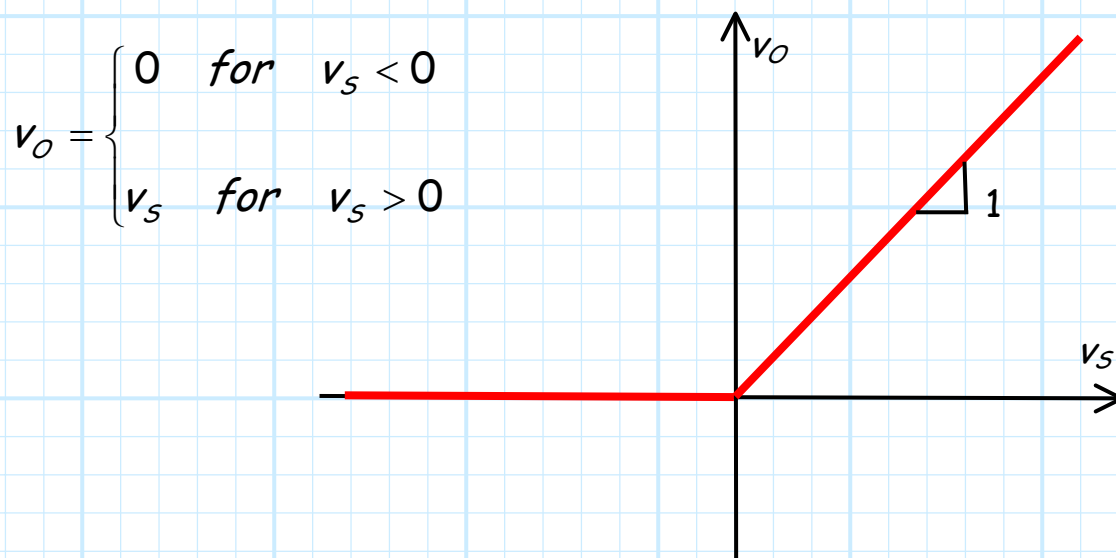If we follow the transfer function **analysis steps** we studied earlier, then we will find that this circuit is indeed an **ideal half-wave rectifier!**



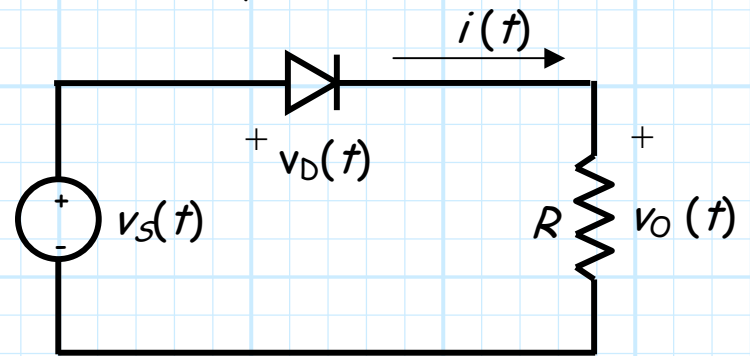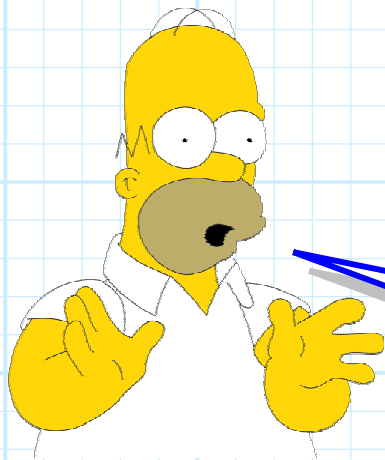
Of course, since **ideal** diodes do **not** exist, we must use a **junction diode** instead:




Q: *This circuit looks so familiar! Haven't we studied it before?*

A: Yes! It was an **example** where we determined the junction diode circuit transfer function. Recall that the **result** was:
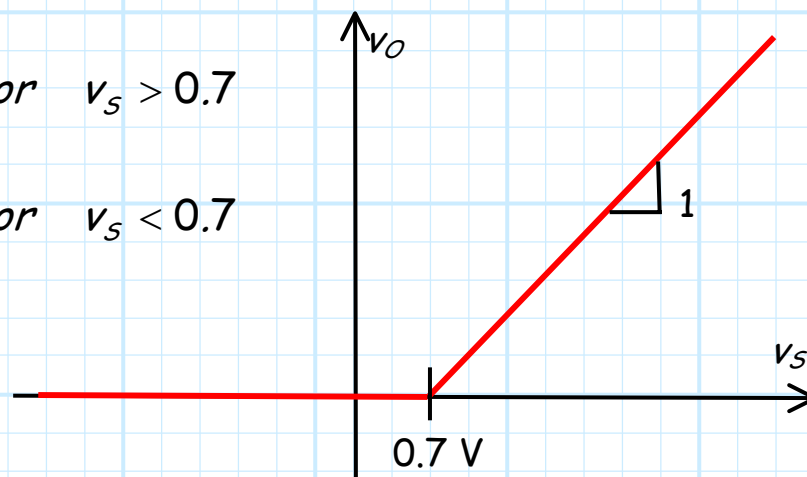
$$v_O = \begin{cases} v_S - 0.7 & \text{for } v_S > 0.7 \\ 0 & \text{for } v_S < 0.7 \end{cases}$$



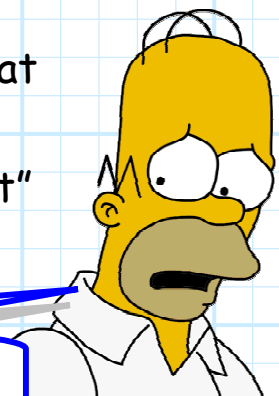Note that this result is **slightly different** from that of the **ideal** half-wave rectifier! The **0.7 V drop** across the junction diode causes a horizontal "shift" of the transfer function from the ideal case.




Q: *So, this junction diode circuit is worthless?*

A: Hardly! Although the transfer function is **not quite** ideal, it works **well enough** to achieve the goal of signal rectification—it takes an input with **no** DC component and creates an output with a **significant** DC component!


Note what the transfer function “**rule**” is now:

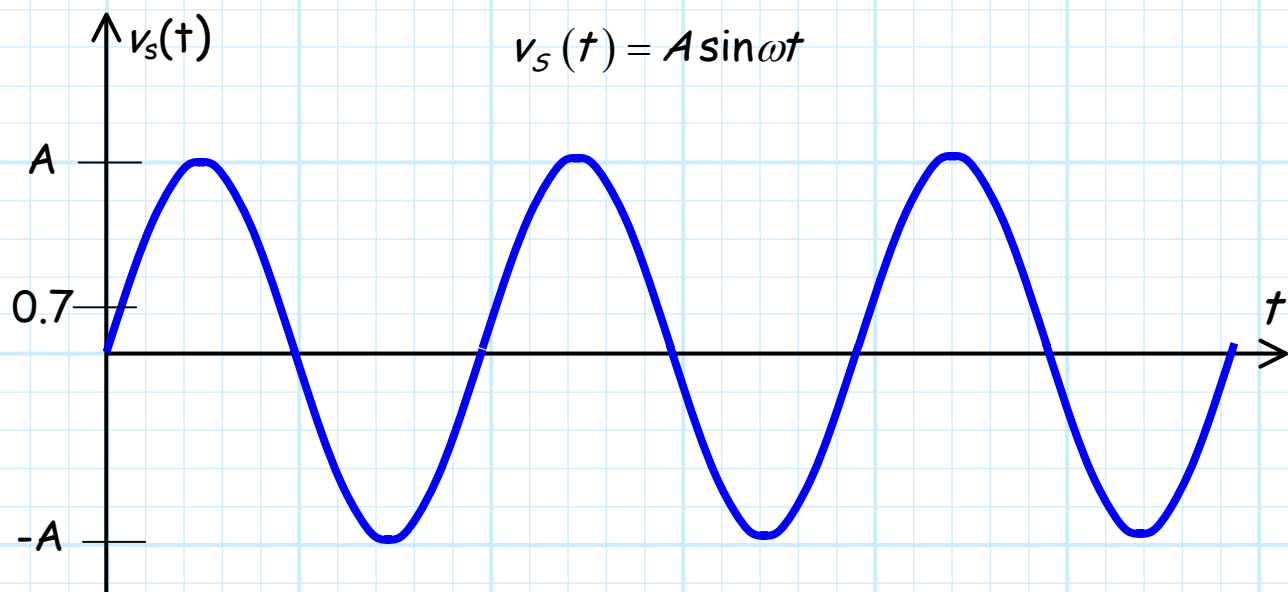1. When the input is **greater** than 0.7 V, the output voltage is **equal** to the input voltage minus 0.7 V.
2. When the input is **less** than 0.7 V, the output voltage is **zero**.

So, let's consider **again** the case where the **source** voltage is **sinusoidal** (just like the source from a “wall socket!”):



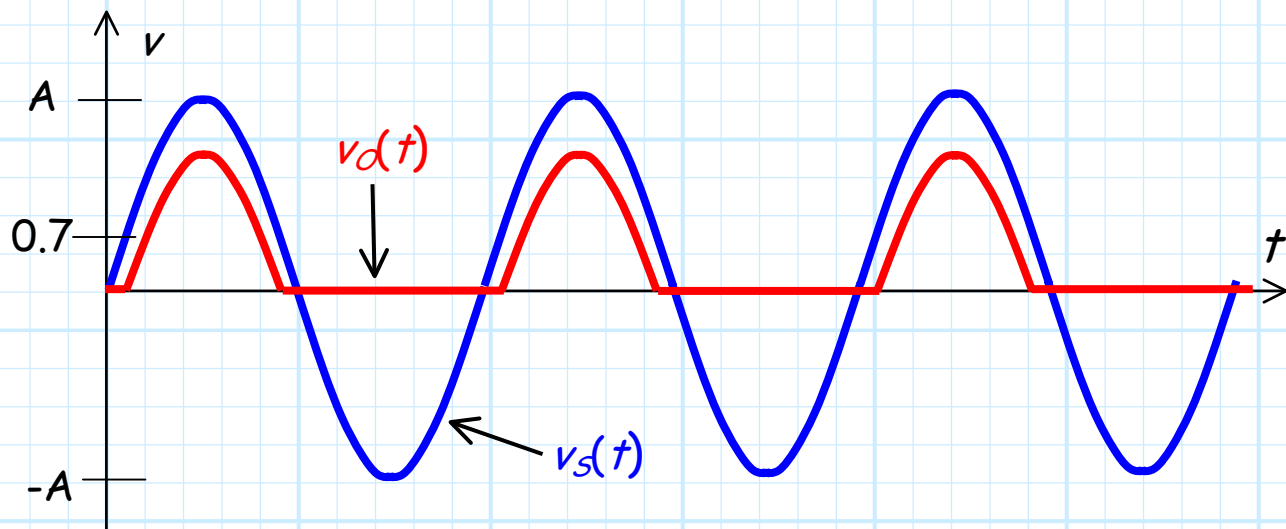The output of our **junction diode** half-wave rectifier would therefore be:




Although the output is **shifted downward** by 0.7 V (note in the plot above this is **exaggerated**, typically $A \gg 0.7\text{V}$), it should be apparent that the **output signal** $v_d(t)$, unlike the input signal $v_s(t)$, has a **non-zero** (positive) **DC component**.

Because of the 0.7 V shift, this DC component is **slightly smaller** than the **ideal** case. In fact, we find that if $A \gg 0.7$, this **DC component** is approximately:


$$V_o \approx \frac{A}{\pi} - 0.35 \text{ V}$$

In other words, **just 350 mV less than ideal!**

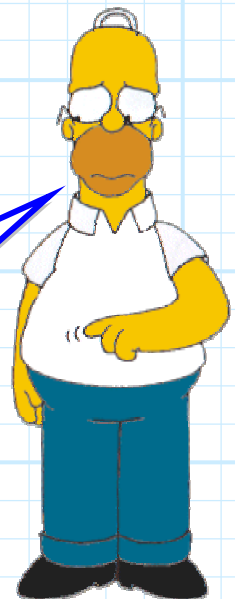
Q: *Way back on the first page you said that there were **two** types of rectifiers. I now understand **half-wave** rectification, but what about these so-called **full-wave** rectifiers?*



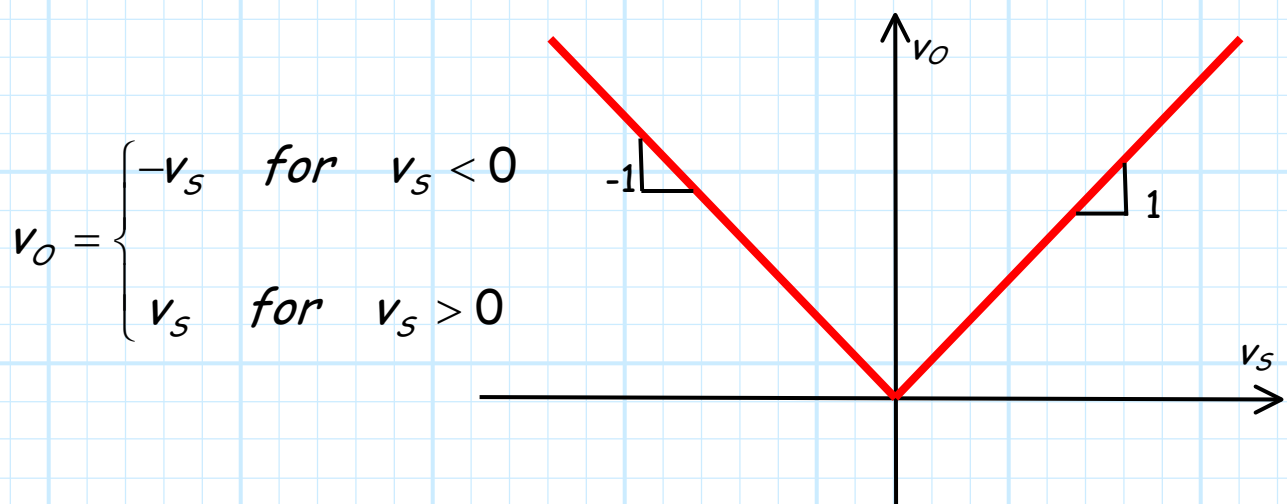A: Almost forgot! Let's examine the transfer function of an ideal full-wave rectifier:





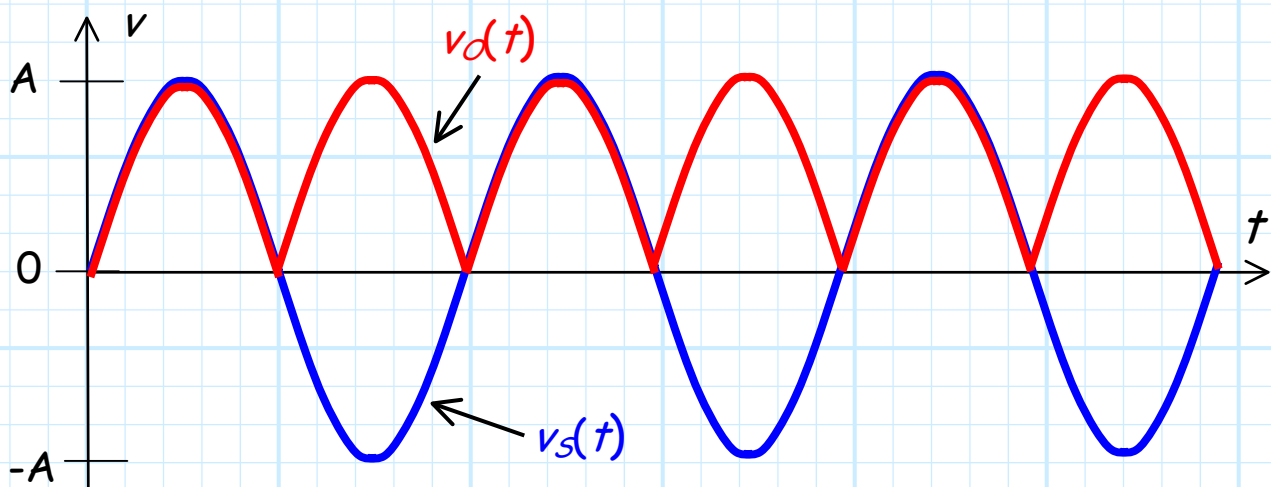If the ideal half-wave rectifier makes **negative** inputs **zero**, the ideal full-wave rectifier makes **negative** inputs—**positive**! For **example**, if we again consider our **sinusoidal** input, we find that the output will be:



The result is that the output signal will have a DC component **twice** that of the ideal half-wave rectifier!
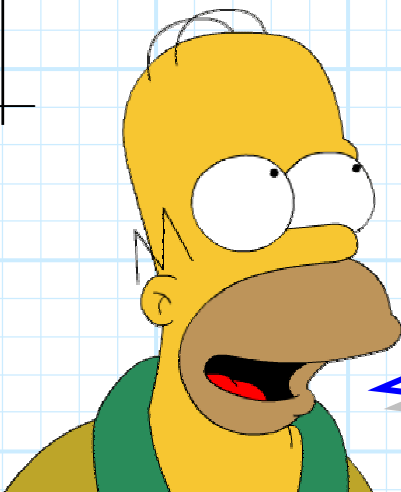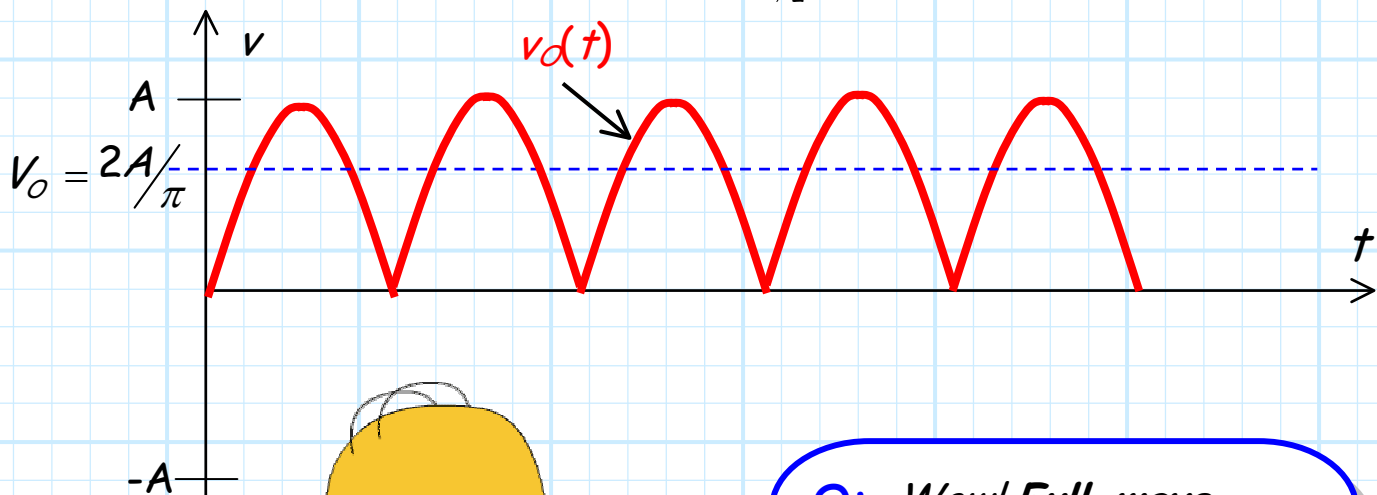
$$\begin{aligned}
 V_o &= \frac{1}{T} \int_0^T v_o(t) dt \\
 &= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt - \frac{1}{T} \int_{T/2}^T A \sin \omega t dt = \frac{2A}{\pi}
 \end{aligned}$$




Q: *Wow! Full-wave rectification appears to be twice as good as half-wave. Can we build an ideal full-wave rectifier with junction diodes?*

A: Although we cannot build an **ideal** full-wave rectifier with **junction** diodes, we can build full-wave rectifiers that are **very close** to ideal with junction diodes!

The Full-Wave Rectifier

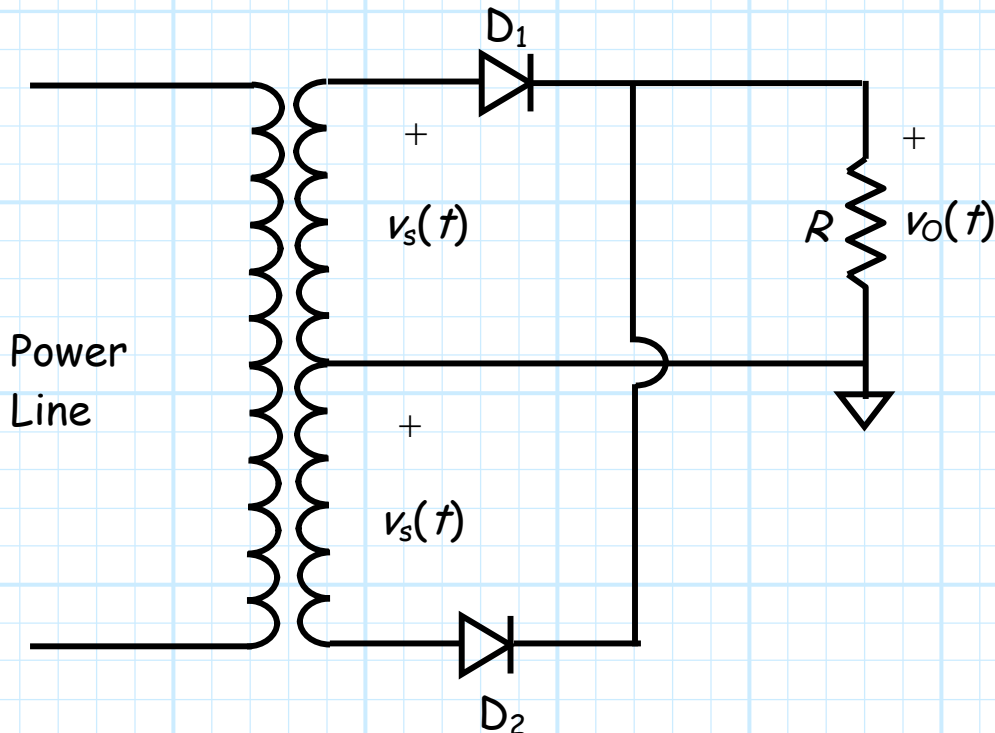
Consider the following **junction diode** circuit:




Note that we are using a **transformer** in this circuit. The job of this transformer is to **step-down** the large voltage on our power line (120 V rms) to some **smaller** magnitude (typically 20-70 V rms).

Note the secondary winding has a **center tap** that is **grounded**. Thus, the secondary voltage is distributed **symmetrically** on either side of this center tap.

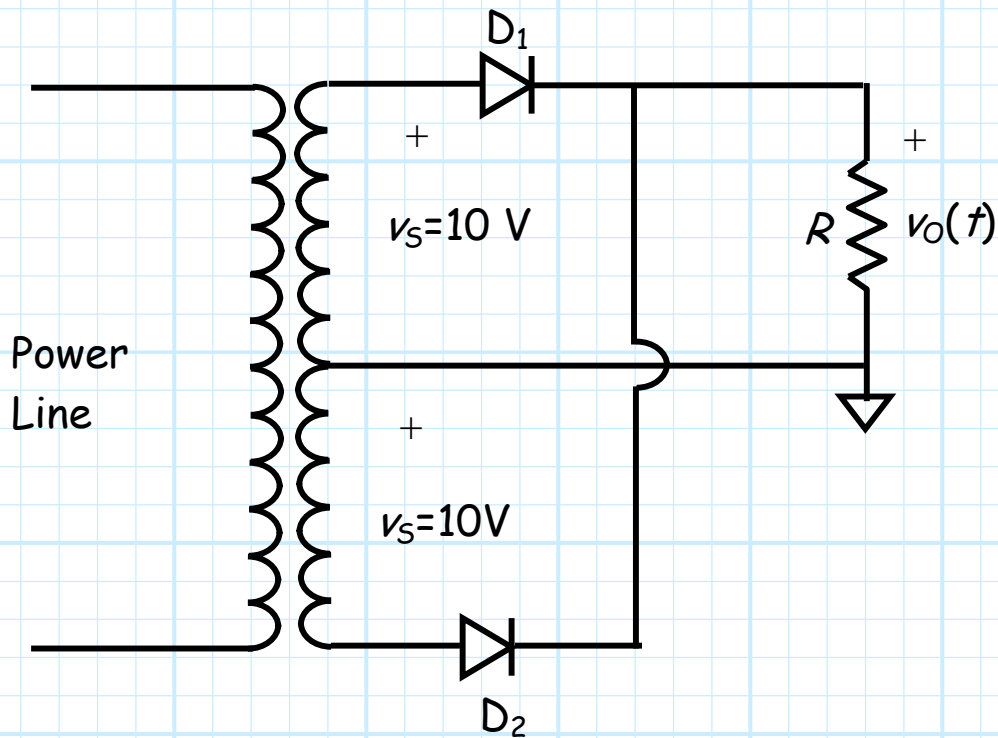For example, if $v_s = 10$ V, the anode of D_1 will be 10V **above** ground potential, while the anode of D_2 will be 10V **below** ground potential (i.e., -10V):




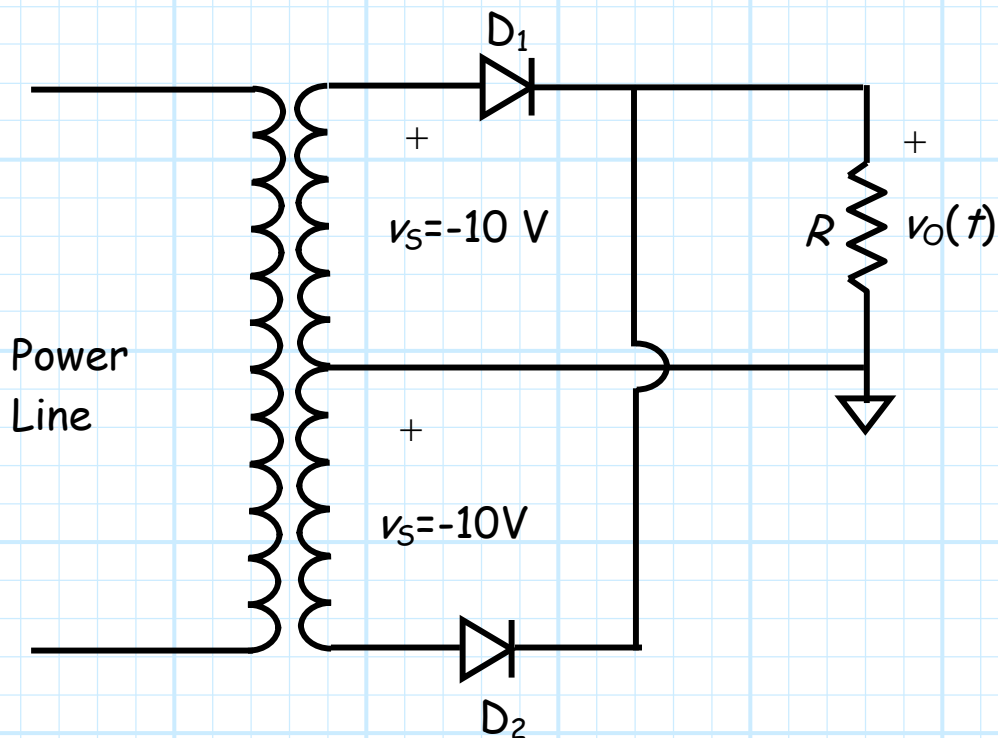Conversely, if $v_s = -10\text{ V}$, the anode of D_1 will be 10V **below** ground potential (i.e., -10V), while the anode of D_2 will be 10V **above** ground potential:




The more important question is, what is the value of **output** v_o ? More specifically, how is v_o related to the value of source v_s —what is the **transfer function** $v_o = f(v_s)$?

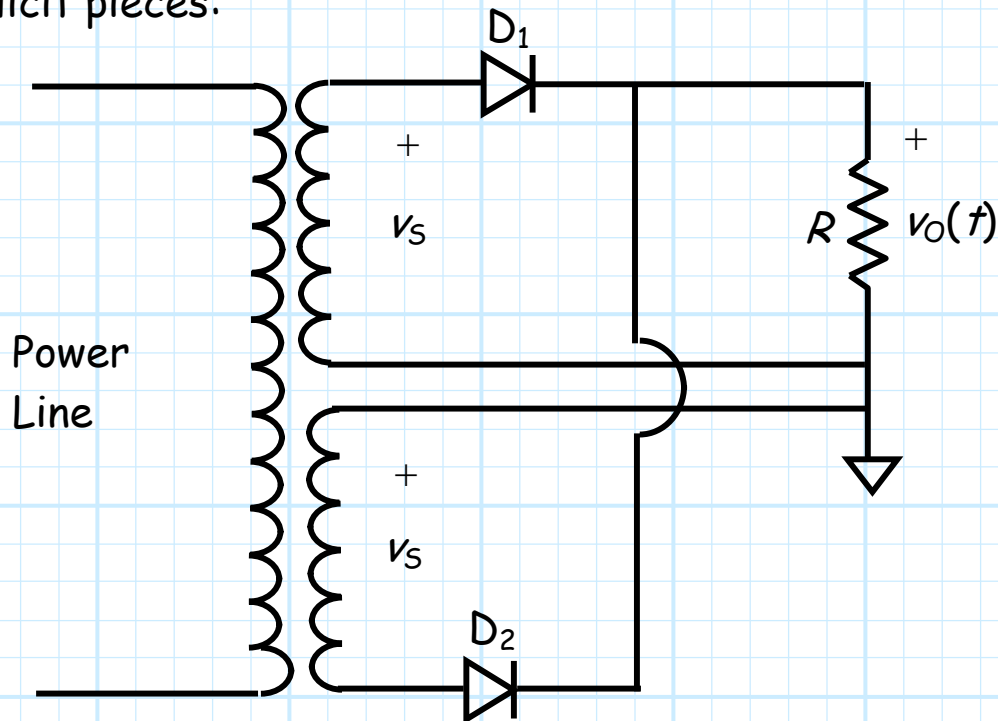
To help simplify our analysis, we are going **redraw** this circuit in another way. First, we will **split** the secondary winding into two explicit pieces:



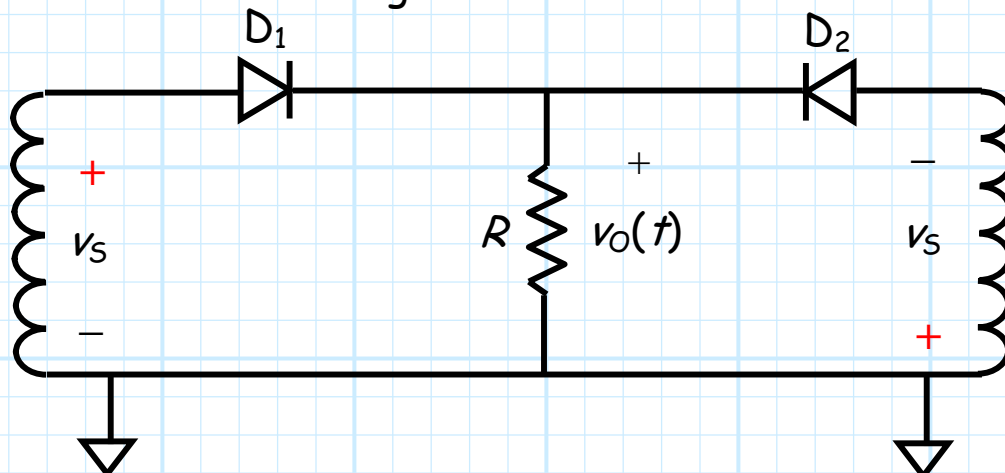We will now **ignore the primary** winding of the transformer and redraw the remaining circuit as:



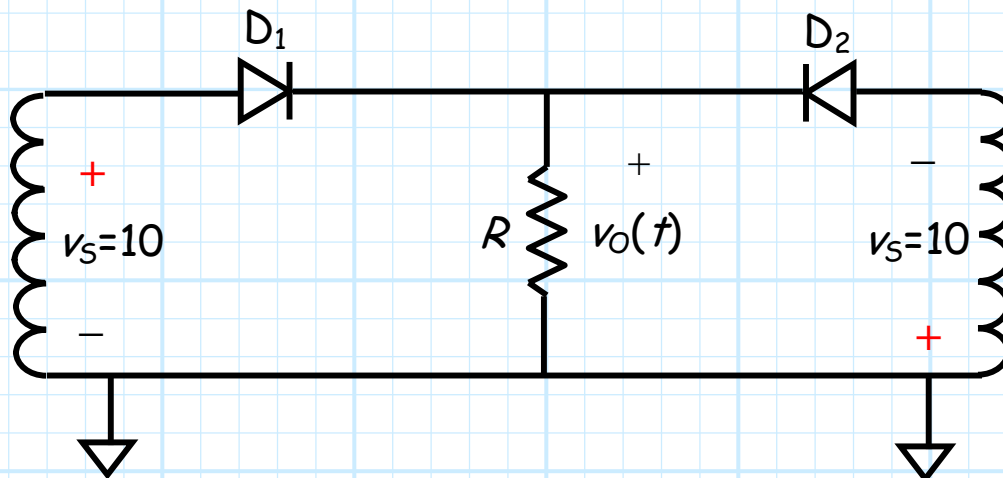
Note that the secondary voltages at either end of this circuit are the **same**, but have **opposite** polarity. As a result, if $v_S=10$, then the anode of diode D_1 will be 10 V **above** ground, and the anode at diode D_2 will be 10V **below** ground—just like before!



Now, let's attempt to determine the **transfer function** $v_O = f(v_S)$ of this circuit.

First, we will replace the junction diodes with **CVD models**.

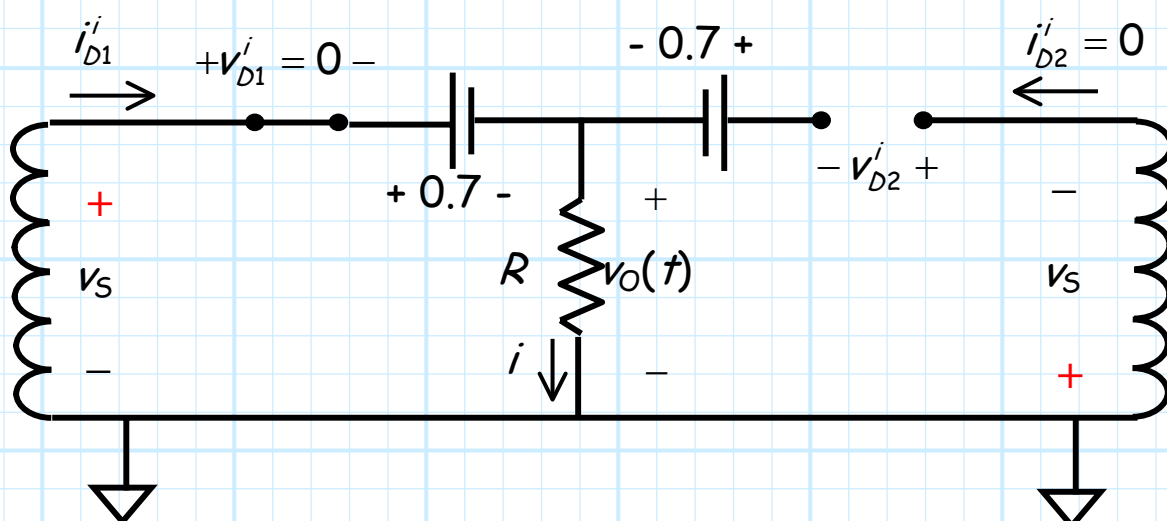Then let's **ASSUME** D_1 is **forward** biased and D_2 is **reverse** biased, thus **ENFORCE** $v_{D1}^i = 0$ and $i_{D2}^i = 0$. Thus **ANALYZE**:



Note that we need to determine **3** things: the **ideal diode current** i_{D1}^i , the **ideal diode voltage** v_{D2}^i , and the **output voltage** v_O . However, **instead** of finding numerical values for these 3 quantities, we must express them in terms of **source voltage** v_S !

From KCL:
$$i = i_{D1}^i + i_{D2}^i = i_{D1}^i + 0 = i_{D1}^i$$

From KVL:
$$v_S - v_{D1}^i - 0.7 - R i_D^i = 0$$

Thus the **ideal diode current** is:

$$i_{D1}^i = \frac{v_S - 0.7}{R}$$

Likewise, from KVL:
$$v_S - v_{D1}^i - 0.7 + 0.7 + v_{D2}^i + v_S = 0$$

Thus, the **ideal diode voltage** is:

$$v_{D2}^i = -2v_S$$

And finally, from KVL:
$$v_S - v_{D1}^i - 0.7 = v_O$$

Thus, the **output voltage** is:

$$v_O = v_S - 0.7$$

Now, we must determine **when** both $i_{D1}^i > 0$ and $v_{D2}^i < 0$. When **both** these conditions are true, the output voltage will be $v_o = v_s - 0.7$. When one **or** both conditions $i_{D1}^i > 0$ and $v_{D2}^i < 0$ are **false**, then our assumptions are **invalid**, and $v_o \neq v_s - 0.7$.

Using the results we just determined, we know that $i_{D1}^i > 0$ **when**:

$$\frac{v_s - 0.7}{R} > 0$$

Solving for v_s :

$$\begin{aligned} \frac{v_s - 0.7}{R} &> 0 \\ v_s - 0.7 &> 0 \\ v_s &> 0.7 \text{ V} \end{aligned}$$

Likewise, we find that $v_{D2}^i < 0$ **when**:

$$-2v_s < 0$$

Solving for v_s :

$$\begin{aligned} -2v_s &< 0 \\ 2v_s &> 0 \\ v_s &> 0 \end{aligned}$$


Thus, our assumptions are correct **when** $v_s > 0.0$ **AND** $v_s > 0.7$. This is the **same** thing as saying our assumptions are valid when $v_s > 0.7$!

Thus, we have found that the following statement is true about this circuit:

$$v_o = v_s - 0.7 \text{ V} \quad \text{when} \quad v_s > 0.7 \text{ V}$$

Note that this statement does **not** constitute a **function** (what about $v_s < 0.7$?), so we must **continue** with our analysis!

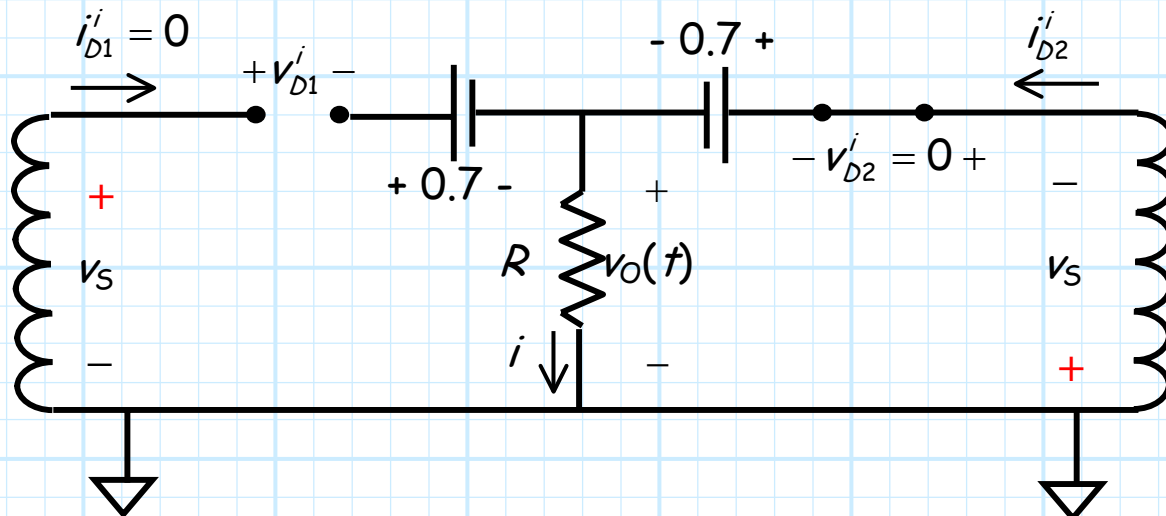Say we now **ASSUME** that D_1 is **reverse** biased and D_2 is **forward** biased, so we **ENFORCE** $i_{D1}^i = 0$ and $v_{D2}^i = 0$. Thus, we **ANALYZE this** circuit:




Using the **same procedure** as before, we find that $v_o = -v_s - 0.7$, and both our assumptions are true **when** $v_s < -0.7 \text{ V}$. In other words:

$$v_o = -v_s - 0.7 \text{ V} \quad \text{when} \quad v_s < -0.7 \text{ V}$$

Note we are still **not** done! We **still** do not have a complete transfer **function** (what happens when $-0.7 \text{ V} < v_s < 0.7 \text{ V}$?).

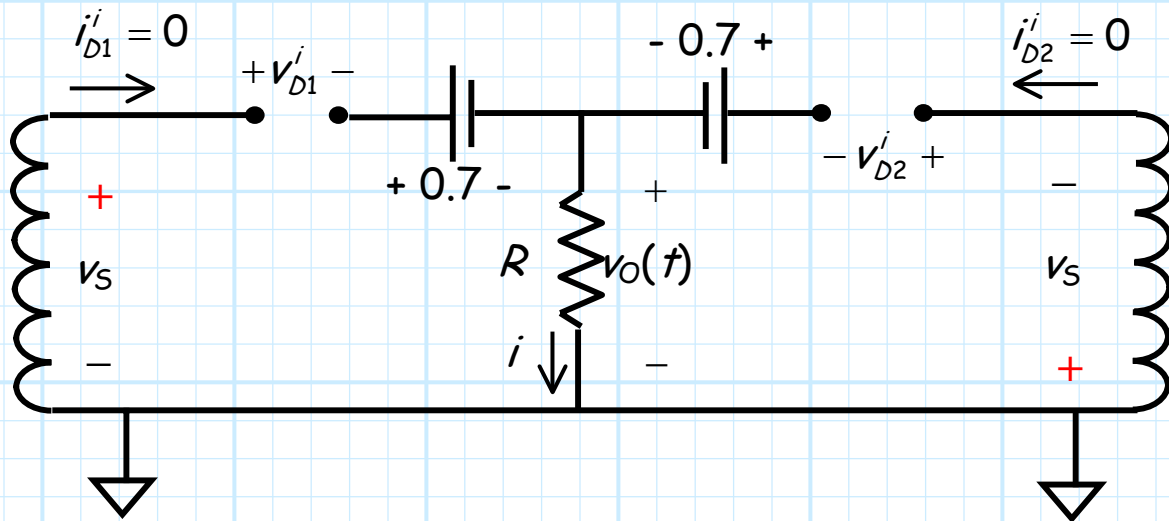Finally then, we ASSUME that **both** ideal diodes are **reverse** biased, so we ENFORCE $i_{D1}^i = 0$ and $i_{D2}^i = 0$. Thus ANALYZE:




Following the **same procedures** as before, we find that $v_S = 0$, and both assumptions are true **when** $-0.7 < v_S < 0.7$. In other words:

$$v_S = 0 \quad \text{when} \quad -0.7 < v_S < 0.7$$


Now we have a function! The transfer function of this circuit is:

$$v_O = \begin{cases} v_S - 0.7V & \text{for } v_S > 0.7V \\ 0V & \text{for } -0.7 > v_S > 0.7V \\ -v_S - 0.7V & \text{for } v_S < -0.7V \end{cases}$$

Plotting this function:

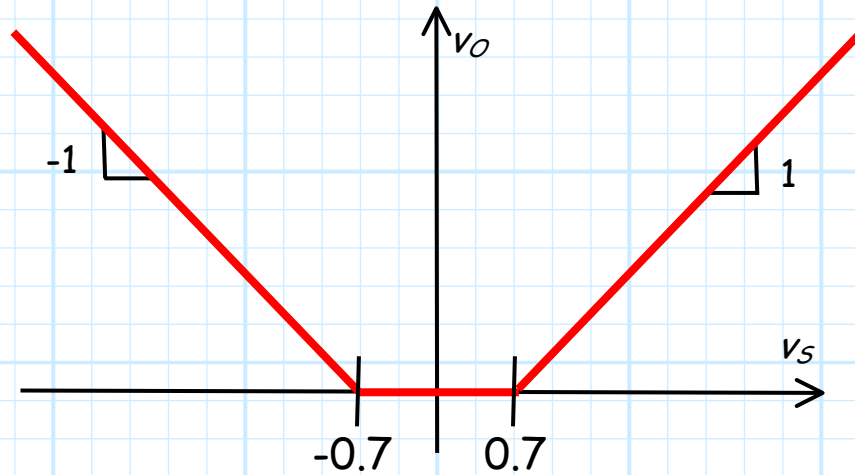


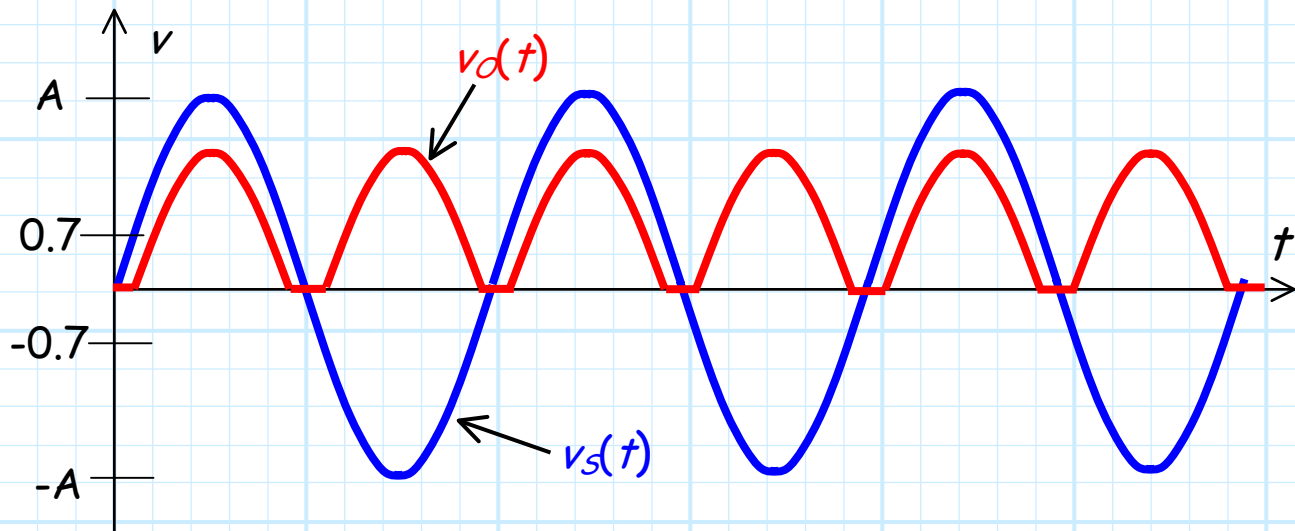The output of this full-wave rectifier with a **sine wave input** is therefore:




Note how this **compares** to the transfer function of the **ideal** full-wave rectifier:
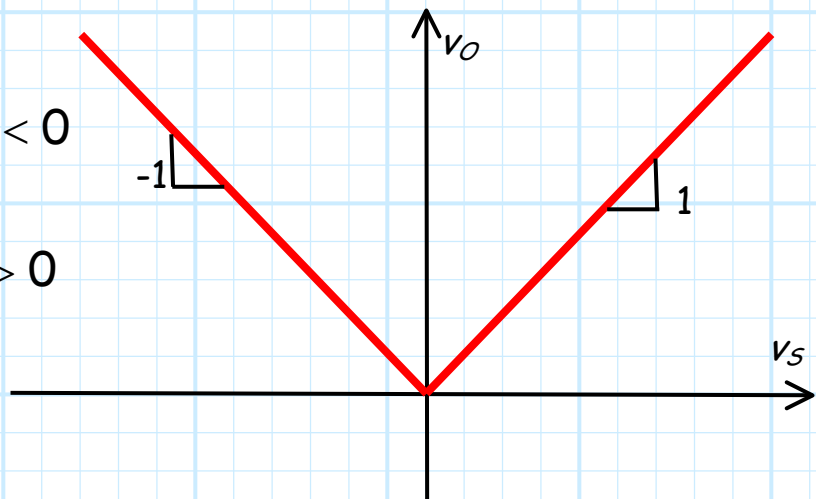
$$v_o = \begin{cases} -v_s & \text{for } v_s < 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$



Very similar!

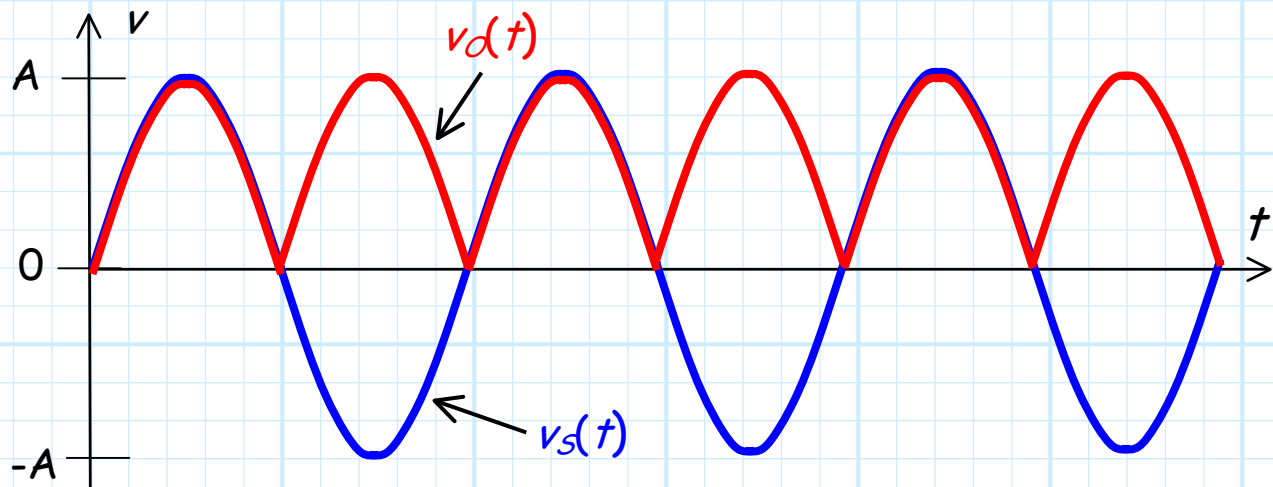Likewise, compare the output of this junction diode full-wave rectifier to the output of an **ideal** full-wave rectifier:




Again we see that the junction diode full-wave rectifier output is **very close** to ideal. In fact, if $A \gg 0.7 \text{ V}$, the **DC component** of this junction diode full wave rectifier is approximately:

$$V_o \approx \frac{2A}{\pi} - 0.7 \text{ V}$$

Just 700 mV less than the **ideal** full-wave rectifier DC component!


The Bridge Rectifier

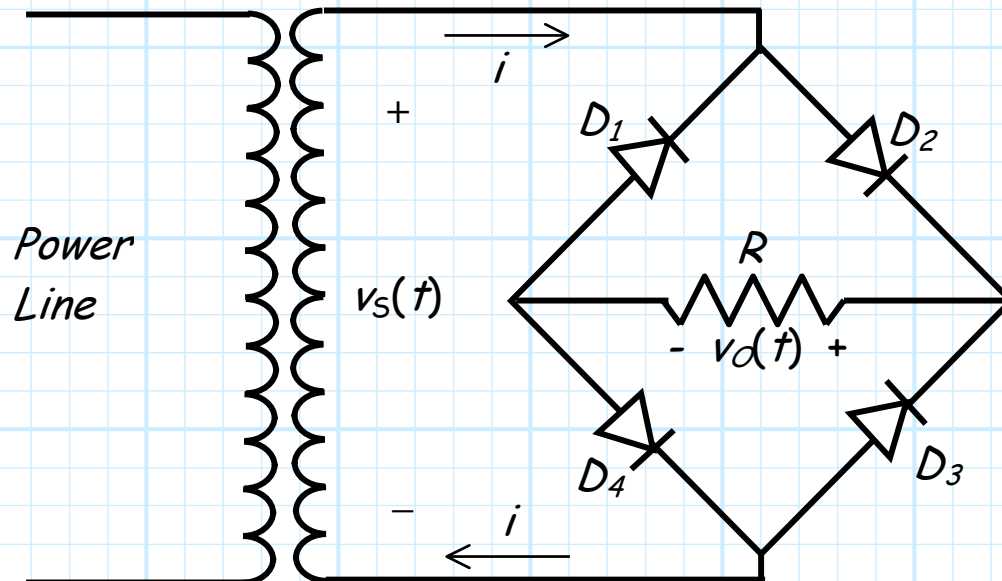Now consider this **junction diode** rectifier circuit:



We call this circuit the **bridge rectifier**. Let's **analyze** it and see what it does!

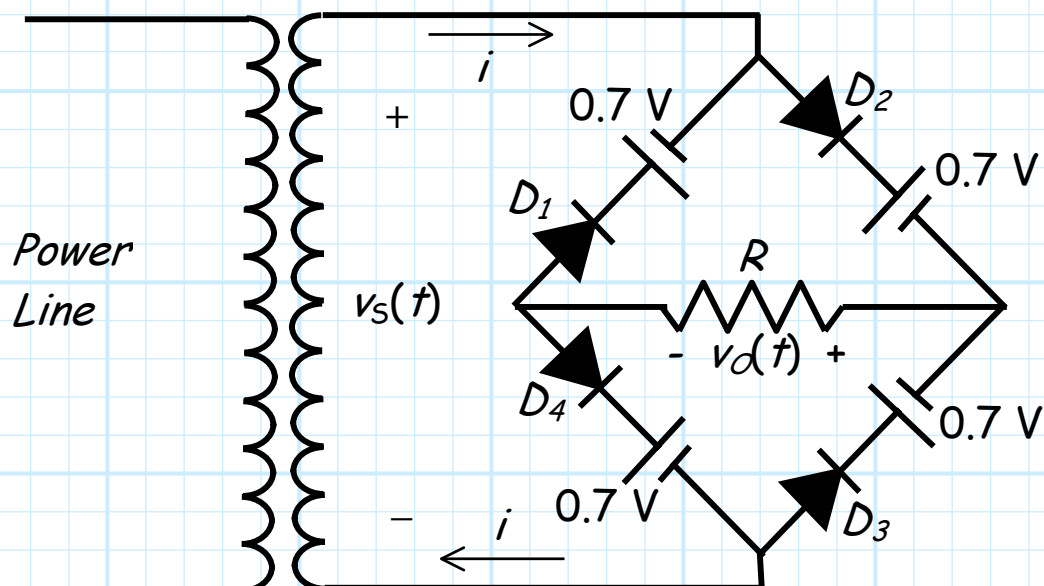First, we **replace** the junction diodes with the **CVD model**:





Q: *Four gul-durn ideal diodes! That means 16 sets of dad-gum assumptions!*

A: True! However, there are only **three** of these sets of assumptions are actually **possible!**

Consider the **current** i flowing through the rectifier. This current of course can be positive, negative, or zero. It turns out that there is only **one** set of diode assumptions that would result in positive current i , **one** set of diode assumptions that would lead to negative current i , and **one** set that would lead to zero current i .

Q: *But what about the remaining 13 sets of dog gone diode assumptions?*



A: **Regardless** of the value of source v_S , the remaining 13 sets of diode assumptions simply **cannot occur** for this particular circuit design!


Let's look at the **three** possible sets of assumptions:

$i > 0$

The rectifier current i can be **positive** only if these assumptions are true:

D_1 and D_3 are reverse biased.

D_2 and D_4 are forward biased.

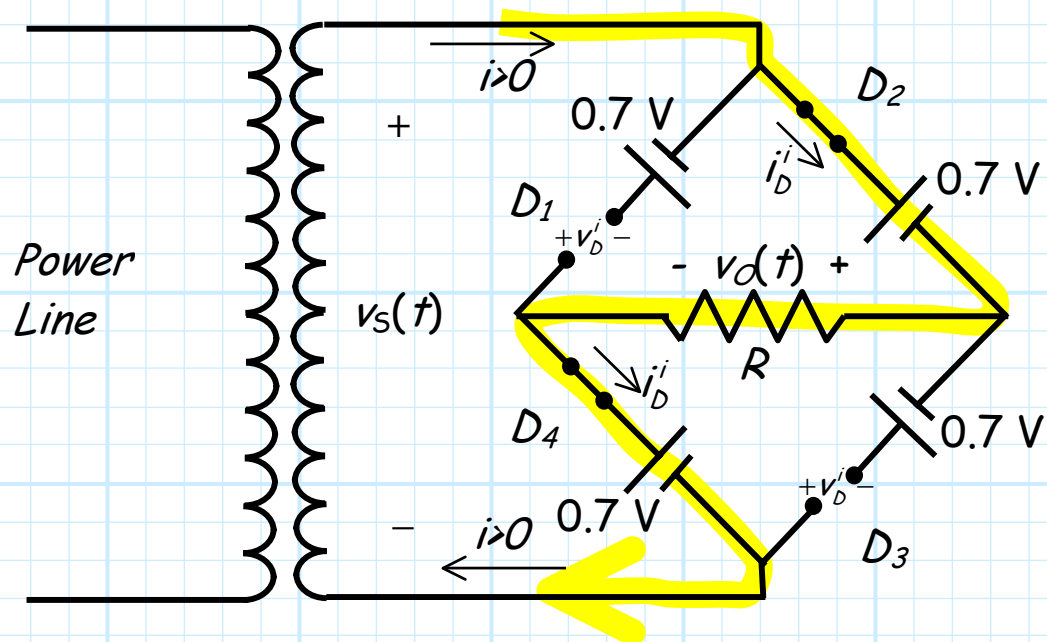

Analyzing this circuit, we find that the **output voltage** is:

$$v_o = v_s - 1.4 \text{ V}$$

and the f.b. ideal diode currents are:

$$i = i_D^j = \frac{v_s - 1.4}{R}$$

and, finally the r.b. **ideal diode voltages** are:

$$v_D^i = -v_S$$

Thus, $i_D^i > 0$ when:

$$\frac{v_S - 1.4}{R} > 0$$

$$v_S - 1.4 > 0$$

$$v_S > 1.4 \text{ V}$$

and $v_D^i < 0$ when:

$$-v_S < 0$$

$$v_S > 0$$

Therefore, we **find** that for this circuit:


$$v_O = v_S - 1.4 \text{ V} \quad \text{when} \quad v_S > 1.4 \text{ V}$$

$i < 0$

The rectifier current i can be **negative** only if these assumptions are true:

D_1 and D_3 are forward biased.

D_2 and D_4 are reverse biased.

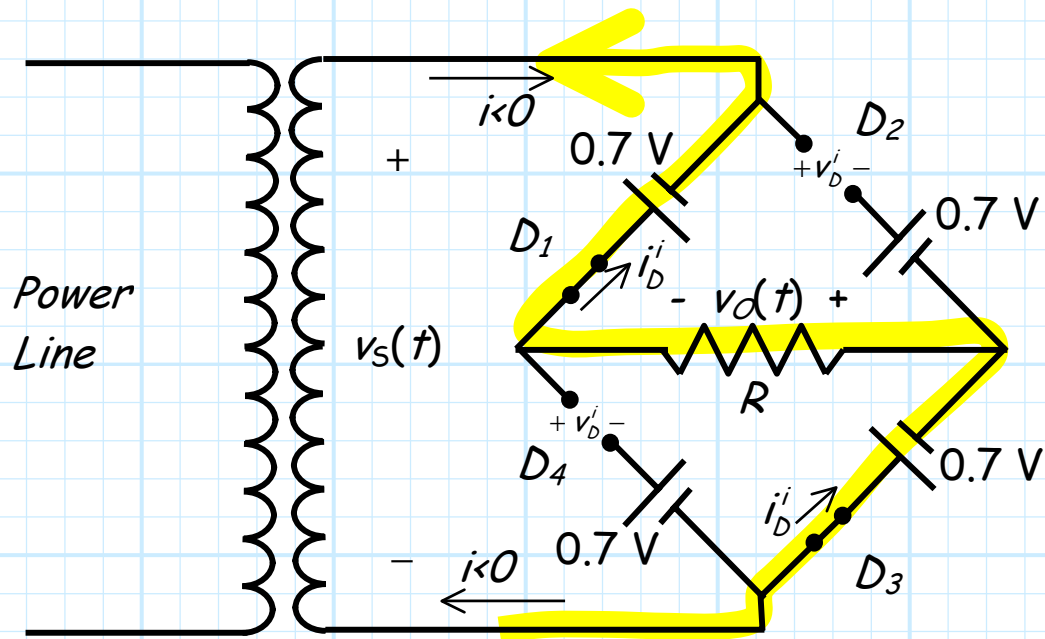

Analyzing this circuit, we find that the **output voltage** is:

$$v_o = -v_s - 1.4\text{ V}$$

while the f.b. **ideal diode currents** are both :

$$-i = i_D^i = \frac{-v_s - 1.4}{R}$$

and the r.b. **ideal diode voltages** are both:

$$v_D^i = v_s$$

Thus, $i_D^i > 0$ when:

$$\frac{-v_s - 1.4}{R} > 0$$

$$-v_s - 1.4 > 0$$

$$-v_s > 1.4 \text{ V}$$

$$v_s < -1.4 \text{ V}$$

and, $v_D^i < 0$ when:

$$v_s < 0$$


Therefore, we likewise find for this circuit:

$$v_o = -v_s - 1.4 \text{ V} \quad \text{when} \quad v_s < -1.4 \text{ V}$$

$i = 0$

The rectifier current i can be **zero** only if these assumptions are true:

All ideal diodes are **reverse** biased!

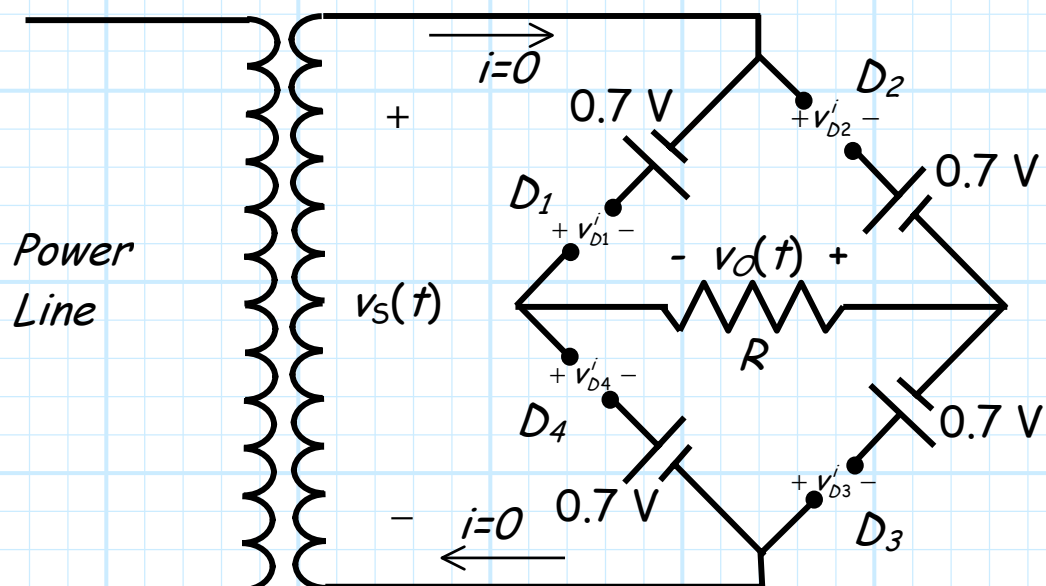

Analyzing this circuit, we find that the **output voltage** is:

$$v_o = Ri = 0$$

while the **ideal diode voltages** of D_2 and D_4 are each:

$$v'_{D2} = \frac{v_s - 1.4}{2} = v'_{D4}$$

and the **ideal diode voltages** of D_1 and D_3 are each:

$$v'_{D1} = \frac{-v_s - 1.4}{2} = v'_{D3}$$

Thus, $v'_{D2} < 0$ when:

$$\begin{aligned} \frac{v_s - 1.4}{2} &< 0 \\ v_s - 1.4 &< 0 \\ v_s &< 1.4 \end{aligned}$$

and, $v'_{D1} < 0$ when:

$$\begin{aligned} \frac{-v_s - 1.4}{2} &< 0 \\ -v_s - 1.4 &< 0 \\ -v_s &< 1.4 \\ v_s &> -1.4 \end{aligned}$$

Therefore, we also find for this circuit that:


$$v_o = 0 \quad \text{when both } v_s < 1.4\text{V and } v_s > -1.4\text{V } (-1.4 < v_s < 1.4\text{V})$$



Q: You know, that dang *Mizzou* grad said we only needed to consider these **three** sets of diode assumptions, yet I am **still** concerned about the other 13. How can we be **sure** that we have analyzed every **possible** set of **valid** diode assumptions?


A: We know that we have considered **every** possible case, because when we combine the three results we find that we have a piece-wise linear **function!** I.E.;
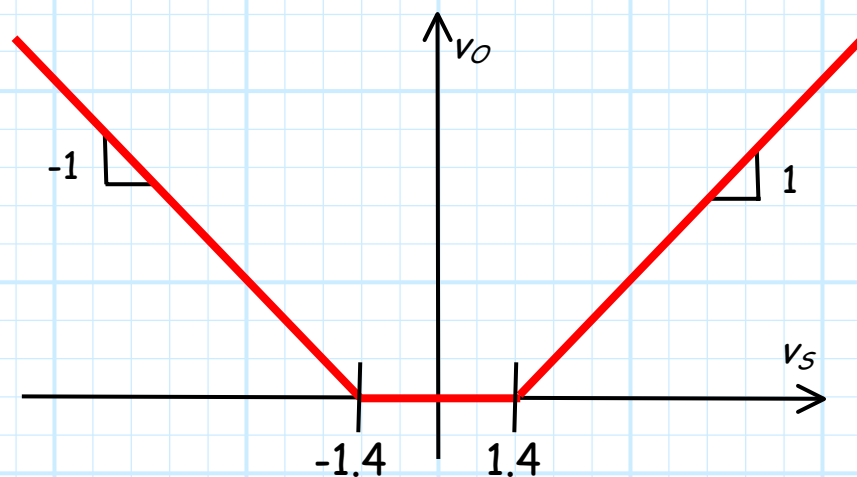
$$v_o = \begin{cases} -v_s - 1.4 \text{ V} & \text{if } v_s < -1.4 \text{ V} \\ 0 & \text{if } -1.4 < v_s < 1.4 \text{ V} \\ v_s - 1.4 \text{ V} & \text{if } v_s > 1.4 \text{ V} \end{cases}$$



Note that the **bridge** rectifier is a **full-wave** rectifier!

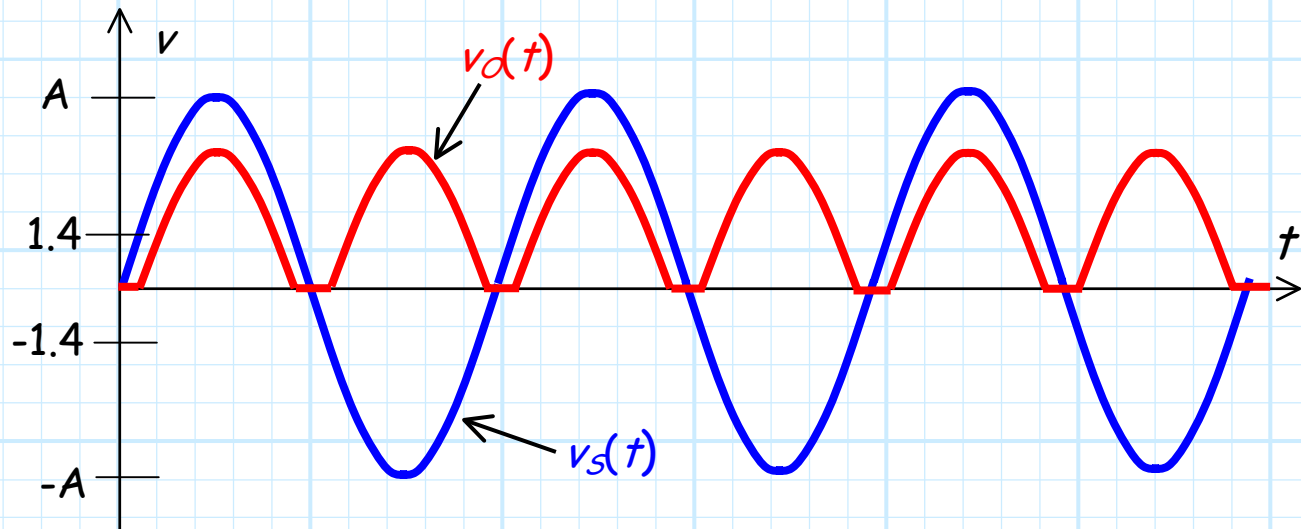If the input to this rectifier is a **sine wave**, we find that the **output** is approximately that of an ideal **full-wave rectifier**:




We see that the junction diode bridge rectifier output is **very close** to ideal. In fact, if $A \gg 1.4$ V, the **DC component** of this junction diode bridge rectifier is approximately:

$$V_o \approx \frac{2A}{\pi} - 1.4 \text{ V}$$

Just 1.4 V less than the **ideal** full-wave rectifier DC component!

Peak Inverse Voltage

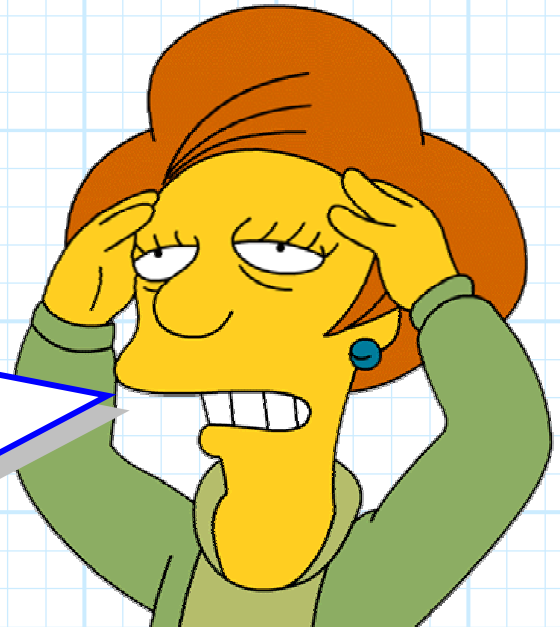Q: *I'm so confused! The bridge rectifier and the full-wave rectifier both provide full-wave rectification. Yet, the bridge rectifier use 4 junction diodes, whereas the full-wave rectifier only uses 2. Why would we ever want to use the bridge rectifier?*



A: First, a slight **confession**—the results we derived for the bridge and full-wave rectifiers are **not** precisely correct!

Recall that we used the junction diode **CVD model** to determine the transfer function of each rectifier circuit. The problem is that the CVD model does **not** predict junction diode **breakdown**!

If the **source** voltage v_S becomes too **large**, the junction diodes can in fact **breakdown**—but the transfer functions we derived do **not** reflect this fact!

Q: *Yikes! You mean that we need to **rework** our analysis and find **new** transfer functions!*



A: Fortunately **no**. Breakdown is an **undesirable** mode for circuit rectification. Our job as engineers is to design a rectifier that **avoids** it—that why the **bridge** rectifier is helpful!

To see why, consider the voltage across a **reversed biased** junction diode in **each** of our rectifier circuit designs.

Recall that the voltage across a **reverse biased ideal diode** in the **full-wave rectifier** design was:

$$v_{D2}' = -2v_S$$

so that the voltage across the **junction diode** is approximately:


$$\begin{aligned} v_D &= v_D' + 0.7 \\ &= -2v_S + 0.7 \end{aligned}$$

Now, assuming that the **source** voltage is a **sine wave** $v_S = A \sin \omega t$, we find that diode voltage is at it **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value A . I.E.;

$$v_D^{min} = -2A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in **forward** bias:

$$v_D^{max} = 0.7 \text{ V}$$

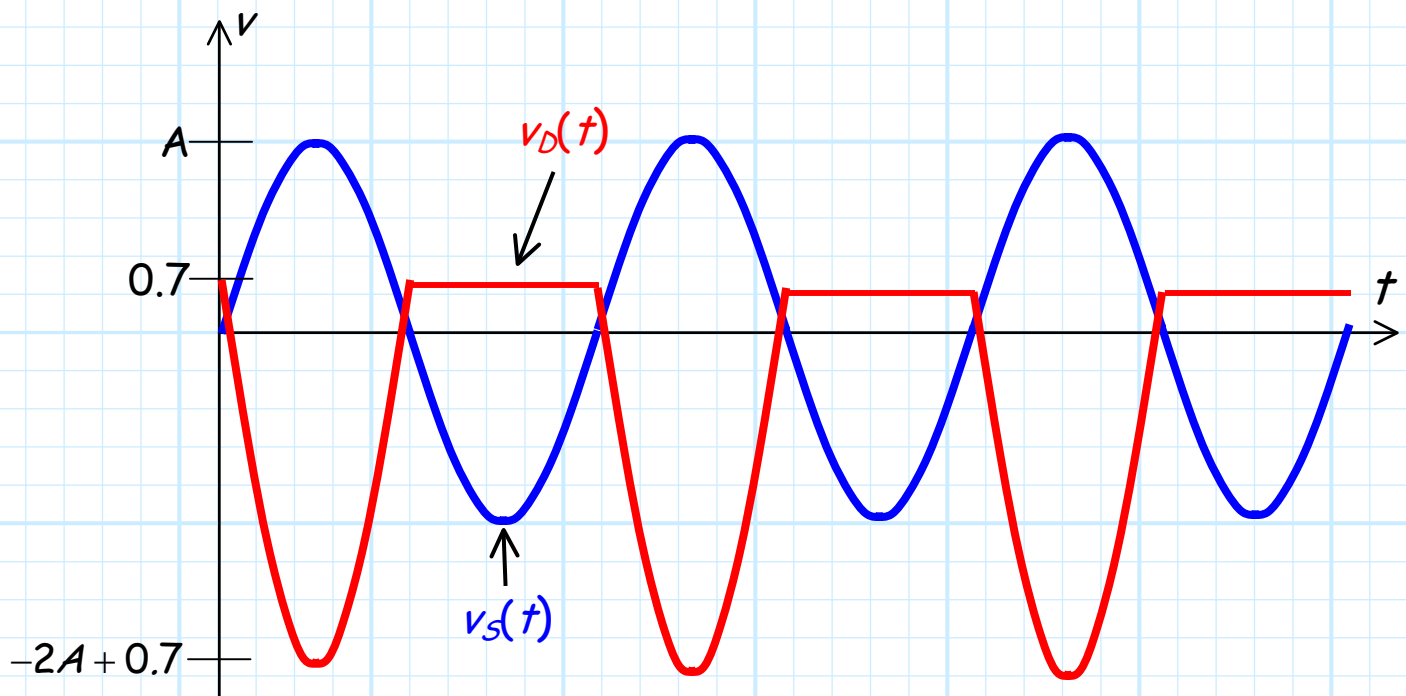

Note that this **minimum** diode voltage v_D is **very negative**, with an absolute value ($|v_D^{min}| = 2A - 0.7$) nearly **twice** as large as the source magnitude A .

We call the absolute value of the minimum diode voltage the **Peak Inverse Voltage (PIV)**:

$$PIV = |v_D^{min}|$$

Note that this value is dependent on **both** the rectifier design **and** the magnitude of the source voltage v_S .



Q: *So, why do we need to determine PIV? I'm not sure I see what difference this value makes.*

A: The Peak Inverse Voltage **answers** one important question—**will** the junction diodes in our rectifier **breakdown**?

→ **If** the PIV is **less** than the Zener breakdown voltage of our rectifier diodes (i.e., if $PIV < V_{ZK}$), then we know that our junction diodes will **remain** in either forward or reverse bias for all time t . The rectifier will operate “properly”!

→ However, **if** the PIV is **greater** than the Zener breakdown voltage of our rectifier diodes (i.e., if $PIV > V_{ZK}$), then we know that our junction diodes will **breakdown** for at least **some** small amount of time t . The rectifier will **NOT** operate properly!



Q: So what do we do if PIV is greater than V_{ZK} ? How do we fix this problem?

A: We have **two** possible **solutions**:

1. Use junction diodes with **larger** values of V_{ZK} (if they exist!).
2. Use the **bridge** rectifier design.

Q: The **bridge** rectifier! How would that solve our **breakdown** problem?



A: To see how a **bridge** rectifier can be **useful**, let's determine its Peak Inverse Voltage **PIV**.

First, we recall that the voltage across the **reverse biased ideal diodes** was:

$$v_D^i = -v_S$$

so that the voltage across the **junction diode** is approximately:


$$\begin{aligned} v_D &= v_D^i + 0.7 \\ &= -v_S + 0.7 \end{aligned}$$

Now, assuming that the **source** voltage is a **sine wave** $v_S = A \sin \omega t$, we find that diode voltage is at its **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value A . I.E.,:

$$v_D^{min} = -A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in forward bias:

$$v_D^{max} = 0.7 \text{ V}$$

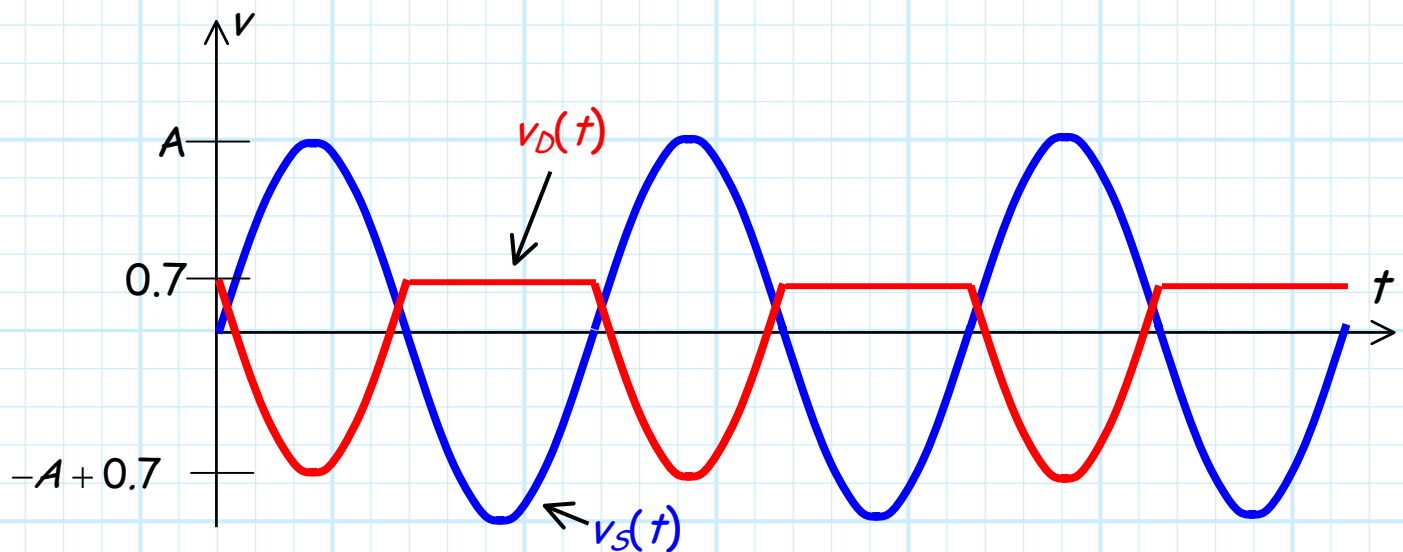

Note that this minimum diode voltage is **very negative**, with an absolute value ($|v_D^{min}| = A - 0.7$), approximately **equal** to the value of the **source magnitude A** .

Thus, the **PIV** for a **bridge** rectifier with a **sinusoidal source** voltage is:

$$PIV = A - 0.7$$

Note that this **bridge** rectifier value is approximately **half** the PIV we determined for the **full-wave** rectifier design!

Thus, the source voltage (and the output DC component) of a **bridge** rectifier can be **twice** that of the full-wave rectifier design—this is why the **bridge** rectifier is a very **useful** rectifier design!