

4.1 The Ideal Diode

Reading Assignment: pp.165-172

Before we get started with ideal diodes, let's first recall **linear device behavior!**

HO: LINEAR DEVICE BEHAVIOR

Now, the **ideal diode** is our first "electronic" circuit device. It is **asymmetric**, and **non-linear**.

Q: *Is it also made from semi-conductors?*

A: Actually, **ideal** diodes are entirely made from our imaginations!

HO: THE IDEAL DIODE

Q: *I see the math, and I see the plots, but I'm still not sure what an ideal diode actually does.*

A: Perhaps an **analogy** would help!

HO: DIODE MECHANICAL ANALOGY

Q: *So we can use these things in circuits?*

A: Sure! But we will find **analyzing** the circuit is **problematic**.

HO: IDEAL DIODE CIRCUITS

Q: *So just how **do** we analyze ideal diode circuits?*

A: Just **carefully** and **precisely** and **patiently** follow the **steps** delineated in "Ideal Diode Circuit Analysis Guide"

HO: THE IDEAL DIODE CIRCUIT ANALYSIS GUIDE

Q: *Can you give us a few **examples** to help illustrate this procedure?*


A:

EXAMPLE: A SIMPLE IDEAL DIODE CIRCUIT


EXAMPLE: ANALYSIS OF A COMPLEX IDEAL DIODE CIRCUIT

Linear Device Behavior

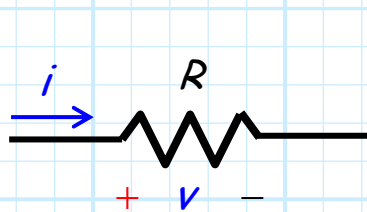
1) Recall the circuit behavior of a **resistor**:




$$i = \frac{v}{R}$$

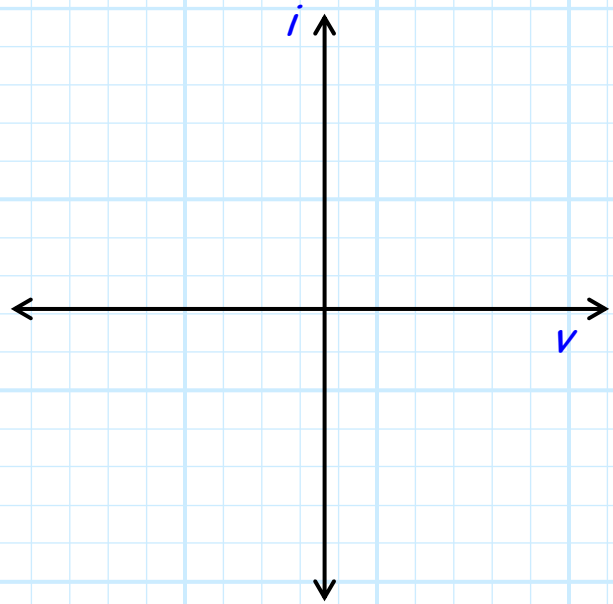

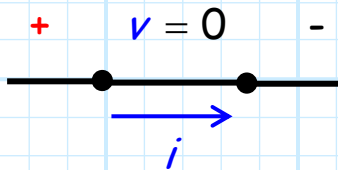
2) If $R = 0$, then we have a **short circuit**:




$$v = 0$$

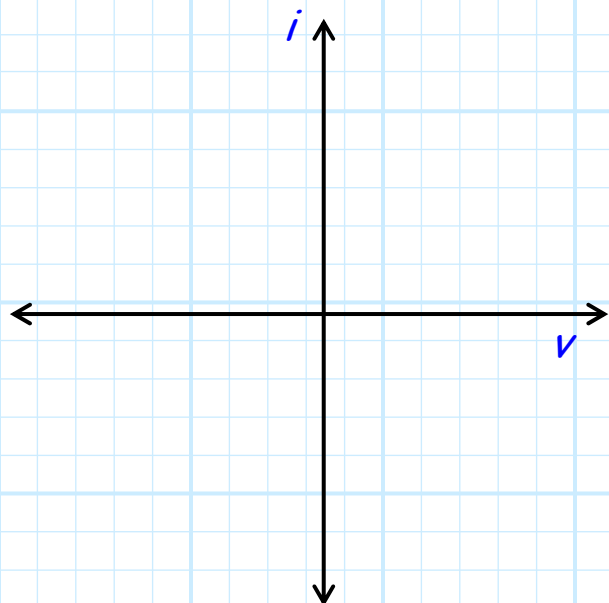




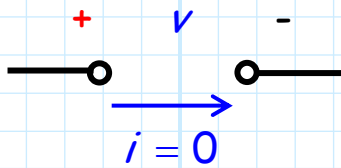
3) If $R = \infty$, then we have a **open circuit**:



$$i = 0$$

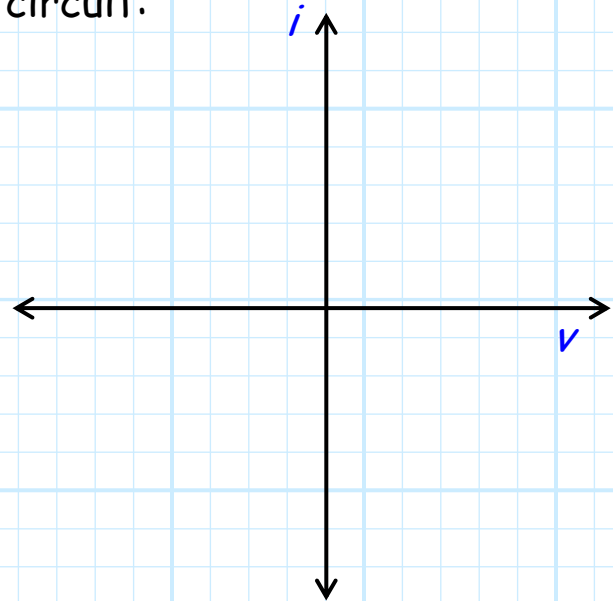

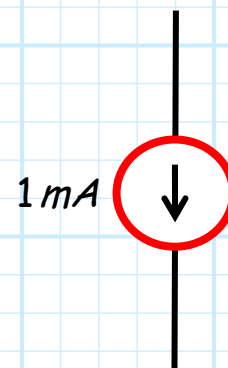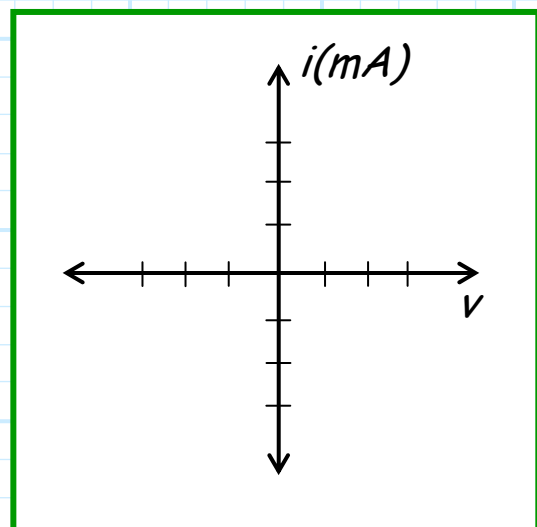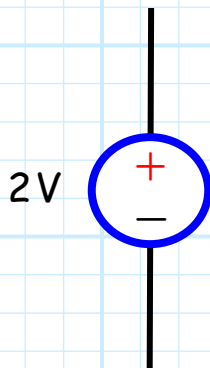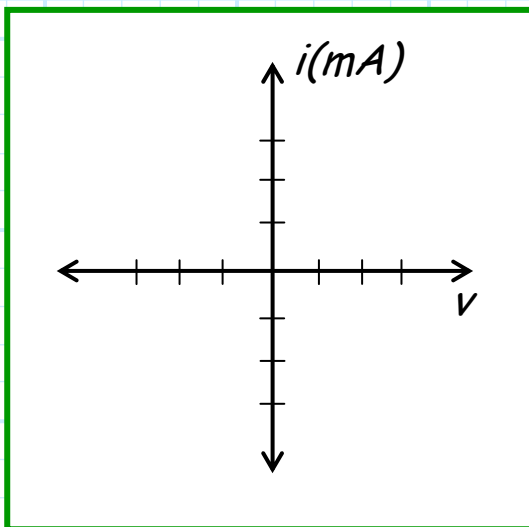4) We can also plot the behavior of both current and voltage sources:



The Ideal Diode

Diodes are perhaps the most **fundamental** of all **non-linear** circuit elements.

- * Like a resistor, inductor, or capacitor, a diode is a **two-terminal** device.
- * Thus, its behavior is characterized by the **relationship** between the **current** through the device, and the **voltage** across it.
- * Unlike **linear** two-terminal devices, the relationship between **diode** voltage and **diode** current is a little **complicated!**

To begin, we consider the **ideal diode**.




As the name implies, this device is **ideally** how a diode would behave—if we knew how to actually build an ideal diode.

Unicorns and leprechauns are more likely

Q: *You mean we're going to study a device that **doesn't really exist**? What's the point in **that**?*

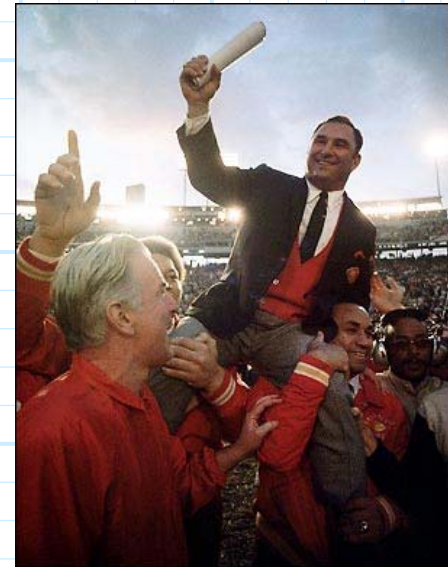A: Like **unicorns** or **leprechauns** or **Kansas City Chiefs' playoff victories**, ideal diodes are **mythical**—they only exist in our **mind**.




However, studying these **imaginary devices** is important and useful, as we will **acquire skills** necessary to understand and analyze **junction diodes**.

Junction diodes we **can** build—they **do** exist—and in many ways they behave **similarly** to ideal diodes.




It's green like a leprechaun

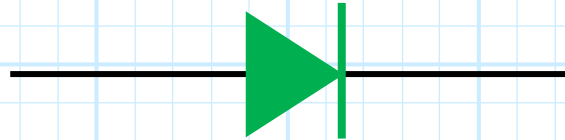
So first, the ideal diode circuit symbol:



Note that it is **asymmetric**—it has an “A” side and a “B” side!

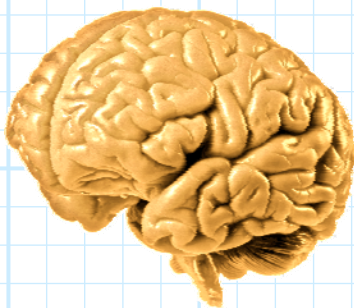One terminal is called the **anode**, and the other is called the **cathode**.




anode —  — **cathode**

Resolve to commit this to memory!

The standard ideal diode notation

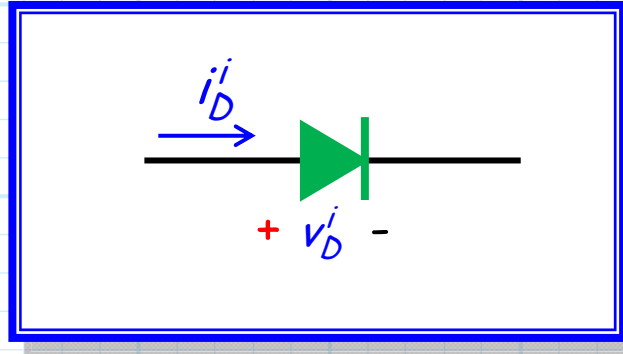With respect to the **current through** and **voltage across** this device, the **standard notation** is:



Thus, we can conclude:

1. Ideal diode current i_D is **positive**, if flowing **from the anode**, to the **cathode**.
2. Ideal diode voltage v_D is **positive**, if the **anode** potential is **greater** than the **cathode** potential.

Resolve to commit **this** to memory as well!



It's complicated in a complicated way

Q: So, what's the *relationship* between ideal diode voltage v_D^i and ideal diode current i_D^i ?

A: It's a little complicated.

Q: I see, since an ideal diode is a **non-linear** device, the ideal diode voltage and ideal diode current is **probably** related by some **crazy non-linear** function, like:


$$i_D^i = \sqrt{\pi (v_D^i)^2 - 62.3 (v_D^i)^3 + e^{v_D^i}}$$

Right?

A: It's **not** complicated like **that**; it's complicated in a **different** sort of way.

Q: ????

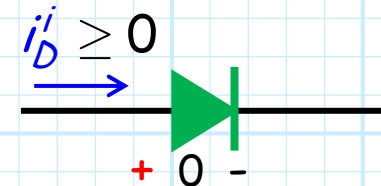
A: For an **ideal diode**, we find that **if** current is flowing from the anode to the cathode (i.e., $i_D^i \geq 0$), then the voltage across the ideal diode is **zero** (i.e., $v_D^i = 0$)—**regardless** of how much positive current is flowing:



See what I mean?

Q: *Hey! That's not complicated at all!*

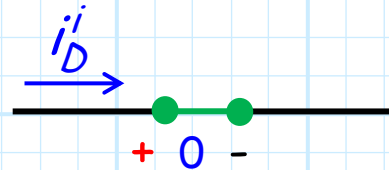*The voltage across it is zero, regardless of the current flowing through it—that describes a **short circuit**:*



Right?

A: Not exactly.

For the **voltage** across an **ideal** diode to be **zero**, the current through the ideal diode **must be positive**.

Current **must** be flowing **from** the anode **to** the cathode.

Q: *What happens if the ideal diode **current is negative**? What happens if it flows from cathode to anode?*


A: Ideal diode current **can't be negative**—it **cannot** flow from cathode to anode!

The adjective is enigmatic

Q: *Sure it can!*



Put a **negative voltage** across the ideal diode—make the cathode potential higher than the anode potential—and I'll bet you get a **bunch** of current flowing from cathode to anode.

Right?

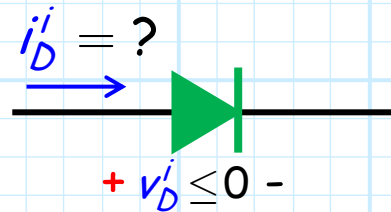

A: Wrong!

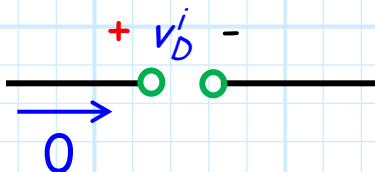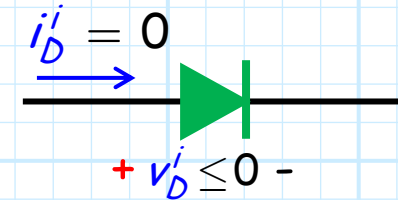It turns out, if we place a **negative voltage**—any negative voltage—across an ideal diode (i.e., $v_D^i \leq 0$), then **no current** will flow through the diode (i.e., $i_D^i = 0$):



Q: *What the heck? This now sounds like an **open circuit**—the **current** through it is **zero**, regardless of the voltage across it.*

A: Yes, but an ideal diode behaves as an **open circuit only** when the **voltage** across it is **negative**.

It's a wonderful device

So, an **ideal diode** "sort of" behaves like a **short-circuit**, and it also "sort of" behaves like an **open-circuit**.



Q: *Look, I don't know how you know these things, but if you know the device equation for this goofy component, you'll tell me.*

Tell me Clarence; please, tell me!

A: You're **not** going to like it.

There are **two** equations—and they're both **conditional**:

$$i_D^i = 0 \quad \text{if} \quad v_D^i \leq 0$$


$$v_D^i = 0 \quad \text{if} \quad i_D^i \geq 0$$

Both equations are necessary to fully describe an ideal diode—the two equations are **not inconsistent**, nor are they in **conflict**.

Plots are always helpful


Perhaps the **best way** to see this is to **plot** the expressions.

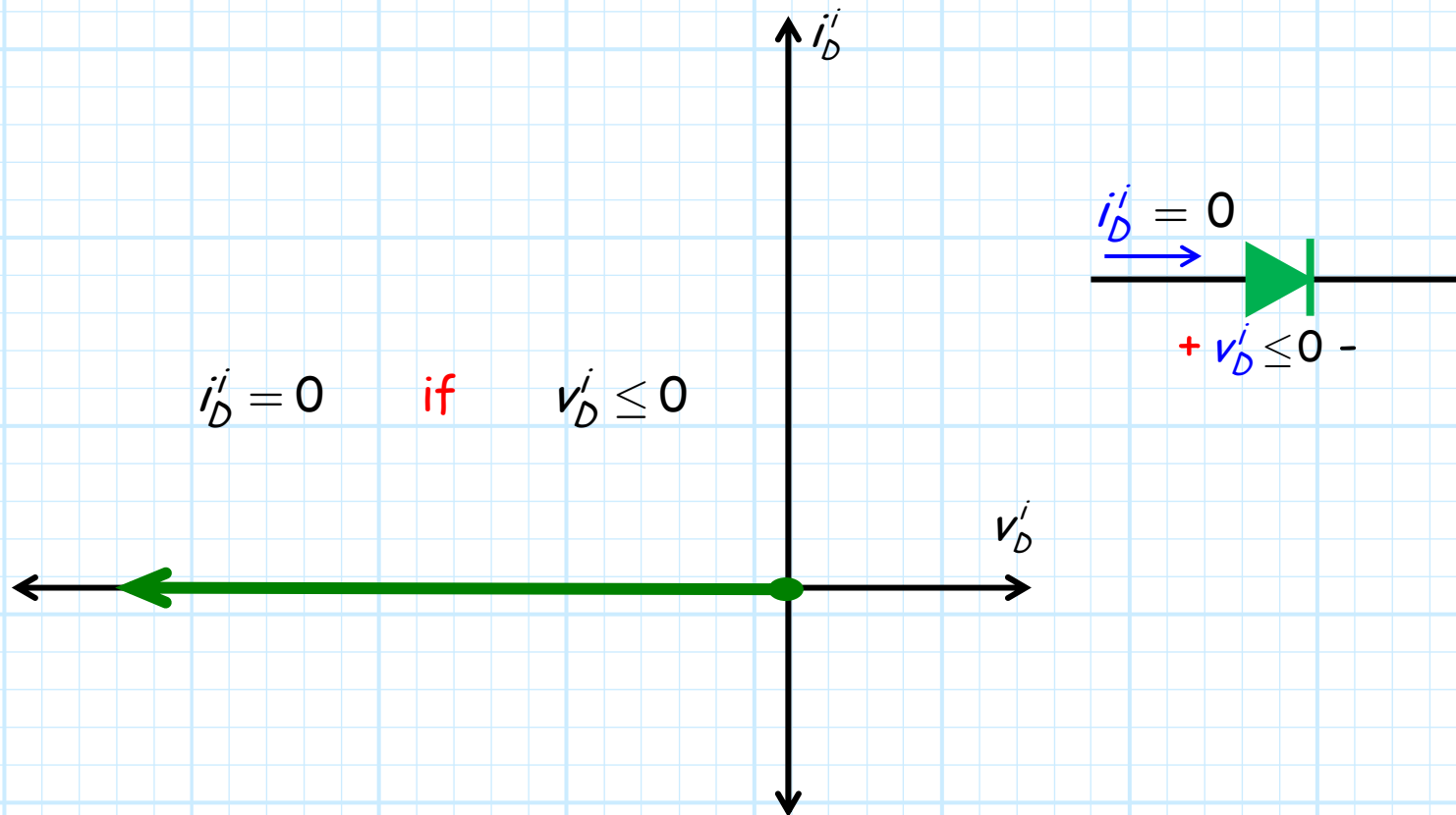The first conditional equation looks like **one-half** of the **open-circuit** "curve"




Half-a-short

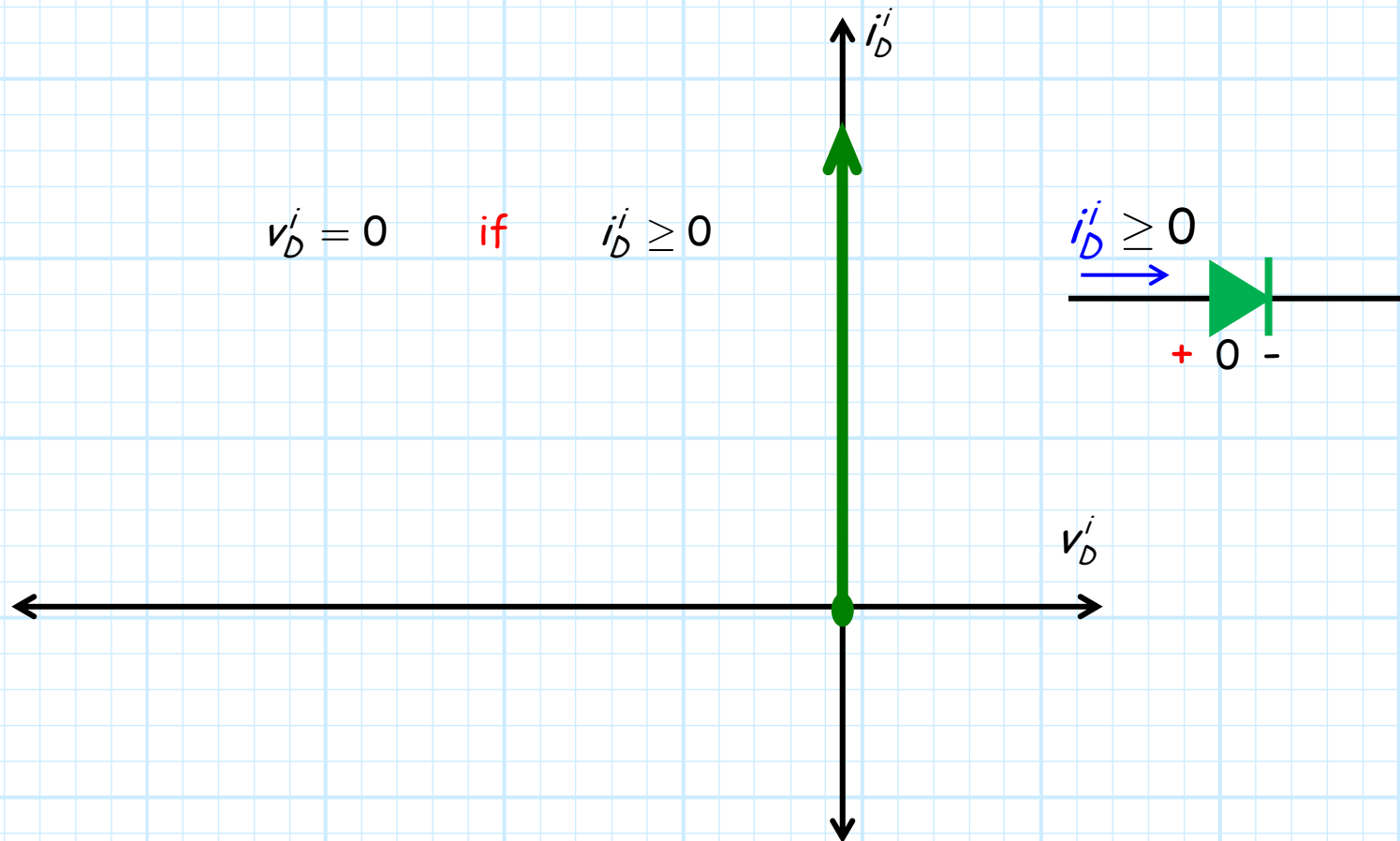The second conditional equation looks like **one-half** of the **short-circuit** "curve":



At least it's continuous

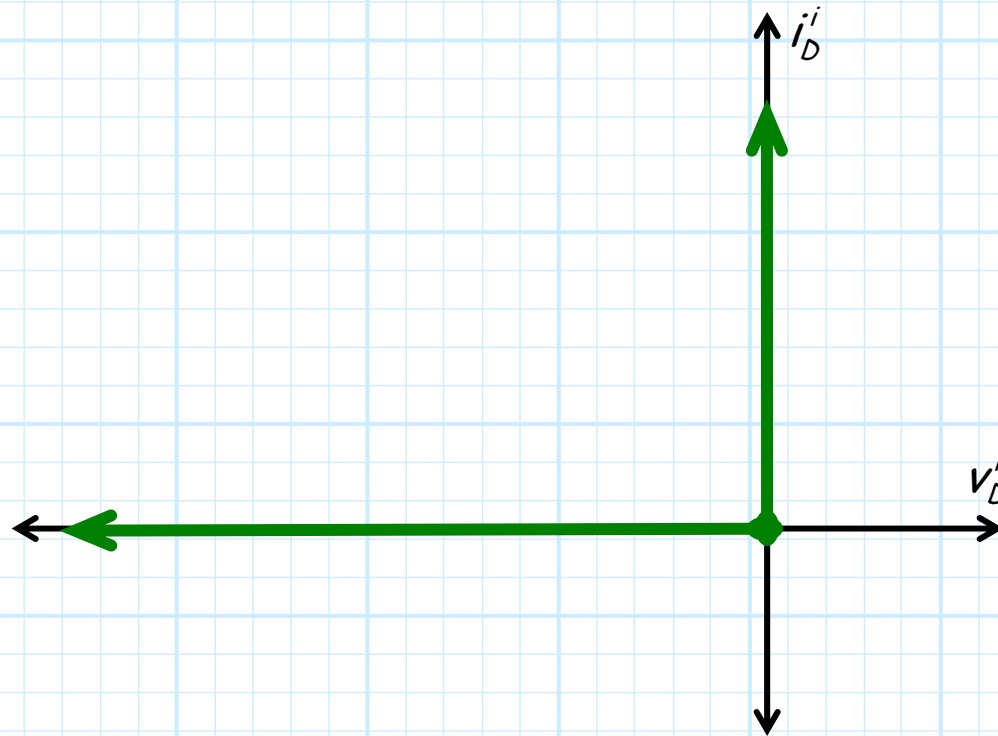Together, we see the plot for the **ideal diode** to be a **continuous** one:



The values of ideal diode **current** i_D^i and ideal diode **voltage** v_D^i must be represented by a point **on** this green "curve".

Thus, the ideal diode **voltage** can **never be positive**, and the ideal diode **current** can **never be negative**!

Because I said so

Q: *Why can't they be? Why can't I place a **positive voltage** across an ideal diode? Why can't I put a **negative current** through an ideal diode?*

A: For the same reason you can't place a **positive voltage** across a **short circuit**, or a **negative current** through an **open circuit**!

Q: *So how do we deal with these two conditional device equations?*

A: As we said, the values of ideal diode current i_D^i and ideal diode voltage v_D^i **must** be represented by a point on the green "curve".

Thus, that point will **either** be on:


1. the **vertical** line, where the ideal diode **voltage is zero** ($v_D^i = 0$), and the ideal diode **current is positive** ($i_D^i \geq 0$), or
2. the **horizontal** line, where the ideal diode **current is zero** ($i_D^i = 0$), and the ideal diode **voltage is negative** ($v_D^i \leq 0$).

They first tried to give us forwardbias43

We give each of these two possibilities a name:


Forward Bias Mode - when the ideal diode voltage is zero ($v_D^i = 0$), and the ideal diode current is positive ($i_D^i \geq 0$), or

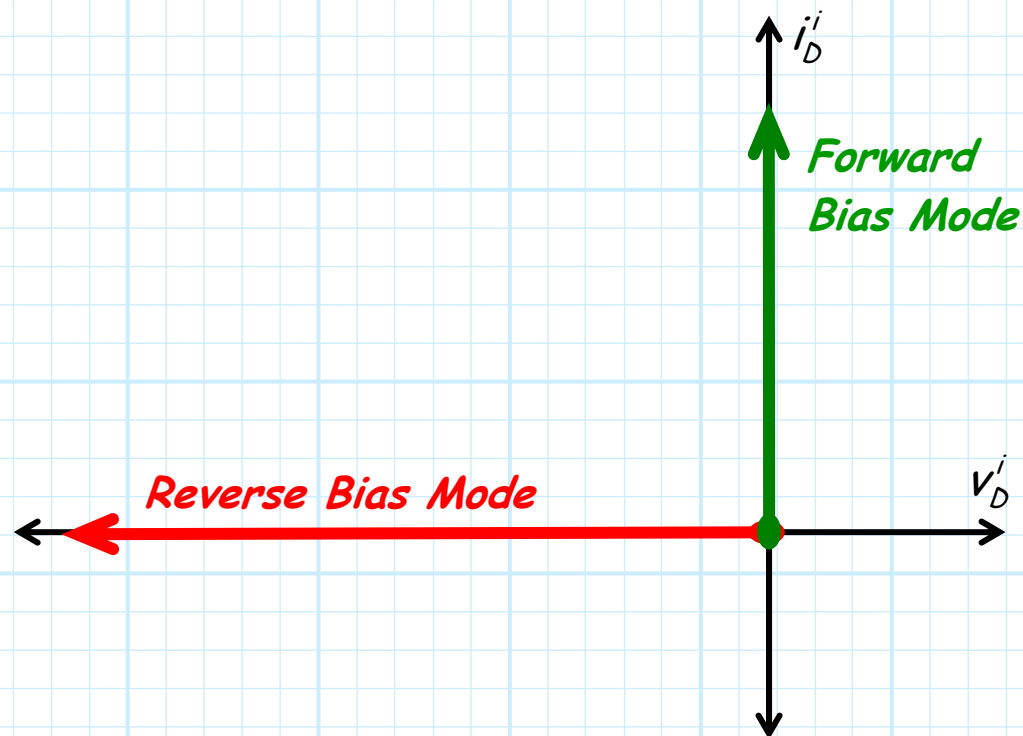Reverse Bias Mode - when the ideal diode current is zero ($i_D^i = 0$), and the ideal diode voltage is negative ($v_D^i \leq 0$).




Trust me: memorize this stuff

Commit this to memory:

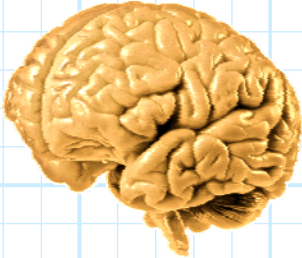

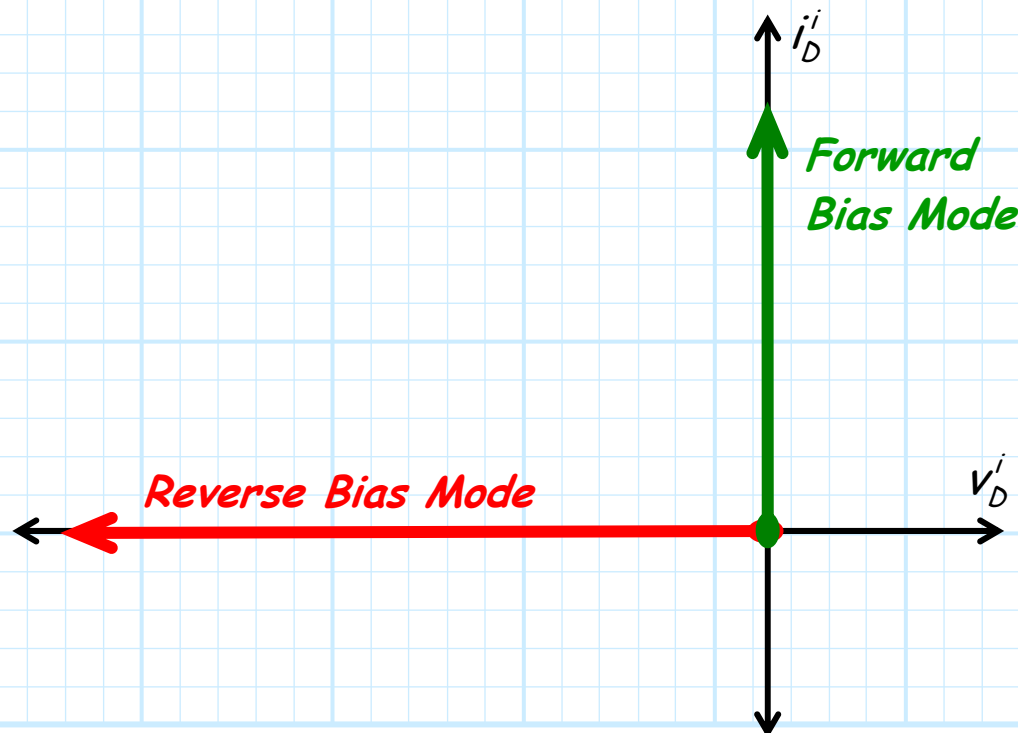
- * for the **forward bias mode**, the ideal diode "acts" like a conditional **short circuit**—the voltage across it is zero, **provided** that the **current** through it is **positive**.
- * for the **reverse bias mode**, the ideal diode "acts" like a conditional **open circuit**—the current through it is zero, **provided** that the **voltage** across it is **negative**.



Why can't you all be more like this student?

Behold the *ideal diode*—the circuit device with a split personality!

→ Is it a *short*? Or is it an *open*?

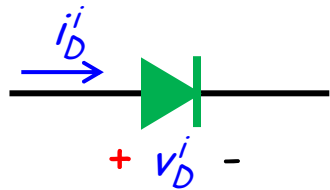

	$v_D^i < 0$	$v_D^i = 0$	$v_D^i > 0$
$i_D^i > 0$	<i>invalid</i>	forward biased	<i>invalid</i>
$i_D^i = 0$	reverse biased	no bias	<i>invalid</i>
$i_D^i < 0$	<i>invalid</i>	<i>invalid</i>	<i>invalid</i>