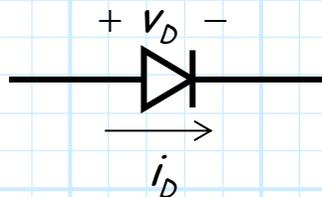


## 3.2 Terminal Characteristics of Junction Diodes (pp.147-153)

A Junction Diode -

I.E., A "real" diode!

Similar to an **ideal** diode, its circuit symbol is:



HO: The Junction Diode Curve

HO: The Junction Diode Equation

A. The Forward Bias Region

Consider when  $v_D \gg nV_T$  (i.e, when  $v_D \gg \approx 25mV$ ).

→

Note then (when  $v_D \gg \approx 25mV$ ) that  $e^{v_D/nV_T} \gg 1$ , so that a **forward biased junction diode approximation** is:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right)$$

$$\approx I_s e^{v_D/nV_T} \quad \text{for } v_D \gg nV_T$$

An exponential curve !



Example:  $I_s = 10^{-12}$ ,  $n=1$

<u><math>v_D</math> [Volts]</u>	<u><math>i_D</math></u>
---------------------------------	-------------------------

0.4

0.5

0.6

0.7

0.8

0.9

∴ A junction diode in forward bias with **significant** but **plausible** current always has a voltage  $v_D$  between **approximately 0.5V and 0.8 V!**

I.E.,  $0.5 < v_D < 0.8$  (aprox.) when in f.b.

Therefore, we often **APPROXIMATE** the **forward biased** junction diode voltage as simply:



Note that this **approximation**:

a)

b)



**HO: The Junction Diode Forward Bias Equation**

**HO: Example: A Junction Diode Circuit**

**B. The Reverse Bias Region**

Now consider when  $v_D \ll -nV_T$  (i.e, when  $v_D \ll \approx -25mV$ ).



Note then that now  $e^{v_D/nV_T} \ll 1$ , so that a **reverse biased junction diode approximation** is:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right)$$
$$\approx -I_s \quad \text{for } v_D \ll -nV_T$$

Therefore, a reverse biased junction diode has a **tiny, negative** current.



## HO: Forward and Reverse Bias Approximations

### C. The Breakdown Region

If  $v_D$  becomes too **negative**, then diode will **breakdown** (b.d.)!


\* I.E., **significant current will** flow from cathode to anode ( $i_D < 0$ !).

- \*  $v_D$  will remain at approximately  $-V_{ZK}$ , **regardless** of  $i_D$ .

Therefore, **breakdown** is describe mathematically as:



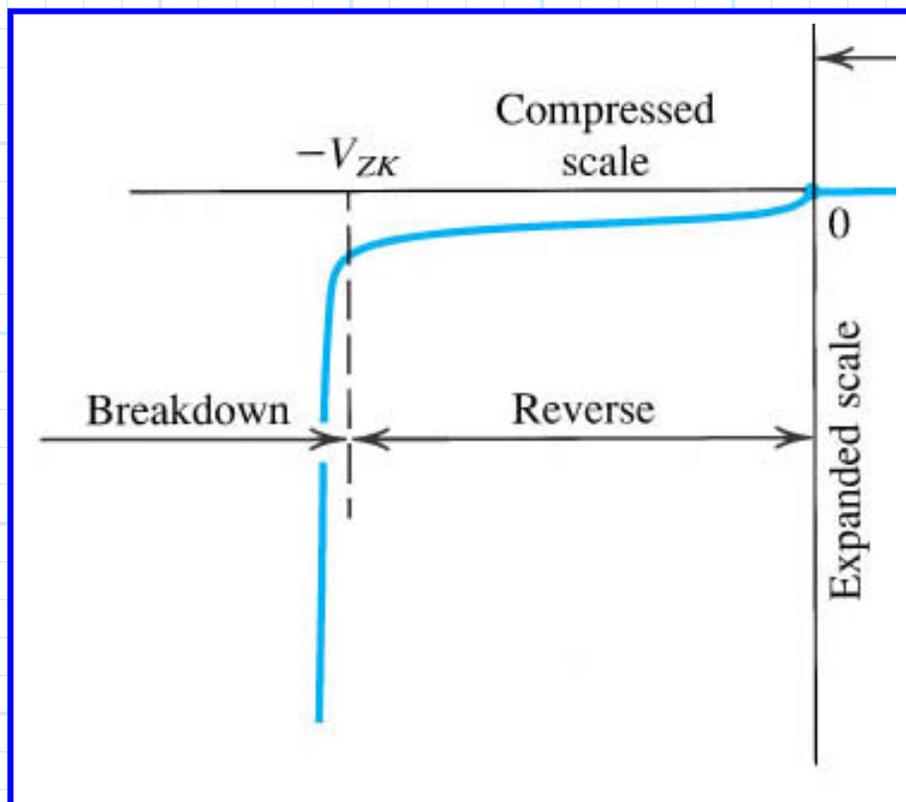Note that  $V_{ZK}$  is a "knee" voltage (i.e., value is **subjective**).



## D. Power Dissipation in Junction Diodes

Consider the **power** dissipated by a junction diode (i.e.,  
 $P = VI$ )

*f.b.* →

*r.b.* →

*b.d.* →




Thus, we typically try to **avoid** breakdown. In other words, we desire  $V_{ZK}$  to be as **big** as possible!
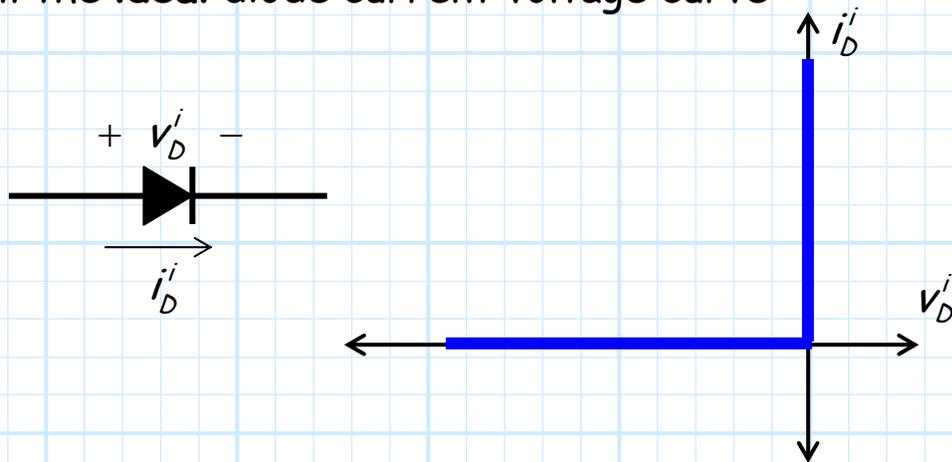
# The Junction Diode Curve


In many ways, **junction** diode (i.e., real diode) behavior is **similar** to that of ideal diodes. However, there are some important and profound **differences!**


First, recall the **ideal** diode current voltage curve:



This curve is piece-wise linear, with two **unambiguous** regions—**reverse** bias (where  $v < 0$  and  $i = 0$ ), and **forward** bias (where  $i > 0$  and  $v = 0$ ).

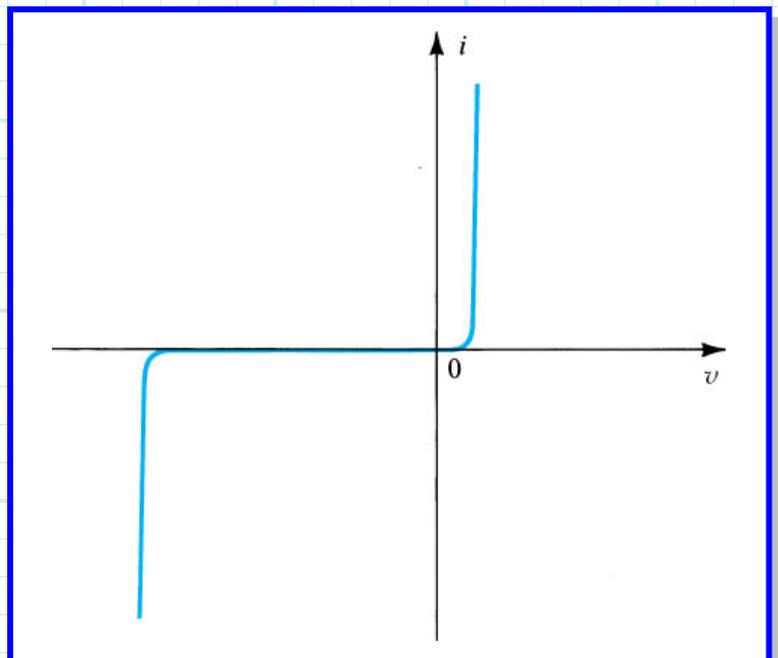Now consider the behavior of a **junction diode**:



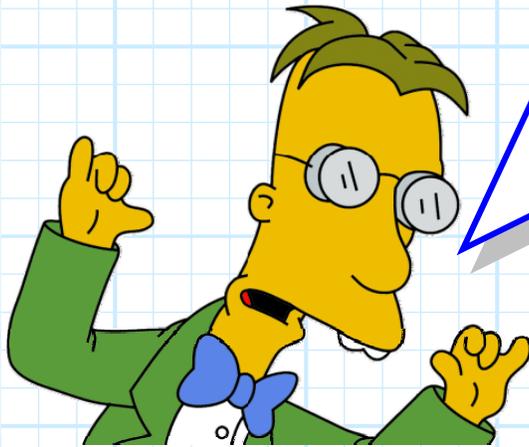


Please note that unlike the ideal diode, the **junction diode curve**:

- is **continuous** (not piece-wise linear).
- Has **three** apparent regions of operation (not two).
- Has, therefore, **ambiguous** boundaries between regions (i.e., continuous **transitions** occur between regions—the curve has two "knees"!).

By comparison to the ideal diode, we likewise define one region of the junction diode curve as the **forward bias** region, and another as the **reverse bias** region.

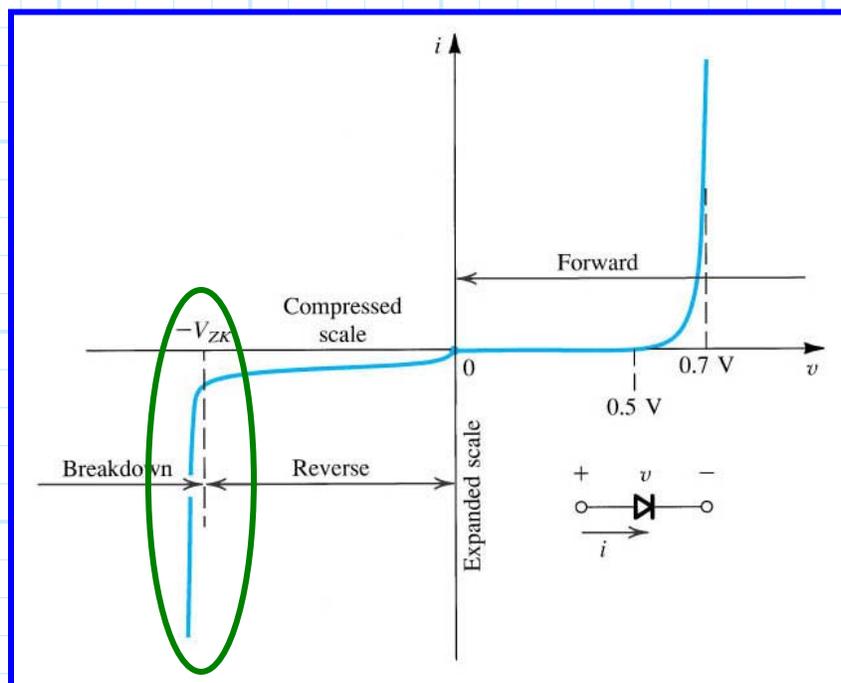The **third** region has **no similarity** with ideal diode behavior (i.e., this is a "new" region). We call this region **breakdown**.



Note that the breakdown region occurs when the junction diode voltage (from anode to cathode) is **approximately** less than or equal to a voltage value  $-V_{ZK}$ . The value  $V_{ZK}$  is known as the **zener breakdown voltage**, and is a fundamental performance parameter of any **junction diode**.

As we shall see later, the behavior of a junction diode in the forward and reverse bias region is a **predictable** result of **semiconductor physics**! As such we can write an **explicit** mathematical expression, simultaneously describing the behavior of a junction diode in **both** the forward and reverse bias regions (but **not** in breakdown!):

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right) \quad \text{for } v_D > -V_{ZK}$$

# The Junction Diode Equation

The relationship between the **current** through a **junction diode** ( $i_D$ ) and the **voltage** across it ( $v_D$ ) is:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right) \quad \text{for } v_D > -V_{ZK}$$

**Note:** this equation describes diode behavior in the forward **and** reverse biased region **only** (i.e., **not** valid for **breakdown**).

**Q:** *Good golly! Just what do those **dog-gone** parameters  $n$ ,  $I_s$  and  $V_T$  mean?*



**A:** Similar to the resistance value  $R$  of a resistor, or the capacitance  $C$  of a capacitor, these **three** parameters specify the performance of a **junction diode**. Specifically, they are:

**1.**  $I_s$  = **Saturation** (or scale) **Current**. Depends on diode material, size, and **temperature**.

**→** Typical values range from  $10^{-8}$  to  $10^{-15}$  A (i.e., **tiny**)!

2.  $V_T = \text{Thermal Voltage} = \frac{kT}{q}$

Where:

$k$  = Boltzman's Constant

$T$  = Diode Temperature ( $^{\circ}\text{K}$ )

$q$  = Charge on an electron (coulombs)



At  $20^{\circ}\text{C}$ ,  $V_T \approx 25\text{ mV}$

**IMPORTANT NOTE!**: Unless **otherwise** stated, we will **assume** that each and every junction diode is at **room temperature** (i.e.,  $T = 20^{\circ}\text{C}$ ). Thus, we will **always** assume that the **thermal voltage**  $V_T$  of **all** junction diodes is **25 mV** (i.e.,  $V_T = 25\text{ mV}$ )!

3.  $n$  = a constant called the **ideality factor** (i.e. a "fudge factor").



Typically,  $1 \leq n \leq 2$



# The Junction Diode Forward Bias Equation

In **forward bias**, we have learned that the diode current  $i_D$  can be related to the diode voltage  $v_D$  using the following **approximation**:

$$i_D = I_S \left( e^{v_D/nV_T} - 1 \right) \approx I_S e^{v_D/nV_T},$$

provided that  $v_D \gg 25 \text{ mV}$ .

We can **invert** this approximation to alternatively express  $v_D$  in terms of diode current  $i_D$ :

$$I_S e^{v_D/nV_T} = i_D$$

$$e^{v_D/nV_T} = \frac{i_D}{I_S}$$

$$\frac{v_D}{nV_T} = \ln \left( \frac{i_D}{I_S} \right)$$

$$v_D = nV_T \ln \left( \frac{i_D}{I_S} \right)$$

Now, say a voltage  $v_1$  across some junction diode results in a current  $i_1$ . Likewise, **different** voltage  $v_2$  across this same diode a diode of course results in a **different** current  $i_2$ . We can define the difference between these two voltages as  $\Delta v = v_2 - v_1$ , and then using the above equation can express this voltage difference as:

$$\begin{aligned}\Delta v &= v_2 - v_1 \\ &= nV_T \ln\left(\frac{i_2}{I_S}\right) - nV_T \ln\left(\frac{i_1}{I_S}\right) \\ &= nV_T \ln\left(\frac{i_2}{I_S} \frac{I_S}{i_1}\right) \\ \Delta v &= nV_T \ln\left(\frac{i_2}{i_1}\right)\end{aligned}$$

Yikes! Look at what this equation says:

- \* The **difference** in the two voltages is dependent on the **ratio** of the two currents.
- \* This voltage difference is **independent** of scale current  $I_S$ .

We can likewise **invert** the above equation and express the ratio of the two currents in terms of the difference of the two voltages:

$$nV_T \ln \left[ \frac{i_2}{i_1} \right] = v_2 - v_1$$

$$\ln \left[ \frac{i_2}{i_1} \right] = \frac{(v_2 - v_1)}{nV_T}$$

$$\frac{i_2}{i_1} = \exp \left[ \frac{(v_2 - v_1)}{nV_T} \right]$$

Again, we find that this expression is **independent** of scale current  $I_s$ .



**Q:** *Stop wasting my time with these pointless derivations! Are these expressions even remotely useful !?!*

**A:** These expressions are often **very** useful! Frequently, instead of explicitly providing **device parameters**  $n$  and  $I_s$ , a junction diode is specified by stating  $n$ , and then a statement of the specific diode current resulting from a specific diode voltage.

For **example**, a junction diode might be specified as:

*"A junction diode with  $n = 1$  pulls 2mA of current at a voltage  $v_D = 0.6$  V."*

The above statement **completely specifies** the performance of this particular junction diode—we can now determine the current flowing through this diode for **any** other value of diode voltage  $v_D$ . Likewise, we can find the voltage across the diode for **any** other diode current value  $i_D$ .

For **example**, say we wish to find the current through the junction diode specified above when a potential difference of  $v_D=0.7$  V is placed across it. We have **two** options for finding this current:

### Option 1:

We know that  $n=1$  and that  $i_D=2$  mA when  $v_D=0.6$  V. Thus, we can use this information to solve for **scale current**  $I_S$ :

$$I_S e^{\frac{v_D}{nV_T}} = i_D$$

$$I_S e^{\frac{0.6}{0.025}} = 2$$

$$I_S = 2 e^{\frac{-0.6}{0.025}}$$

$$I_S = 7.55 \times 10^{-11} \text{ mA}$$

**Now**, we use the forward-biased junction diode equation to determine the current through this device at the new voltage of  $v_D=0.7$  V:

$$i_D = I_S e^{\frac{v_D}{nV_T}}$$

$$= (7.55 \times 10^{-11}) e^{\frac{0.7}{0.025}}$$

$$= 109.2 \text{ mA}$$

## Option 2

Here, we directly determine the current at  $v_D = 0.7$  using one of the expressions derived earlier in **this** handout! Using  $i_1 = 2 \text{ mA}$  and  $v_1 = 0.6$  we can state the relationship between current  $i_2$  as and voltage  $v_2$  as:

$$\begin{aligned} i_2 &= i_1 \exp\left[\frac{(v_2 - v_1)}{nV_T}\right] \\ &= 2 \exp\left[\frac{(v_2 - 0.6)}{0.025}\right] \end{aligned}$$


For  $v_2 = 0.7 \text{ V}$  we can therefore find current  $i_2$  as:

$$\begin{aligned} i_2 &= 2 \exp\left[\frac{(0.7 - 0.6)}{0.025}\right] \\ &= \mathbf{109.2 \text{ mA}} \end{aligned}$$

Option 2 (using the equations we derived in this handout) is obviously **quicker** and **easier** (note in option 2 we did **not** have to deal with **annoying numbers** like  $7.55 \times 10^{-11}$ !).

Finally, we should also note that junction diodes are often specified **simply** as "a 2mA diode" or "a 10 mA diode" or "a 100 mA diode". These statement **implicitly** provide the diode current at the **standard** diode test voltage of  $v_D = 0.7 \text{ V}$ .

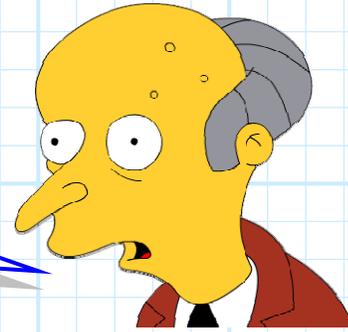**Q:** *But what about the value of junction diode ideality factor  $n$ ?*



**A:** If no value of  $n$  is provided (and there is not sufficient information given to determine it), we typically just **assume** that  $n = 1$ .

For **example**, consider the following problem:

*"Determine the voltage across a 100 mA junction diode when there is 2 mA of current flowing through it."*

A "100 mA junction diode" simply means a junction diode that will have a current of 100 mA flowing through it ( $i_D = 100$  mA) if the voltage across it is  $v_D = 0.7$  V. We will **assume** that  $n = 1$ , since no other information about that parameter was given.

Thus, using  $v_1 = 0.7$ ,  $i_1 = 100$  mA, and  $i_2 = 2$  mA, we can determine the value of  $v_2$ :

$$v_2 - v_1 = nV_T \ln\left(\frac{i_2}{i_1}\right)$$

$$v_2 - 0.7 = (0.025) \ln\left(\frac{2}{100}\right)$$


$$\begin{aligned} v_2 &= 0.7 - 0.10 \\ &= 0.60 \text{ V} \end{aligned}$$

**EXCELLENT!**


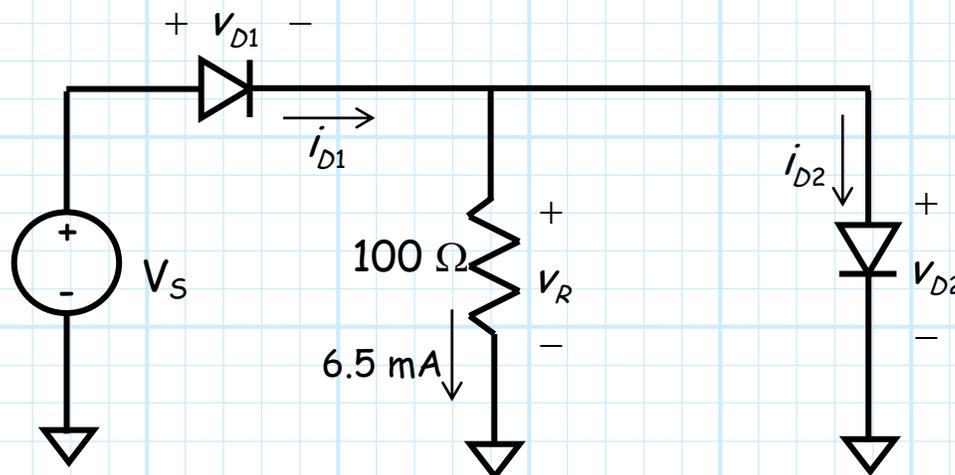
# Example: A Junction Diode Circuit

Consider the following circuit with two junction diodes:




The diodes are identical, with  $n = 1$  and  $I_S = 10^{-14}\ \text{A}$ .

**Q:** *If the current through the resistor is  $6.5\ \text{mA}$ , what is the voltage of source  $V_S$ ??*

**A:** This is a **difficult** problem to solve ! Certainly, we cannot just write:

$$V_S =$$

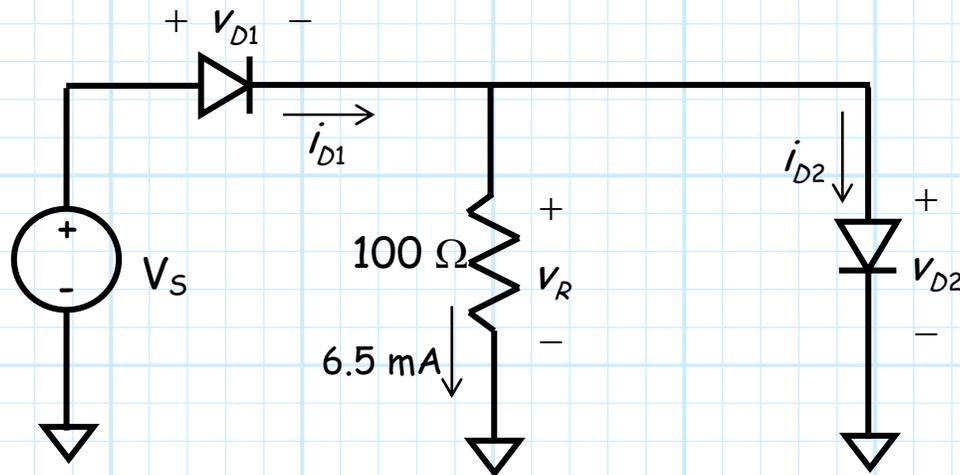and then the answer. Instead, let's just determine **what we can**, and see what happens !



1) If 6.5 mA flows through a 0.1 K resistor, the voltage across that resistor is:

$$V_R = 0.1(6.5) = 0.65 \text{ V}$$

2) If the voltage across the resistor is 0.65 V, then the voltage across the diode  $D_2$ , which is **parallel** to the resistor, is the **same** value:


$$V_{D2} = V_R = 0.65 \text{ V}$$

3) If we know the **voltage** across a p-n junction diode, then we also know its **current** !

$$i_{D2} = I_S \exp\left[\frac{V_{D2}}{nV_T}\right] = 10^{-14} \exp\left[\frac{0.650}{0.025}\right] = 1.96 \text{ mA}$$

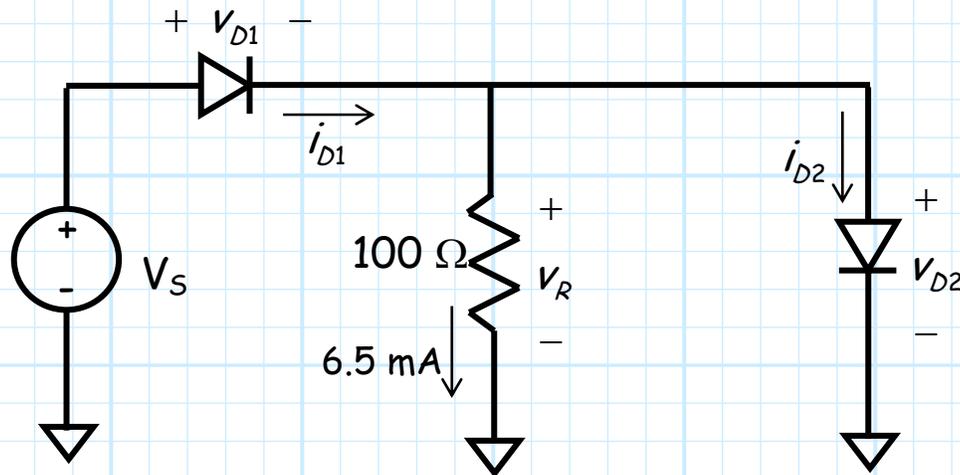4) If we know  $i_{D2}$  and the current through the resistor, we know (using KCL) the current through  $D_1$  :

$$\begin{aligned} i_{D1} &= 6.5 + i_{D2} \\ &= 6.5 + 1.96 \\ &= 8.46 \text{ mA} \end{aligned}$$



1) If 6.5 mA flows through a 0.1 K resistor, the voltage across that resistor is:

$$V_R = 0.1(6.5) = 0.65\ \text{V}$$

2) If the voltage across the resistor is 0.65 V, then the voltage across the diode  $D_2$ , which is **parallel** to the resistor, is the **same** value:


$$V_{D2} = V_R = 0.65\ \text{V}$$

3) If we know the **voltage** across a p-n junction diode, then we also know its **current** !

$$i_{D2} = I_S \exp\left[\frac{V_{D2}}{nV_T}\right] = 10^{-14} \exp\left[\frac{0.650}{0.025}\right] = 1.96\ \text{mA}$$

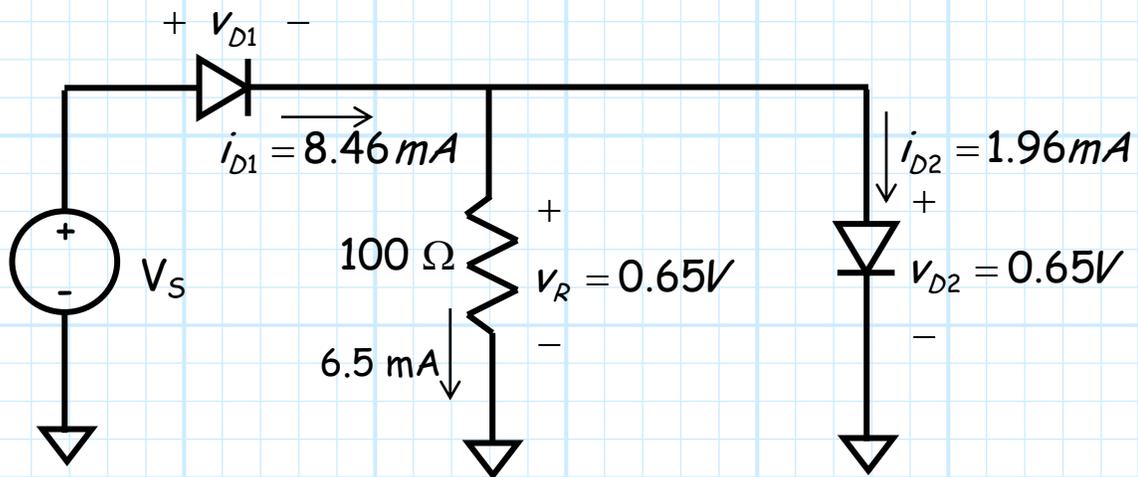4) If we know  $i_{D2}$  and the current through the resistor, we know (using KCL) the current through  $D_1$  :

$$\begin{aligned} i_{D1} &= 6.5 + i_{D2} \\ &= 6.5 + 1.96 \\ &= 8.46\ \text{mA} \end{aligned}$$




- 5) If we know the **current** through a junction diode, then we can find the **voltage** across it:

$$v_{D1} = nV_T \ln\left(\frac{i_{D1}}{I_S}\right) = 0.025 \ln\left(\frac{0.00846}{10^{-14}}\right) = 0.69V$$

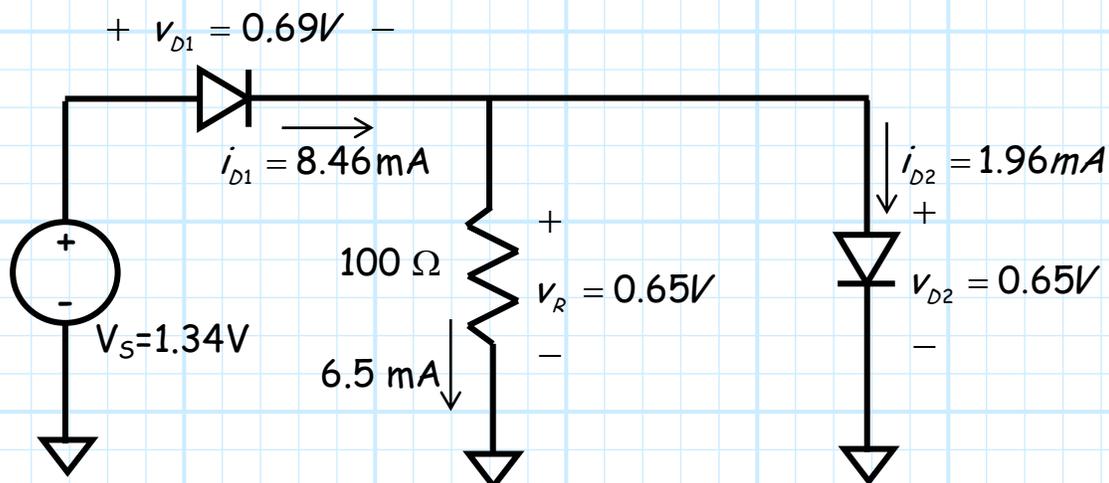- 6) Finally, if we know  $v_{D1}$  and  $v_{D2}$ , we can find  $V_S$  using KVL:

$$V_S = v_{D1} + v_{D2} = 0.69 + 0.65 = 1.34V$$



# Forward and Reverse Bias Approximations



**Q:** Man, am I ever *befuddled*! Is the behavior of a junction diode in the *forward biased* region described as *this*:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right) ?$$

or as *this*:

$$i_D = I_s e^{v_D/nV_T} ?$$

or as *this*

$$i_D > 0 \quad \text{and} \quad v_D = 0.7 \text{ V} ???$$

**A:** Actually, **all three** of the above statements are true (or, at least, **approximately** so)!

Let's **review** what we know about the junction diode in forward and reversed bias:

**1.** First, we know that if the diode is **not** in breakdown, the relationship between current and voltage can be precisely described as:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right) \quad \text{for} \quad v_D > -V_{ZK}$$

**Q:** *Here's where I get confused. Is this equation valid for reverse bias, or is it valid for forward bias?*

**A:** The above expression is valid for forward bias, **and** it is valid for reverse bias, **and** it is also valid for the transition region between forward and reverse bias!



In other words, the above equation is a **very accurate** description of the junction diode behavior—with the important **exception** of when the junction diode is in **breakdown**.

**2.** Now, let's **simplify** the previous expression further, **separately** examining the cases when the junction diode is in forward bias (i.e.,  $v_D \gg nV_T$ ), and reverse bias (i.e.,  $-V_{ZK} < v_D \ll -nV_T$ ).

For the **forward bias** case, we find that:

$$e^{v_D/nV_T} \gg 1 \quad \text{if} \quad v_D \gg nV_T$$

Therefore, we can approximate the junction diode behavior in **forward bias** mode as:

$$i_D \approx I_s e^{v_D/nV_T} \quad \text{for} \quad v_D \gg nV_T \quad (\text{i.e., forward biased})$$

Likewise, for the **reverse bias** case, we find that:

$$e^{v_D/nV_T} \ll 1 \quad \text{if} \quad v_D \ll -nV_T$$

Therefore, we can approximate the junction diode behavior in **reverse bias** mode as:

$$i_D \approx -I_s \quad \text{for} \quad -V_{ZK} < v_D \ll -nV_T \quad (\text{i.e., reversed biased})$$

Combining, we can approximate the expression at the top of the previous page as:

$$i_D \approx \begin{cases} I_s e^{v_D/nV_T} & \text{for} \quad v_D \gg nV_T \quad (\text{i.e., forward biased}) \\ -I_s & \text{for} \quad -V_{ZK} < v_D \ll -nV_T \quad (\text{i.e., reversed biased}) \end{cases}$$

**3.** We can now simplify these expressions even **further!** We rewrite the above approximation for forward bias so that the junction diode **voltage** is a function of junction diode current:

$$I_s e^{v_D/nV_T} = i_D$$

$$e^{v_D/nV_T} = \frac{i_D}{I_s}$$

$$\frac{v_D}{nV_T} = \ln \left[ \frac{i_D}{I_s} \right]$$

$$v_D = nV_T \ln \left[ \frac{i_D}{I_s} \right]$$

As a previous example demonstrated, as we vary the value of diode **current**  $i_D$  from microamps to kiloamps, the diode voltage will vary **only** a few hundred millivolts, from about 0.5 V to 0.9 V.

Thus, we can assume that if any appreciable current is flowing from junction diode anode to junction diode cathode (i.e., forward bias condition), the junction diode voltage will be **approximately** (i.e., within a few hundred millivolts) **0.7 V**.

**Q:** *It looks to me that you are saying a **forward biased** junction diode exhibits a diode voltage of  $v_D = 700\text{mV}$ , regardless of the diode current  $i_D$ , right?*



**A:** **NO!** This is **not** what I am saying! As is evident in the previous two equations, the junction diode current in forward bias is directly **dependent** on diode current—as the **current** increases, the **voltage** increases! For each possible diode **current**, there is a **specific** (and different) diode **voltage**.

- \* However, we find that this increase is **logarithmically** related to diode current, such that the voltage increases very **slowly** with increasing current—it takes a **bunch** of additional junction diode current to increase the junction diode voltage even a **small** amount.
- \* Thus, we are simply saying that for all appreciable (and plausible) diode currents, the junction diode voltage will be within of few hundred millivolts of, say, 700 mV.
- \* As a result,  $v_D = 0.7 \text{ V}$  is not a bad **approximation** for **forward biased** junction diodes!

Now, we can likewise simplify further our approximation for a **reverse biased** junction diode. Recall that we now approximate the reverse bias diode current as  $i_D = -I_s$ .

However, recall that the diode saturation current  $I_s$  is a very small value, typically  $10^{-8}$  to  $10^{-15}$  Amps!



**Q:** *A billionth of an amp!? That's so tiny it might as well be zero!*

**A: Precisely!** The reverse bias current value  $i_D = -I_s$  is so small that we can approximate it as **zero**:

$$i_D \approx 0 \quad \text{if} \quad -V_{ZK} < v_D \ll -nV_T \quad (\text{reverse bias})$$

Thus, we arrive at an **even simpler** (albeit **less accurate**) approximation of junction diode behavior in forward and reverse bias:

$$v_D \approx 0.7 \quad \text{if} \quad i_D > 0 \quad (\text{forward bias})$$

$$i_D \approx 0 \quad \text{if} \quad -V_{ZK} < v_D < 0 \quad (\text{reverse bias})$$

Each of the **three** expressions examined in this handout can be used to describe the behavior of junction diodes in **forward** and/or **reverse** bias. The **first** expression we examined is the **most** accurate, but it is likewise the most mathematically **complex**. Conversely, the **third** expression above is the **simplest**, but is likewise the **least** accurate.

We will find that **all** three of the expressions are **useful** to us, depending on **what** specifically we are attempting to determine, and how **accurately** we need to determine it!

