

# 1.7 Digital Logic Inverters

Reading Assignment: *pp. 40-48*

Consider the **ideal** digital logic inverter.

Q:

A: HO: The Ideal Inverter

Q:

A:

HO: Noise Margins


HO: Power Dissipation

HO: Propagation Delay

HO: The Delay-Power Product
 
# The Ideal Inverter

**Q:** How would the "perfect" inverter behave?



**A:** Clearly, if  $v_I = 0$ , then  $v_O = V^+$ , and if  $v_I = V^+$ , then  $v_O = 0$ .

$v_I$	$v_O$
0	$V^+$
$V^+$	0

But what happens if  $v_I$  is **not** equal to precisely 0.0 or  $V^+$  ??

In other words, what is the **ideal transfer function**  $v_O = f(v_I)$  of a digital inverter?

For example, say  $V^+ = 5V$ . How should the inverter respond to  $v_I = 1V$ , or  $v_I = 2V$ , or  $v_I = 4V$  ??

Since  $v_I = 1V$  and  $v_I = 2V$  are closer to  $0.0 V$  (low level) than they are to  $5.0 V$  (high level), the inverter **should** interpret them as **low** inputs and the output should then be placed precisely at the high state  $v_O = 5V$ .


Similarly, for  $v_I = 4V$ , the inverter **should** interpret it as **high** input and thus the output should be placed precisely at the low state  $v_O = 0V$ .

Therefore, we can say that an **ideal** digital inverter will interpret **input** values **less** than  $V^+/2$  (i.e.,  $< 2.5 V$ ) as **low** inputs, and thus produce an **ideal output** of  $V^+$  (i.e.,  $5.0 V$ ).

Likewise, any **input** values **greater** than  $V^+/2$  (i.e.,  $>2.5 V$ ) will be interpreted as a **high** input, and thus an **ideal low** value of  $0.0 V$  will be placed at the output.

Thus, the **ideal transfer function** for a digital inverter is:
 
$$v_O = \begin{cases} V^+ & \text{if } v_I < V^+ / 2 \\ 0 & \text{if } v_I > V^+ / 2 \end{cases}$$



By the way, the ideal inverter has **noise margins (NM)** of:

$$NM = \frac{V^+}{2}$$

This is the **largest possible** noise margin, therefore the **ideal noise margin!**




**Q:** *Arrgh! Just what is exactly is a "noise margin"?*

**A:** The subject of the **next** handout!
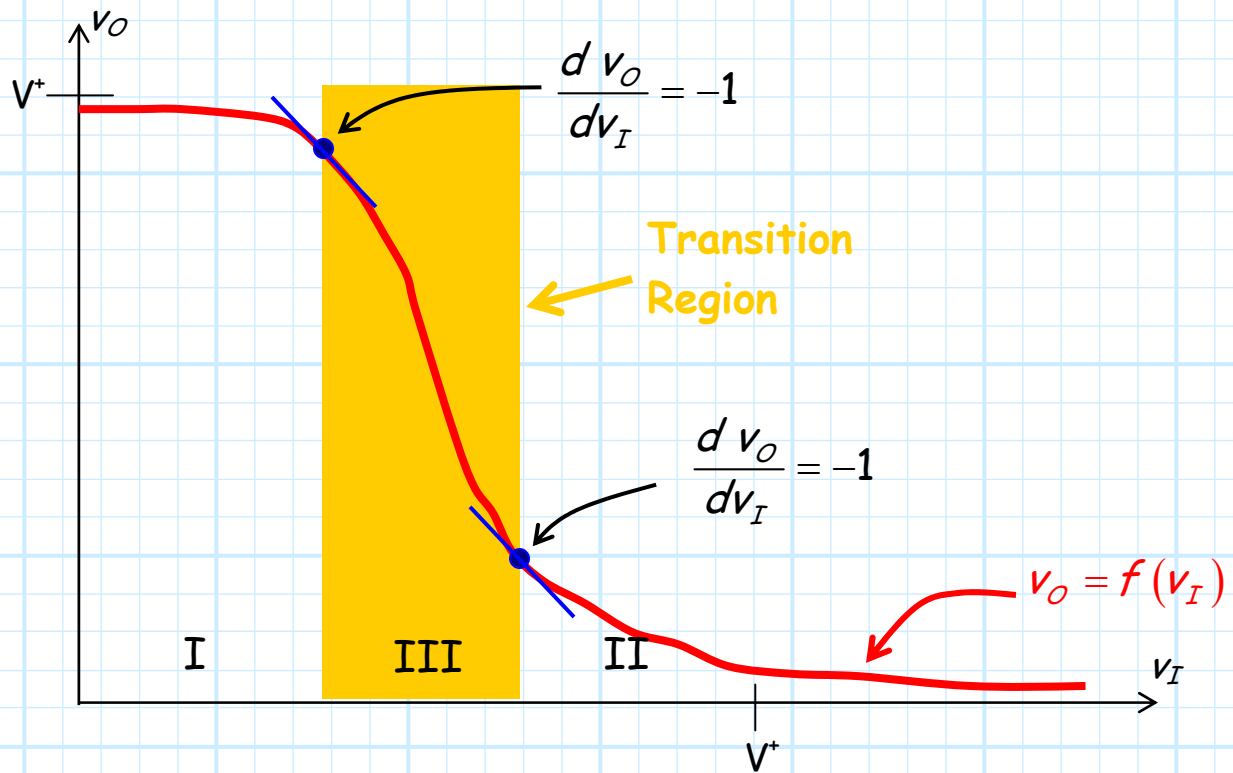
# Noise Margins

The transfer function of a digital inverter will typically look something like this:



Note that there are essentially **three** regions to this curve:

- I.** The region where  $v_I$  is relatively **low**, so that the output voltage  $v_O$  is **high**.
- II.** The region where  $v_I$  is relatively **high**, so that the output voltage  $v_O$  is **low**.
- III.** The **transition region**, where the input/output voltage is in an **indeterminate state** (i.e., an **ambiguous** region between high and low).

Note that the **transition region** is rather **arbitrarily** defined by the points on the transfer function where the magnitude of the **slope** is **greater than one** (i.e., where  $|dv_O/dv_I| > 1.0$ ).

Although this transfer function **looks** rather simple, there are actually **several parameters** that we use to **characterize** this transfer function—and thus characterize the digital inverter **as well!**

**1.** First of all, let's consider the case when  $v_I=0$ . The **output** of the digital inverter in this condition is **defined** as  $V_{OH}$  (i.e., OH  $\rightarrow$  "output high"), i.e.:


$$V_{OH} \doteq v_O \text{ when } v_I = 0$$

Thus,  $V_{OH}$  is essentially the "**ideal**" inverter **high** output, as it is the output voltage when the inverter input is at its ideal low input value  $v_I=0$ . Typically,  $V_{OH}$  is a value just **slightly** less than supply voltage  $V^+$ .

 **2.** Now, let's consider the case when  $v_I=V^+$ . The output of the digital inverter in this condition is **defined** as  $V_{OL}$  (i.e., OL  $\rightarrow$  "output low"), i.e.:

$$V_{OL} \doteq v_O \text{ when } v_I = V^+$$

Thus,  $V_{OL}$  is essentially the "ideal" inverter low output, as it is the output voltage when the inverter input is at its ideal high input value  $v_I = V^+$ . Typically,  $V_{OL}$  is a value just **slightly** greater than 0.



3. The "boundary" between region I and the transition region of the transfer function is denoted as  $V_{IL}$  (i.e., IL  $\rightarrow$  "input low"). Specifically, this is the value of the **input** voltage that corresponds to the **first** point on the transfer function where the **slope** is equal to -1.0 (i.e., where  $dv_O/dv_I = -1.0$ ).


Effectively, the value  $V_{IL}$  places an **upper bound** on an acceptably "low" value of input  $v_I$ —any  $v_I$  **greater** than  $V_{IL}$  is **not** considered to be a "low" input value. I.E.:

$v_I$  considered "low" only if  $v_I < V_{IL}$

 4. Likewise, the "boundary" between region II and the transition region of the transfer function is denoted as  $V_{IH}$  (i.e., IH  $\rightarrow$  "input high"). Specifically, this is the value of the input voltage that corresponds to the **second** point on the transfer function where the **slope** is equal to -1.0 (i.e., where  $dv_o/dv_I = -1.0$ ).

Effectively, the value  $V_{IH}$  places a **lower bound** on an acceptably "high" value of input  $v_I$ —any  $v_I$  **lower** than  $V_{IH}$  is **not** considered to be a "high" input value. I.E.:

$v_I$  considered "high" only if  $v_I > V_{IH}$





Note then that the **input** voltages of the **transition region** (i.e.,  $V_{IL} < v_I < V_{IH}$ ) are **ambiguous** values—we **cannot** classify them as either a digital “low” value or a digital “high” value.

Accordingly, the **output** voltages in the transition region are both significantly less than  $V_{OH}$  and significantly larger than  $V_{OL}$ . Thus, the **output** voltages that occur in the transition region are **likewise ambiguous** (cannot be assigned a logical state).

**Lesson learned** → Stay away from the transition region!

In other words, we must ensure that an **input** voltage representing a logical “low” value is **significantly lower** than  $V_{IL}$ , and an **input** voltage representing a logical “high” value is **significantly higher** than  $V_{IH}$ .




**Q:** *Seems simple enough! Why don't we **end** this exceedingly dull handout and **move on** to something more interesting!?*



**A:** Actually, staying **out** of the transition region is sometimes **more difficult** than you might first imagine!

The reason for this is that in a **digital system**, the devices are **connected** together—the input of one device is the output of the other, and vice versa.

For example:

 

  Say that the **input** to the **first** digital inverter is  $v_{I1} = V^+$ . The **output** of that inverter is therefore  $v_{O1} = V_{OL}$ . Thus, the **input** to the **second** inverter is **likewise** equal to  $V_{OL}$  (i.e.,  $v_{I2} = v_{O2} = V_{OL}$ ).




**Q:** *So? This doesn't seem to be a problem—after all, isn't  $V_{OL}$  much lower than  $V_{IL}$ ??*

**A:** True enough! The input  $v_{I2}=V_{OL}$  is typically **well below** the maximum acceptable value  $V_{IL}$ . In fact, we have a specific name for the **difference** between  $V_{IL}$  and  $V_{OL}$ —we call this value **Noise Margin (NM)**:


$$NM_L = V_{IL} - V_{OL} \quad [Volts]$$

The noise margin essentially tells us **how close** we are to the **ambiguous** transition region for a typical case where  $v_I = V_{OL}$ . Of course, we do **not** wish to be close to this transition region at all, so **ideally** this noise margin is **very large**!

 Now, consider the **alternate** case where  $v_{I1}=0.0$  V. The **output** of the **first** inverter is therefore  $v_{O1} = V_{OH}$ . Thus, the **input** to the **second** inverter is **likewise** equal to  $V_{OH}$  (i.e.,  $v_{I2} = v_{O2} = V_{OH}$ ).



 **Q:** *This still doesn't seem to be a problem—after all, isn't  $V_{OH}$  much larger than  $V_{IH}$ ??*




**A:** Again, this is **true** enough! The input  $v_{I2}=V_{OH}$  is typically **well** above the minimum acceptable value  $V_{IH}$ . We can **again** specify the **difference** between  $V_{IH}$  and  $V_{OH}$  as a **noise margin** (NM):


$$NM_H = V_{OH} - V_{IH} \quad [Volts]$$

This **noise margin** essentially tells us how **close** we are to the ambiguous **transition region** for a typical case where  $v_I = 0.0V$ . Of course, we do **not** wish to be close to this transition region at all, so ideally this noise margin is **very large**!

 
**Q:** *I don't see why we care about the values of these "noise margins". Isn't the simple fact that  $V_{OL} < V_{IL}$  and  $V_{OH} > V_{IH}$  sufficient?*



 **A:** **Ideally** yes. However, in our example we have made one important **assumption** that in fact may **not** be true! It turns out that in a **real** digital circuit,  $v_{I2}$  may **not** be equal to  $v_{O1}$  !!



 **Q:** *What! How can this be possible? It appears to me that  $v_{I2}$  **must** be equal to  $v_{O1}$  !?*




**A:** It turns out that for a **real** digital circuit, a lot can happen **between** the output of one device and the input to another. The voltage at the input of a device might be affected by **many** sources—**only one** of which is the output device connected to it!

Examples of these “**extra**” sources include:

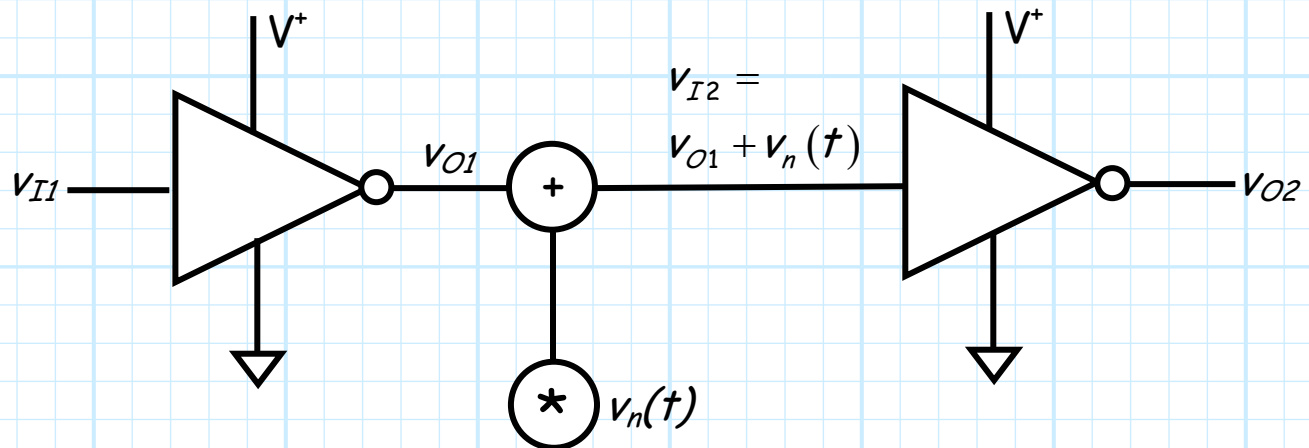
1. Thermal **noise**
2. Coupled signals
3. Power supply **transients**

We will **combine** the effect of **all** of these sources together into one “**noise**” source  $v_n(t)$ . Thus, a **better model** for our digital circuit example is:



Now, let's **reconsider** the case where  $V_{I1} = V^+$ . We find that the **input** to the **second** digital inverter is then

$$V_{I2} = V_{OL} + v_n(t):$$

 

Now we see the **problem!** If the **noise** voltage is **too large**, then the **input** to the **second** inverter will **exceed** the maximum low input level of  $V_{IL}$ —we will have entered the dreaded **transition region!!!!**

To **avoid** the transition region, we find that the **input** to the **second** inverter must be less than  $V_{IL}$ :

$$V_{OL} + v_n(t) < V_{IL}$$

$$v_n(t) < V_{IL} - V_{OL}$$

$$v_n(t) < NM_L$$

**Look** at what this means! It says to avoid the transition region (i.e., for the input voltage to have an unambiguously "low" digital level), the **noise** must be **less** than **noise margin**  $NM_L$  for **all time** !

Thus, if the **noise margin**  $NM_L$  is **large**, the noise  $v_n(t)$  can be large **without** causing any deleterious effect (deleterious effect  $\rightarrow$  transition region). Conversely, if the noise margin  $NM_L$  is **small**, then the noise **must** be small to avoid **ambiguous** voltage levels.

**Lesson learned**  $\rightarrow$  **Large noise margins are very desirable!**

Considering **again** the example circuit, only this time with  $v_I = 0.0$  V, we find that to **avoid** the transition region (verify this for yourself!):

$$V_{OH} + v_n(t) > V_{IH}$$

$$v_n(t) > V_{IH} - V_{OH}$$

$$v_n(t) > -NM_H$$

$$-v_n(t) < NM_H$$

Note that the noise  $v_n(t)$  is **as likely** to be positive as negative—it is in fact **negative** valued noise that will send  $v_{I2}$  to a value **less** than  $V_{IH}$ !

Thus, we can make the statement that the **magnitude** of the **noise**  $v_n(t)$  must be **less** than the **noise margins** to avoid the ambiguous values of the disturbing **transition region!** I.E., make sure that:

$$|v_n(t)| < NM \quad \text{for all time } t$$



# Gate Power Dissipation

Every digital gate will require some amount of **power**. It must **dissipate** this power in the form of heat. We consider **two** types of power:

**Static  $P_D$**  - Power dissipated when gate is **not** changing state.

**Dynamic  $P_D$**  - Power dissipated when gate is changing states.

Typically we find that:

$$\text{Dynamic } P_D \geq \text{Static } P_D$$


In fact, for *CMOS* logic gates (e.g., a *CMOS* digital inverter), we will find that the **static  $P_D$**  is nearly **zero**!

However, we will find that it **always** takes some power to **change** the output state of a digital logic gate.

**Q:** *Why is that??*

 **A:** **Capacitance!** When we change the **voltage** at the output, we must charge or discharge the **capacitance** associated with the output. This requires **current!**

Although engineers work very hard to **minimize** the output capacitance of digital circuits, we **cannot** fully eliminate it.



Note that the **displacement current**  $i_d(t)$  flowing "through" this capacitor is proportional to the **time derivative** of the output voltage.

- \* Thus, if the output state is **static** (i.e., it is not changing), this derivative is **zero**, as is the current.
- \* However, if the output is **dynamic** (i.e. it is changing with time), the derivative is **non-zero**, and thus displacement current **flows** in the capacitor.
- \* Note that the **faster** we change the output, the **more** displacement current is produced, meaning **more power** is required!
- \* Thus, we come to the (correct) conclusion that **dynamic** power dissipation is **dependent** on the speed (e.g., clock frequency) of the digital logic—the "**faster**" the logic, the **higher** the dynamic power dissipation!
- \* As a result, dynamic  $P_D$  is typically **specified** as a function of **frequency**.

# Gate Propagation Delay

Say the **input** to a logic gate changes its state (e.g., 0 to  $V^+$ , or  $V^+$  to 0). The **output** of the gate will likely change state as a result.

However, the output will **not change instantaneously** when the input changes. Instead, the output will change **after a small delay**.

We call this delay the **propagation delay**. Ideally, this delay is as **small** as possible; typically, it is on the order of a few **nanoseconds** or less.

Often, the delay when the output changes from **low to high** is a **different value** than the delay when the output changes from **high to low**. Therefore, we can define:

$t_{pHL}$  = delay for output changing from high to low

$t_{pLH}$  = delay for output changing from low to high

We can therefore define the **propagation delay**  $t_p$  as the **average** of these values:


$$t_p = \frac{t_{pHL} + t_{pLH}}{2}$$

**Q:** *Why does this delay occur?*

 **A:** Again, the reason is **output capacitance!**

It takes a **non-zero** amount of time to **charge** or **discharge** a capacitor. In other words, the output voltage **cannot** change instantaneously to a change in the input.

Propagation delay is a particularly disturbing **problem** when we construct a **complex** digital circuit consisting of **many** interconnecting stages. For example:



The **total** propagation delay for this complex digital circuit is therefore:

$$t_p = t_{pHL1} + t_{pHL2} + t_{pHL3} + t_{pHL4}$$

Thus, although the propagation delay of **one** individual logic gate may be insignificant, the **total delay** through a complex digital circuit consisting of many stages and gates can be quite **large!**

This can cause **big problems** in the precise timing required of sophisticated and complex digital systems!

# Delay-Power Product


**Q:** *So, an ideal digital technology would have BOTH very small propagation delay  $t_p$ , AND very small power dissipation  $P_D$ , right ?*

**A:** True ! But, there is a problem. Designing a "faster" (e.g., lower  $t_p$ ) digital gate usually requires **greater power**. And designing a gate to minimize power consumption usually **slows down** the digital device.

Propagation delay and power dissipation generally form a **design trade off** - improve one and you degrade the other !



 To quantify how effective, or efficient a digital design technology is in terms of delay and power, we use the product of the **propagation delay** and the **power dissipation**:



The **delay-power product (DP)** !

The delay-power product is therefore **defined** as:

$$DP = P_D t_p$$

- \* Note we could define either a **static** or **dynamic** delay-power product, depending on  $P_D$ .
- \* Note also the **unit** of the delay-power product—**Joules** !!

The delay-power product is a **figure of merit** for digital technologies.

