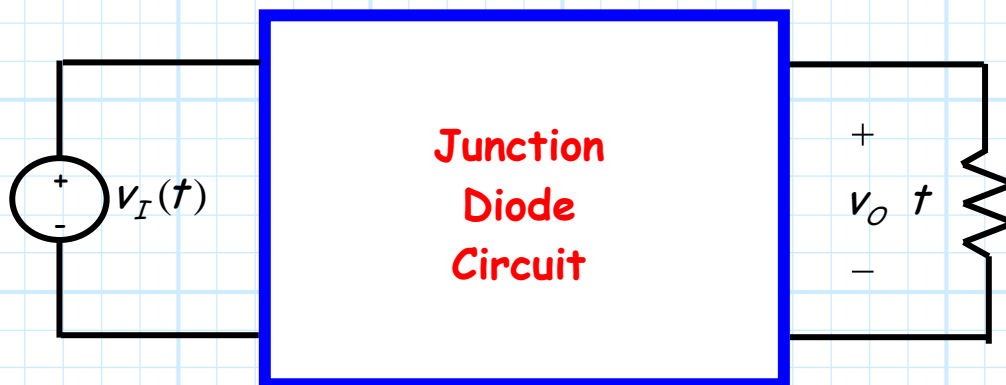


4.5 Rectifier Circuits

Reading Assignment: pp. 194-200

A. Junction Diode 2-Port Networks

Consider when junction diodes appear in a 2-port network (i.e., a circuit with an **input** and an **output**).



We can characterize a 2-port network with its **transfer function**.

HO: THE TRANSFER FUNCTION OF DIODE CIRCUITS

Finding this transfer function is **similar** to our previous diode circuit analysis—but with a few **very** important **differences**!

HO: STEPS FOR FINDING A JUNCTION DIODE CIRCUIT TRANSFER FUNCTION

EXAMPLE: DIODE CIRCUIT TRANSFER FUNCTION

The **input** voltage is almost always a function of **time**, which means the **output** voltage is as well.

HO: TIME-DOMAIN ANALYSIS OF DIODE CIRCUITS

B. Diode Rectifiers

Many important **diode circuits** appear in a standard **AC to DC power supply**!

HO: POWER SUPPLIES

The signal **rectifier** is an important component of a power supply—it's what creates the **DC component**.

HO: SIGNAL RECTIFICATION

One standard rectifier design is called the **full-wave rectifier**.

HO: THE FULL-WAVE RECTIFIER

But the **bridge rectifier** also provides full-wave rectification.

HO: THE BRIDGE RECTIFIER

The bridge rectifier is more **complex**, but results in a lower **Peak Inverse Voltage**.

HO: PEAK INVERSE VOLTAGE


Make sure **you** can determine the **PIV** of a diode circuit. It depends on **both** the specific circuit, **and** the specific input voltage!

EXAMPLE: PEAK INVERSE VOLTAGE

The Transfer Function of Diode Circuits

For many junction diode circuits, we find that one of the voltage sources is in fact **unknown!**

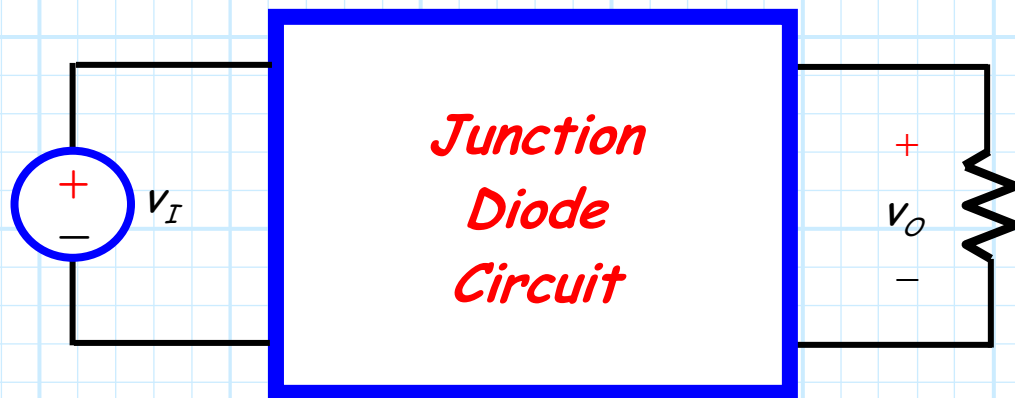This unknown voltage is typically some **input** signal of the form v_I , which results in an output voltage v_O .




Q: How the heck do you expect us to determine v_O if we have **no idea** what v_I is??



The (large-signal) transfer function

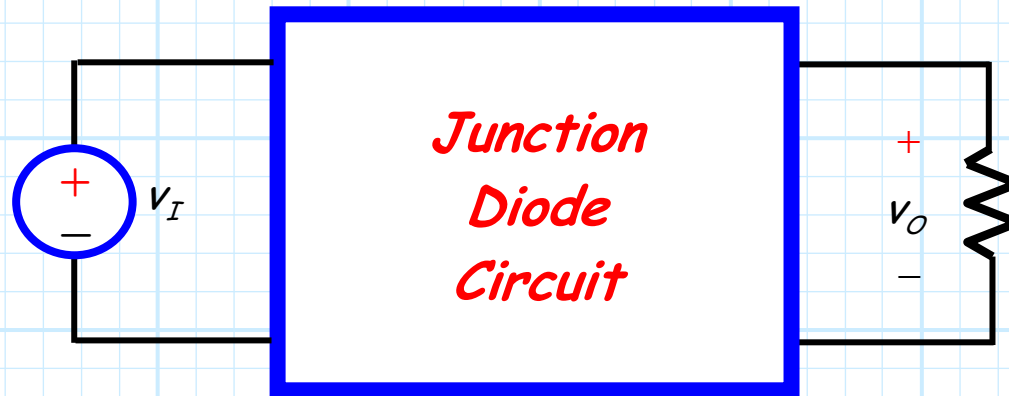A: We of course cannot determine an **explicit** value or expression for v_O , since it **depends** on the input v_I .



Instead, we will attempt to explicitly determine this **dependence** of v_O on v_I !

In other words, we seek to find an expression for v_O in **terms** of v_I .
Mathematically speaking, our goal is to determine the **function**:

$$v_O = f(v_I)$$

→ We refer to this as the (large-signal) circuit **transfer function**.


Plotting the transfer function

Note that we can **plot** a circuit transfer function on a 2-dimensional plane, just as if the function related values x and y (e.g. $y = f(x)$).

For **example**, say our circuit transfer function is:

$$\begin{aligned}v_O &= f(v_I) \\ &= 3v_I + 2\end{aligned}$$

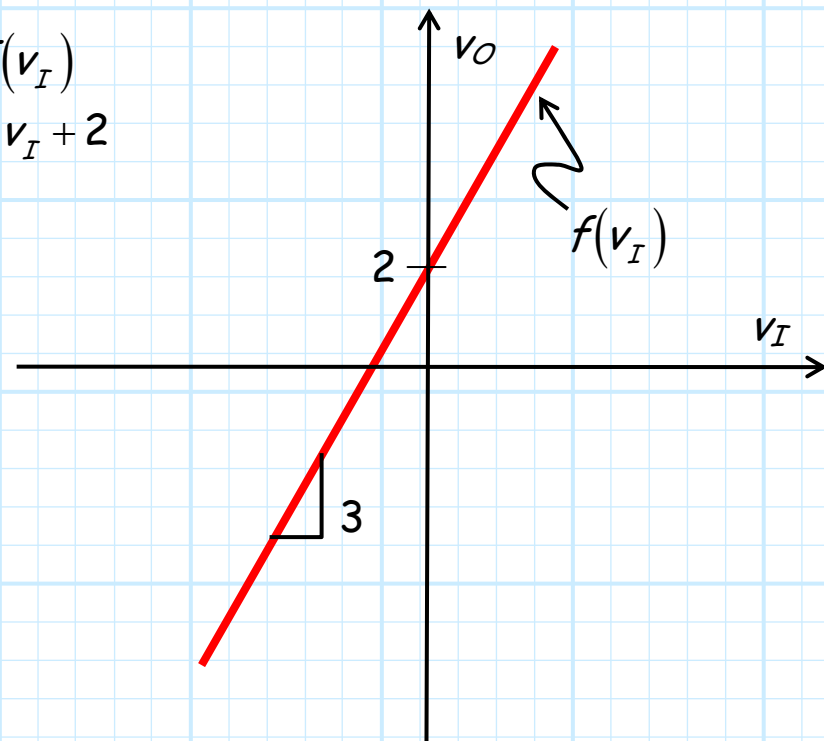Note this is simply the **equation of a line** (e.g., $y = 3x + 2$), with slope $m=3$ and y -intercept $b=2$.



Actually, a rare moment when I'm not being annoying and pretentions

Q: A "function" eh?

*Isn't a "function" just your annoyingly pretentious way of saying we need to find some mathematic **equation** relating v_O and v_I ?*



A: Actually **no!** Although a function is a mathematical equation, there are in fact **scads** of equations relating v_O and v_I that are **not** functions!


→ The set of all possible functions $y = f(x)$ are a **subset** of the set of all possible equations relating y and x .

A **function** $v_O = f(v_I)$ is a mathematical expression such that for **any** value of v_I (i.e., $-\infty < v_I < \infty$), there is **one, but only one**, value v_O .

The transfer function must *be* a function!


Note this definition of a function is consistent with our **physical** understanding of circuits—we can place **any** voltage on the input that we want (i.e., $-\infty < v_I < \infty$), and the result will be **one** specific voltage value v_O on the output.

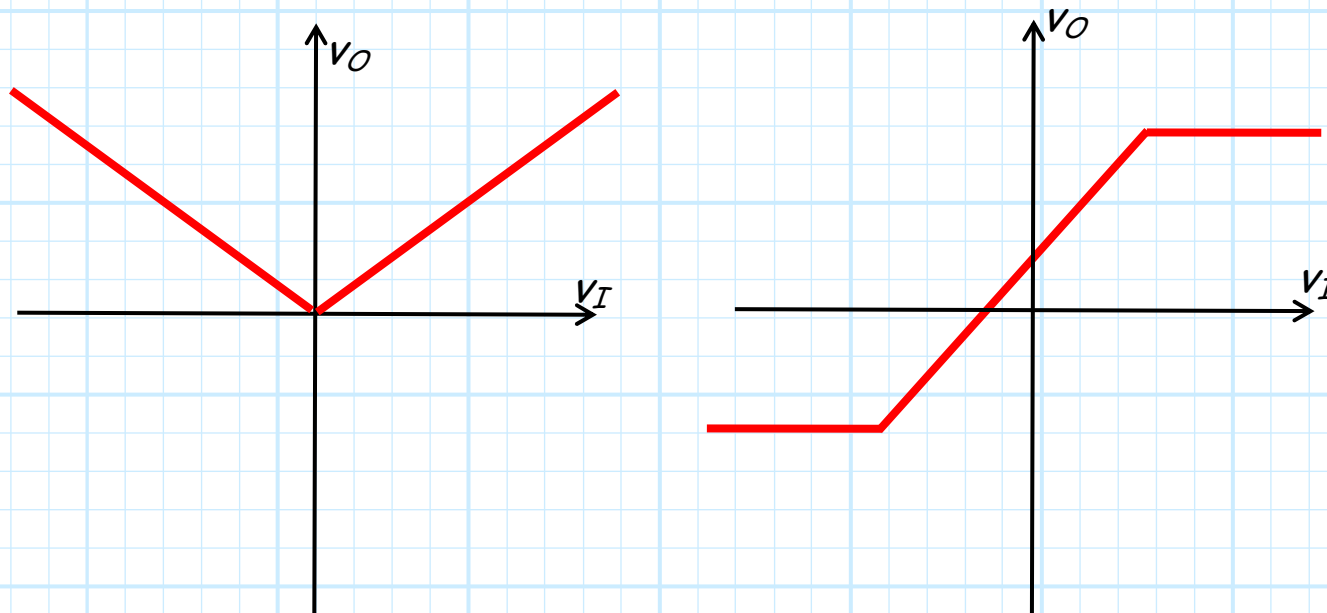Therefore, examples of **valid** circuit transfer functions include:




These are functions—NOT!

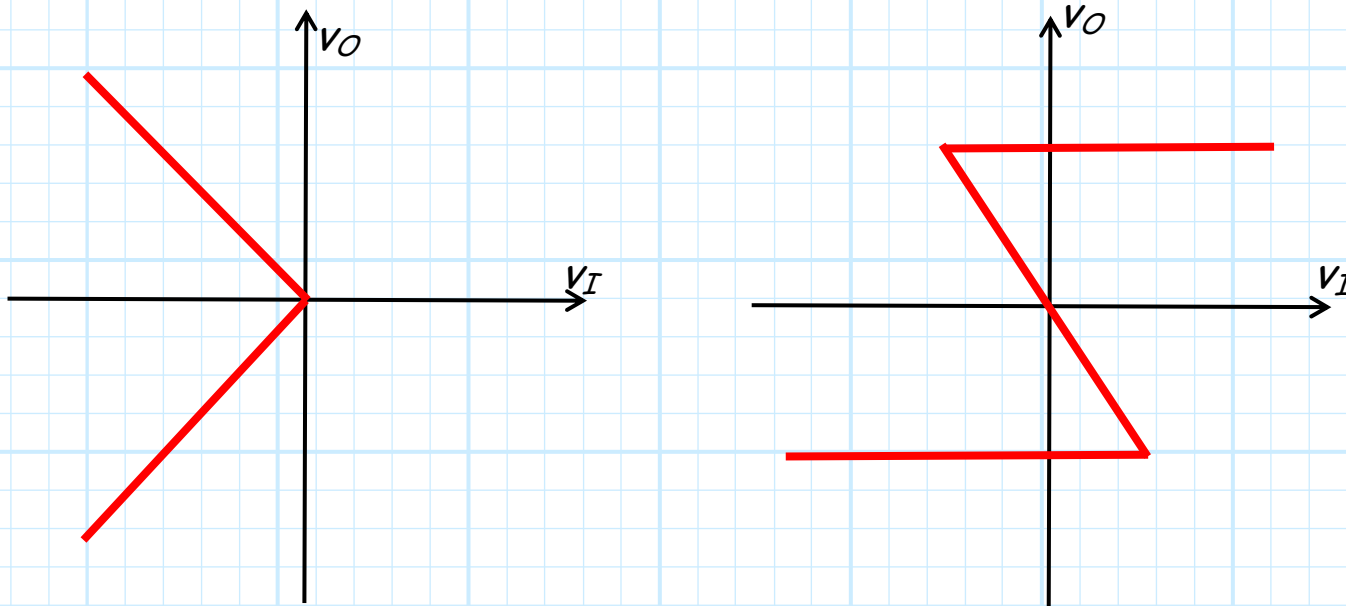Conversely, the transfer "functions" below are **invalid**—they **cannot** represent the behavior of circuits, since they **are not** functions!




The transfer function must be continuous

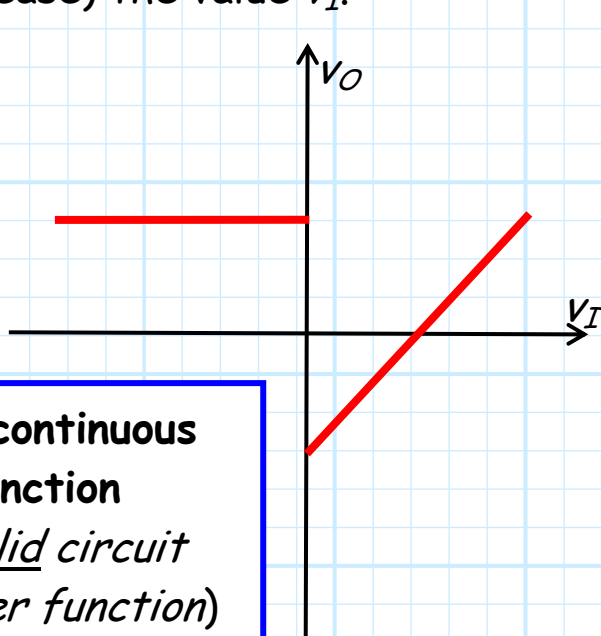Moreover, we find that **circuit** transfer functions must be **continuous**. That is, v_O **cannot** "instantaneously change" from one value to another as we increase (or decrease) the value v_I .



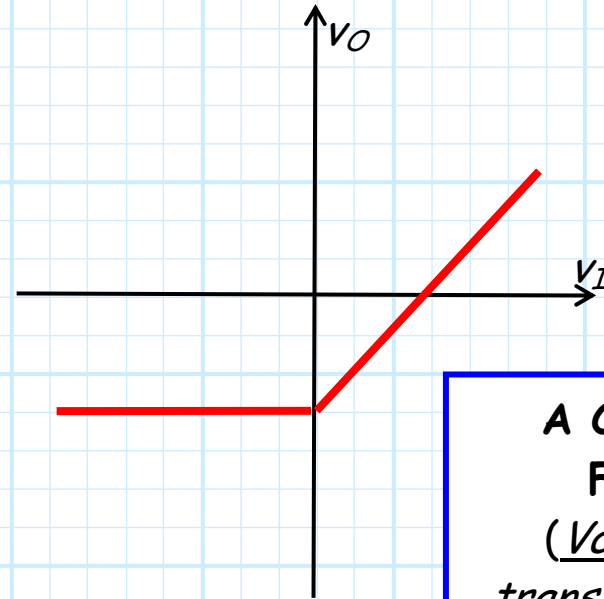**A Discontinuous
Function**
(*Invalid circuit
transfer function*)



**A Continuous
Function**
(*Valid circuit
transfer function*)



Remember, the transfer function of every junction diode circuit must be a continuous function.

If it is not, you've done something wrong!

Steps for Finding a Junction Diode Circuit Transfer Function

Determining the **transfer function** of a junction diode circuit is in many ways **very similar** to the analysis steps we followed when analyzing previous junction diode circuits (i.e., circuits where all sources were **explicitly known**).

However, there are also some **important differences** that we must understand completely if we wish to successfully determine the **correct transfer function!**

Step 1: *Replace all junction diodes with an appropriate junction diode model.*

Just like before! We will now have an **IDEAL** diode circuit.

Step 2: *ASSUME some mode for all ideal diodes.*

Just like before! An **IDEAL** diode can be either forward or reverse biased.

Step 3: *ENFORCE the bias assumption.*

Just like before! ENFORCE the bias assumption by replacing the **ideal** diode with short circuit or open circuit.

Step 4: *ANALYZE the remaining circuit.*

Sort of, kind of, like before!

1. If we assumed an IDEAL diode was forward biased, we must determine i_D^i —**just** like before!

However, **instead** of finding the numeric value of i_D^i , we determine i_D^i as a **function** of the unknown source (e.g., $i_D^i = f(v_I)$).

2. Or, if we assumed an IDEAL diode was reversed biased, we must determine v_D^i —**just** like before!

However, **instead** of finding the numeric value of v_D^i , we determine v_D^i as a **function** of the unknown source (e.g., $v_D^i = f(v_I)$).

3. Finally, we must determine all the **other** voltages and/or currents we are interested in (e.g., v_O)—**just** like before!

However, **instead** of finding its numeric value, we determine it as a **function** of the unknown source (e.g., $v_o = f(v_I)$).

Step 5: Determine **WHEN** the assumption is valid.

Q: OK, we get the picture. Now we have to **CHECK** to see if our **IDEAL** diode assumption was correct, right?



A: Actually, **no!** This step is **very different** from what we did before!

We **cannot** determine **IF** $i_D^i > 0$ (forward bias assumption), or **IF** $v_D^i < 0$ (reverse bias assumption), since we **cannot** say for certain what the value of i_D^i or v_D^i is!

Recall that i_D^i and v_D^i are **functions** of the unknown voltage source (e.g., $i_D^i = f(v_I)$ and $v_D^i = f(v_I)$).

Thus, the values of i_D^i or v_D^i are **dependent** on the unknown source (v_I , say).

For **some** values of v_I , we will find that $i_D^i > 0$ or $v_D^i < 0$, and so our assumption (and thus our solution for $v_o = f(v_I)$) will be! **correct**

However, for **other** values of v_I , we will find that $i_D^i < 0$ or $v_D^i > 0$, and so our assumption (and thus our solution for $v_O = f(v_I)$) will be **incorrect!**



Q: *Yikes! What do we do?*

*How can we determine the circuit transfer function if we can't determine **IF** our ideal diode assumption is correct??*

A: Instead of determining **IF** our assumption is correct, we must determine **WHEN** our assumption is correct!

In other words, we must determine for **what values** of v_I is $i_D^i > 0$ (forward bias), or for **what values** of v_I is $v_D^i < 0$ (reverse bias).

We can do this since we earlier (in step 4) determined the function $i_D^i = f(v_I)$ or the function $v_D^i = f(v_I)$.

Perhaps this step is best explained by an **example**. Let's say we assumed that our ideal diode was **forward biased** and, say we determined (in step 4) that v_O is related to v_I as:

$$\begin{aligned} v_O &= f(v_I) \\ &= 2v_I - 3 \end{aligned}$$

Likewise, say that we determined (in step 4) that our ideal diode current is related to v_I as:

$$i_D^i = f(v_I) \\ > \frac{v_I - 5}{4}$$

Thus, in order for our forward bias assumption to be **correct**, the function $i_D^i = f(v_I)$ must be **greater than zero**:

$$i_D^i > 0 \\ f(v_I) > 0 \\ \frac{v_I - 5}{4} > 0$$

We can now "solve" this **inequality** for v_I :

$$\frac{v_I - 5}{4} > 0 \\ v_I - 5 > 0 \\ v_I > 5$$

Q: *What does **this** mean? Does it mean that v_I is some value **greater than 5.0V**??*



A: **NO!** Recall that v_I can be **any** value.

What the inequality above means is that $i_D' > 0$ (i.e., the ideal diode is forward biased) **WHEN** $v_D' > 5.0$.

Thus, we know $v_O = 2v_I - 3$ is valid **WHEN** the ideal diode is forward biased, and the ideal diode is forward biased **WHEN** (for this example) $v_D' > 5.0$.

As a result, we can mathematically state that:

$$v_O = 2v_I - 3 \quad \text{when} \quad v_I > 5.0 \text{ V}$$

Conversely, this means that if $v_I < 5.0 \text{ V}$, the ideal diode will be **reverse biased**—our forward bias assumption would **not** be valid, and thus our expression $v_O = 2v_I - 3$ is **not** correct ($v_O \neq 2v_I - 3$ for $v_I < 5.0 \text{ V}$)!

Q: *So how do we determine v_O for values of $v_I < 5.0 \text{ V}$?*



A: Time to move to the last step!

Step 6: *Change assumption and repeat steps 2 through 5!*

For our **example**, we would change our bias assumption and now **ASSUME** reverse bias.

We then **ENFORCE** $i_D^i = 0$, and then **ANALYZE** the circuit to find both $v_D^i = f(v_I)$ and a **new** expression $v_O = f(v_I)$ (it will **no longer** be $v_O = 2v_I - 3$!).

We then determine **WHEN** our reverse bias assumption is valid, by solving the **inequality** $v_D^i = f(v_I) > 0$ for v_I .

For the example used here, we would find that the **IDEAL** diode is reverse biased **WHEN** $v_I < 5.0$ V.


For junction diode circuits with **multiple** diodes, we may have to repeat this entire process **multiple** times, until **all possible** bias conditions are analyzed.

If we have done our analysis **properly**, the result will be a valid **continuous function!**


That is, we will have an expression (but only **one** expression) relating v_O to **all** possible values of v_I .

This transfer function will typically be **piecewise linear**.

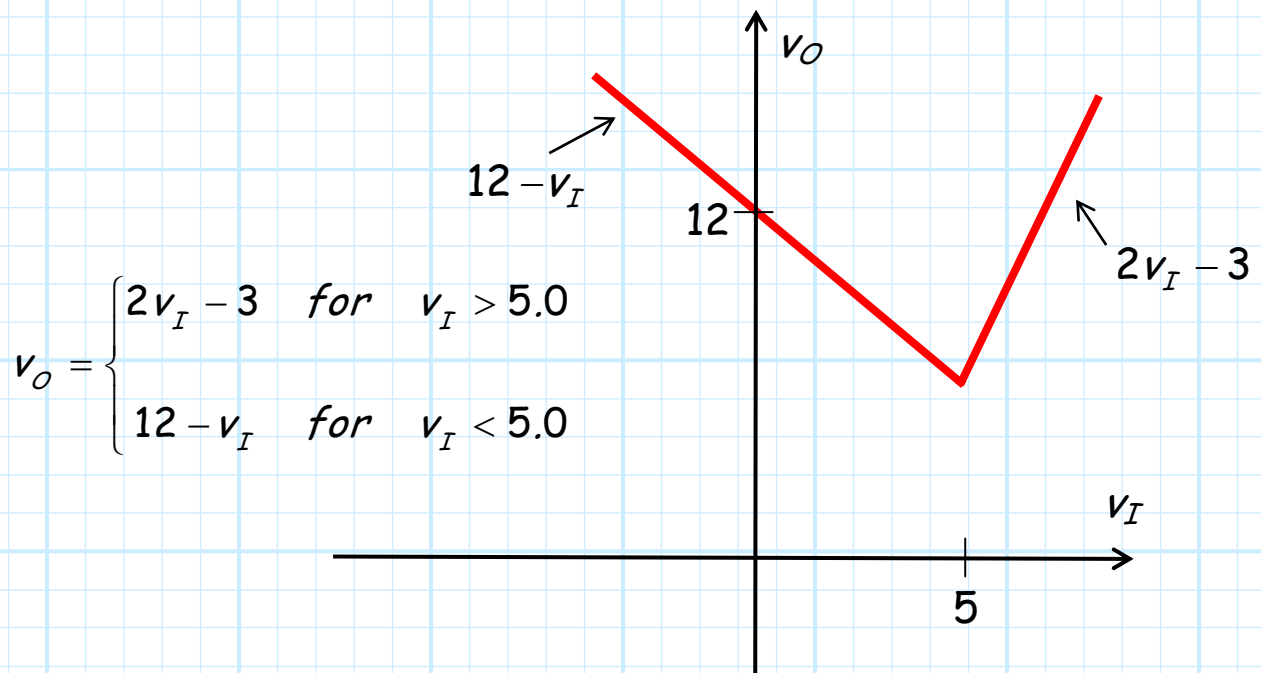
An **example** of a piece-wise linear transfer function is:



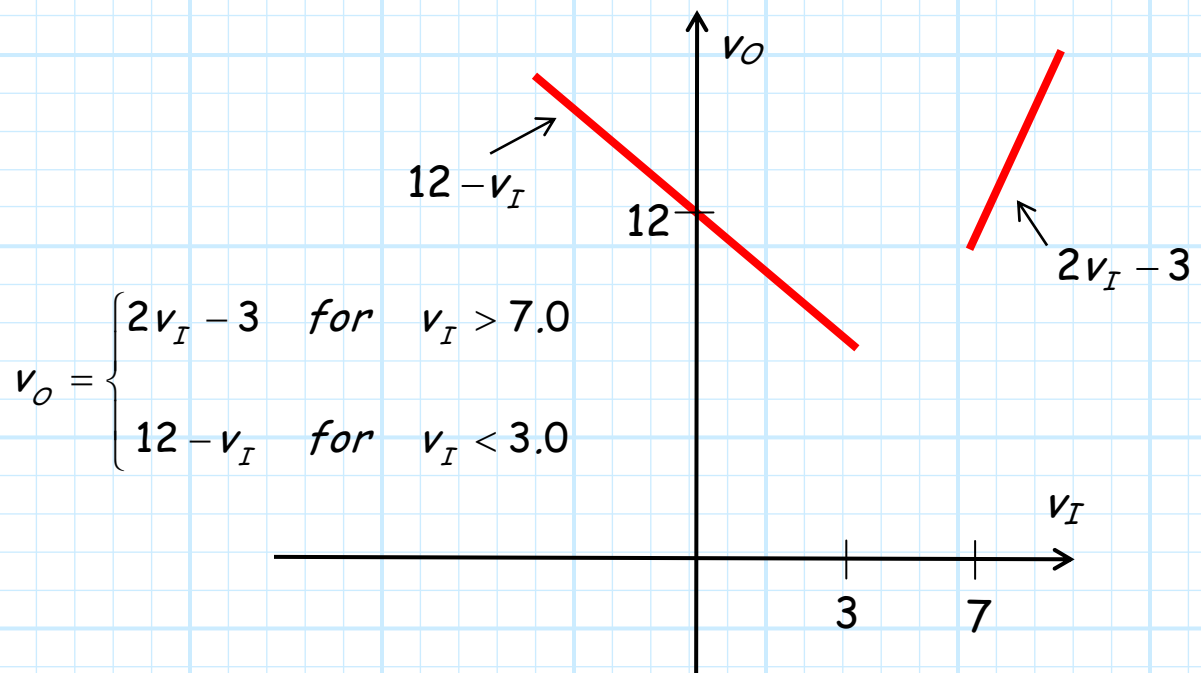
Just to make **sure** that we understand what a function is, note that the following expression is **not** a function:



Nor is this expression a function:

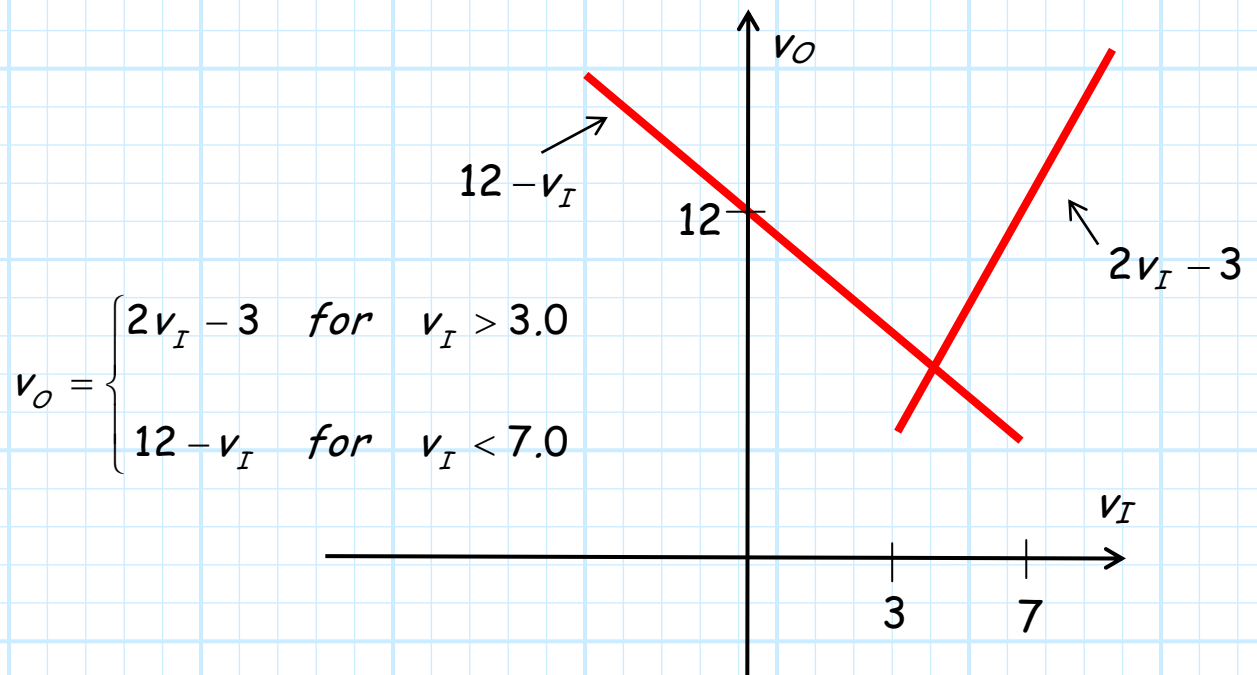

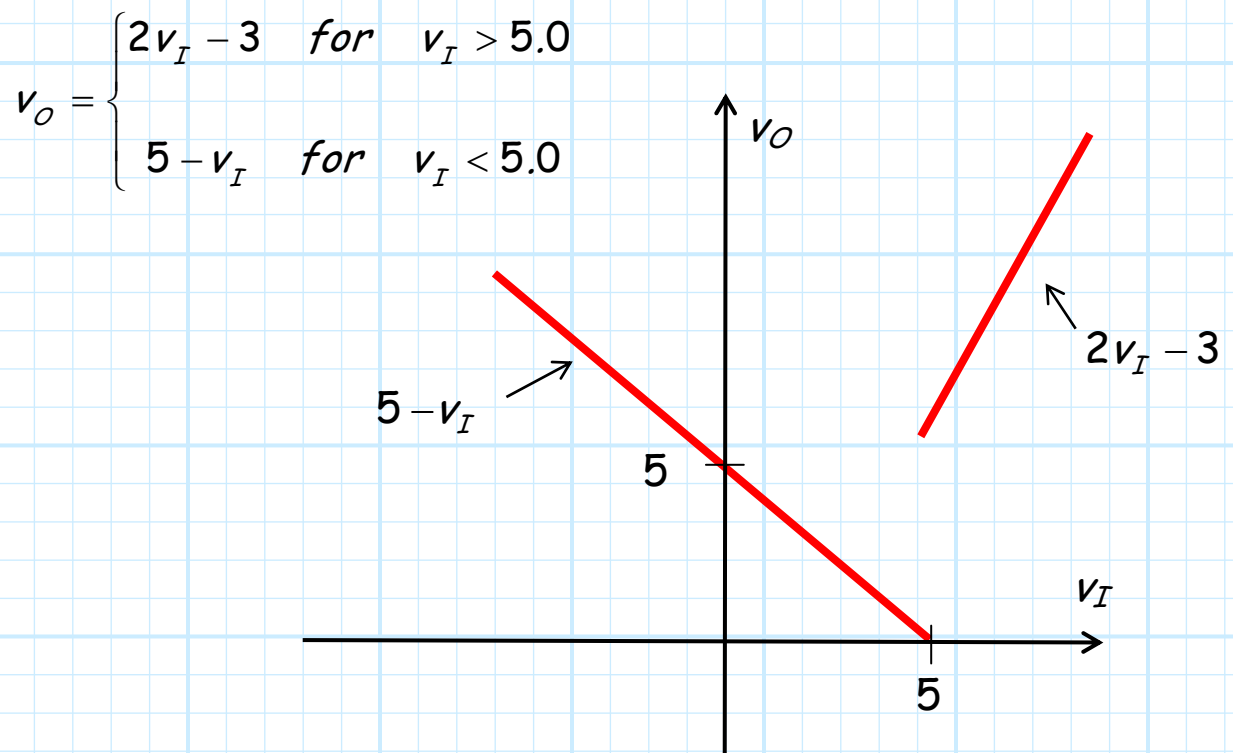Finally, note that the following expression is a function, but it is **not continuous**:







Make sure that the piece-wise transfer function that you determine is in fact a function, and is continuous!

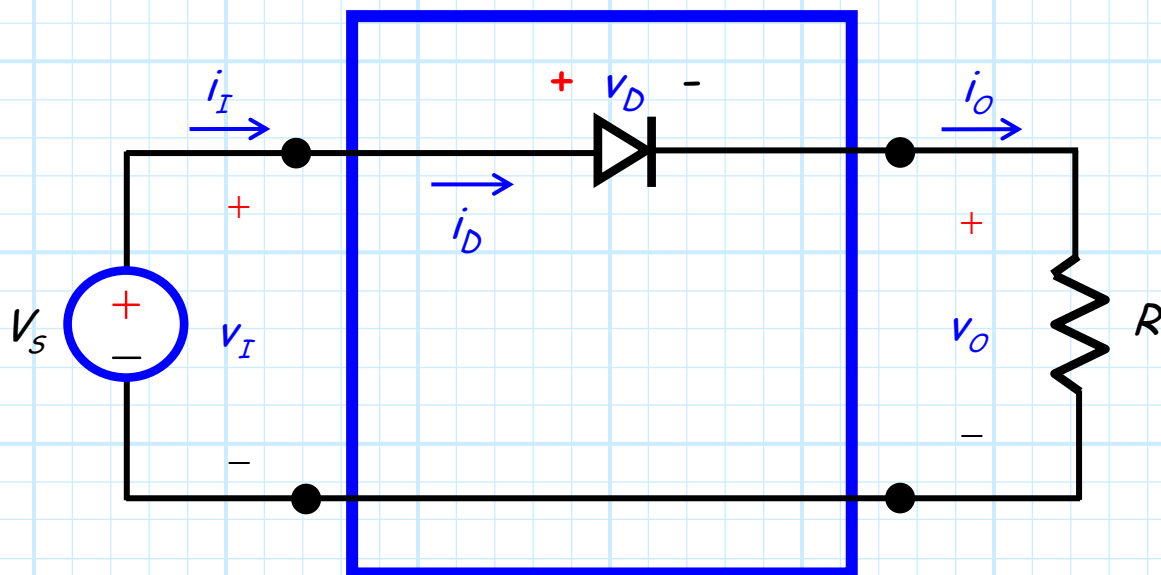Example: Diode Circuit Transfer Function

Consider the following circuit, called a **half-wave rectifier**:




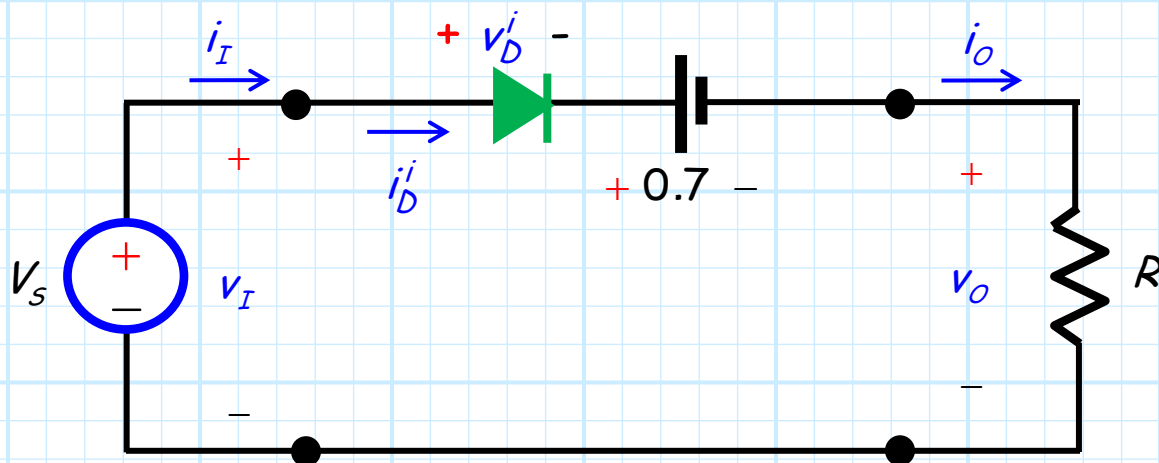Let's use the **CVD model** to determine the output voltage v_o in terms of the input voltage v_I .



In other words, let's determine the diode circuit **transfer function** $v_o = f(v_I)$!

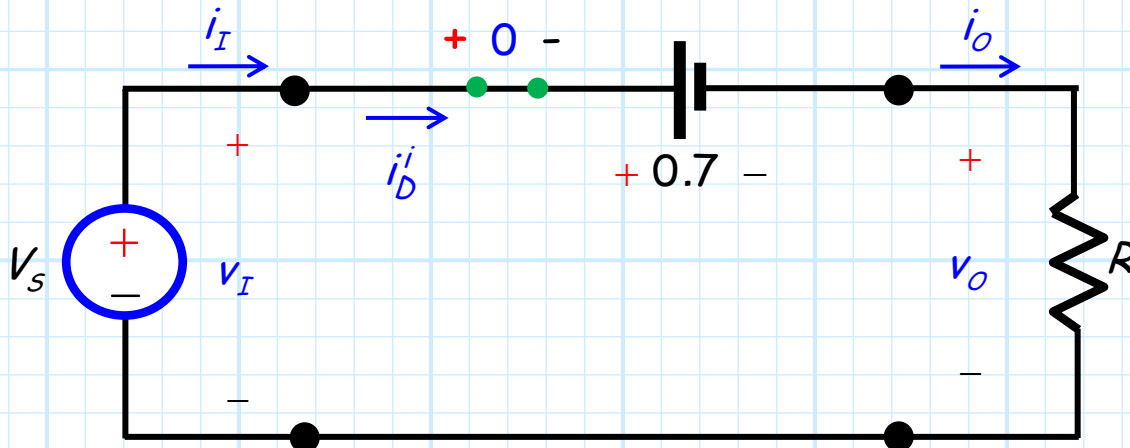ASSUME the **ideal** diode is **forward** biased, ENFORCE $v_D' = 0$.



From KVL, we find that:

$$v_I - 0 - 0.7 = v_o \quad \Rightarrow \quad \therefore v_o = v_I - 0.7$$


This result is of course true **if** our original assumption is correct—it is valid **if** the ideal diode is forward biased (i.e., $i_D' > 0$)!

From **KCL** and **Ohm's Law**, we find that:

$$i_D' = i_o = \frac{v_o}{R} = \frac{v_I - 0.7}{R}$$

Q: *I'm so **confused!** Is this current **greater** than zero or **less** than zero?*

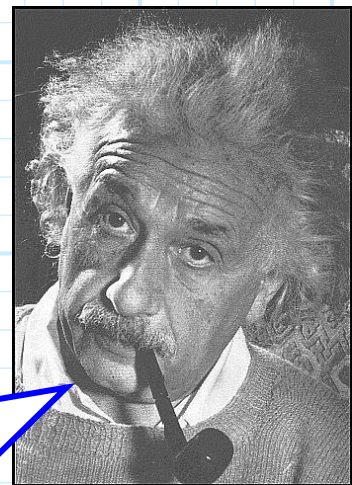*Is our assumption correct? **How** can we tell?*




A: The ideal diode current is **dependent** on the value of source voltage v_I . As such, we **cannot** determine if our assumption is correct, we **instead** must find out **when** our assumption is correct!

In other words, we know that the forward bias assumption is correct **when** $i_D^i > 0$. We can rearrange our diode current expression to determine for what values of source voltage v_S this is true:

$$\begin{aligned} i_D^i &> 0 \\ \frac{v_I - 0.7}{R} &> 0 \\ v_I - 0.7 &> 0 \\ v_I &> 0.7 \end{aligned}$$

So, we have found that **when** the source voltage v_I is greater than 0.7 V, the output voltage v_O is:


$$v_O = v_I - 0.7$$

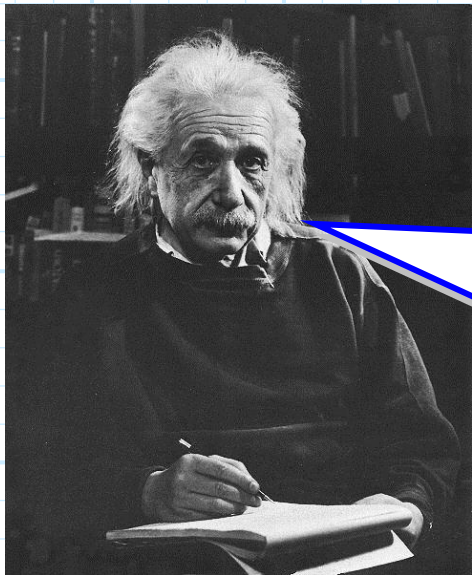

Q: OK, I've got this result written down.

However, I still don't know what the output voltage v_O is **when** the source voltage v_I is **less** than 0.7V!?!?

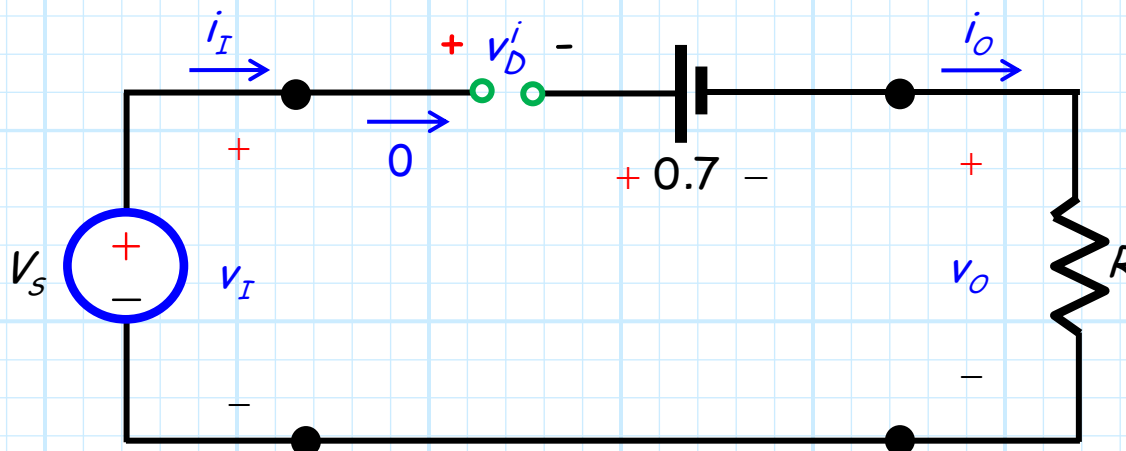Now we **change** our assumption and **ASSUME** the ideal diode in the CVD model is **reverse** biased, an assumption **ENFORCED** with the condition that $i_D^i = 0$ (i.e., an open circuit).




From KCL:

$$i_o = i_D^i = 0$$

From Ohm's Law, we find that the output voltage is:

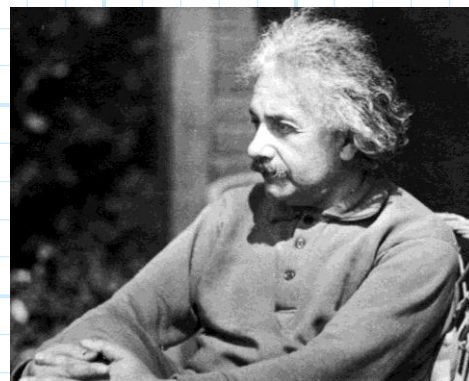
$$\begin{aligned} v_o &= R i_o \\ &= R(0) \\ &= 0 \text{ V !!!} \end{aligned}$$



Q: Fascinating! The output voltage is **zero** when the ideal diode is **reverse biased**.

But, precisely **when is** the ideal diode reverse biased? For **what** values of v_I does this occur ?

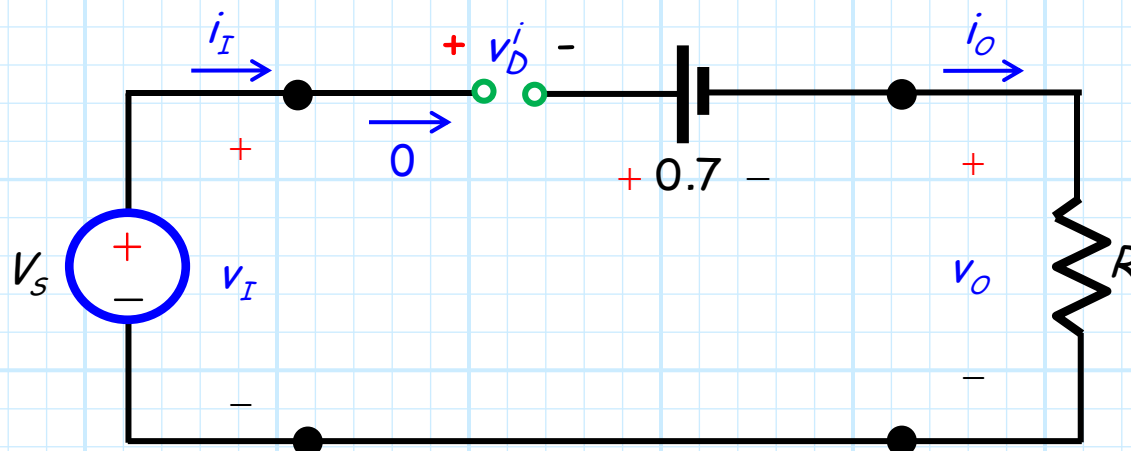A: To answer these questions, we must determine the **ideal** diode voltage in terms of v_S (i.e., $v_D^i = f(v_I)$).



From KVL:

$$v_I - v_D^i - 0.7 = v_O$$

Therefore:

$$\begin{aligned} v_D^i &= v_I - 0.7 - v_O \\ &= v_I - 0.7 - 0.0 \\ &= v_I - 0.7 \end{aligned}$$

Thus, the ideal diode is in reverse bias **when:**


$$\begin{aligned} v_D^i &< 0 \\ v_I - 0.7 &< 0 \end{aligned}$$

Solving for v_I , we find:

$$\begin{aligned} v_I - 0.7 &< 0 \\ v_I &< 0.7 \text{ V} \end{aligned}$$

In other words, we have determined that the **ideal** diode will be reverse biased **when** $v_I < 0.7 \text{ V}$, and that the output voltage will be $v_o = 0$.

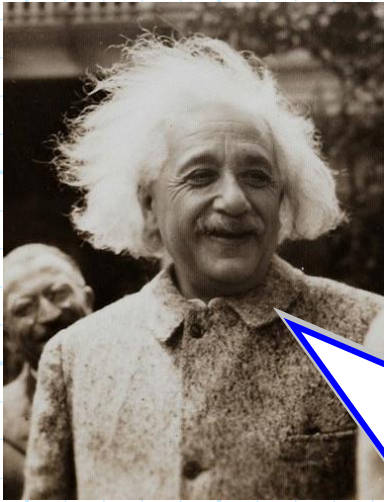A: That's right! The **transfer function** for this circuit is therefore:



$$v_o = \begin{cases} v_s - 0.7 & \text{for } v_s > 0.7 \\ 0 & \text{for } v_s < 0.7 \end{cases}$$


Q: So, I see we have found that:

$$v_o = v_I - 0.7 \quad \text{when } v_I > 0.7 \text{ V}$$

and,

$$v_o = 0.0 \quad \text{when } v_I < 0.7 \text{ V}$$

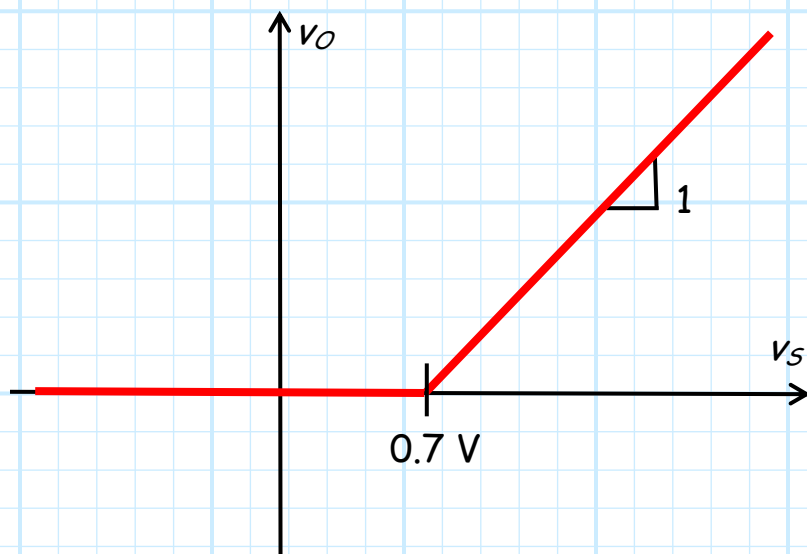
It appears we have a valid, continuous, function!



*Like $E = mc^2$, the circuit in this example may seem trivial, but it is actually **very important!***


*This circuit is called a **half-wave rectifier**, and provides signal **rectification**.*

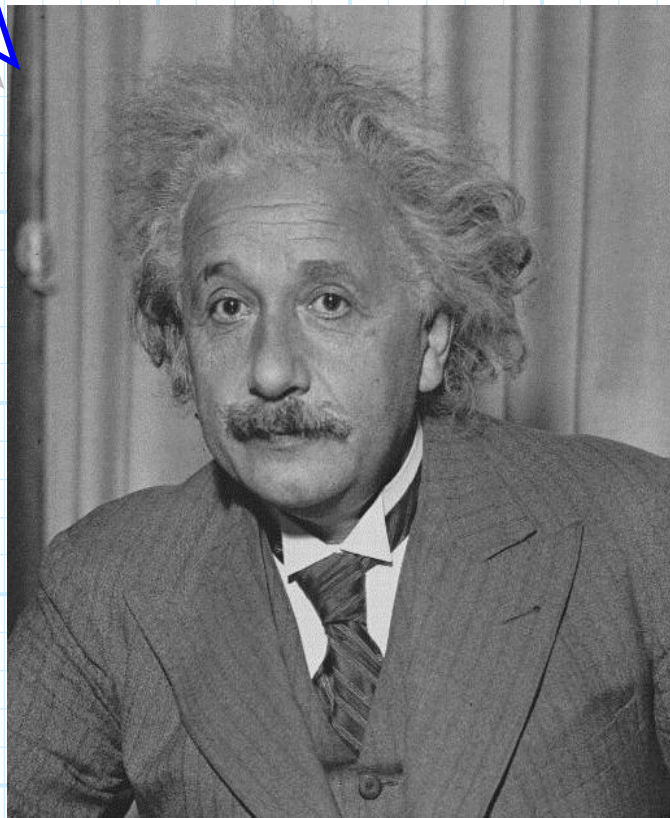*Rectifiers are an **essential part** of every AC to DC power supply!*



Time-domain Analysis of Diode Circuits

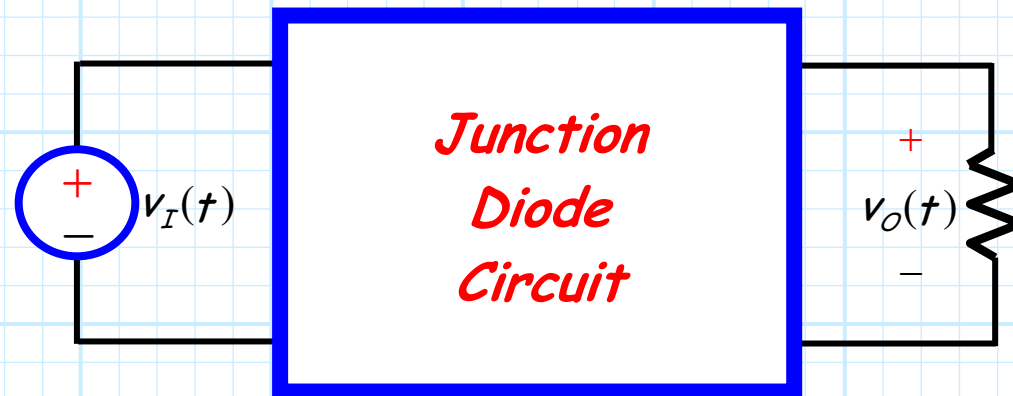Let's consider what happens when the input to a junction diode circuit **varies with time!**



The **output** will **likewise** vary with time!

If we know the large signal **transfer function** of diode circuit:

$$v_O = f(v_I)$$


Then the **time-varying output** (assuming the input is not changing **too fast!**) is expressed as:

$$v_O(t) = f(v_I(t))$$

For example...


For **example**, say our circuit transfer function is:
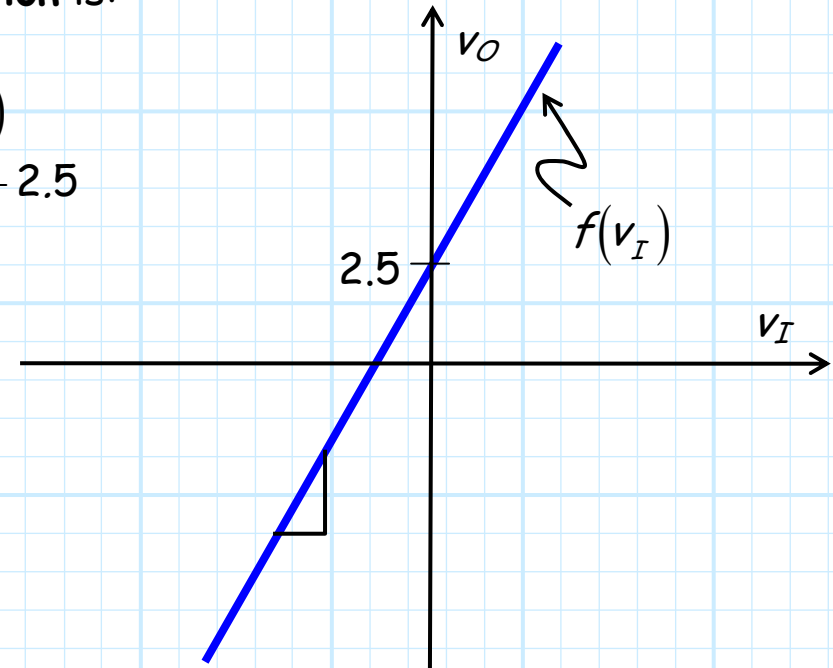
$$\begin{aligned} v_o &= f(v_I) \\ &= 2v_I + 2.5 \end{aligned}$$



And, the **input signal** varies with time as:



$$v_I(t) = 0.5 \cos[\pi t]$$

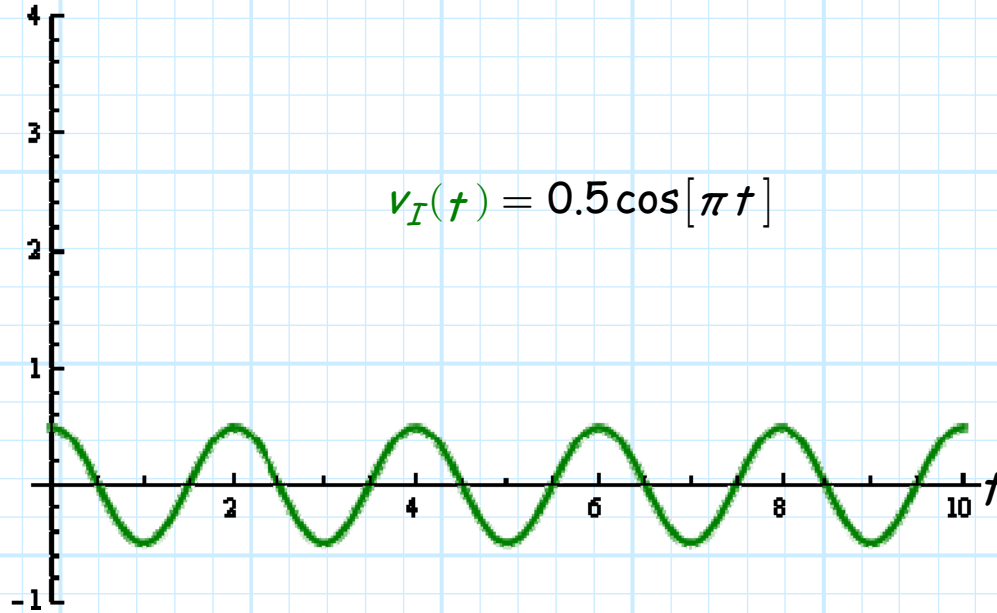

Make this make sense to you

The **output signal** is thus:

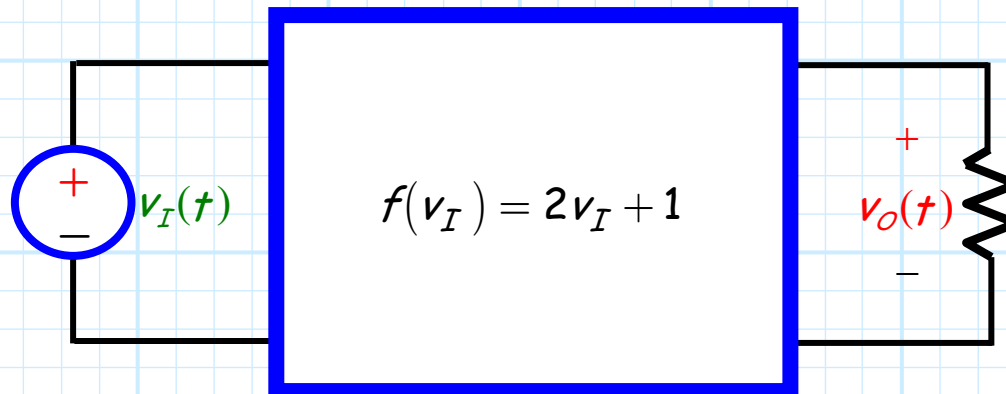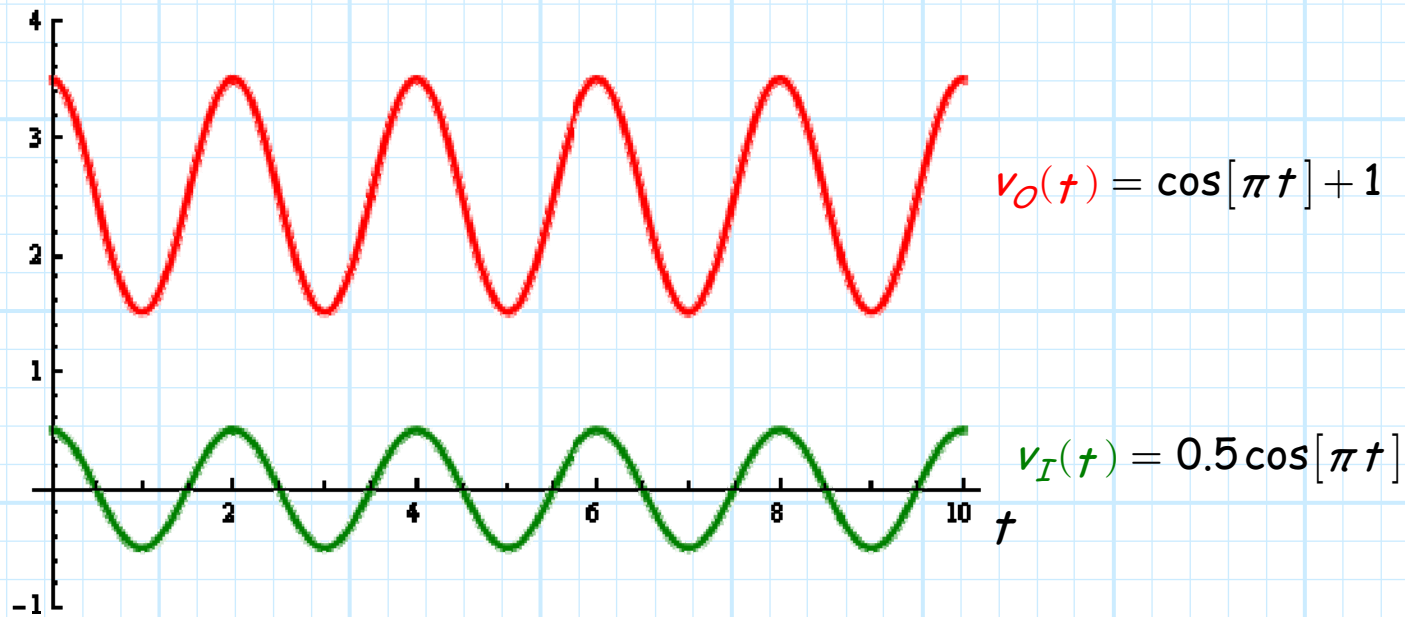
$$\begin{aligned} v_O(t) &= 2 v_I(t) + 1 \\ &= 2(0.5 \cos[\pi t]) + 1 \\ &= \cos[\pi t] + 1 \end{aligned}$$



A trickier example...



Or, consider a diode circuit with **this** transfer function:
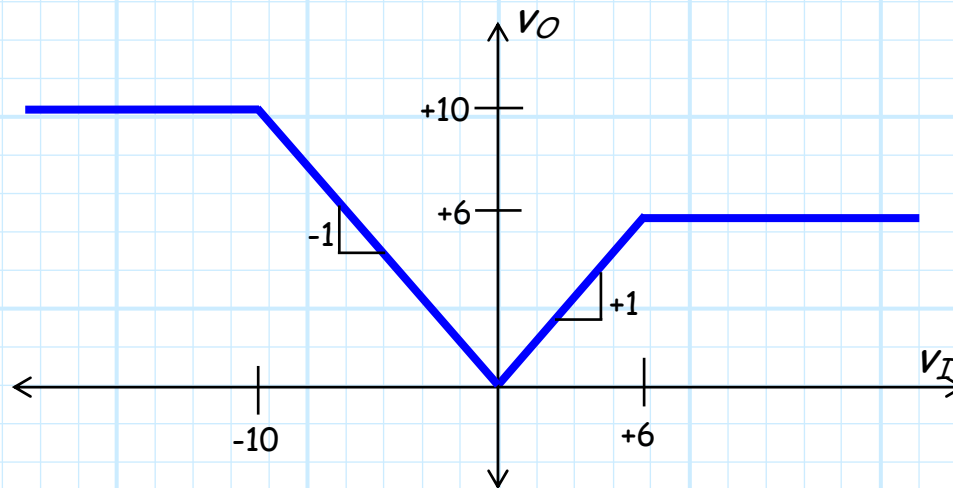
$$v_o = \begin{cases} 6.0 & \text{for } v_I > 6.0 \\ v_I & \text{for } 0 < v_I < 6.0 \\ -v_I & \text{for } -10.0 < v_I < 0 \\ 10.0 & \text{for } v_I < -10.0 \end{cases}$$




What is the output?

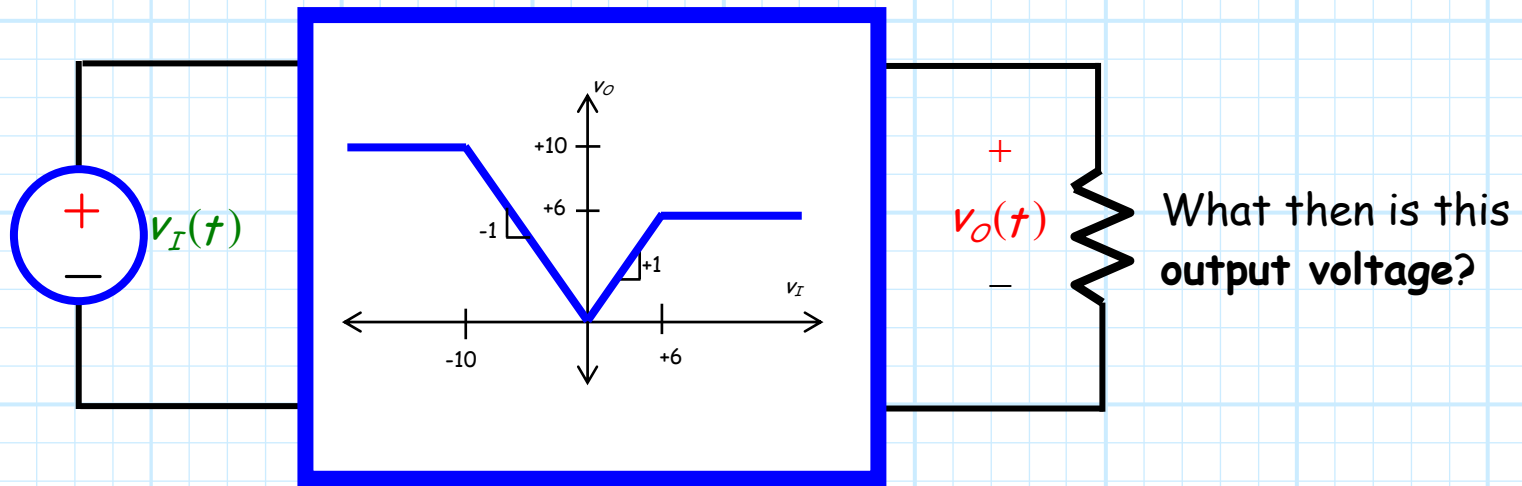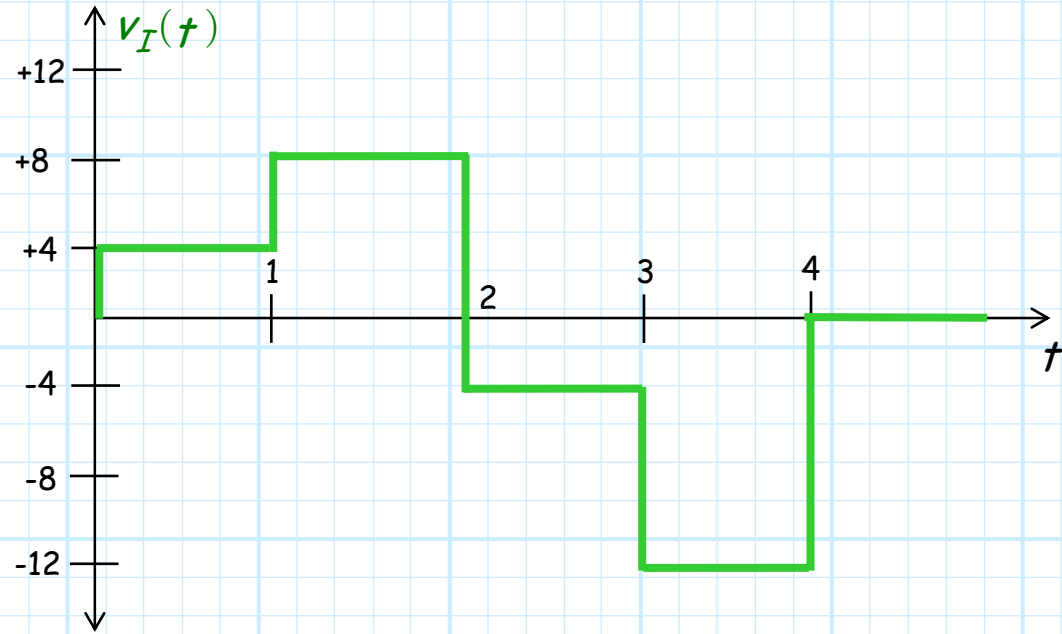Say that **this** time-varying signal appears at its **input**:




The answer is simple—if you think

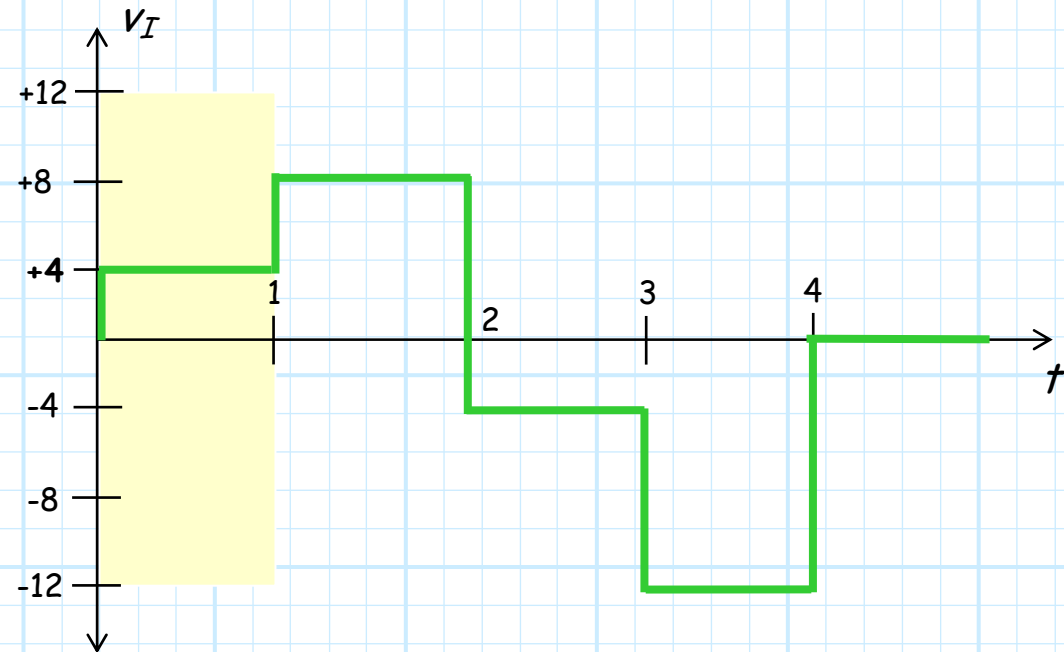Note that for time $0 < t < 1$,
the input voltage is **4.0 V**



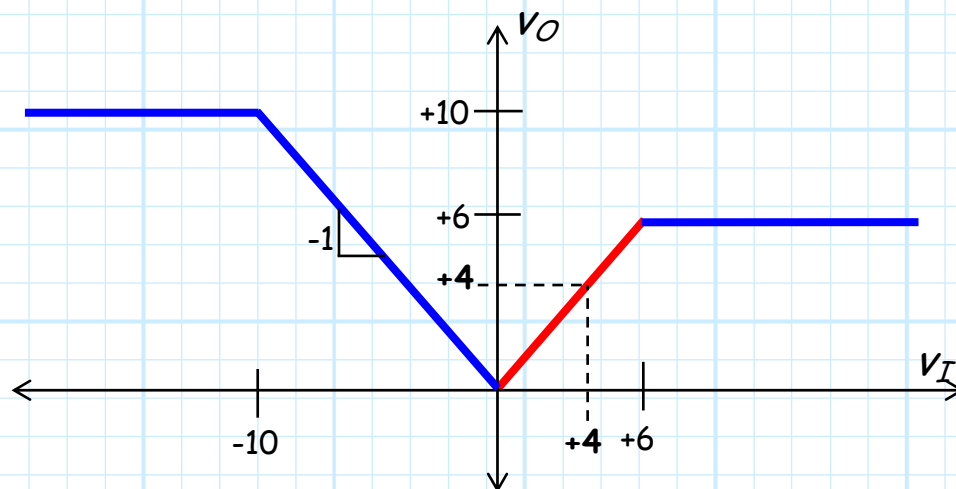
Since $v_I = 4.0$ volts is greater than zero, but less than 6.0 V, ($0 < v_I < 6.0$) the output voltage during this time period is $v_O = v_I = 4.0$ V:




$$v_O = 4.0 = \begin{cases} 6.0 & \text{for } v_I > 6.0 \\ v_I & \text{for } 0 < v_I < 6.0 \\ -v_I & \text{for } -10.0 < v_I < 0 \\ 10.0 & \text{for } v_I < -10.0 \end{cases}$$

What is the output now?

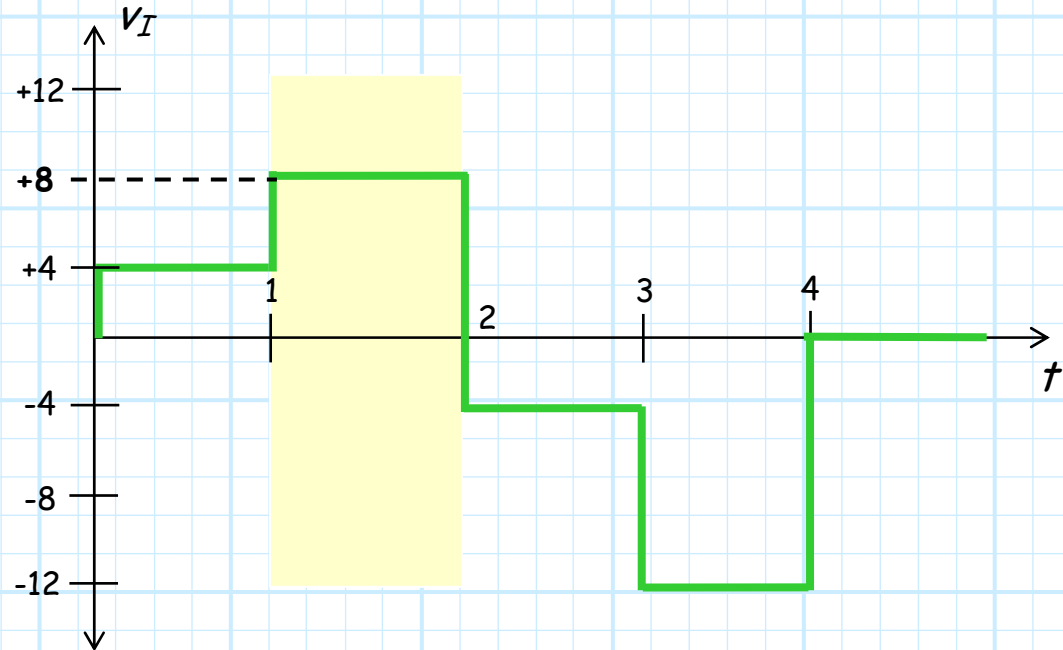Now for time $1 < t < 2$, the input voltage is **8.0 V**



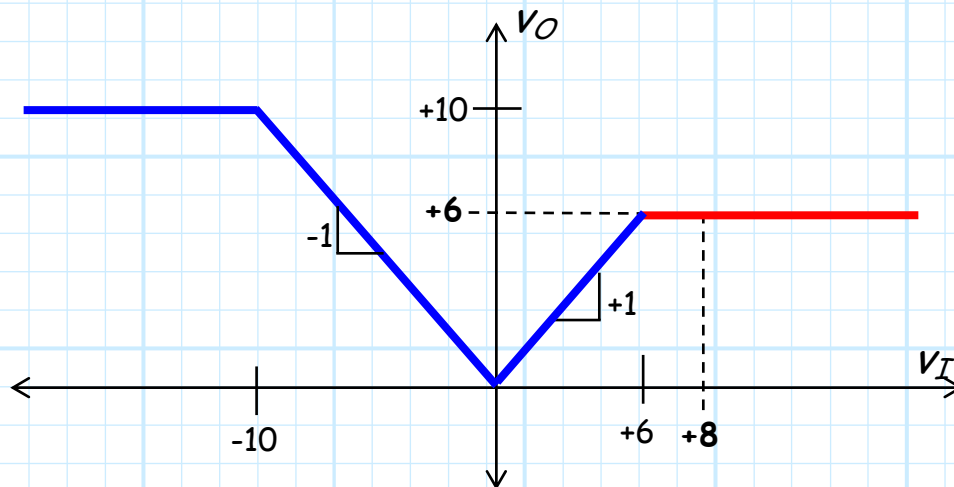
Since $v_I = 8.0$ volts is greater than 6.0 V, ($v_I > 6.0$) the output voltage during this time period is $v_o = 6.0$ V:




$$v_o = 6.0 = \begin{cases} 6.0 & \text{for } v_I > 6.0 \\ v_I & \text{for } 0 < v_I < 6.0 \\ -v_I & \text{for } -10.0 < v_I < 0 \\ 10.0 & \text{for } v_I < -10.0 \end{cases}$$

The hardest one yet!

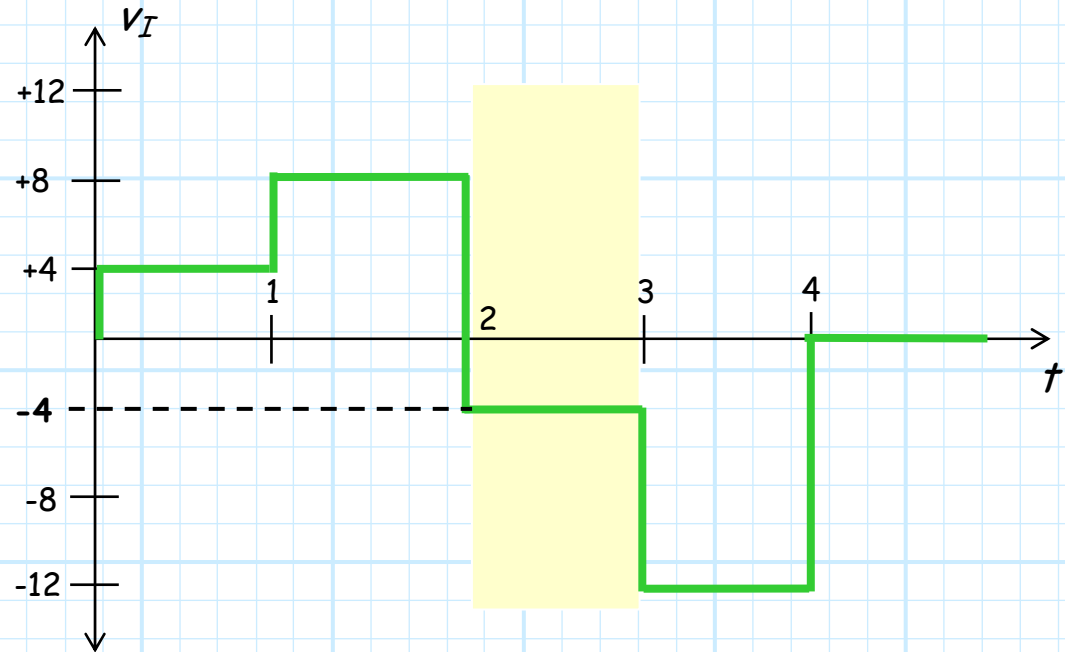Now for time $2 < t < 3$, the input voltage is **-4.0 V**.



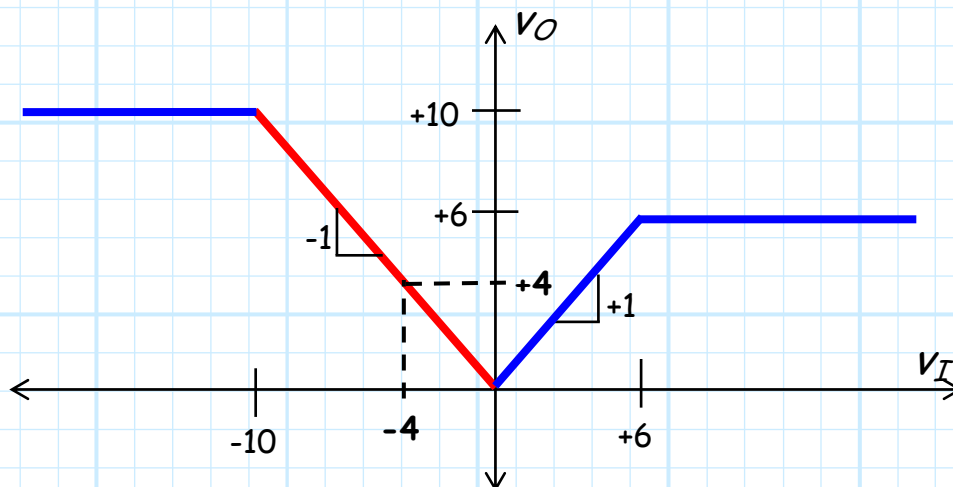
Since $v_I = -4.0$ volts is less than 0 V but greater than -10.0 V, ($-10 > v_I > 0$) the output voltage during this time period is $v_O = -v_I = +4.0$ V:




$$v_O = 4.0 = \begin{cases} 6.0 & \text{for } v_I > 6.0 \\ v_I & \text{for } 0 < v_I < 6.0 \\ -v_I & \text{for } -10.0 < v_I < 0 \\ 10.0 & \text{for } v_I < -10.0 \end{cases}$$

One last bit of scholarly effort

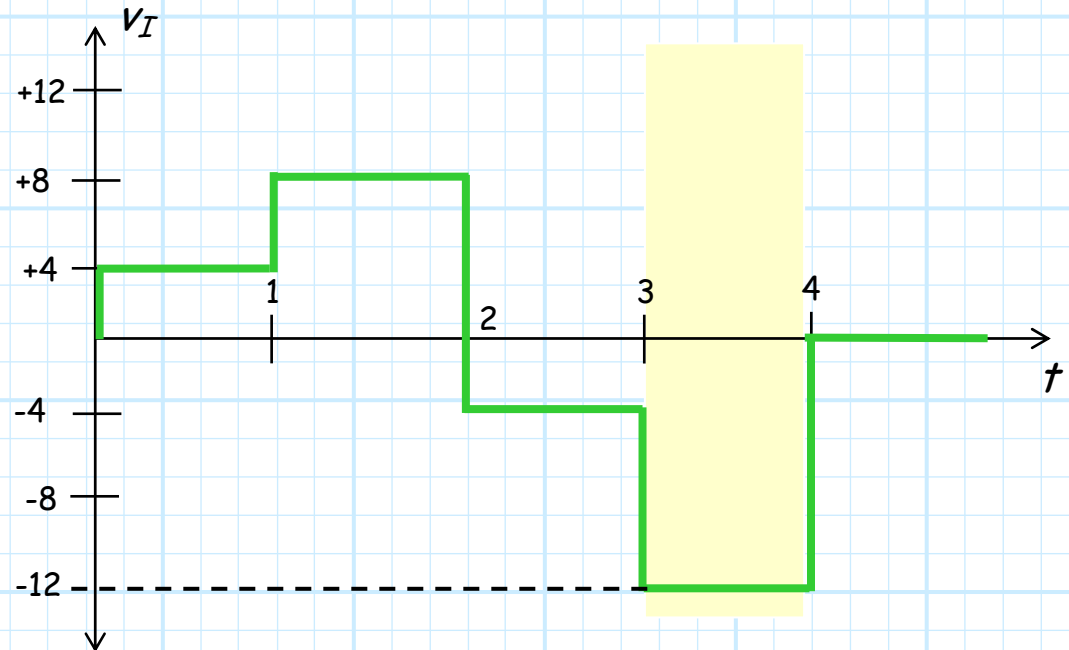Now for time $3 < t < 4$, the input voltage is -12.0 V



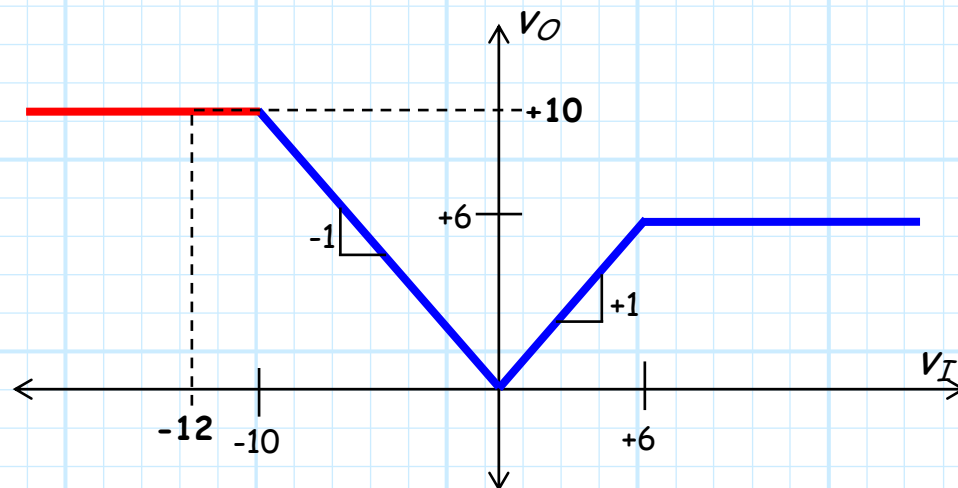
Since $v_I = -12.0$ volts is less than -10.0 V , ($v_I < -10.0$) the output voltage during this time period is $v_o = 10.0 \text{ V}$:




$$v_o = 10.0 = \begin{cases} 6.0 & \text{for } v_I > 6.0 \\ v_I & \text{for } 0 < v_I < 6.0 \\ -v_I & \text{for } -10.0 < v_I < 0 \\ 10.0 & \text{for } v_I < -10.0 \end{cases}$$

Put the pieces together; our output is revealed




Thus, we find that the
output signal is:

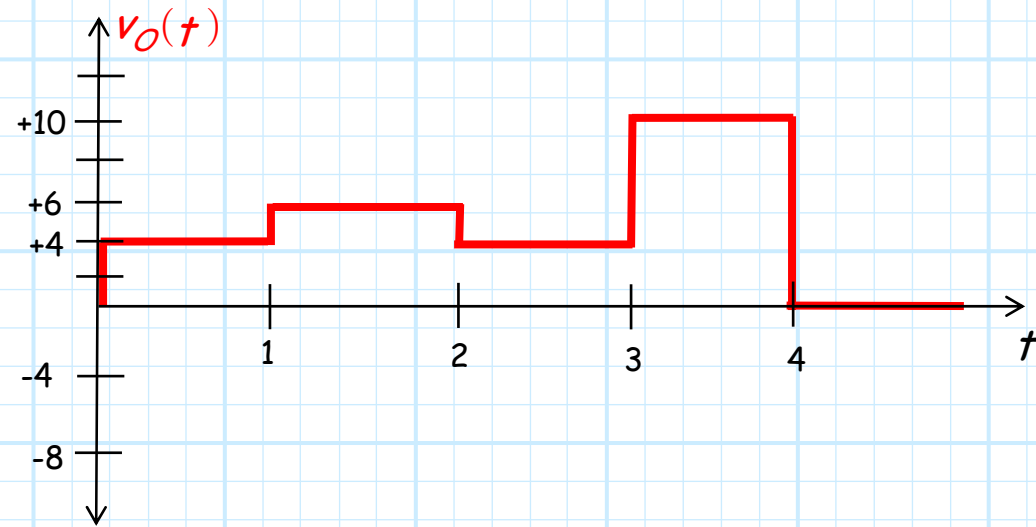

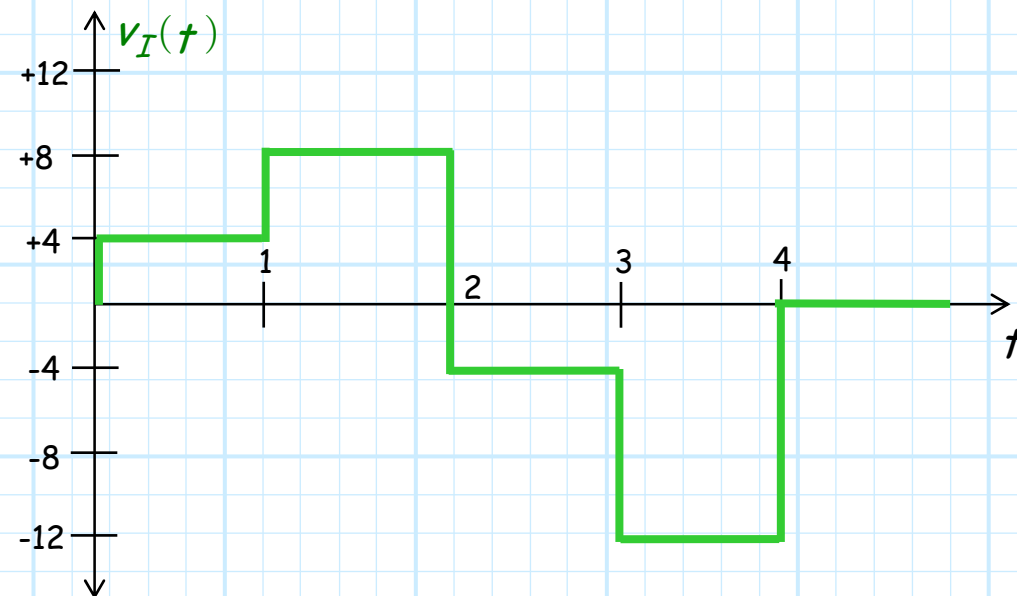That is, the output when
this is the input signal.




Make this make sense to you

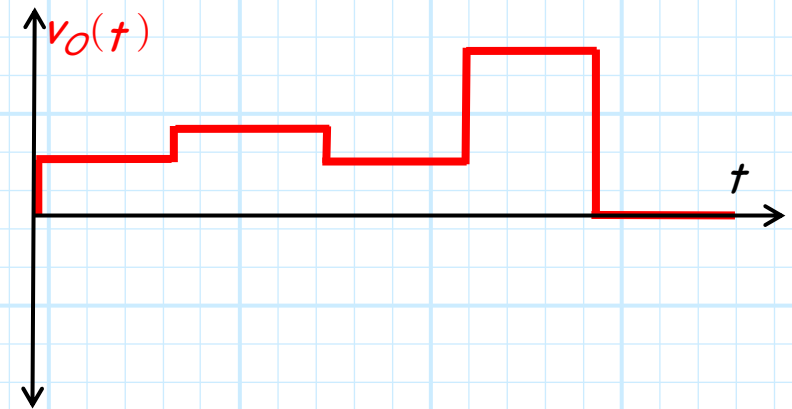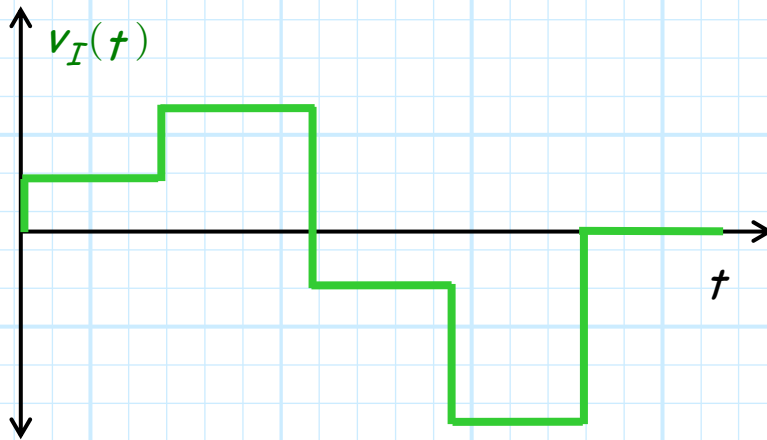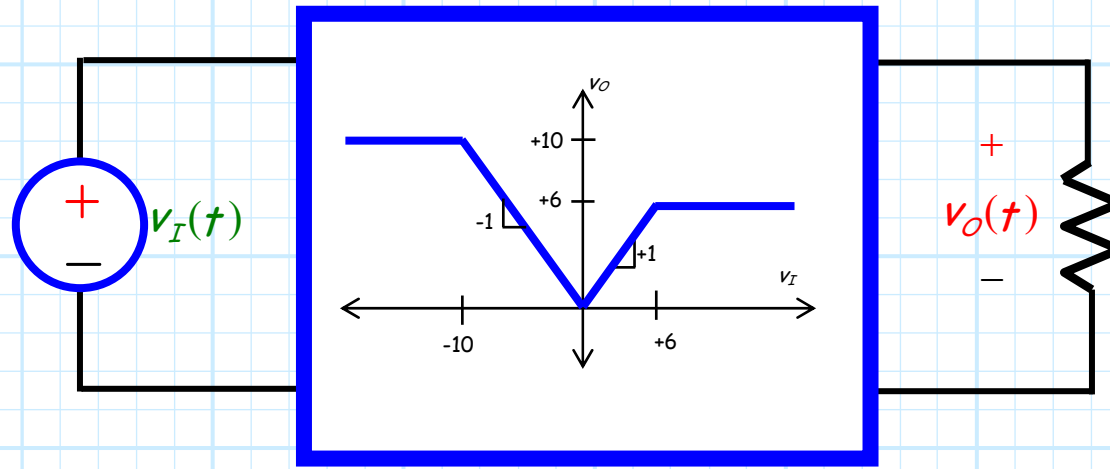


Power Supplies

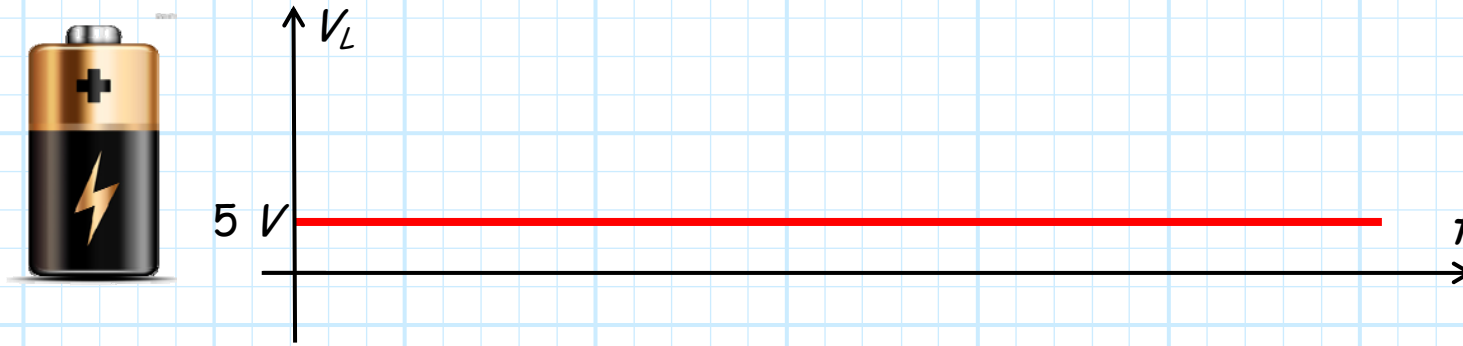Most modern electronic circuits and devices require one or more relatively **low DC voltages** (e.g., 5.0 V) for biasing and for supplying power to the circuit.



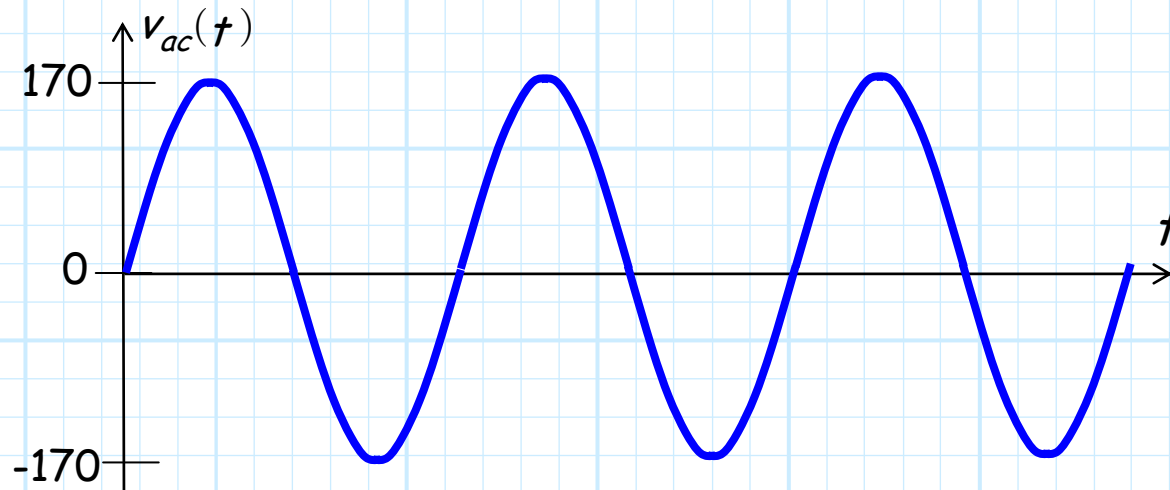Big Problem → Our electrical power distribution system provides a **high-voltage AC output**—a 120 V_{rms} , 60Hz sinewave!




The power supply



Thus, a major component in electronic systems (e.g., computers, televisions, etc.) is the **power supply**.

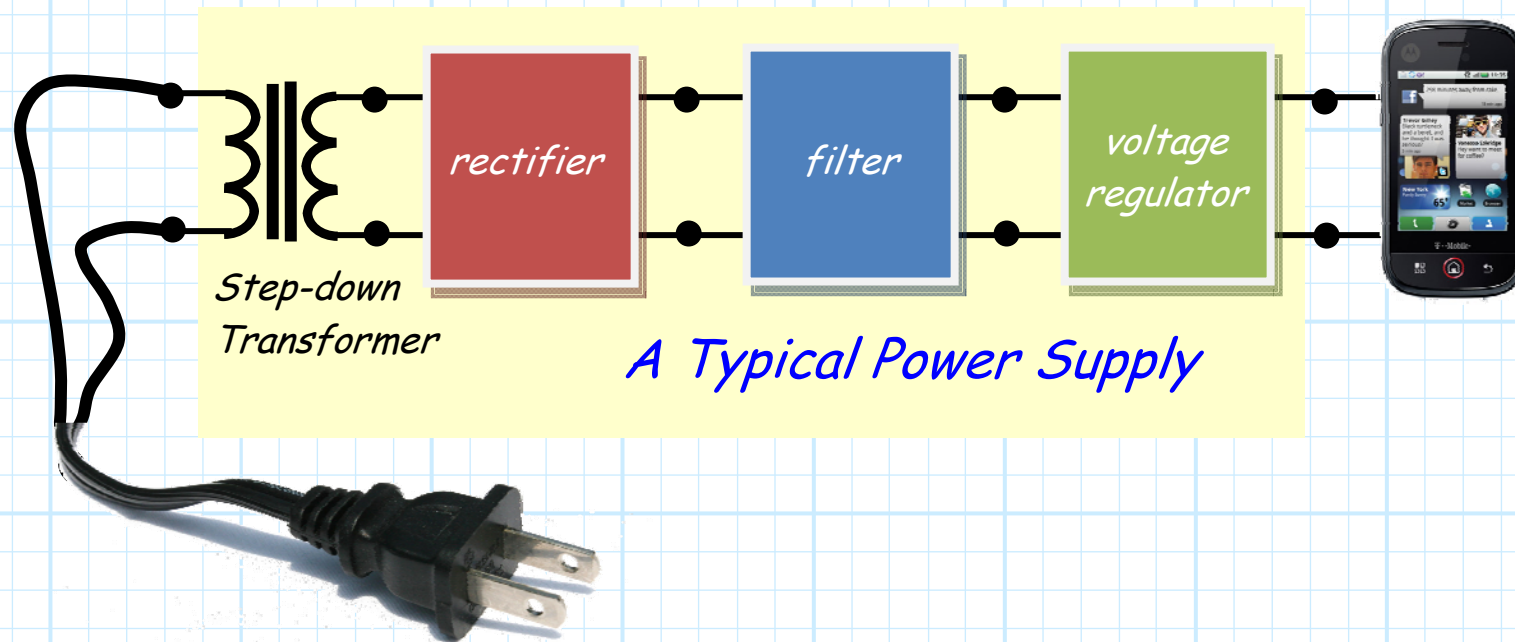The purpose of the power supply is simply to **convert high voltage AC** into one or more **low DC voltages**.




The functional schematic of a power supply

A typical power supply consists of four major sections:

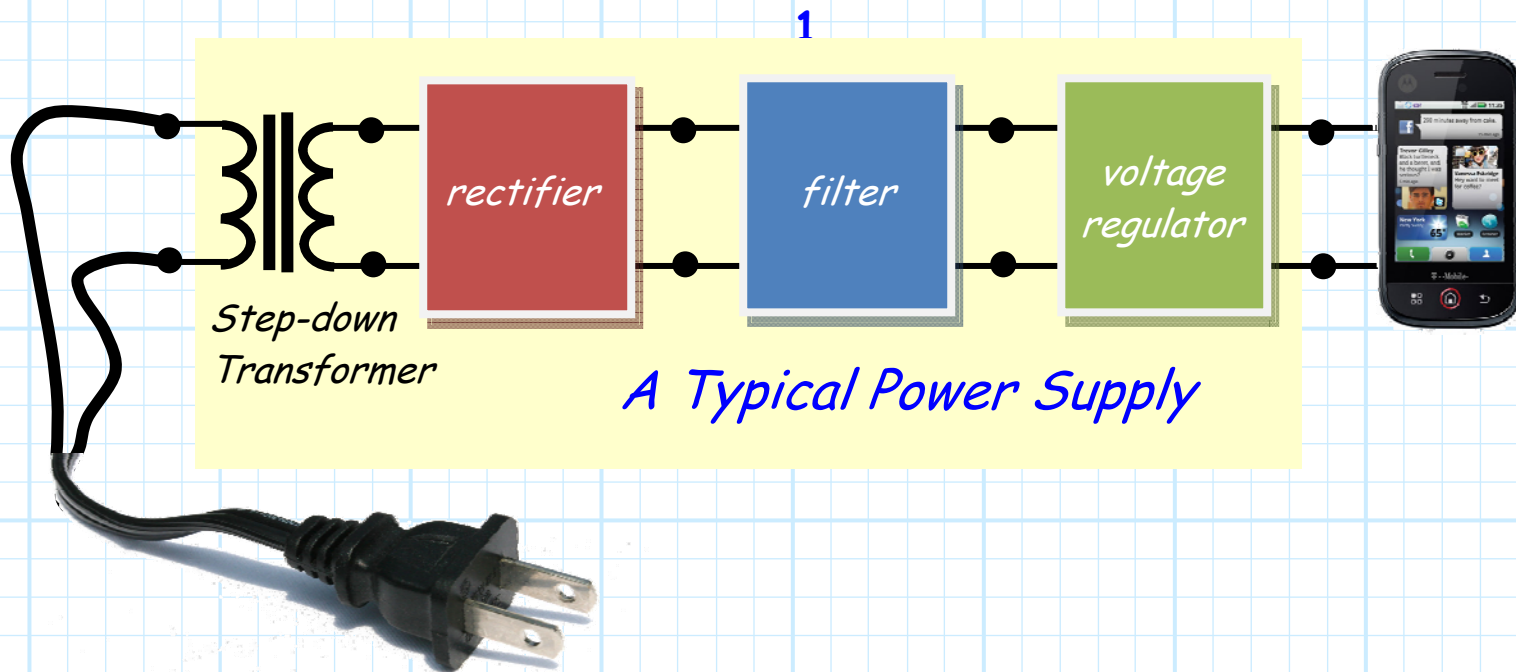1. Step-Down Transformer
2. Signal Rectifier
3. Filter
4. Voltage Regulator

Let's look at each of these devices individually!




1. The Step-Down Transformer



A voltage $120 V_{rms}$ is simply too big!

The first thing to be accomplished is to "step-down" the AC to a more manageable (e.g., safe) level.

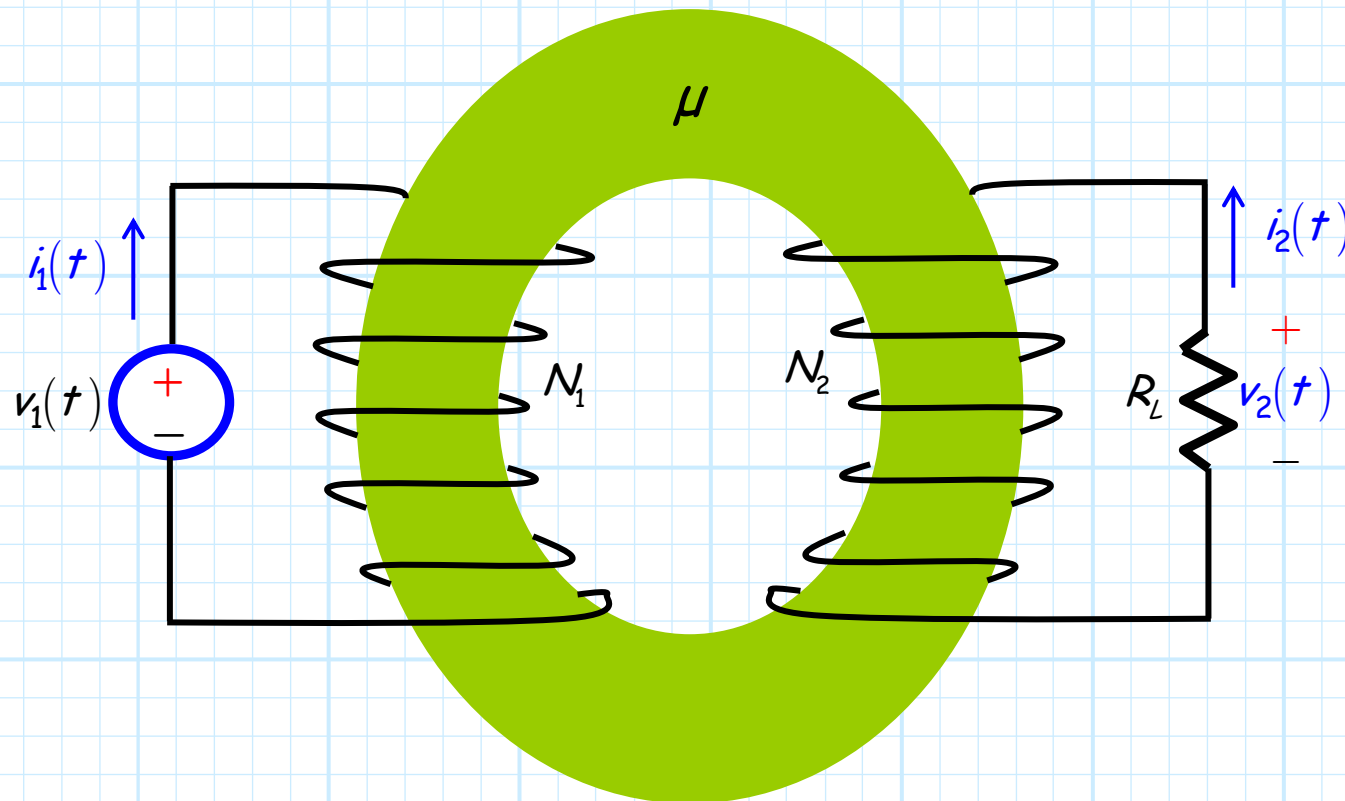
We do this with a **step down transformer**.



You remember—don't you?

You will recall that the important design parameters of a transformer are the number of “turns” on each side of the transformer.

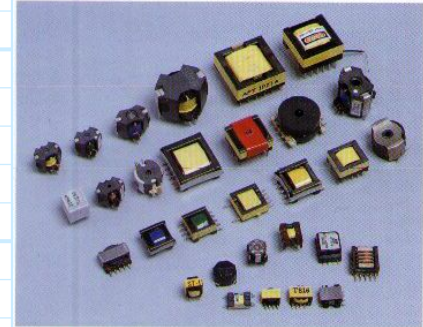The integer value N_1 represents the number of turns on the **primary** side, whereas N_2 represents the number of turns on the **secondary** side.



The voltage on the **secondary** side is related to the voltage on the **primary** side as:

$$v_2(t) = \frac{N_2}{N_1} v_1(t)$$



Thus, if we wish to **step-down** the voltage (i.e., make $v_2(t) < v_1(t)$), we need to make the number of primary turns **larger** than the number of secondary turns (i.e., $N_1 > N_2$).

→ **Typically**, a step-down transformer will lower the AC voltage to around **30**
 V_{rms} .

And Michael Faraday never even attended college—so now what's your excuse?

Remember, a transformer is a fundamental application of **Faraday's Law**—one of Maxwell's equations!

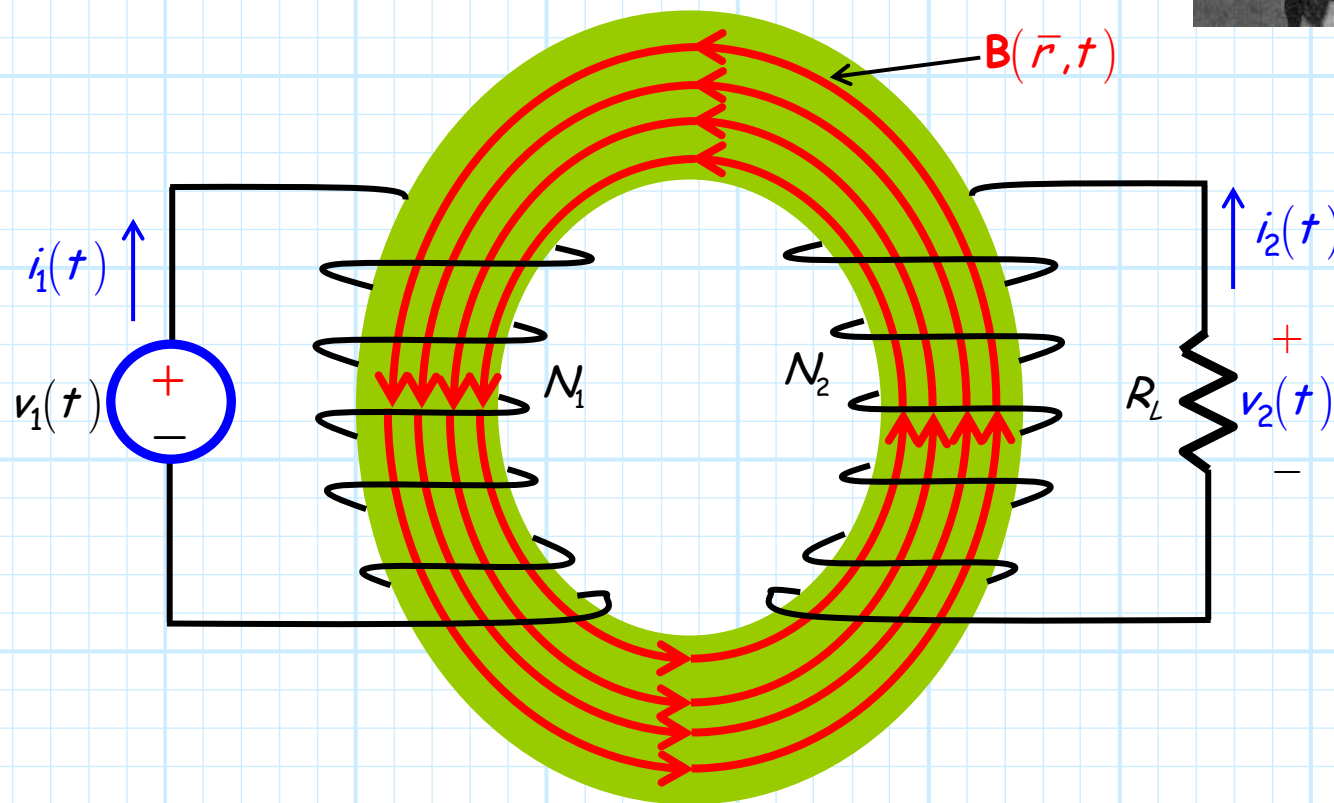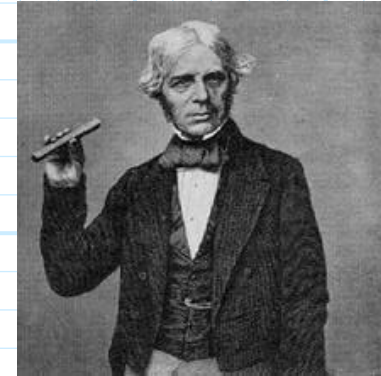
$$\oint_{C_1} \mathbf{E}(\vec{r}) \cdot d\vec{\ell} = -\frac{\partial}{\partial t} \iint_{S_1} \mathbf{B}(\vec{r}, t) \cdot d\vec{s}$$




Pure AC; no DC

Recall that the output of the step-down transformer is a **sinusoid**—a “pure” AC signal.

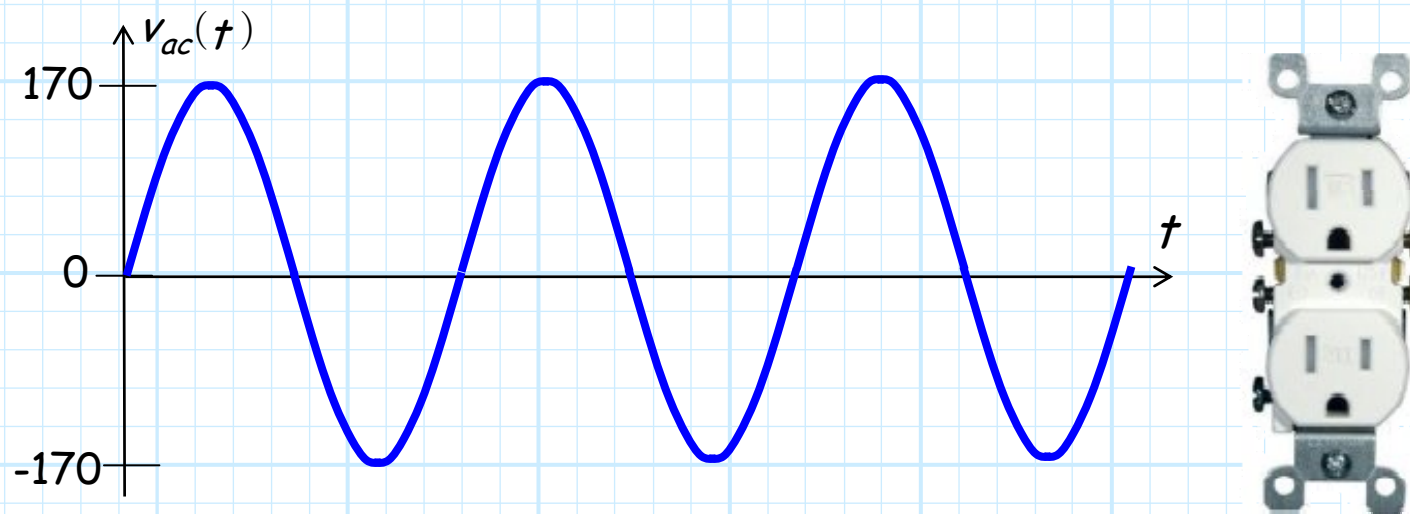In other words, the output has **no DC component**.




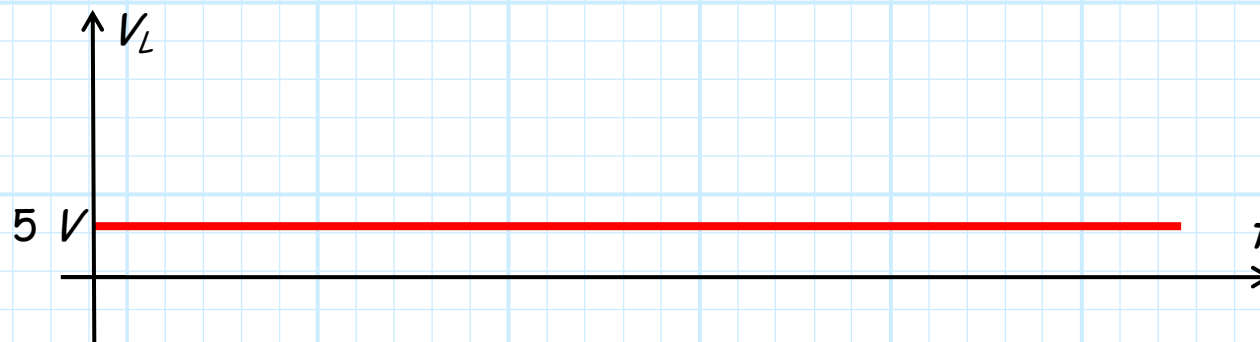But this is a problem, as we need a **DC signal** at the power supply output!



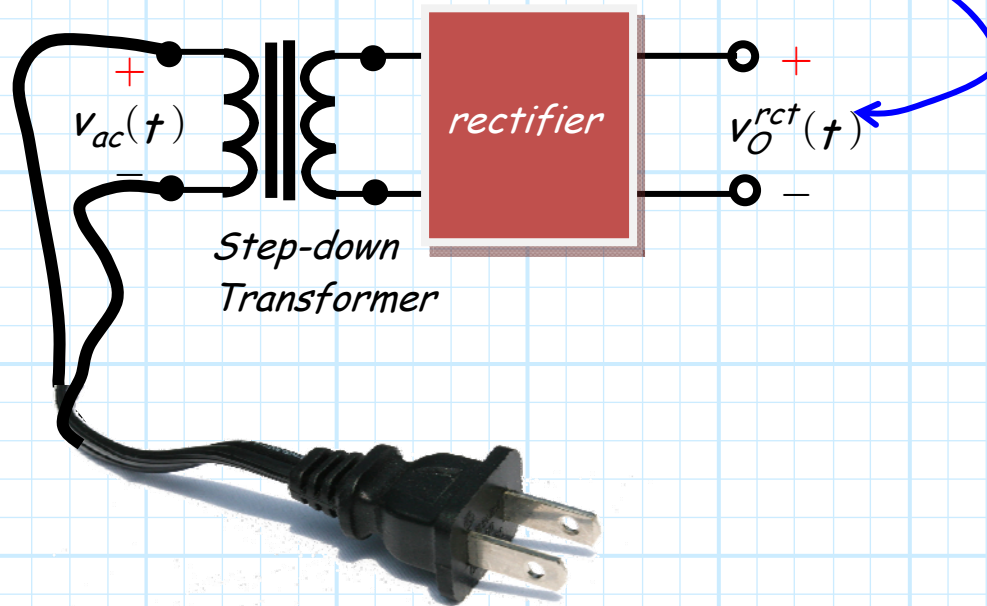2. The Signal Rectifier

This is where the signal rectifier comes in—its job is to take an AC signal, and produce a signal with a DC component.



Q: *So, the output of a rectifier is a DC signal?*

A: **NO!** I didn't say that! The output of a rectifier has a **DC component**.

However, it likewise has an **AC component**—the signal output is still **time varying!**

AC/DC

Q: Huh?

A: Most signals are **neither** "purely" AC (a time-varying signal with a **time-averaged** value of **zero**), or "purely" DC (a **constant** with respect to time).



Most signals are a **combination** of AC and DC—they have both an **AC component** and a **DC component**.

I.E., they can be expressed as the **sum** of a DC and AC signal:

$$v(t) = V_{DC} + v_{ac}(t)$$

The **DC component** of a signal $v(t)$ is simply its **time-averaged** value:

$$V_{DC} = \frac{1}{T} \int_0^T v(t) dt$$

and the **AC component** of a signal $v(t)$ is simply the signal $v(t)$ with its **DC component removed**:

$$v_{ac}(t) = v(t) - V_{DC}$$

Most time-varying signals are *not* AC signals

The important fact about an **AC** component is that it has a **time-averaged value of zero!**

$$\begin{aligned}\frac{1}{T} \int_0^T v_{ac}(t) dt &= \frac{1}{T} \int_0^T (v(t) - V_{DC}) dt \\ &= \frac{1}{T} \int_0^T v(t) dt - \frac{1}{T} \int_0^T V_{DC} dt \\ &= V_{DC} - V_{DC} \frac{1}{T} \int_0^T dt \\ &= V_{DC} - V_{DC} \frac{1}{T} (T - 0) \\ &= V_{DC} - V_{DC} \\ &= 0\end{aligned}$$

Pay attention: an **AC** signal is defined as a **time-varying** signal whose **average value is zero!**

Please tell me this is obvious


For **example**, a signal might have the form: $v(t) = 0.66 + 0.001\cos\omega t$

It is **hopefully evident**
that this signal has a
DC component:

$$\begin{aligned} V_{DC} &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{T} \int_0^T (0.66 + 0.001\cos\omega t) dt \\ &= \frac{0.66}{T} \int_0^T dt + \frac{0.001}{T} \int_0^T \cos\omega t dt \\ &= 0.66 + 0 = 0.66 \end{aligned}$$

and an **AC component**:
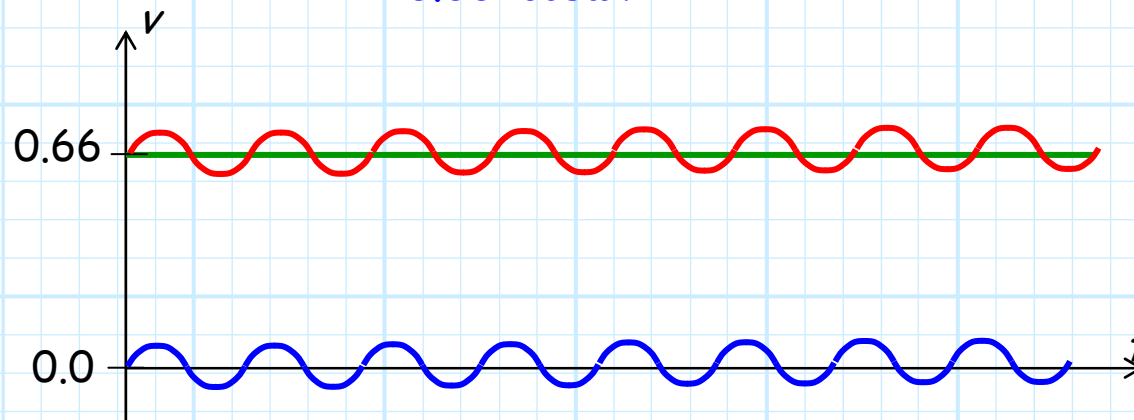
$$\begin{aligned} v_{ac}(t) &= v(t) - V_{DC} \\ &= (0.66 + 0.001\cos\omega t) - 0.66 \\ &= 0.001\cos\omega t \end{aligned}$$




A time-varying signal with an DC component

Since the **input** to the rectifier is a 60Hz “sine wave”, it has no DC component—the time averaged value of a sine function is **zero**.

Thus, the input is a “pure” AC signal.


The **output** of a rectifier is likewise time-varying—it has an AC component.

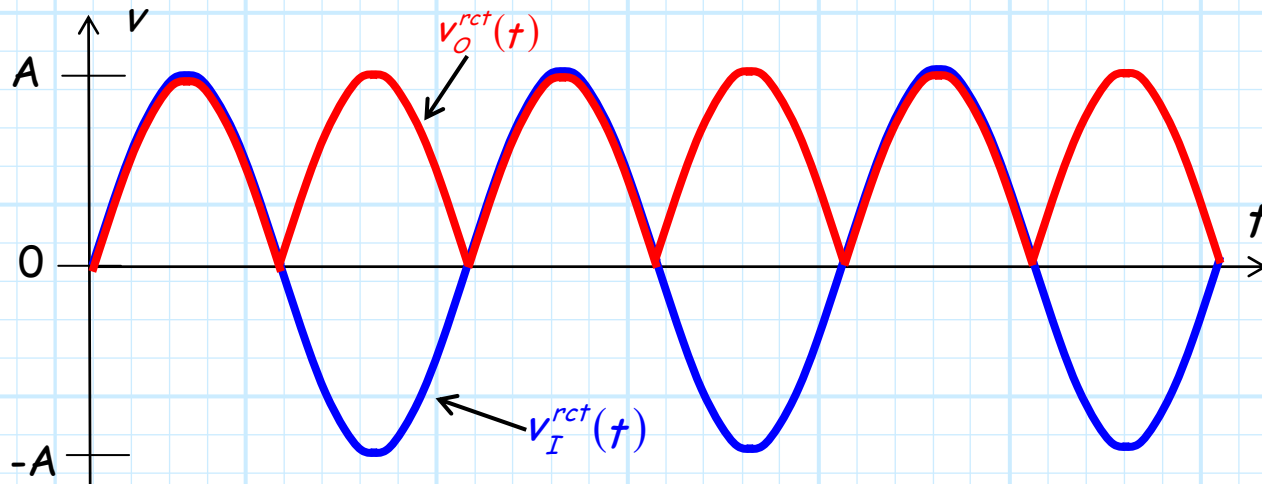However, the time-averaged value of this output is **non-zero**—the **output** also has a **DC component**!



The Rectifier creates a DC component; but the AC component is still there

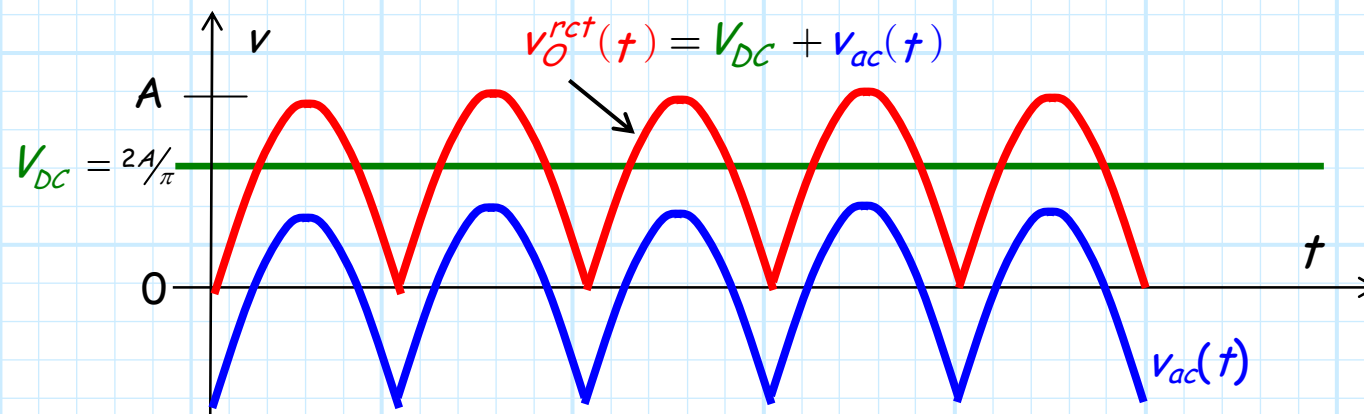Thus, a rectifier creates a **DC component** on the output, a component that does not exist on the **input!**





3. The Filter

So, the rectifier has added a **DC component** to the signal—but the output of the rectifier is not DC, it has an **AC component** as well.

The job of any filter is to **remove unwanted components**, while allowing the **desired components** to pass through.

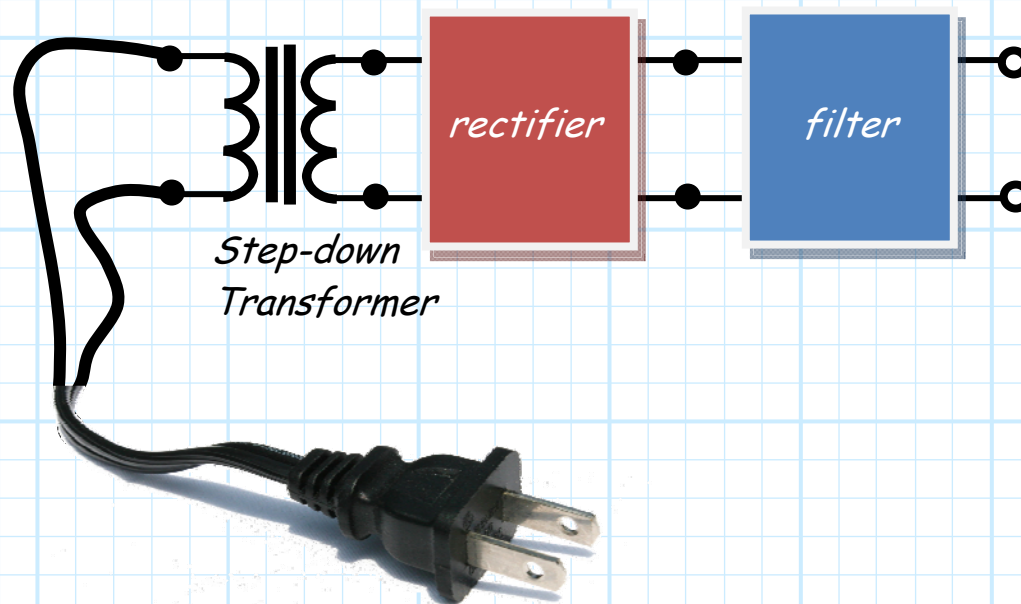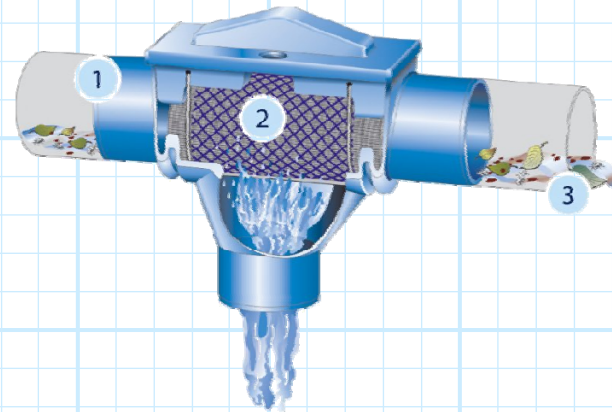For this **electrical filter**, the **unwanted component** is the **AC signal**, and the **desired component** is the **DC signal**!




We do this with what is essentially a **low pass filter**.

The DC component passes through the filter unchanged

Ideally, the low-pass filter would **eliminate** the **AC component**, leaving only a constant, **DC signal**.

However, a low-pass filter will typically just **attenuate** the **AC signal**, leaving a **small AC component** at the filter output.

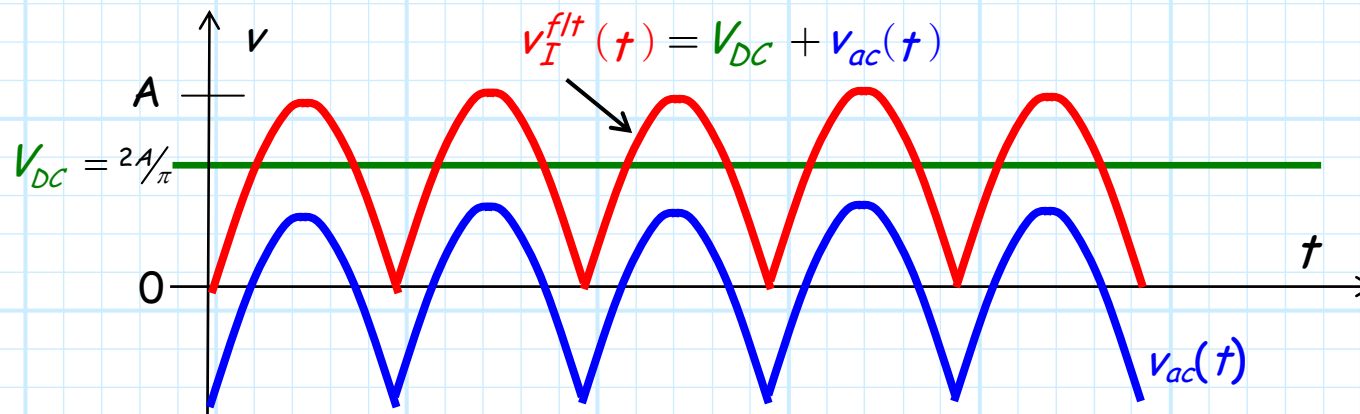
For example, the **output** of the rectifier is now the **input to filter**:



→ The **DC component** passes through the low-pass filter **unscathed**—it's the **same** at the output as the input.

Ripple voltage!

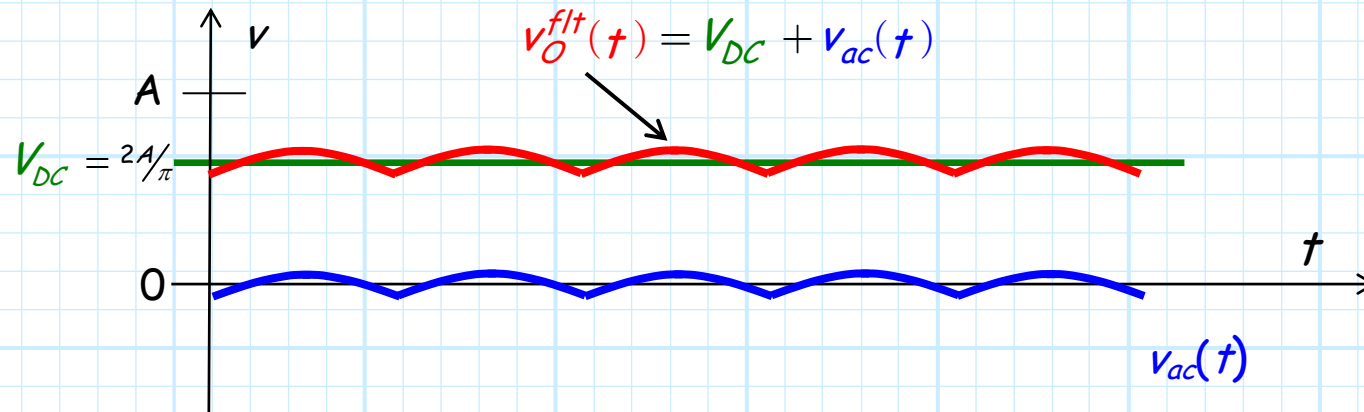But; the **AC** component is **greatly attenuated**. Thus, the output is **almost** a DC signal—it is a **DC signal** with a **small AC** “ripple voltage”.



Q: *Yikes! Our load (e.g., computer, HDTV, DVR, DVD, etc.) will **require** a better **regulated voltage** than that!*

Won't the "ripple voltage" cause all sorts of problems—if it is used to supply power to the load!


A: Yes, and it's **even worse** than that!

→ You see, the 120 V_{rms} , 60 Hz signal from our wall socket may **not be exactly** that!

It will be 60 Hz; it might not be 120 V_{rms}

Q: *You mean it might not be exactly 60 Hz?*

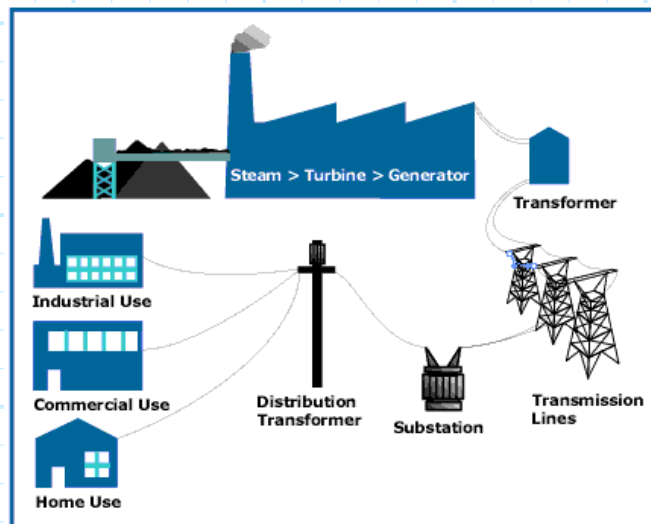A: Actually, a 60 Hz sinusoid is the one thing we **can** count on—the AC power signal **will** have a frequency of **exactly**, precisely 60Hz.



However, the **magnitude** of this AC power signal (nominally 120 V_{rms}) is a bit more problematic.

Power lines, transformers—all the **stuff** that the AC power must pass through—exhibit **resistance**.

The more **current** passing through the power system, the more this resistance results in a **voltage drop** (it's just **Ohm's Law** at work!).

→ As a result, the AC voltage at **your** wall plug will be only **approximately** 120 V_{rms} .

When all those air conditioners are "on"

Say after a brutally **hot** July day, it's still 93 degrees F at 8:30 p.m.

The whole town is at **home**; lights on, watching TV, playing Wii.

And, most importantly, running their **air conditioners!**



All this stuff requires **energy**—for this case, energy delivered at a **particularly high rate**.



Thus, the AC current flowing into all these cool and content homes is **particularly large**, meaning that the "Ohmic Loss"—the **voltage drop** that occurs between the power plant to your home—is likewise **particularly large**.

Therefore, the AC voltage at your wall socket on this **sweltering** day may be **significantly less** than $120 V_{rms}$!

It's all proportional to the AC power voltage

Q: *Is this a problem?*

A: Absolutely!


If the voltage of the AC power lessens, a **proportionate reduction** will occur at the output of the step-down transformer.

Therefore the **DC component** at the output of the rectifier (and thus at the output of the filter) will also **reduce proportionately!**

Q: *So in addition to the ripple voltage, the DC component of the signal can drift up or down—isn't this DC supply voltage horribly regulated?*

A: That's exactly correct—which is why we need, as the last component of the power supply, a **voltage regulator!**

4. The Voltage Regulator

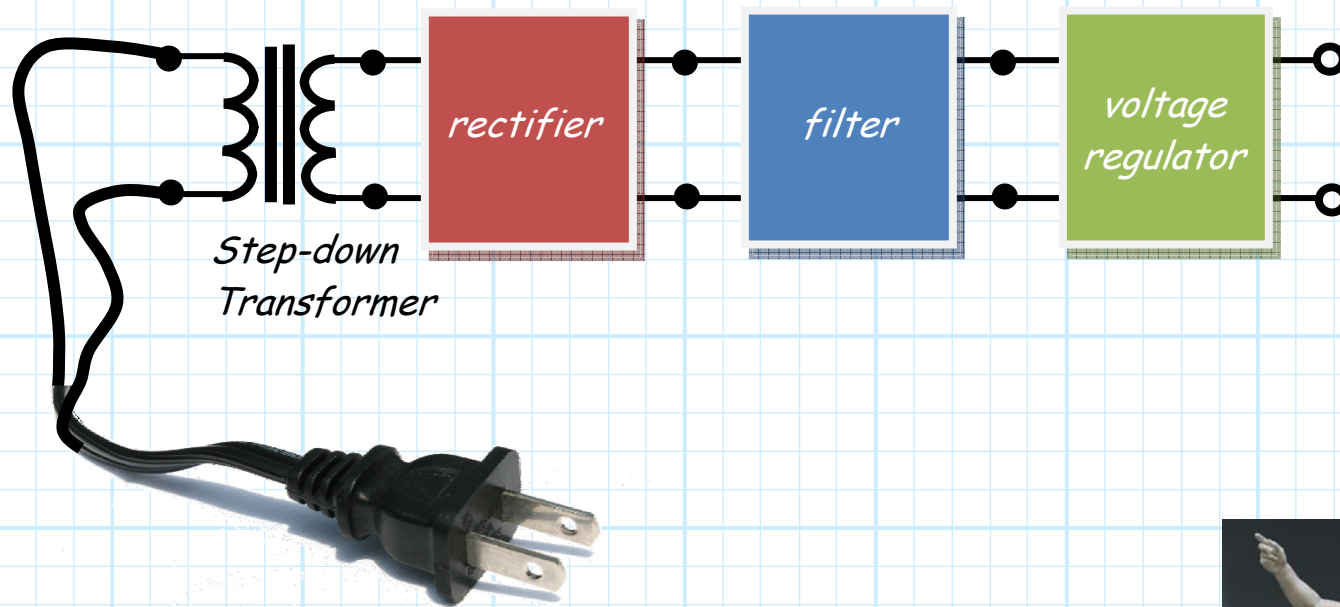

This regulator of course provides at its output a **regulated DC voltage**—a voltage that stays a **rock-solid** constant, regardless of **how many air-conditioners** are running (i.e., great line regulation).

And, regardless of the current drawn by the load (great **load regulation**).




This **voltage regulator** could of course either be a **linear** or **switching** regulator.


We often need several regulators

Moreover, we find that the **power supplies** of most complex loads (e.g., computers, TVs, etc.) employ components that require **several different DC** source voltages.

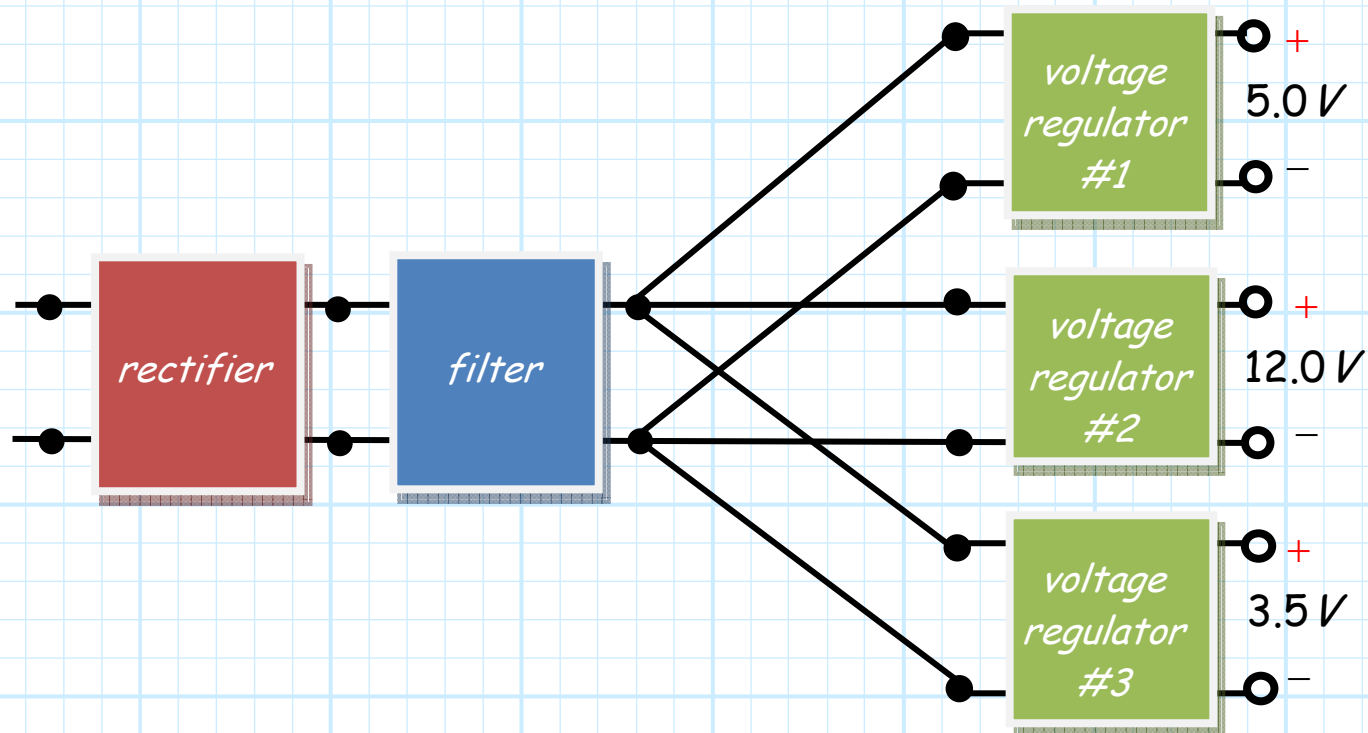As a result, power supplies often use **many regulators**, each with a **different DC voltage** :



This circuit will be on the final

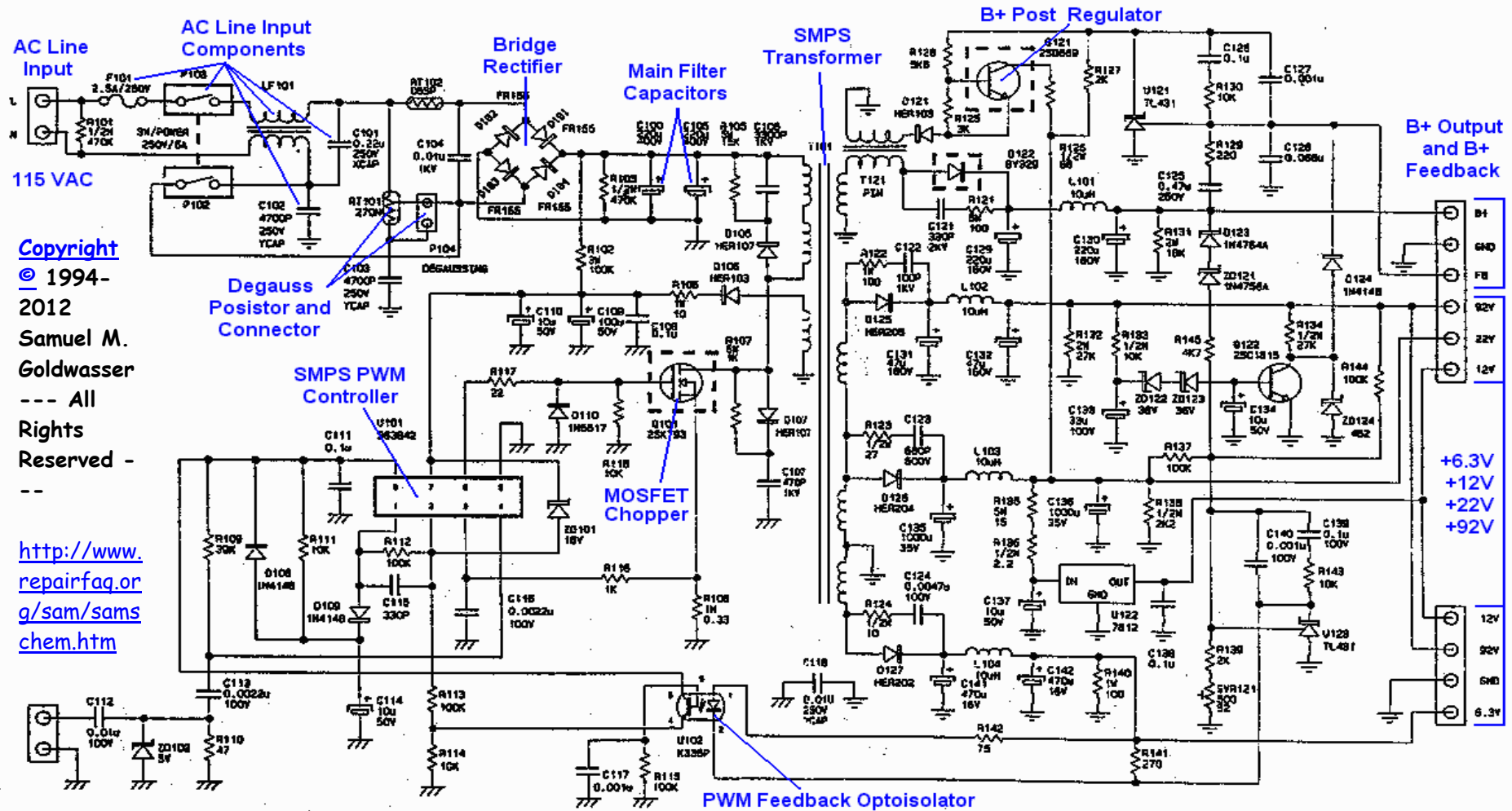

Copyright © 1994-2012 Samuel M. Goldwasser --- All Rights Reserved --
<http://www.repairfaq.org/sam/samschem.htm>

Typical Switchmode Power Supply for Small SVGA Color Monitor


The power supply: make sure you know why it's needed; what it does; and how it does it!

Signal Rectification

An important application of junction diodes is **signal rectification**.


There are **two** types of signal rectifiers, **half-wave** and **full-wave**.

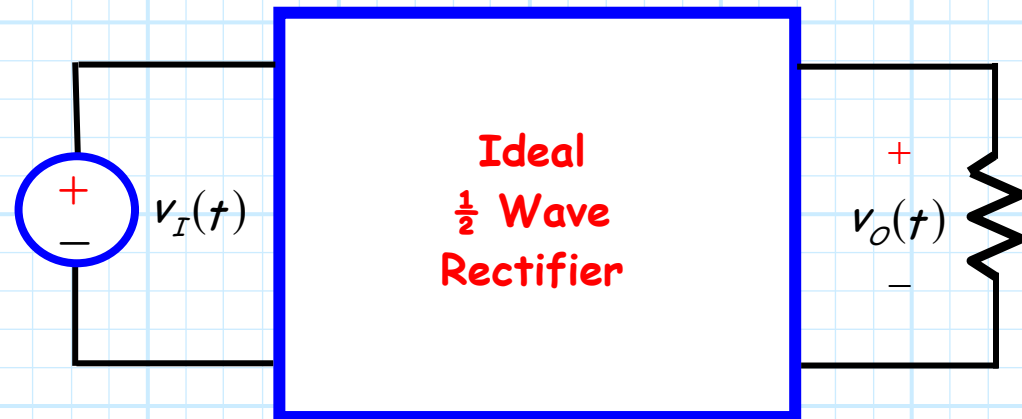Let's first consider the **ideal half-wave rectifier**.




It is a circuit with the transfer function $v_O = f(v_I)$:
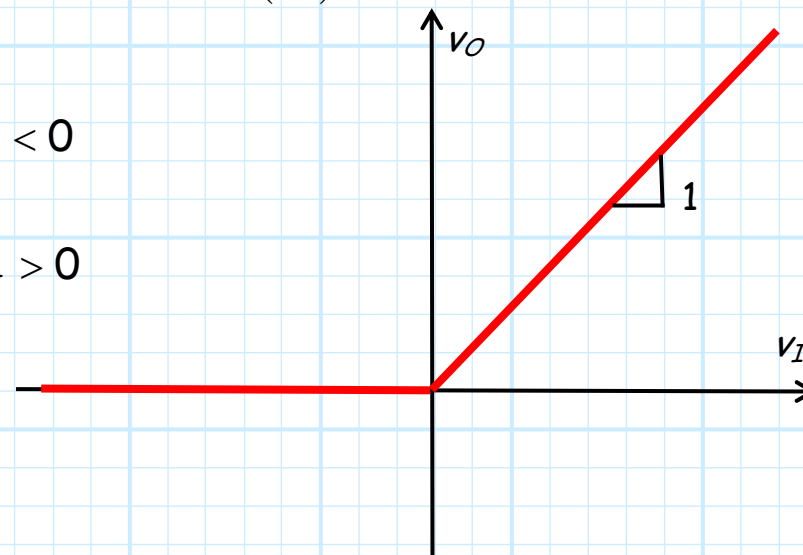
$$v_O = \begin{cases} 0 & \text{for } v_I < 0 \\ v_I & \text{for } v_I > 0 \end{cases}$$



It's the same—or zero

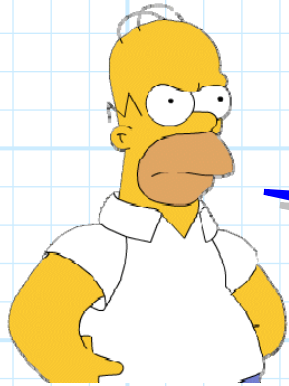


Pretty simple! **When** the input is negative, the output is **zero**, whereas **when** the input is positive, the output is the **same** as the input.

Q: *Pretty **pointless** I'd say.*

*This appears to be your most **useless** circuit yet.*

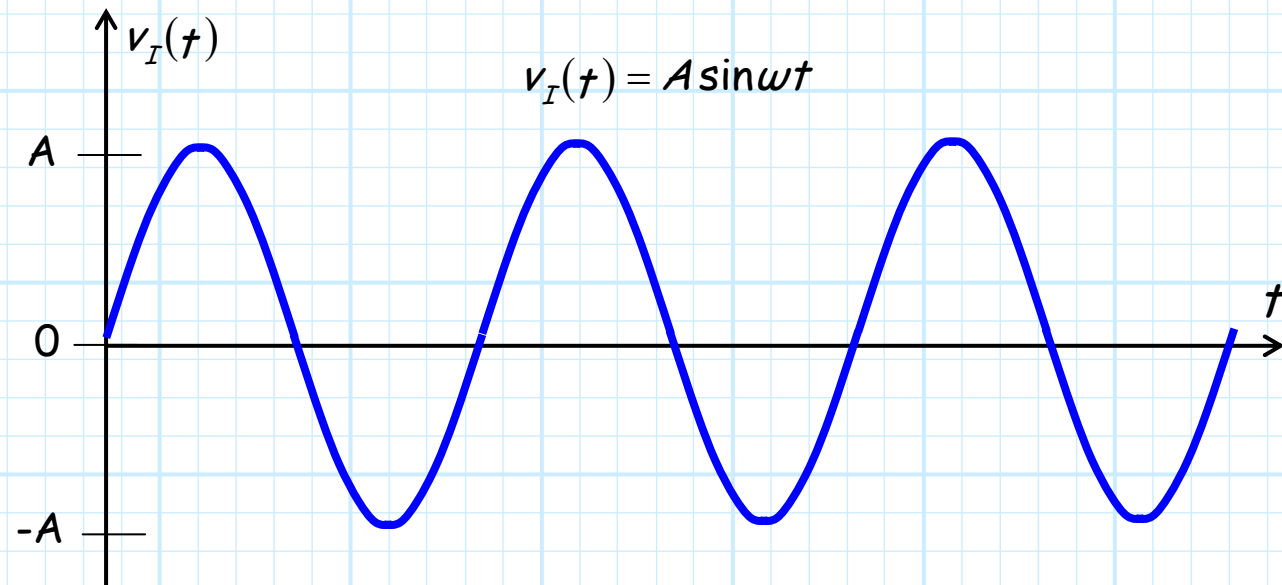A: To see **why** a half-wave rectifier is useful, consider the **typical** case where the input source voltage is a **sinusoidal** signal with **frequency** ω and peak **magnitude** A :




Half a sine wave




Think about what the **output** of the half-wave rectifier would be!

Remember the rule: when $v_I(t)$ is **negative**, the output is **zero**,
when $v_I(t)$ is **positive**, the output is **equal** to the input.

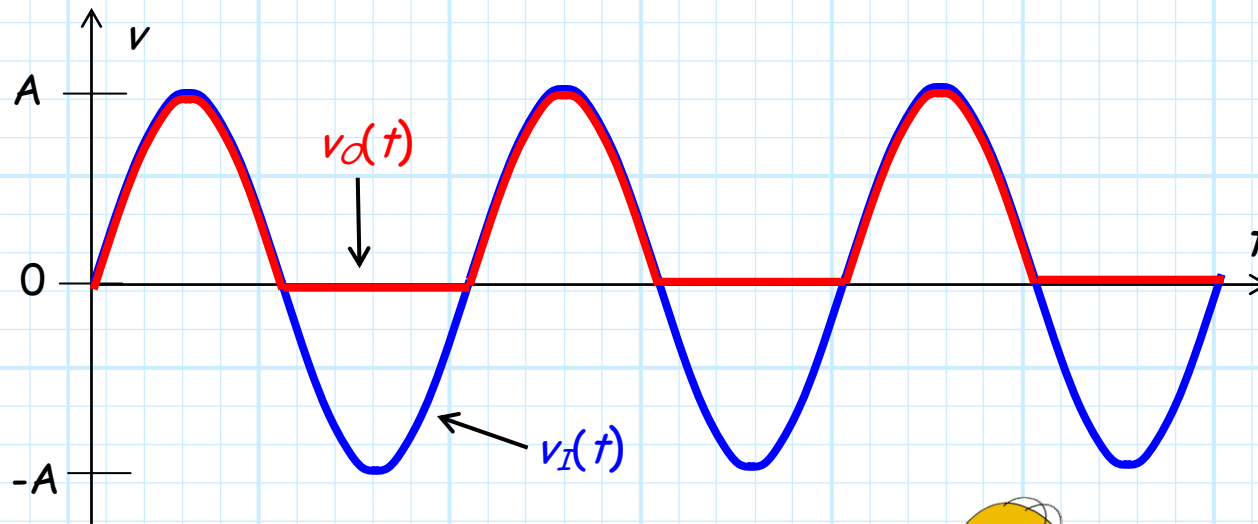The **output** of the half-wave rectifier for **this** example is therefore:



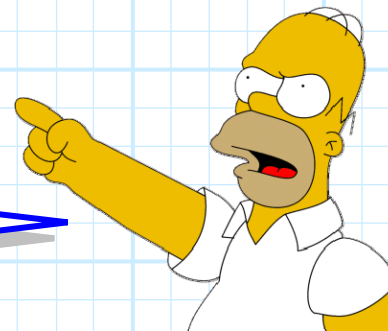Q: A *half* a sine wave? What kind of lame signal is *that*?



The input is a pure AC signal...

A: Although it may appear that our rectifier had **little** useful effect on the input signal $v_I(t)$, in fact the difference between input $v_I(t)$ and output $v_O(t)$ is both **important** and **profound**.

To see how, consider first the **DC component** (i.e. the time-averaged value) of the **input** sine wave:

$$\begin{aligned}V_I &= \frac{1}{T} \int_0^T v_I(t) dt \\ &= \frac{1}{T} \int_0^T A \sin \omega t dt = 0\end{aligned}$$

Thus, (as you probably already knew) the **DC component** of a sine wave is **zero**—a sine wave is an **AC signal**!

...but the output has a DC component as well



Now, contrast this with the output $v_d(t)$ of our half-wave rectifier.

The DC component of the output is:

$$V_{DC} = \frac{1}{T} \int_0^T v_o(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt + \frac{1}{T} \int_{T/2}^T 0 dt = \frac{A}{\pi}$$

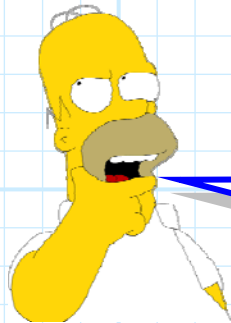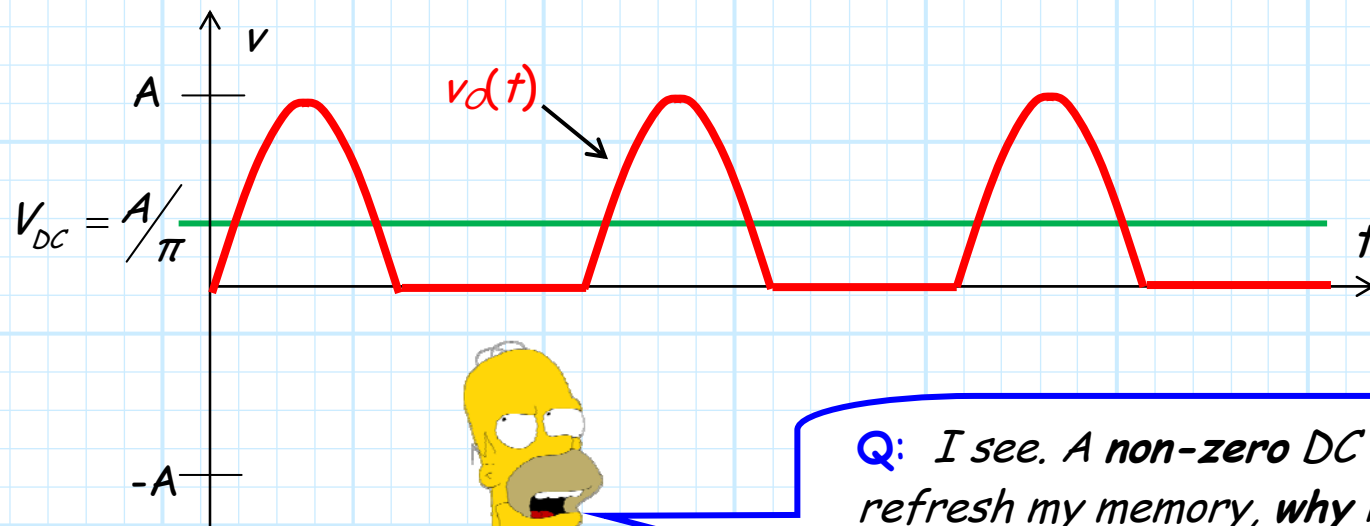Unlike the input, the output has a **non-zero (positive) DC component** ($V_{DC} = A/\pi$)!



Q: I see. A non-zero DC component eh? So refresh my memory, why is that important?


A DC component is required

A: Recall that the **power distribution system** we use is an **AC** system.

The source voltage $v_I(t)$ that we get when we plug our “**power cord**” into the wall socket is a 60 Hz **sinewave**—a source with a **zero DC component!**



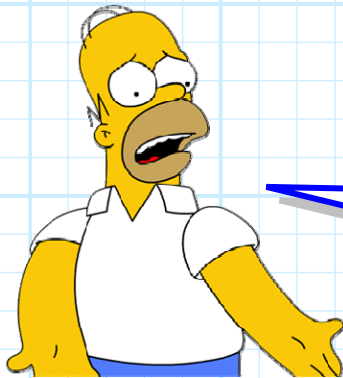The **problem** with this is that most **electronic devices** and systems, such as TVs, stereos, computers, etc., require a **DC voltage(s)** to operate!



Q: *But, how can we create a DC supply voltage if our power source $v_I(t)$ has no DC component??*


A: That's **why** the half-wave rectifier is so **important!**

It takes an **AC** source with **no DC** component and creates a signal with **both** a **AC** and **DC** component.


Remember this?

We can then pass the output of a half-wave rectifier through a **low-pass filter**, which **suppresses** the AC component but lets the DC value ($V_o = A/\pi$) pass through.

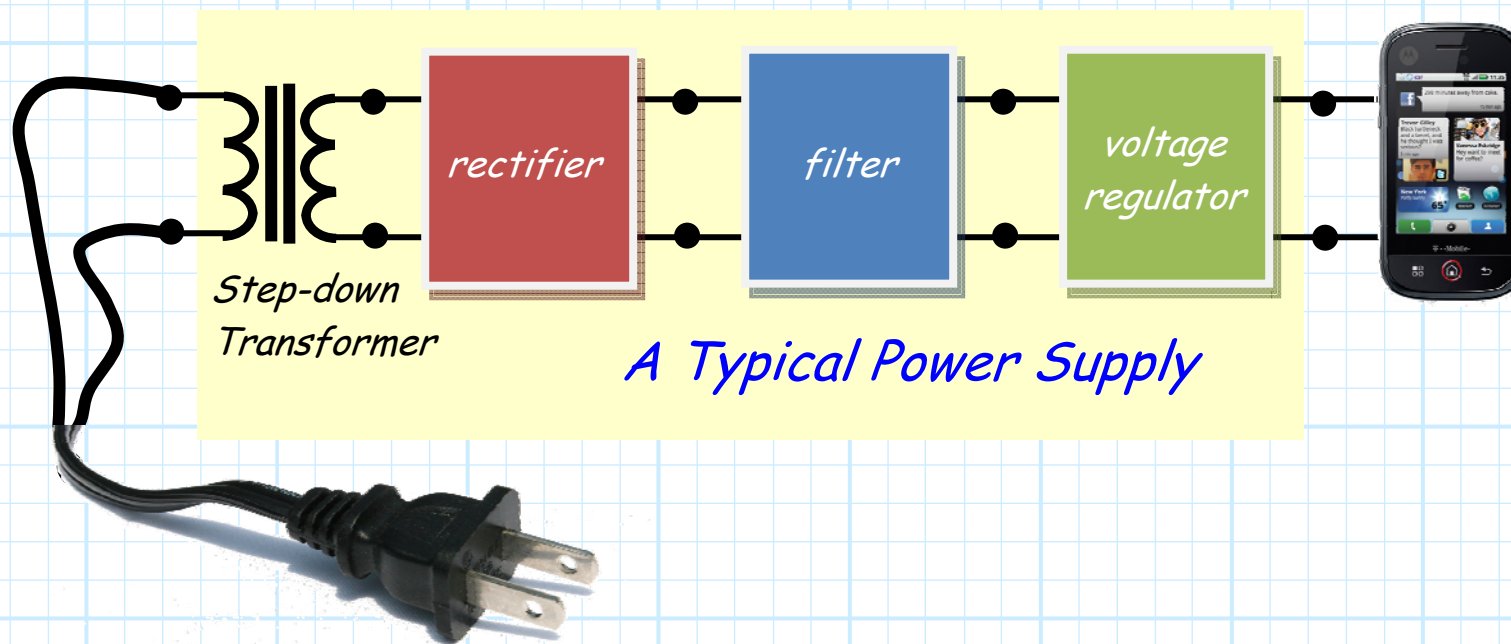
We then **regulate** this output and form a **useful DC voltage source**—one suitable for powering our electronic systems!



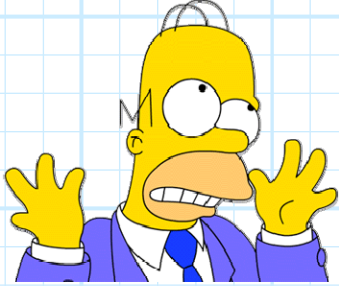An ideal rectifier requires an ideal diode



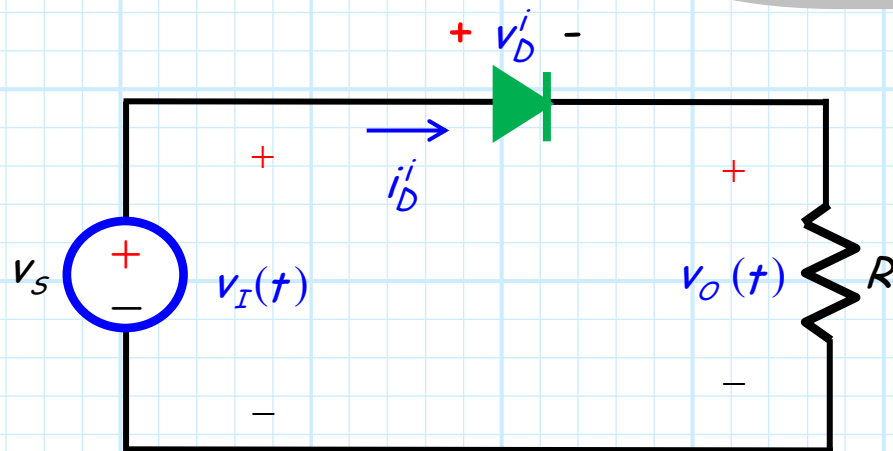
Q: OK, now I see why the ideal half-wave rectifier might be useful. But, is there any way to actually **build** this magical device?



A: An **ideal** half-wave rectifier can be "built" if we use an **ideal** diode.


If we follow the transfer function **analysis steps** we studied earlier, then we will find that this circuit is indeed an **ideal half-wave rectifier!**
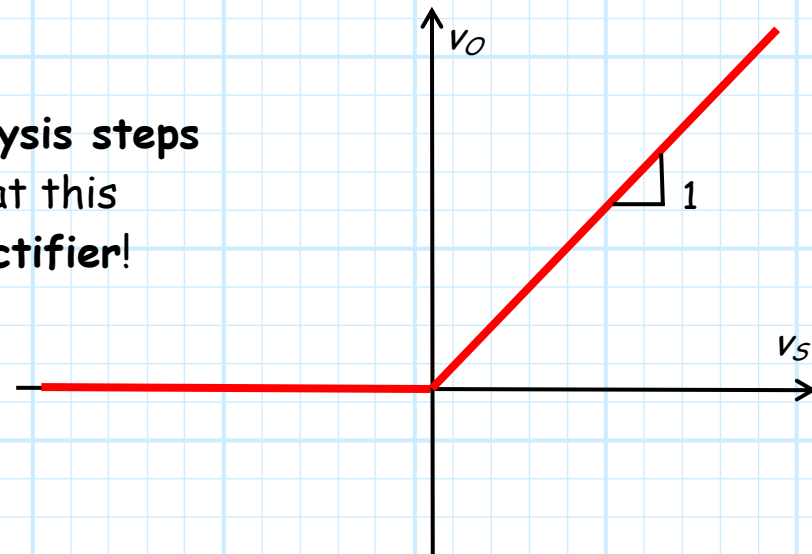
$$v_o = \begin{cases} 0 & \text{for } v_I < 0 \\ v_s & \text{for } v_I > 0 \end{cases}$$



But a junction diode works as well

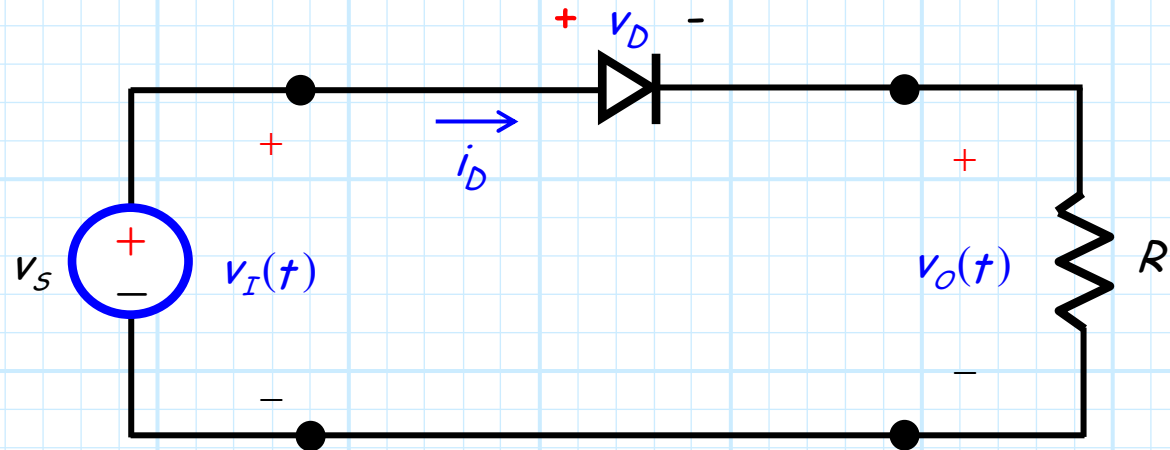Of course, since **ideal** diodes do **not** exist, we must use a **junction** diode instead:



Q: *This circuit looks so familiar!
Haven't we studied it before?*


A: Yes!

It was an **example** where we determined the junction diode circuit transfer function.

It's a little different from ideal

Recall that the **result** was:

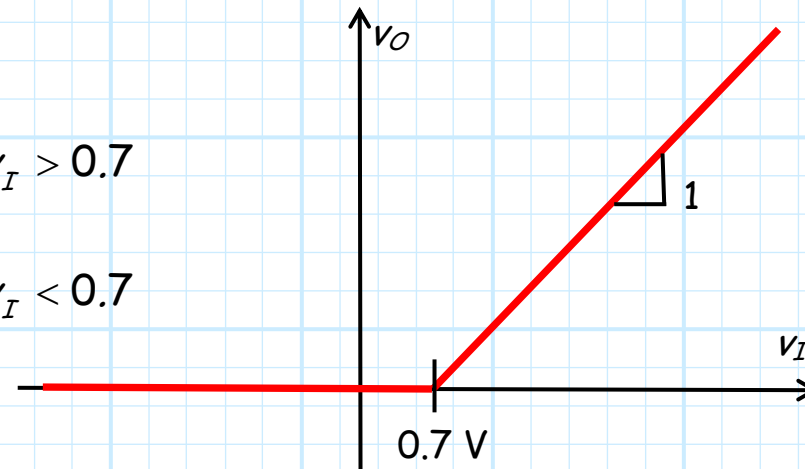
$$v_o = \begin{cases} v_I - 0.7 & \text{for } v_I > 0.7 \\ 0 & \text{for } v_I < 0.7 \end{cases}$$



Note that this result is **slightly different** from that of the **ideal** half-wave rectifier!

The **0.7 V drop** across the junction diode causes a horizontal "shift" of the transfer function from the ideal case.

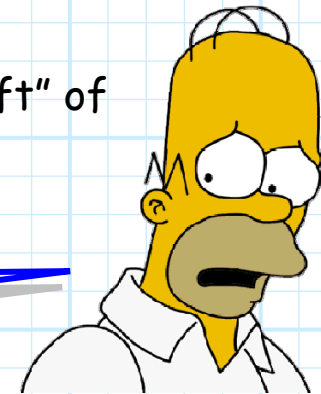Q: *So then this junction diode circuit is worthless?*




A: Hardly! Although the transfer function is **not quite** ideal, it works **well enough** to achieve the goal of signal **rectification**—it takes an input with **no** DC component and creates an output with a **significant** DC component!

Let's determine the output

Note what the transfer function "rule" is now:

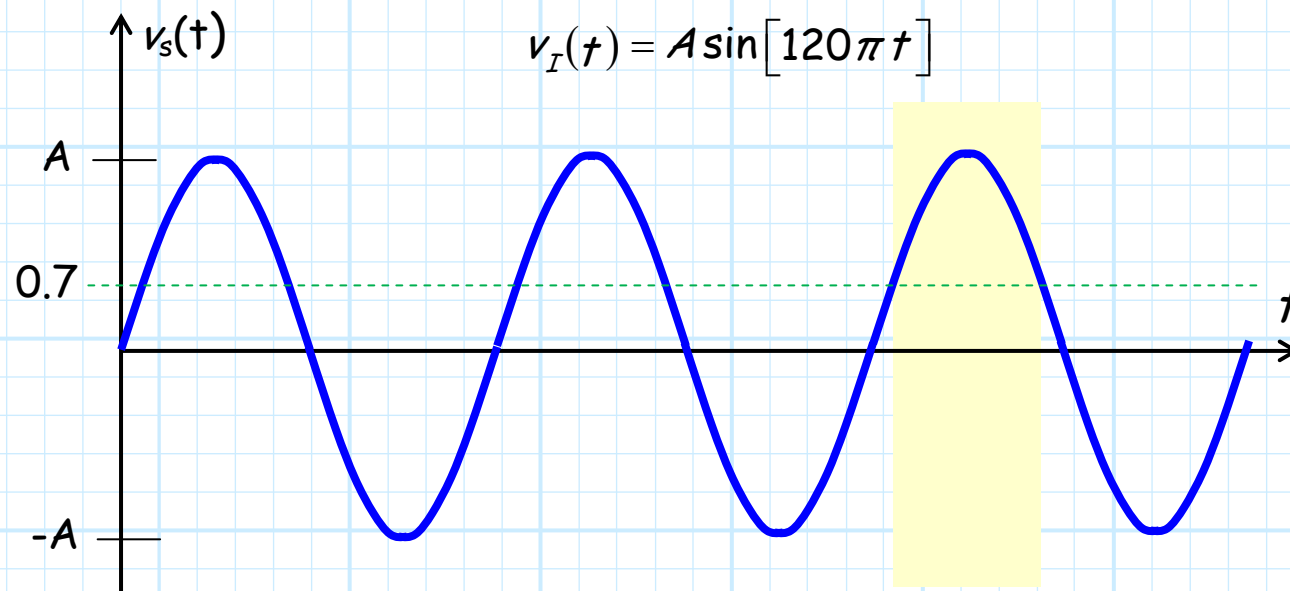
1. When the input is **greater** than 0.7 V, the output voltage is **equal** to the input voltage minus 0.7 V.
2. When the input is **less** than 0.7 V, the output voltage is **zero**.

So, let's consider **again** the case where the **source** voltage is **sinusoidal** (just like the source from a "wall socket"!):



Close to ideal—and still plenty of DC

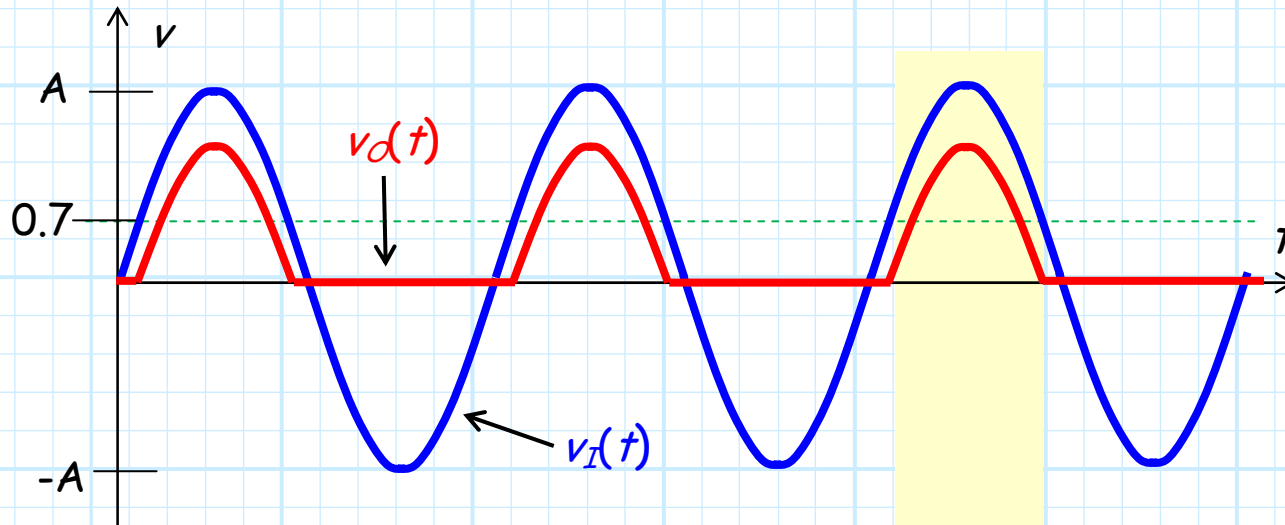The output of our **junction diode** half-wave rectifier would therefore be:



Although the output is **shifted downward** by 0.7 V (note in the plot above this is **exaggerated**, typically $A \gg 0.7 \text{ V}$), it should be apparent that the **output signal** $v_d(t)$, unlike the input signal $v_I(t)$, has a **non-zero** (positive) **DC component**.

Because of the 0.7 V shift, this DC component is **slightly smaller** than the **ideal** case. In fact, we find that if $A \gg 0.7$, this **DC component** is approximately:

$$V_{DC} \approx \frac{A}{\pi} - 0.35 \text{ V}$$

In other words, **just 350 mV less than ideal!**

The ideal full-wave rectifier

Q: Way back on the first page you said that there were *two* types of rectifiers.


I now understand *half-wave* rectification, but what about these so-called *full-wave* rectifiers?



A: Almost forgot!

Let's examine the transfer function of an **ideal full-wave rectifier**:

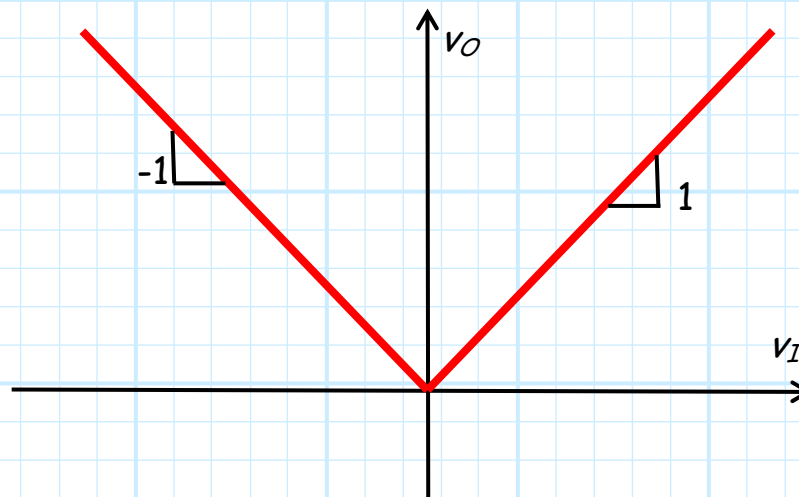
$$v_O = \begin{cases} -v_I & \text{for } v_I < 0 \\ v_I & \text{for } v_I > 0 \end{cases}$$



The DC component is twice as big

If the ideal half-wave rectifier makes **negative** inputs **zero**, the ideal full-wave rectifier makes **negative** inputs—**positive**!

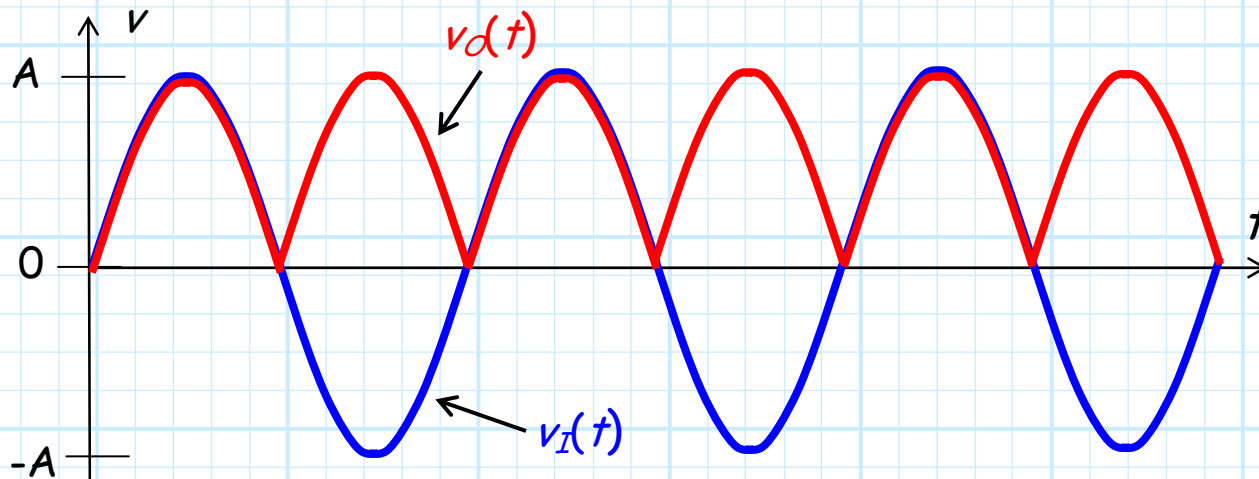
For **example**, if we again consider our **sinusoidal** input, we find that the output will be:



The result is that the output signal will have a DC component **twice** that of the ideal half-wave rectifier!

$$\begin{aligned}
 V_{DC} &= \frac{1}{T} \int_0^T v_O(t) dt \\
 &= \frac{1}{T} \int_0^{T/2} A \sin \omega t dt - \frac{1}{T} \int_{T/2}^T A \sin \omega t dt = \frac{2A}{\pi}
 \end{aligned}$$

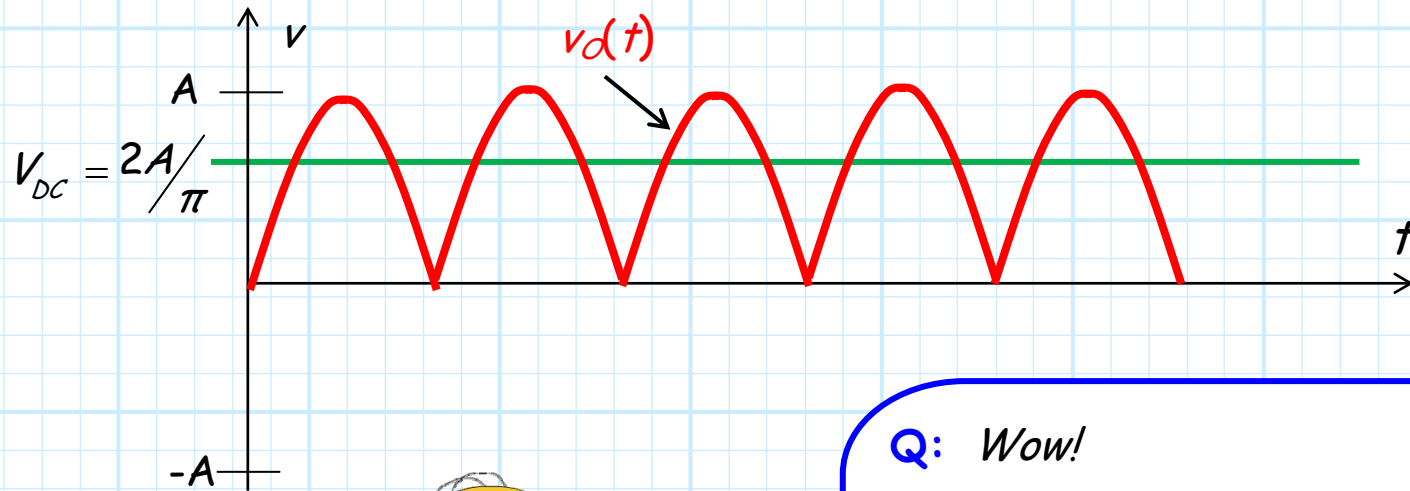We can build a *nearly* ideal full-wave rectifier with *junction* diodes



Q: *Wow!*


*Full-wave rectification appears to be **twice** as good as half-wave.*

*Can we **build** an ideal full-wave rectifier with **junction** diodes?*

A: Although we cannot build an **ideal** full-wave rectifier with **junction** diodes, we can build full-wave rectifiers that are **very close** to ideal with junction diodes!

The Full-Wave Rectifier

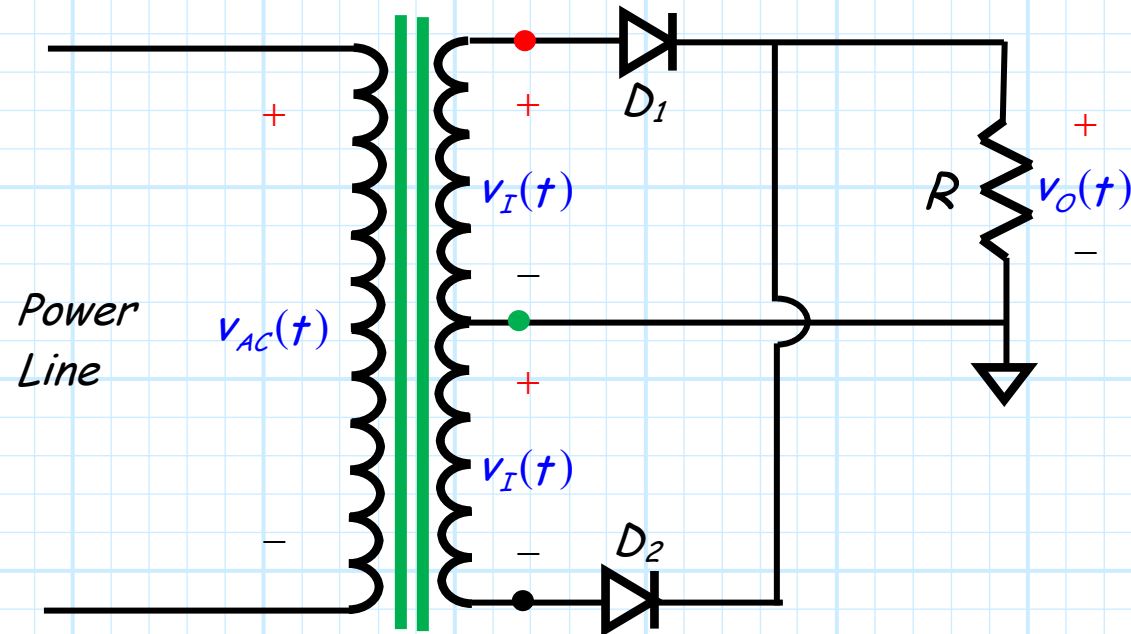Consider the following junction diode circuit:



Note that we are using a **transformer** in this circuit.

The job of this transformer is to **step-down** the large voltage on our power line (120 V_{rms}) to some **smaller** magnitude (typically 20-70 V_{rms}).


This point is very important!

Note the secondary winding has a **center tap** that is **grounded**.

Thus, the secondary voltage is distributed **symmetrically** on either side of this center tap.


For **example**, if $v_I = 10\text{ V}$, the anode of D_1 will be 10 V **above** ground potential.

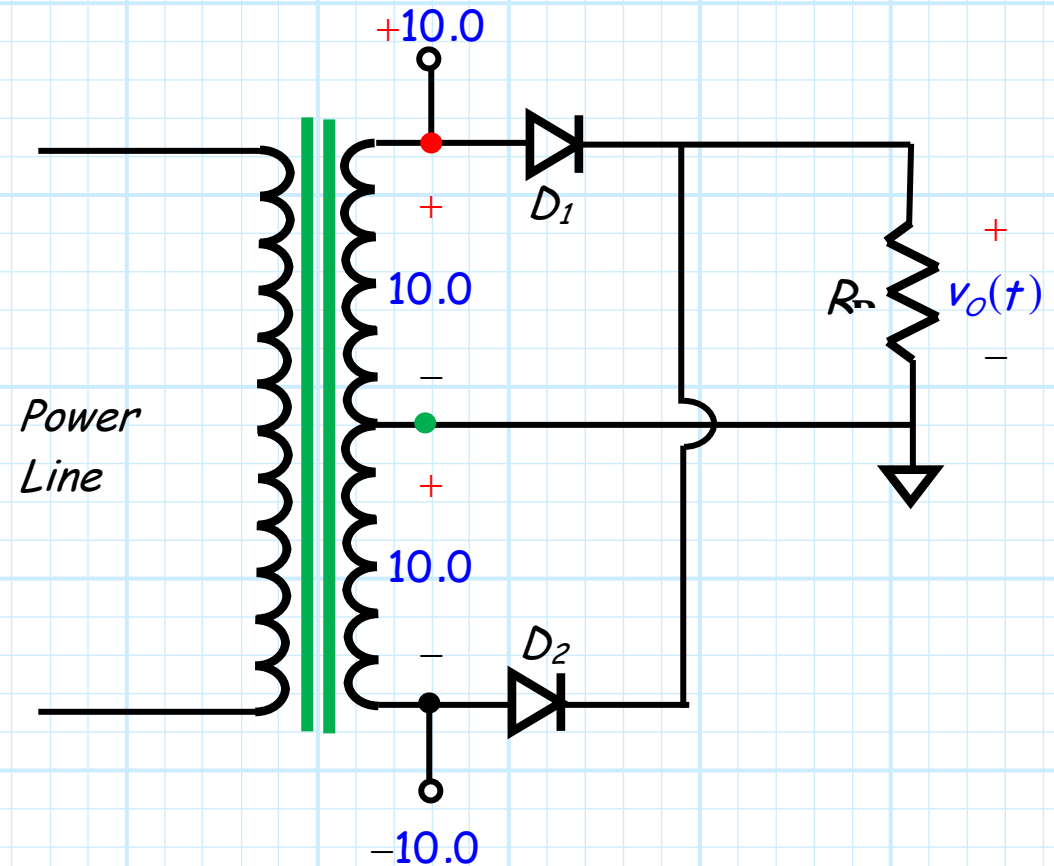While, the anode of D_2 will be 10 V **below** ground potential (i.e., -10 V):



Make this make sense

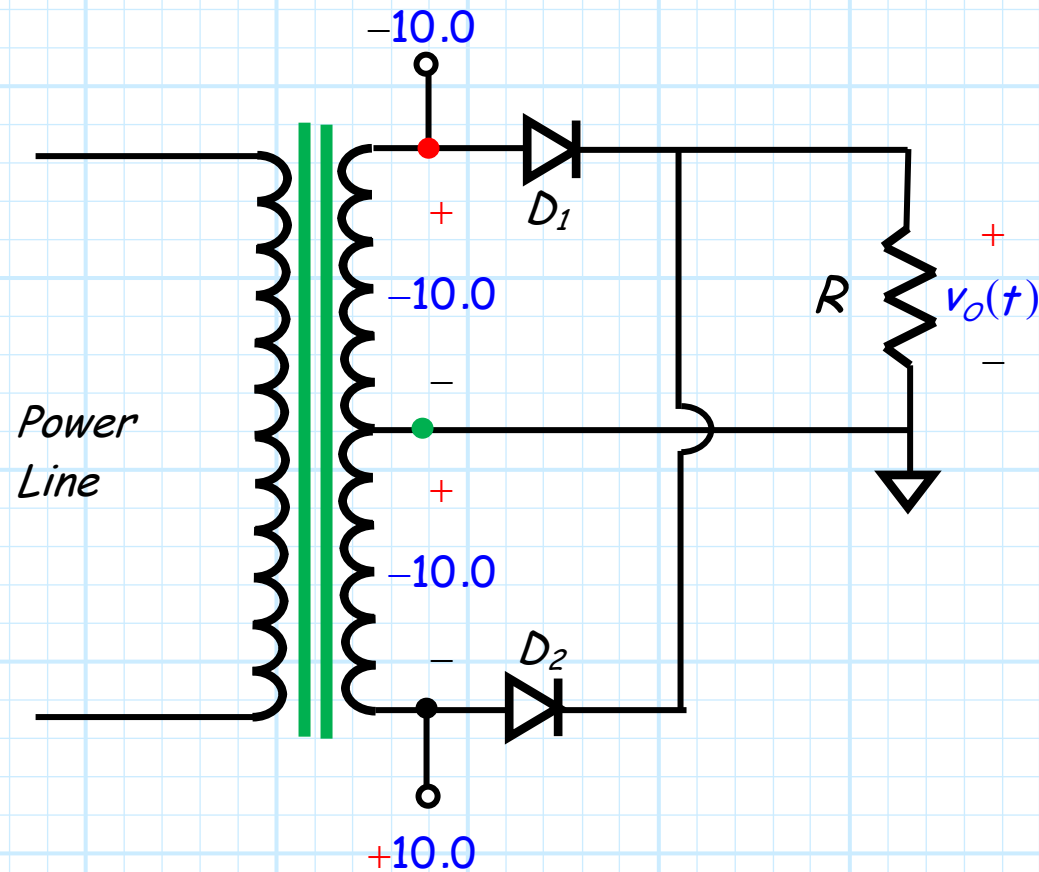Conversely, if $v_I = -10$ V, the anode of D_1 will be 10V **below** ground potential (i.e., -10V), while the anode of D_2 will be 10V **above** ground potential:




Let's redraw the circuit...

The more important question is, what is the value of **output** v_O ?


More specifically, how is v_O related to the value of source v_I —what is the **transfer function** $v_O = f(v_I)$?

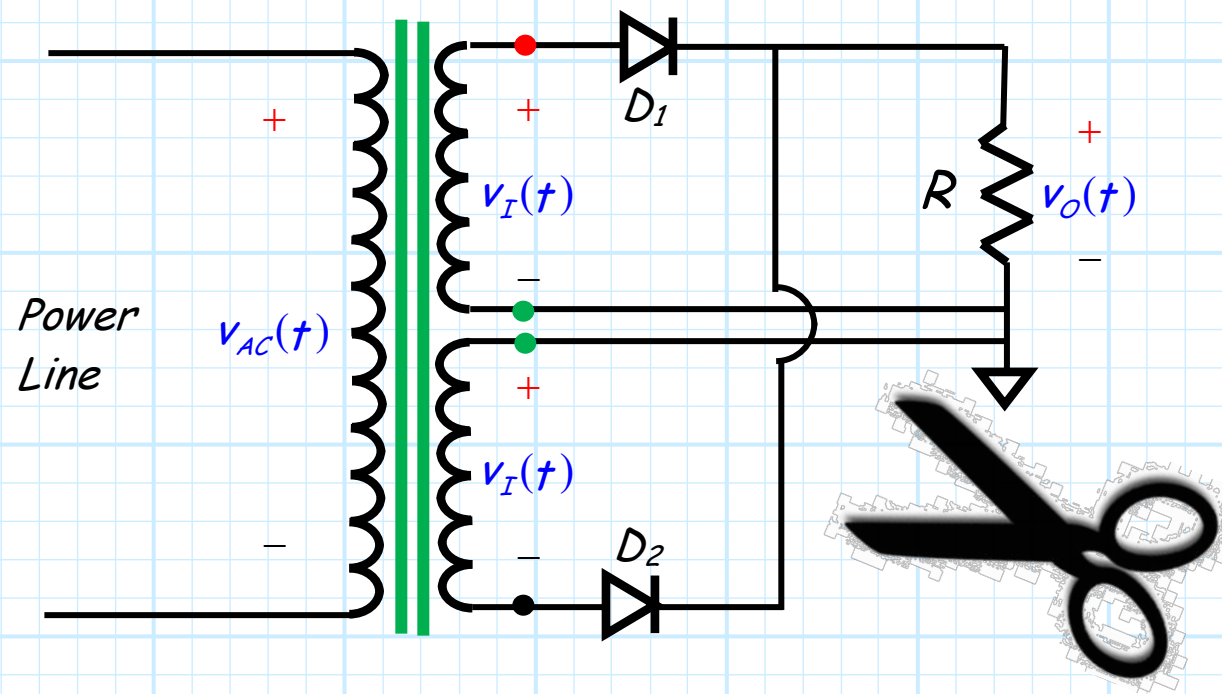To help simplify our analysis, we are going **redraw** this circuit in another way. First, we will **split** the secondary winding into two explicit pieces:



...nothing has changed—it's the same circuit


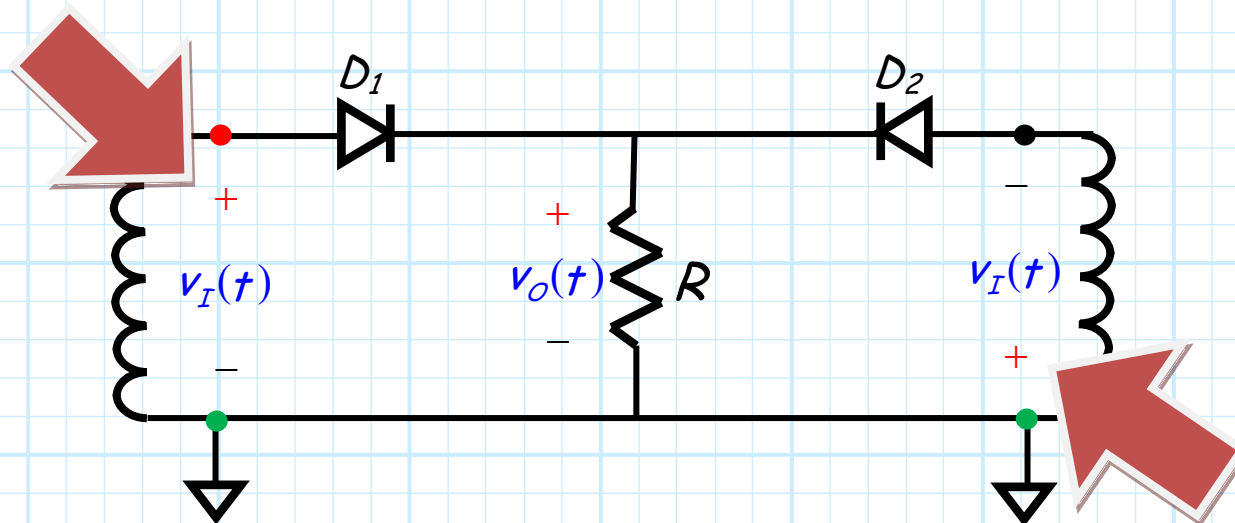
We will now ignore the primary winding of the transformer and redraw the remaining circuit as:



Note that the secondary voltages at either end of this circuit are the **same**, but have **opposite** polarity.


Just like a teeter-totter; one side goes up, the other side goes down

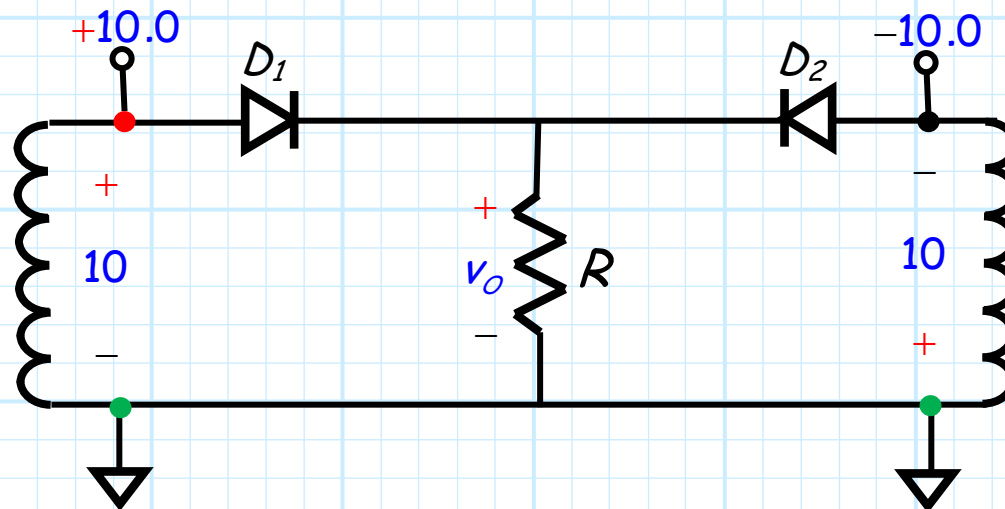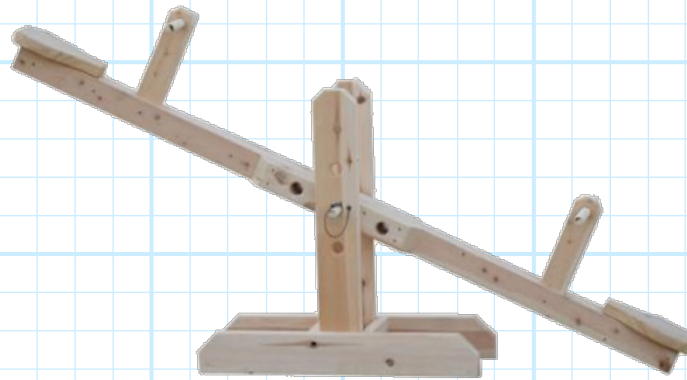As a result, if $v_I = 10$, then the anode of diode D_1 will be 10 V **above** ground, and the anode at diode D_2 will be 10 V **below** ground—just like before!



And vice vesa

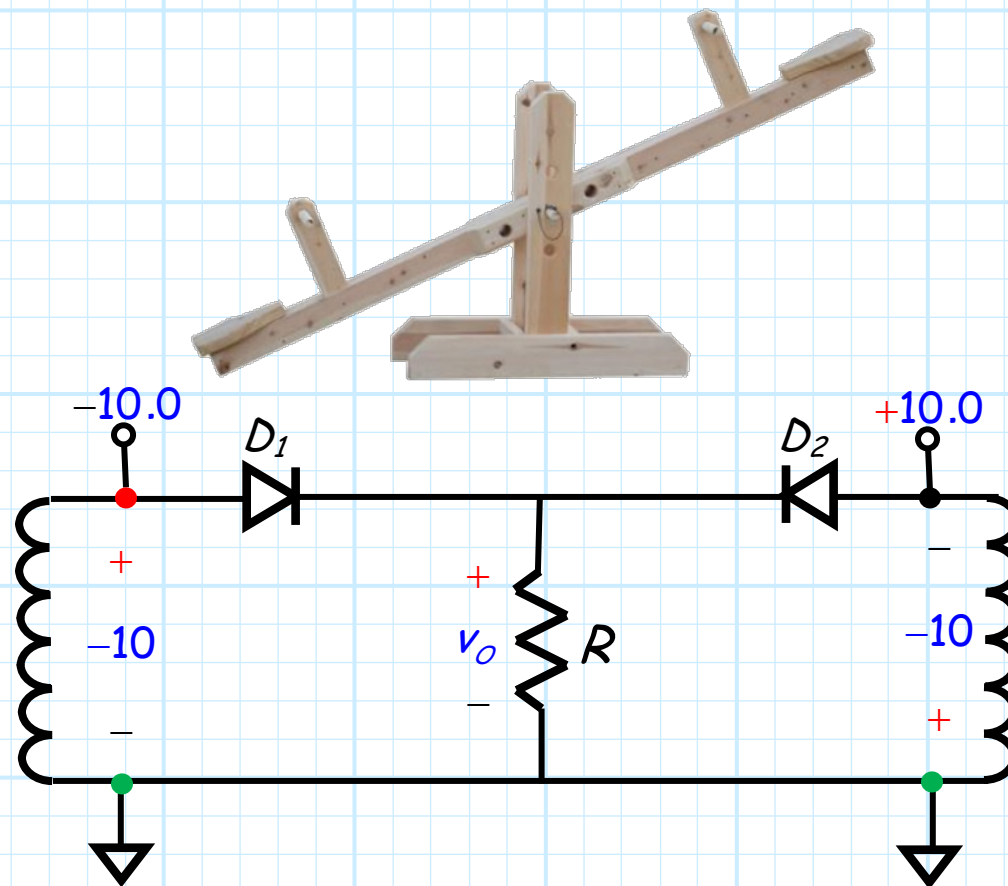And, if $v_I = -10$, then the anode of diode D_1 will be 10V **below** ground, and the anode at diode D_2 will be 10V **above** ground—just like before!




Now, let's attempt to determine the **transfer function** $v_o = f(v_I)$ of this circuit!

Yikes! Three things to find!

First, we will replace the junction diodes with **CVD models**.

Then let's **ASSUME** D_1 is **forward** biased and D_2 is **reverse** biased, thus **ENFORCE** $v_{D1}^i = 0$ and $i_{D2}^i = 0$.

Thus **ANALYZE**:

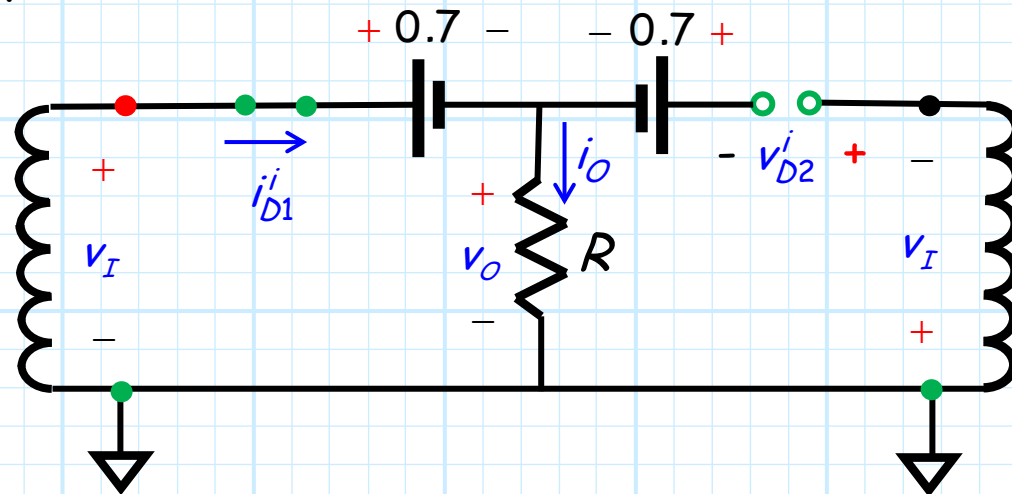


Note that we need to determine **3** things:

- * the **ideal diode current** i_{D1}^i ,
- * the **ideal diode voltage** v_{D2}^i ,
- * and the **output voltage** v_o .

Sprinkle on some KVL pixie dust

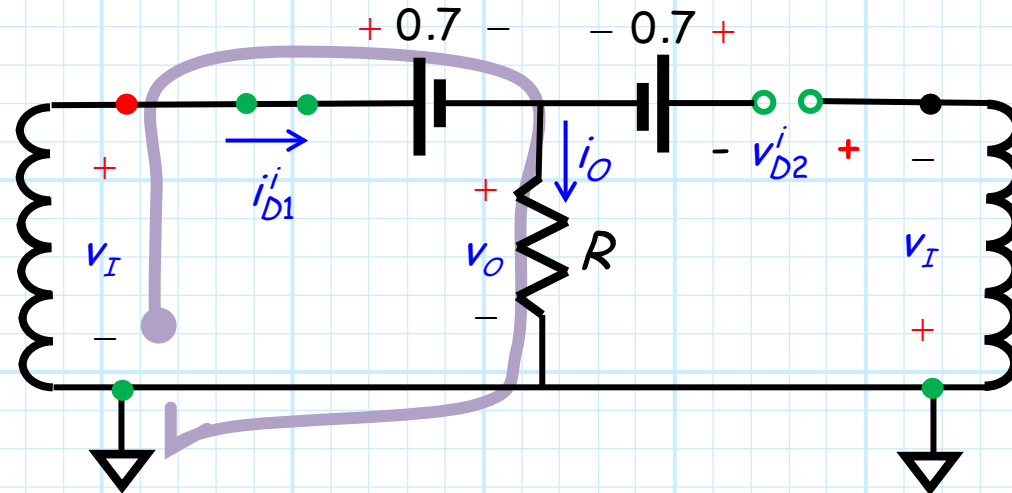However, **instead** of finding numerical values for these 3 quantities, we must express them in terms of **input voltage v_I** !



From **KCL**:

$$i_o = i_{D1}^i + i_{D2}^i = i_{D1}^i + 0 = i_{D1}^i$$


From **KVL**:

$$v_I - 0 - 0.7 - R i_{D1}^i = 0$$

Thus the **ideal diode current** is:

$$i_{D1}^i = \frac{v_I - 0.7}{R}$$

It's getting dusty in here

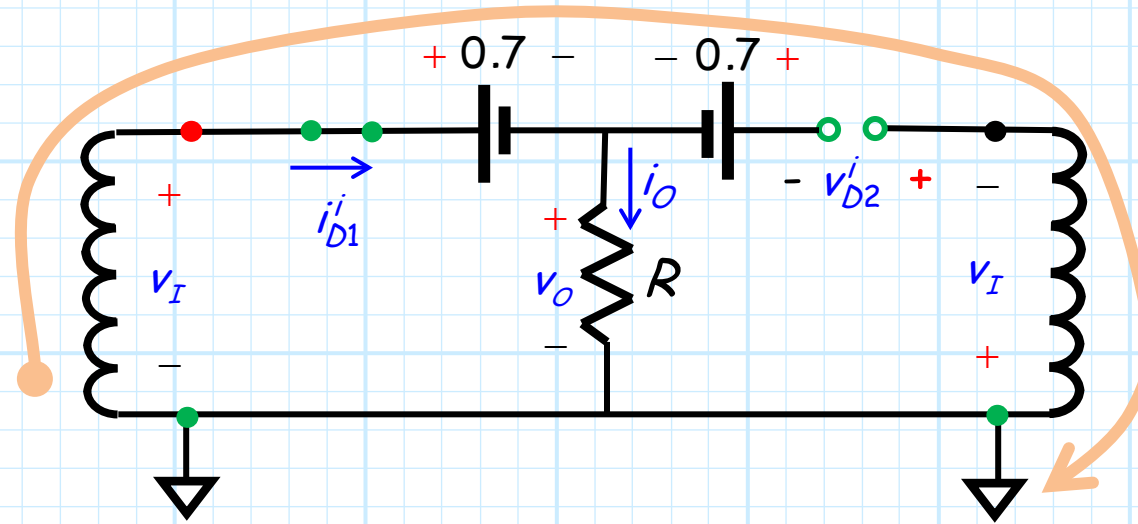

Likewise, from **KVL**:

$$v_I - 0 - 0.7 + 0.7 + v_{D2}' + v_I = 0$$

Thus, the **ideal diode voltage** is:

$$v_{D2}' = -v_I - v_I + 0.7 - 0.7 = -2v_I$$

And finally, from Ohm's Law:

$$v_o = i_{D1}' R = \left(\frac{v_I - 0.7}{R} \right) R = v_I - 0.7$$

Does not mean that v_I is bigger than 0.7

Thus, the output voltage is:

$$v_o = v_I - 0.7$$

Now, we must determine **when** both $i_{D1}^i > 0$ and $v_{D2}^i < 0$.

When **both** these conditions are true, the output voltage will be $v_o = v_I - 0.7$.

When one **or** both conditions $i_{D1}^i > 0$ and $v_{D2}^i < 0$ are **false**, then our assumptions are **invalid**, and $v_o \neq v_I - 0.7$.

Using the results we just determined, we know that $i_{D1}^i > 0$ **when**:

$$\frac{v_I - 0.7}{R} > 0$$

Solving for v_I :

$$\frac{v_I - 0.7}{R} > 0$$

$$v_I - 0.7 > 0$$

$$v_I > 0.7 \text{ V}$$

Make this make sense

Likewise, we find that $v_{D2}' < 0$ when:

$$-2v_I < 0$$

Solving for v_I :

$$-2v_I < 0$$

$$2v_I > 0$$

$$v_I > 0$$



Thus, our assumptions are correct **when** $v_I > 0.0$ **AND** $v_I > 0.7$.

→ **THINK** about this. This is the **same** thing as saying our assumptions are valid when $v_I > 0.7$!

Thus, we have found that the following statement is true about **this** (but only this!) circuit:

$$\rightarrow v_O = v_I - 0.7 \text{ V} \quad \text{when} \quad v_I > 0.7 \text{ V}$$

We're not done yet!

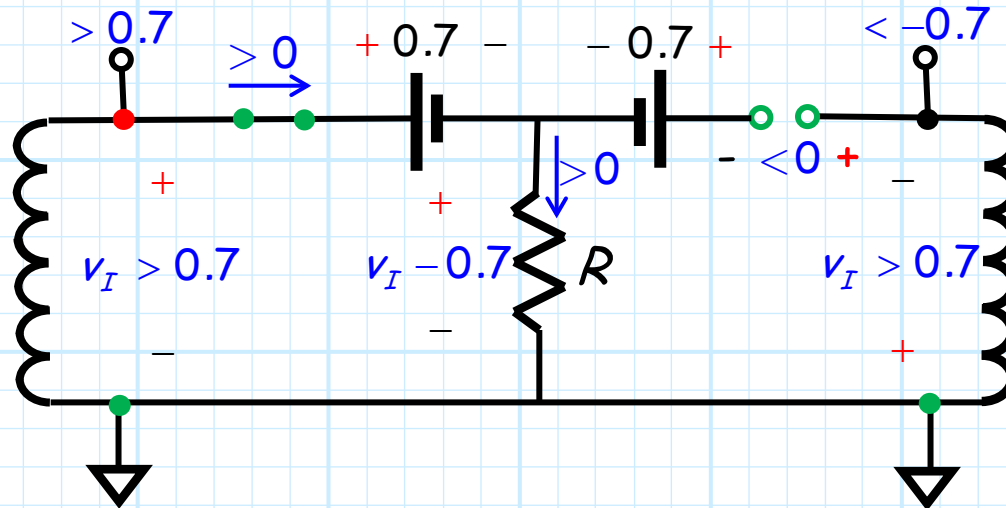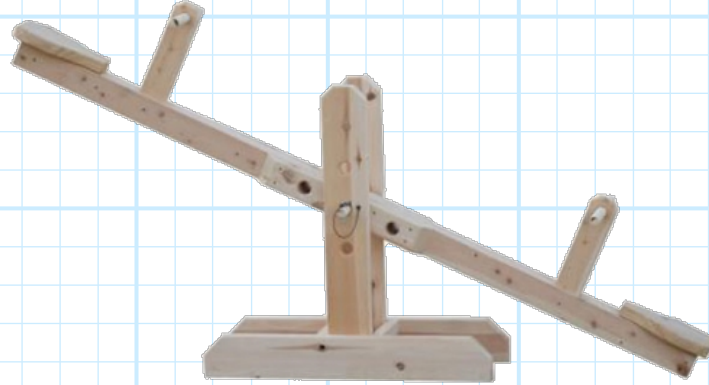

$$\rightarrow v_O = v_I - 0.7 \text{ V} \quad \text{when } v_I > 0.7 \text{ V}$$

Note that this statement does **not** constitute a **function** (what about $v_I < 0.7$?), so we must **continue** with our analysis!

A good engineer is fretful, paranoid and fatalistic

Q: *Wait! I'm concerned about something.*

We found that the voltage across the second ideal diode is:

$$v_{D_2}^i = -2v_I$$



From the CVD model, that means the voltage across junction diode D_2 is approximately:

$$v_{D_2} = 0.7 + v_{D_2}^i = 0.7 - 2v_I$$

Since we know this is true only when:

$$v_I > 0.7 \text{ V}$$


the diode voltage $v_{D_2} = 0.7 - 2v_I$ must be negative.

Avoid breakdown!

Moreover, this negative voltage is proportional to twice the input voltage!

Thus, if the input voltage is large, the voltage across this junction diode might be very, very negative.

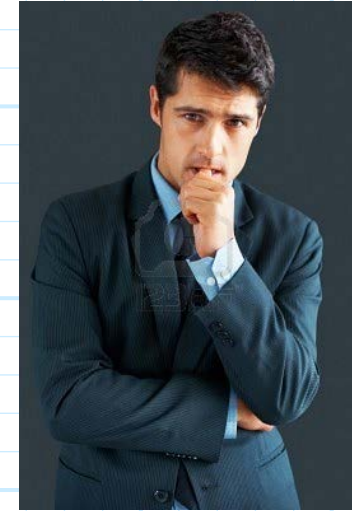Shouldn't I be concerned about this junction diode going into breakdown?



A: You sure should!

If the junction diode goes into **breakdown**, the transfer function will **not** be what we expected.

You'd better use junction diodes with sufficiently large **Zener breakdown voltages!**

Peak Inverse Voltage: more on this later

Q: *But how large is sufficiently large?*

A: If we know precisely the **input** voltage function $v_I(t)$, we can find the **“worst case” scenario**—the **most** negative voltage value that occurs across this junction diode.


We call the magnitude of this value the **Peak Inverse Voltage** (more on this later)—the V_{ZK} of our Zener diodes had better be larger than this value!



Back to the analysis; I'll skip some stuff

OK, back to the analysis, say we **now** ASSUME that D_1 is **reverse** biased and D_2 is **forward** biased, so we ENFORCE $i_{D1}^i = 0$ and $v_{D2}^i = 0$.

Thus, we ANALYZE **this** circuit:

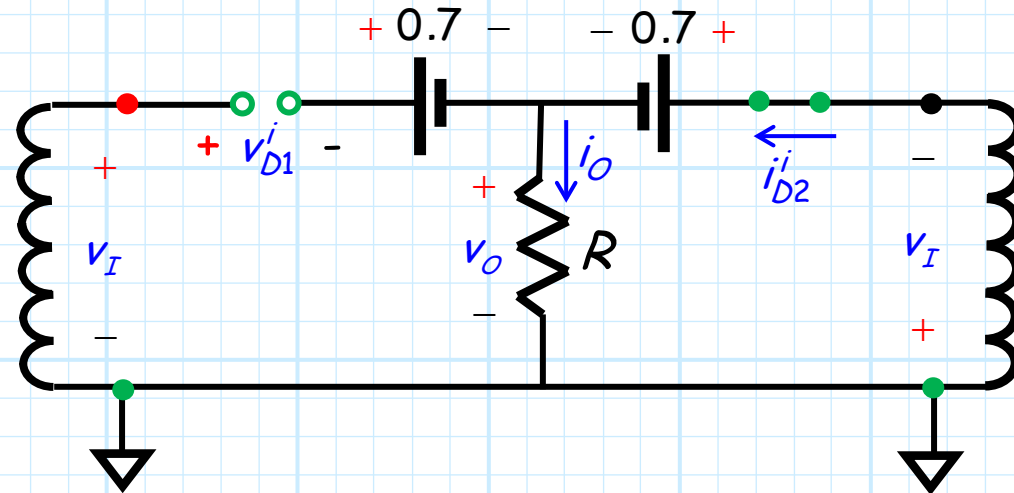


Using the **same procedure** as before, we find that $v_o = -v_I - 0.7$, and both our assumptions are true **when** $v_I < -0.7$ V.

And we're still not finished!

In other "words":
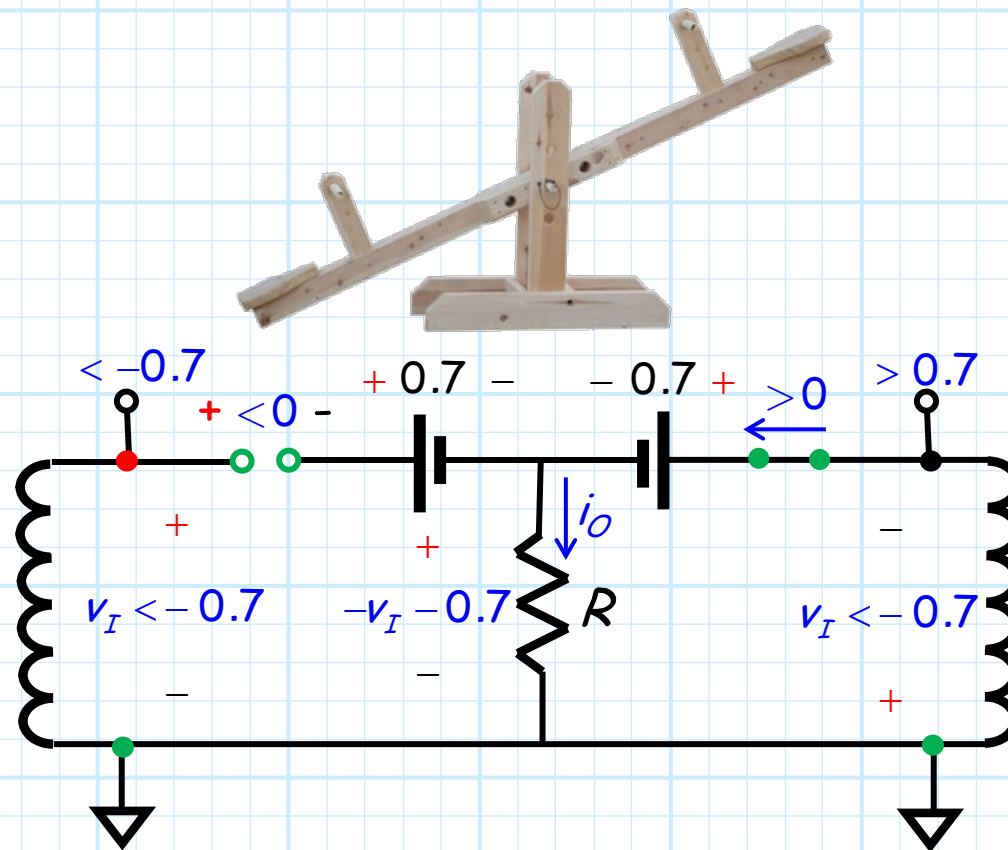
$$\rightarrow v_o = -v_I - 0.7 \text{ V} \quad \text{when} \quad v_I < -0.7 \text{ V}$$




Note we are still **not** done!

We do not have a complete transfer function (what happens when $-0.7 \text{ V} < v_I < 0.7 \text{ V}$?).

Now we're done!

Finally then, we ASSUME that both ideal diodes are **reverse** biased, so we ENFORCE $i_{D1}^i = 0$ and $i_{D2}^i = 0$.

Thus ANALYZE:


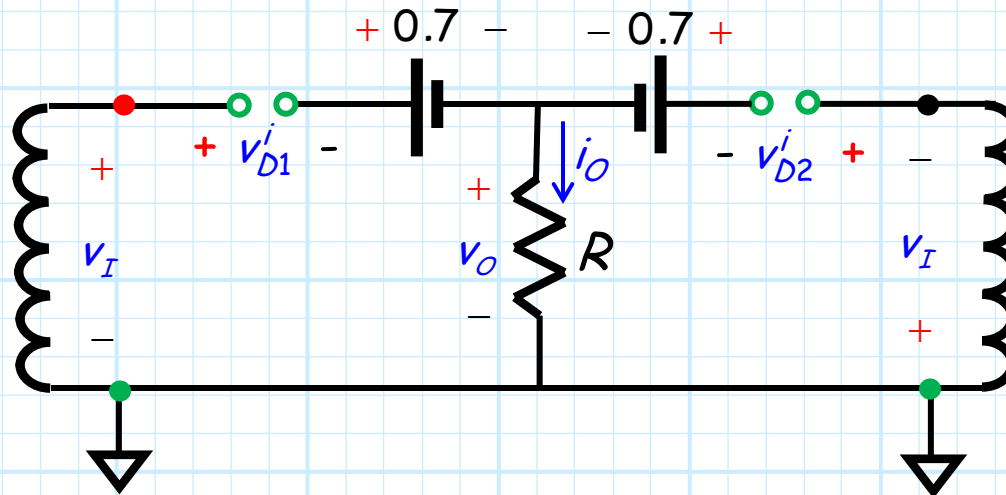


Following the **same procedures** as before, we find that $v_I = 0$, and both assumptions are true **when** $-0.7 < v_I < 0.7$.

In other words:

$$\rightarrow v_I = 0 \quad \text{when} \quad -0.7 < v_I < 0.7$$


A simple analysis

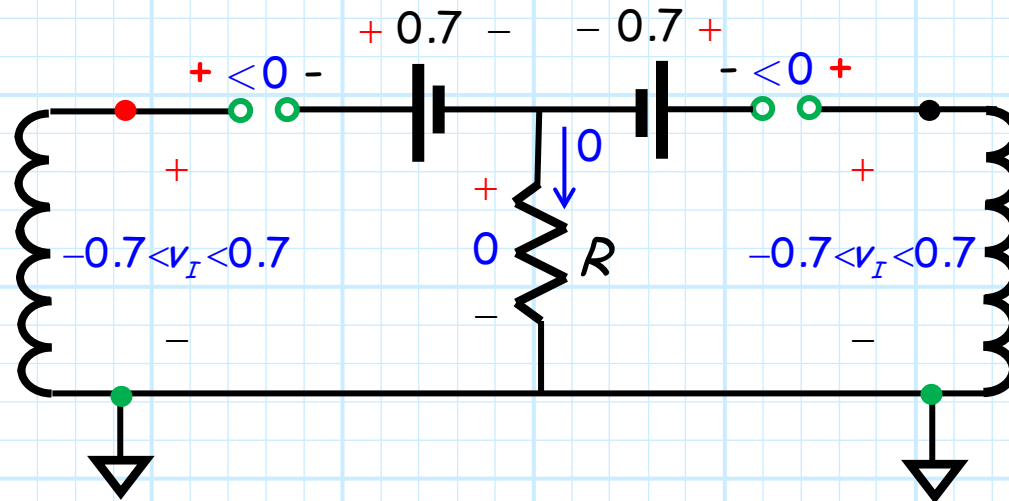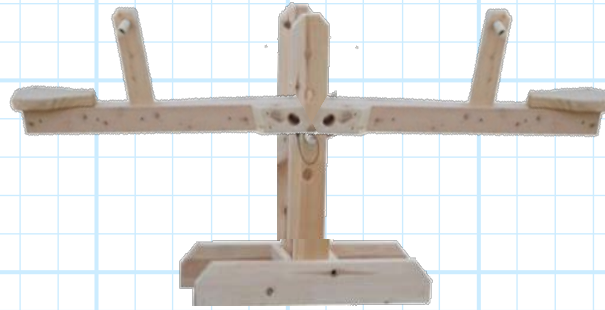


Now we have a function!

Smells like an ideal full-wave rectifier!

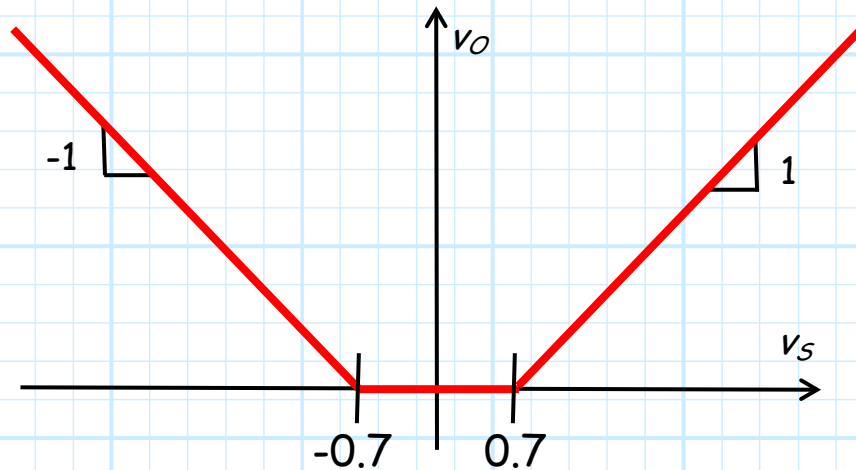
The transfer function of this circuit is:


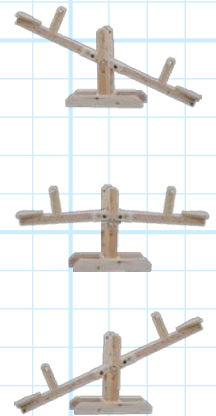
$$v_o = \begin{cases} v_I - 0.7V & \text{for } v_I > 0.7V \\ 0V & \text{for } -0.7 > v_I > 0.7V \\ -v_I - 0.7V & \text{for } v_I < -0.7V \end{cases}$$



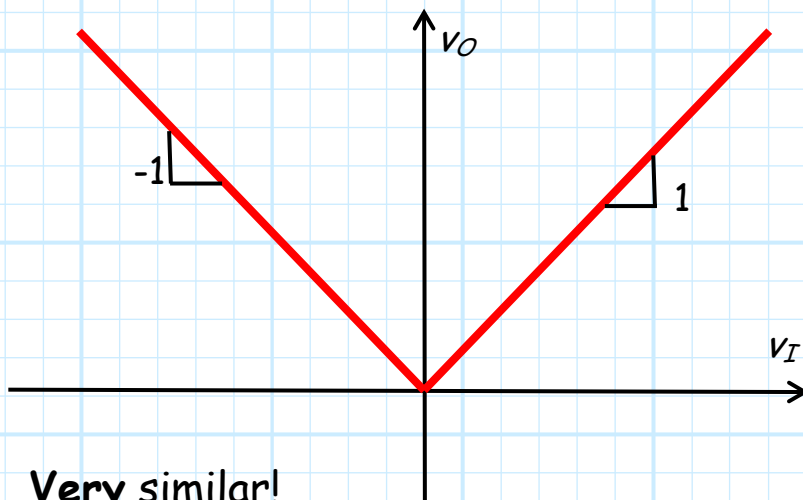Note how this **compares** to the transfer function of the **ideal** full-wave rectifier:




$$v_o = \begin{cases} -v_I & \text{for } v_I < 0 \\ v_I & \text{for } v_I > 0 \end{cases}$$


Very similar!

See?

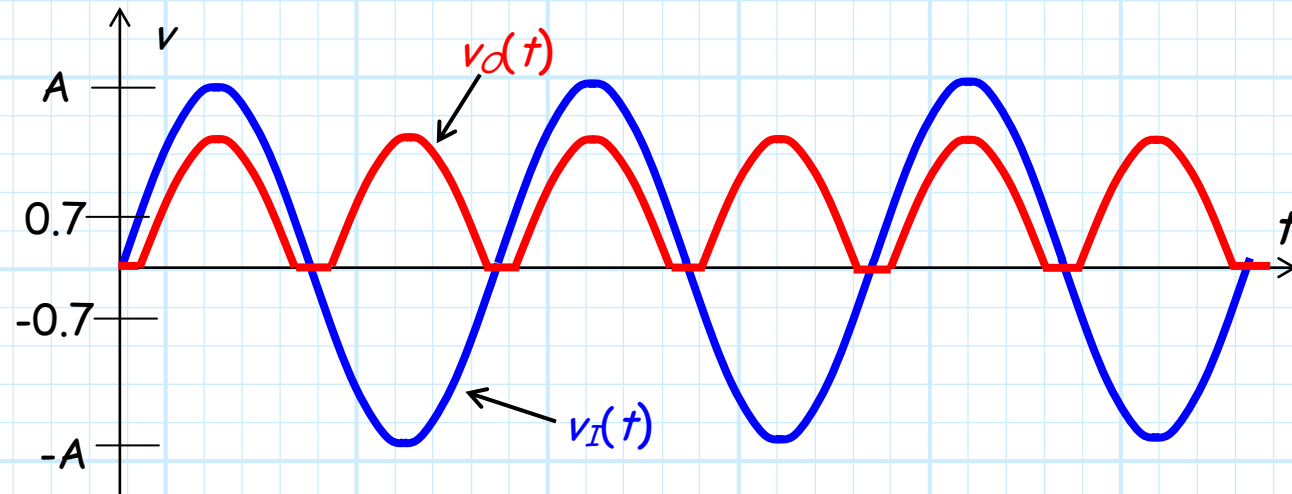Likewise, compare the output of this junction diode full-wave rectifier:



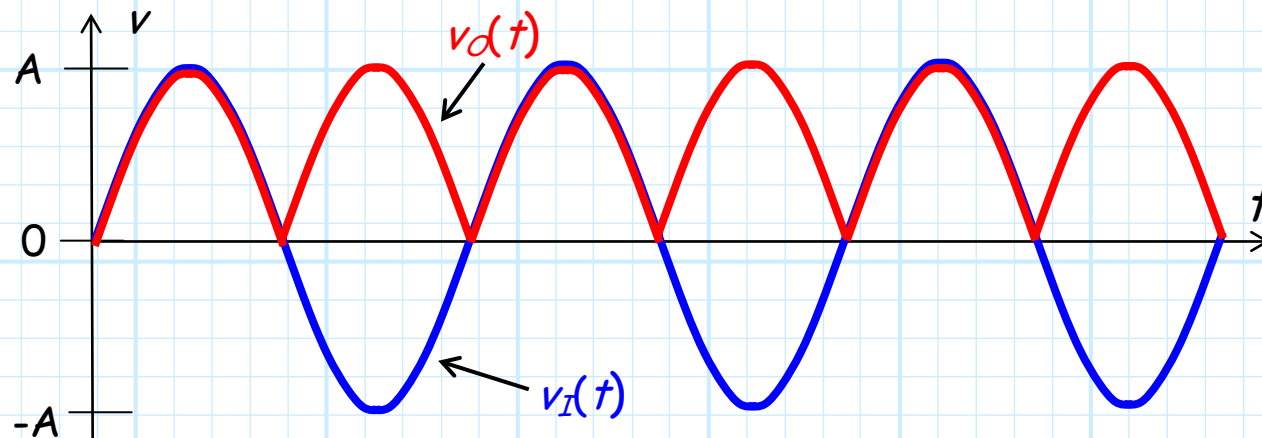to the output of an **ideal** full-wave rectifier:




Again we see that the junction diode full-wave rectifier output is **very close** to ideal.

The DC component of the output is *nearly* ideal!

In fact, if $A \gg 0.7 \text{ V}$, the **DC component** of this junction diode full wave rectifier is approximately:


$$V_{DC} \approx \frac{2A}{\pi} - 0.7 \text{ V}$$

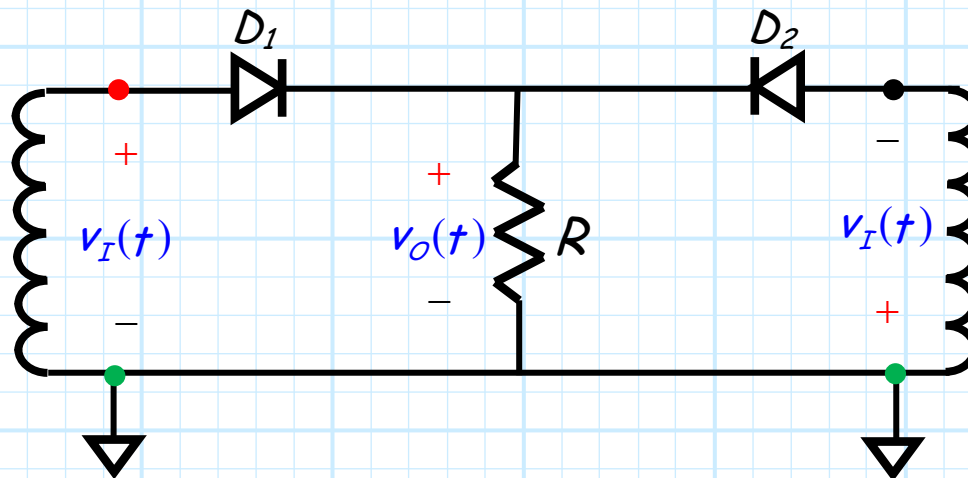Just 700 mV less than the *ideal* full-wave rectifier DC component!



The Bridge Rectifier

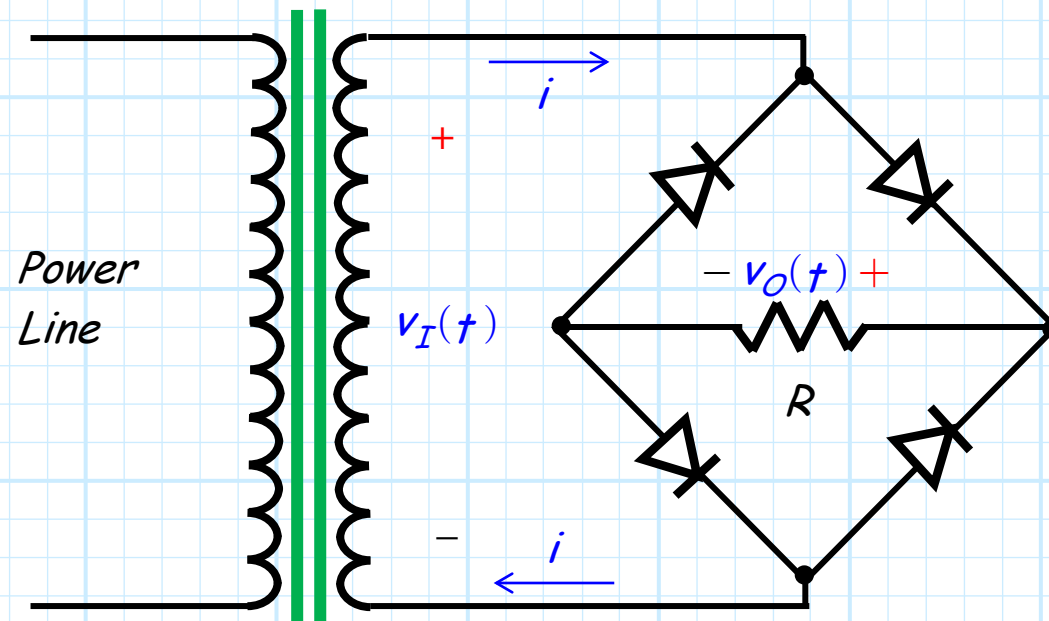Now consider this **junction diode** rectifier circuit:




We call this circuit the **bridge rectifier**.

→ Let's **analyze** it and see what it does!

16 possible assumptions!

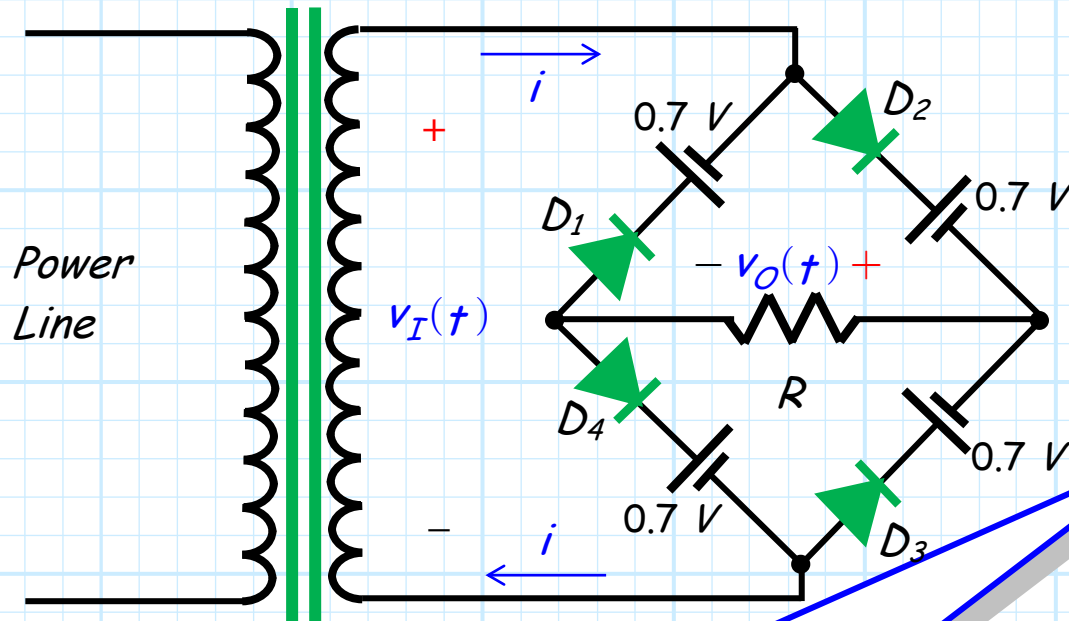First, we **replace** the junction diodes with the **CVD model**:




Q: *Four gul-durn ideal diodes! That means 16 sets of dad-gum assumptions!*

A: True! However, there are only **three** of these sets of assumptions are actually **possible!**

But only 3 sets are possible

Consider the **current** i flowing through the rectifier.

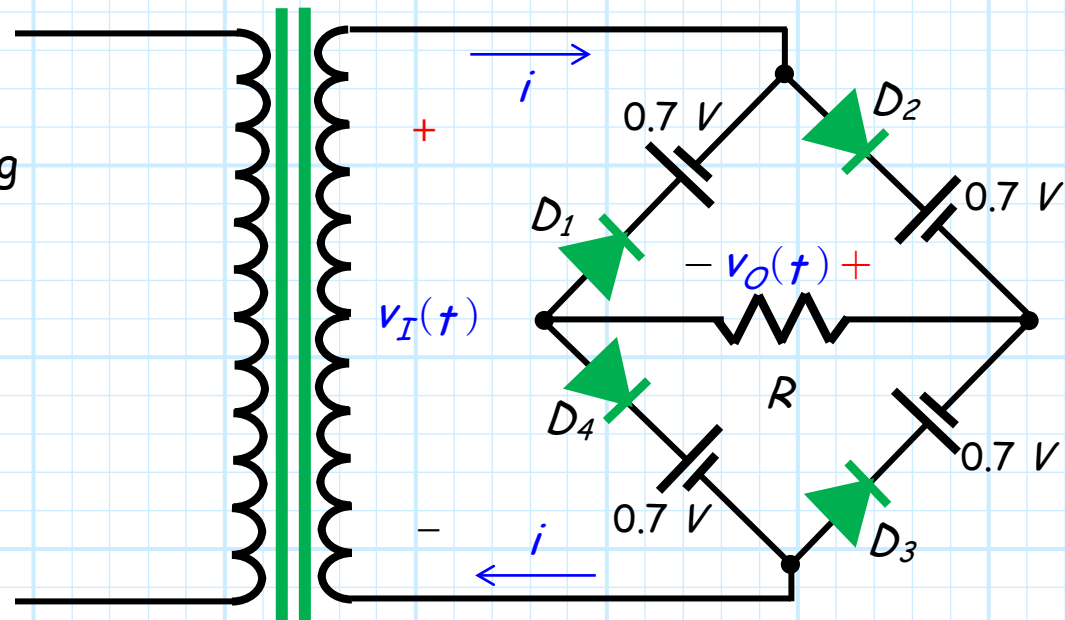This current of course can be positive, negative, or zero.



It turns out that there is only **one** set of diode assumptions that would result in positive current i , **one** set of diode assumptions that would lead to negative current i , and **one** set that would lead to zero current i .

Q: *But what about the remaining 13 sets of dog gone diode assumptions?*

A: **Regardless** of the value of source v_S , the remaining 13 sets of diode assumptions simply **cannot occur** for this particular circuit design!




$$\underline{i > 0}$$

Let's look at the **three** possible sets of assumptions, first starting with $i > 0$.

The rectifier current i can be **positive** only if these assumptions are true:

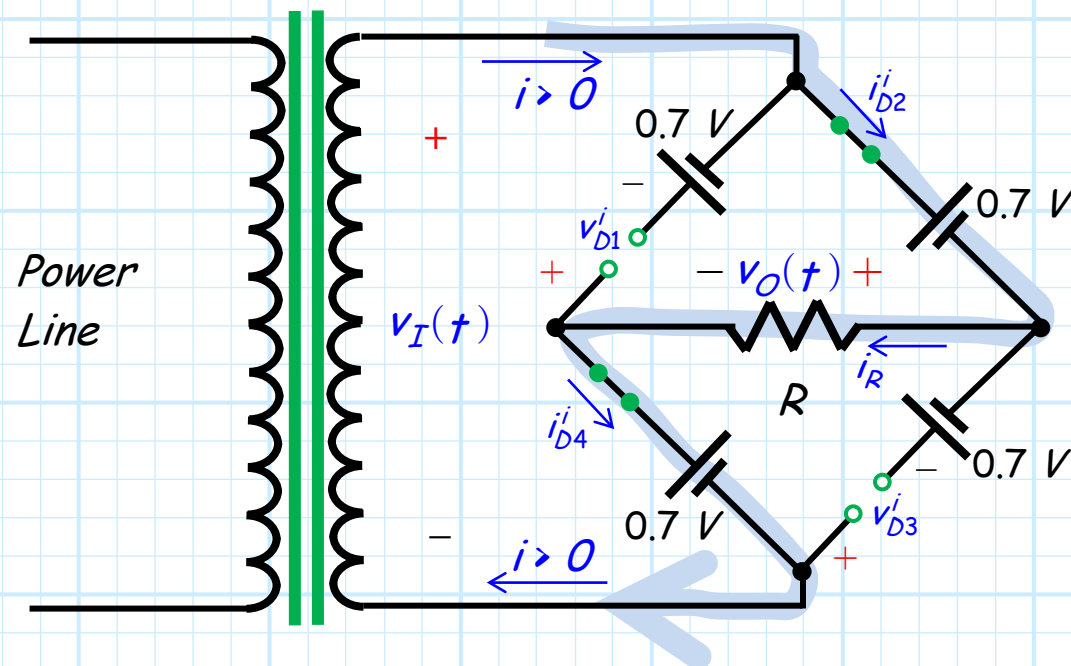- * Ideal diodes D_1 and D_3 are **reverse** biased.
- * Ideal diodes D_2 and D_4 are **forward** biased.



Breakdown: it appears to be less likely

Analyzing this circuit, we find from KVL that the **output voltage** is:

$$v_O = v_I - 1.4 \text{ V}$$

and the forward biased **ideal diode currents** are from KCL and Ohm's Law:

$$i = i_{D2}^i = i_{D4}^i = i_R = \frac{v_I - 1.4}{R}$$

and, finally the reverse biased **ideal diode voltages** are from KVL:

$$v_D^i = -v_I$$

Q: *Hey! I notice that the reverse bias voltage for this bridge rectifier is much less negative than that of the full-wave rectifier (i.e., $v_D^i = -2v_I$ for the full-wave rectifier).*

Does that mean breakdown is less likely?

A: Absolutely! This is an **important feature** of the bridge rectifier (more on this later!).

Way to be paranoid!

Now, back to the analysis...

Thus, $i'_D > 0$ when:

$$\frac{v_I - 1.4}{R} > 0$$

$$v_I - 1.4 > 0$$

$$v_I > 1.4 \text{ V}$$

and $v'_D < 0$ when:

$$-v_I < 0$$

$$v_I > 0$$

Therefore, we find that for this circuit that:

$$v_O = v_I - 1.4 \text{ V} \quad \text{when} \quad v_I > 0 \quad \text{and} \quad v_I > 1.4 \text{ V}$$


Applying some logic, we see that this simply means

$$\rightarrow v_O = v_I - 1.4 \text{ V} \quad \text{when} \quad v_I > 1.4 \text{ V}$$

$$\underline{i < 0}$$

The rectifier current i can be **negative** only if these assumptions are true:

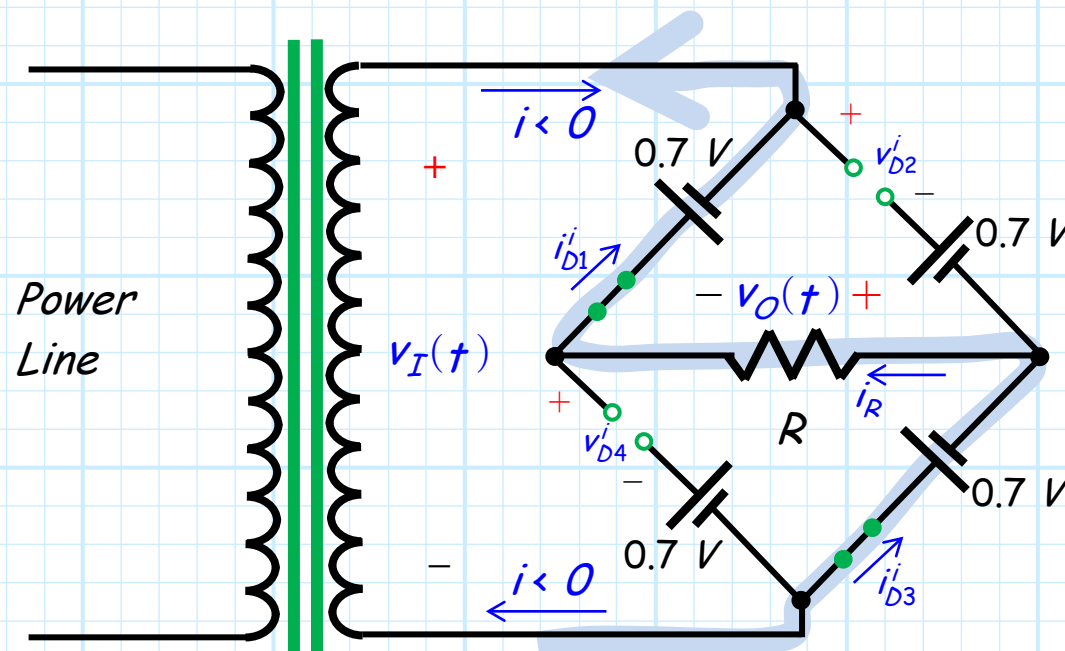- * Ideal diodes D_1 and D_3 are **forward** biased.
- * Ideal diodes D_2 and D_4 are **reverse** biased.



Verify this yourself

Analyzing this circuit, we find from KVL that the **output voltage** is:


$$v_O = -v_I - 1.4 \text{ V}$$

while the forward biased **ideal diode currents** are both determined from KCL and Ohm's Law:

$$-i = i_{D1}^i = i_{D3}^i = i_R = \frac{-v_S - 1.4}{R}$$

and the reverse biased **ideal diode voltages** are found from KVL to be:
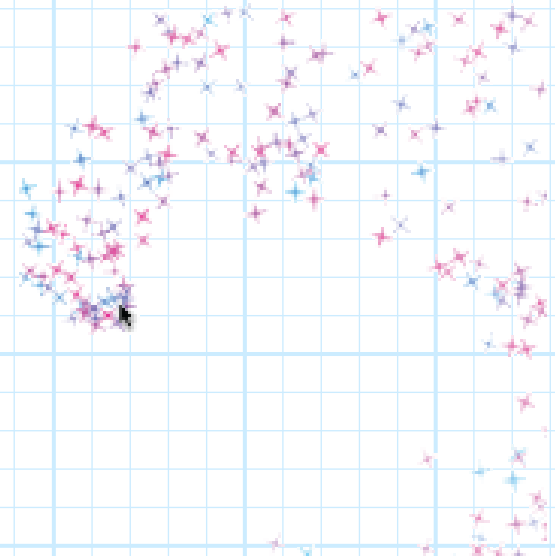
$$v_{D1}^r = v_{D3}^r = v_I \quad (\text{remember this for later!})$$



Applying logic: it will get you far in life

Thus, $i_D^i > 0$ when:

$$\begin{aligned} \frac{-v_I - 1.4}{R} &> 0 \\ -v_I - 1.4 &> 0 \\ -v_I &> 1.4 \text{ V} \\ v_I &< -1.4 \text{ V} \end{aligned}$$

and, $v_D^i < 0$ when:

$$v_I < 0$$

Therefore, we find that for this circuit that:

$$v_O = v_I - 1.4 \text{ V} \quad \text{when } v_I < 0 \quad \text{and} \quad v_I < -1.4 \text{ V}$$


Applying some **logic**, we see that this simply means:

$$\rightarrow v_O = -v_I - 1.4 \text{ V} \quad \text{when } v_I < -1.4 \text{ V}$$

$$\underline{i = 0}$$

The rectifier current i can be **zero** only if these assumptions are true:

All ideal diodes are reverse biased!

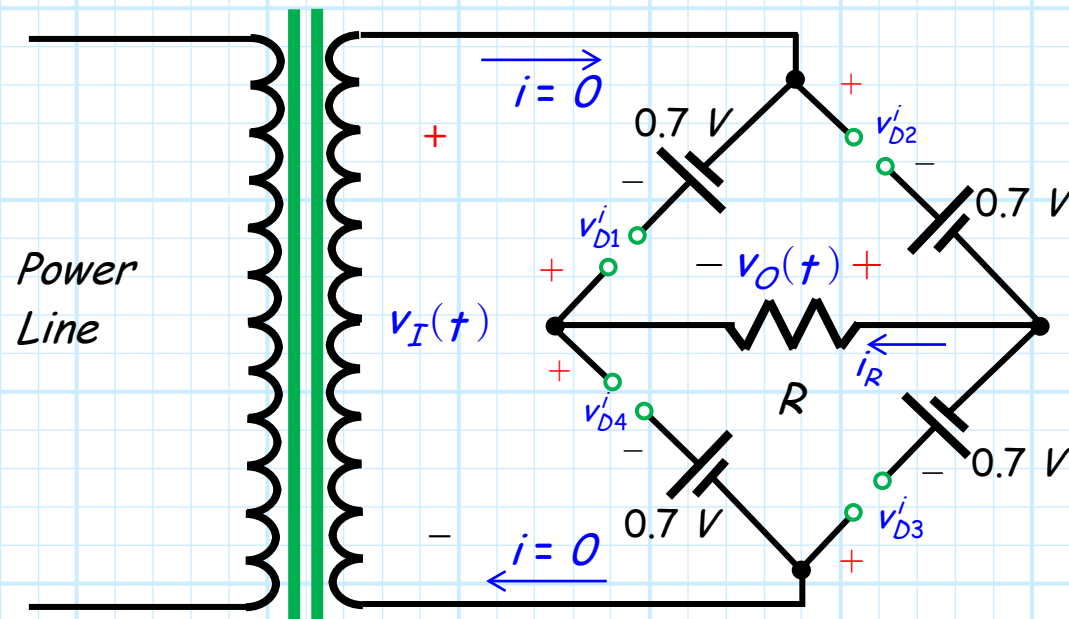

Verify this yourself

Analyzing this circuit, we find that the **output voltage** is:


$$v_O = R i_R = R i = 0$$

while the **ideal diode voltages** of D_2 and D_4 are each:

$$v_{D2}^i = \frac{v_I - 1.4}{2} = v_{D4}^i$$

and the **ideal diode voltages** of D_1 and D_3 are each:
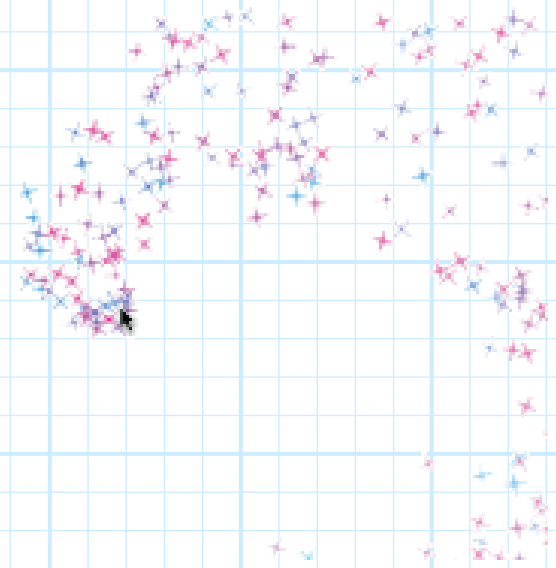
$$v_{D1}^i = \frac{-v_I - 1.4}{2} = v_{D3}^i$$



This logic is a bit simpler

Thus, $v_{D2}^i < 0$ when:

$$\frac{v_I - 1.4}{2} < 0$$

$$v_I - 1.4 < 0$$

$$v_I < 1.4$$

and, $v_{D1}^i < 0$ when:

$$\frac{-v_I - 1.4}{2} < 0$$

$$-v_I - 1.4 < 0$$

$$-v_I < 1.4$$

$$v_I > -1.4$$

Therefore, we also find for this circuit that:

$$v_o = 0 \quad \text{when both} \quad v_s < 1.4V \quad \text{and} \quad v_s > -1.4V$$

Or, in other "words":

$$\rightarrow v_o = 0 \quad \text{when} \quad -1.4V < v_I < 1.4V$$

It's true: class of 1983!




Q: You know, that dang *Mizzou* grad said we only needed to consider these *three sets of diode assumptions*, yet I am *still concerned about the other 13*.

How can we be *sure* that we have analyzed every *possible set of valid diode assumptions*?

A: We know that we have considered **every** possible case, because when we combine the three results we find that we have a piece-wise linear **function!**

Smells like a full-wave rectifier!

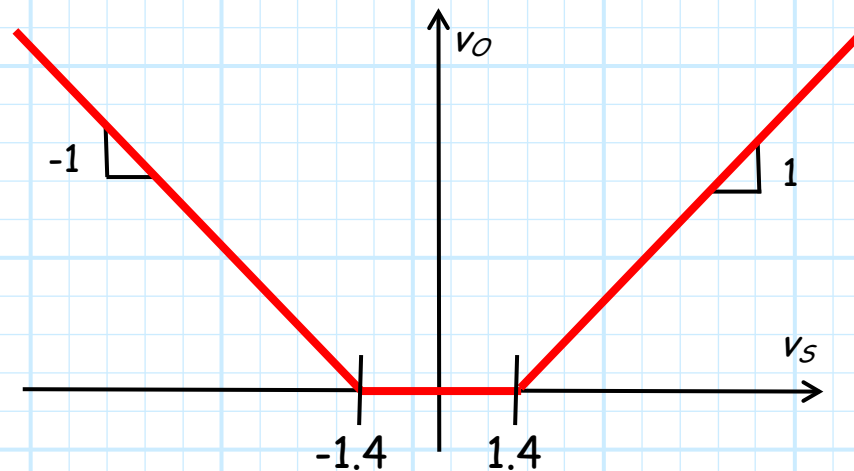
$$v_o = \begin{cases} -v_s - 1.4V & \text{if } v_s < -1.4V \\ 0 & \text{if } -1.4 < v_s < 1.4V \\ v_s - 1.4V & \text{if } v_s > 1.4V \end{cases}$$



Note that the **bridge** rectifier is a **full-wave** rectifier!

Close to the ideal result

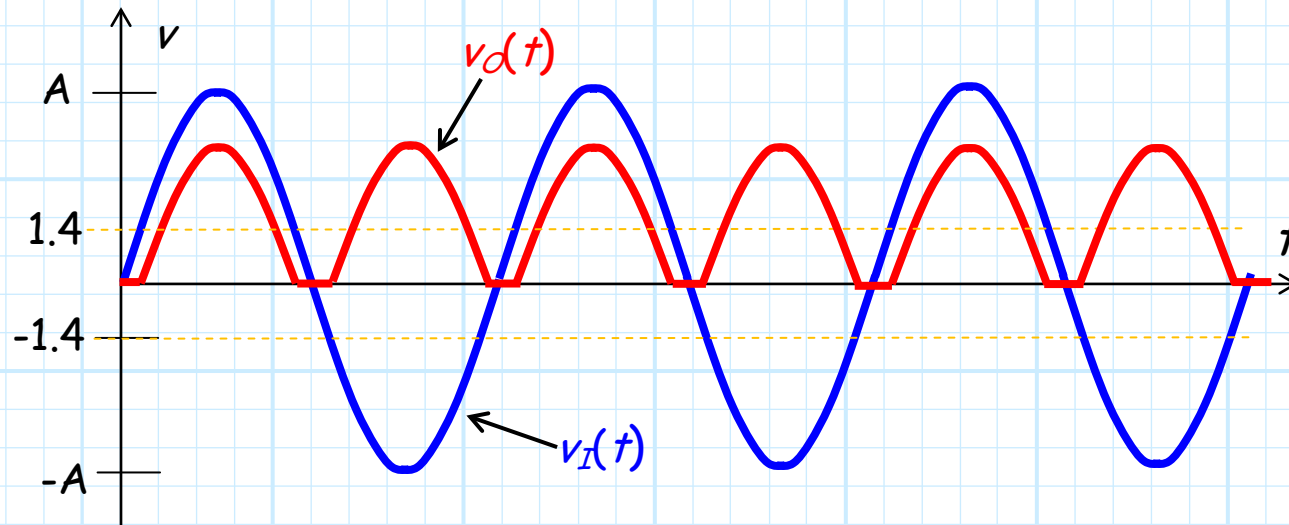If the input to this rectifier is a **sine wave**, we find that the **output** is approximately that of an ideal **full-wave rectifier**:



We see that the junction diode bridge rectifier output is **very close** to ideal.

In fact, if $A \gg 1.4 \text{ V}$, the **DC component** of this junction diode bridge rectifier is approximately:

$$V_{DC} \approx \frac{2A}{\pi} - 1.4 \text{ V}$$


Just 1.4 V less than the ideal full-wave rectifier DC component!

Peak Inverse Voltage

Q: *I'm so **confused!** The bridge rectifier and the full-wave rectifier **both** provide full-wave rectification.*

*Yet, the bridge rectifier use **4** junction diodes, whereas the full-wave rectifier only uses **2**.*

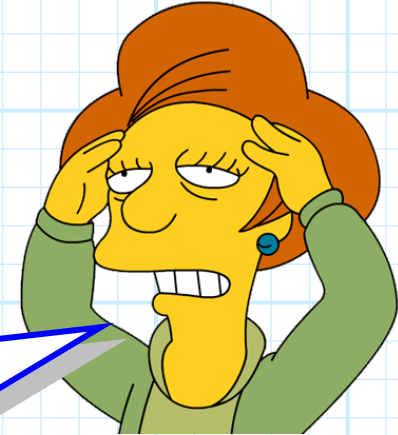*Why would we **ever** want to use the bridge rectifier?*



A: First, a slight **confession**—the results we derived for the **bridge** and **full-wave** rectifiers are **not precisely** correct!

Recall that we used the junction diode **CVD model** to determine the transfer function of each rectifier circuit.

→ The problem is that the CVD model does **not** predict junction diode **breakdown!**

Doc, it hurts when I do this

If the **input** voltage v_I becomes too **large**, the junction diodes can in fact **breakdown**—but the transfer functions we derived do **not** reflect this fact!

Q: *You mean that we must **rework** our analysis and find **new** transfer functions!?*



A: Fortunately no.


Breakdown is an **undesirable** mode for circuit rectification.

Our job as engineers is to design a rectifier that **prevents** it from occurring—that's why the **bridge** rectifier is helpful!



Whew! That's a big negative number

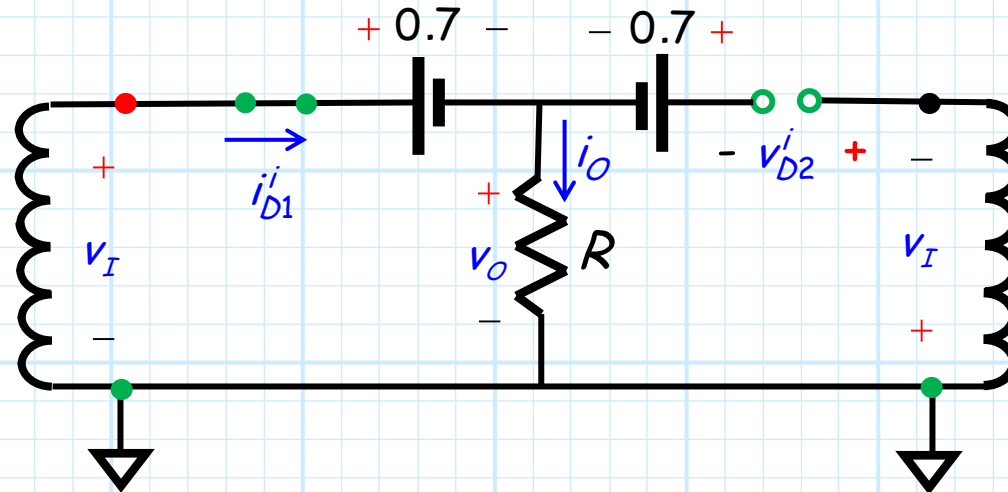To see **why**, consider the voltage across a **reversed biased** junction diode in **each** of our rectifier circuit designs.



Recall that the voltage across a **reverse biased ideal diode** in the **full-wave rectifier** design was:

$$v_{D2}^i = -2v_I$$

so that the voltage across the **junction** diode is approximately (according to the CVD model):

$$v_{D2} = v_{D2}^i + 0.7 = -2v_I + 0.7$$

Like getting me for all your classes

Now, we wish to determine the **worst case** scenario, with respect to **negative** diode voltage.


We seek v_D^{\min} , the **minimum** (i.e., most **negative**) value that the diode voltage will **ever** be—at least, for a **given** input $v_I t$.

I.E.:

$$v_D^{\min} \leq v_D t \text{ for all time } t$$

→ The value v_D^{\min} is a **negative** number!

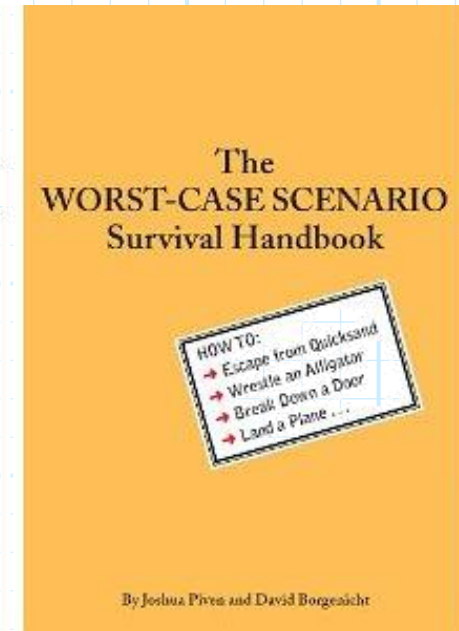Recall that for the junction diode to avoid **breakdown**, the diode voltage must be **greater** than $-V_{ZK}$ for all time t (i.e., $v_D t > -V_{ZK}$).



He's not trying to fly; he's indicating "safe"

The **worst case** scenario occurs at the **time** when the diode voltage is at its **most negative** (i.e., when $v_D t = v_D^{\min}$).

Thus, we know we are **safe** (no breakdown—**ever!**) **IF**:

$$v_D^{\min} > -V_{ZK}$$



Now, assume that the **source** voltage is a **sine wave** $v_I t = A \sin \omega t$.

We find that diode voltage is at its **most negative** (i.e., breakdown danger!) when the **source** voltage is at its **maximum** value $v_I^{\max} = A$.

Therefore:


$$v_D^{\min} = -2v_I^{\max} + 0.7 = -2A + 0.7$$

Of course, the **largest** junction diode voltage occurs when in **forward** bias:

$$v_D^{\max} \cong 0.7 V$$

Wow; that diode voltage goes way negative!

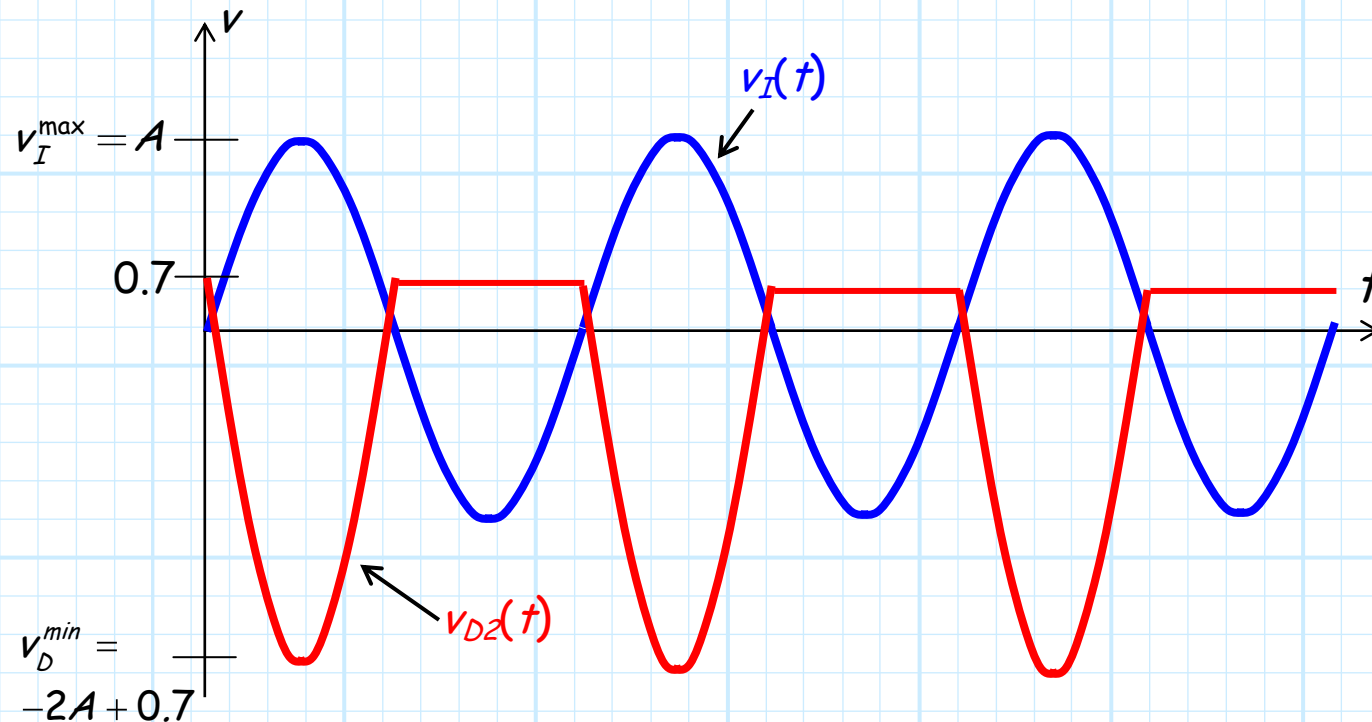Plotting both input $v_I(t) = A \sin \omega t$ and diode voltage $v_{D2}(t)$ for the full-wave rectifier:



Note that this **minimum** diode voltage v_D^{\min} is **very negative**, with an absolute value ($|v_D^{\min}| = 2A - 0.7$) nearly **twice** as large as the source magnitude A .

Peak Inverse Voltage: it's a positive value

Since v_D^{\min} is negative, we take its magnitude, "converting" it into a positive value we call the **Peak Inverse Voltage (PIV)**:

$$PIV = |v_D^{\min}|$$

→ The PIV is a **positive number!**

For example, the PIV of this **full-wave rectifier**, with a **sinusoidal input** is:

$$PIV = |v_D^{\min}| = 2A - 0.7$$



The input and the circuit— PIV depends on both !

It is **crucial** that you understand that the Peak Inverse Voltage (PIV) is dependent on **two** things:

1. the rectifier **circuit design**, and
2. the **input voltage** v_I .



Q: *So, why do we need to determine PIV?*

*I'm not sure I see what **difference** this value makes.*

A: The Peak Inverse Voltage specifies the **worst case scenario** with respect to **negative** diode voltage.

It allows us to **answer** one important question—**will** the junction diodes in our rectifier **breakdown**?

You're safe if PIV is less than V_{ZK}

To avoid breakdown, we earlier found that v_D^{\min} must be greater than $-V_{ZK}$:

$$v_D^{\min} > -V_{ZK} \text{ to avoid breakdown}$$

Multiplying by -1, we **equivalently** state:

$$-v_D^{\min} < V_{ZK} \text{ to avoid breakdown}$$

But since v_D^{\min} is negative, the value $-v_D^{\min}$ is **positive**, and so

$$-v_D^{\min} = |v_D^{\min}| = PIV$$

Inserting the result in the earlier inequality, we find that breakdown is avoided **if**:

$$PIV < V_{ZK}$$



In summary:

→ If the PIV is **less** than the Zener breakdown voltage of your rectifier diodes. I.E.,

$$\text{if } PIV < V_{ZK},$$

then we know that your junction diodes will **remain** in either **forward** or **reverse** bias for **all time** t .



Your rectifier will operate "properly"!

→ However, if the PIV is **greater** than the Zener breakdown voltage of your rectifier diodes. I.E.:

$$\text{if } PIV > V_{ZK},$$

then you know that our junction diodes will **breakdown** for at least **some** small amount of time t .



*Then the rectifier will **NOT** operate properly!*

But what if PIV is too big?



Q: So what do we do if PIV is greater than V_{ZK} ?

How do we *fix* this problem?

A: We have **three** possible solutions:


1. Use junction diodes with **larger** values of V_{ZK} (**but** they exist!).
2. Reduce the input voltage (e.g., magnitude A), **but** this will decrease you DC component V_{DC}
3. Use the **bridge** rectifier design—**no but**s about it!




The bridge rectifier to the rescue

Q: *The bridge rectifier!*

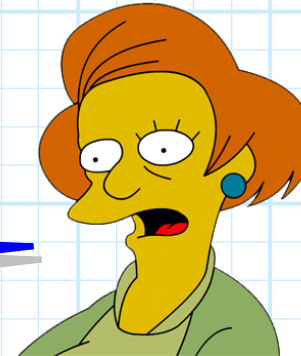*How does that solve our
breakdown problem?*



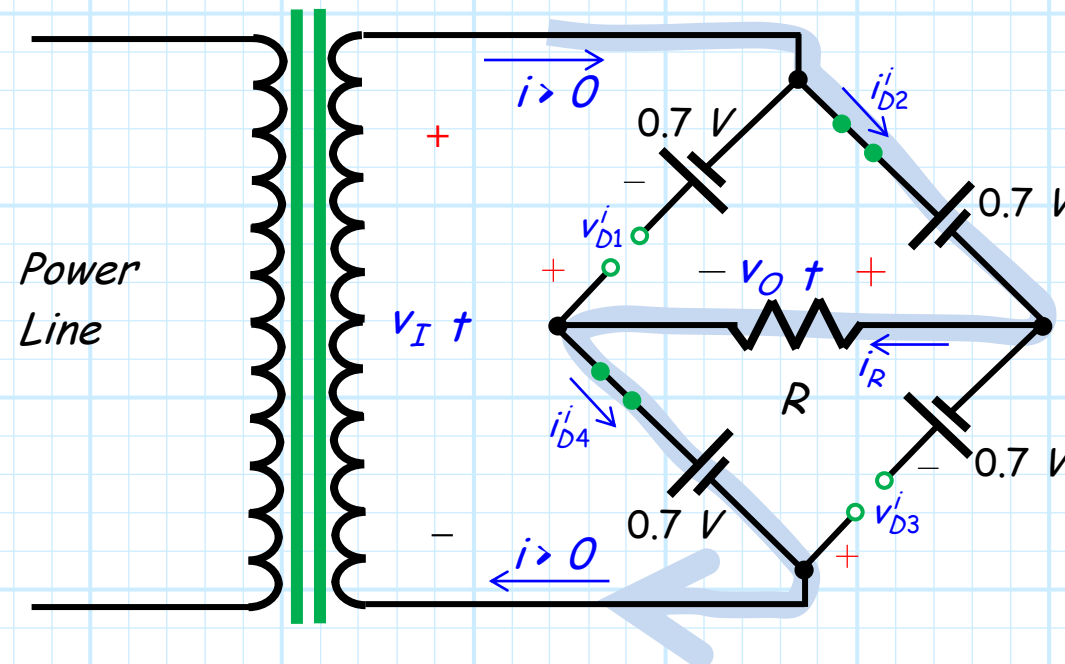A: To see how a **bridge** rectifier can be **useful**, let's determine its Peak Inverse Voltage **PIV**.




Danger, danger!

First, we recall that the voltage across a **reverse biased ideal diode** was:

$$v_{D1}^i = -v_s$$

so that the voltage across the **junction** diode is approximately:
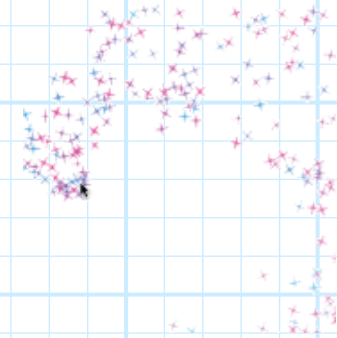
$$\begin{aligned} v_{D1} &= v_{D1}^i + 0.7 \\ &= -v_I + 0.7 \end{aligned}$$



Now, assume that the **source** voltage is a **sine wave** $v_I t = A \sin \omega t$.

We found that diode voltage is at its **most negative** (i.e., breakdown **danger!**) when the **source** voltage is at its **maximum** value $v_I^{max} = A$.

I.E.:

$$v_D^{min} = -v_I^{max} + 0.7 = -A + 0.7$$




Hmm... It's negative, but not extremely so

Of course, the **largest** junction diode voltage occurs when in forward bias:

$$v_D^{max} = 0.7 \text{ V}$$

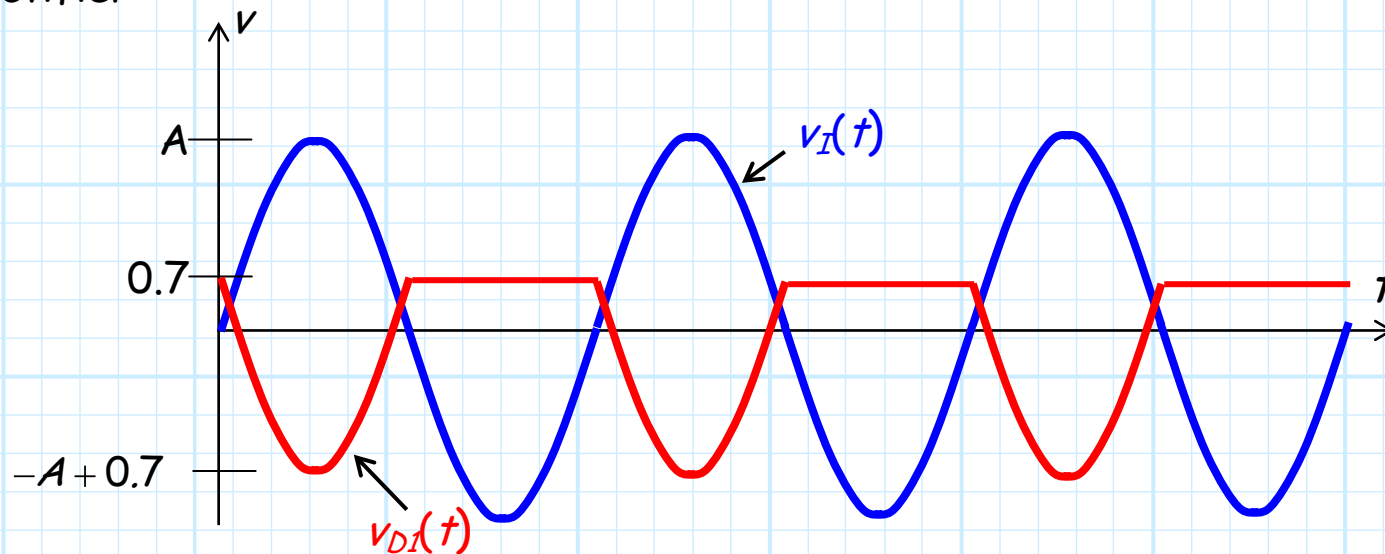Plotting both **input** $v_I(t) = A \sin \omega t$ and **diode voltage** $v_{D1}(t)$ for the **bridge** rectifier:



Note that this minimum diode voltage is **negative**, with an absolute value ($|v_D^{min}| = A - 0.7$), approximately **equal** to the value of the **source magnitude** A .

The bridge rectifier PIV is about half the full-wave PIV

Thus, the **PIV** for a **bridge** rectifier with a **sinusoidal** source voltage is:

$$PIV_{brg} = |V_D^{\min}| = A - 0.7$$

Note that this bridge rectifier value is approximately **half** the PIV we determined for the **full-wave** rectifier design:

$$PIV_{fw} = |V_D^{\min}| = 2A - 0.7$$


Thus, the source voltage (and the output DC component) of a **bridge** rectifier can be **twice** that of the full-wave rectifier design.

→ This is why the **bridge** rectifier is a very **useful** rectifier design!




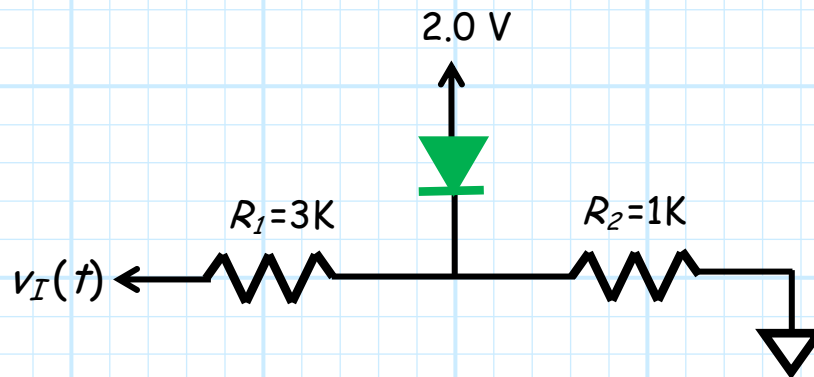Example: Peak Inverse Voltage

The diode in the circuit below is **IDEAL**.



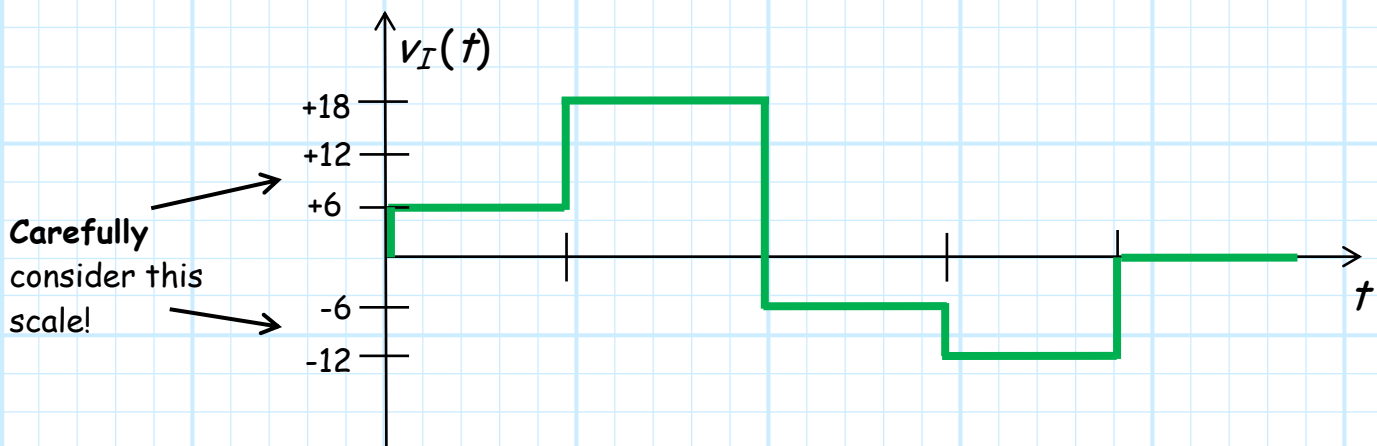The input to this circuit ($v_I(t)$) is plotted below.



Let's determine the **Peak Inverse Voltage (PIV)** of the ideal diode in this circuit.

Q: *This is so confusing! Is this the right equation:*


$$PIV = A - 0.7$$

Or, do I use this equation:

$$PIV = 2A - 0.7 \quad ??$$

Likewise, is $A=18$, or is $A=12$, or is it some other number?

A: None of the above!

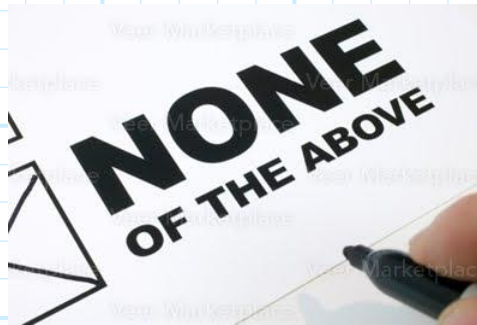


The result:

$$PIV = A - 0.7$$


is the PIV for the following **specific** situation—and this situation **only**:

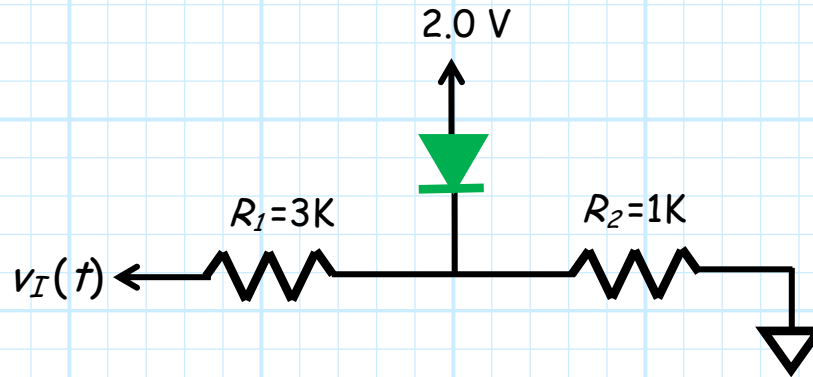- 1.** the diode circuit is a **bridge rectifier**, with
- 2.** an input signal $v_I(t) = A \sin \omega t$

Of course, the circuit for **this** problem is **most definitely not** a bridge rectifier (it doesn't even have an output!):



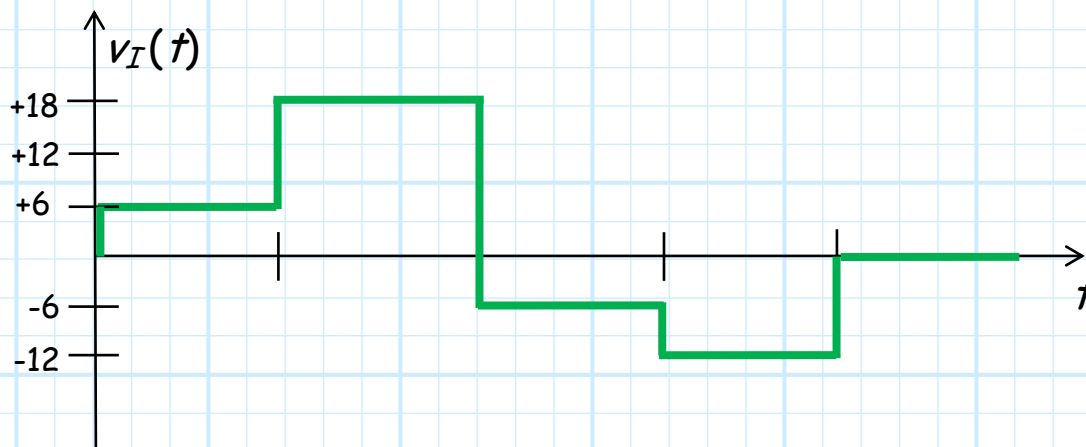And the input signal is **most definitely not** a sinusoid.



Thus, $PIV = A - 0.7$ is **most definitely not** "the right equation"!

Q: *Oh, so then I should use the other one:*

$$PIV = 2A - 0.7 \quad ?$$

A: Ahem; the result:


$$PIV = 2A - 0.7$$

is the PIV for this **specific** situation—and this situation **only**:

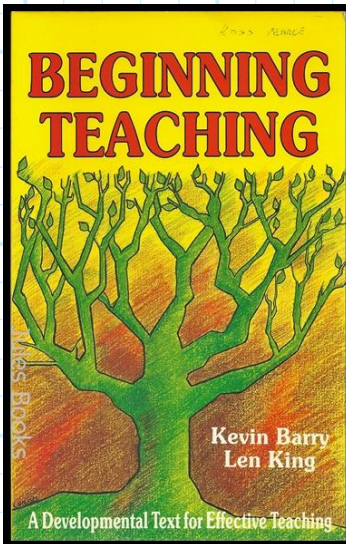1. the diode circuit is a **full-wave rectifier**, with
2. an input signal $v_I(t) = A \sin \omega t$

Of course, the circuit in this problem is **not** a full-wave rectifier (it **doesn't** even have an **output!**), and the input signal is **not** a sinusiod.

Thus, you most definitely **do not** "use" the equation $PIV = 2A - 0.7!$




Q: *Apparently, you could "use" a book on teaching, because these are the **only two PIV equations that you gave us!***

A: I did not "give" you these equations—they appeared as a result of a careful and detailed analysis of the **specific situations** we encountered.

You **now** have encountered (with this problem) a completely **different** situation—you can find the "right equation to use" only after you carefully, patiently, completely analyze this **new, specific** situation!

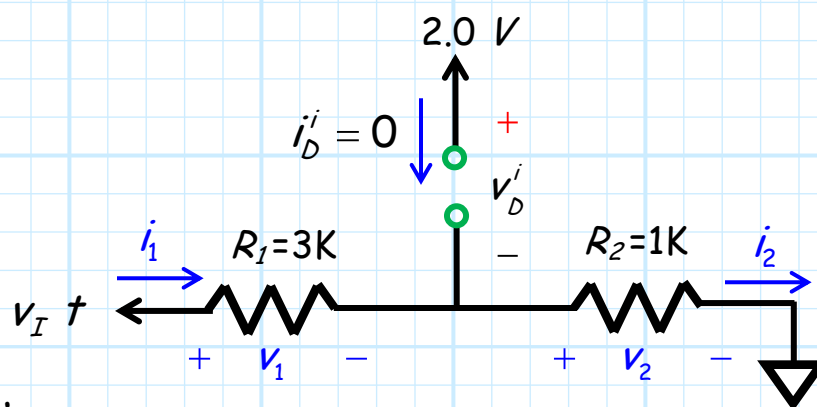To begin, you first **ASSUME** that the ideal diode is **reverse** biased, and thus **ENFORCE** the condition that $i_D' = 0$:




From KCL:

$$\begin{aligned} i_2 &= i_1 + i_D^i \\ &= i_1 + 0 \\ &= i_1 \end{aligned}$$

From Ohm's Law and the results above:
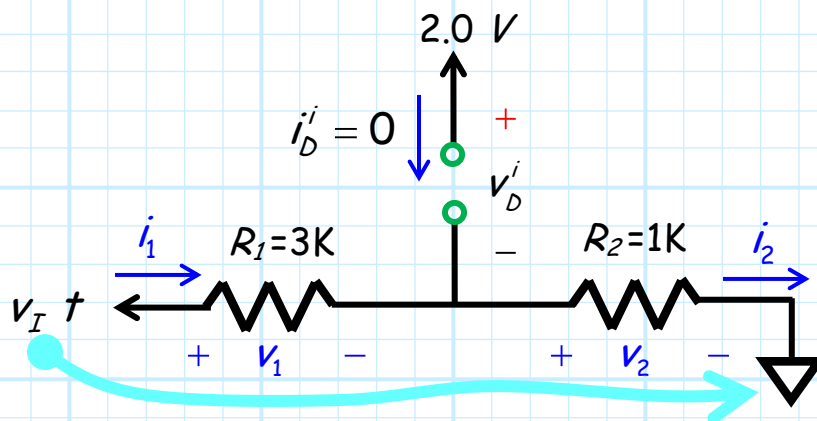
$$v_1 = i_1 R_1 = 3 i_1 \qquad v_2 = i_2 R_2 = 1 i_2 = 1 i_1$$



Now from KVL:

$$v_I - v_1 - v_2 = 0$$

Therefore,


$$\begin{aligned} v_I &= v_1 + v_2 \\ &= 3 i_1 + 1 i_1 \\ &= 4 i_1 \end{aligned}$$

And so:

$$i_1 = 0.25 v_I$$

meaning:

$$v_2 = 1 i_1 = 0.25 v_I$$

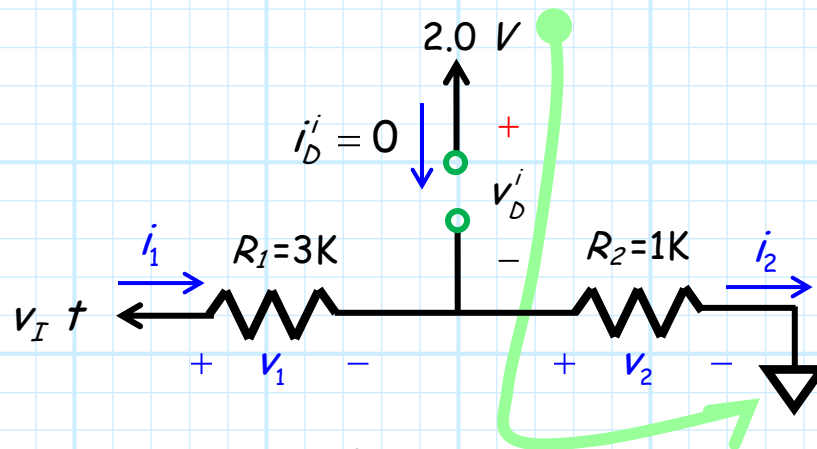

Now you can write a **second KVL**:

$$2 - v_D^i - v_2 = 0 \quad \Rightarrow \quad v_D^i = 2 - v_2 = 2 - 0.25 v_I$$

So you have concluded that the (reverse biased) **ideal diode voltage** is:

$$v_D^i = 2 - 0.25 v_I$$

This result is true, provided that(!) your reverse bias **assumption** is correct ($v_D^i < 0$)! You can quickly solve the inequality to determine **WHEN** this is true:

$$2 - 0.25 v_I < 0$$

$$-0.25 v_I < -2$$

$$-v_I < -8$$

$$v_I > 8$$



Thus:

$$\rightarrow v_D^i = 2 - 0.25 v_I \quad \text{when } v_I > 8$$

The important (**very important!**) thing to note here is that the ideal **diode voltage** is **negative only** when the **input voltage** is significantly **positive** (i.e., $v_I > 8$).


Moreover, the **larger** (i.e., more positive) the **input voltage** becomes, the **more negative** the ideal **diode voltage** becomes!

Thus, you come to the conclusion for **this** specific circuit (it may **not** be true for other circuits!), that the **minimum** ideal diode voltage ($v_D^{i \min}$) occurs when the input voltage is at its **maximum** (most positive). I.E.:

$$v_D^{i \min} = 2 - 0.25 v_I^{\max}$$

Q: *But how do I know what v_I^{\max} is? You said that $v_I^{\max} \neq A$; so then what is the "right equation" to "use"?*

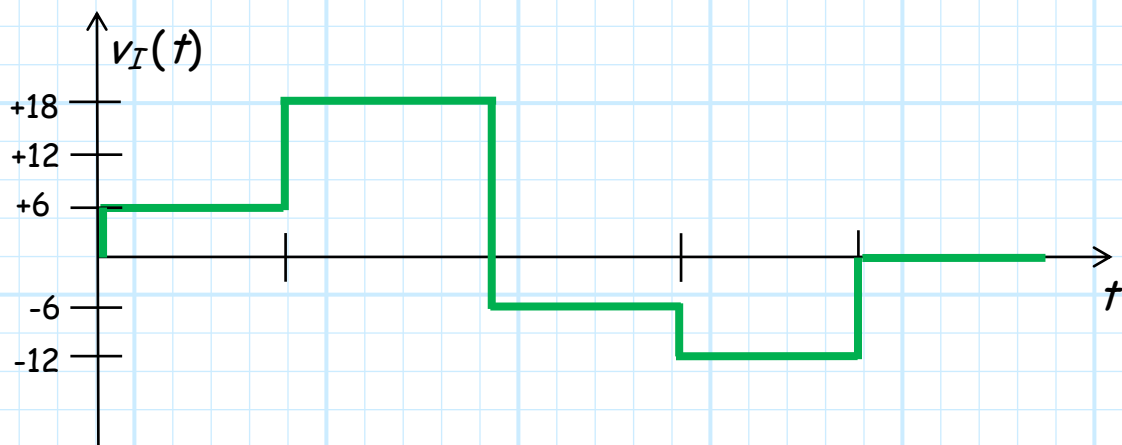A: **Sigh;** there is no equation. You know what the input voltage is—it is given in the **problem statement**:




Note that the **input voltage changes** with respect to **time**.

At **first**, the input voltage is **6.0 V**, later on it is at **-6.0 V** and then after that **-12.0 V**. The **important** question is: when is the input voltage at its **maximum** (i.e., most positive)?

Hopefully, by simply **looking** at the input voltage signal (**no equations required!**) it is evident that **18.0 V** is the most positive the input voltage **ever** is!

Thus,

$$v_I^{max} = 18.0$$

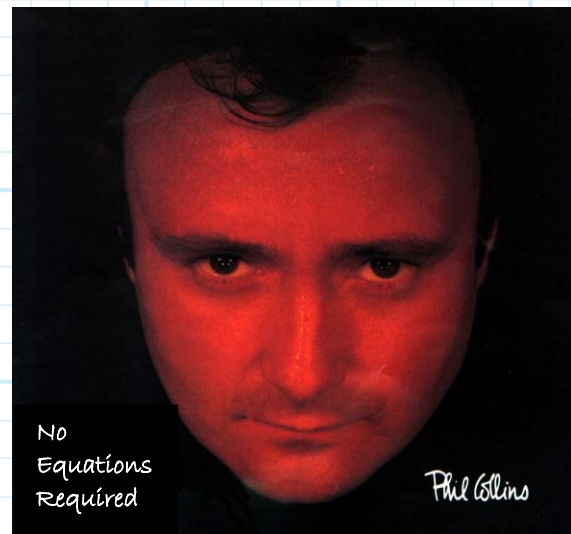

Note that $v_I^{max} = 18.0 > 8.0$; the ideal diode is **definitely** reverse biased!

And so, during the **time period** when the input voltage is at this **maximum** value, the ideal **diode voltage** will be at its **minimum** (i.e., most negative):

$$\begin{aligned} v_D^{i min} &= 2 - 0.25 v_I^{max} \\ &= 2 - 0.25 \cdot 18.0 \\ &= -2.5 V \end{aligned}$$

Thus, the **Peak Inverse Voltage (PIV)** is:

$$PIV = |v_D^{i min}| = |-2.5| = \underline{\underline{2.5 V}}$$

To confirm this, let's **plot the ideal diode voltage** as a function of **time**.

Q: *Wait! We only know the ideal diode voltage when $v_I > 8.0V$.*

What is the ideal diode voltage when $v_I < 8.0V$?


A: Remember, the ideal diode is **reverse** biased when $v_I > 8.0V$. Thus, when $v_I < 8.0V$ the ideal diode is **forward** biased.

→ And you know the voltage of a **forward biased ideal diode!**


$$v_D^i = 0 \text{ if forward biased}$$

Thus, the **continuous** function relating the ideal diode voltage to the input voltage is:
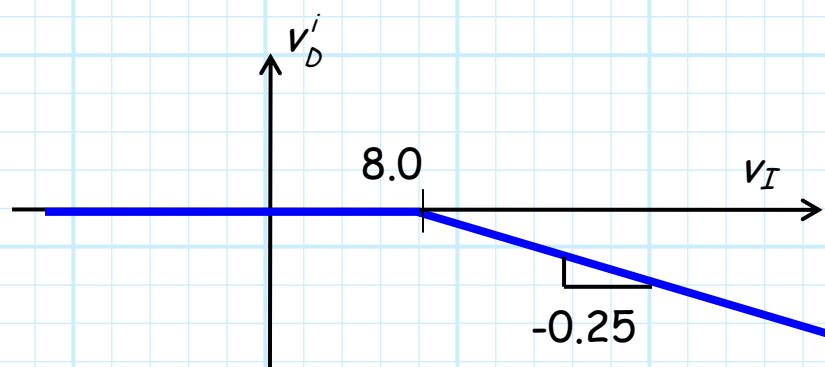
$$v_D^i = f v_I = \begin{cases} 2 - 0.25 v_I & \text{when } v_I > 8.0V \\ 0 & \text{when } v_I < 8.0V \end{cases}$$




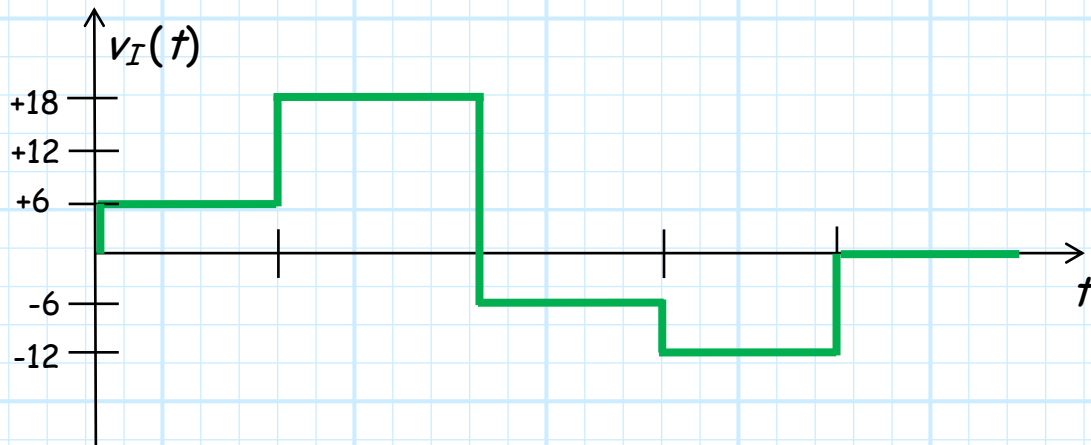Evaluating this with the **input** signal:



you see that the input is greater than 8.0 V **only** during the period when it is equal to **18.0 V**! Thus, **only** during this time period is the ideal diode voltage **non-zero**.

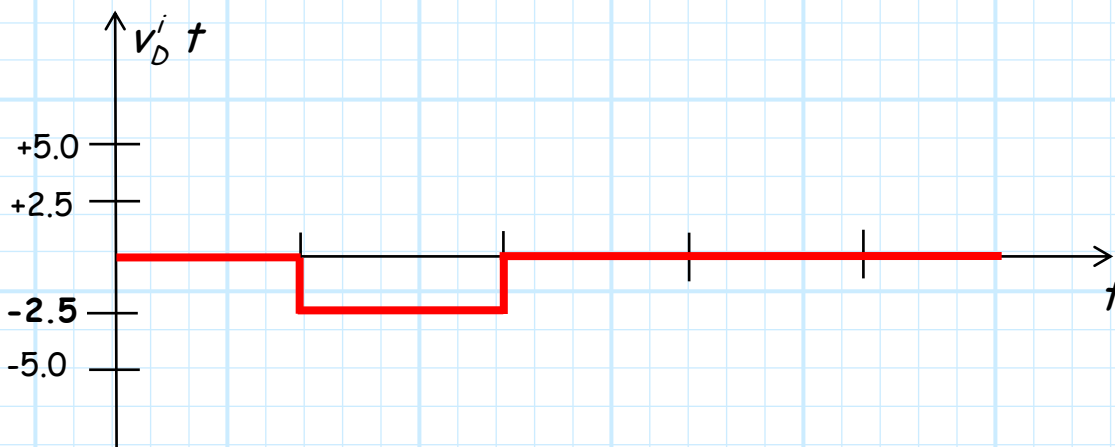Specifically, you have found that **when** $v_I = v_I^{max} = 18.0$, the ideal **diode voltage** is $v_D^i = -2.5 V$.



Thus, you have **confirmed** that $v_D^{i min} = -2.5 V$, and so:

$$PIV = |v_D^{i min}| = |-2.5| = \underline{\underline{2.5 V}}$$

Q: *Wasn't this a bit of an **academic exercise**; I mean after all, an **ideal diode doesn't have a breakdown region!***

A: True enough, this **was** an academic exercise. It did this to **simplify** the analysis a bit.

However, **if** you are analyzing a circuit with a **junction diode**, you still need to first find the minimum **ideal diode voltage** $v_D^{i\ min}$ of the **ideal diode** in the **CVD model**.

Then, the minimum voltage of the **junction diode** is simply the minimum voltage across the **CVD model**, which (of course!) is:

$$v_D^{min} = v_D^{i\ min} + 0.7$$

Thus, the PIV is:

$$PIV = |v_D^{min}| = |v_D^{i\ min} + 0.7|$$

Now this PIV value had **better** be **smaller** than the Zener breakdown voltage of the junction diode, or else **breakdown will occur!**