 


## 4.3 MOSFET Circuits at DC

Reading Assignment: pp. 262-270



A: HO: Steps for DC Analysis of MOSFET Circuits

Example: NMOS Circuit Analysis

Example: PMOS Circuit Analysis

Example: Another PMOS Circuit Analysis

# Steps for D.C Analysis of MOSFET Circuits

To analyze MOSFET circuit with D.C. sources, we **must** follow these **five steps**:

1. *ASSUME* an operating mode
2. *ENFORCE* the equality conditions of that mode.
3. *ANALYZE* the circuit with the enforced conditions.
4. *CHECK* the inequality conditions of the mode for consistency with original assumption. If consistent, the analysis is complete; if inconsistent, go to step 5.
5. *MODIFY* your original assumption and repeat all steps.

Let's specifically look at each step in **detail**.

## 1. *ASSUME*

Here we have **three** choices—cutoff, triode, or saturation. You can make an "**educated guess**" here, but remember, until you **CHECK**, it's just a guess!

## 2. ENFORCE

For all three operating regions, we must ENFORCE just **one** equality.

### Cutoff

Since **no** channel is induced, we ENFORCE the equality:

$$I_D = 0$$

### Triode

Since the conducting channel **is** induced but **not** in pinch-off, we ENFORCE the equality:

$$I_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

### Saturation

Since the conducting channel **is** induced and **is** in pinch-off, we ENFORCE the equality:

$$I_D = K (V_{GS} - V_t)^2$$

Note for all cases the constant  $K$  is:

$$K \doteq \frac{1}{2} k' \left( \frac{W}{L} \right)$$

and  $V_T$  is the MOSFET **threshold voltage**.

### 3. ANALYZE

The task in D.C. analysis of a MOSFET circuit is to find **one current** and **two voltages**!

a) Since the gate current  $I_G$  is zero ( $I_G = 0$ ) for all MOSFETS in all modes, we need **only** to find the **drain current**  $I_D$  -- this current value must be **positive** (or zero).

b) We also need to find **two** of the three **voltages** associated with the MOSFET. Typically, these two voltages are  $V_{GS}$  and  $V_{DS}$ , but given any two voltages, we can find the third using KVL:

$$V_{DS} = V_{DG} + V_{GS}$$

Some hints for MOSFET DC analysis:

1) Gate current  $I_G = 0$  **always** !!!

2) Equations sometimes have **two** solutions! Choose solution that is **consistent** with the original ASSUMPTION.

## 4. CHECK

You do not know if your D.C. analysis is correct unless you **CHECK** to see if it is consistent with your original assumption!

**WARNING!**-Failure to **CHECK** the original assumption will result in a **SIGNIFICANT REDUCTION** in credit on exams, regardless of the accuracy of the analysis !!!

**Q:** *What exactly do we CHECK?*

**A:** We **ENFORCED** the mode **equalities**, we **CHECK** the mode **inequalities**.

We must **CHECK two** separate inequalities after analyzing a MOSFET circuit. Essentially, we check if we have/have not induced a conducting channel, and then we check if we have/have not pinched-off the channel (if it is conducting).

### Cutoff

We must only **CHECK** to see if the MOSFET has a **conducting channel**. If **not**, the MOSFET is indeed in **cutoff**. We therefore **CHECK** to see if:

$$V_{GS} < V_t \quad (\text{NMOS})$$

$$V_{GS} > V_t \quad (\text{PMOS})$$

## Triode

Here we must first CHECK to see if a channel has been induced, i.e.:

$$V_{GS} > V_t \quad (\text{NMOS})$$

$$V_{GS} < V_t \quad (\text{PMOS})$$

Likewise, we must CHECK to see if the channel has reached **pinchoff**. If **not**, the MOSFET is indeed in the **triode** region. We therefore CHECK to see if:

$$V_{DS} < V_{GS} - V_t \quad (\text{NMOS})$$

$$V_{DS} > V_{GS} - V_t \quad (\text{PMOS})$$

## Saturation

Here we must first CHECK to see if a channel has been induced, i.e.:

$$V_{GS} > V_t \quad (\text{NMOS})$$

$$V_{GS} < V_t \quad (\text{PMOS})$$

Likewise, we must CHECK to see if the channel has reached **pinchoff**. If it **has**, the MOSFET is indeed in the **saturation** region. We therefore CHECK to see if:

$$V_{DS} > V_{GS} - V_t \quad (\text{NMOS})$$

$$V_{DS} < V_{GS} - V_t \quad (\text{PMOS})$$

If the results of our analysis are consistent with **each** of these inequalities, then we have made the **correct** assumption! The **numeric** results of our analysis are then likewise **correct**. We can **stop** working!

However, if **even one** of the results of our analysis is **inconsistent** with our ASSUMPTION, then we have made the **wrong** assumption! → Time to move to step 5.

## 5. MODIFY


If **one or more** of the circuit MOSFETs are **not** in their ASSUMED mode, we must change our assumptions and start **completely** over!

In general, **all** of the results of our previous analysis are incorrect, and thus must be **completely** scraped!

# Example: NMOS Circuit

## Analysis

Consider this DC MOSFET circuit:

 

Let's ASSUME the NMOS device is in saturation.

Thus, we must ENFORCE the condition that:

$$I_D = K (V_{GS} - V_t)^2$$

Now we must ANALYZE the circuit.

**Q:** *What now? How do we proceed with this analysis?*

**A:** It's certainly not clear. Let's write the circuit equations and see what happens.

From the Gate-Source loop KVL:

$$0.0 - V_{GS} - (1)I_D = -5.0$$

Therefore, rearranging:


$$I_D = 5.0 - V_{GS}$$

And from the Drain-Source loop KVL:

$$5.0 - (1)I_D - V_{DS} - (1)I_D = -5.0$$

Therefore, rearranging:

$$V_{DS} = 10.0 - 2I_D$$

 

Look! We can equate the NMOS device equation and G-S equation to find  $V_{GS}$ .

$$I_D = K(V_{GS} - V_t)^2 = 5.0 - V_{GS}$$

$$\therefore 0 = K V_{GS}^2 + V_{GS}(1 - 2K V_t) + (K V_t^2 - 5.0)$$

A quadratic equation!

The solutions to this equation are:

$$V_{GS} = 3.76 V \quad \text{or} \quad V_{GS} = -2.26 V$$

**Q:** *Yikes! Two solutions! Which one is correct?*

**A:** Note we **assumed** saturation. If the MOSFET is in saturation, we know that:

$$V_{GS} > V_t = 2.0$$

Only one solution of the quadratic satisfies this condition, i.e.:

$$V_{GS} = 3.76 > V_t$$

Thus, we use  $V_{GS} = 3.76 V$  --the solution that is consistent with our original assumption.

Inserting this voltage into the Gate-Source KVL equation, we find that the drain current is:

$$\begin{aligned}I_D &= 5.0 - V_{GS} \\ &= 5.0 - 3.76 \\ &= 2.24 \text{ mA}\end{aligned}$$

And using the Drain-Source KVL, we find the remaining voltage:

$$\begin{aligned}V_{DS} &= 10.0 - 2.0I_D \\ &= 10.0 - 2(2.24) \\ &= 5.52 \text{ V}\end{aligned}$$

Even though we have answers (one current and two voltages), we still are not finished, as we now must CHECK our solution to see if it is consistent with the saturation mode inequalities.

$$3.76 = V_{GS} > V_t = 2.0 \quad \checkmark$$


$$5.52 = V_{DS} > V_{GS} - V_t = 1.76 \quad \checkmark$$

Both answers are consistent! Our solutions are correct!

# Example: PMOS Circuit

## Analysis

Consider this PMOS circuit:

 

For this problem, we know that the **drain voltage**  $V_D = 4.0\text{ V}$  (with respect to ground), but we do **not** know the value of the voltage source  $V_{GG}$ .

Let's attempt to **find** this value  $V_{GG}$ !


First, let's **ASSUME** that the PMOS is in **saturation** mode.

Therefore, we **ENFORCE** the **saturation** drain current equation  $I_D = K(V_{GS} - V_t)^2$ .

Now we must ANALYZE this circuit!

Q: *Yikes! Where do we start?*

 A: The best way to start is by "picking the low-hanging fruit". In other words, determine the obvious and easy values. Don't ask, "What is  $V_{GG}$ ?", but instead ask, "What do I know?"!



There are lots of things that we can quickly determine about this circuit!

$$I_G = 0.0 \text{ mA}$$

$$V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0}{4} = \frac{4.0 - 0}{4} = 1 \text{ mA}$$

$$V_G = V_{GG} - 10 I_G = V_{GG} - 10(0) = V_{GG}$$

Therefore, we can likewise determine:

$$V_{DS} = V_D - V_S = 4.0 - 5.0 = -1.0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5.0 \text{ V}$$

Note what we have **quickly determined**—the **numeric** value of drain current ( $I_D=1.0$  mA) and the voltage drain-to-source ( $V_{DS}=-1.0$ ) Moreover, we have determined the value  $V_{GS}$  in terms of **unknown** voltage  $V_{GG}$  ( $V_{GS} = V_{GG} - 5.0$ ).

We've determined all the **important stuff** (i.e.,  $V_{GS}, V_{DS}, I_D$ )!

We can now relate these values using our PMOS **drain current equation**. Recall that we **ASSUMED saturation**, so if this assumption is correct:

$$I_D = K(V_{GS} - V_T)^2$$

**Inserting** into this equation our knowledge from above, along with our **PMOS** values  $K=0.2$  mA/V<sup>2</sup> and  $V_T=-2.0$ , we get:

$$\begin{aligned} I_D &= K(V_{GS} - V_T)^2 \\ 1.0 &= 0.2(V_{GS} - (-2.0))^2 \\ 5.0 &= (V_{GS} + 2.0)^2 \end{aligned}$$

Be **careful** here! Note in the above equation that threshold voltage  $V_T$  is **negative** (since PMOS) and that  $I_D$  and  $K$  are both written in terms of **milliamps** (mA).

Now, we solve this equation to find the value of  $V_{GS}$ !

$$5.0 = (V_{GS} + 2.0)^2$$

$$\pm\sqrt{5} = V_{GS} + 2.0$$

$$\pm\sqrt{5} - 2.0 = V_{GS}$$

**Q:** So  $V_{GS}$  is **both**  $\sqrt{5} - 2.0 = 0.24 \text{ V}$  **and**  $-\sqrt{5} - 2.0 = -4.23 \text{ V}$ ?  
How can this be possible?

**A:** It's **not** possible! The solution is **either**  $V_{GS} = 0.24 \text{ V}$  **or**  $V_{GS} = -4.23 \text{ V}$ .

**Q:** But how can we tell **which** solution is correct?

**A:** We must choose a solution that is **consistent** with our original ASSUMPTION. Note that **neither** of the solutions **must** be consistent with the saturation ASSUMPTION, an event meaning that our ASSUMPTION was wrong.

However, **one** (but **only one!**) of the two solutions may be consistent with our saturation ASSUMPTION—**this** is the value that we choose for  $V_{GS}$ !

For this example, where we have ASSUMED that the PMOS device is in **saturation**, the voltage gate-to-source  $V_{GS}$  must be **less** (remember, it's a **PMOS** device!) than the **threshold voltage**:

$$V_{GS} < V_t$$

$$V_{GS} < -2.0 \text{ V}$$

Clearly, one of our solutions **does** satisfy this equation ( $V_{GS} = -4.23 < -2.0$ ), and therefore we choose the **solution**  $V_{GS} = -4.23 \text{ V}$ .

**Q:** *Does this mean our saturation ASSUMPTION is correct?*

**A:** **NO!** It merely means that our saturation ASSUMPTION **might** be correct! We need to **CHECK** the other inequalities to know for **sure**.

Now, returning to our circuit **analysis**, we can quickly determine the **unknown** value of  $V_{GG}$ . Recall that we **earlier** determined that:

$$V_{GS} = V_{GG} - 5.0$$

And now, since we "know" that the  $V_{GS} = -4.23 \text{ V}$ , we can determine that:

$$\begin{aligned} V_{GG} &= V_{GS} + 5.0 \\ &= -4.23 + 5.0 \\ &= 0.77 \text{ V} \end{aligned}$$

This solution ( $V_{GG} = 0.77 \text{ V}$ ) is of course true **only if** our original ASSUMPTION was correct. Thus, we must **CHECK** to see if our **inequalities** are valid:

We of course already know that the **first** inequality is true—a p-type channel is induced:

$$V_{GS} = -4.23 < -2.0 = V_t \quad \checkmark$$

And, since the **excess gate voltage** is  $V_{GS} - V_t = -2.23 \text{ V}$ , the **second inequality**:

$$V_{DS} = -1.0 > -2.23 = V_{GS} - V_t \quad \times$$

shows us that our **ASSUMPTION** was **incorrect!**

→ Time to make a **new ASSUMPTION** and **start over!**

So, let's **now ASSUME** the PMOS device is in **triode** region.

Therefore **ENFORCE** the drain current equation:

$$i_D = K \left[ 2(V_{GS} - V_t)V_{DS} - V_{DS}^2 \right]$$

Now let's **ANALYZE** our circuit!

Note that most of our **original** analysis was **independent** of our PMOS mode **ASSUMPTION**. Thus, we **again** conclude that:

$$I_G = 0.0 \text{ mA}$$

$$V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0}{4} = \frac{4.0 - 0}{4} = 1 \text{ mA}$$

$$V_G = V_{GG} - 10 I_G = V_{GG} - 10(0) = V_{GG}$$

Therefore,

$$V_{DS} = V_D - V_S = 4.0 - 5.0 = -1.0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5.0 \text{ V}$$

Now, inserting these values in the **triode drain current equation**:

$$i_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

$$1.0 = 0.2 [2(V_{GS} - (-2))(-1) - (-1)^2]$$

$$5.0 = [-2(V_{GS} + 2) - 1]$$

Look! **One** equation and **one** unknown! Solving for  $V_{GS}$  we find:

$$5.0 = [-2(V_{GS} + 2) - 1]$$

$$6.0 = -2(V_{GS} + 2)$$

$$-3.0 = V_{GS} + 2$$

$$-5.0 = V_{GS}$$

Thus, we find that  $V_{GS} = -5.0 \text{ V}$ , so that we can find the **value** of voltage source  $V_{GG}$ :

$$V_{GS} = V_{GG} - 5.0$$

$$-5.0 = V_{GG} - 5.0$$

$$0.0 = V_{GG}$$

The voltage source  $V_{GG}$  is equal to **zero**—provided that our triode **ASSUMPTION** was **correct**.

To find out if the **ASSUMPTION** is correct, we must **CHECK** our **triode inequalities**.

First, we **CHECK** to see if a channel has indeed been **induced**:

$$V_{GS} = -5.0 < -2.0 = V_t \quad \checkmark$$


Next, we **CHECK** to make sure that our channel is **not** in pinch-off. Noting that the **excess gate voltage** is  $V_{GS} - V_t = -5.0 - (-2.0) = -3.0 \text{ V}$ , we find that:

$$V_{DS} = -1.0 > -3.0 = V_{GS} - V_t \quad \checkmark$$

Our **triode ASSUMPTION** is **correct**! Thus, the voltage source  $V_{GG} = 0.0 \text{ V}$ .
 
# Example: Another PMOS Circuit Analysis

Consider the PMOS circuit below, where we know (somehow) that  $V_{GS} = -4.0$  V, but don't know (for some reason) the value of resistor  $R$ .



Let's see if we can determine the value of resistor  $R$ .

First, let's ASSUME that the MOSFET is in saturation, and therefore ENFORCE the drain current equation:


$$I_D = K(V_{GS} - V_t)^2$$

Now we ANALYZE the circuit:



**Q:** OK, this first part was easy, but what do we do now? How can we determine the value of resistor  $R$ ?

 **A:** The key to "unlocking" this circuit analysis is recognizing that the potential difference across resistor  $R_2$  is simply the voltage  $V_{GS}$ —and we know the value of  $V_{GS}$  ( $V_{GS} = -4.0\text{V}$ )!



Thus, we can immediately determine that current  $I_2$  is:

$$I_2 = \frac{V_{GS}}{R_2} = \frac{-4.0}{1} = -4.0\text{ mA}$$


Likewise, from KCL, we find:

$$I_1 + I_G = I_2$$

But since gate current  $I_G = 0$ , we conclude:

$$I_1 = I_2 = -4.0 \text{ mA}$$

 Now we can determine much about this circuit!




For example, from KVL, we find the gate voltage:

$$\begin{aligned} V_G &= 0.0 - I_1 R_1 \\ &= -(-4.0)1 \\ &= 4.0 \text{ V} \end{aligned}$$

And likewise the source voltage:
 
$$\begin{aligned} V_S &= V_G - I_2 R_2 \\ &= 4.0 - (-4.0)1 \\ &= 8.0 \text{ V} \end{aligned}$$



Likewise, from KCL, we can determine the current through resistor  $R$ :

$$\begin{aligned} I &= I_D - I_2 \\ &= 3.0 - (-4.0) \\ &= 7.0 \text{ mA} \end{aligned}$$

And thus from Ohm's Law we can find the value of  $R$ :

$$\begin{aligned} R &= \frac{15.0 - V_S}{I} \\ &= \frac{15.0 - 8.0}{7.0} \\ &= 1 \text{ K} \end{aligned}$$

But wait! We're still not done! We must CHECK to see if our original ASSUMPTION was correct.

First, we CHECK to see if the channel is induced:

$$V_{GS} = -4.0 < -2.0 = V_t \quad \checkmark$$

Next, we CHECK to see if the channel is pinched off. Here, we note that  $V_{DS} = V_D - V_S = 3.0 - 8.0 = -5.0 \text{ V}$ , and excess gate voltage is  $V_{GS} - V_t = -4.0 - (-2.0) = -2.0 \text{ V}$ . Therefore:

$$V_{DS} = -5.0 < -2.0 = V_{GS} - V_t \quad \checkmark$$

Hence, our ASSUMPTION is correct, and  $R=1\text{K}$ .